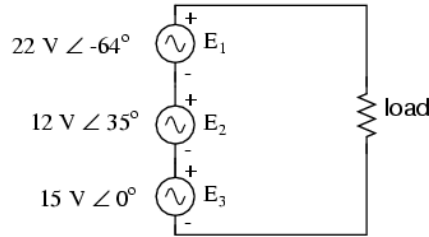



**SOLUTION**

Q1. Find the total voltage across the load resistor. Also draw the phasor diagram.



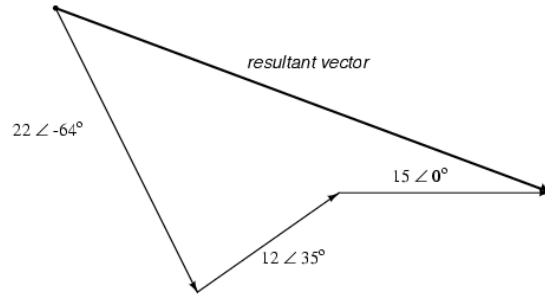
**Solution:**

$$\begin{aligned} \text{Total voltage} &= 34.47 - j12.89 \text{ V} \\ &= 36.8 \angle -20.5^\circ \end{aligned}$$



Q2. An ac circuit consisting of a pure resistance of  $10\Omega$  is connected to an ac supply of 230 V, 50 Hz. Calculate the (i) current (ii) power consumed and (iii) equations for voltage and current.


**Solution:**

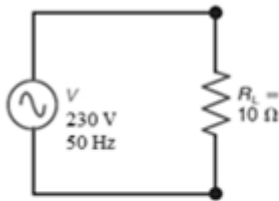

$$\begin{aligned} (i) I &= \frac{V}{R} = \frac{230}{10} = 23 \text{ A} \\ (ii) P &= VI = 230 \times 23 = 5260 \text{ W} \\ (iii) V_m &= \sqrt{2}V = 325.27 \text{ V} \\ I_m &= \sqrt{2}I = 32.52 \text{ A} \\ \omega &= 2\pi f = 314 \text{ rad/sec} \\ v &= 325.25 \sin 314t \\ i &= 32.52 \sin 314t \end{aligned}$$

Q3. A pure inductive coil allows a current of 10A to flow from a 230V, 50 Hz supply. Find (i) inductance of the coil (ii) power absorbed, and (iii) equations for voltage and current. Also draw the phasor diagram.

**Solution:**

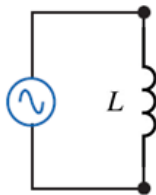


$$\begin{aligned} (i) X_L &= \frac{V}{I} = \frac{230}{10} = 23 \Omega \\ X_L &= 2\pi fL \\ L &= \frac{X_L}{2\pi f} = 0.073 \text{ H} \\ (ii) P &= 0 \\ (iii) V_m &= \sqrt{2}V = 325.27 \text{ V} \\ I_m &= \sqrt{2}I = 14.14 \text{ A} \\ \omega &= 2\pi f = 314 \text{ rad/sec} \\ v &= 325.25 \sin 314t \\ i &= 14.14 \sin(314t - \pi/2) \end{aligned}$$

**SOLUTION**

Q4. A 318μF capacitor is connected across a 230V, 50 Hz system. Find (i) the capacitive reactance (ii) rms value of current and (iii) equations for voltage and current.

**Solution:**

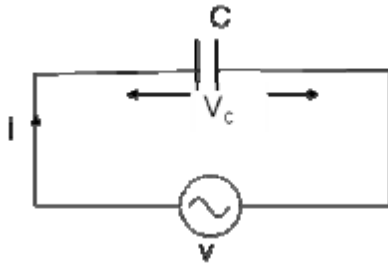

$$(i) X_c = \frac{1}{2\pi f C} = 10\Omega$$

$$(ii) I = \frac{V}{X_c} = 23A$$

$$(iii) V_m = \sqrt{2}V = 325.27V$$

$$I_m = \sqrt{2}I = 32.53A$$

$$\omega = 2\pi f = 314 \text{ rad/sec}$$

$$v = 325.25 \sin 314t$$

$$i = 32.53 \sin(314t + \pi/2)$$

Q5. Calculate the total impedance of the circuit shown below.

**Solution:**

$$X_L = 2\pi f L = (2)(\pi)(60 \text{ Hz})(650 \text{ mH}) = 245.04 \Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{(2)(\pi)(60 \text{ Hz})(1.5 \mu\text{F})}$$

$$X_C = 1.7684 \text{ k}\Omega$$



$$Z_R = 250 + j0 \Omega \text{ or } 250 \Omega \angle 0^\circ$$

$$Z_L = 0 + j245.04 \Omega \text{ or } 245.04 \Omega \angle 90^\circ$$

$$Z_C = 0 - j1.7684 \text{ k}\Omega \text{ or } 1.7684 \text{ k}\Omega \angle -90^\circ$$

$$Z_{\text{total}} = (250 + j0 \Omega) + (0 + j245.04 \Omega) + (0 - j1.7684 \text{ k}\Omega)$$
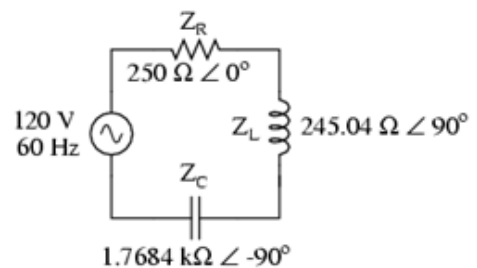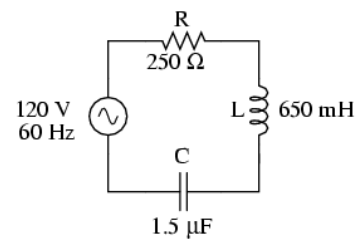
$$Z_{\text{total}} = 250 - j1.5233 \text{ k}\Omega \text{ or } 1.5437 \text{ k}\Omega \angle -80.680^\circ$$



Q6. A coil having a resistance of 7Ω and an inductance of 31.8mH is connected to 230V, 50Hz supply. Calculate (i) the circuit current (ii) phase angle (iii) power factor (iv) power consumed, (v) reactive power and (vi) apparent power. Also draw the phasor diagram.

**Solution:**

$$X_L = 2\pi f L = 2 \times 3.14 \times 50 \times 31.8 \times 10^{-3} = 10\Omega$$

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{7^2 + 10^2} = 12.2\Omega$$

$$(i) I = \frac{V}{Z} = \frac{230}{12.2} = 18.85A$$


$$(ii) \phi = \tan^{-1}\left(\frac{X_L}{R}\right) = \tan^{-1}\left(\frac{10}{7}\right) = 55^\circ \text{ lag}$$

$$(iii) PF = \cos \Phi = \cos(55^\circ) = 0.573 \text{ lag}$$

$$(iv) P = VI \cos \Phi = 230 \times 18.85 \times 0.573 = 2484.24W$$

$$v) \text{ Reactive power } Q = VI \sin \phi = 230 \times 18.85 \times 0.795 = 3.46 \text{ kVAR}$$
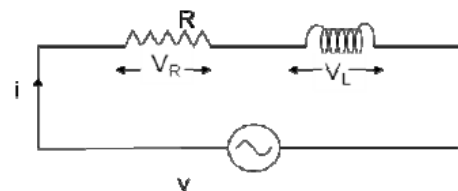
$$vi) \text{ Apparent power} = 4.25 \text{ kVA}$$



**SOLUTION**

Q7. A 200 V, 50 Hz, inductive circuit takes a current of 10A, lagging 30 degree. Find (i) the resistance (ii) reactance (iii) inductance of the coil.

**Solution:**

$$Z = \frac{V}{I} = \frac{200}{10} = 20\Omega$$

$$(i) R = Z \cos \phi = 20 \times \cos 30^\circ = 17.32\Omega$$

$$(ii) X_L = Z \sin \phi = 20 \times \sin 30^\circ = 10\Omega$$

$$(iii) L = \frac{X_L}{2\pi f} = \frac{10}{2 \times 3.14 \times 50} = 0.0318H$$

Q8. A Capacitor of capacitance 79.5 $\mu$ F is connected in series with a non-inductive resistance of 30 $\Omega$  across a 100V, 50Hz supply. Find (i) impedance (ii) current (iii) phase angle (iv) equation for the instantaneous value of current. Also draw the phasor diagram.

**Solution:**

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2 \times 3.14 \times 50 \times 79.5 \times 10^{-6}} = 40\Omega$$

$$(i) Z = \sqrt{R^2 + X_C^2} = \sqrt{30^2 + 40^2} = 50\Omega$$


$$(ii) I = \frac{V}{Z} = \frac{100}{50} = 2A$$

$$(iii) \Phi = \tan^{-1} \left( \frac{X_C}{R} \right) = \tan^{-1} \left( \frac{40}{30} \right) = 53^\circ \text{ lead}$$

$$(iv) I_m = \sqrt{2} I = \sqrt{2} \times 2 = 2.828A$$

$$\omega = 2\pi f = 2 \times 3.14 \times 50 = 314 \text{ rad/sec}$$

$$i = 2.828 \sin(314t + 53^\circ)$$

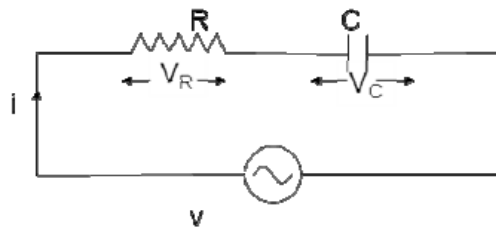

Q9. A 230 V, 50 Hz ac supply is applied to a coil of 0.06 H inductance and 2.5  $\Omega$  resistance connected in series with a 6.8  $\mu$ F capacitor. Calculate (i) Impedance (ii) Current (iii) Phase angle between current and voltage (iv) power factor (v) power consumed

**Solution:**

$$X_L = 2\pi f L = 2 \times 3.14 \times 50 \times 0.06 = 18.84\Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2 \times 3.14 \times 50 \times 6.8 \times 10^{-6}} = 468\Omega$$

$$(i) Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{2.5^2 + (18.84 - 468)^2} = 449.2\Omega$$

$$(ii) I = \frac{V}{Z} = \frac{230}{449.2} = 0.512 A$$

$$(iii) \Phi = \tan^{-1} \left( \frac{X_L - X_C}{R} \right) = \tan^{-1} \left( \frac{18.84 - 468}{2.5} \right) = -89.7^\circ$$

$$(iv) pf = \cos \Phi = \cos 89.7 = 0.0056 \text{ lead}$$

$$(v) P = VI \cos \Phi = 230 \times 0.512 \times 0.0056 = 0.66W$$

**SOLUTION**

Q10. A resistance R, an inductance L=0.01 H and a capacitance C are connected in series. When an alternating voltage  $v=400 \sin(3000t-20^\circ)$  is applied to the series combination, the current flowing is  $10\sqrt{2} \sin(3000t-65^\circ)$ . Find the values of R and C.

**Solution:**

$$\Phi = 65^\circ - 20^\circ = 45^\circ \text{ lag}$$

$$X_L = \omega L = 3000 \times 0.01 = 30\Omega$$

$$\tan \Phi = \tan 45^\circ = 1$$

$$\tan \Phi = \frac{X_L - X_C}{R} = 1$$

$$R = X_L - X_C$$

$$Z = \frac{V_m}{I_m} = \frac{400}{10\sqrt{2}} = 28.3\Omega Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{R^2 + R^2}$$

$$\sqrt{2}R = 28.3$$

$$R = 20\Omega$$

$$X_L - X_C = 20\Omega$$

$$X_C = 30 - 20 = 10\Omega$$

$$C = \frac{1}{\omega X_C} = \frac{1}{3000 \times 10} = 33.3\mu F$$

Q11. A coil of pf 0.6 is in series with a  $100\mu F$  capacitor. When connected to a 50Hz supply, the potential difference across the coil is equal to the potential difference across the capacitor. Find the resistance and inductance of the coil.

**Solution:**

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2 \times 3.14 \times 50 \times 100 \times 10^{-6}} = 31.83\Omega$$

$$V_{\text{coil}} = V_C$$


$$IZ_{\text{coil}} = IX_C$$

$$Z_{\text{coil}} = X_C = 31.83\Omega$$

$$R = Z_{\text{coil}} \cos \Phi_{\text{coil}} = 31.83 \times 0.6 = 19.09\Omega$$

$$X_L = \sqrt{Z_{\text{coil}}^2 - R^2} = \sqrt{31.83^2 - 19.09^2} = 25.46\Omega$$
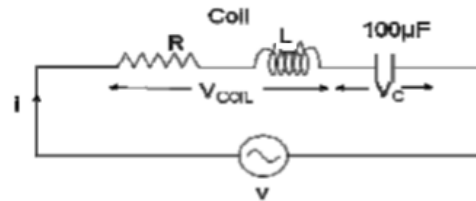
$$L = \frac{1}{2\pi f L} = \frac{1}{2 \times 3.14 \times 50 \times 25.46} = 0.081H$$



Q12. A current of  $(120-j50)A$  flows through a circuit when the applied voltage is  $(8+j12)V$ . Determine (i) impedance (ii) power factor (iii) power consumed and reactive power.

**Solution:**

$$\bar{V} = 8 + j12$$

$$\bar{I} = 120 - j50$$

$$(i) \bar{Z} = \frac{\bar{V}}{\bar{I}} = \frac{8 + j12}{120 - j50} = 0.02 + j0.11 = 0.11 \angle 79.7^\circ$$

$$Z = 0.11\Omega$$

$$\Phi = 79.7^\circ$$

$$(ii) pf = \cos \Phi = \cos 79.7^\circ = 0.179 \text{ lag}$$

$$(iii) S = VI^* = (8 + j12) \times (120 + j50) = 360 + j1840$$

$$S = P + jQ$$

$$P = 360W$$

$$Q = 1840VAR$$

Q13. The complex Volt Amperes in a series circuit are  $(4330-j2500)$  and the current is  $(25+j43.3)A$ . Find the applied voltage.

**Solution:**

$$\bar{S} = 4330 + j2500$$

$$\bar{I} = 25 + j43.3$$

$$\bar{V} = \frac{\bar{S}}{\bar{I}^*} = \frac{4330 + j2500}{25 - j43.3} = 86.6 + j50$$

**SOLUTION**

Q14. Calculate the total impedance of the circuit.


**Solution:**

$$X_L = \omega L = 2\pi fL = 2\pi \cdot 60 \cdot 142 \times 10^{-3} = 53.54 \Omega$$


$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi fC} = \frac{1}{2\pi \cdot 60 \cdot 160 \times 10^{-6}} = 16.58 \Omega$$

$$Z = \frac{1}{\sqrt{\left(\frac{1}{R}\right)^2 + \left(\frac{1}{X_L} - \frac{1}{X_C}\right)^2}} = \frac{1}{\sqrt{\left(\frac{1}{1000}\right)^2 + \left(\frac{1}{53.54} - \frac{1}{16.58}\right)^2}}$$
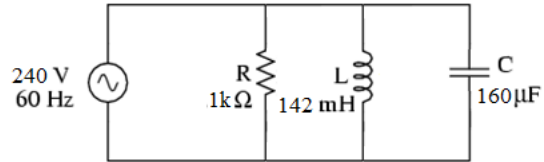
$$Z = \frac{1}{\sqrt{1.0 \times 10^{-6} + 1.734 \times 10^{-3}}} = \frac{1}{0.0417} = 24.0 \Omega$$



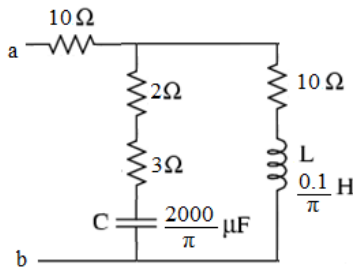Q15. Find the impedance across the terminals a-b. Consider the supply frequency as 50Hz.



**Solution:**

$$Z_{ab} = 16 - j1.99 \Omega$$

Q16. A parallel circuit comprises of a resistor of 20Ω in series with an inductive reactance 15Ω in one branch and a resistor of 30Ω in series with a capacitive reactance of 20Ω in the other branch. Determine the current and power dissipated in each branch if the total current drawn by the parallel circuit is 10∠-30° A.

**Solution:**

$$Z_1 = 20 + j15$$

$$Z_2 = 30 - j20$$

$$I = 10 \angle -30^\circ = 8.66 - j5$$

$$I_1 = I \frac{Z_2}{Z_1 + Z_2} = (8.66 - j5) \times \frac{(30 - j20)}{(20 + j15) + (30 - j20)}$$

$$I_1 = 3.8 - j6.08 = 7.17 \angle -60^\circ$$

$$I_2 = I - I_1 = (8.66 - j5) - (3.8 - j6.08)$$

$$I_2 = 4.86 + j1.08 = 4.98 \angle -12.5^\circ$$

$$P_1 = I_1^2 R_1 = 7.17^2 \times 20 = 1028.2W$$

$$P_2 = I_2^2 R_2 = 4.98^2 \times 30 = 744W$$



Q17. An impedance coil in parallel with a 100μF capacitor is connected across a 200V, 50Hz supply. The coil takes a current of 4A and the power loss in the coil is 600W. Calculate (i) the resistance of the coil (ii) the inductance of the coil (iii) the power factor of the entire circuit.

**Solution:**

$$Z_{coil} = \frac{V}{I} = \frac{200}{4} = 50 \Omega$$

$$P = I^2 R = 600W$$

$$R = \frac{600}{I^2} = \frac{600}{4^2} = 37.5 \Omega$$

$$X_L = \sqrt{Z_{coil}^2 - R^2} = \sqrt{50^2 - 37.5^2} = 33.07 \Omega$$

## SOLUTION

$$L = \frac{X_L}{2\pi f} = \frac{33.07}{2 \times 3.14 \times 50} = 0.105H$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2 \times 3.14 \times 50 \times 100 \times 10^{-6}} = 31.83\Omega$$

$$Z_1 = R + jX_L = 37.5 + j33.07$$

$$Z_2 = -jX_C = -j31.83$$

$$Z = \frac{Z_1 Z_2}{Z_1 + Z_2} = \frac{(37.5 + j33.07)(-j31.83)}{(37.5 + j33.07) + (-j31.83)}$$

$$Z = 27 - j32.72 = 42.42\angle -50.5^\circ$$

$$\Phi = -50.5^\circ$$

$$pf = \cos\Phi = \cos(-50.5^\circ) = 0.6365$$

Q18. A circuit having a resistance of  $20\Omega$  and inductance of  $0.07H$  is connected in parallel with a series combination of  $50\Omega$  resistance and  $60\mu F$  capacitance. Calculate the total current, when the parallel combination is connected across  $230V$ ,  $50Hz$  supply.

**Solution:**

$$X_L = 2\pi f L = 2 \times 3.14 \times 50 \times 0.07 = 22\Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2 \times 3.14 \times 50 \times 60 \times 10^{-6}} = 53\Omega$$

$$Z_1 = 20 + j22$$

$$Z_2 = 50 - j53$$

$$Z = \frac{Z_1 Z_2}{Z_1 + Z_2} = \frac{(20 + j22)(50 - j53)}{(20 + j22) + (50 - j53)} = 25.7 + j11.9$$

$$I = \frac{V}{Z} = \frac{230}{Z} = 7.4 - j3.4 = 8.13\angle -24.9^\circ$$

Q19. Two impedances  $Z_1 = 12 - j10$  and  $Z_2 = 10 + j12$  are connected in parallel across a  $230V$ ,  $50Hz$  supply. Calculate the equivalent impedance, current, power factor and power consumed.

**Solution:**

$$Z_1 = 12 - j10 = 15.62\angle -40 \text{ ohms}$$


$$Z_2 = 10 + j12 = 15.62\angle 50 \text{ ohms}$$

$$Z = 11.12\angle 15 \text{ ohms}$$

$$\text{Current, } I = 20.68\angle -15 \text{ A}$$

$$Pf = 0.96 \text{ lagging}$$
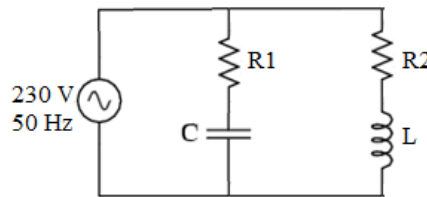
$$\text{Power} = VI \cos\phi = 4.566 \text{ kW}$$



Q20. Three impedances  $Z_1$ ,  $Z_2$ ,  $Z_3$  are connected in parallel across a  $230V$ ,  $50Hz$  supply. The values are  $Z_1 = 12\angle 30^\circ$ ,  $Z_2 = 8\angle -30^\circ$  and  $Z_3 = 10\angle 60^\circ$ . Calculate the total impedance, total current, power factor and power consumed by the whole circuit.

**Solution:**

$$\text{Total impedance, } Z = 4.25\angle 14^\circ \Omega$$

$$\text{Total current, } I = 54.05\angle -14^\circ \text{ A}$$

$$\text{Power factor} = 0.97 \text{ lagging}$$

$$\text{Power, } P = 12.058 \text{ kW}$$