

# CHAPTER

# 2


## INDUCTORS, CAPASITORS AND ALTERNATING CURRENT CIRCUITS

### 2.0 INTRODUCTION

This chapter is explaining about the inductors, capacitors and AC circuits. The learning outcome for this chapter are the students should be able to apply correctly the basic principles of inductors, capacitors and AC circuits that contains R, L and C to solve problems.

### 2.1 INDUCTOR

Inductor, choke or coil is the electric component that has the characteristics against the change of the current. Inductor made by winding the wire/conductor around the ferromagnetic material. There are two types of inductor which is often used in electronic circuits: fixed type and variable type. The symbol for inductor is as show in Figure 2.1.

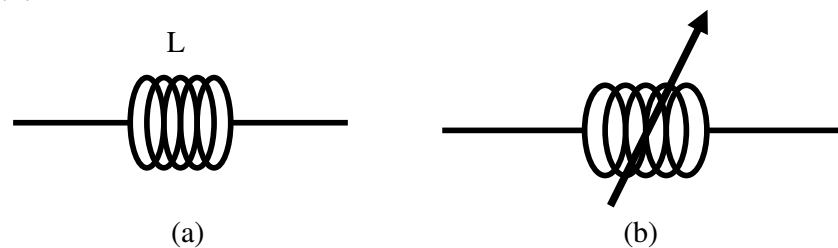


**Figure 2.1: (a) Fixed type inductor (b) variable type inductor**

Unit for inductor is Henry and the symbol is L. 1 Henry is equal to the total inductance of winding when the current is in the rate of 1 ampere per second and producing the induced voltage for 1 volt. Table 2.1 show the equivalent value and unit for inductor.

**Table 2.1: Equivalent value and unit for inductor**

Value		Units	
1	1	1 Henry	1 H
1000	$1 \times 10^3$	1 kiloHenry	1 kH
0.001	$1 \times 10^{-3}$	1 miliHenry	1 mH
0.000001	$1 \times 10^{-6}$	1 mikroHenry	1 $\mu$ H

Inductor is a spiral structure coil of wire which creates a magnetic field when current passes through it. The magnetic field through the middle of the coil is directed from left to right, and is highly intensified.

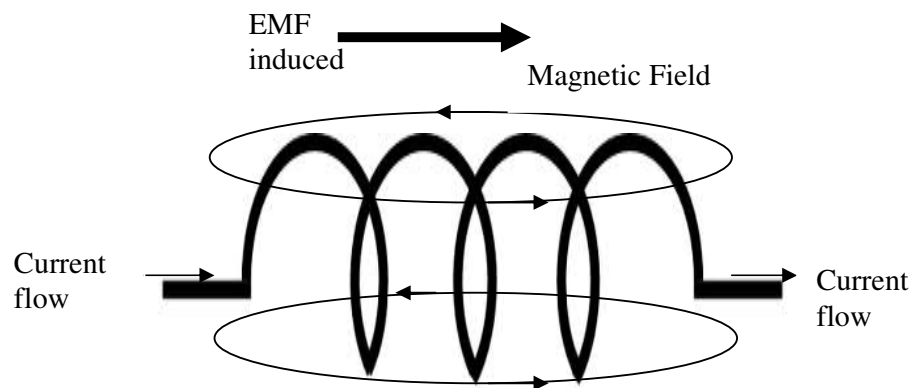**Figure 2.2: EMF Induced**

This magnetic field gives the coil some interesting and useful properties known as inductance. Increase the current in a coil will create a changing in magnetic field that will generate an electromotive force (emf) in the coil. Generated emf is opposes the applied voltage. The current through an inductance can only change gradually, it cannot change instantaneously as it could with only resistors in the circuit. The coil will store or release energy in its magnetic field as rapidly as necessary to oppose any such change.

The effects of inductor as the electrical device in the circuit are to:

- Smooth wave ripples in the DC circuit.
- Improve the transmission characteristics of waves in the telephone line


## 2.2 INDUCTANCE

Inductance is a characteristic of the inductor that opposes any change in current through itself. There are two types of inductance:

- a) Self Inductance (L)
- b) Mutual Inductance (M)

### 2.2.1 Self Inductance (L)

Self inductance occurs when a current flows in the coil causing the changing of flux in the winding. The electromotive force (emf) produced is opposite in direction to the direction of the applied voltage.

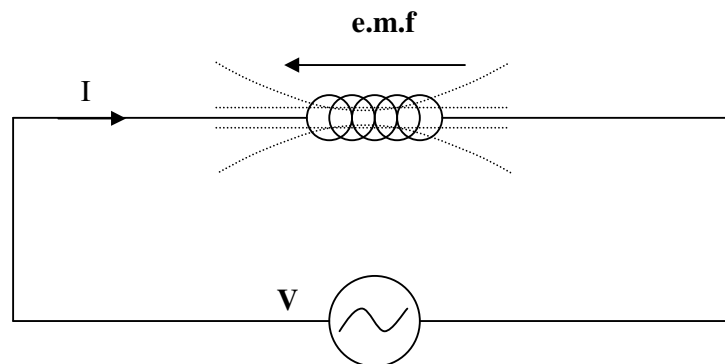

**Figure 2.3: Self Inductance**

The emf produced is opposite in direction to the current flow.

EMF generated due to changes of magnetic flux,

$$e_1 = -N \frac{d\phi}{dt} \quad \dots\dots\dots (2.1)$$

EMF generated due to changes of current,

$$e_2 = -L \frac{di}{dt} \quad \dots\dots\dots (2.2)$$

Faraday's Law;

$$e_1 = e_2 \quad \dots\dots\dots (2.3)$$

$$-N \frac{d\phi}{dt} = -L \frac{di}{dt}$$

$$L = N \frac{d\phi}{dt} \bullet \frac{dt}{di}$$

Self Inductance,  $L = N \frac{d\phi}{di}$

Where :

- L = Self Inductance
- N = Number of turns
- $\frac{d\phi}{dt}$  = flux change against time
- $\frac{di}{dt}$  = current change against time

### 2.2.2 Mutual Inductance (M)

Mutual inductance is the ability of a first coil to produce 1 emf in the nearest coil through induction or when the current in the first coil is changing.

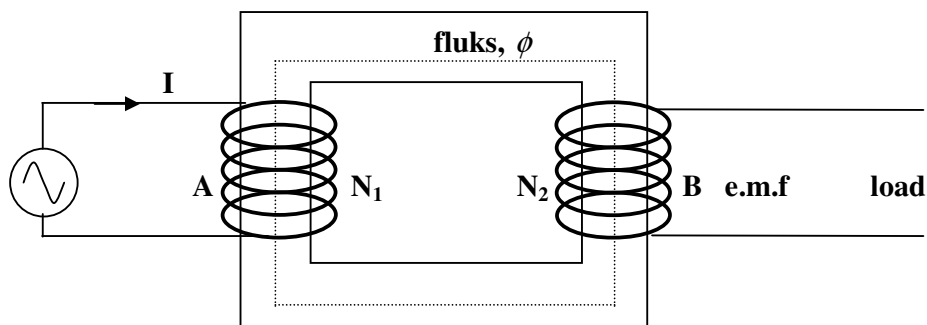


Figure 2.4: Mutual Inductance

When current flow in the first loop, flux will be produce in the first coil. The continuos current causes flux flow to the next coil and then generate emf in the second coil. Emf produced in second coil will cut the conductor and produce the voltage in second loop.

## 2.3 INDUCTOR CIRCUIT ANALYSIS

Inductors can be connected in two different ways. The two simplest of these are called series and parallel and occur very frequently.

### 2.3.1 Series Inductors

Inductors connected in series are connected along a single path, so the same current flows through all of the components. Figure 2.5 is the connection for series inductors. Total inductance ( $L_T$ ) for a series circuit is the sum of all values of inductance in the circuit.

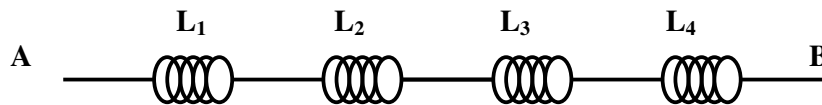


Figure 2.5: Series Inductors

$$L_T = L_1 + L_2 + L_3 + L_4 \quad (2.4)$$

### 2.2.2 Parallel Inductors

Inductors connected in parallel are opposite to each other as in Figure 2.6. The same voltage is applied to each component but the total current will split into each branches. The total inductance of inductors in parallel is equal to the reciprocal of the sum of the reciprocals of their individual inductances. Total inductance for parallel circuit can calculate using equation (2.5).

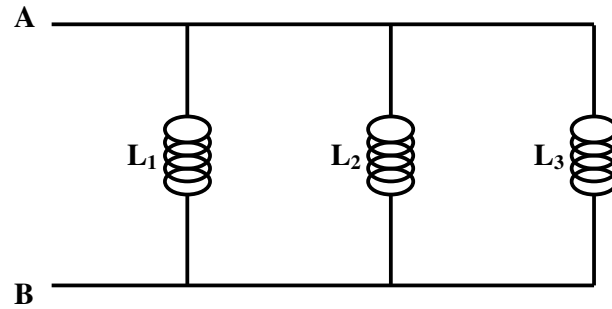


Figure 2.6: Parallel Inductors

$$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} \quad \dots\dots\dots (2.5)$$

**Example 2.1**

Calculate the total inductance ( $L_T$ ) for the three coil when the value of each inductor is 0.02H, 44mH, 400  $\mu$  H if the connection is in:

- a) Series
- b) Parallel

**Solution 2.1**

$$L_1 = 0.02\text{H}$$

$$L_2 = 44\text{mH} = 44 \times 10^{-3} = 0.044\text{H}$$

$$L_3 = 400\mu\text{H} = 400 \times 10^{-6} = 0.0004\text{H}$$

- a) series

$$L_T = L_1 + L_2 + L_3$$

$$= 0.02 + 0.044 + 0.0004 = 0.0644\text{H}$$

- b) parallel

$$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$

$$\begin{aligned}
 &= \frac{1}{0.02} + \frac{1}{0.044} + \frac{1}{0.0004} \\
 &= 2572.73 \\
 \therefore L_T &= \frac{1}{2572.73} = 389 \times 10^{-6} = 389 \mu\text{H}
 \end{aligned}$$

## 2.4 INDUCTIANCE REACTANCE, $X_L$

The alternating current (AC) is changing continuously which in turn produced continuous opposed induces emf as well. The opposition to the current flow is called inductance reactance. The symbol for inductance reactance is  $X_L$  and the unit is Ohm ( $\Omega$ ). The value of Inductance reactance in a circuit depends on the inductance of the circuit due to the current change in the circuit. The rate of current change depends on the frequency of the supply voltage. Mathematically, equation (2.7) is use to calculate inductance reactance.

$$X_L = 2\pi fL \quad \dots\dots\dots (2.6)$$

where :  $X_L$  = Inductance Reactance ( $\Omega$ )  
 $f$  = Frequency (Hz)  
 $L$  = Inductor (Henry)

### Example 2.2

A coil with 0.2H connected with AC 200V, 50Hz. Calculate the inductance reactance in the circuit.

### Solution 2.2

$$\begin{aligned}
 X_L &= 2\pi fL \\
 &= 2\pi(50)(0.2) \\
 &= 62.8 \Omega.
 \end{aligned}$$

## 2.5 ENERGY IN INDUCTOR

Energy in the inductor can be calculate using the equation 2.4 below. The unit for energy is Joule (J)

$$E = \frac{1}{2} LI^2 \quad (2.7)$$

## 2.6 CAPASITOR

Capacitor is an electrical device which is capable of storing electrical energy. Unit is Farad (F) and symbol is C. The quantity and duration of energy can be saved depends on the capacitance of the capacitor. Electrical energy stored in the capacitor is in a form of charge. A plate will has a negative charge (-ve) and the other plate is positive charge (+ve).

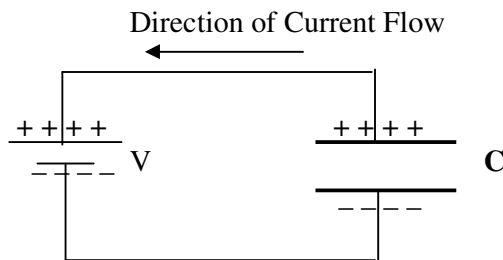


Figure 2.7 : Charges on the plate

Capacitor or condenser built with two-conductor or plate arranged opposite each other. It separated by insulating material called the dielectric as shown in Figure 6.2(a), Figure 6.2(b) show the symbol and unit for the capasitor.

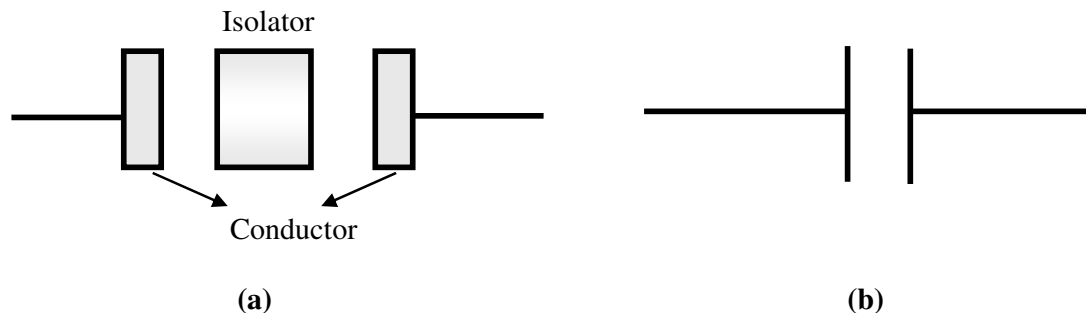


Figure 2.8 :Capasitor (a) Design Structure (b) Symbol Schematic



There are many types of capacitor which is Dielectric Air Convertible Capacitor, Paper Capacitor, Polyester Capacitor, Mica Capacitor, Ceramic Capacitor, Electrolytic Capacitor and Tantalum Capacitor

The effects of capacitor as the electrical device in the circuit are to:

1. Increasing the circuit power factor.
2. Reducing the fireworks during the switch is on inside the circuit.
3. Reduce radio interference test in the starter circuit pendafLOUR light.
4. Strengthen the electric current.
5. Store electrical charges.

## 2.7 CAPACITANCE

Capacitance is a characteristic of a capacitor to store electrical energy. It is define as the quantity or amount of electric charge needed to make a difference between the two plates. Capacitance of 1 Farad means a capacitor can store 1 coulomb of electrical charge when voltage is applied to the capacitor is 1 volt.

$$\text{Capacitance, (Farad)} = \frac{\text{Cas(Coulomb)}}{\text{Voltage(Volt)}}$$

$$C = \frac{Q}{V} \quad (2.8)$$

Typically the unit use for capacitor are microFarad ( $\mu\text{F}$ ) or pikoFarad ( $\text{pF}$ ). Table 2.2 show the equivalent value and unit for capacitor.

**Table 2.2: Equivalent value and unit for capacitor**

Value		Units	
1	1	1 Farad	1 F
0.000001	$1 \times 10^{-6}$	1 mikroFarad	1 $\mu\text{H}$
0.000000000001	$1 \times 10^{-12}$	1 pikoFarad	1 $\text{pH}$

Three (3) factors affecting the value of the capacitance of a capacitor:

1. Area of the Plate,  $A$

Capacitance is directly proportional to the cross sectional area of the plates. Capacitance of a capacitor varies with the capacitor plate area. Area of large plates to accommodate many electrons, and can save a lot of charge.

$$C \propto A.$$

2. The Distance Between Two Plates,  $d$

Capacitance is inversely proportional to the distance between the plates. Capacitance of a capacitor change when the distance between the plates changes. Capacitance will increase when the plates when the plate is brought closer and less-plates removed.

$$C \propto \frac{1}{d}$$

3. Permeability,  $\epsilon$

Capacitance is proportional to the permeability of the conductor.

$$C \propto \epsilon$$

## 2.8 CAPACITOR CIRCUIT ANALYSIS

The method of the capacitor circuit analysis is different with the method of circuit analysis for inductance. There are 3 types of circuit analysis in capacitor:

1. Series
2. Parallel
3. Combination of series and parallel

### 2.8.1 Series Capacitors

When capacitors are connected in series, the total capacitance ( $C_T$ ) is less than any one of the series capacitors' individual capacitances. If two or more capacitors are connected in series, the overall effect is that of a single (equivalent) capacitor having the sum total of the plate spacings of the individual capacitors.

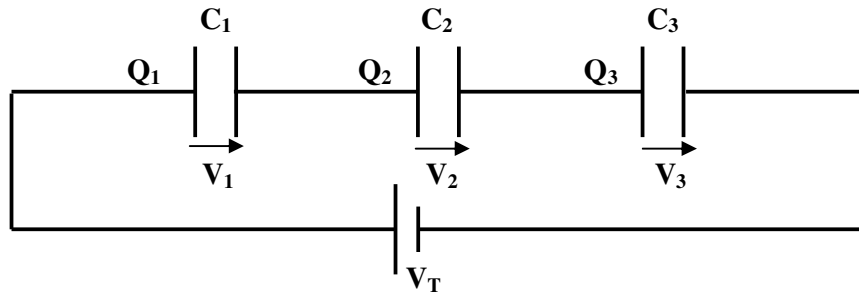


Figure 2.9 : Series Capacitors

The total capacitance is less than any one of the individual capacitors' capacitances. The formula for calculating the series total capacitance is as Equation 2.9. It is the same form as for calculating parallel resistances.

$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \quad \dots \dots \dots (2.9)$$

Equation 2.9 can be written as Equation 2.10 below.

$$C_T = \frac{C_1 C_2 C_3}{C_1 C_2 + C_1 C_3 + C_2 C_3} \quad \dots \dots \dots (2.10)$$


Charges for each capacitor connected in series are the same.

$$Q_1 = Q_2 = Q_3 = Q_T, \text{ di mana } Q_T = C_T V_T \dots \dots \dots (2.11)$$

Voltage drop for each capacitors can be calculate using Equation 2.12).

$$V_{C1} = \frac{Q_T}{C_1}, \quad V_{C2} = \frac{Q_T}{C_2} \quad \text{dan} \quad V_{C3} = \frac{Q_T}{C_3} \quad \dots\dots\dots (2.12)$$

Untuk dua(2) buah pemuat seperti litar Rajah 6.4 di bawah, kemuatan jumlah juga boleh dikira dengan menggunakan persamaan (6.9).

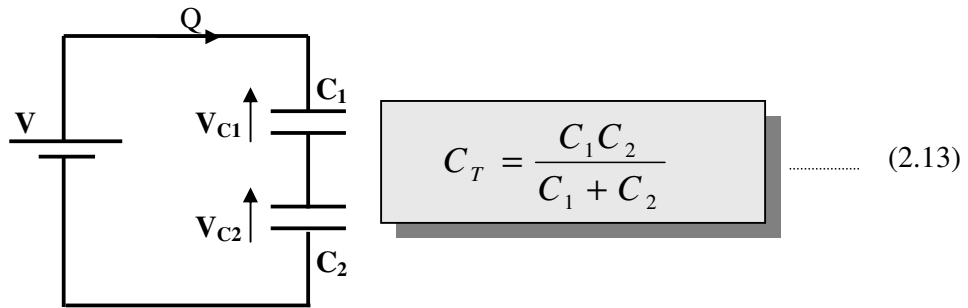

**Figure 2.10: Series with Two Capacitors**

Voltage drop for each capacitors can be calculate using Equation 2.14.

$$\left. \begin{aligned} V_{C1} &= \left( \frac{C_2}{C_1 + C_2} \right) V_T \\ V_{C2} &= \left( \frac{C_1}{C_1 + C_2} \right) V_T \end{aligned} \right\} \dots\dots\dots (2.14)$$

Charges are equal for each capacitors which connected in series.

$$Q_1 = Q_2 = Q_T$$

### 2.8.2 Parallel Capacitors

The total capacitance of capacitors in parallel is equal to the sum of their individual capacitances.

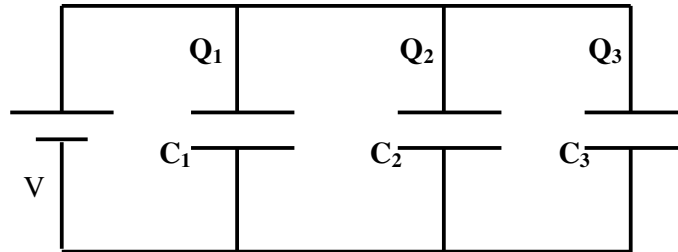


Figure 2.11: Parallel Capacitors

$$C_T = C_1 + C_2 + C_3 \quad (2.15)$$

Voltage drop at each capacitors are equal.

$$V_{C_1} = V_{C_2} = V_{C_3} = V_T \quad (2.16)$$

Value of charges through each parallel capacitor are different and can be calculated using Equation 2.17.

$$Q_{C_1} = C_1 V_T, \quad Q_{C_2} = C_2 V_T \quad \text{and} \quad Q_{C_3} = C_3 V_T \quad (2.17)$$

**Example 2.3**

Calculate the total capacitance of the three (3) capacitor where the value of each capacitance is  $120\mu\text{F}$  when it is connected in:

- Parallel
- Series

**Solution 2.3**

$$\text{a. } C_T = C_1 + C_2 + C_3 = (120+120+120) \times 10^{-6} = 360 \times 10^{-6} = 360 \mu\text{F}$$

$$\text{b. } \frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} = \frac{1}{120} + \frac{1}{120} + \frac{1}{120} = \frac{3}{120} = \frac{1}{40}$$

$$\therefore C_T = 40 \mu\text{F} .$$

**Example 2.4**

Two capacitors each value is  $6\mu\text{F}$  and  $10\mu\text{F}$  is connected in series with a  $200\text{V}$  power supply. Calculate;

- Total capacitance
- Charge in each capacitor
- Voltage across each capacitor.

**Solution 2.4**

- Total capacitance,  $C_T$

$$C_T = \frac{C_1 C_2}{C_1 + C_2} = \frac{(6)(10)}{6+10} = 3.75 \mu\text{F}$$

- The value of charges for each capacitors in series are the same,

$$Q_T = C_T V_T = (3.75 \times 10^{-6})(200) = 750 \times 10^{-6} = 750 \mu\text{C}$$

Therefore,

$$Q_1 = Q_2 = Q_T = 750 \mu\text{C}$$

- c. Voltage drop for each capacitors are different

$$V_1 = \frac{Q_T}{C_1} = \frac{750 \times 10^{-6}}{6 \times 10^{-6}} = 125V$$

$$V_2 = \frac{Q_T}{C_2} = \frac{750 \times 10^{-6}}{10 \times 10^{-6}} = 75V$$

## 2.9 CAPACITANCE REACTANCE, $X_C$

Capacitance reactance is the opposition to the flow of the current by the capacitor. Capacitance reactance value is inversely proportional to the frequency of the alternating current voltage. Symbol for capacitance reactance is  $X_C$  and the unit is ohm ( $\Omega$ ). Equation 2.18 is formula to calculate capacitance reactance.

$$X_C = \frac{1}{\omega C}, \text{ where } \omega = 2\pi f.$$

$$X_C = \frac{1}{2\pi f C} \quad \dots\dots\dots (2.18)$$

Where ,  $C = \text{Capacitance (F)}$   
 $f = \text{Frequency (Hz)}$   
 $\omega = \text{angular velocity (rads}^{-1}\text{)}$   
 $2\pi = \text{constant}$

### Example 2.5

$8\mu\text{F}$  capacitor connected to the supply of 240V, 50Hz. Calculate the value of capacitance reactance.

**Solution 2.5**

$$X_c = \frac{1}{2\pi fC} = \frac{1}{2\pi(8 \times 10^{-6})} = 397.9\Omega$$

**2.10 ENERGY IN CAPASITOR**

Energy can be calculate using Equation 2.19 below. The unit for energy is Joule.

$$E = \frac{1}{2}QV \quad \dots\dots\dots (2.19)$$

Equation 2.19 can be transform to another form in calculating energy by inserting Equation 2.8 in 2.19.

$$E = \frac{1}{2}CV^2 \quad \text{and} \quad \dots\dots\dots (2.20)$$

$$E = \frac{1}{2}\left(\frac{Q^2}{C}\right) \quad \dots\dots\dots (2.21)$$

**Example 2.6**

Capacitor with 8pF connected to the 600V power supply. Calculate the charge and energy that can be stored by the capacitor.

**Solution 2.6**

Charge,  $Q = CV = (8 \times 10^{-12})(600) = 4.8 \times 10^{-7} \text{ C}$

Energy,  $E = \frac{1}{2}QV = (4.8 \times 10^{-7})(600) = 2.88 \times 10^{-9} \text{ Joule}$



## 2.11 ALTERNATING CURRENT (AC)

Alternating Current is a current flowing in two conditions whether at negative or positive values. The current flows from zero to positive maximum, to zero again and further to negative maximum and back to zero.

Alternating voltage can be generated in 2 ways:

1. Conductors cut the magnetic flux which is the conductor is moving and the magnetic flux is stationary.
2. Magnetic flux cut the conductor where the flux is moving and conductor is stationary.

AC waveform is same as the form of sinus wave as shown in Figure 2.12


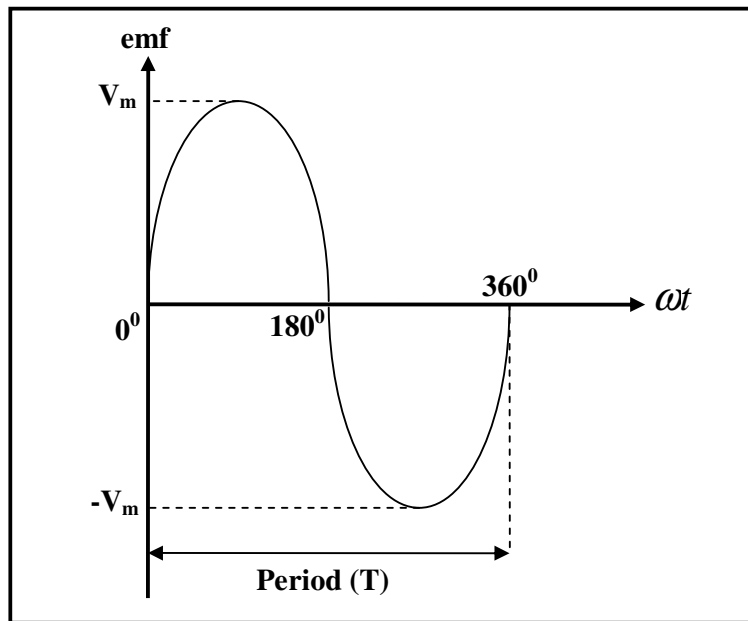


Figure 2.12: AC Waveform

$$v(t) = v_m \sin \omega t \quad \dots\dots\dots (2.22)$$

where  $v(t)$  = Instantaneous voltage (volt)  
 $v_m$  = Maximum/peak voltage (volt)  
 $\omega t$  = Phase angle against time (rad/degree)  
 $T = \frac{2\pi}{\omega}$  (second)

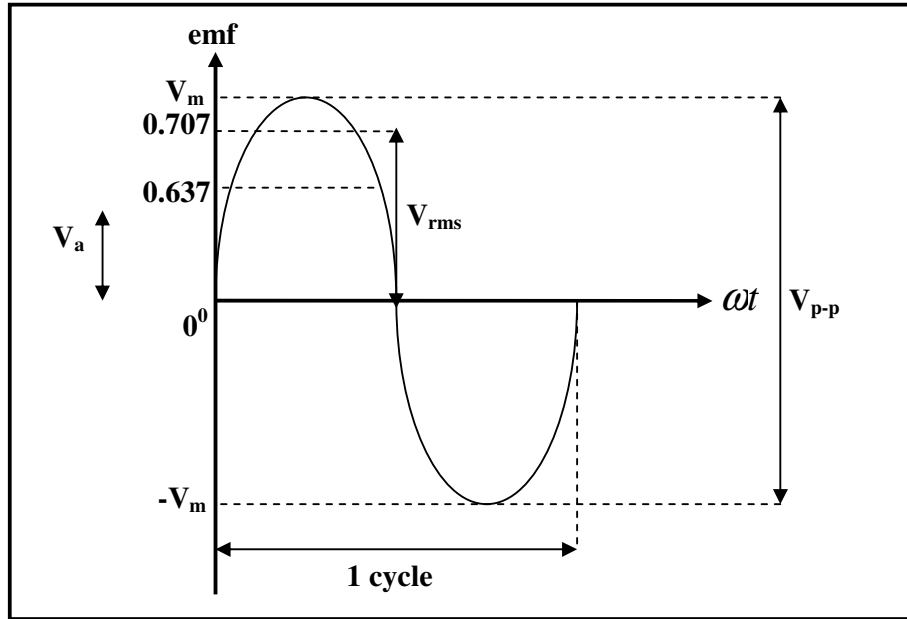

**Figure 2.13: Terms in AC Waveform**

A complete cycle/period of sine wave is  $360^\circ$  degree where  $360^\circ = 2\pi$  radian. The terms related to the AC waveform:

- a)  $V_P$  (peak voltage) is the maximum voltage ( $V_m$ ) from the waveform.

$$\boxed{V_P = V_m} \quad \dots\dots\dots (2.23)$$

- b)  $V_{PP}$  (peak to peak voltage) is the value that start from +ve maximum to -ve maximum.

$$\boxed{V_{PP} = 2V_m} \quad \dots\dots\dots (2.24)$$

- c)  $V_a$  (average voltage) is the average value for sinus wave where the value is calculated for the area under ac wave line. The value is 63.7% of maximum voltage value.

$$\boxed{V_a = 0.637 V_m} \quad \dots\dots\dots (2.25)$$

- d)  $V_{rms}$  (root mean square voltage) is the important value in electric circuits. The most of meter indicate the reading of value in rms that equal to 70.7% of the ac peak voltage value.


$$\boxed{V_{rms} = 0.707 V_m} \quad \dots\dots\dots (2.26)$$

## 2.12 TYPES OF AC WAVEFORM

There are 2 types of waveforms in AC:

1. In Phase Waveform
2. Different Phase Waveform

### 2.12.1 In Phase Waveform

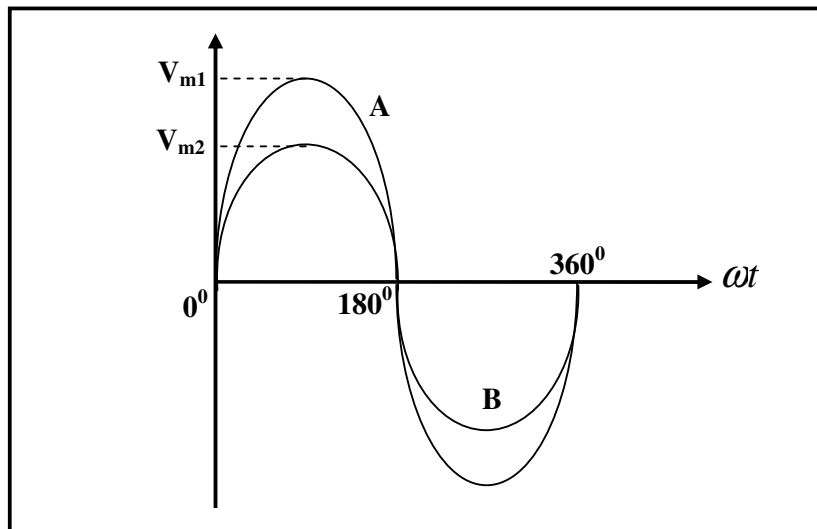


**Figure 2.14: In Phase Waveform with Different Value of  $V_m$**

Sine wave for A and sine wave for B are in phase because there is no difference in phase angle between them. But, both waves have different value of maximum voltage. The maximum voltage for A is  $V_{m1}$  while the maximum voltage for B is  $V_{m2}$ . Therefore, both waves may be described by use trigonometry Equation 2.27

$$\left. \begin{array}{l} A : v(t) = V_{m1} \sin \omega t \\ B : v(t) = V_{m2} \sin \omega t \end{array} \right\} \quad \dots\dots\dots (2.27)$$

### 2.12.2 Different Phase Waveform

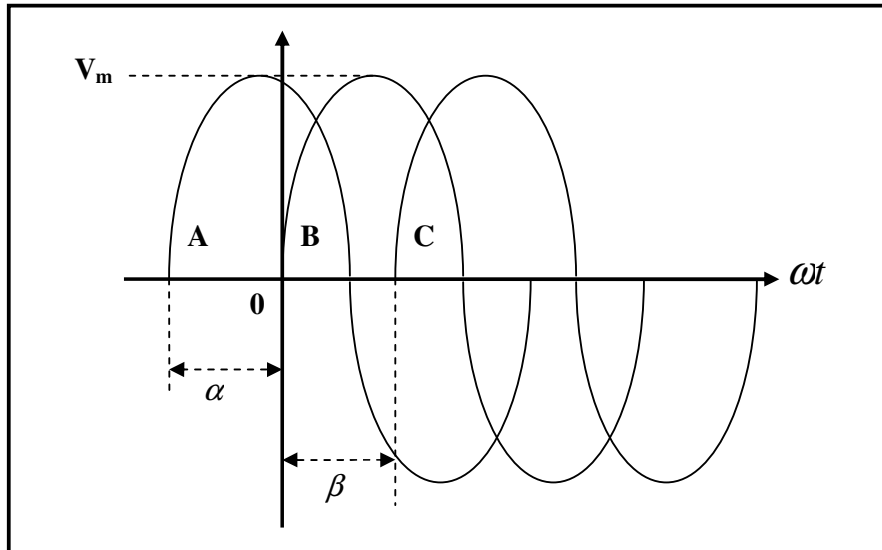

**Figure 2.15: Different Phase with Same Value of  $V_m$**

In this case, all waves have the same maximum voltage ( $V_m$ ), but reach at different period/time. Thus, there are phase differences between all waves. The phase difference is depend on the phase angle value ( $\alpha$  and  $\beta$ ). The wave through the  $0^0$  will be the reference point.

Therefore the trigonometry equations for three waves above are as below:

- a) Wave B is the reference point for the three waves.


$$v(t) = V_m \sin \omega t$$

- b) Wave A leads the wave B by a phase angle  $\alpha$

$$v(t) = V_m \sin(\omega t + \alpha) \quad \dots\dots\dots (2.28)$$

- c) Wave C lags behind the wave B by a phase angle  $\beta$


$$v(t) = V_m \sin(\omega t - \beta) \quad \dots\dots\dots (2.29)$$

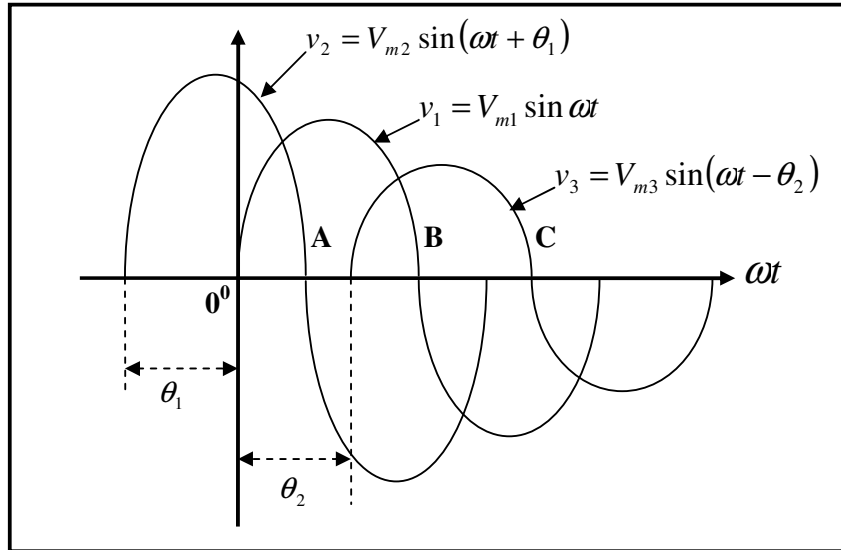

**Figure 2.16: Different Phase with Different Value of  $V_m$**

### 2.13 VECTOR/PHASOR DIAGRAM

Vector diagram is a graph provides the information of the magnitude (amplitude) and direction (phase) of a sinusoidal wave. The vector diagram is drawn corresponding to a fix zero point or known as point of origin. A vectors magnitude is the peak value of the sinusoid while a phase magnitude is the rms value of the sinusoid.

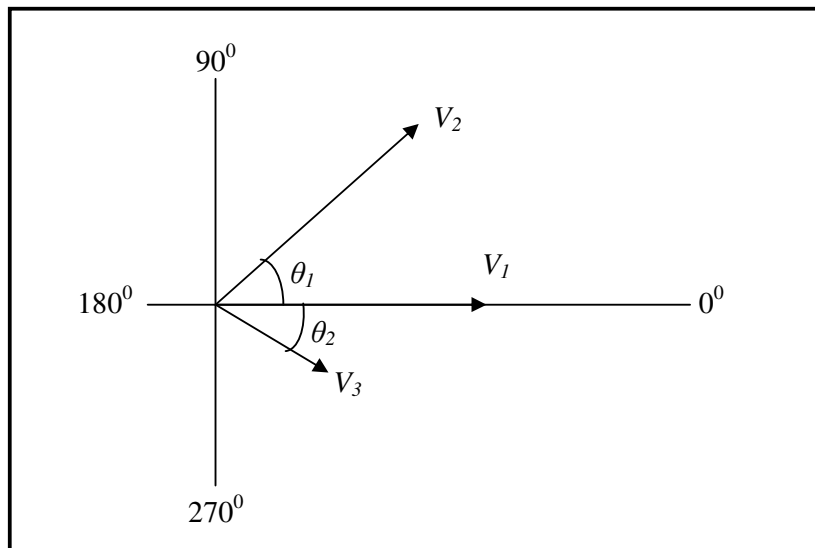

**Figure 2.17: Vector Diagram**


Figure 2.17 is a vector diagram for the AC wave in Figure 2.16. The length of the arrow refers to the magnitude which depend on the peak value of each wave. Meanwhile the direction the vectors are located based on the phase different of each waves started at zero ( $0^0$ ) or origin point.

## 2.14 BASIC TYPES OF AC CIRCUIT

There are 3 basic types of AC circuit:

1. Purely Resistance
2. Purely Inductance
3. Purely Capacitance

### 2.14.1 Purely Resistance

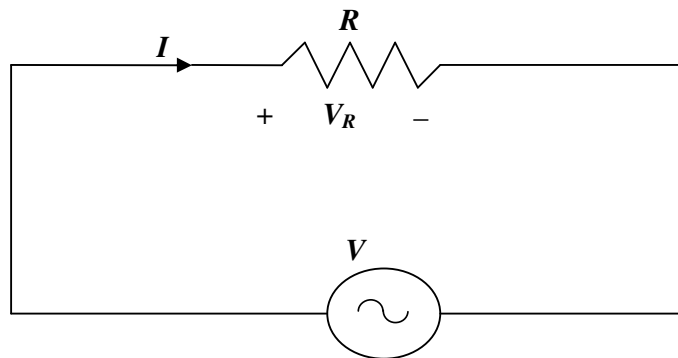


**Figure 2.18: Purely Resistance Circuit**

By applying an alternating voltage to a circuit that contain the resistor, the alternating current value in the circuit can be determined by Ohm's Law as equation 2.30

$$I = \frac{V}{R} \quad \dots\dots\dots (2.30)$$

In a purely resistance circuit, the current and the voltage are in phase because there is no difference angle. Hence, the wave diagram and the vector diagram are shown in Figure 2.19

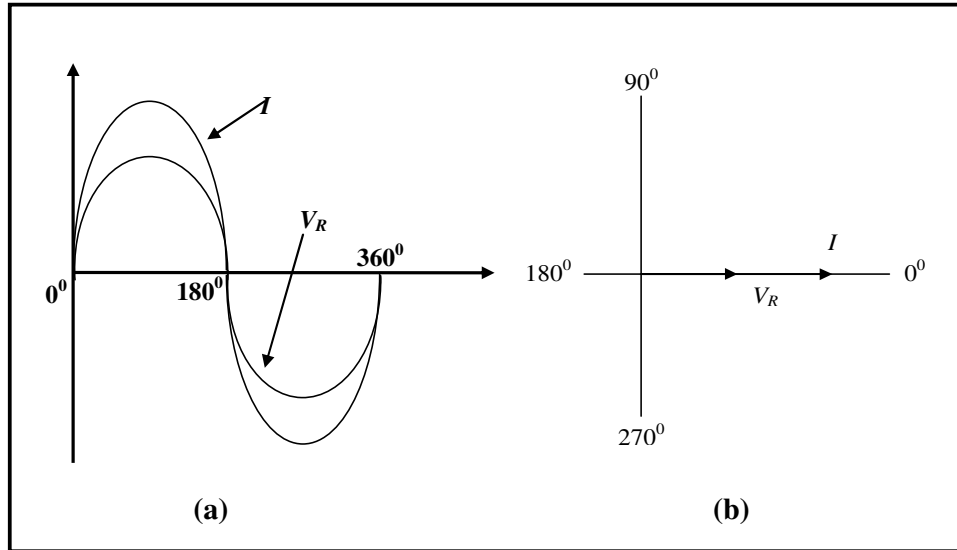

**Figure 2.19: Purely Resistance (a) Waveform (b) Vector Diagram**


The effects of resistance in AC circuit are:

- a) If the resistance increases then the current decreases.
- b) If the resistance decreases then the current increases.

AC current flow which flow in ac circuit with purely resistance is not influence by the value of the frequency.


### 2.14.2 Purely Inductance

Purely inductance ac circuit is a circuit containing only an inductor. When the currents flow in the inductance coil, the coil becomes an electromagnet. The electromagnet will generate the induced voltage that opposes the flowing of current in the coil circuit.

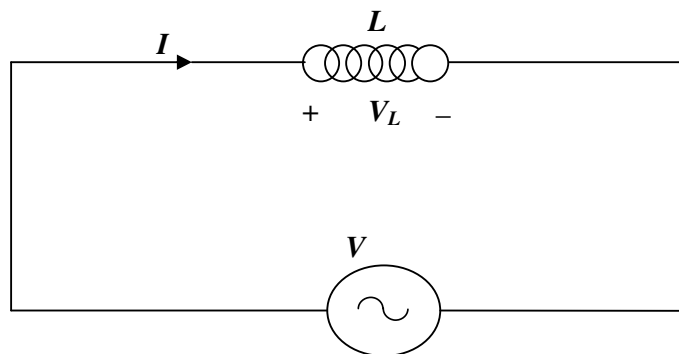

**Figure 2.30: Purely Inductance Circuit**

The current in purely inductance circuit lags behind the voltage by a phase angle of  $90^\circ$ . Therefore, Figure 2.31 shows the waveform and vector diagram for purely inductance circuit.

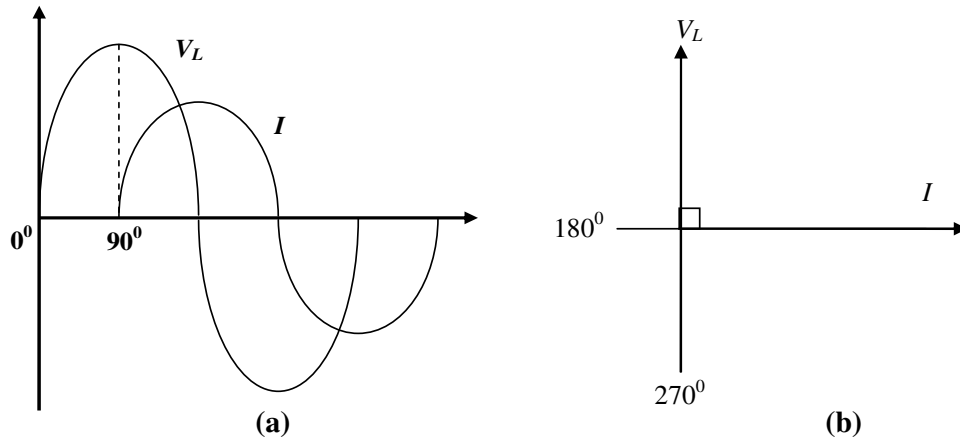


**Figure 2.31: Purely inductance (a) Waveform (b) Vector Diagram**

The effects of inductance in AC circuit are:

- a) The value of inductance reactance is equal to resistance of resistor.
- b) The inductance reactance is directly proportional to the frequency. When the frequency is increases, the voltage also increases and the reactance is increases too.

### 2.14.3 Purely Capacitance


Purely capacitance is an ac circuit containing only a capacitor.

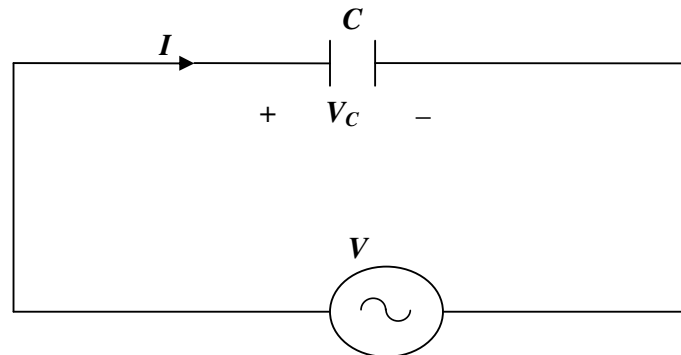

**Figure 2.32: Purely Capacitance Circuit**



In purely capacitance circuit, the current leads the voltage by a phase angle of  $90^\circ$ .

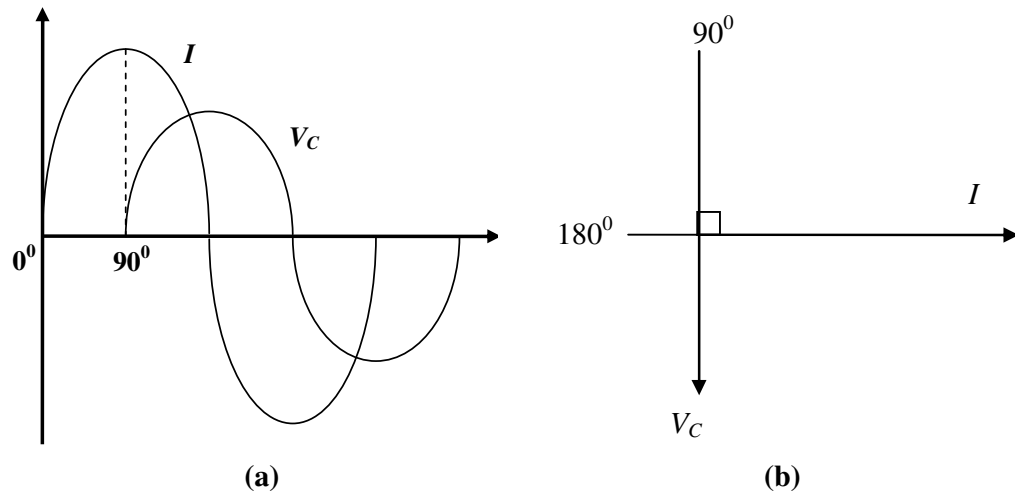

**Figure 2.33: Purely capacitance (a) Waveform (b) Vector Diagram**

The effects of capacitance in AC circuit are:

- a) Capacitance reactance value is equal to the resistance value of resistor.
- b) The capacitance reactance is directly proportional to the frequency. When frequency is increases, hence capacitance reactance is also increases.

NOTE:

### CIVIL

**C (CAPACITANCE) – I V** (The current leads the voltage by a phase angle of  $90^\circ$ )

**L (INDUCTANCE) – V I** (The voltage leads the current by a phase angle of  $90^\circ$ )


Resistance (R) and reactance ( $X_L$  or  $X_C$ ) are different although same in unit ( $\Omega$ ).

- ✓ Resistance is oppose to the current flow in both DC and AC circuits.
- ✓ Reactance is oppose to the current flow only in AC circuit
- ✓ Impedance (Z) also oppose to the current flow in only AC circuit.

## 2.15 AC CIRCUIT ANALYSIS


### 2.15.1 Series Resistance and Inductance (RL)

The RL circuit is the combination between resistor and inductor in series. In a series circuit, the current value is the same for each load. Thus, the current ( $I$ ) become the reference factor in the vector diagram.

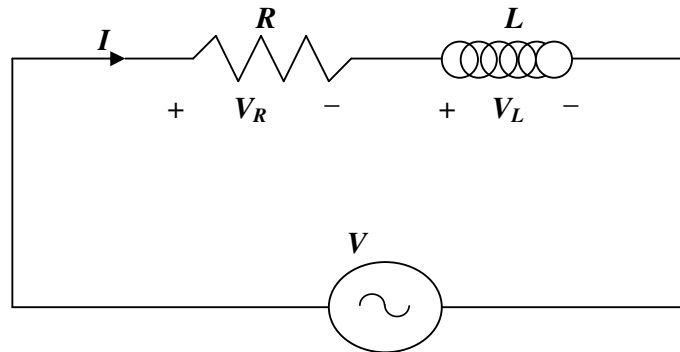

**Figure 2.34: Series RL Circuit**

The value of the current is limited by resistance and inductance reactance. The current flows through the resistance,  $R$  is in phase with the voltage but lags behind the voltage by a phase angle of  $90^\circ$  when flows through the inductance reactance,  $X_L$ .

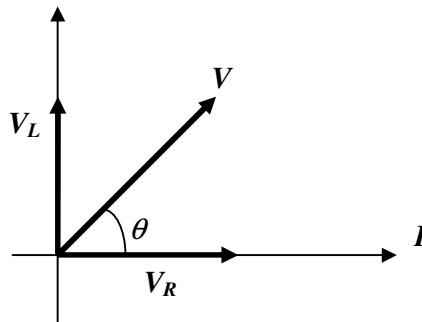

**Figure 2.35: Vector Diagram for Series RL Circuit**


Based on Figure 2.34, the magnitude of the supply voltage ( $V$ ) can determine using Pythagoras theorem.

$$V = \sqrt{V_R^2 + V_L^2} \quad \text{..... (2.31)}$$

The voltage drop at each components can be calculate using equations below;

$$V_R = IR_L \text{ and } V_L = IX_L \quad \text{..... (2.32)}$$

The impedance is the amount of impediment/resistance that exist in the ac circuit. The symbol for impedance is  $Z$  and unit is Ohm ( $\Omega$ ). An impedance triangle in Figure 2.36 show the relationship between the resistance ( $R$ ), inductance reactance ( $X_L$ ) and impedance ( $Z$ ) can be generated based on the Figure 2.35.

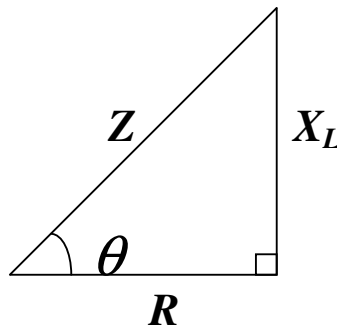

**Figure 2.36: Impedance Triangle for RL**

Impedance can be calculates using Equation 2.33.

$$Z = \sqrt{R^2 + X_L^2} \quad \text{..... (2.33)}$$

Or

$$Z = R + jX_L$$

$$Z = r < \theta$$

Where  $X_L = 2\pi fL$

Phase angle and power factor for RL circuit can be calculated using equations below:

$$\text{Phase angle, } \theta = \tan^{-1}\left(\frac{X_L}{R}\right) \quad \dots\dots\dots (2.34)$$

$$\text{Power factor, pf} = \cos \theta = \frac{R}{Z} \quad \dots\dots\dots (2.35)$$

### Example 2.7

The RL series circuit have 10Ω resistor, 0.2H inductor and supplied with 250v 50Hz AC supply. Calculate;

- i. Impedance, Z
- ii. Current, I
- iii. Phase angle,  $\theta$

### Solution 2.7

- i. Impedance, Z

$$X_L = 2\pi fL = 2\pi(50)(0.2) = 62.83 \Omega$$

$$\begin{aligned} Z &= R + jX_L \\ &= 10 + j62.83 \\ &= 63.62 \angle 80.95^\circ \Omega \end{aligned}$$

- ii. Current, I


$$\begin{aligned} I &= V/Z \\ &= \frac{250 \angle 0^\circ}{63.62 \angle 80.95^\circ} \\ &= 3.929 \angle -80.95^\circ \text{ A} \end{aligned}$$

- iii. Phase angle,  $\theta$

$$\begin{aligned} \theta &= \tan^{-1}(X_L/R) \\ &= \tan^{-1}(62.83/10) \\ &= 80.95^\circ \end{aligned}$$


### 2.15.2 Series Resistance and Capacitance (RC)

The RC circuit is the combination between resistor and capacitors in series. The current value is the same for each load. Thus, the current ( $I$ ) become the reference factor in the vector diagram.

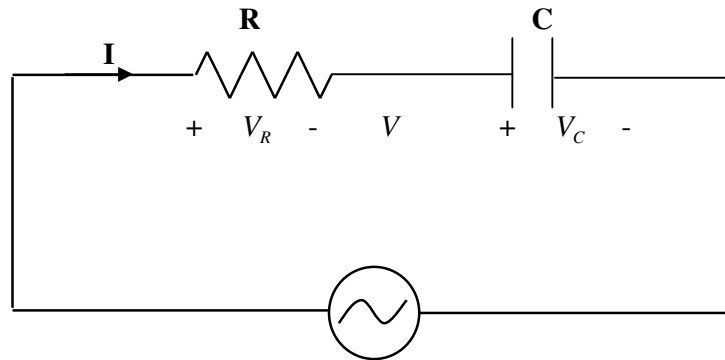

**Figure 2.37: Series RC Circuit**

The value of the current is limited by resistance,  $R$  and capacitance reactance,  $X_C$ . The current flows through  $R$  is in phase with the voltage but leading by a phase angle of  $90^\circ$  when flows through inductance reactance. Figure 2.38 is a vector diagram for series RC circuit.

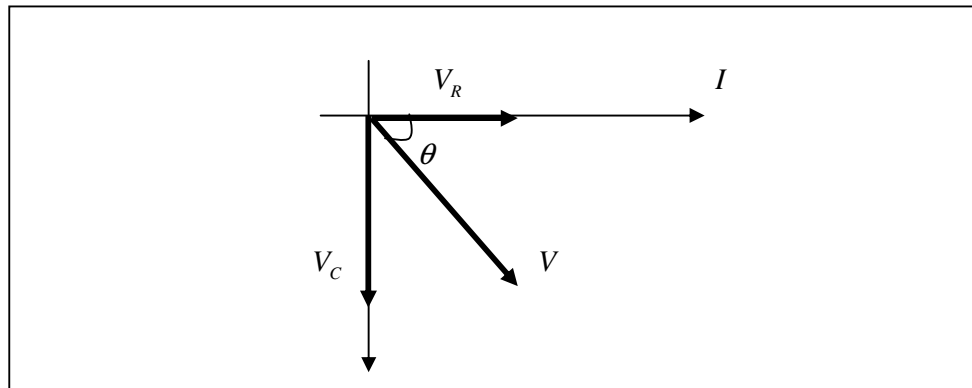

**Figure 2.38: Vector Diagram for Series RC Circuit**


Based on Figure 2.38, the magnitude of the supply voltage ( $V$ ) can determine using Pythagoras theorem.

$$V = \sqrt{V_R^2 + V_L^2} \dots\dots\dots (2.36)$$

The voltage drop at each components can be calculate using equations below;

$$V_R = IR_L \text{ and } V_C = IX_C \text{..... (2.37)}$$

An impedance triangle in Figure 2.39 show the relationship between the resistance (R), capacitance reactance ( $X_C$ ) and impedance (Z) which generated based on the Figure 2.38.

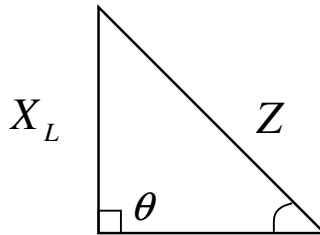

**Figure 2.39: Impedance Triangle for RC**

Impedance can be calculates using Equation 2.38.

$$Z = \sqrt{R^2 + X_C^2} \text{..... (2.38)}$$

Or

$$Z = R - jX_C$$

$$Z = r < -\theta$$

Where  $X_C = 1 / (2\pi fC)$

Phase angle and power factor for RC circuit can be calculates using equations below:

$$\text{Phase angle, } \theta = \tan^{-1}\left(\frac{X_C}{R}\right) \text{..... (2.39)}$$

$$\text{Power factor, pf} = \cos \theta = \frac{R}{Z} \text{..... (2.40)}$$

**Example 2.8:**

A  $10\Omega$  resistor and  $200\mu\text{F}$  capacitor are connected in series across a 120V, 50V AC supply. Calculate:

- i. Impedance,  $Z$
- ii. Current,  $I$
- iii. Power factor, pf

**Solution 2.8:**


Given:  $R = 10\Omega$ ,  $C = 200\mu\text{F}$ ,  $V = 75\text{V}$  dan  $f = 50\text{Hz}$ .

$$\text{where, } X_c = \frac{1}{2\pi f C} = \frac{1}{2\pi(50)(200 \times 10^{-6})} = 15.92\Omega$$

- i. Impedance,  $Z = R - jX_c$   
 $= 10 - j15.92$   
 $= 18.8 \angle -57.86^\circ \Omega$
- ii. Current,  $I = V/Z$   
 $= \frac{75 \angle 0^\circ}{18.8 \angle -57.86^\circ}$   
 $= 3.989 \angle 57.86^\circ$
- iii. Power Factor, pf =  $\cos \theta = \frac{R}{Z} = \frac{10}{15.92} = 0.628$

**2.15.3 Series Resistance, Inductance and Capacitance (RLC)**


The RLC circuit is the combination of resistor, inductor and capacitor in series with AC supply. The current value is the same for each load. Thus, the current ( $I$ ) become the reference factor in the vector diagram.

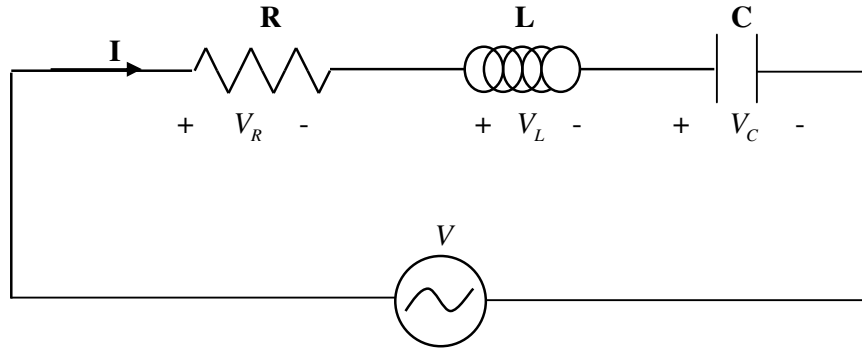

**Figure 2.40: Series RLC Circuit**

In RLC there are (2) conditions should to be consider;

- a) inductance reactance is greather than capacitance reactance,  $X_L > X_C$

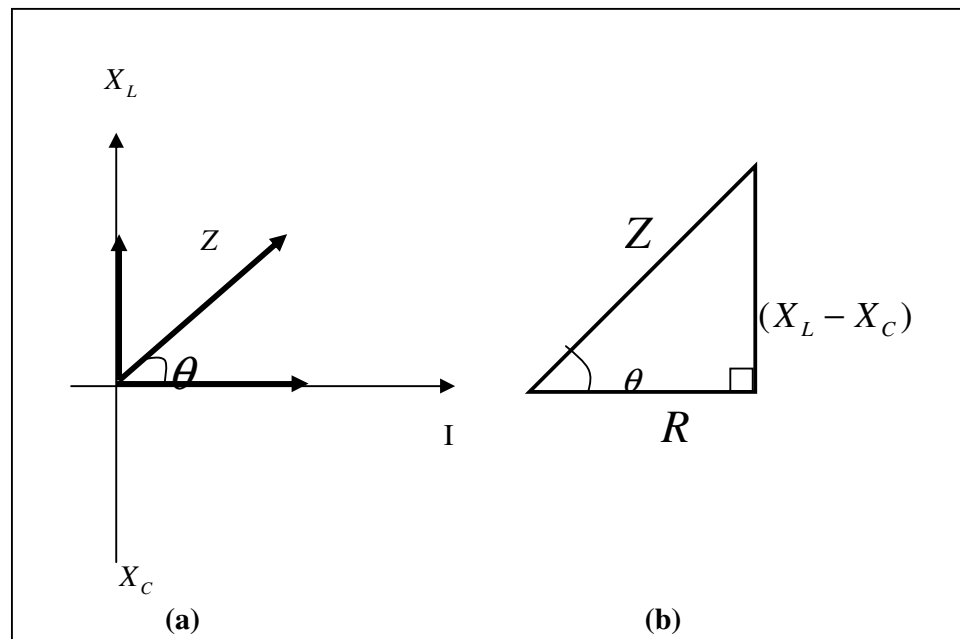

**Figure 2.41: (a) Vector Diagram (b) Impedance Triangle for  $X_L > X_C$**

The impedance for RLC can be calculate using Equation 2.41 below:

$$Z = \sqrt{R^2 + (X_L - X_C)^2} \quad \text{..... (2.41)}$$



Or

$$Z = R - j(X_L - X_C)$$

$$Z = r < \theta$$

Voltages drop at each components can be calculate using equations below;

$$V_R = IR, V_C = IX_C \text{ and } V_L = IX_L \quad \dots\dots\dots (2.42)$$

Phase angle and power factor for RC circuit can be calculates using equations below:

$$\text{Phase angle, } \theta = \tan^{-1}\left(\frac{X_L - X_C}{R}\right) \quad \dots\dots\dots (2.43)$$

$$\text{Power factor, pf} = \cos \theta = \frac{R}{Z} \quad \dots\dots\dots (2.44)$$

b) Capacitance reactance is greater than inductance reactance,  $X_C > X_L$

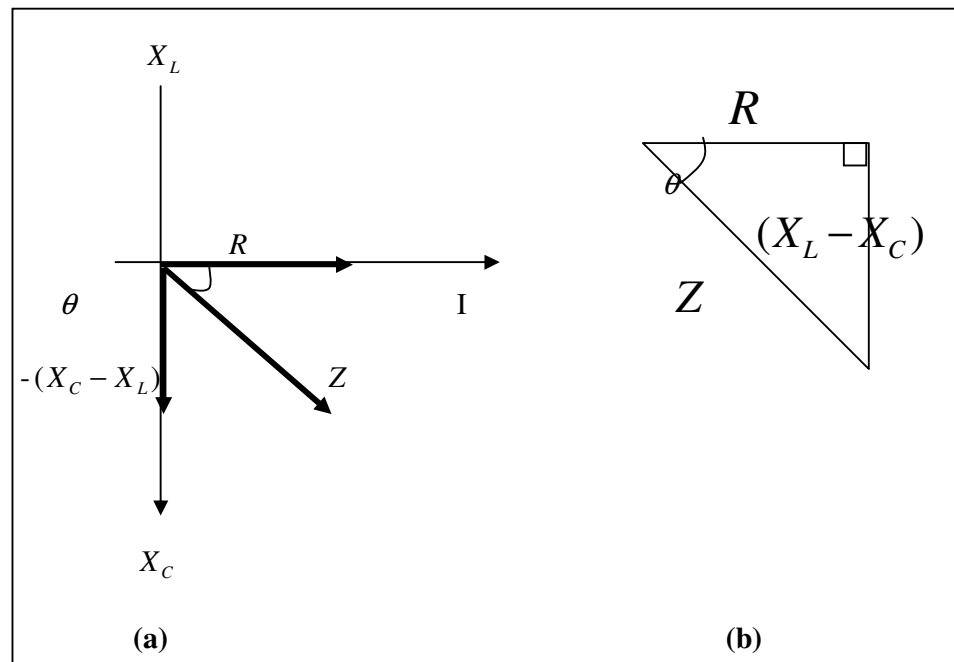


Figure 2.42: (a) Vector Diagram (b) Impedance Triangle for  $X_C > X_L$

The analysis for calculating impedance, current, voltage drop at each components, phase angle and power factor are same as  $X_L > X_C$ . The different only at the value of phase which is -ve that show the direction of the angle.

$$Z = r < -\theta$$

## 2.16 POWER FACTOR

Power factor can be express in the form of percentage (%) or fractional numbers. It is known as  $\cos \theta$  and referred to as leading (lead) or lagging (lag) in which the phase angle between voltage and current.

- a. Power factor is a ratio between real power and apparent power.

$$\cos \theta = \frac{P}{S} \quad \dots\dots\dots (2.45)$$

- b. Power factor is a ratio between resistance and impedance.

$$\cos \theta = \frac{R}{Z} \quad \dots\dots\dots (2.46)$$

- c. Leading power factor is voltage leading the current when voltage as reference factor and value of the voltage is positive.
- d. Lagging power factor is voltage lagging the current the when voltage as reference factor and value of the voltage is negative.
- e. Best value of power factor is where  $\cos \theta = 1$  or nearly 1.

## 2.17 POWER IN AC CIRCUIT

There are 3 types of power in the ac circuit;

- a) Apparent power, S
- b) Real Power, P
- c) Reactive Power, Q

### 2.17.1 Apparent power , S

Power is reduced due to the existence of the reactance that cause current and voltage is not in phase. The separation of current and voltage caused the power in the circuit will be reduced. The simbol is S and unit is Volt –Ampere (VA)

Apparent Power = Voltage x Current

$$S = VI \quad \text{..... (2.47)}$$

### 2.17.2 Real Power, P

Real power or active power is the power consumed or absorbed by the resistor components in ac circuits. The symbol is P and the unit is watt (w).

Real Power = Voltage x Current x Power Factor

$$P = VI \cos \theta \quad \text{..... (2.48)}$$

### 2.17.3 Reactive Power, Q

Reactive Power or Reactance Power is the power consumed or absorbed by the capacitor or inductor components in ac circuits . The simbol is Q and unit is Volt Ampere Reactive (VAR)

Reactive Power = Voltage x Current x Sin  $\theta$

$$Q = VI \sin \theta \quad \text{..... (2.49)}$$

## 2.18 POWER TRIANGLE

Power triangle shows the relationship between the apparent power, real power and the reactive power.

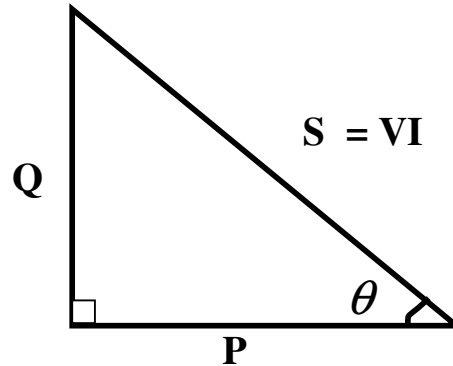


Figure 2.43: Power Triangle

### Example 2.9:

A RLC circuit was connected in series with 100 ohms resistor, 200mikroF capacitor and 100mH inductor then supplied with AC power supply 240V, 50Hz. Calculate;

- i. Impedance,  $Z$
- ii. Current,  $I$
- iii. Power factor and phase angle
- iv. Power in kVA, kW and kVAR .

### Solution 2.9:

$$X_L = 2\pi fL = 2\pi(50)(100 \times 10^{-3}) = 31.42\Omega$$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(50)(200 \times 10^{-6})} = 15.91\Omega$$

- i. Impedance,  $Z = R + j(X_L - X_C)$   
 $Z = 100 + j(31.42 - 15.91)$

$$Z = 100 + j 15.51$$

$$Z = 101.19 \angle 8.9^\circ \Omega$$

$$\begin{aligned} \text{ii. } I &= \frac{V}{Z} \\ &= \frac{240 \angle 0^\circ}{101.19 \angle 8.9^\circ} \\ &= 2.37 \angle -8.9^\circ \end{aligned}$$

$$\text{iii. Power factor, pf} = \cos \theta = \frac{R}{Z} = \frac{100}{101.2} = 0.988$$

$$\text{Phase Angle, } \theta = \cos^{-1}\left(\frac{R}{Z}\right) = \cos^{-1}(0.988) = 8.9^\circ$$

iv. Apparent Power, S in kVA,

$$S = VI = (240)(2.37) = 568.8 = 0.57 \text{ kVA}$$

Real Power in kW,

$$P = VI \cos \theta = (568.8)(0.988) = 562 = 0.562 \text{ kW}$$

Reactive Power in kVAR,

$$Q = VI \sin \theta = (568.8)(\sin 8.9^\circ) = 88 = 0.09 \text{ kVAR}$$

## REFERENCES




Hughes, E., 1960, "Electrical Technology 3<sup>rd</sup> Edition", University of Michigan, Longmans

Erickson, W.H., 1952, "Electrical engineering, theory and practice", University of Wisconsin – Madison, Wiley


## PROBLEMS

1. Calculate the total inductance ( $L_T$ ) which connected in series and parallel for combination of three coils below:
  - i. 0.02H, 44mH and 400 $\mu$ H,
  - ii. 0.05H, 30mH and 755 $\mu$ H
  - iii. 0.08 H, 400mH and 400 $\mu$ H
  - iv. 15 mH, 50 mH and 75 mH.  
(64.4mH, 388 $\mu$ H, 80.7mH, 725.7 $\mu$ H, 480mH, 397.6  $\mu$ H, 140mH, 10mH)

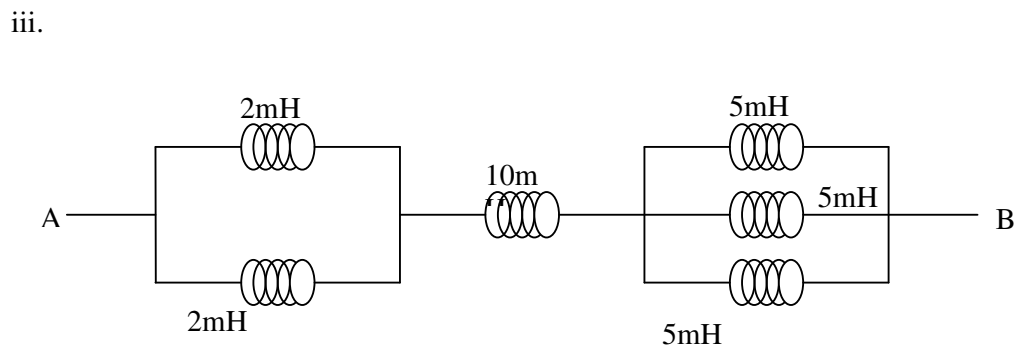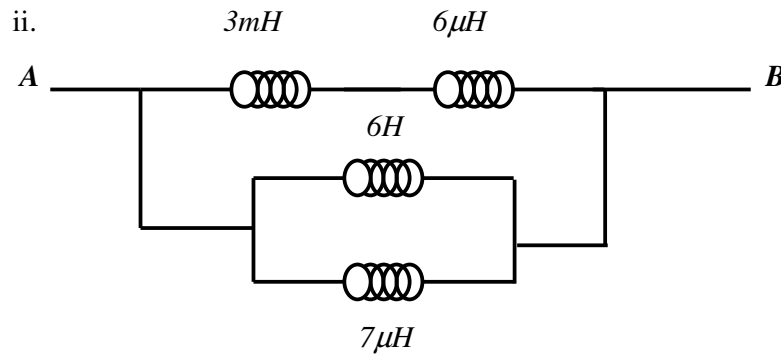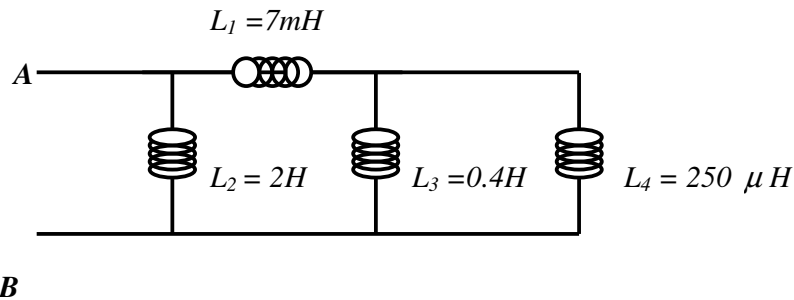
2. Based on figure below, calculate the total inductance ( $L_T$ ) if measured at point A and B.
  - i.




iv.

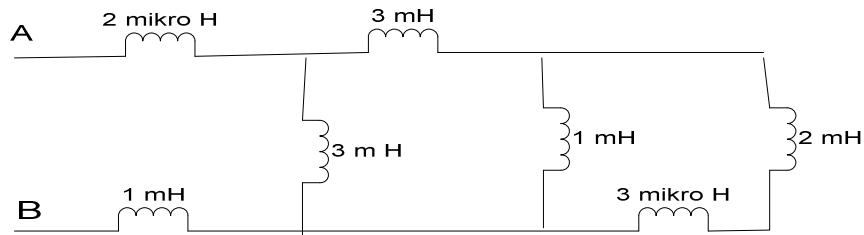

v.

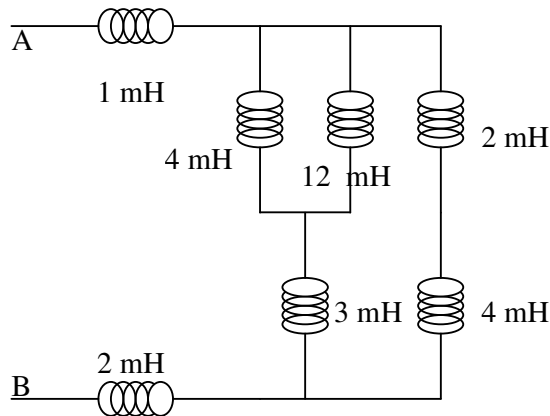


vi.

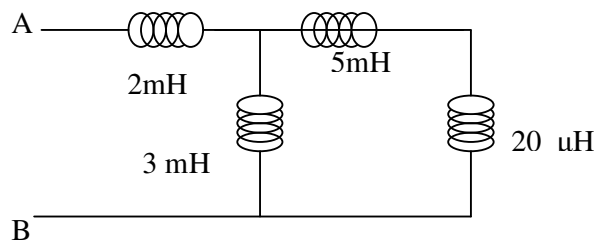

(10mH, 6.98μH, 12.6mH, 4.65mH, 6mH, 3.88mH)


3. Coil with 0.2H connected with AC circuit 200V, 50Hz. Calculate the Inductive reactance.  
(62.8Ω)
4. A coil with 6H connected to AC 12 V 50 Hz. Calculate the current flow.  
(0.19A)
5. A capacitor with 50μF connected to AC 115 V 60 Hz. Calculate capacitance reactance and current flow.  
(53.1Ω, 2.167A)
6. A capacitor with 120μF connected with 500 V 50 Hz. Calculate capacitance reactance and current flow.  
(26.52Ω, 18.8A)

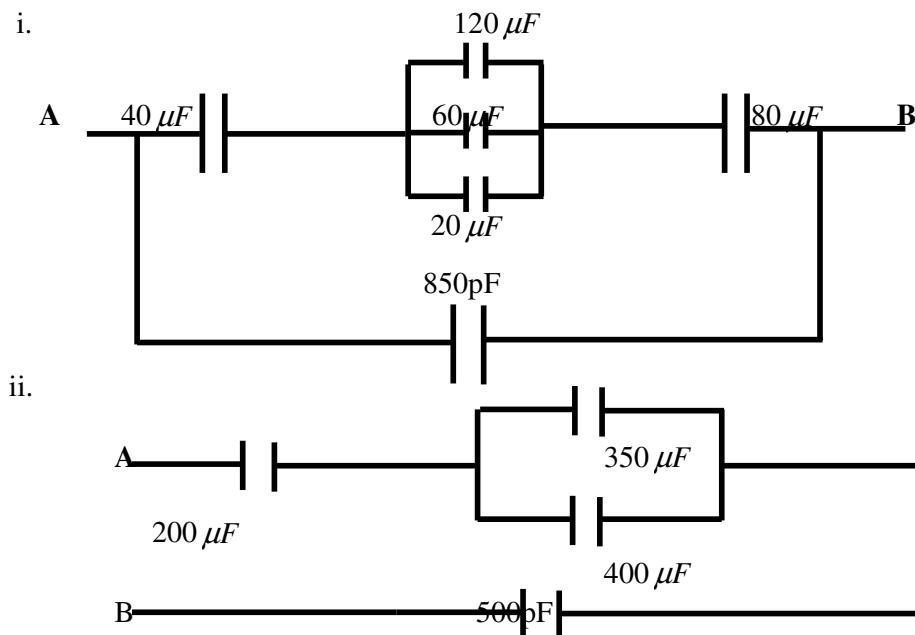7. A capacitor  $1000\mu\text{F}$  connected to AC 20 V 50 Hz.
- Calculate current flow
  - What is the effect of the current if the frequency change to 1000Hz.  
(6.28A, increasing)
8. Capacitor with  $50\mu\text{F}$  connected with 240V power supply. Calculate the charge and energy stored in the capacitor.  
(0.012 C, 1.44 J)
9. Capacitor with  $8\mu\text{F}$  connected with 240V, 50Hz power supply. Calculate the Capacitance Reactance.  
(397.88 $\Omega$ )
10. Calculate the total capacitance ( $C_T$ ) which connected in series and parallel for combination of three capacitors below:
- $120\mu\text{F}$ ,  $240\mu\text{F}$  dan  $360\mu\text{F}$   
(65.45 $\mu\text{F}$ , 720 $\mu\text{F}$ )
11. Calculate the value of capacitor which is connected in series with other  $60\mu\text{F}$  capacitor, where the total capacitance is  $15\mu\text{F}$ .  
(20 $\mu\text{F}$ )
12. 2 capacitors with values  $6\mu\text{F}$  and  $10\mu\text{F}$  respectively, connected in series with 200V power supply. Calculate ;
- Total Capacitance
  - Charge at each capacitors
  - Voltage drop at each capacitors  
(3.75 $\mu\text{F}$ ,  $750 \times 10^{-6}\text{C}$ , 125V and 75V)
13. Based on figure below, calculate the total capacitance ( $C_T$ )







iii.

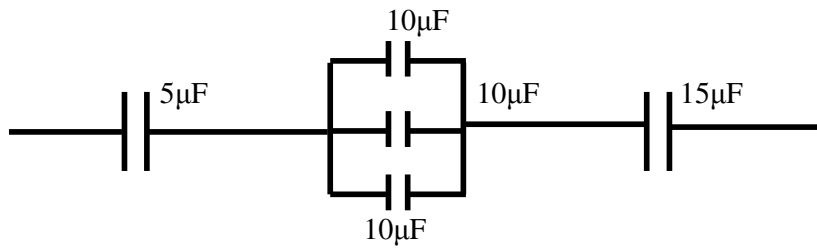

iv.

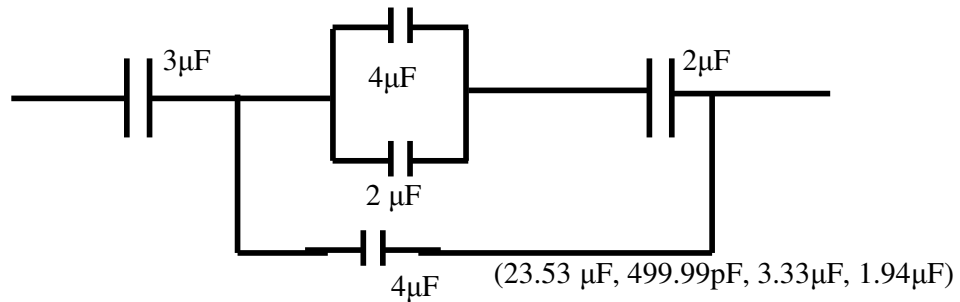

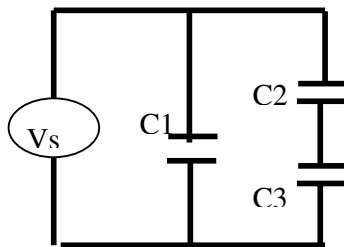
14. 3 capacitors  $C_1 = 6 \mu\text{F}$ ,  $C_2 = 12 \mu\text{F}$  dan  $C_3 = 16 \mu\text{F}$  connected with 60 v power supply as shown in figure below. Calculate:



- Total Capacitance
- Charge at each capacitors
- Voltage drops at each components
- Energy used.

( $12.85 \mu\text{F}$ ,  $3.6 \times 10^{-4} \text{ C}$ ,  $4.12 \times 10^{-4} \text{ C}$ , 60v, 34.28v, 25.72v, 0.023J)

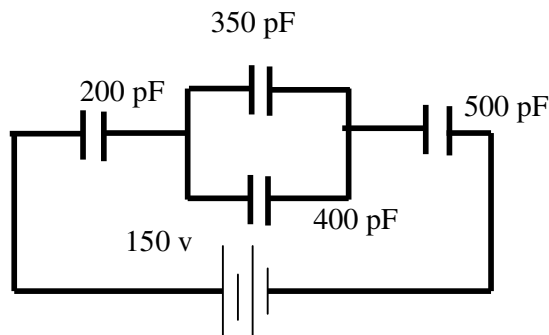15. Based on figure below, calculate total capacitance,  $C_T$  and total charge,  $Q_T$ .



( $120 \text{ pF}$ ,  $18 \times 10^{-9} \text{ C}$ )

16. A circuit with 3 capacitors  $C_1$ ,  $C_2$  and  $C_3$  connected in series with values  $3\mu\text{F}$ ,  $4\text{pF}$  and  $1\mu\text{F}$  respectively. If the voltage supply is  $100\text{V}$ , calculate:
- Total capacitance,  $C_T$
  - Total Charge,  $Q_T$
  - Voltage drop at  $C_1$
- ( $3.99\text{pF}$ ,  $3.99 \times 10^{-10}\text{C}$ ,  $0.133\text{mV}$ )
17. Series RL with  $25\Omega$  and  $25\text{mH}$  connected to AC  $60\text{V}$ ,  $100\text{Hz}$ . Calculate the current and phase angle referred to supplied voltage.
- ( $2.03 \angle 0^\circ\text{V}$ ,  $32.12^\circ$ )
18. Series RLC with  $R=33\Omega$ ,  $L=50\text{mH}$  and  $C=10\mu\text{F}$ . Voltage supply  $75\text{V}$ ,  $200\text{Hz}$ . Calculate  $I$ ,  $V_R$ ,  $V_C$ ,  $V_L$  and phase angle referred to supplied voltage.
- ( $2.02 \angle 26.89^\circ\text{A}$ ,  $66.7 \angle 26.89^\circ\text{V}$ ,  $126.9 \angle 116.89^\circ\text{V}$ ,  $150.7 \angle 60.11^\circ\text{V}$ )
19. A circuit with  $25\Omega$  resistance,  $0.2\text{H}$  inductance and  $1\mu\text{F}$  capacitance connected in series to AC  $100\text{V}$ ,  $50\text{Hz}$ . Calculate:
- Impedance,  $Z$ .
  - Current,  $I$
- ( $67.62 \angle 68.3^\circ\Omega$ ,  $1.47 \angle -68.3^\circ\text{A}$ )
20. Series RLC circuit with  $20\Omega$ ,  $0.1\text{H}$  and  $40\mu\text{F}$  respectively was connected to AC  $230\text{V}$ ,  $50\text{Hz}$ . Calculate:
- Impedance,  $Z$ .
  - Current,  $I$
  - Voltage drop at each component  $V_R$ ,  $V_C$  and  $V_L$
  - Power factor
  - Draw the vector diagram
- ( $52.14 \angle -67.44^\circ\Omega$ ,  $4.41 \angle 67.44^\circ\text{A}$ ,  $88.2 \angle 67.44^\circ\text{V}$ ,  $138.5 \angle 157.44^\circ\text{V}$ ,  $350.9 \angle -22.56^\circ\text{V}$ ,  $0.384$ )
21. A circuit with resistance  $50\Omega$ , inductance  $0.15\text{H}$  and capacitance  $100\mu\text{F}$  connected in series with AC  $100\text{V}$ ,  $50\text{Hz}$ . Calculate:
- Inductive reactance, capacitive reactance and impedance
  - Current
  - Voltage drop at each component  $V_R$ ,  $V_C$  and  $V_L$
- ( $94.24\Omega$ ,  $15.9\Omega$ ,  $92.9 \angle 57.43^\circ\Omega$ ,  $1.1 \angle -57.43^\circ\text{A}$ ,  $55 \angle -57.43^\circ\text{V}$ ,  $103.6 \angle 32.57^\circ\text{V}$ ,  $17.49 \angle -147.43^\circ\text{V}$ )
22. AC circuit  $200\text{V}$ ,  $50\text{Hz}$  connected in series with resistance  $40\Omega$ , inductive reactance  $20\Omega$  and capacitive reactance  $12\Omega$ . Calculate:
- Impedance,  $Z$ .
  - Current,  $I$

- iii. Voltage drop at each components  $V_R$ ,  $V_C$  and  $V_L$
  - iv. Phase angle
  - v. Power factor
  - vi. Faktor kuasa
  - vii. Draw the Vector diagram
- ( $40.79\angle 11.3^\circ\Omega$ ,  $4.9\angle -11.3^\circ\text{A}$ ,  $196\angle 11.3^\circ\text{V}$ ,  $98\angle 101.3^\circ\text{V}$ ,  $58.8\angle -78.7^\circ\text{V}$ )
23. The RLC series circuit connected to AC 250V, 50 Hz with reactance  $40\Omega$ , inductance 0.4H and capacitance  $150\mu\text{F}$ . Calculate:
- i. Impedance, Z.
  - ii. Current, I
  - iii. Voltage drop at each components  $V_R$ ,  $V_L$  and  $V_C$
  - iv. Phase angle
  - v. Power factor
  - vi. Apparent power
- ( $111.83\angle 69^\circ\Omega$ ,  $2.23\angle -69^\circ\text{A}$ ,  $89.2\angle 69^\circ\text{V}$ ,  $280.22\angle 159^\circ\text{V}$ ,  $47.32\angle -21^\circ\text{V}$ ,  $69^\circ$ , 0.358, 557.5VA)
24. Series RLC circuit with  $50\Omega$ , 10mH and  $100\mu\text{F}$ . Supplied with AC  $240\angle 30^\circ\text{V}$  50 Hz. Calculate:
- i. Impedance, Z.
  - ii. Current, I
  - iii. Voltage drop at each components  $V_R$ ,  $V_L$  and  $V_C$
  - iv. Power factor
- ( $57.64\angle -29.84^\circ\Omega$ ,  $4.16\angle 59.84^\circ\text{A}$ ,  $208.18\angle 59.84^\circ\text{V}$ ,  $13.06\angle 149.84^\circ\text{V}$ ,  $132.41\angle -30.16^\circ\text{V}$ , 0.867)