

# 3. Diodes and Diode Circuits

## 3.1 Diode Characteristics

### Small-Signal Diodes

**Diode:** a semiconductor device, which conduct the current in one direction only.


Two terminals: **anode** and **cathode**.

When the positive polarity is at the anode – the diode is **forward biased** and is conducting.


When the positive polarity is at the cathode – the diode is **reversed biased** and is not conducting.

If the reverse-biasing voltage is sufficiently large the diode is in **reverse-breakdown** region and large current flows through it.

**Breakdown voltage.**

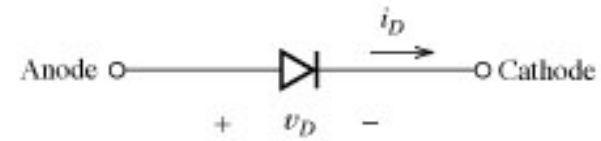


(a) Circuit symbol

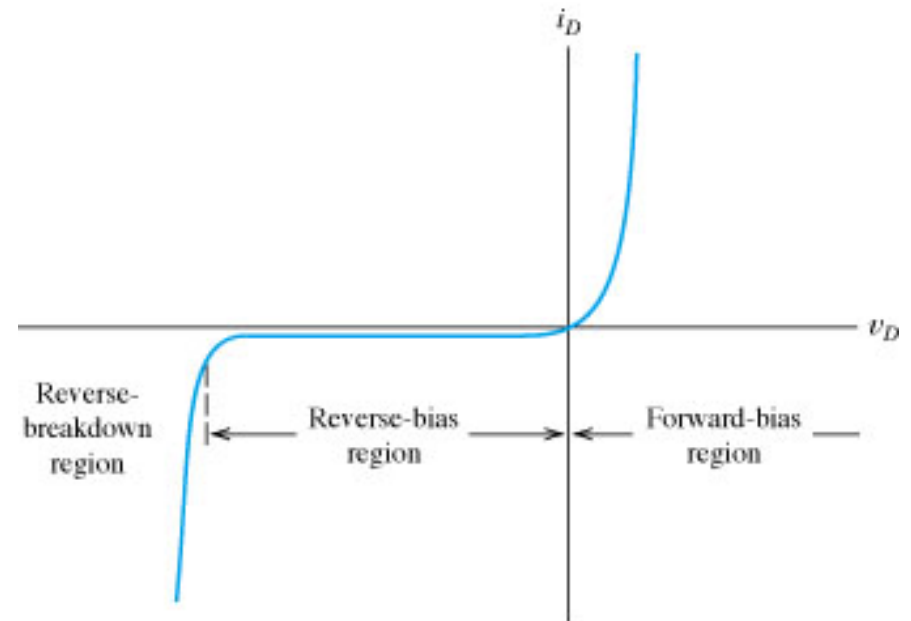

(b) Volt-ampere characteristic

Figure 3.1 Semiconductor diode.

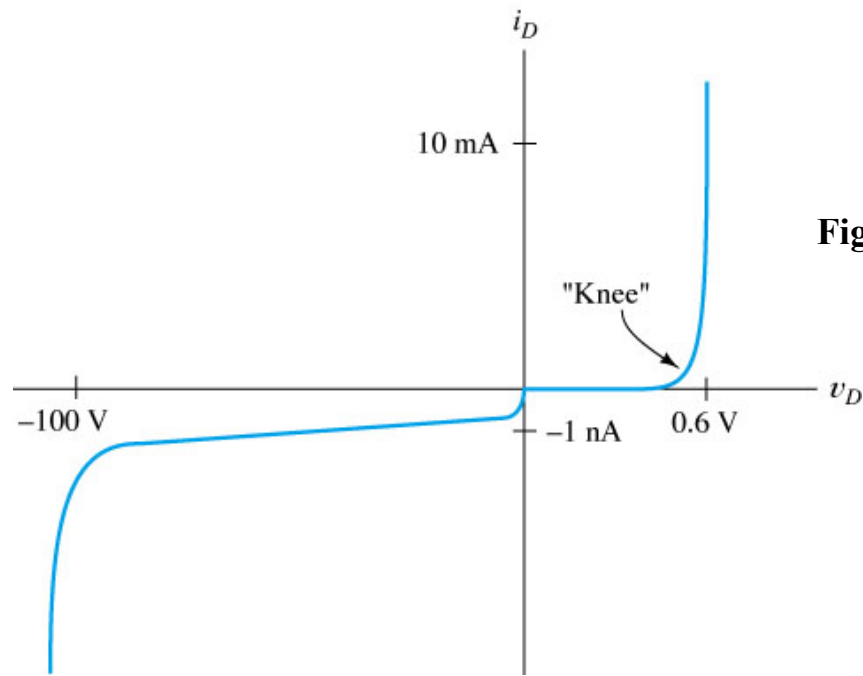

**Figure 3.2** Volt-ampere characteristic for a typical small-signal silicon diode at a temperature of 300 K. Notice the changes of scale.

Voltage drop across the diode when forward biased: **0.6-0.7V**.

The current through the diode when reversed biased: **~ 1nA** ( $10^{-9}A$ )

Temperature dependence:

- As the temperature increases, the voltage of the knee decreases by 2mV/K.
- The reverse current doubles for each 10K increase in the temperature.

## Zener Diodes

**Zener diodes:** diodes intended to operate in breakdown region.

If breakdown voltage  $> 6V$ :  
**avalanche** breakdown.

If breakdown voltage  $< 6V$ :  
**tunneling** mechanism of breakdown.



**Figure 3.3** Zener diode symbol.

### 3.3 The Ideal - Diode Model

#### Ideal diode:

- perfect conductor with zero voltage drop when the diode is forward biased;
- open circuit, when the diode is reversed biased.


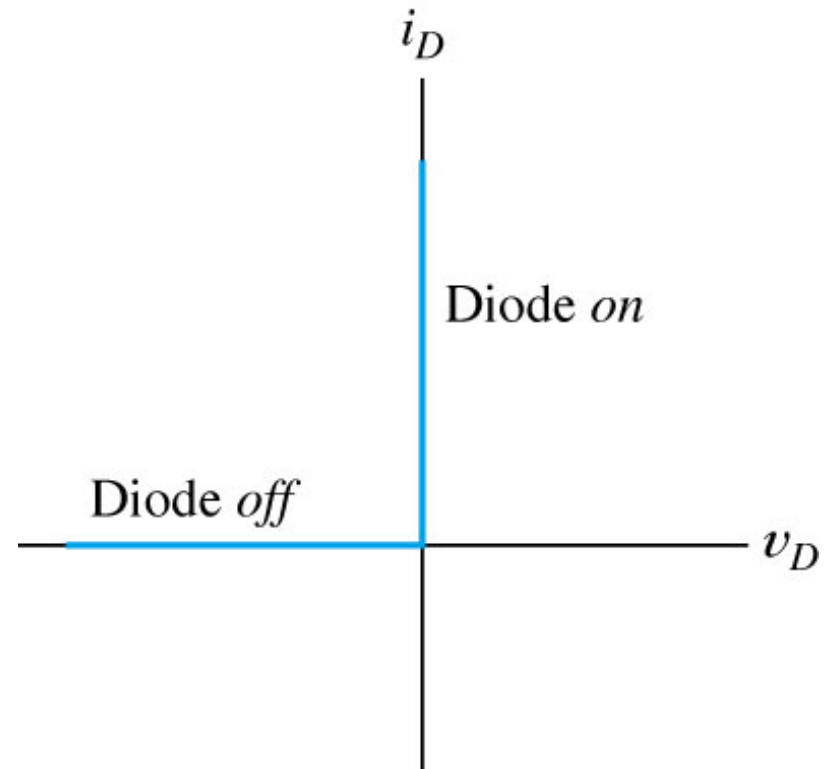


Figure 3.8 Ideal-diode volt-ampere characteristic.

## Assumed States for Analysis of Ideal - Diode Circuits

### Example 3.3 Circuit Solution By Assumed Diode States

Analyze the circuit illustrated in Figure 3.9a using the ideal - diode model.

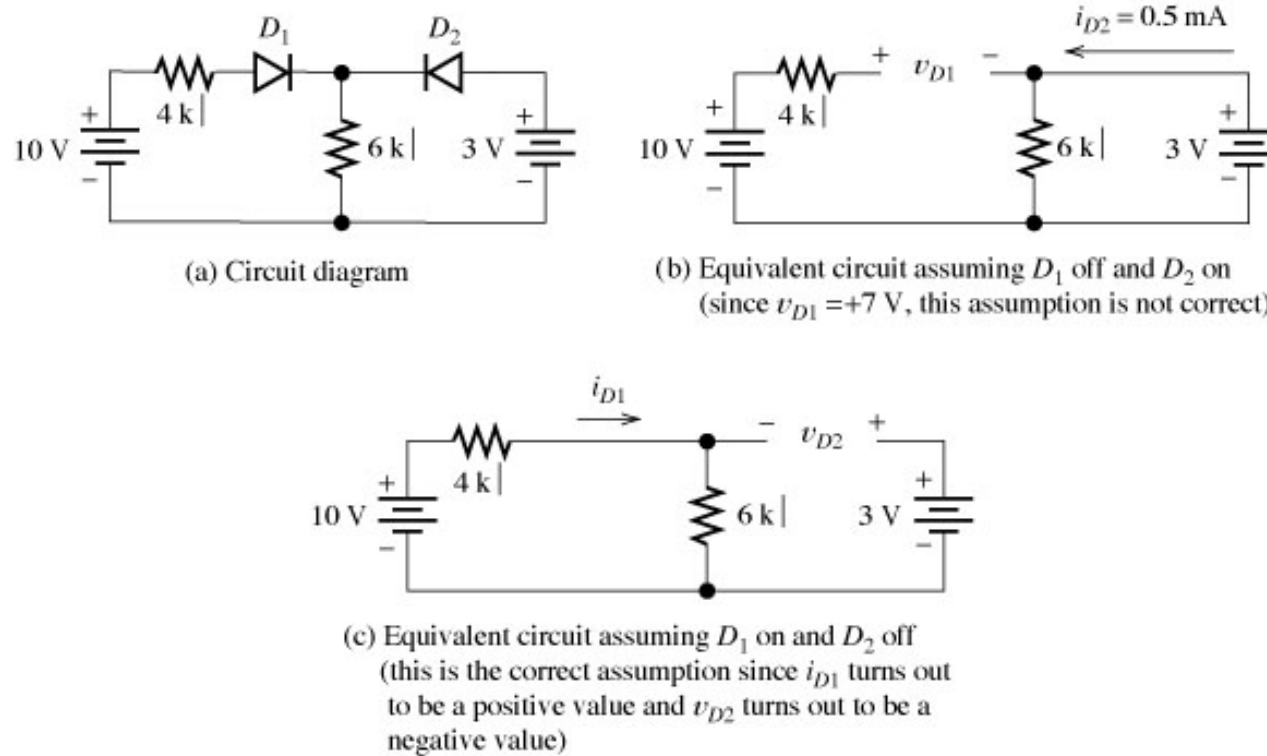

**Figure 3.9** Analysis of a diode circuit using the ideal-diode model.

### Solution

Step 1. We start by *assuming that  $D_1$  is off and  $D_2$  is on.*

Step 2. The equivalent circuit is shown in Figure 3.9b.  $i_{D2} = 0.5\text{ mA}$  and  $v_{D1} = 7\text{ V}$ .

Step 3. We have  $v_{D1} = +7\text{ V}$ , which is not consistent with our assumption.

### Another Assumption


Step 1. We assume that  *$D_1$  is on and  $D_2$  is off.*

Step 2. The equivalent circuit is shown in Figure 3.5c.  $i_{D1} = 1\text{ mA}$  and  $v_{D2} = -3\text{ V}$ .

Step 3. These conditions are consistent with the assumption.
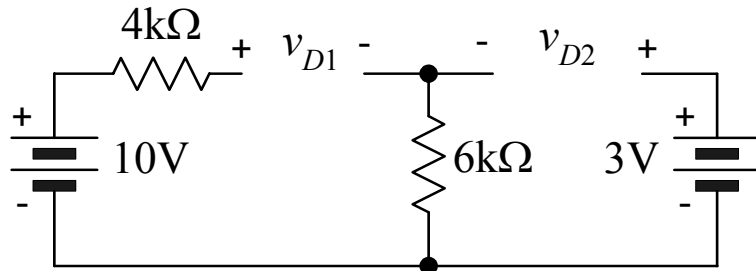
### Exercise 3.2

Show that the condition  $D_1$  off and  $D_2$  off is not valid for the circuit of the Figure 3.9a.



Equivalent circuit to Figure 3.9a when  $D_1$  is off and  $D_2$  is off.


### Solution

$$v_{D1} = 10\text{V}; v_{D2} = 3\text{V}.$$

The both diodes must be on since the voltages across them are positive.
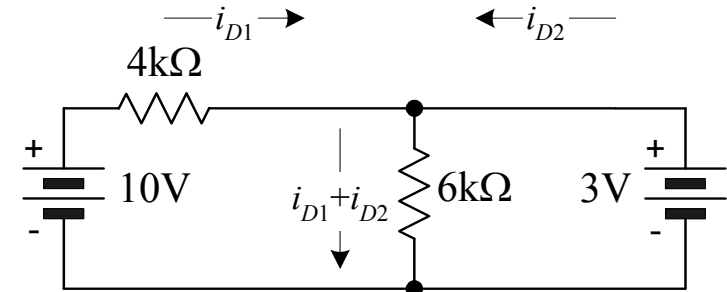
### Exercise 3.3

Show that the condition  $D_1$  on and  $D_2$  on is not valid for the circuit of the Figure 3.9a.



Equivalent circuit to Figure 3.9a when  $D_1$  is on and  $D_2$  is on.

### Solution

$$i_{D1} + i_{D2} = \frac{3\text{V}}{6\text{k}\Omega} = 0.5\text{mA}$$

$$i_{D1} = \frac{10\text{V} - 3\text{V}}{4\text{k}\Omega} = 1.75\text{mA}$$


$$i_{D2} = (i_{D1} + i_{D2}) - i_{D1} = 0.5 - 1.75 = -1.25\text{mA}$$

The negative sign of  $i_{D2}$  means that it flows in the opposite direction to the assumed, i.e. from the cathode to the anode of  $D_2$ . This is impossible.

## 3.4 Rectifier Circuits

**Rectifiers:** circuits, which convert ac power into dc power.

### Half - Wave Rectifier Circuits

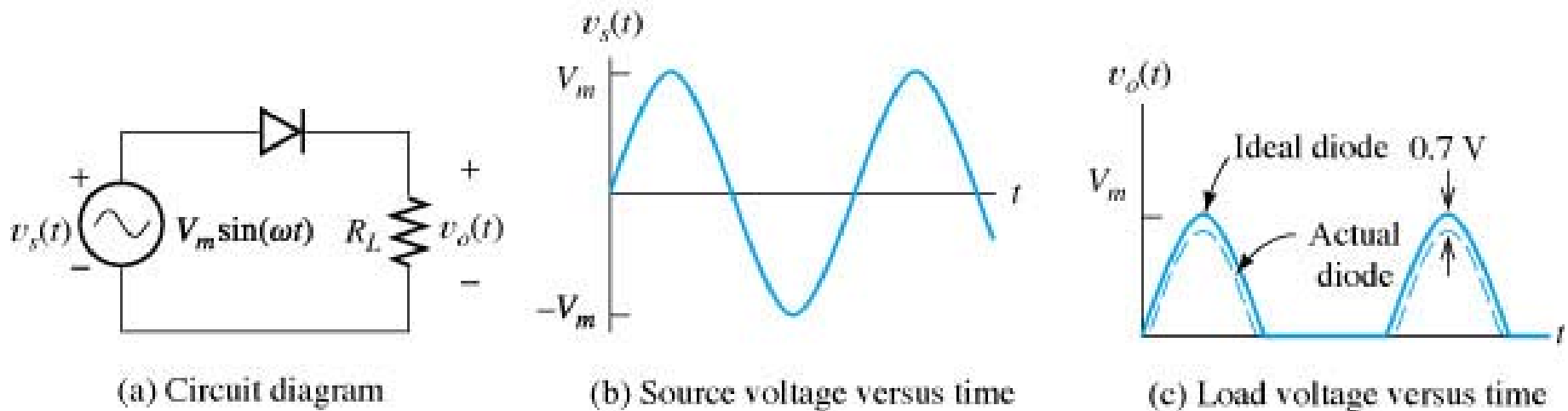

**Figure 3.11** Half-wave rectifier with resistive load.

# Half - Wave Rectifier with Smoothing Capacitor

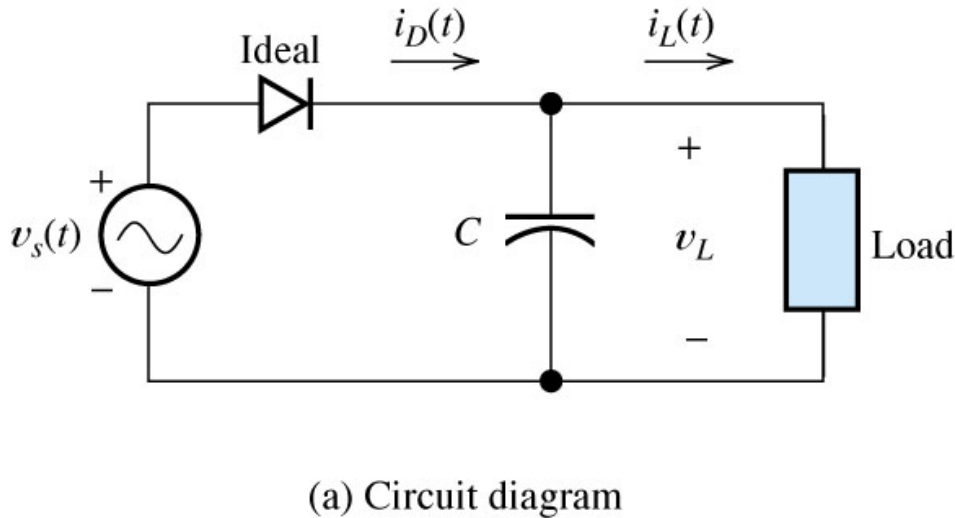


Figure 3.12a Half-wave rectifier with smoothing capacitor.

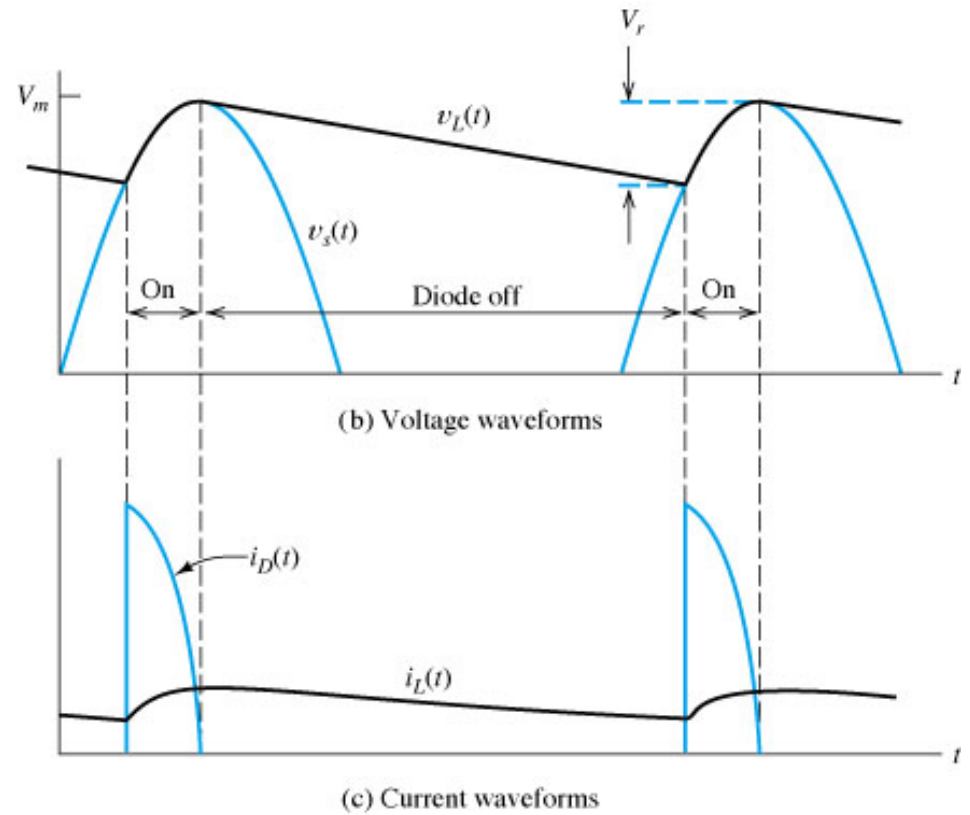


Figure 3.12b & c Half-wave rectifier with smoothing capacitor.

## Peak Inverse Voltage

**Peak inverse voltage (PIV)** across the diode: a parameter, which defines the choice of the diode.

For Figure 3.11  $PIV = V_m$ ;

For Figure 3.12  $PIV \approx 2V_m$ .



### Problem 3.24 Half-wave battery charger.

Consider the battery charging circuit in Figure P3.24 with  $V_m = 20\text{V}$ ,  $R = 10\Omega$  and  $V_B = 14\text{V}$ . Find the peak current assuming an ideal diode. Also, find the percentage of each cycle in which the diode is in on state. Sketch  $v_s(t)$  and  $i(t)$  to scale against time.

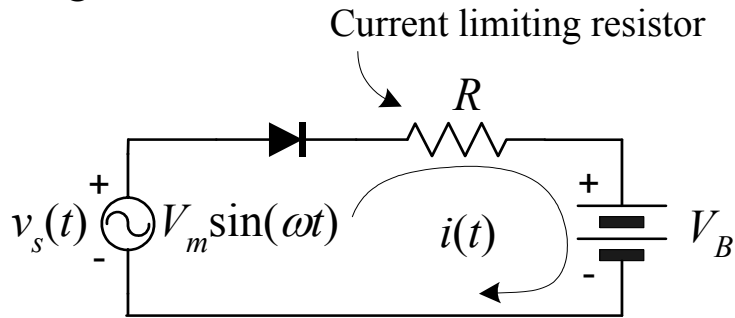


Figure P3.24 Half-wave battery charger.

### Solution:

The diode is on when

$$V_m \sin(\omega t) > V_B \quad \text{or} \quad 20 \sin(\omega t) > 14$$

The diode goes to on state at

$$20 \sin(\omega t) = 14$$


$$\omega t = \arcsin \frac{14}{20} = \arcsin 0.7 \approx 45^\circ; 135^\circ$$

The diode is on for  $45^\circ \leq \omega t \leq 135^\circ$  or for  $90^\circ$  of the phase angle. The whole period is  $360^\circ$ , so the diode is on for

$$\frac{90^\circ}{360^\circ} = 0.25 = 25\% \text{ of the time.}$$

The peak current is when the ac voltage is at the peak and is
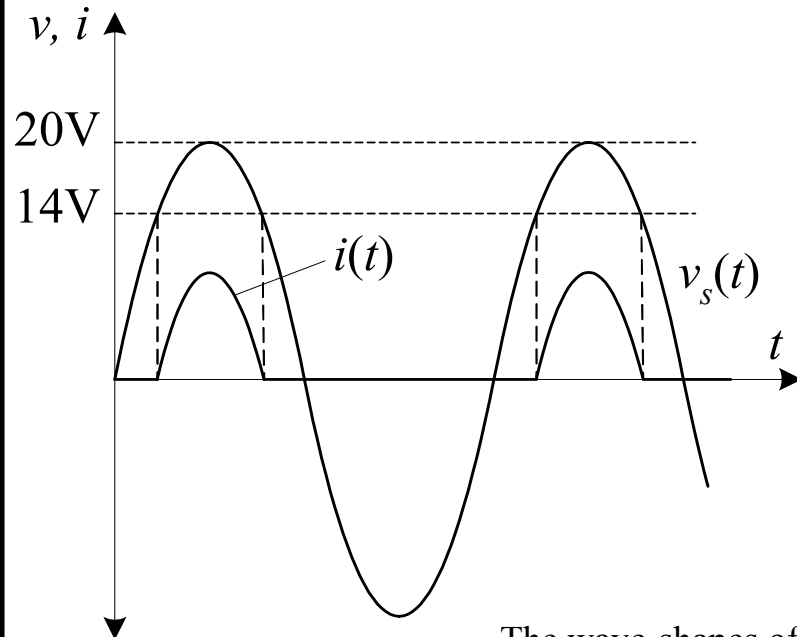
$$I_m = \frac{V_m - V_B}{R} = \frac{20 - 14}{10} = 0.6\text{A}$$



The wave-shapes of  $v_s(t)$  and  $i(t)$ .

# Full - Wave Rectifier Circuits

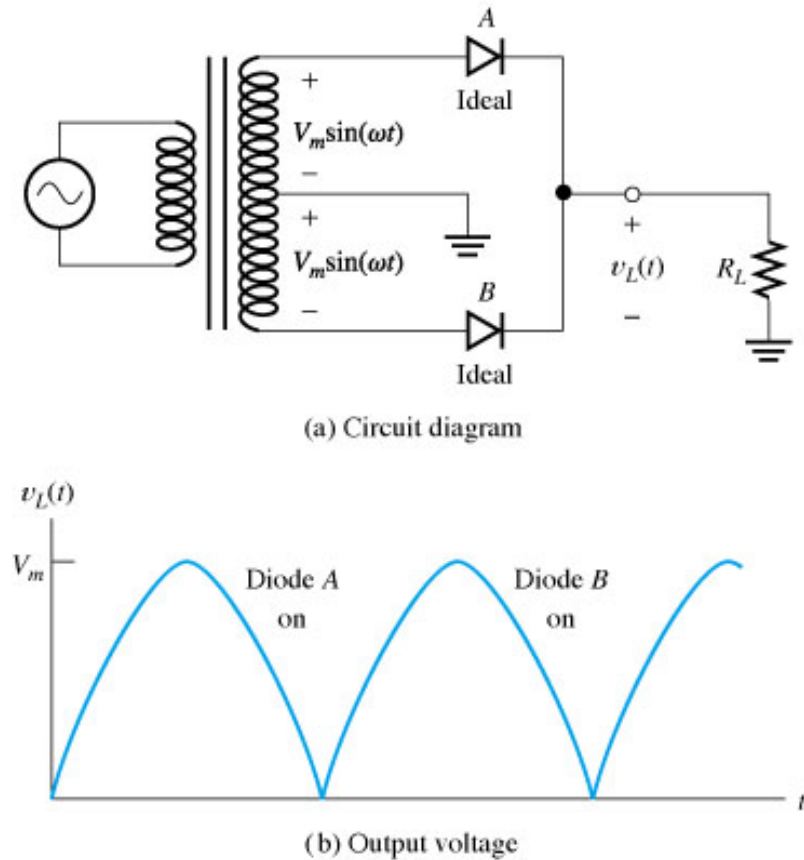


Figure 3.13 Full-wave rectifier.

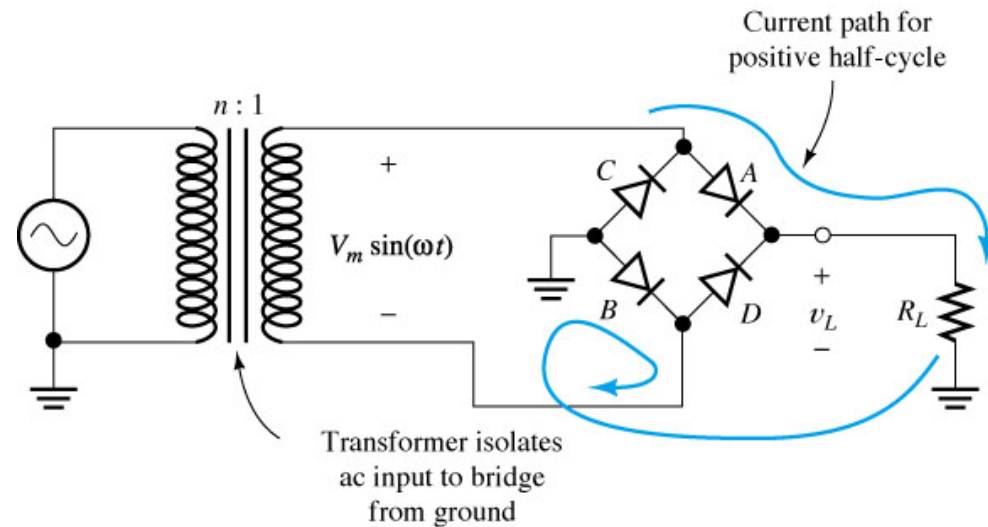
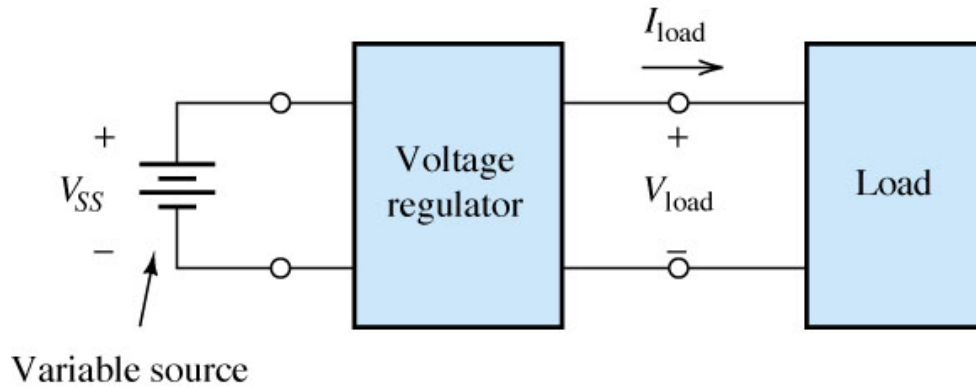



Figure 3.14 Diode-bridge full-wave rectifier.
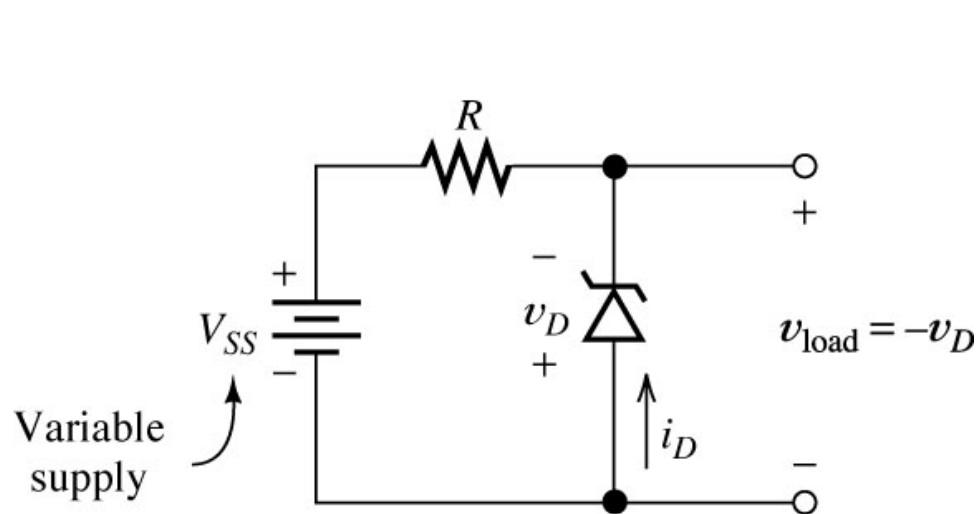
## 3.7 Voltage - Regulator Circuits

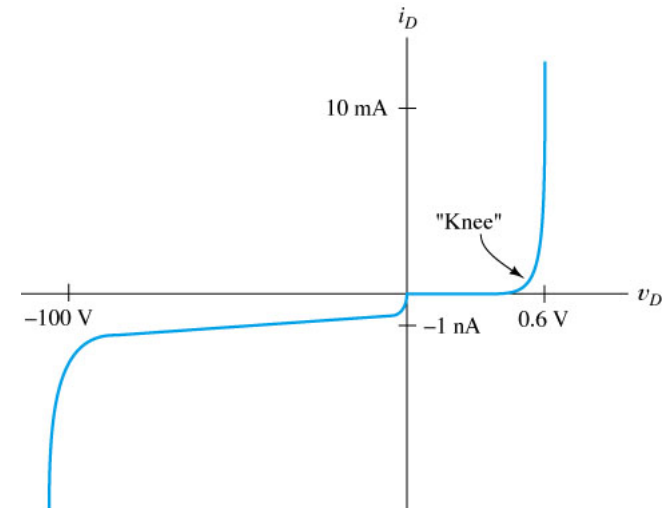


**Figure 3.24** A voltage regulator supplies constant voltage to a load.

### A Simple Zener-Diode Voltage Regulator



**Figure 3.25** A simple regulator circuit that provides a nearly constant output voltage from a variable supply voltage.



In the voltage regulator the zener-diode operates in the breakdown region, which ensures approximately constant voltage across it.

## 3.6 Linear Small - Signal Equivalent Circuits

### Dynamic Resistance

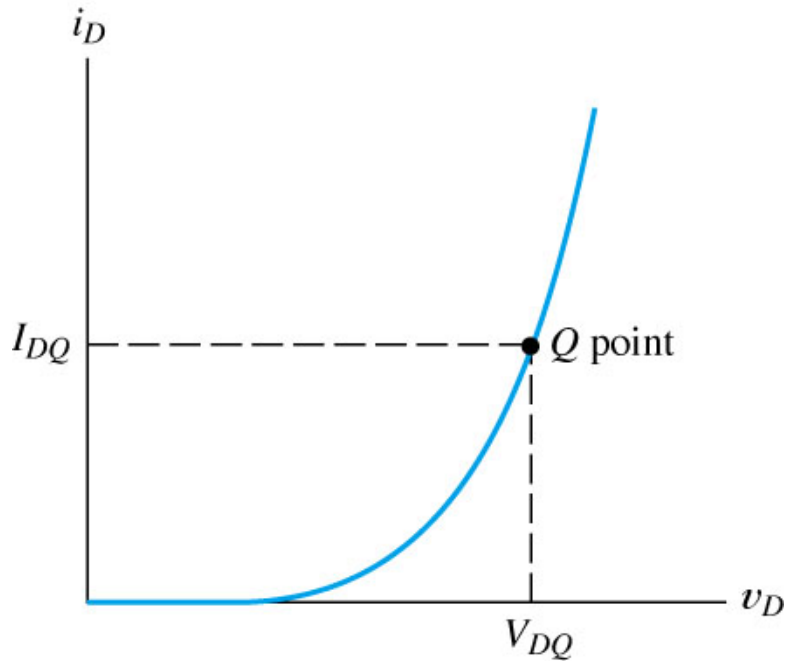


Figure 3.31 Diode characteristic, illustrating the  $Q$ -point.

$$\Delta i_D \cong \left( \frac{di_D}{dv_D} \right)_Q \Delta v_D \quad (3.11)$$

$$r_D \cong \left[ \left( \frac{di_D}{dv_D} \right)_Q \right]^{-1} \quad (3.12)$$

$$\Delta i_D \cong \frac{\Delta v_D}{r_D} \quad (3.13)$$

$$i_D = \frac{v_D}{r_D} \quad (3.14)$$

## The Shockley Equation

$$i_D = I_s \left[ \exp\left(\frac{v_D}{nV_T}\right) - 1 \right] \quad (3.15)$$

$I_s$  – **saturation current**. For small signal diodes at 300K:  $I_s \sim 10^{-14}$ A.

$n$  – **emission coefficient**;  $n = 1 \dots 2$  for small-signal diodes.

$V_T$  – thermal voltage:

$$V_T = \frac{kT}{q} \quad (3.16)$$

$T$  – absolute temperature in K;


$k = 1.38 \times 10^{-23}$ J/K – the Boltzmann's constant;

$q = 1.60 \times 10^{-19}$ C – the charge of the electron;

At  $T = 300$ K  $V_T \approx \mathbf{0.026V = 26mV}$

## 3.7 Basic Semiconductor Concepts


### Intrinsic Silicon

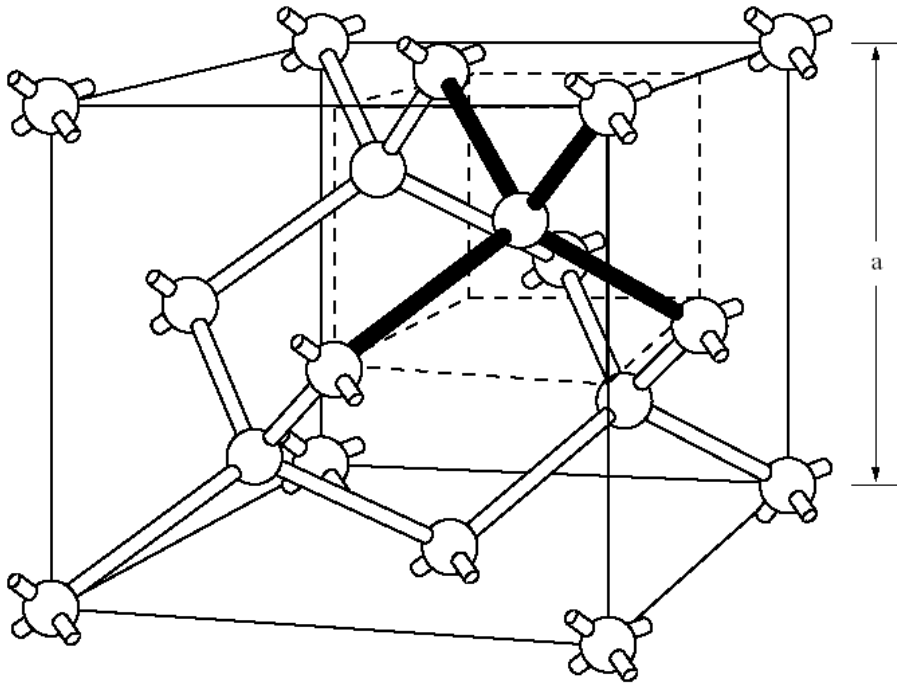


Crystalline lattice of intrinsic silicon in the space.

Bohr model of the silicon atom:

- 14 electrons surround the nucleus;
- Electron orbits grouped in shells
- Outermost orbit contains 4 electrons – **valence shell**;
- Atoms are arranged in crystalline lattice;
- Each pair of neighbor atoms in the lattice form a **covalent bond**;
- The covalent bond consists from two electrons that orbit around the both atoms. Each atom contributes one electron in the pair.
- At 0K temperature all valence electrons are in bound in the covalence bonds and the conductivity is 0.

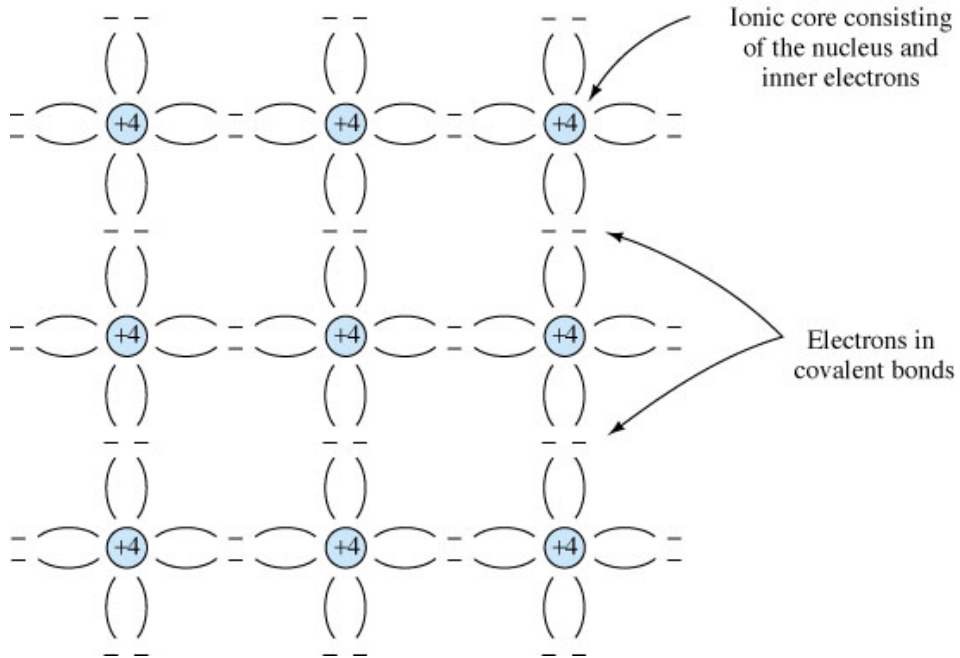

**Figure 3.36** Intrinsic silicon crystal (simplified picture in the plane).

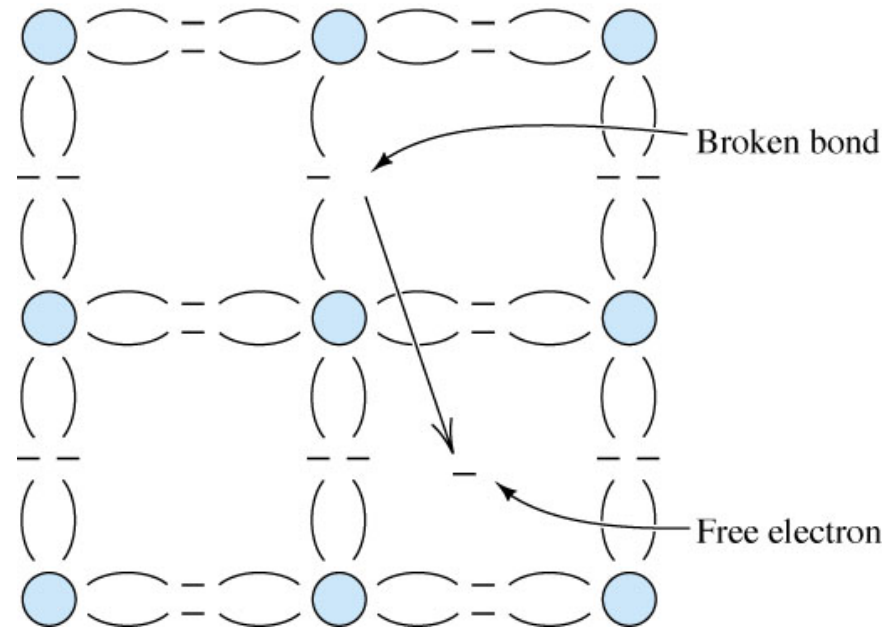


**Figure 3.37** Thermal energy can break a bond, creating a vacancy and a free electron, both of which can move freely through the crystal.

**Free electrons** appear at room temperature due to breaking of the covalent bonds. Only one per  $1.4 \times 10^{13}$  bonds is broken.

The concentration of the free electrons is small,  $n_i \approx 10^{14}$  free electrons per  $\text{cm}^3$ .

The conductivity is small: **semiconductor**.

## Conduction by Holes

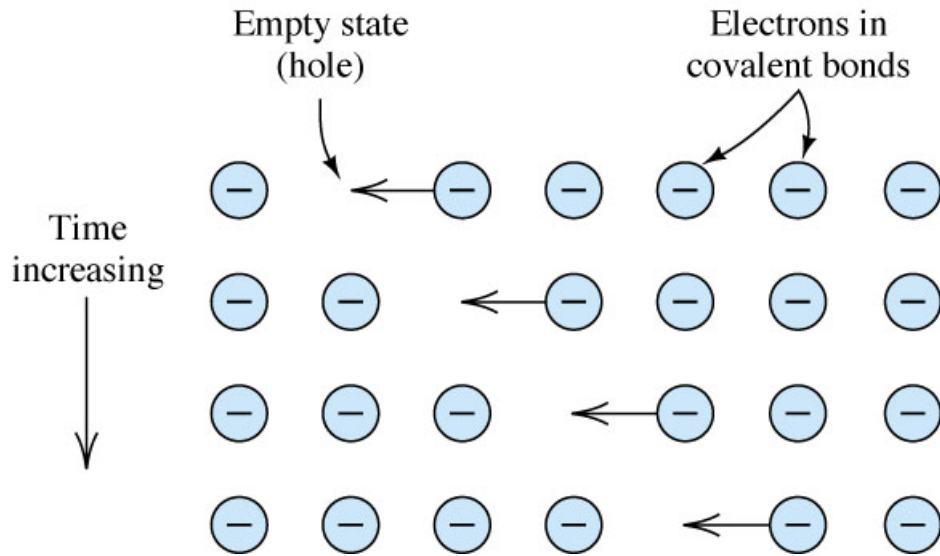

**Figure 3.38** As electrons move to the left to fill a hole, the hole moves to the right.

After breaking the bond the atom is positive charged and the vacancy of the electron is called **hole**.

In the intrinsic silicon the concentration of the electrons  $n_i$  is equal to the concentration of the holes  $p_i$ :

$$n_i = p_i \quad (3.24)$$

## Generation and Recombination

**Generation:** breaking the covalent bonds and appearing free electrons and holes.


**Recombination:** free electron encounters a hole.

At higher temperature the rate of the generation is higher.

When the temperature is constant, the generation and recombination are in equilibrium.



## *n* - Type Semiconductor Material

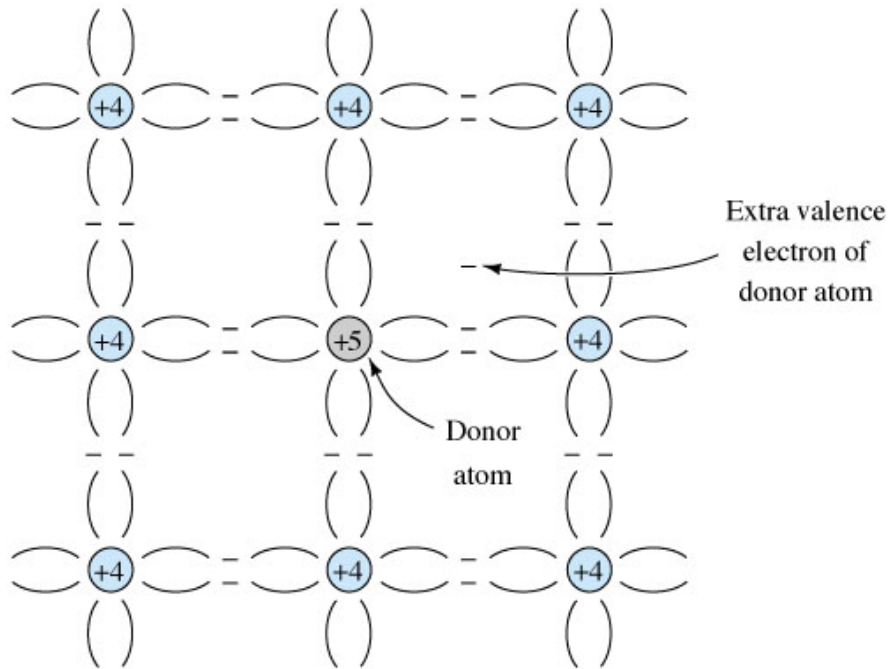

**Figure 3.39** *n*-type silicon is created by adding valence five impurity atoms.

**Extrinsic semiconductor:** silicon with small concentration of impurities, which change its conductivity.

**Donor atom:** atom of 5<sup>th</sup> valence. Example: phosphorus.

The extra valence electron of the phosphorus always is free electron.


$$n = p + N_D \quad (3.25)$$

***n*-type semiconductor:** semiconductor with 5<sup>th</sup> valence impurities and conductivity, based on the free electrons mostly.

**Majority carriers** in *n*-type silicon: *electrons*.

**Minority carriers** in *n*-type silicon: *holes*.

## *p* - Type Semiconductor Material

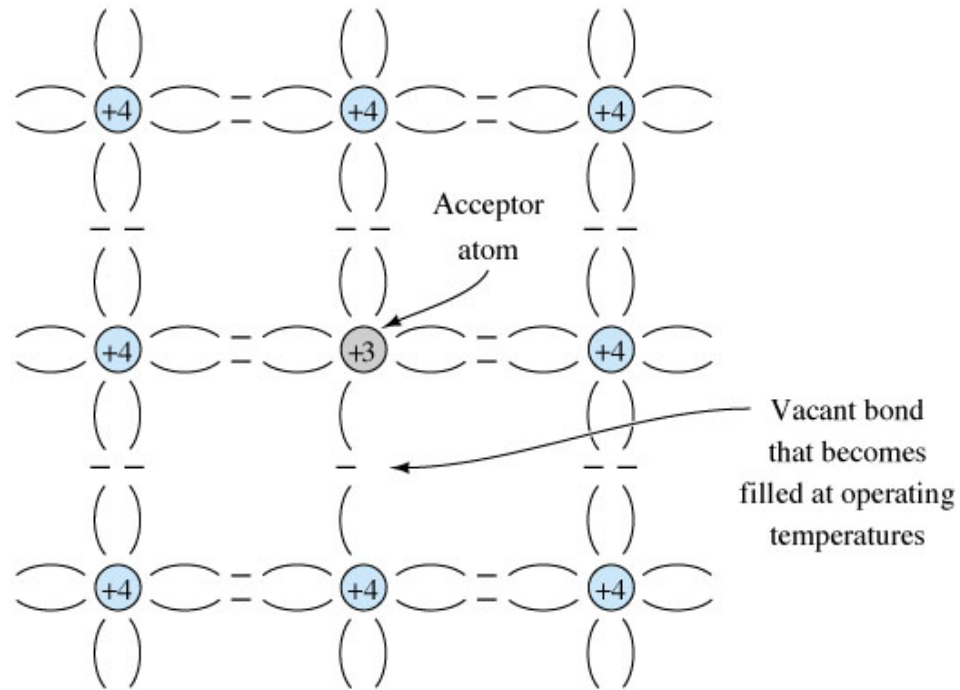

**Figure 3.40** *p*-type silicon is created by adding valence three impurity atoms.

**Acceptor:** atom of 3<sup>rd</sup> valence. Example: boron.

The acceptor atoms always accept an extra electron, creating negative ionized cores and shortage of free electrons.

$$N_A + n = p \quad (3.28)$$

***p*-type semiconductor:** semiconductor with 3<sup>rd</sup> valence impurities and conductivity, based on the holes mostly.

**Majority carriers** in *p*-type silicon: *holes*.

**Minority carriers** in *p*-type silicon: *electrons*.

### The Mass - Action Law

$$pn = p_i n_i \quad (3.26)$$

Since  $p_i = n_i$

$$pn = n_i^2 \quad (3.27)$$

## Cycling the type of the material

In fabricating the integrated circuits the impurities are added in stages, changing every time the type of the conductivity

$$p + N_D = n + N_A \quad (3.29)$$

## Drift

- The carriers move in random fashion in the crystal due to thermal agitation.
- If electric field is applied to the random motion is added a constant component.
- The averaged motion of the charge carriers due to the electric field: **drift**.
- Drift velocity is proportional to the electric field vector.

$$\mathbf{V}_n = -\mu_n \mathbf{E} \quad (3.30)$$

$$\mathbf{V}_p = \mu_p \mathbf{E} \quad (3.31)$$

$\mu_n$  is the mobility of the free electrons;  
 $\mu_p$  is the mobility of the holes.


$$\mu_p < \mu_n$$

## Diffusion



If there is a difference in the concentration of the charges in the crystal, appears a flow of charges toward the region with small concentration, determining **diffusion current**.

## 3.8 Physics of the Junction Diode

### The Unbiased $pn$ Junction

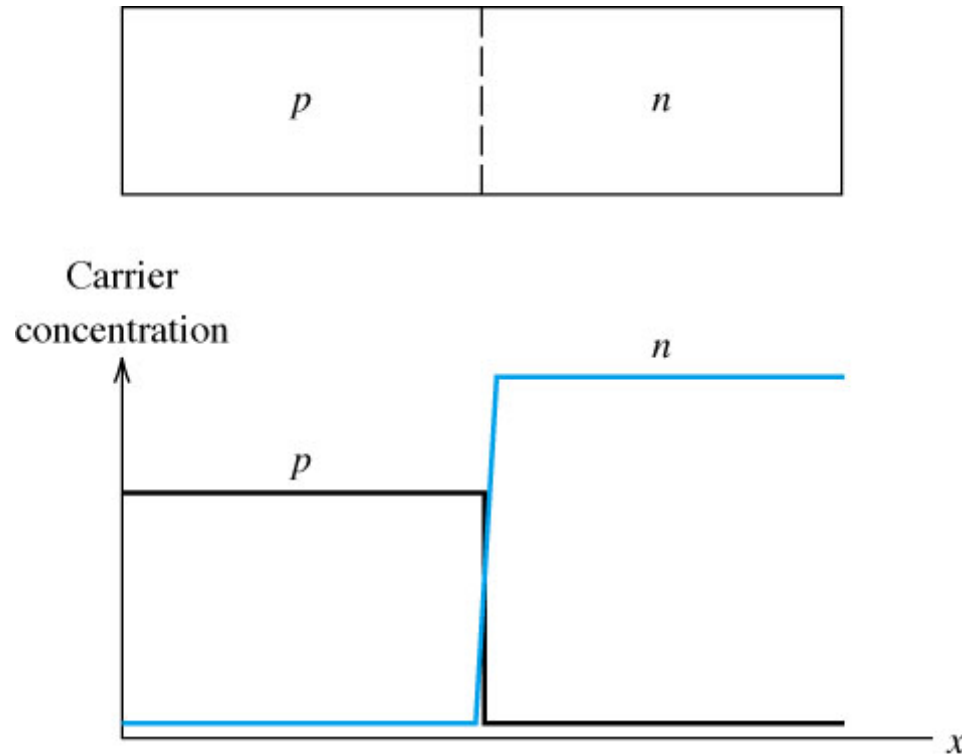


**Figure 3.42** If a  $pn$  junction could be formed by joining a  $p$ -type crystal to an  $n$ -type crystal, a sharp gradient of hole concentration and electron concentration would exist at the junction immediately after joining the crystals.

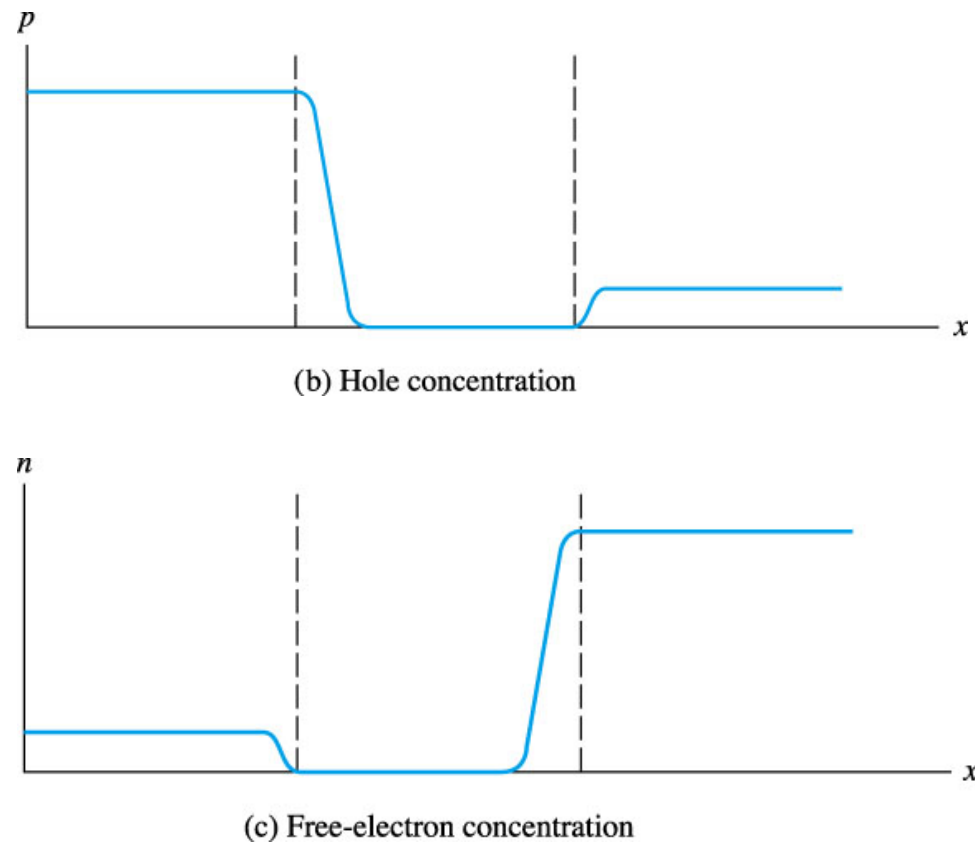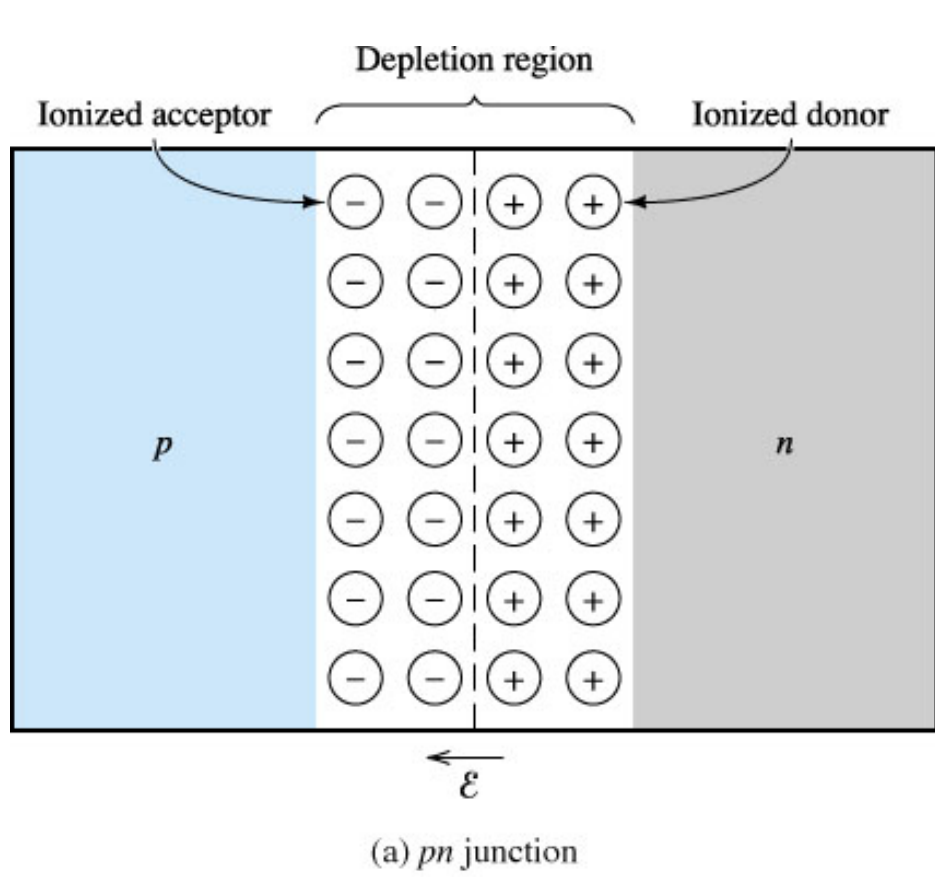

**Figure 3.43** Diffusion of majority carriers into the opposite sides causes a **depletion region** to appear at the junction.

The field of depletion region prevents the flow of majority carriers.  
 A **built-in barrier potential** exists for them due to depletion region.

## The $pn$ Junction with Reverse Bias

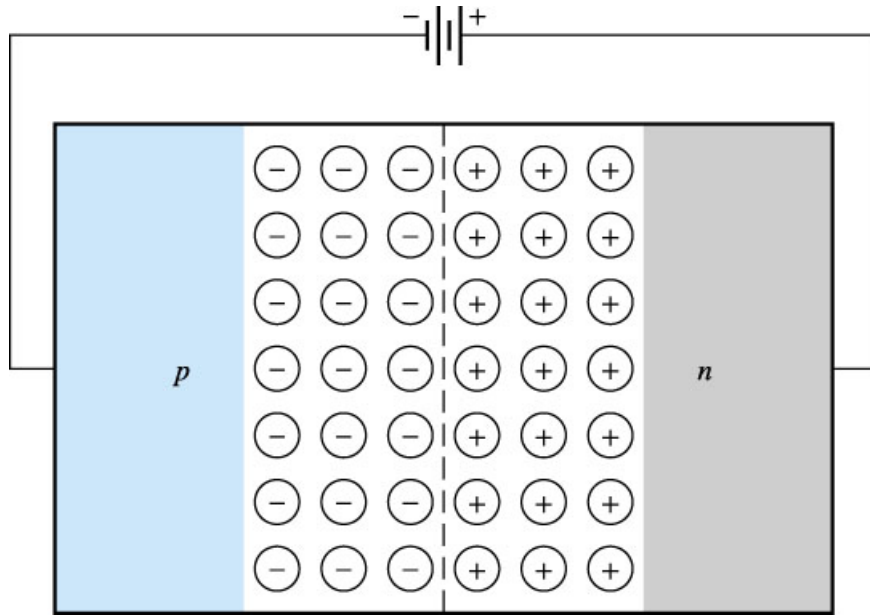

**Figure 3.44** Under reverse bias, the depletion region becomes wider.


**Reverse bias:** when the external voltage has the same polarity as the field of the depletion region.

Reversed biasing extends the depletion region and fully stops the current through the diode.

## The $pn$ Junction with Forward Bias

**Forward bias:** when the external voltage has opposite polarity to the field of the depletion region.

Forward biasing narrows the depletion region and reduces the barrier potential. When the barrier potential is reduced to 0, a significant current flows through the diode.

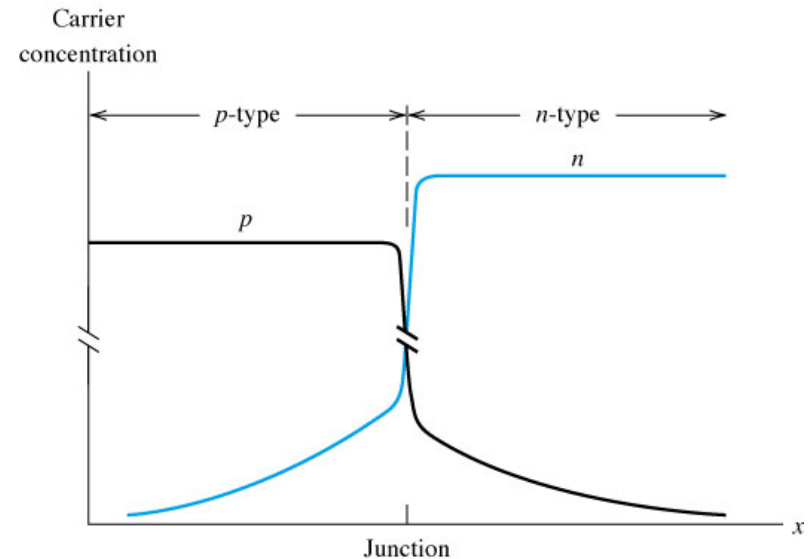

**Figure 3.45** Carrier concentration versus distance for a forward biased  $pn$  junction.

# 3.9 Switching and High - Frequency Behavior

## Review of Capacitance


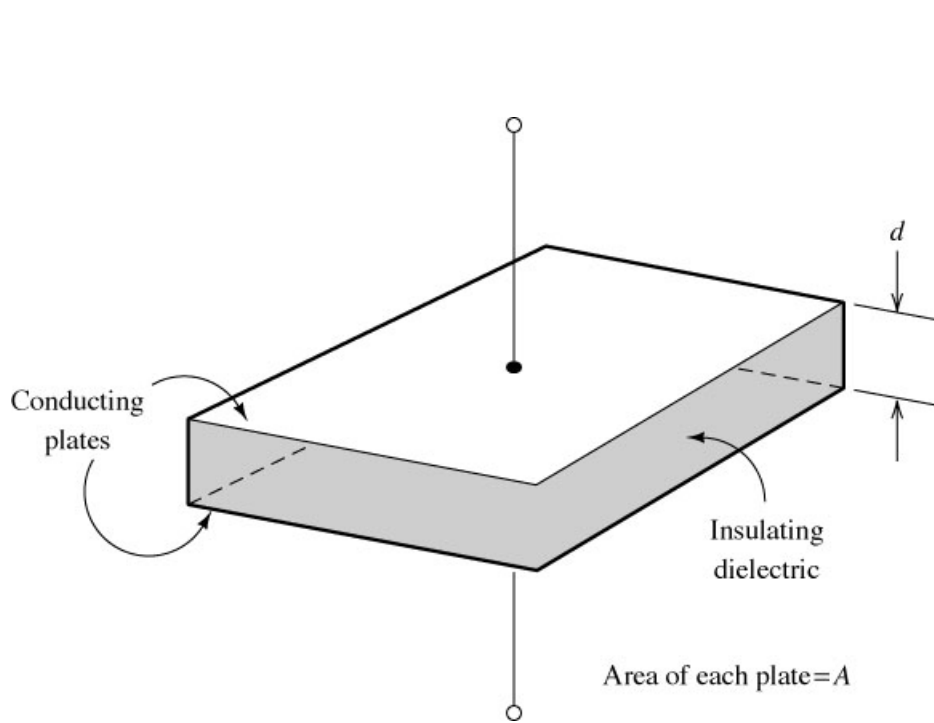


Figure 3.46 Parallel-plate capacitor.

$$Q = CV \quad (3.33)$$

$$C = \frac{\epsilon A}{d} \quad (3.34)$$


## Depletion Capacitance

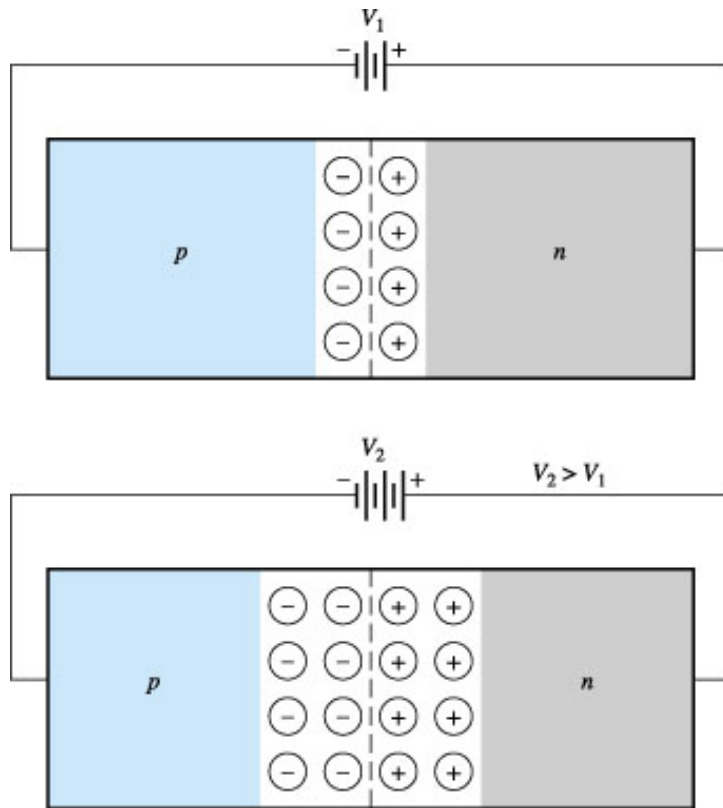

**Figure 3.46** As the reverse bias voltage becomes greater, the charge stored in the depletion region increases.

$$C = \left| \frac{dQ}{dv_D} \right| \quad (3.36)$$


$$C = \frac{C_{j0}}{\left[ 1 - (V_{DQ} / \phi_0) \right]^m} \quad (3.37)$$

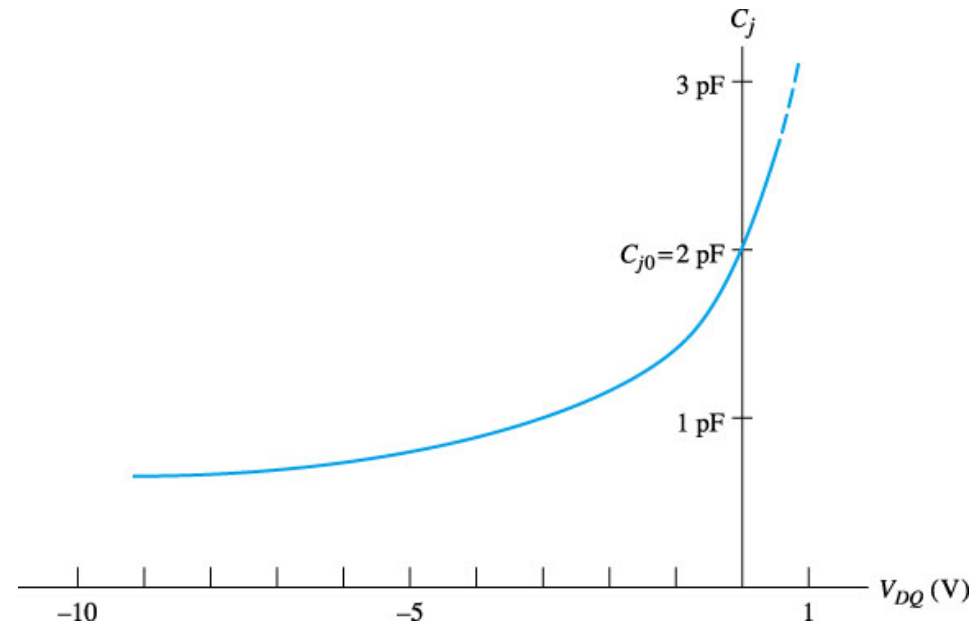

**Figure 3.48** Depletion capacitance versus bias voltage for the 1N4148 diode.




# Diffusion Capacitance

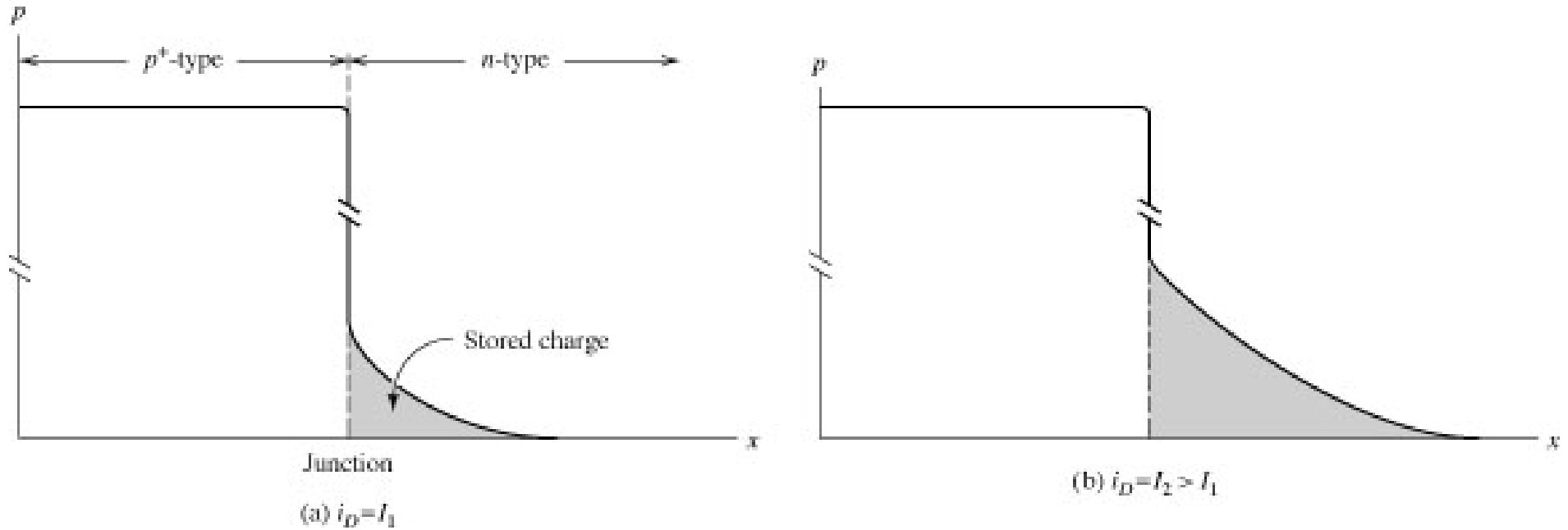

**Figure 3.49** Hole concentration versus distance for two values of forward current.


$$C_{dif} = \frac{\tau_T I_{DQ}}{V_T} \quad (3.38)$$

## Complete Small - Signal Diode Model

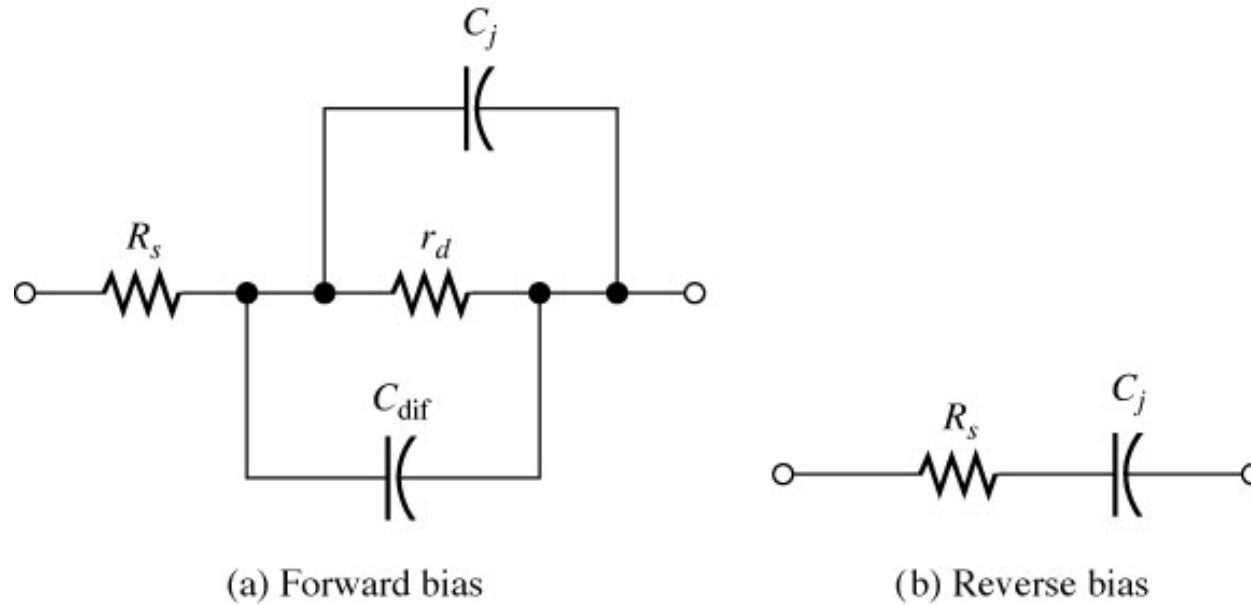

**Figure 3.50** Small-signal linear circuits for the  $pn$ -junction diode.

# Large - Signal Switching Behavior

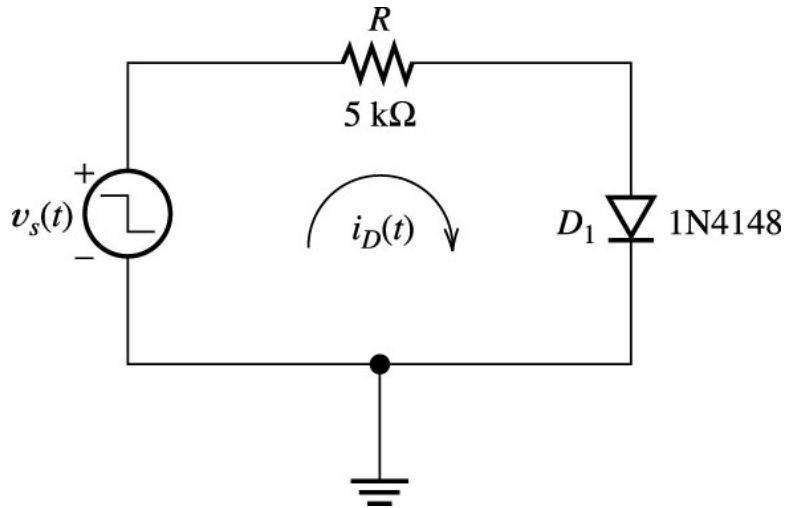


**Figure 3.51** Circuit illustrating switching behavior of a  $pn$ -junction diode.

$t_s$  – **storage interval;**


$t_t$  – **transition time;**

$t_{rr}$  – **reverse recovery time:** total time in which the diode is open after switching

$$t_{rr} = t_s + t_t \quad (3.40)$$

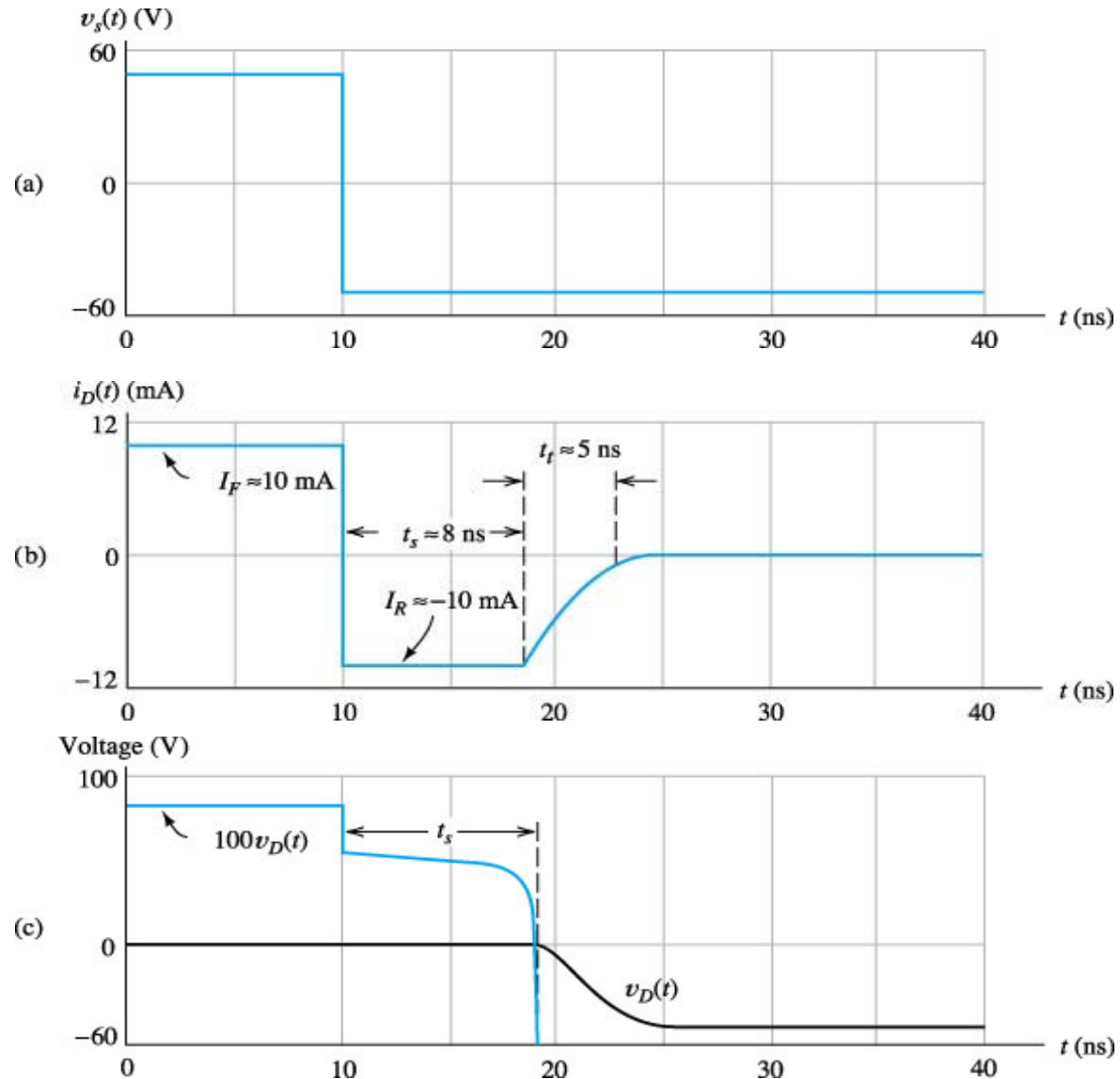

**Figure 3.52** Waveforms for the circuit of Figure 3.51.

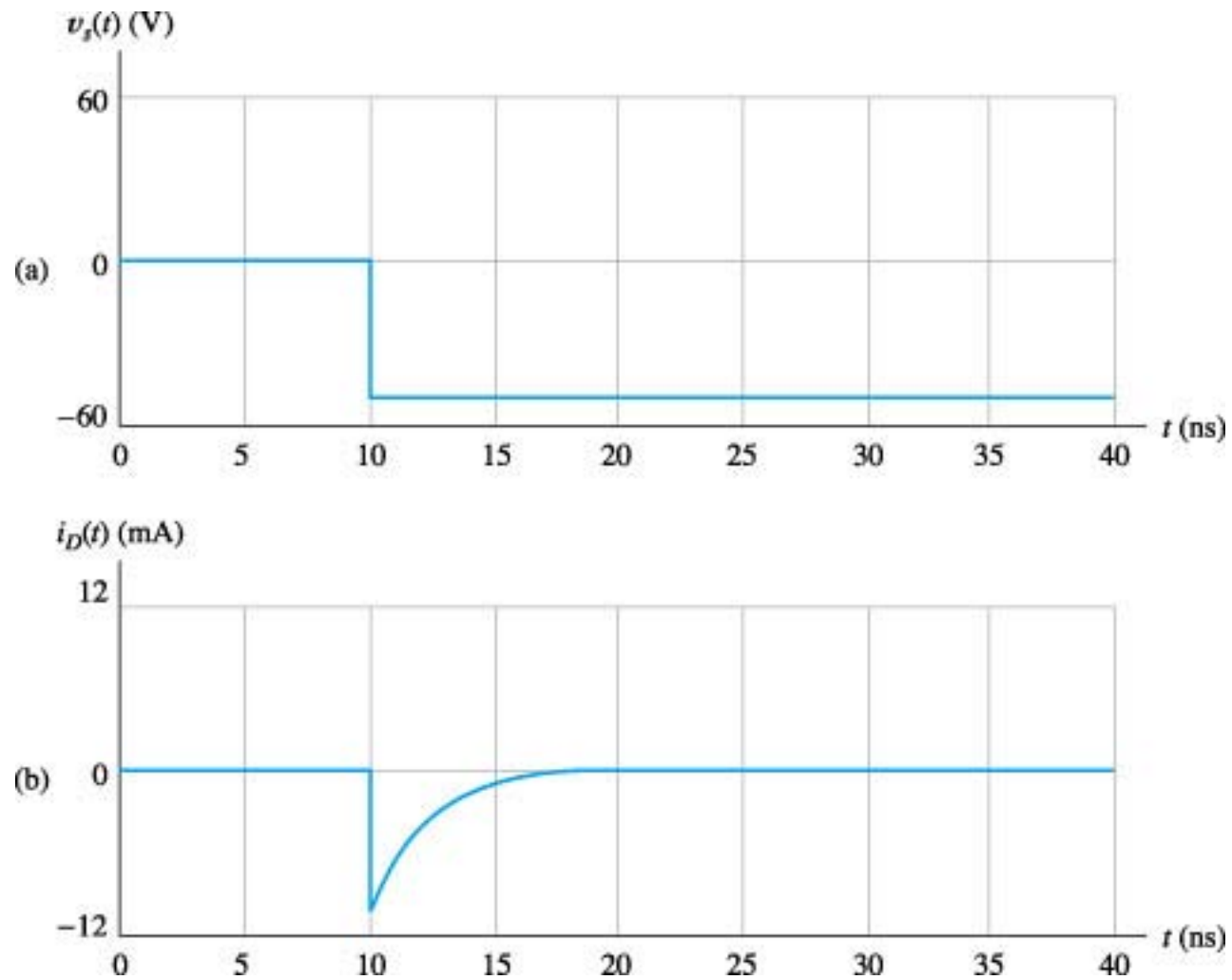

**Figure 3.53** Another set of waveforms for the circuit of Figure 3.51. Notice the absence of a storage interval.