



**Philadelphia University**  
**Faculty of Engineering**  
*Communication and Electronics Engineering*

## Amplifier Circuits-II

### BJT and FET Frequency Response Characteristics:

#### - *Logarithms and Decibels:*

- Logarithms taken to the base 10 are referred to as *common logarithms*, while logarithms taken to the base  $e$  are referred to as *natural logarithms*. In summary:

$$\text{Common logarithm: } x = \log_{10} a$$

$$\text{Natural logarithm: } y = \log_e a$$

The two are related by

$$\log_e a = 2.3 \log_{10} a$$

- Some relationships hold true for logarithms to any base

$$\log_{10} 1 = 0$$

$$\log_{10} \frac{a}{b} = \log_{10} a - \log_{10} b$$

$$\log_{10} \frac{1}{b} = -\log_{10} b$$

$$\log_{10} ab = \log_{10} a + \log_{10} b$$

- The background surrounding the term *decibel* (dB) has its origin in the established fact that power and audio levels are related on a logarithmic basis.
- That is, an increase in power level, say 4 to 16 W, does not result in an audio level increase by a factor of  $16/4 = 4$ . It will increase by a factor of 2 as derived from the power of 4 in the following manner:  $(4)^2 = 16$ .
- The term *bel* was derived from the surname of Alexander Graham Bell. For standardization, the bel (B) was defined by the following equation to relate power levels  $P_1$  and  $P_2$ :

$$G = \log_{10} \frac{P_2}{P_1} \quad \text{bel}$$

- It was found, however, that the bel was too large a unit of measurement for practical purposes, so the decibel (dB) was defined such that 10 decibels=1 bel. Therefore,

$$G_{\text{dB}} = 10 \log_{10} \frac{P_2}{P_1} \quad \text{dB}$$

- There exists a second equation for decibels that is applied frequently. It can be best described through the system with  $R_i$ , as an input resistance.

$$G_{\text{dB}} = 10 \log_{10} \frac{P_2}{P_1} = 10 \log_{10} \frac{V_2^2/R_i}{V_1^2/R_i} = 10 \log_{10} \left( \frac{V_2}{V_1} \right)^2$$

and

$$G_{\text{dB}} = 20 \log_{10} \frac{V_2}{V_1} \quad \text{dB}$$

- One of the advantages of the logarithmic relationship is the manner in which it can be applied to cascaded stages. In words, the equation states that the decibel gain of a cascaded system is simply the sum of the decibel gains of each stage.



### - **General Frequency Considerations:**

- The frequency of the applied signal can have a pronounced effect on the response of a single-stage or multistage network. The analysis thus far has been for the midfrequency spectrum.
- At low frequencies, we shall find that the coupling and bypass capacitors can no longer be replaced by the short-circuit approximation because of the increase in reactance of these elements.
- The frequency-dependent parameters of the small-signal equivalent circuits and the stray capacitive elements associated with the active device and the network will limit the high-frequency response of the system.
- An increase in the number of stages of a cascaded system will also limit both the high- and low-frequency responses.
- For any system, there is a band of frequencies in which the magnitude of the gain is either equal or relatively close to the midband value.
- To fix the frequency boundaries of relatively high gain,  $0.707A_{\text{vmid}}$  was chosen to be the gain at the cutoff levels. The corresponding frequencies  $f_1$  and  $f_2$  are generally called the *corner*, *cutoff*, *band*, *break*, or *half-power frequencies*. The multiplier 0.707 was chosen because at this level the output power is half the midband power output, that is, at midfrequencies.

- The bandwidth (or passband) of each system is determined by  $f_1$  and  $f_2$ , that is,

$$\text{bandwidth (BW)} = f_2 - f_1$$


- For applications of a communications nature (audio, video), a decibel plot of the voltage gain versus frequency is more useful.
- Before obtaining the logarithmic plot, however, the curve is generally normalized as shown in Fig. 9.6. In this figure, the gain at each frequency is divided by the midband value. Obviously, the midband value is then 1 as indicated. At the half-power frequencies, the resulting level is  $0.707 = 1/\sqrt{2}$ .

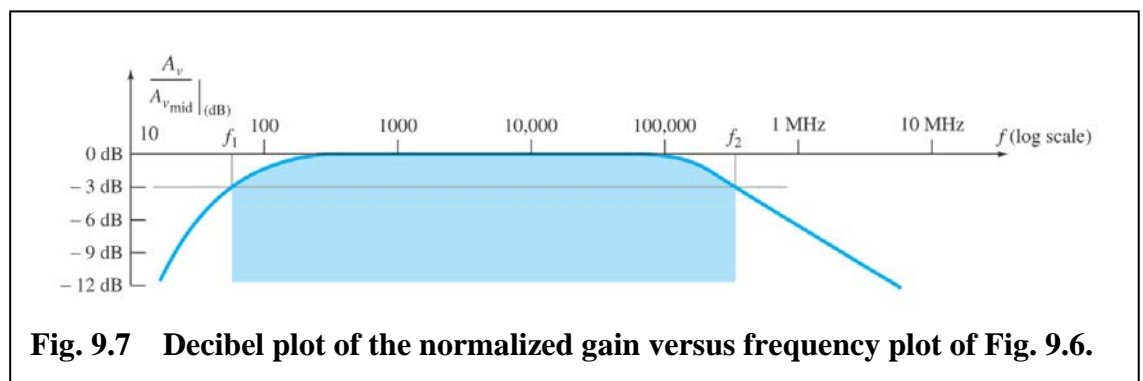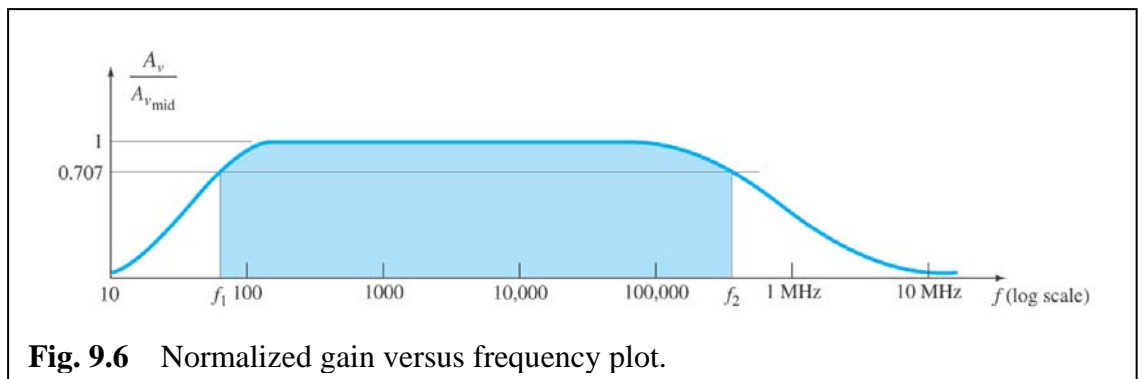

- *Low Frequency Analysis:*

- In the low-frequency region of the single-stage amplifier, it is the *R-C* combinations formed by the network capacitors  $C_c$ ,  $C_E$ , and  $C_s$  and the network resistive parameters that determine the cutoff frequencies.

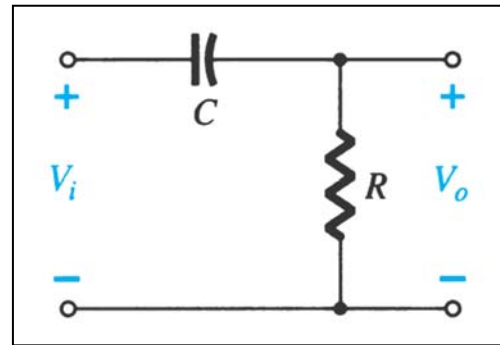- The analysis, therefore, will begin with the series *R-C* combination of the given Fig. and the development of a procedure that will result in a plot of the frequency response with a minimum of time and effort.



- 1) At very high frequencies,

$$X_C = \frac{1}{2\pi fC} \cong 0 \Omega$$


A short-circuit equivalent can be substituted for the capacitor. The result is that  $V_o = V_i$  at high frequencies.

- 2) At  $f = 0$  Hz,

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(0)C} = \infty \Omega$$

An open-circuit approximation can be applied, with the result that  $V_o = 0$  V.

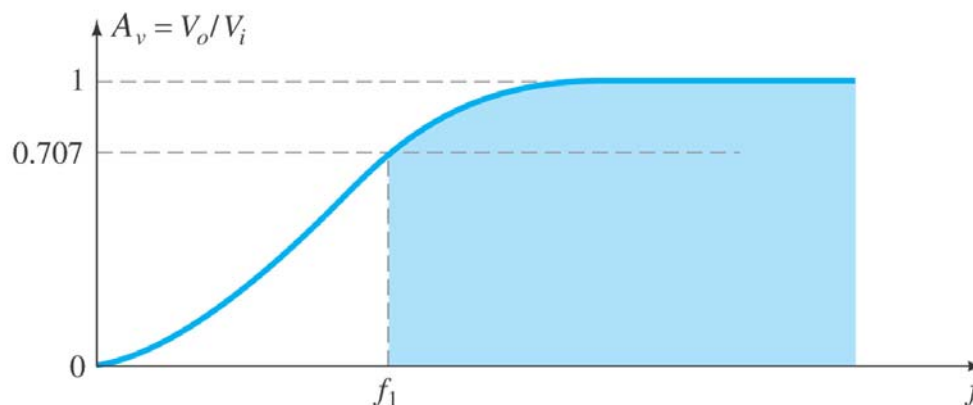- 3) Between the two extremes, the ratio  $A_v = V_o/V_i$  will vary as shown below. As the frequency increases, the capacitive reactance decreases and more of the input voltage appears across the output terminals.



- The output and input voltages are related by the voltage-divider rule in the following manner:

$$V_o = \frac{R V_i}{R + X_C}$$

- The magnitude of  $V_o$  determined by

$$V_o = \frac{R V_i}{\sqrt{R^2 + X_C^2}}$$

- For the special case where  $X_C = R$ ,

$$V_o = \frac{R V_i}{\sqrt{R^2 + X_C^2}} = \frac{R V_i}{\sqrt{R^2 + R^2}} = \frac{1}{\sqrt{2}} V_i$$

$$\Rightarrow |A_v| = \frac{V_o}{V_i} = \frac{1}{\sqrt{2}} = 0.707 = -3dB$$

- The frequency of which  $X_C = R$  (**the output will be 70.7% of the input**) is determined as:

$$X_C = \frac{1}{2\pi f_1 C} = R \Rightarrow f_1 = \frac{1}{2\pi CR}$$

$$A_v = \frac{R}{R - jX_C} = \frac{1}{1 - j\left(\frac{X_C}{R}\right)} = \frac{1}{1 - j\left(\frac{1}{\omega CR}\right)} = \frac{1}{1 - j\left(\frac{1}{2\pi f CR}\right)}$$

$$\Rightarrow A_v = \frac{1}{1 - j\left(\frac{f_1}{f}\right)} = \frac{1}{\underbrace{\sqrt{1 + \left(\frac{f_1}{f}\right)^2}}_{\text{magnitude of } A_v}} \angle \underbrace{\tan^{-1}(f_1/f)}_{\text{phase by which } V_o \text{ leads } V_i} = -10 \log \left[ 1 + \left(\frac{f_1}{f}\right)^2 \right] dB$$

- For frequencies where  $f \ll f_1$  or  $(f_1/f)^2 \gg 1$ , the equation above can be approximated as

$$A_v = -10 \log \left[ \left(\frac{f_1}{f}\right)^2 \right] dB = -20 \log \left(\frac{f_1}{f}\right) dB$$


- Ignoring the previous condition for a moment, a plot on a frequency log scale will yield a result of a very useful nature for future decibel plots.

At  $f = f_1 \Rightarrow -20\log(1) = 0dB$

At  $f = \frac{f_1}{2} \Rightarrow -20\log(2) \cong -6dB$

At  $f = \frac{f_1}{4} \Rightarrow -20\log(4) \cong -12dB$

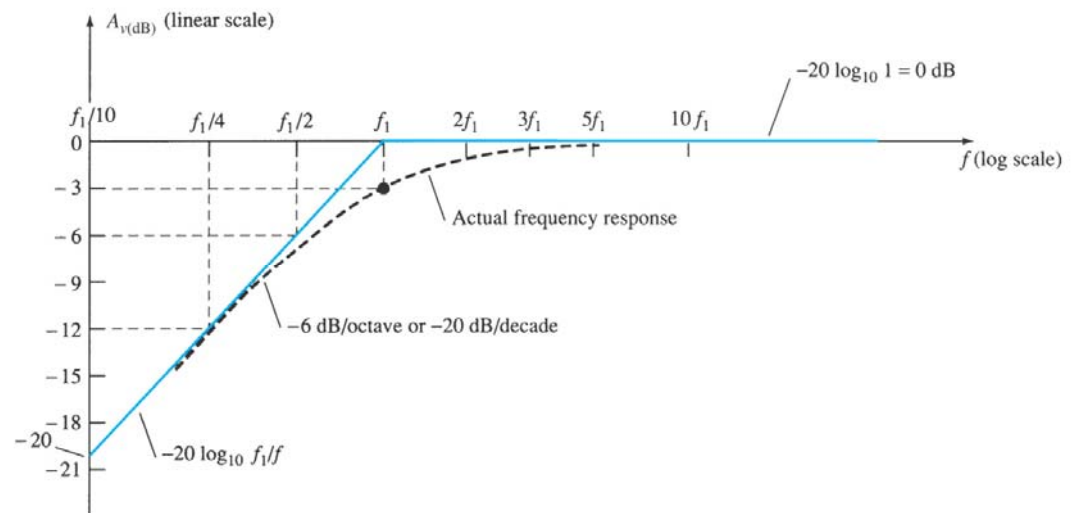At  $f = \frac{f_1}{10} \Rightarrow -20\log(10) = -20dB$




*-A change in frequency by a factor of 2, equivalent to 1 octave, results in a 6-dB change in the ratio as noted by the change in gain from  $f_1/2$  to  $f_1$ .*

*-For a 10:1 change in frequency, equivalent to 1 decade, there is a 20-dB change in the ratio as demonstrated between the frequencies of*

**Ex.** For the given network:

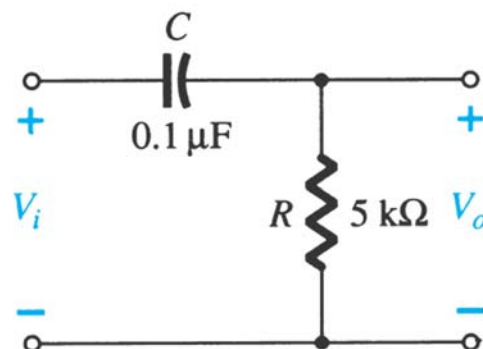
- (a) Determine the break frequency.
- (b) Sketch the asymptotes and locate the -3-dB point.
- (c) Sketch the frequency response curve.



**Solution:**


(a)  $f_1 = \frac{1}{2\pi RC} = \frac{1}{2\pi(5 \times 10^3 \Omega)(0.1 \times 10^{-6} \text{ F})} \cong 318.5\text{Hz}$

(b) See Figure below

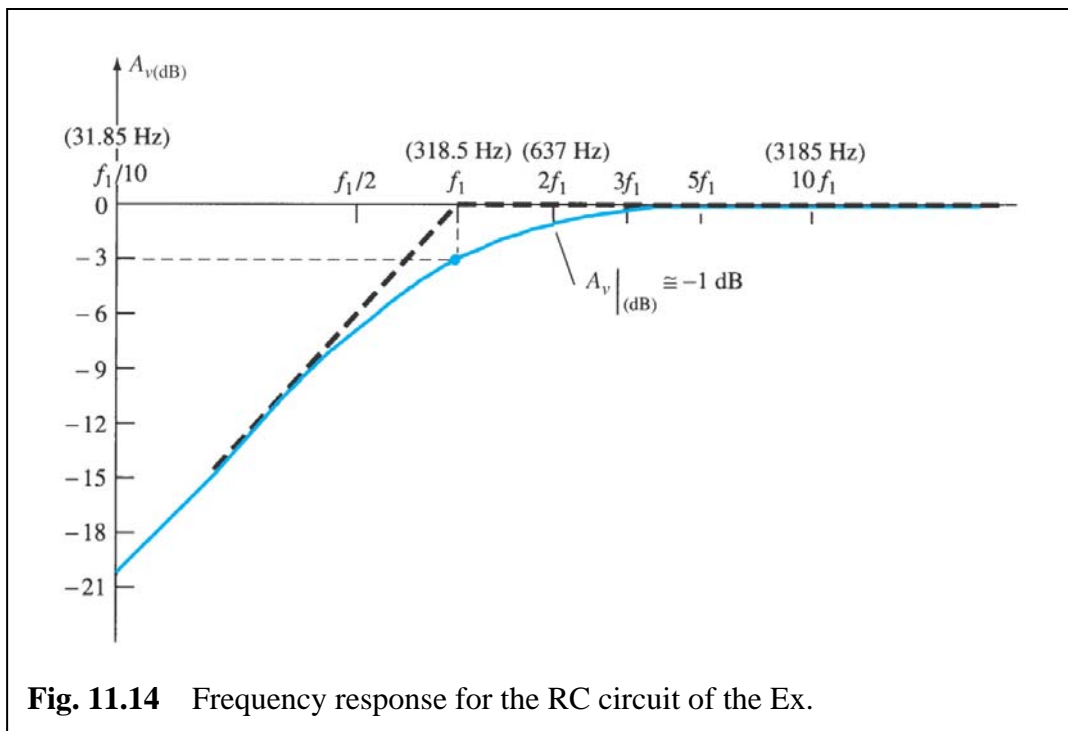


- **Low Frequency Analysis-BJT Amplifiers:**

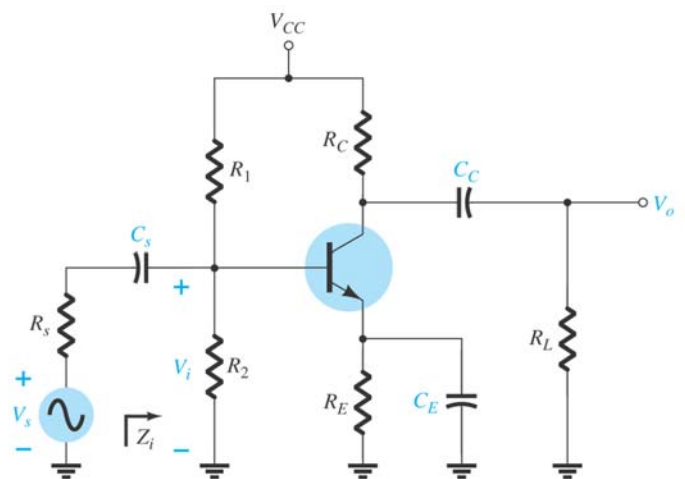- The analysis of this section will employ the loaded voltage-divider BJT bias configuration, but the results can be applied to any BJT configuration.
- It will simply be necessary to find the appropriate equivalent resistance for the R-C combination (for the capacitors  $C_s$ ,  $C_C$ , and  $C_E$ , which will determine the low-frequency response).



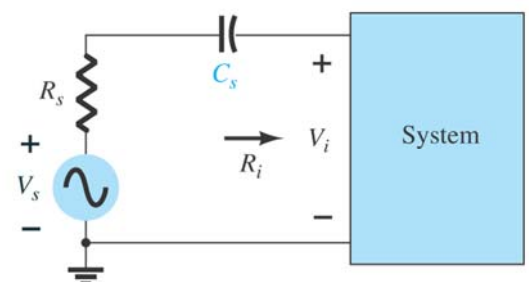1) The effect of  $C_s$ :

- Since  $C_s$  is normally connected between the applied source and the active device, the total resistance is now  $R_s + R_i$ , and the cutoff frequency will be modified to be as:




$$f_{Ls} = \frac{1}{2\pi(R_s + R_i)C_s}$$

- At mid or high frequencies, the reactance of the capacitor will be sufficiently small to permit a short-circuit approximation for the element. The voltage  $V_i$  will then be related to  $V_s$  by

$$V_i |_{mid} = V_s \frac{R_i}{R_i + R_s}$$

- The voltage  $V_i$  applied to the input of the active device can be calculated using the voltage-divider rule:


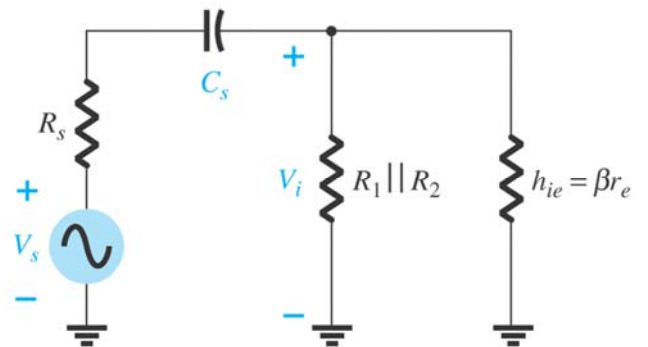
$$V_i = V_s \frac{R_i}{R_s + R_i - jX_{C_s}}$$



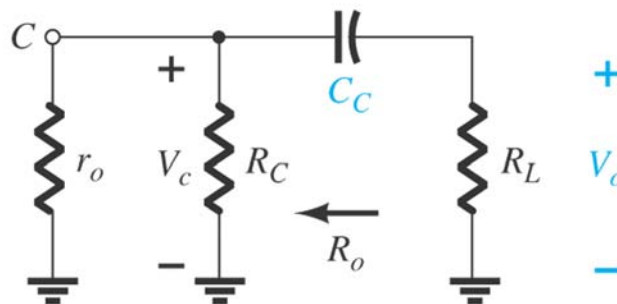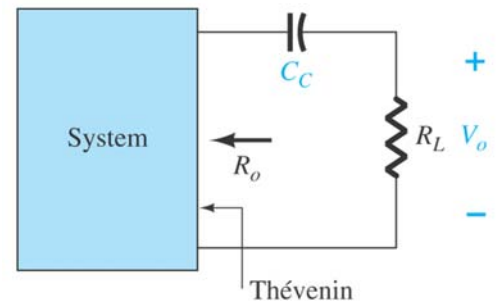2) The effect of  $C_C$ :

- Since  $C_C$  the coupling capacitor is normally connected between the output of the active device and the applied load, the total resistance is now  $R_o + R_L$ , and the cutoff frequency will be modified to be as:

$$f_{LC} = \frac{1}{2\pi(R_o + R_L)C_C}$$





3) The effect of  $C_E$ :


- To determine  $f_{LE}$ , the network “seen” by  $C_E$  must be determined as shown in the Fig. below. Once the level of  $R_e$  is established, the cutoff frequency due to  $C_E$  can be determined using the following equation:

$$f_{LE} = \frac{1}{2\pi(R_e)C_E}$$

where  $R_e$  could be calculated as:

$$R_e = R_E // \left( \frac{R_S // R_1 // R_2}{\beta} + r_e \right)$$

where  $R_S // R_1 // R_2 = R'_S$

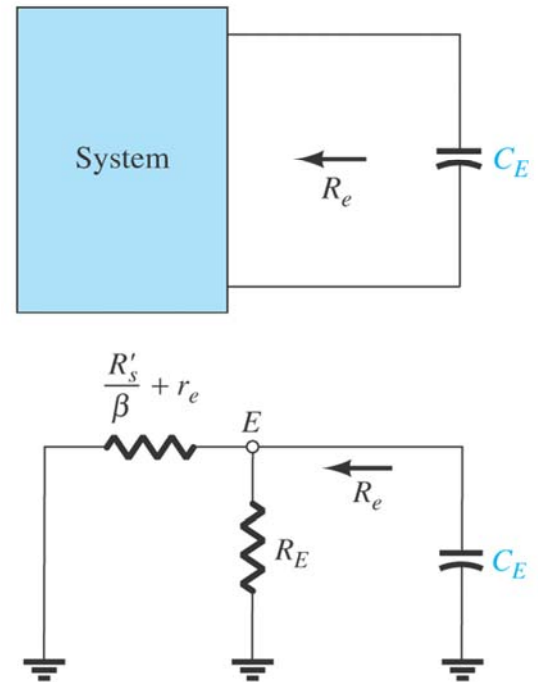

**Ex.** (a) Determine the lower cutoff frequency for the voltage-divider BJT bias configuration network using the following parameters:

$C_S = 10\mu\text{F}$ ,  $C_E = 20\mu\text{F}$ ,  $C_C = 1\mu\text{F}$ ,  $R_S = 1\text{k}\Omega$ ,  $R_1 = 40\text{k}\Omega$ ,  $R_2 = 10\text{k}\Omega$ ,  $R_E = 2\text{k}\Omega$ ,  $R_C = 4\text{k}\Omega$ ,  $R_L = 2.2\text{ k}\Omega$ ,  $\beta = 100$ ,  $r_o = \infty$ ,  $V_{CC} = 20\text{V}$ .

(b) Sketch the frequency response using a Bode plot.

**Solution:**

(a) Determining  $r_e$  for dc conditions:

$$\beta R_E = (100)(2\text{ k}\Omega) = 200\text{ k}\Omega \gg 10R_2 = 100\text{ k}\Omega$$

The result is:

$$V_B \cong \frac{R_2 V_{CC}}{R_2 + R_1} = \frac{10\text{ k}\Omega(20\text{ V})}{10\text{ k}\Omega + 40\text{ k}\Omega} = \frac{200\text{ V}}{50} = 4\text{ V}$$

with 
$$I_E = \frac{V_E}{R_E} = \frac{4\text{ V} - 0.7\text{ V}}{2\text{ k}\Omega} = \frac{3.3\text{ V}}{2\text{ k}\Omega} = 1.65\text{ mA}$$

so that 
$$r_e = \frac{26\text{ mV}}{1.65\text{ mA}} \cong 15.76\ \Omega$$

and 
$$\beta r_e = 100(15.76\ \Omega) = 1576\ \Omega = 1.576\text{ k}\Omega$$

$$\text{Midband Gain } A_v = \frac{V_o}{V_i} = \frac{-R_C || R_L}{r_e} = -\frac{(4 \text{ k}\Omega) || (2.2 \text{ k}\Omega)}{15.76 \text{ }\Omega} \cong -90$$

$$\begin{aligned} \text{The input impedance } Z_i = R_i = R_1 || R_2 || \beta r_e \\ = 40 \text{ k}\Omega || 10 \text{ k}\Omega || 1.576 \text{ k}\Omega \\ \cong 1.32 \text{ k}\Omega \end{aligned}$$

and

$$V_i = \frac{R_i V_s}{R_i + R_s}$$

$$\text{or } \frac{V_i}{V_s} = \frac{R_i}{R_i + R_s} = \frac{1.32 \text{ k}\Omega}{1.32 \text{ k}\Omega + 1 \text{ k}\Omega} = 0.569$$

$$\begin{aligned} \text{so that } A_{v_s} = \frac{V_o}{V_s} = \frac{V_o}{V_i} \frac{V_i}{V_s} = (-90)(0.569) \\ = -51.21 \end{aligned}$$

 $C_s$ 

$$R_i = R_1 || R_2 || \beta r_e = 40 \text{ k}\Omega || 10 \text{ k}\Omega || 1.576 \text{ k}\Omega \cong 1.32 \text{ k}\Omega$$

$$\begin{aligned} f_{L_s} = \frac{1}{2\pi (R_s + R_i) C_s} = \frac{1}{(6.28)(1 \text{ k}\Omega + 1.32 \text{ k}\Omega)(10 \text{ }\mu\text{F})} \\ f_{L_s} \cong 6.86 \text{ Hz} \end{aligned}$$

 $C_C$ 

$$\begin{aligned} f_{L_C} = \frac{1}{2\pi (R_C + R_L) C_C} \\ = \frac{1}{(6.28)(4 \text{ k}\Omega + 2.2 \text{ k}\Omega)(1 \text{ }\mu\text{F})} \\ \cong 25.68 \text{ Hz} \end{aligned}$$


 $C_E$ 

$$R'_s = R_s || R_1 || R_2 = 1 \text{ k}\Omega || 40 \text{ k}\Omega || 10 \text{ k}\Omega \cong 0.889 \text{ k}\Omega$$

$$\begin{aligned} R_e = R_E || \left( \frac{R'_s}{\beta} + r_e \right) = 2 \text{ k}\Omega || \left( \frac{0.889 \text{ k}\Omega}{100} + 15.76 \text{ }\Omega \right) \\ = 2 \text{ k}\Omega || (8.89 \text{ }\Omega + 15.76 \text{ }\Omega) = 2 \text{ k}\Omega || 24.65 \text{ }\Omega \cong 24.35 \text{ }\Omega \end{aligned}$$


$$f_{L_E} = \frac{1}{2\pi R_e C_E} = \frac{1}{(6.28)(24.35 \text{ }\Omega)(20 \text{ }\mu\text{F})} = \frac{10^6}{3058.36} \cong 327 \text{ Hz}$$

(b)

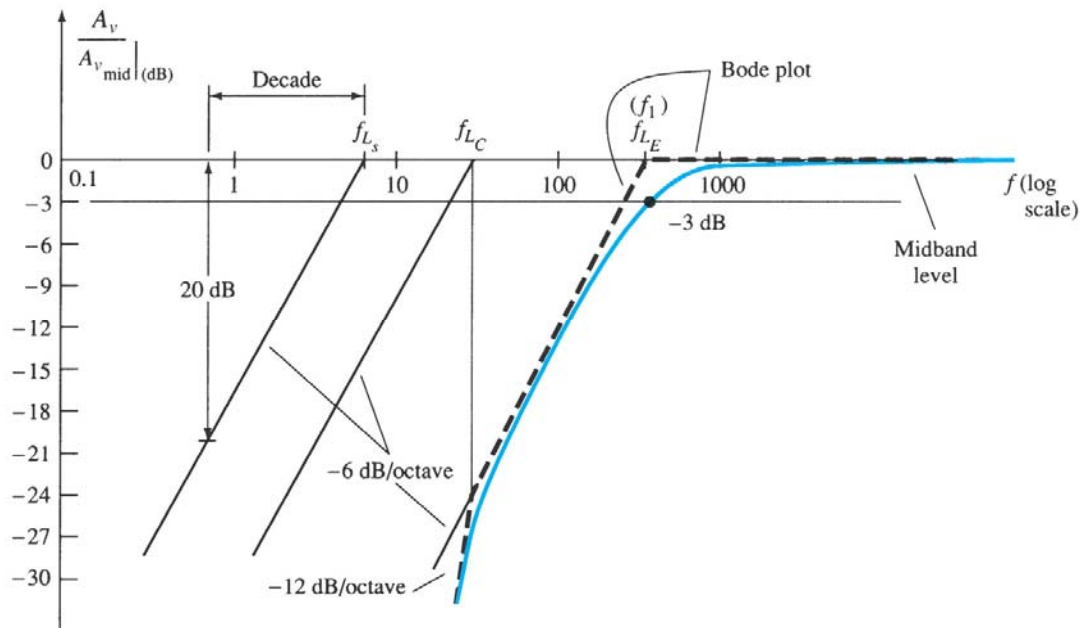

- **Low Frequency Analysis-FET Amplifiers:**

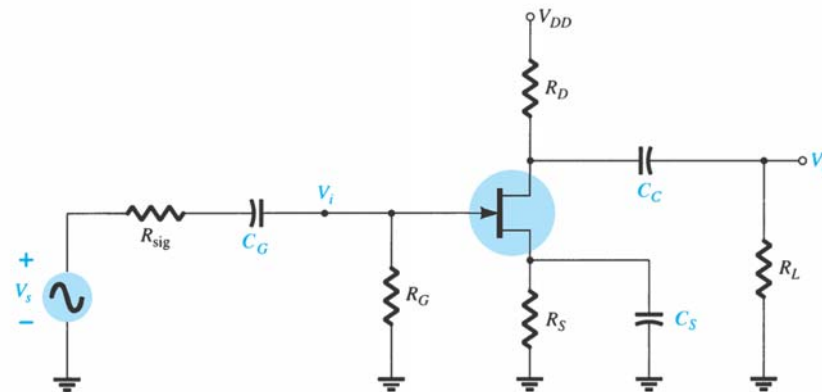
- The analysis of the analysis of the FET amplifier in the low-frequency region will be quite similar to that of the BJT amplifier. There are again three capacitors of primary concern as appearing in the given network:  $C_G$ ,  $C_C$ , and  $C_S$ .



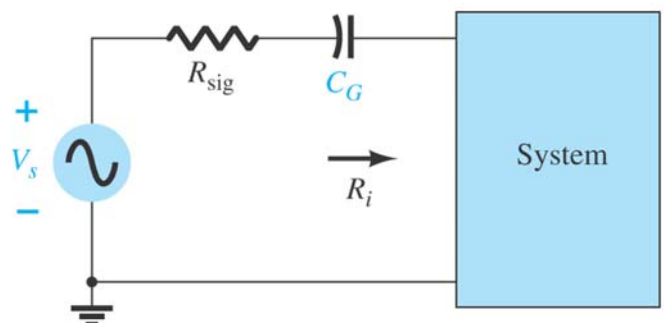1) The effect of  $C_G$ :

The cutoff frequency determined by  $C_G$  will then be

$$f_{LG} = \frac{1}{2\pi(R_G + R_{sig})C_G}$$




2) The effect of  $C_C$ :

The cutoff frequency determined by  $C_C$  will then be

$$f_{LC} = \frac{1}{2\pi(R_L + R_o)C_C}$$

where  $R_o = R_D // r_d$

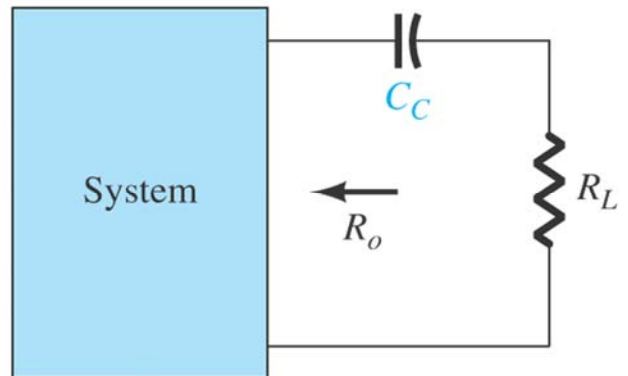

3) The effect of  $C_S$ :


The cutoff frequency determined by  $C_S$  will then be

$$f_{LS} = \frac{1}{2\pi(R_{eg})C_S}$$

$$\text{where } R_{eg} = \frac{R_S}{1 + \left[ \frac{R_S(1 + g_m r_d)}{r_d + R_G // R_L} \right]}$$

which for  $r_d \cong \infty$  becomes
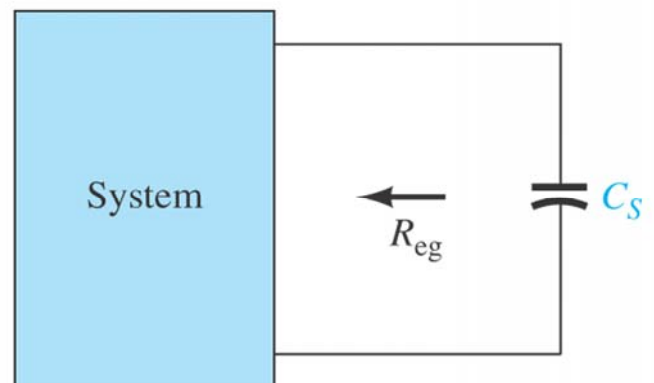
$$R_{eg} = R_S // \left( \frac{1}{g_m} \right)$$



**Ex.** (a) Determine the lower cutoff frequency for the CS FET bias configuration network using the following parameters:

$C_G = 0.01\mu\text{F}$ ,  $C_C = 0.5\mu\text{F}$ ,  $C_S = 2\mu\text{F}$ ,  $R_{sig} = 10\text{k}\Omega$ ,  $R_G = 1\text{M}\Omega$ ,  $R_D = 4.7\text{k}\Omega$ ,  $R_S = 1\text{k}\Omega$ ,  $R_L = 2.2\text{k}\Omega$ ,  $I_{DSS} = 8\text{mA}$ ,  $V_P = -4\text{V}$ ,  $r_d = \infty$ ,  $V_{DD} = 20\text{V}$ .

(b) Sketch the frequency response using a Bode plot.

**Solution:**

(a) DC Analysis: Plotting the transfer curve of  $I_D = I_{DSS}(1 - V_{GS}/V_P)^2$  and superimposing the curve defined by  $V_{GS} = -I_D R_S$  will result in an intersection at  $V_{GS_Q} = -2\text{V}$  and  $I_{D_Q} = 2\text{mA}$ . In addition,

$$g_{m0} = \frac{2I_{DSS}}{|V_P|} = \frac{2(8\text{mA})}{4\text{V}} = 4\text{mS}$$

$$g_m = g_{m0} \left( 1 - \frac{V_{GS_Q}}{V_P} \right) = 4\text{mS} \left( 1 - \frac{-2\text{V}}{-4\text{V}} \right) = 2\text{mS}$$

$$C_G \quad f_{L_G} = \frac{1}{2\pi (10 \text{ k}\Omega + 1 \text{ M}\Omega)(0.01 \text{ }\mu\text{F})} \cong 15.8 \text{ Hz}$$

$$C_C \quad f_{L_C} = \frac{1}{2\pi (4.7 \text{ k}\Omega + 2.2 \text{ k}\Omega)(0.5 \text{ }\mu\text{F})} \cong 46.13 \text{ Hz}$$

$$C_S \quad R_{\text{eq}} = R_S \parallel \frac{1}{g_m} = 1 \text{ k}\Omega \parallel \frac{1}{2 \text{ mS}} = 1 \text{ k}\Omega \parallel 0.5 \text{ k}\Omega = 333.33 \text{ }\Omega$$

$$f_{L_S} = \frac{1}{2\pi (333.33 \text{ }\Omega)(2 \text{ }\mu\text{F})} = 238.73 \text{ Hz}$$


Since  $f_{L_S}$  is the largest of the three cutoff frequencies, it defines the low cutoff frequency for the network.

(b) The midband gain of the system is determined by

$$A_{v_{\text{mid}}} = \frac{V_o}{V_i} = -g_m(R_D \parallel R_L) = -(2 \text{ mS})(4.7 \text{ k}\Omega \parallel 2.2 \text{ k}\Omega)$$

$$= -(2 \text{ mS})(1.499 \text{ k}\Omega)$$

$$\cong -3$$

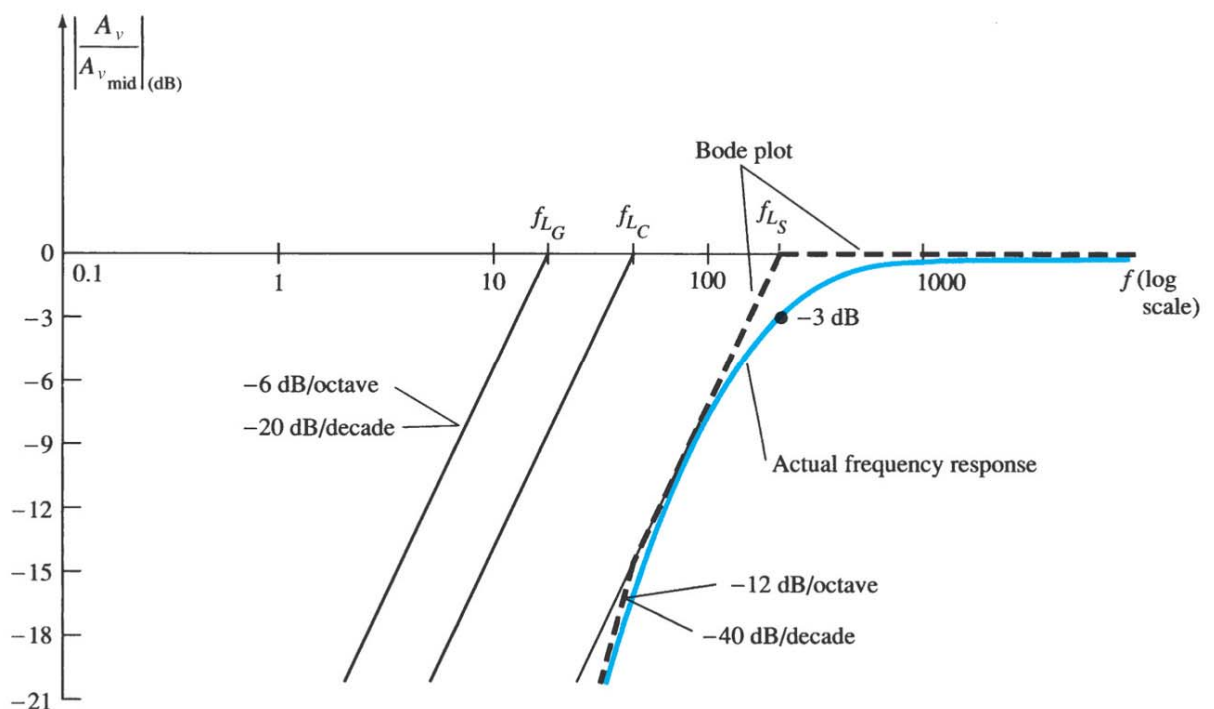

- **Miller Effect capacitance:**

In the high-frequency region, the capacitive elements of importance are the interelectrode (between terminals) capacitances internal to the active device and the wiring capacitance between leads of the network. The large capacitors of the network that controlled the low-frequency response have all been replaced by their short-circuit equivalent due to their very low reactance levels.

▪ **Miller input capacitance**

$$C_{Mi} = (1 - A_v)C_f$$

where  $C_f$  is the feedback capacitance.

▪ **Miller output capacitance**


$$C_{Mo} = \left(1 - \frac{1}{A_v}\right)C_f \cong_{|A_v \gg 1} C_f$$

where  $C_f$  is the feedback capacitance.


- **High Frequency Analysis-BJT Amplifiers:**

In the high-frequency region, the RC network of concern has the configuration appearing in given Fig. At increasing frequencies, the reactance  $X_C$  will decrease in magnitude, resulting in a shorting effect across the output and a decrease in gain.

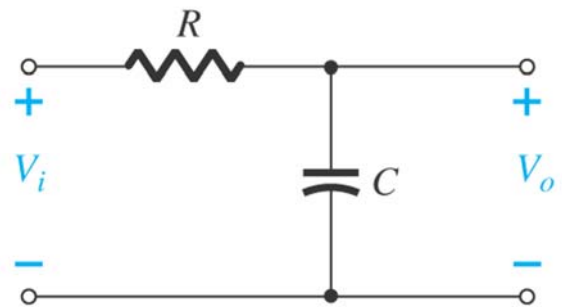The derivation leading to the corner frequency for this RC configuration follows along similar lines to that encountered for the low-frequency region. The most significant difference is in the general form of  $A_v$  appearing below:


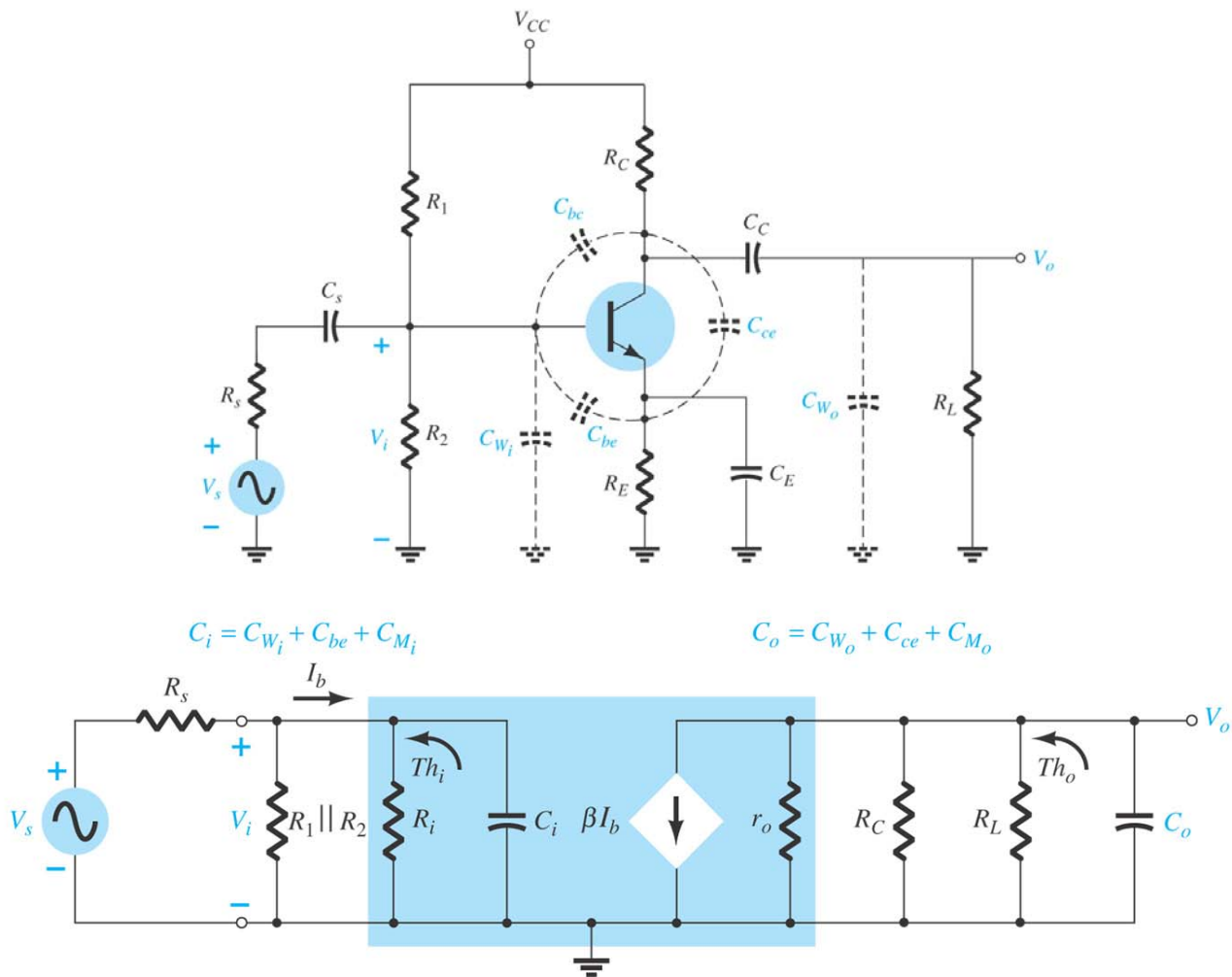
$$A_v = \frac{1}{1 + j\left(\frac{f}{f_2}\right)}$$



- In the above Fig., the various parasitic capacitances ( $C_{be}$ ,  $C_{bc}$ ,  $C_{ce}$ ) of the transistor have been included with the wiring capacitances ( $C_{W_i}$ ,  $C_{W_o}$ ) introduced during construction.
- In the high-frequency equivalent model for the network, note the absence of the capacitors  $C_s$ ,  $C_C$ , and  $C_E$ , which are all assumed to be in the short-circuit state at these frequencies.
- The capacitance  $C_i$  includes the input wiring capacitance  $C_{W_i}$ , the transition capacitance  $C_{be}$ , and the Miller capacitance  $C_{M_i}$ .
- The capacitance  $C_o$  includes the output wiring capacitance  $C_{W_o}$ , the parasitic capacitance  $C_{ce}$ , and the output Miller capacitance  $C_{M_o}$ .
- In general, the capacitance  $C_{be}$  is the largest of the parasitic capacitances, with  $C_{ce}$  the smallest. In fact, most specification sheets simply provide the levels of  $C_{be}$  and  $C_{bc}$  and do not include  $C_{ce}$  unless it will affect the response of a particular type of transistor in a specific area of application.

1) For the input network,  $C_i$ :

For the input network, the -3-dB frequency is defined by

$$f_{Hi} = \frac{1}{2\pi R_{Thi} C_i}$$

where

$$R_{Th1} = R_s || R_1 || R_2 || R_i$$

$$C_i = C_{Wi} + C_{be} + C_{Mi} = C_{Wi} + C_{be} + (1 - A_v) C_{bc}$$

2) For the output network,  $C_o$ :

$$f_{Ho} = \frac{1}{2\pi R_{Th2} C_o}$$

$$R_{Th2} = R_C || R_L || r_o$$

$$C_o = C_{Wo} + C_{ce} + C_{Mo}$$

**Ex.** For the given network, with the following parameters:

$C_s = 10\mu\text{F}$ ,  $C_E = 20\mu\text{F}$ ,  $C_C = 1\mu\text{F}$ ,  $R_s = 1\text{k}\Omega$ ,  $R_1 = 40\text{k}\Omega$ ,  $R_2 = 10\text{k}\Omega$ ,  $R_E = 2\text{k}\Omega$ ,  $R_C = 4\text{k}\Omega$ ,  $R_L = 2.2\text{ k}\Omega$ ,  $\beta = 100$ ,  $r_o = \infty$ ,  $V_{CC} = 20\text{V}$ .

with the addition of

$C_{be} = 36\text{pF}$ ,  $C_{bc} = 4\text{pF}$ ,  $C_{ce} = 1\text{pF}$ ,  $C_{Wi} = 6\text{pF}$ ,  $C_{Wo} = 8\text{pF}$

(a) Determine  $f_{Hi}$  and  $f_{Ho}$ .

(b) Sketch the total frequency response for the low- and high-frequency regions.

**Solution:**

(a) from previous example

$$R_i = 1.32\text{ k}\Omega, \quad A_{v_{mid}}(\text{amplifier}) = -90$$

$$\text{and} \quad R_{Th1} = R_s || R_1 || R_2 || R_i = 1\text{ k}\Omega || 40\text{ k}\Omega || 10\text{ k}\Omega || 1.32\text{ k}\Omega \\ \cong 0.531\text{ k}\Omega$$



with

$$C_i = C_{W_i} + C_{be} + (1 - A_v)C_{be}$$

$$= 6 \text{ pF} + 36 \text{ pF} + [1 - (-90)]4 \text{ pF}$$

$$= 406 \text{ pF}$$

$$f_{H_i} = \frac{1}{2\pi R_{Th_1} C_i} = \frac{1}{2\pi (0.531 \text{ k}\Omega)(406 \text{ pF})}$$

$$= 738.24 \text{ kHz}$$

$$R_{Th_2} = R_C || R_L = 4 \text{ k}\Omega || 2.2 \text{ k}\Omega = 1.419 \text{ k}\Omega$$


$$C_o = C_{W_o} + C_{ce} + C_{M_o} = 8 \text{ pF} + 1 \text{ pF} + \left(1 - \frac{1}{-90}\right) 4 \text{ pF}$$

$$= 13.04 \text{ pF}$$

$$f_{H_o} = \frac{1}{2\pi R_{Th_2} C_o} = \frac{1}{2\pi (1.419 \text{ k}\Omega)(13.04 \text{ pF})}$$


$$= 8.6 \text{ MHz}$$

(b)

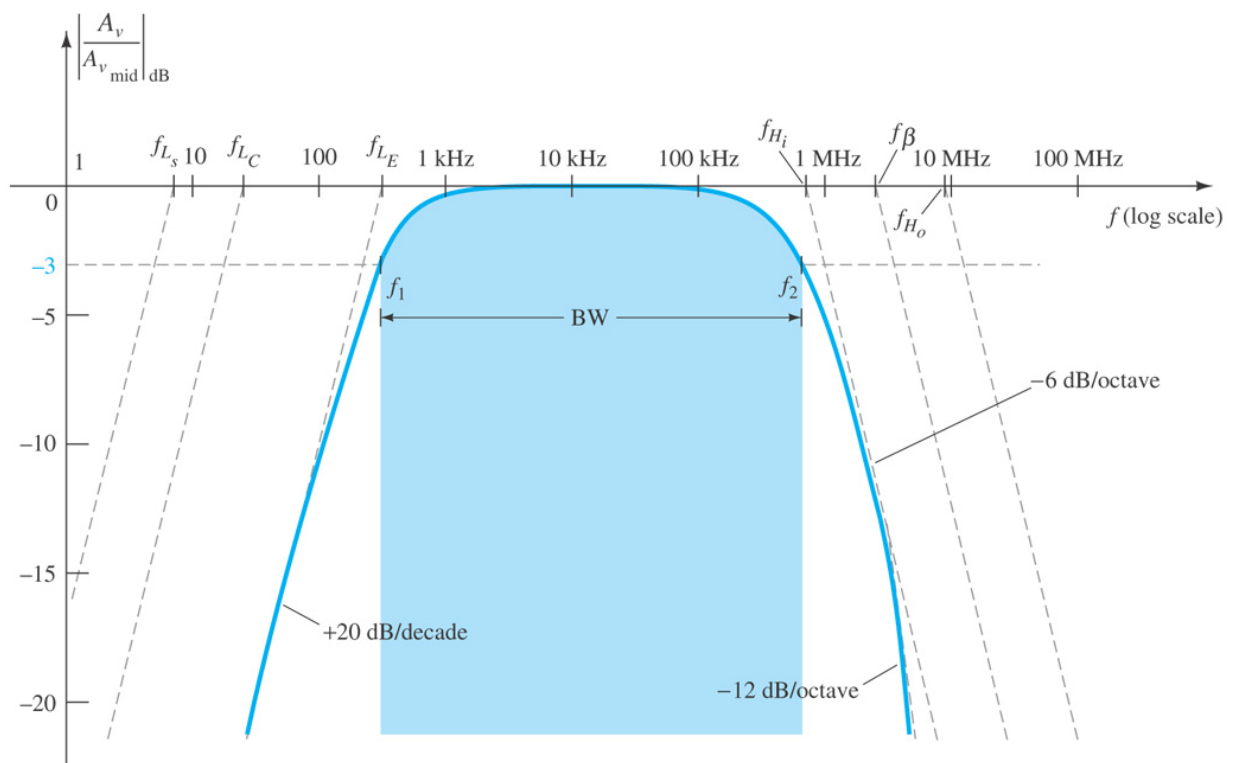

- **High Frequency Analysis-FET Amplifiers:**

- The analysis of the high-frequency response of the FET amplifier will proceed in a very similar manner to that encountered for the BJT amplifier. There are interelectrode and wiring capacitances that will determine the high-frequency characteristics of the amplifier.
- The capacitors  $C_{gs}$  and  $C_{gd}$  typically vary from 1 to 10 pF, while the capacitance  $C_{ds}$  is usually quite a bit smaller, ranging from 0.1 to 1 pF.
- At high frequencies,  $C_i$  will approach a short-circuit equivalent and  $V_{gs}$  will drop in value and reduce the overall gain. At frequencies where  $C_o$  approaches its short circuit equivalent, the parallel output voltage  $V_o$  will drop in magnitude.

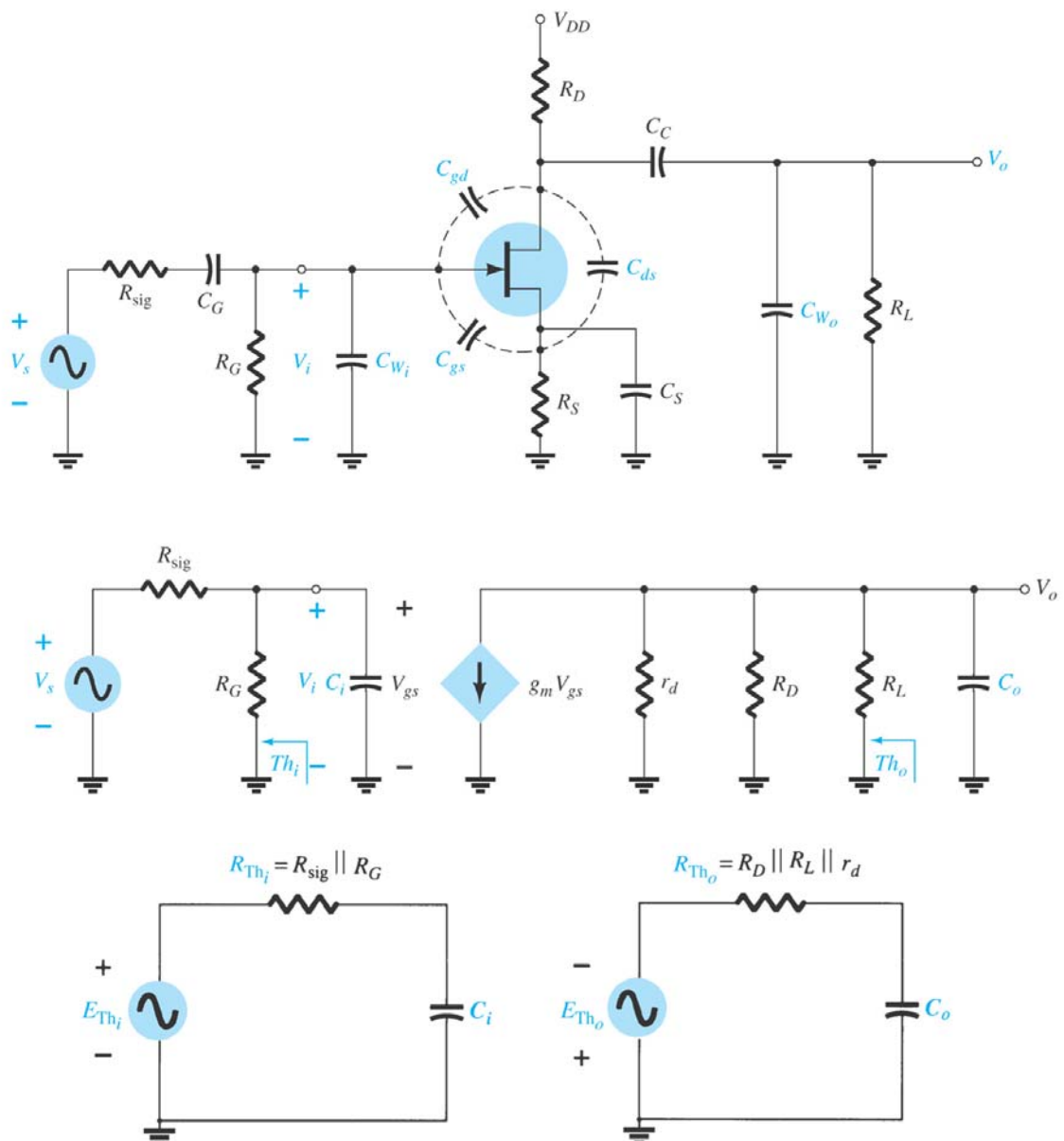

$$f_{H_i} = \frac{1}{2\pi R_{Th_1} C_i}$$

and

$$R_{Th_1} = R_{sig} || R_G$$

with

$$C_i = C_{W_i} + C_{gs} + C_{M_i}$$

and

$$C_{M_i} = (1 - A_v) C_{gd}$$

and for the output circuit,

$$f_{H_o} = \frac{1}{2\pi R_{Th_2} C_o}$$

with

$$R_{Th_2} = R_D || R_L || r_d$$

and

$$C_o = C_{W_o} + C_{ds} + C_{M_o}$$

and

$$C_{M_o} = \left(1 - \frac{1}{A_v}\right) C_{gd}$$

**Ex.** (a) Determine the high cutoff frequencies for the CS FET bias configuration network using the following parameters:

$C_G = 0.01\mu\text{F}$ ,  $C_C = 0.5\mu\text{F}$ ,  $C_S = 2\mu\text{F}$ ,  $R_{sig} = 10\text{k}\Omega$ ,  $R_G = 1\text{M}\Omega$ ,  $R_D = 4.7\text{k}\Omega$ ,  $R_S = 1\text{k}\Omega$ ,  $R_L = 2.2\text{k}\Omega$ ,  $I_{DSS} = 8\text{mA}$ ,  $V_p = -4\text{V}$ ,  $r_d = \infty$ ,  $V_{DD} = 20\text{V}$ .

$C_{gd} = 2\text{pF}$ ,  $C_{gs} = 4\text{pF}$ ,  $C_{ds} = 0.5\text{pF}$ ,  $C_{W_i} = 5\text{pF}$ ,  $C_{W_o} = 6\text{pF}$

**Solution:**

(a) From the previous example

$$R_{Th_1} = R_{sig} || R_G = 10\text{ k}\Omega || 1\text{ M}\Omega = 9.9\text{ k}\Omega$$

$$A_v = -3.$$

$$\begin{aligned}
 C_i &= C_{W_i} + C_{gs} + (1 - A_v)C_{gd} \\
 &= 5 \text{ pF} + 4 \text{ pF} + (1 + 3)2 \text{ pF} \\
 &= 9 \text{ pF} + 8 \text{ pF} \\
 &= 17 \text{ pF}
 \end{aligned}$$

$$\begin{aligned}
 f_{Hi} &= \frac{1}{2\pi R_{Th_1} C_i} \\
 &= \frac{1}{2\pi(9.9 \text{ k}\Omega)(17 \text{ pF})} = 945.67 \text{ kHz}
 \end{aligned}$$

$$\begin{aligned}
 R_{Th_2} &= R_D || R_L \\
 &= 4.7 \text{ k}\Omega || 2.2 \text{ k}\Omega \\
 &\cong 1.5 \text{ k}\Omega
 \end{aligned}$$

$$C_o = C_{W_o} + C_{ds} + C_{M_o} = 6 \text{ pF} + 0.5 \text{ pF} + \left(1 - \frac{1}{-3}\right)2 \text{ pF} = 9.17 \text{ pF}$$

$$f_{Ho} = \frac{1}{2\pi(1.5 \text{ k}\Omega)(9.17 \text{ pF})} = 11.57 \text{ MHz}$$


- **Multistage Frequency Effect:**

- **For Low Frequency region**

$$f'_1 = \frac{f_1}{\sqrt{2\left(\frac{1}{n}\right) - 1}}$$

- **For High Frequency region**

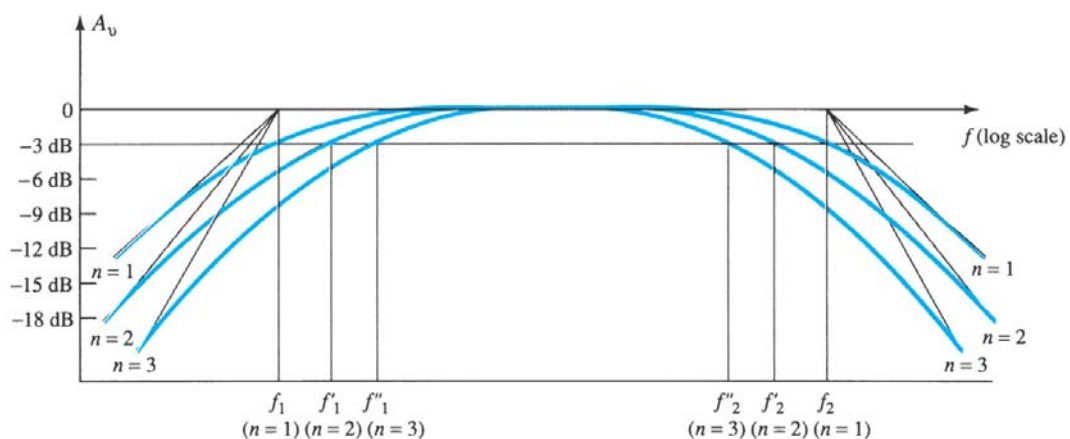
$$f'_2 = \left( \sqrt{2\left(\frac{1}{n}\right) - 1} \right) f_2$$



- **Square wave Testing:**

- Experimentally, the sense for the frequency response can be determined by applying a square wave signal to the amplifier and noting the output response.
- The reason for choosing a square-wave signal for the testing process is best described by examining the Fourier series expansion of a square wave composed of a series of sinusoidal components of different magnitudes and frequencies. The summation of the terms of the series will result in the original waveform. In other words, even though a waveform may not be sinusoidal, it can be reproduced by a series of sinusoidal terms of different frequencies and magnitudes.
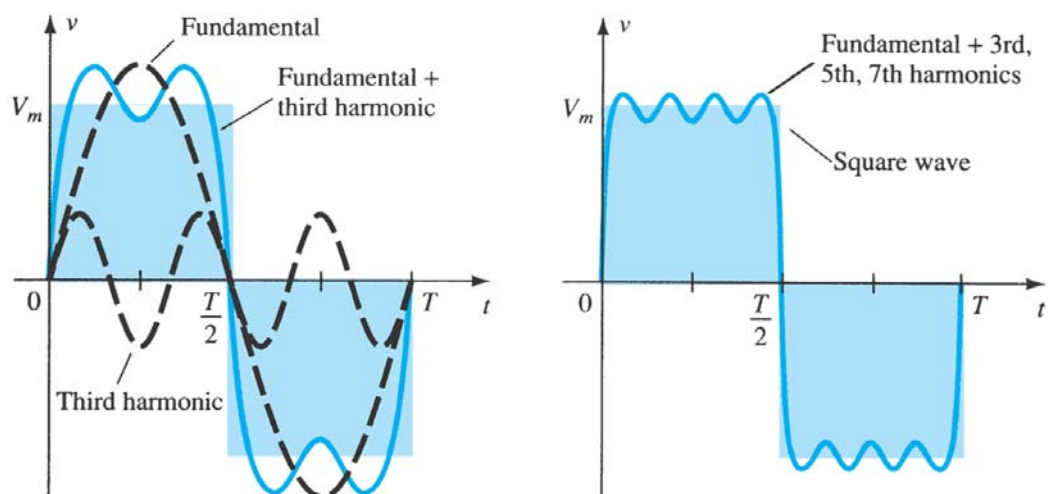
$$v = \frac{4}{\pi} V_m \left( \sin 2\pi f_s t + \frac{1}{3} \sin 2\pi(3f_s)t + \frac{1}{5} \sin 2\pi(5f_s)t + \frac{1}{7} \sin 2\pi(7f_s)t + \frac{1}{9} \sin 2\pi(9f_s)t + \dots + \frac{1}{n} \sin 2\pi(nf_s)t \right)$$




- Since the ninth harmonic has a magnitude greater than 10% of the fundamental term, the fundamental term through the ninth harmonic are the major contributors to the Fourier series expansion of the square-wave function.


Ex. For a specific application (Audio amplifier with 20kHz Bandwidth), what is the maximum frequency could be amplified?

$$\frac{20\text{kHz}}{9} = 2.2\text{kHz}$$

- If the response of an amplifier to an applied square wave is an undistorted replica of the input, the frequency response (or BW) of the amplifier is obviously sufficient for the applied frequency.
- If the response is as shown in Fig. 11.60a and b, the low frequencies are not being amplified properly and the low cutoff frequency has to be investigated.
- If the waveform has the appearance of Fig. 11.60c, the high-frequency components are not receiving sufficient amplification and the high cutoff frequency (or BW) has to be reviewed.

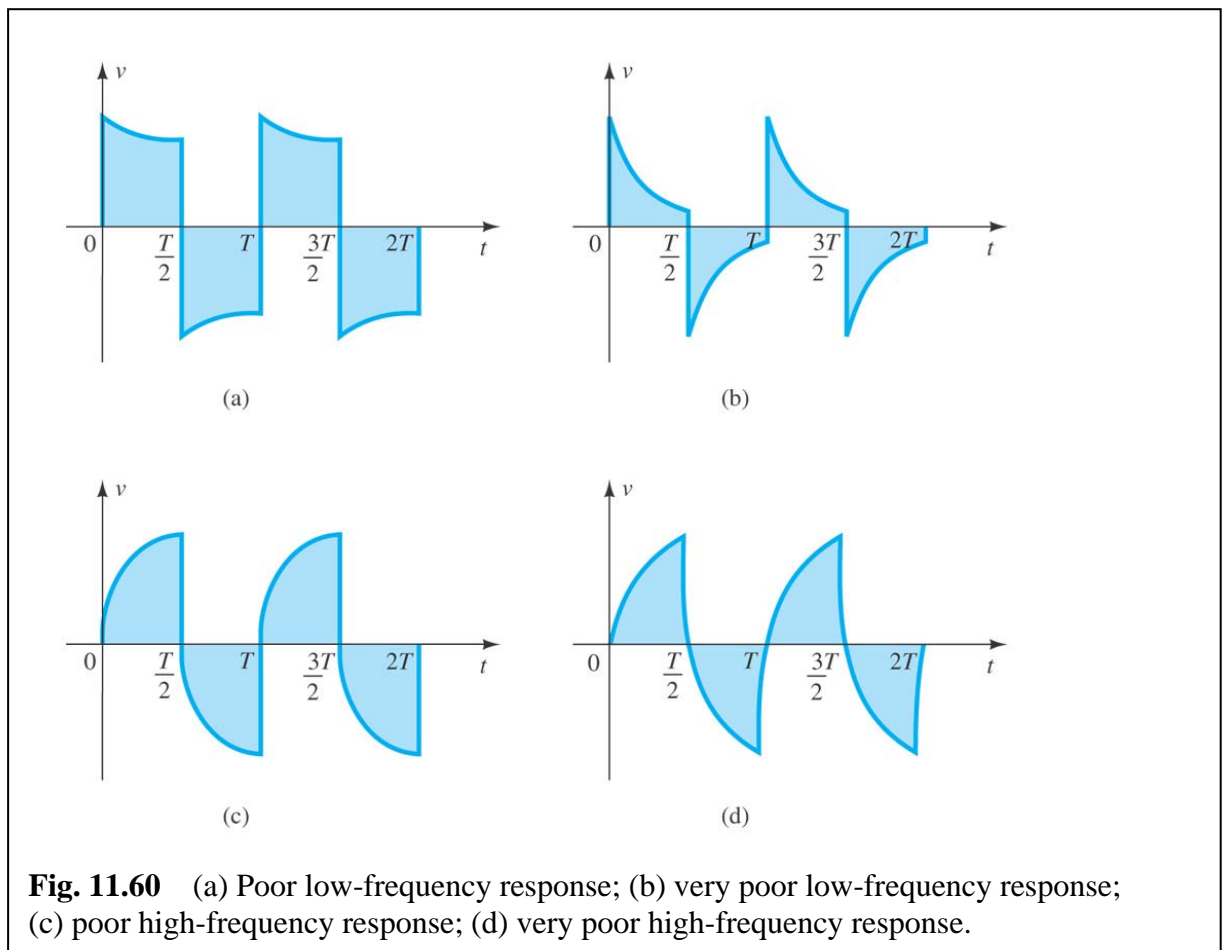

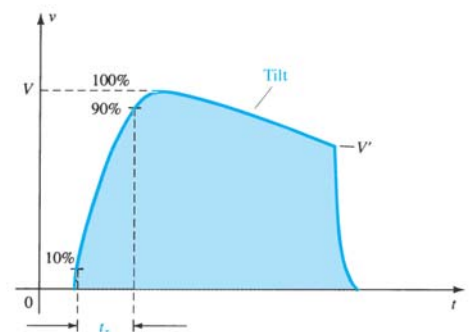- The actual high cutoff frequency (or BW) can be determined from the output waveform by carefully measuring the rise time defined between 10% and 90% of the peak value, as shown in the Fig. below.
- Substituting into the following equation



will provide the upper cutoff frequency, and since  $BW = f_{Hi} - f_{Lo} \cong f_{Hi}$ , the equation also provides an indication of the BW of the amplifier.

$$BW \cong f_{Hi} = \frac{0.35}{t_r}$$

- The low cutoff frequency can be determined from the output response by carefully measuring the tilt and substituting into one of the following equations:


$$\begin{aligned} \% \text{ tilt} = P\% &= \frac{V - V'}{V} \times 100\% \\ &= P = \frac{V - V'}{V} \quad (\text{decimal form}) \end{aligned}$$

- The low cutoff frequency is then determined from

$$f_{Lo} = \frac{P}{\pi} f_s$$

**Ex.** The application of a 1-mV, 5-kHz square wave to an amplifier resulted in the output waveform of the given Fig.

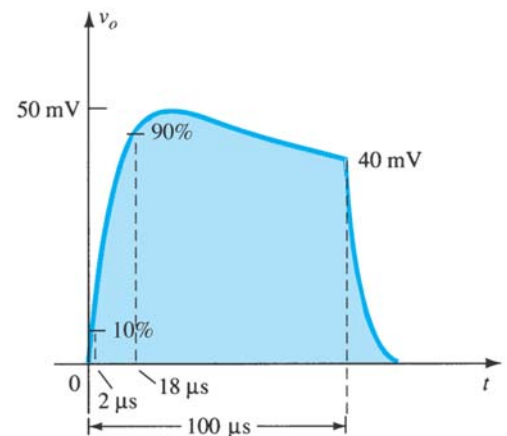- Write the Fourier series expansion for the square wave through the ninth harmonic.
- Determine the bandwidth of the amplifier.



**Solution:**

$$\begin{aligned} \text{(a) } v_i &= \frac{4 \text{ mV}}{\pi} \left( \sin 2\pi (5 \times 10^3)t + \frac{1}{3} \sin 2\pi(15 \times 10^3)t + \frac{1}{5} \sin 2\pi(25 \times 10^3)t \right. \\ &\quad \left. + \frac{1}{7} \sin 2\pi(35 \times 10^3)t + \frac{1}{9} \sin 2\pi(45 \times 10^3)t \right) \end{aligned}$$

$$\text{(b) } t_r = 18 \mu s - 2 \mu s = 16 \mu s$$

$$BW = \frac{0.35}{t_r} = \frac{0.35}{16 \mu s} = 21,875 \text{ Hz} \cong 4.4f_s$$

$$\text{(c) } P = \frac{V - V'}{V} = \frac{50 \text{ mV} - 40 \text{ mV}}{50 \text{ mV}} = 0.2$$

$$f_{Lo} = \frac{P}{\pi} f_s = \left( \frac{0.2}{\pi} \right) (5 \text{ kHz}) = 318.31 \text{ Hz}$$