 


An Introduction to VLSI (Very Large Scale Integrated) Circuit Design

***Presented at EE1001
Oct. 16th, 2012***

By Hua Tang


The First Computer




**The Babbage
Difference Engine
(1832)**

**25,000 parts
cost: £17,470**

The first electronic computer (1946)

 


First Transistor (Bipolar)

 

First transistor
Bell Labs, 1948

The First Integrated Circuits

 


*Bipolar logic
1960's*


ECL 3-input Gate
Motorola 1966

Basic IC circuit component: MOS transistor

MOS: Metal Oxide Semiconductor

 

Intel 4004 Micro-Processor

 


1971

1000 transistors

< 1MHz operation

10 μ m technology

Intel Pentium (IV) microprocessor

 

2001

42 Million transistors

1.5 GHz operation

0.18 μ m technology

More recent Processors

2006

291 Million transistors

3 GHz operation

65nm technology

2007

800 Million transistors

2 GHz operation

45nm technology (the biggest change in CMOS transistor technologies in 40 years)

2010 Core i7

1.2 Billion transistors

3.3 GHz operation


32nm technology

Moore's Law


- In 1965, Gordon Moore noted that the number of transistors on a chip doubled every 18 to 24 months.
- He made a prediction that semiconductor technology will double its effectiveness every 18 months

Moore's law in Microprocessors

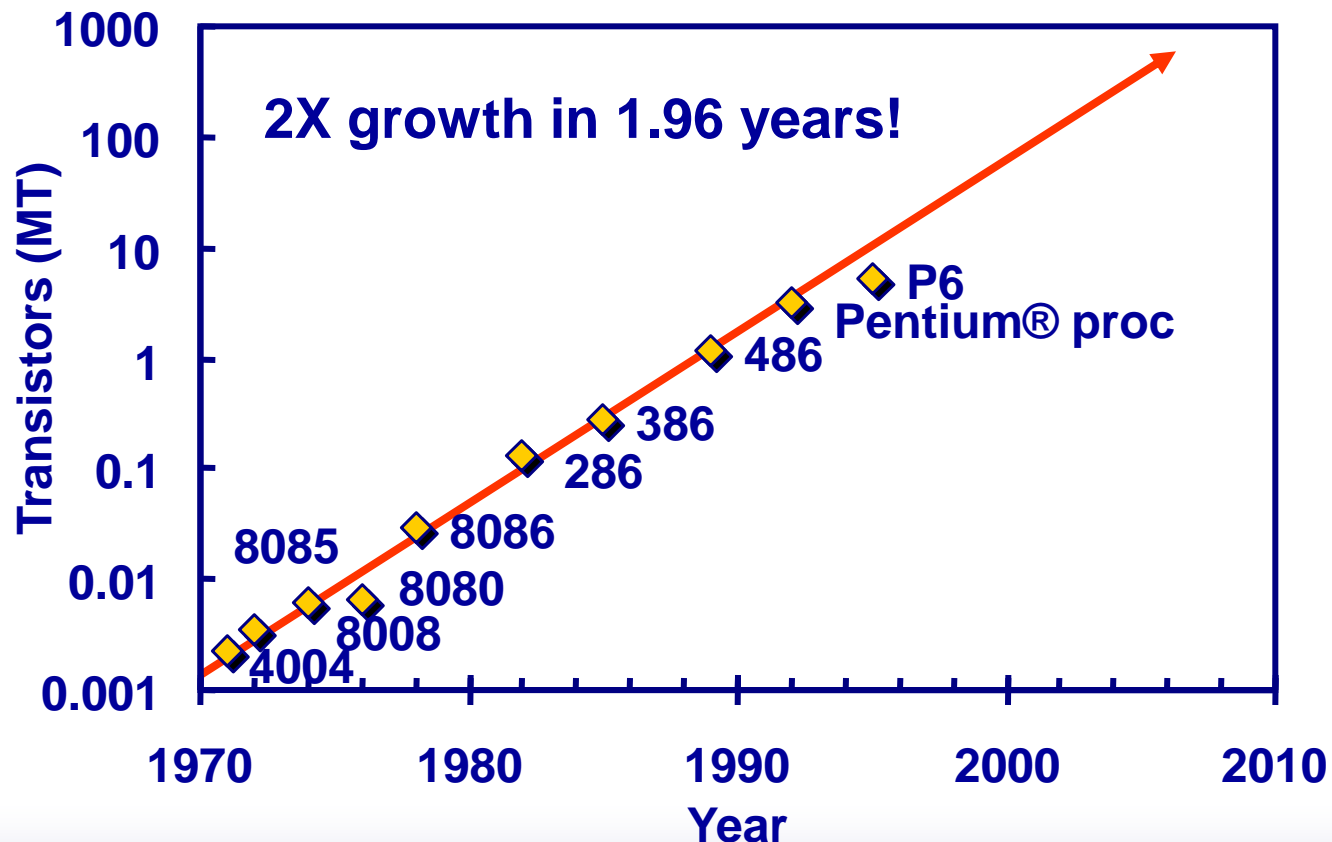Transistors on Lead Microprocessors double every 2 years



Frequency

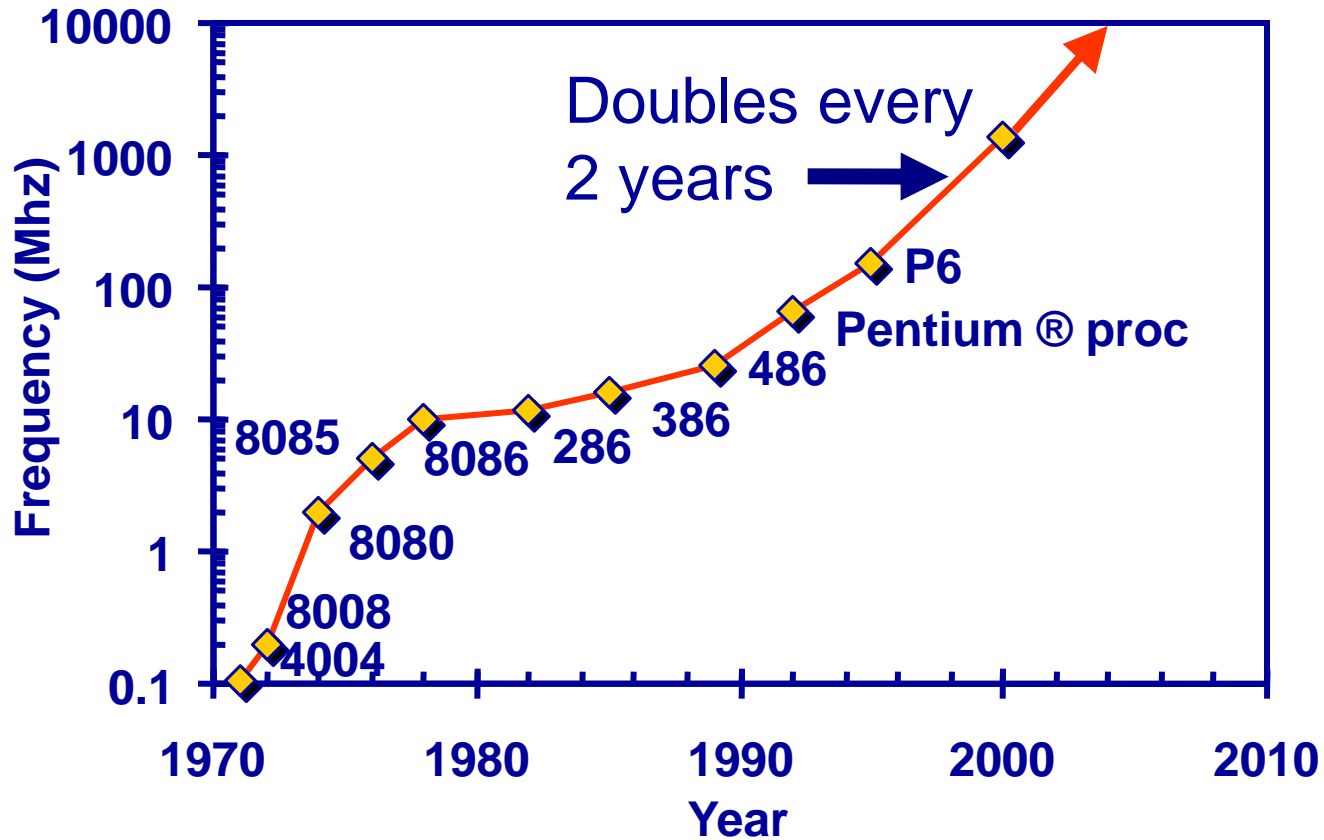

Lead Microprocessors frequency doubles every 2 years


Not Only Microprocessors

Cell Phone

HDTV

PDA

....


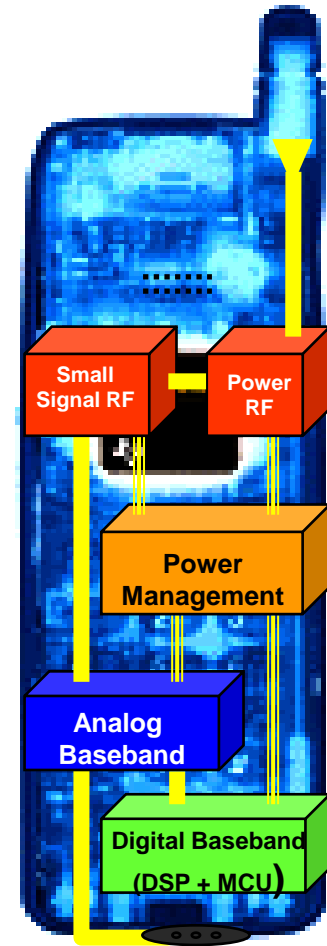


What is a MOS Transistor?


A Switch!



An MOS Transistor

  


MOS Transistors - Types and Symbols

 

if $G = "1"$ or V_{dd}
switch on


NMOS

 

if $G = "0"$ or ground
switch on



PMOS

The CMOS Inverter: A First Glance

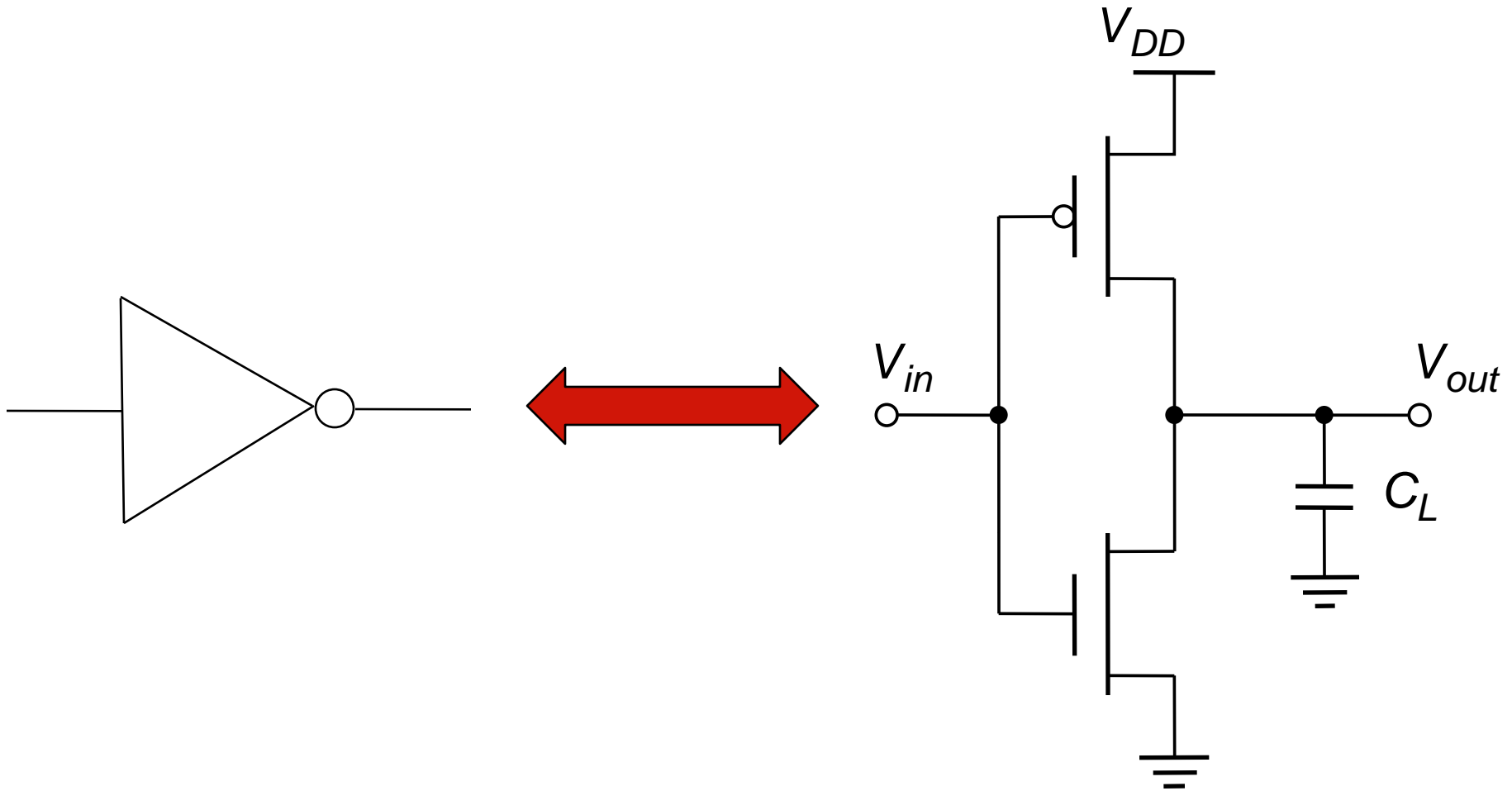


CMOS Inverter

First-Order DC Analysis

  


Transient Response

 

The delay
Essentially
determines the
clock speed of the
processor



Static CMOS (Complementary MOS)

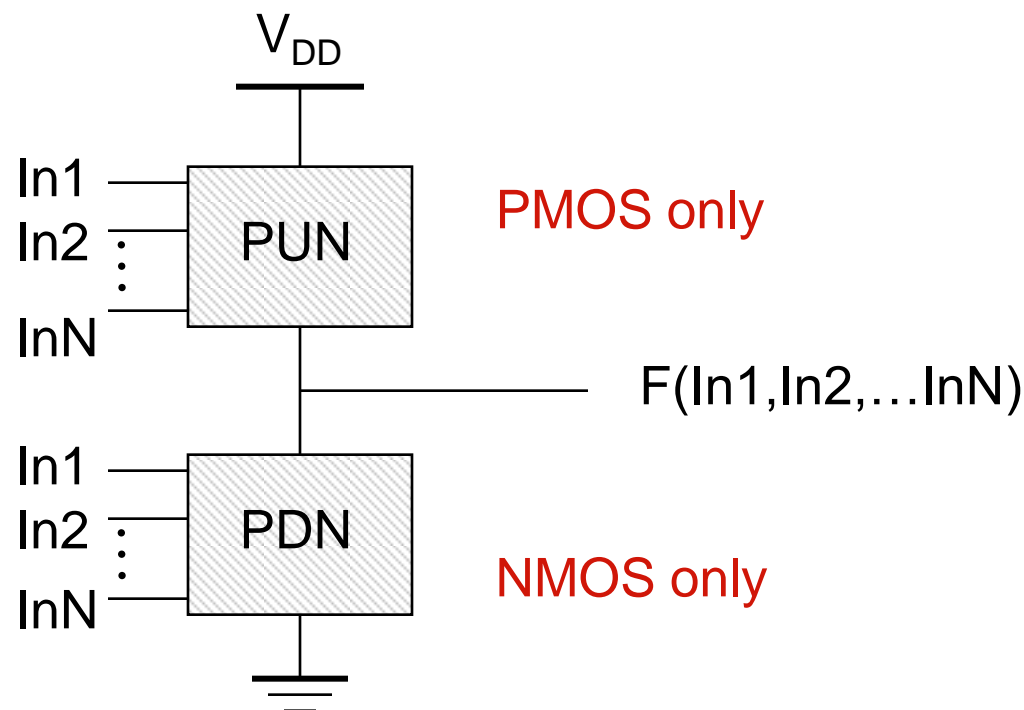

PUN and PDN are **dual** logic networks

NMOS Transistors in Series/Parallel Connection

 
 
Transistors can be thought as a switch controlled by its gate signal
NMOS switch closes when switch control input is high



NMOS Transistors pass a “strong” 0 but a “weak” 1

PMOS Transistors in Series/Parallel Connection

  PMOS switch closes when switch control input is low




PMOS Transistors pass a “strong” 1 but a “weak” 0

Example Gate: NAND

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

Truth Table of a 2 input NAND gate

 

PDN: $G = A B \Rightarrow$ Conduction to GND


PUN: $F = \overline{A} + \overline{B} = \overline{AB} \Rightarrow$ Conduction to V_{DD}

$$\overline{G(In_1, In_2, In_3, \dots)} \equiv F(\overline{In_1}, \overline{In_2}, \overline{In_3}, \dots)$$


Example Gate: NOR

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

Truth Table of a 2 input NOR gate

 


Full-Adder

 


A	B	C_i	S	C_o
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

The Binary Adder

 


$$\begin{aligned} S &= A \oplus B \oplus C_i \\ &= A\bar{B}\bar{C}_i + \bar{A}B\bar{C}_i + \bar{A}\bar{B}C_i + ABC_i \\ C_o &= AB + BC_i + AC_i \end{aligned}$$

Complimentary Static CMOS Full Adder

 


28 Transistors

The Ripple-Carry Adder

 

SRAM Memory cell

 

The add-up

32-bit adder:	>3,000
32-bit comparator:	>3,000
32-bit multiplier:	>50,000
1k SRAM:	6,000
...	

Design Metrics

- How to evaluate performance of a digital circuit (gate, block, ...)?
 - Cost
 - Reliability
 - Scalability
 - Speed (delay, operating frequency)
 - Power dissipation
 - Energy to perform a function

Future Design Challenges

- ❑ Processor architecture (multiple-core; interconnections)
- ❑ Semi-conductor materials (current leakage; process variation)
- ❑ Power consumption (power density; thermal dissipation)


Career in VLSI design

VLSI circuit design and design automation

- Intel, IBM, AMD, Texas Ins., Agilent,...
- Qualcomm, Broadcom, Samsung,...
- Micron, Seagate, WesternDigital...
- Cadence, Synopsys, MentorGraphics...
- Xilinx, Altera,
-

VLSI Design: FFT Butterfly

 - ❑ Widely used in signal processing
- ❑ Design Butterfly Unit for 2-point FFT
- ❑ Components include multiplier, adder, subtractor, and data management




8-point FFT composed of 12 butterflies

Image from www.cmlab.csie.ntu.edu.tw/cml/dsp/training/coding/transform/fft.html

By: Spencer Strunic
Matt Webb

FFT Butterfly Unit Layout

 

VLSI Design: 8-bit CPU

□ Registers

- Store data
- Manipulate data

□ ALU

- Select between many different operations to output

□ Adder


- Adds two 8-bit numbers

□ Multiplier

- Multiplies two 8-bit numbers

By: Brian Linder
Matt Leines

8-bit CPU Layout

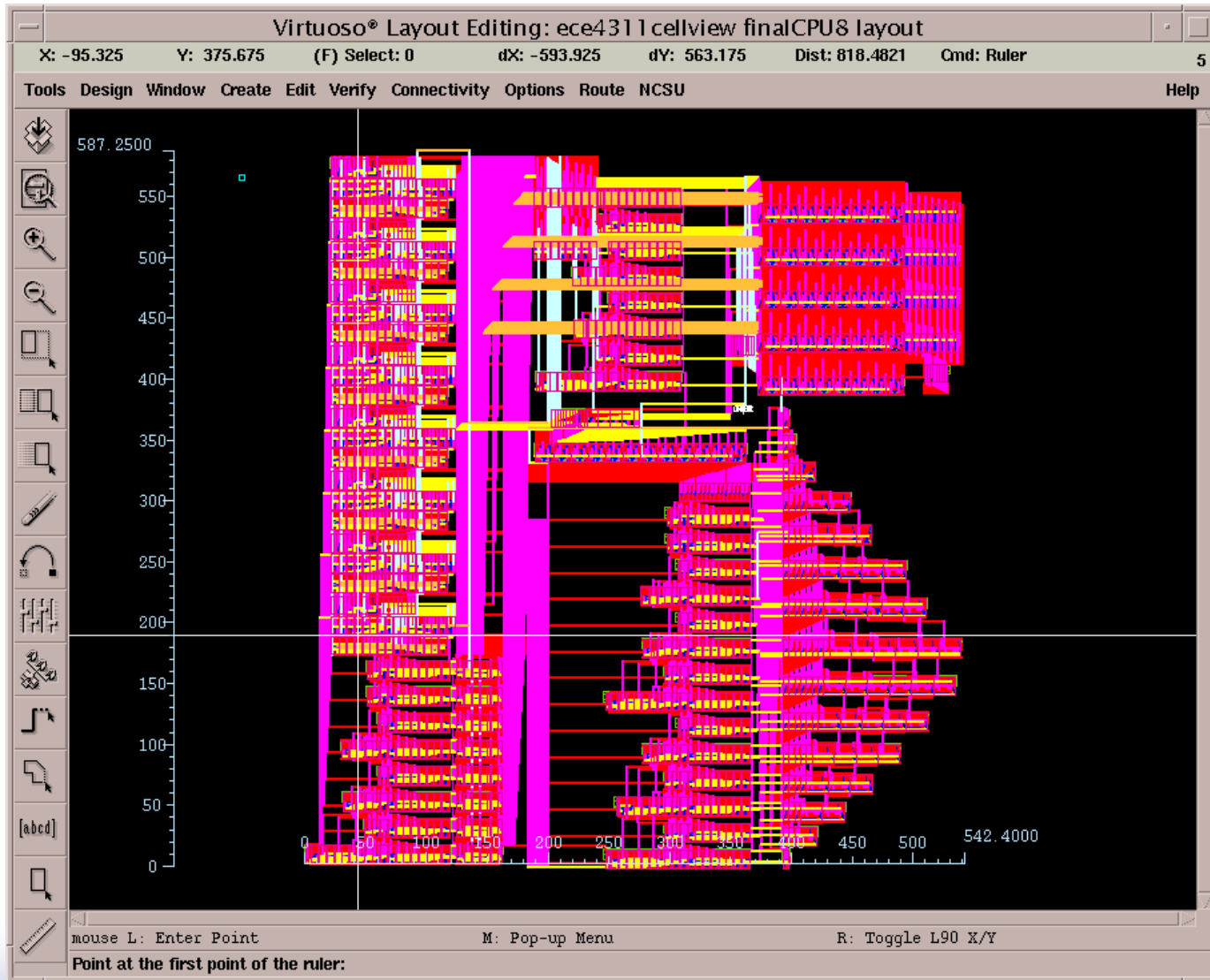

FIR Filter


- FIR – Finite-Impulse Response
- Involves calculations of finite convolution sums in discrete-time systems
- Useful for Digital Signal Processing
- Equation -

$$y[n] = \sum_{k=0}^{N-1} h[k]x[n - k]$$

- x is the input signal, h is the finite impulse response, y is the sum output and N is the order of the filter

By: Craig Bristow
Joliot Chu

FIR Filter System Design

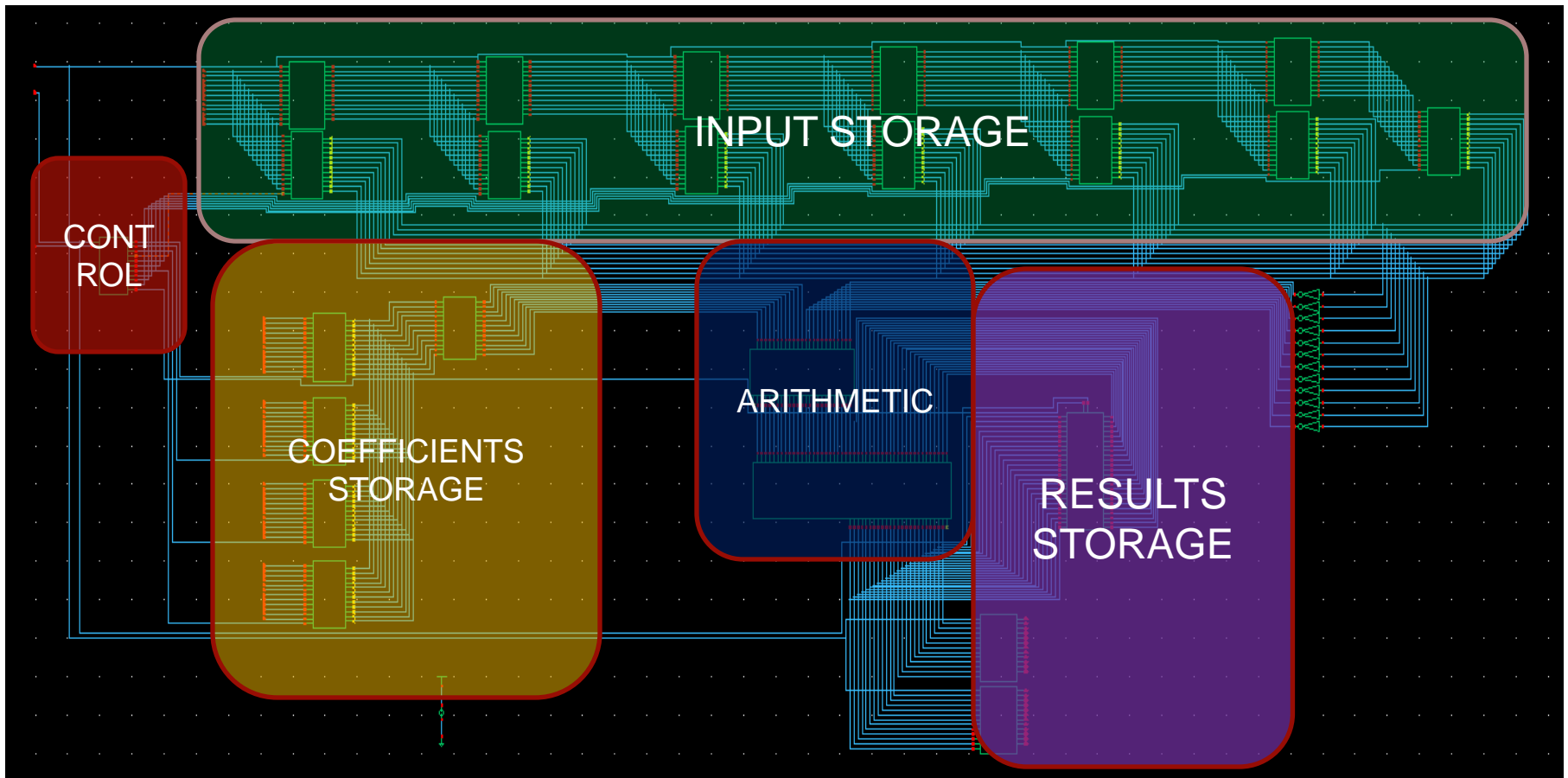

Module 1 – Control Module



Module 2 – Input Module

Module 3 – Coefficients Module



Module 4 – Arithmetic Module

Module 5 – Results Storage

A Delta-Sigma Converter for WCDMA

 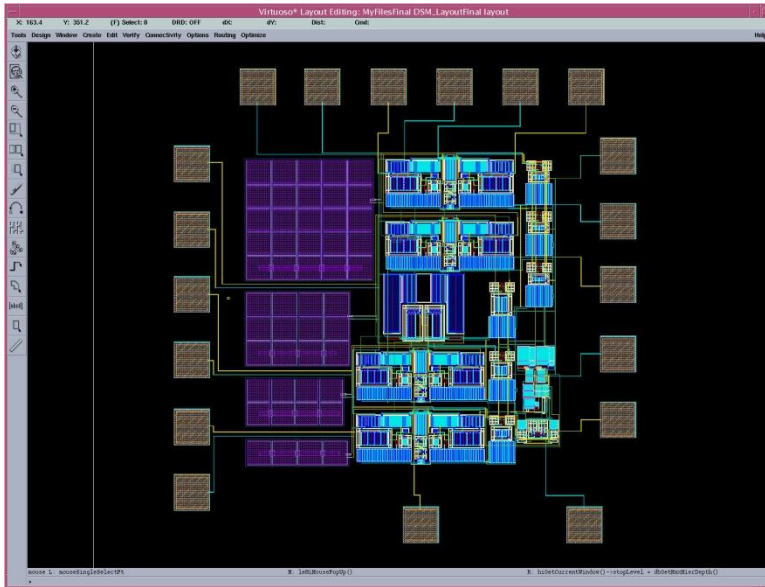


  Nowdays, many electronic systems on a single chip have both analog and digital (called Mixed-signal SoC (System on Chip))



From Texas Instruments

Why A-D Interface?

 

- Nature is analog, not digital.
- A-D interface's role is “translator”.

Contact Information:

Office: MWAH 276

Hour: 3-5pm MW

Phone: 726-7095

Email: htang@d.umn.edu

Http: www.d.umn.edu/~htang