

Arithmetic Logic Unit (ALU)

Introduction to Computer
Yung-Yu Chuang

with slides by Sedgewick & Wayne (introcs.cs.princeton.edu), Nisan & Schocken (www.nand2tetris.org) and Harris & Harris (DDCA)

Let's Make an Adder Circuit

Goal. $x + y = z$ for 4-bit integers.

- We build 4-bit adder: 9 inputs, 4 outputs.
- Same idea scales to 128-bit adder.
- Key computer component.

	1	1	1	0
	2	4	8	7
+	3	5	7	9
	6	0	6	6

Binary addition

Assuming a 4-bit system:

$$\begin{array}{r} 0\ 0\ 0\ 1 \\ 1\ 0\ 0\ 1 \\ 0\ 1\ 0\ 1 \\ \hline \end{array} +$$

0 1 1 1 0

no overflow

$$\begin{array}{r} 1\ 1\ 1\ 1 \\ 1\ 0\ 1\ 1 \\ 0\ 1\ 1\ 1 \\ \hline \end{array} +$$

1 0 0 1 0

overflow

- Algorithm: exactly the same as in decimal addition
- Overflow (MSB carry) has to be dealt with.

Representing negative numbers (4-bit system)

0	0000		
1	0001	1111	-1
2	0010	1110	-2
3	0011	1101	-3
4	0100	1100	-4
5	0101	1011	-5
6	0110	1010	-6
7	0111	1001	-7
		1000	-8


- The codes of all positive numbers begin with a "0"
- The codes of all negative numbers begin with a "1"
- To convert a number: leave all trailing 0's and first 1 intact, and flip all the remaining bits

Example: $2 - 5 = 2 + (-5) =$ 0 0 1 0

$$\begin{array}{r} + 1\ 0\ 1\ 1 \\ \hline 1\ 1\ 0\ 1 \end{array} = -3$$

Let's Make an Adder Circuit

 Step 1. Represent input and output in binary.



5

Let's Make an Adder Circuit

Goal. $x + y = z$ for 4-bit integers.

	c_{out}				c_{in}
		x_3	x_2	x_1	x_0
+		y_3	y_2	y_1	y_0
		z_3	z_2	z_1	z_0

Step 2. [first attempt]

• Build truth table.

4-Bit Adder Truth Table

c_0	x_3	x_2	x_1	x_0	y_3	y_2	y_1	y_0	z_3	z_2	z_1	z_0
0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	0	0	1	1	0	0	1	1	0
0	0	0	0	0	1	0	0	0	1	0	0	1
.
1	1	1	1	1	1	1	1	1	1	1	1	1

} $2^{8+1} = 512$ rows!

Q. Why is this a bad idea?

A. 128-bit adder: 2^{256+1} rows \gg # electrons in universe!


6

1-bit half adder

We add numbers one bit at a time.




x	y	s	c

 

7


1-bit full adder

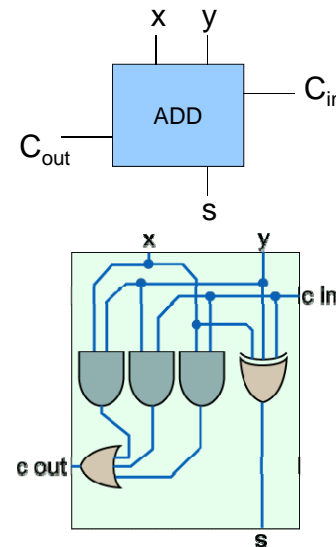

x	y	c_{in}	c_{out}	s

8

8-bit adder

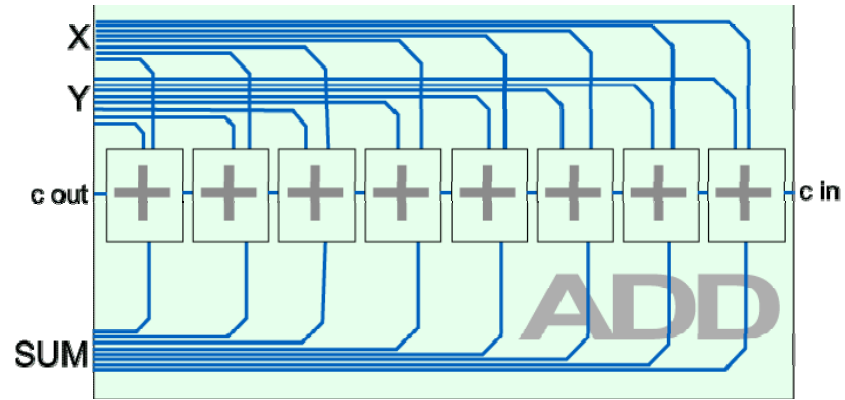

9

Let's Make an Adder Circuit

Goal. $x + y = z$ for 4-bit integers. $c_{out} \ c_3 \ c_2 \ c_1 \ c_0 = 0$

	c_3	c_2	c_1	$c_0 = 0$
x_3	x_2	x_1	x_0	
$+$	y_3	y_2	y_1	y_0
	z_3	z_2	z_1	z_0

Step 2. [do one bit at a time]

- Build truth table for carry bit.
- Build truth table for summand bit.

Carry Bit

x_i	y_i	c_i	c_{i+1}
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Summand Bit

x_i	y_i	c_i	z_i
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

10

Let's Make an Adder Circuit

Goal. $x + y = z$ for 4-bit integers.

Step 3.

- Derive (simplified) Boolean expression.

Carry Bit

x_i	y_i	c_i	c_{i+1}	MAJ
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	1	1
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

Summand Bit

x_i	y_i	c_i	z_i	ODD
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1


11

Let's Make an Adder Circuit

Goal. $x + y = z$ for 4-bit integers.


Step 4.

 - Transform Boolean expression into circuit.
- Chain together 1-bit adders.




12


Adder: Interface

 

Adder: Component Level View

 

Adder: Switch Level View

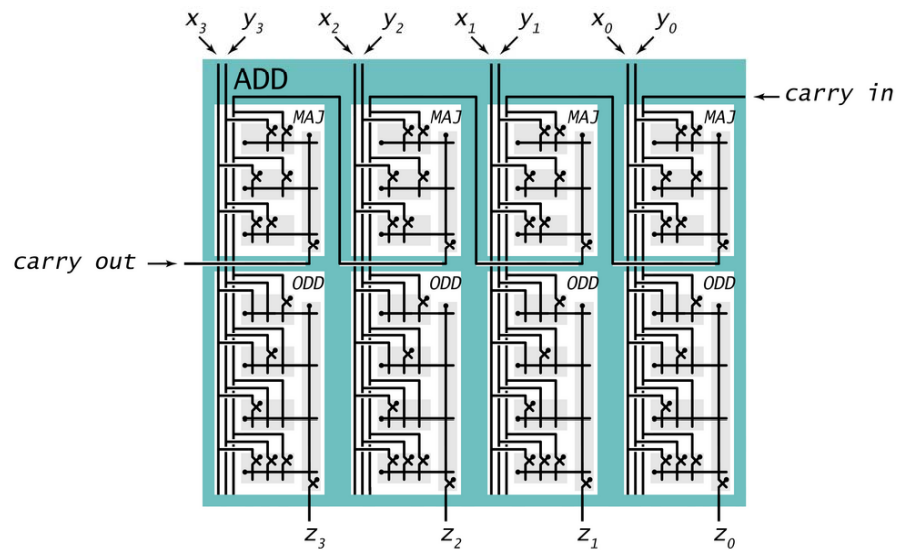

Subtractor

Subtractor circuit: $z = x - y$.

- One approach: design like adder circuit

Subtractor

Subtractor circuit: $z = x - y$.


- One approach: design like adder circuit
- Better idea: reuse adder circuit
 - 2's complement: to negate an integer, flip bits, then add 1

17


Subtractor

Subtractor circuit: $z = x - y$.

 - One approach: design like adder circuit
- Better idea: reuse adder circuit
 - 2's complement: to negate an integer, flip bits, then add 1



4-Bit Subtractor Interface

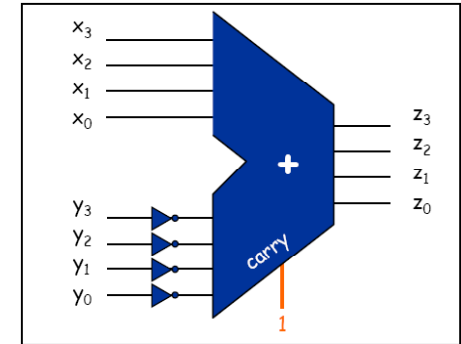


4-Bit Subtractor Implementation

18

Shifter

Only one of them will be on at a time.

 

4-bit Shifter

19

Shifter

	z_0	z_1	z_2	z_3
s_0				
s_1				
s_2				
s_3				

20


Shifter

	z_0	z_1	z_2	z_3
s_0	x_0	x_1	x_2	x_3
s_1	0	x_0	x_1	x_2
s_2	0	0	x_0	x_1
s_3	0	0	0	x_0

$$\begin{aligned} z_0 &= s_0 \cdot x_0 + s_1 \cdot 0 + s_2 \cdot 0 + s_3 \cdot 0 \\ z_1 &= s_0 \cdot x_1 + s_1 \cdot x_0 + s_2 \cdot 0 + s_3 \cdot 0 \\ z_2 &= s_0 \cdot x_2 + s_1 \cdot x_1 + s_2 \cdot x_0 + s_3 \cdot 0 \\ z_3 &= s_0 \cdot x_3 + s_1 \cdot x_2 + s_2 \cdot x_1 + s_3 \cdot x_0 \end{aligned}$$

21

Shifter

 

Right-shifter


$$\begin{aligned} z_0 &= s_0 \cdot x_0 + s_1 \cdot 0 + s_2 \cdot 0 + s_3 \cdot 0 \\ z_1 &= s_0 \cdot x_1 + s_1 \cdot x_0 + s_2 \cdot 0 + s_3 \cdot 0 \\ z_2 &= s_0 \cdot x_2 + s_1 \cdot x_1 + s_2 \cdot x_0 + s_3 \cdot 0 \\ z_3 &= s_0 \cdot x_3 + s_1 \cdot x_2 + s_2 \cdot x_1 + s_3 \cdot x_0 \end{aligned}$$

22


N-bit Decoder

N-bit decoder

 - N address inputs, 2^N data outputs
- Address output bit is 1; all others are 0



3-bit Decoder Interface

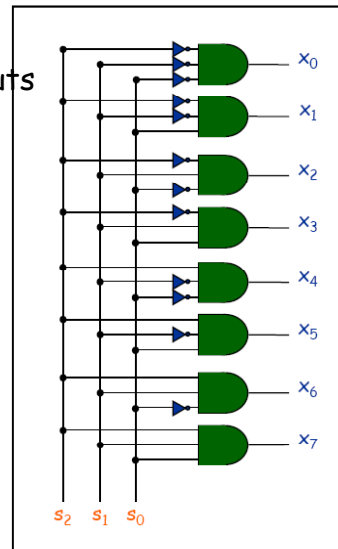


3-bit Decoder Implementation

23


N-bit Decoder

N-bit decoder

 - N address inputs, 2^N data outputs
- Address output bit is 1; all others are 0



3-bit Decoder Interface

 


Decoder

24

2-Bit Decoder Controlling 4-Bit Shifter

 Ex. Put in a binary amount r_0r_1 to shift.



Right-shifter with decoder

25

Arithmetic Logic Unit

Arithmetic logic unit (ALU). Computes all operations in parallel.

- Add and subtract.
- Xor.
- And.
- Shift left or right.

Q. How to select desired answer?

26

1 Hot OR


1 hot OR.

- All devices compute their answer; we pick one.
- Exactly one select line is on.
- Implies exactly one output line is relevant.

$$x \cdot 1 = x$$

$$x \cdot 0 = 0$$


$$x + 0 = x$$

 

Output select with one-hot OR

27

1 Hot OR

 


28

Bus


16-bit bus

 - Bundle of 16 wires
- Memory transfer
- Register transfer



8-bit bus

- Bundle of 8 wires
- TOY memory address

 

4-bit bus

- Bundle of 4 wires
- TOY register address




29


Bitwise AND, XOR, NOT

Bitwise logical operations

 - Inputs x and y : n bits each
- Output z : n bits
- Apply logical operation to each corresponding pair of bits



Bitwise And Interface

 

Bitwise And Implementation


30

TOY ALU

TOY ALU

- Big combinational logic
- 16-bit bus
- Add, subtract, and, xor, shift left, shift right.

op	2	1	0
+, -	0	0	0
&	0	0	1
^	0	1	0
<<, >>	0	1	1
input 2	1	0	0

 

31

Device Interface Using Buses


16-bit words for TOY memory

Device. Processes a word at a time.

Input bus. Wires on top.

Output bus. Wires on bottom.

Control. Individual wires on side.

 

32

ALU


Arithmetic logic unit.

- Add and subtract.
- Xor.
- And.
- Shift left or right.


Arithmetic logic unit.

- Computes all operations in parallel.
- Uses 1-hot OR to pick each bit answer.

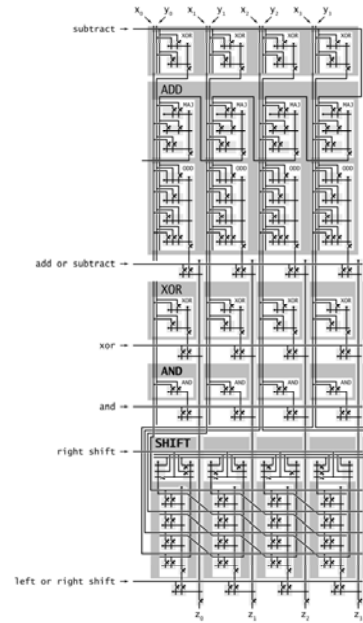
How to convert opcode to 1-hot OR signal?



33


 


34

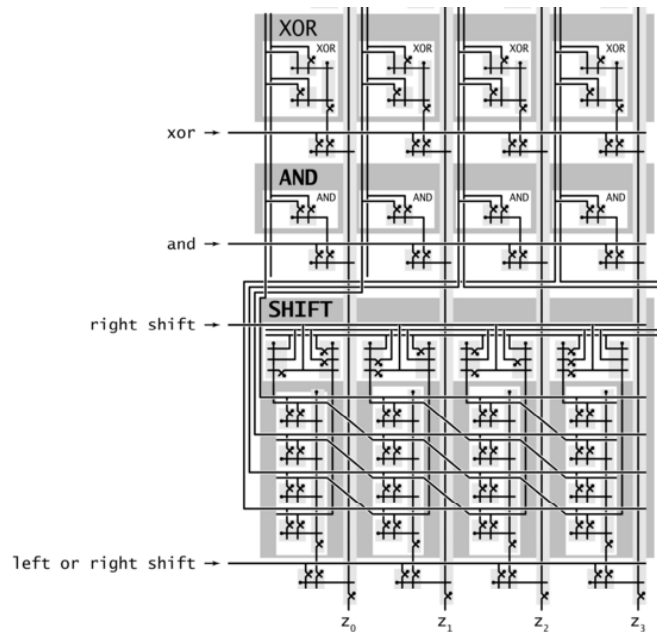

35

Hack ALU

  


$out(x, y, control\ bits) =$

- $x+y, x-y, y-x,$
- $0, 1, -1,$
- $x, y, -x, -y,$
- $x!, y!,$
- $x+1, y+1, x-1, y-1,$
- $x\&y, x|y$

Hack ALU

These bits instruct how to preset the x input		These bits instruct how to preset the y input		This bit selects between + / And	This bit inst. how to postset out	Resulting ALU output
zx	nx	zy	ny	f	no	out=
if zx then x=0	if nx then x=!x	if zy then y=0	if ny then y=!y	if f then out=x+y else out=x&y	if no then out=!out	f(x,y)=
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	-1
0	0	1	1	0	0	x
1	1	0	0	0	0	y
0	0	1	1	0	1	!x
1	1	0	0	0	1	!y
0	0	1	1	1	1	-x
1	1	0	0	1	1	-y
0	1	1	1	1	1	x+1
1	1	0	1	1	1	y+1
0	0	1	1	1	0	x-1
1	1	0	0	1	0	y-1
0	0	0	0	1	0	x+y
0	1	0	0	1	1	x-y
0	0	0	1	1	1	y-x
0	0	0	0	0	0	x&y
0	1	0	1	0	1	x y

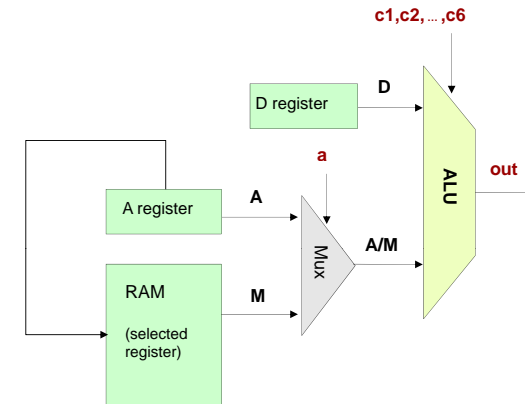The ALU in the CPU context (a sneak preview of the Hack platform)



Perspective

- Combinational logic
- Our adder design is very basic: no parallelism
- It pays to optimize adders
- Our ALU is also very basic: no multiplication, no division
- Where is the seat of more advanced math operations?
a typical hardware/software tradeoff.