

CANARA

ENGINEERING COLLEGE

Benjanapadavu, Mangalore-574219



Subject
Code:
10ESL37

ANALOG ELECTRONICS LAB MANUAL



DEPARTMENT OF
ELECTRONICS & COMMUNICATION
ENGINEERING

CONTENTS

<i>Sl. No.</i>	<i>Experiments</i>	<i>Page No.</i>
1	Diode Clipping Circuits	2
2	Clamping Circuits	10
3	Rectifier Circuits	16
4	RC-Coupled Amplifier	24
5	Darlington Emitter Follower	29
6	R.C. Phase Shift Oscillator	33
7	Verification of Network Theorems	36
8	Series & Parallel Resonance Circuits	40
9	Voltage Series Feedback Amplifier	44
10	Class 'B' Push-Pull Amplifier	49
11	Crystal Oscillator	51
12	FET Hartley & Colpitts Oscillator	53
	Viva Questions	57
	Bibliography	60

For more information and queries visit:
www.ajaybolar.weebly.com

DIODE CLIPPING CIRCUITS



Aim: To design and test diode clipping circuits for peak clipping and peak detection.


Components required:

- Power Supply
- Diodes IN4007or BY127
- Resistors

Procedure:

- Make the Connections as shown in the circuit diagram
- Apply sinusoidal input V_i of 1 KHz and of amplitude 8V P-P to the circuit.
- Observe the output signal in the CRO and verify it with given waveforms.
- Apply V_i and V_o to the X and Y channel of CRO and observe the transfer characteristic waveform and verify it.

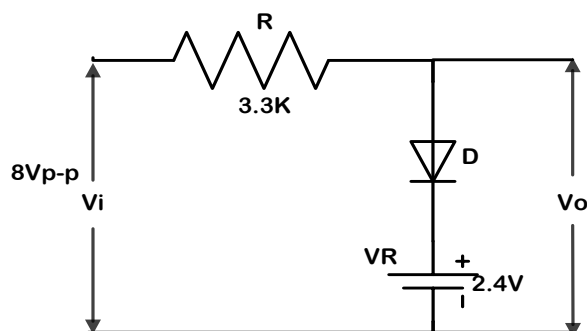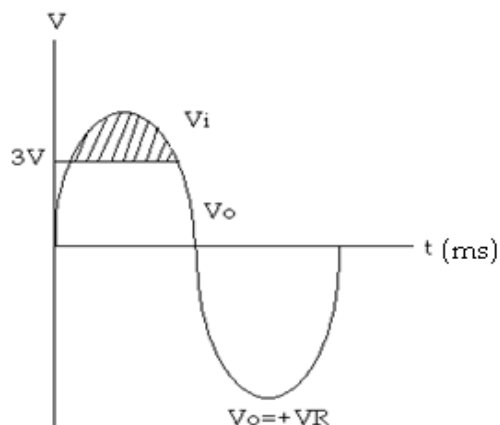I) Positive Clipping Circuit:**Circuit Diagram:****Waveforms:**

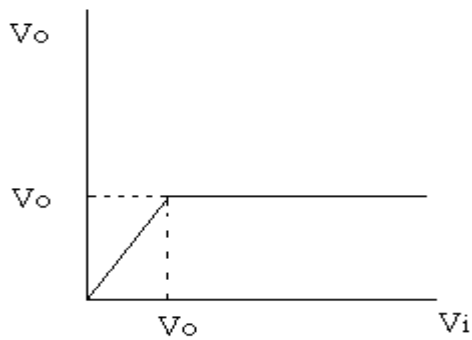Transfer Characteristics:**To find the value of R:**

Given: $R_f = 100\Omega$, $R_r = 100K\Omega$

R_f - Diode forward resistance

R_r - Diode reverse resistance

$$R = \sqrt{R_f R_r} = \sqrt{100 \times 100 \times 10^3} = 3.16K\Omega$$

Choose R as 10 K Ω

Let the output voltage be clipped at +3V

$$\therefore V_{\text{omax}} = 3V$$

From the circuit diagram,

$$V_{\text{omax}} = V_r + V_{\text{ref}}$$

Where V_r is the diode drop = 0.6V


$$\therefore V_{\text{ref}} = V_{\text{omax}} - V_r$$

$$= 3 - 0.7$$


$$\mathbf{V_{\text{ref}} = 2.3 V}$$

II) Negative Clipping Circuit:


Circuit Diagram:

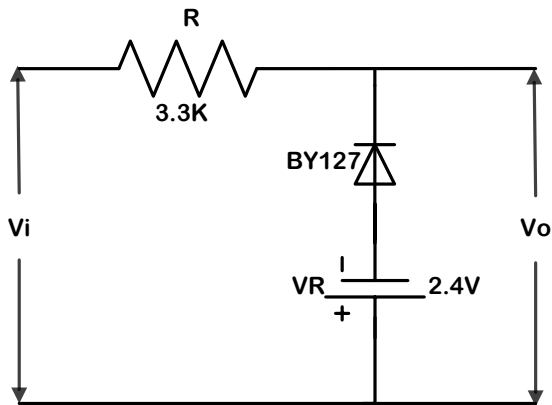

Waveforms:

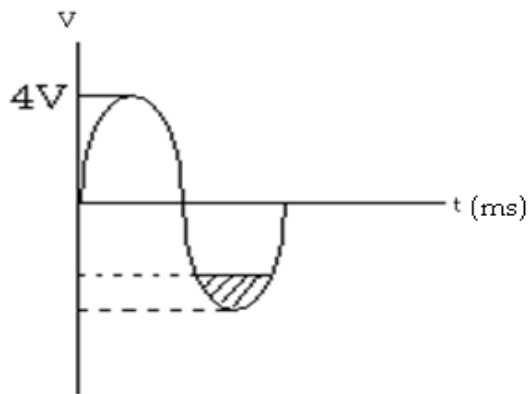

Transfer Characteristics:

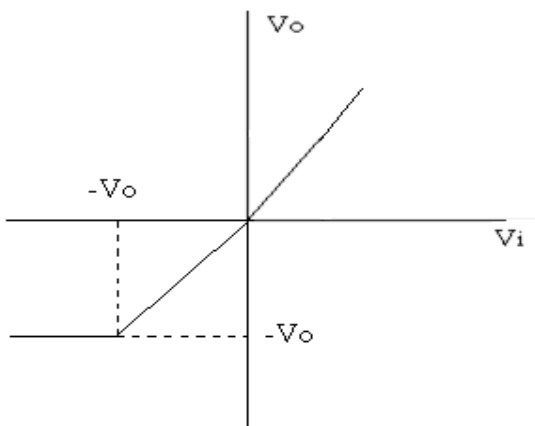

Let the output voltage be clipped at $-3V$

$$V_{\text{omin}} = -3V$$


$$V_{\text{omin}} = -V_r + V_{\text{ref}}$$

$$V_{\text{ref}} = V_{\text{omin}} + V_r = -3 + 0.7$$


$$V_{\text{ref}} = -2.3V$$

III) Diode Series Clipping/ Positive Peak Clipper:


Circuit Diagram:

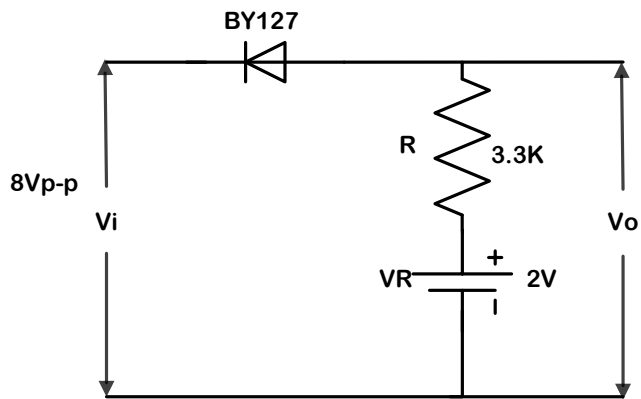

Waveforms:

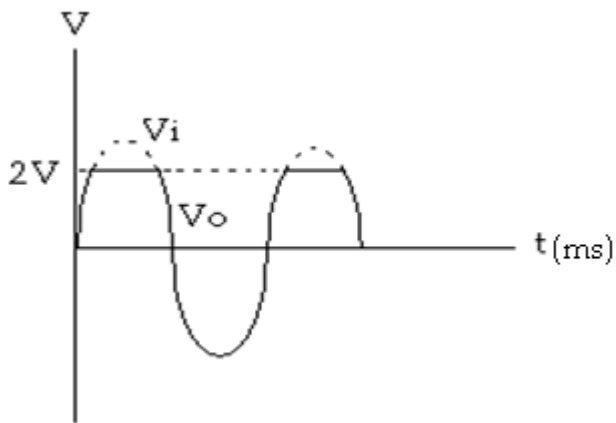

Transfer Characteristics:

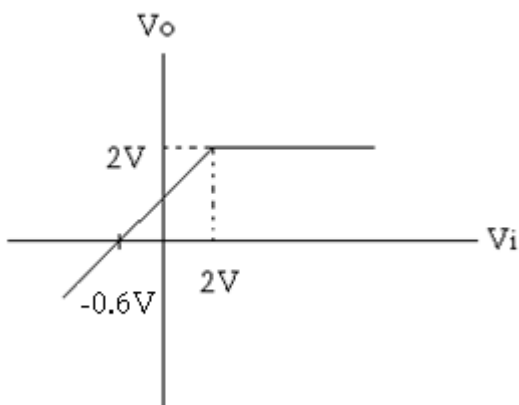


Let the output voltage be clipped at 2V


$$V_{o\max} = V_{\text{ref}} = 2V$$

IV) Negative Peak Clipper:


Circuit Diagram:

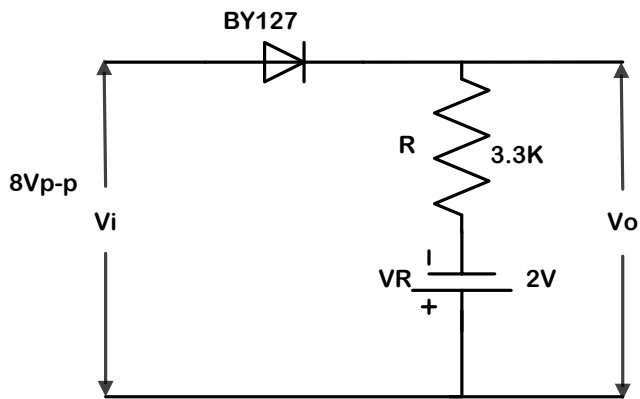

Waveforms:

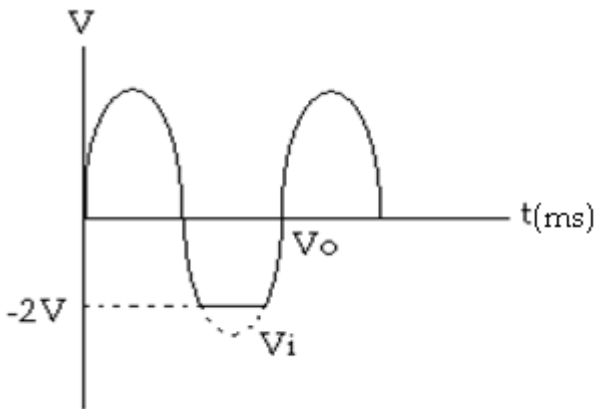

Transfer Characteristics:

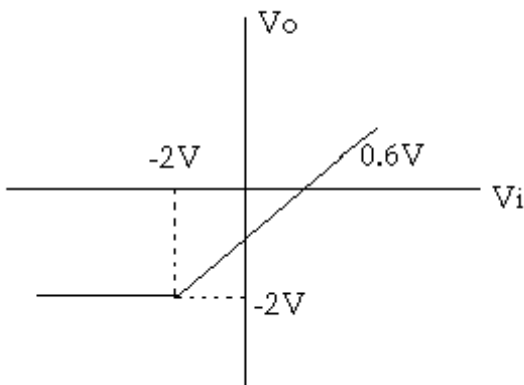


Let the output voltage be clipped at -2V


$$V_{omin} = V_{ref} = -2V$$

V) Clipping at two independent levels:


Circuit Diagram:

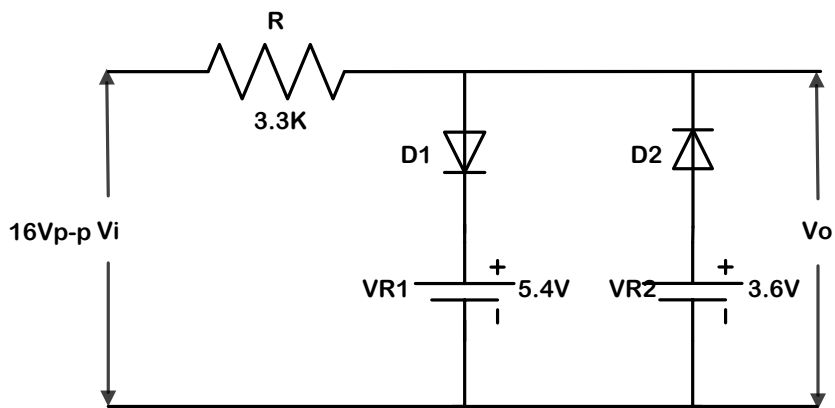

Waveforms:

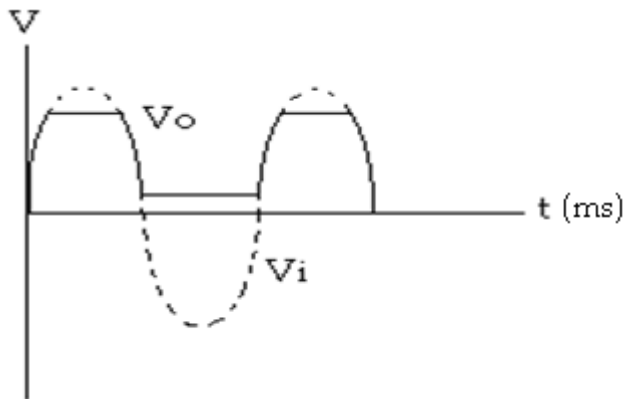

Transfer Characteristics:

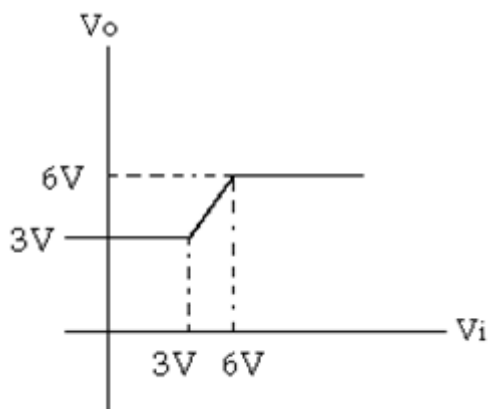

Let $V_{\text{omax}} = 6\text{V}$ and $V_{\text{omin}} = 3\text{V}$

$$\therefore V_{\text{omax}} = V_{r1} + V_r$$


$$V_{r1} = V_{\text{omax}} - V_r = 6 - 0.7 = 5.3\text{V}$$

$$V_{\text{omin}} = V_{r2} - V_r$$


$$V_{r2} = V_{\text{omin}} + V_r = 3 + 0.7 = 3.7\text{V}$$

VI) Double ended clipper to generate a symmetric square wave:


Circuit Diagram:

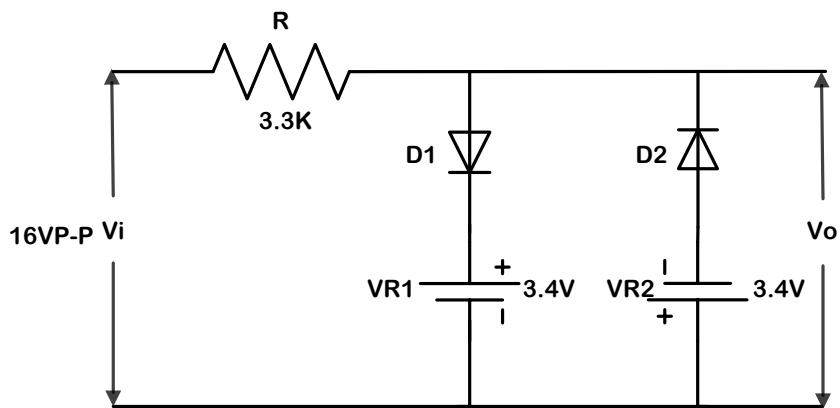

Waveforms:

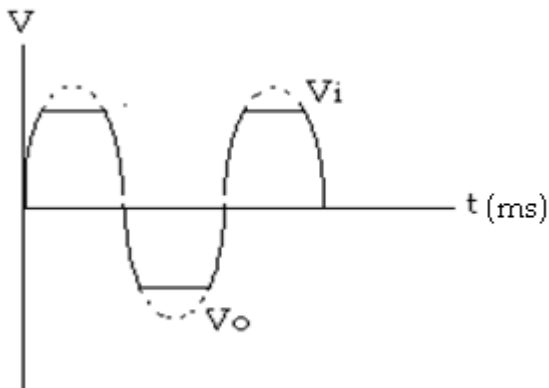

Transfer Characteristics:

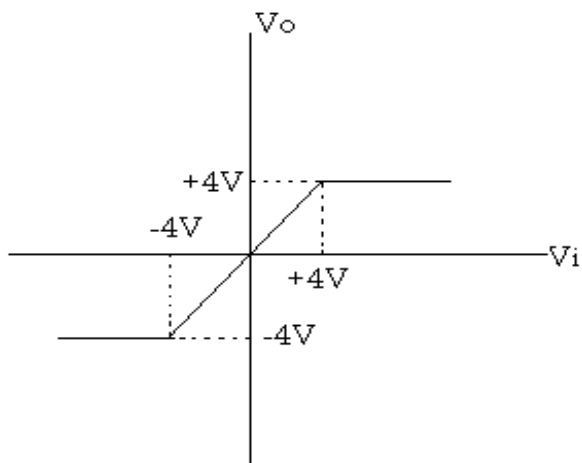

$$\text{Let } V_{R1} = V_{R2} = V_R, V_{\text{omax}} = 4V$$


$$V_{\text{omax}} = V_R + V_r$$

$$V_R = V_{\text{omax}} - V_r = 4 - 0.7$$


$$V_R = 3.3V$$

VII) To Clip a sine wave between +2V and -3V level:

Circuit Diagram:

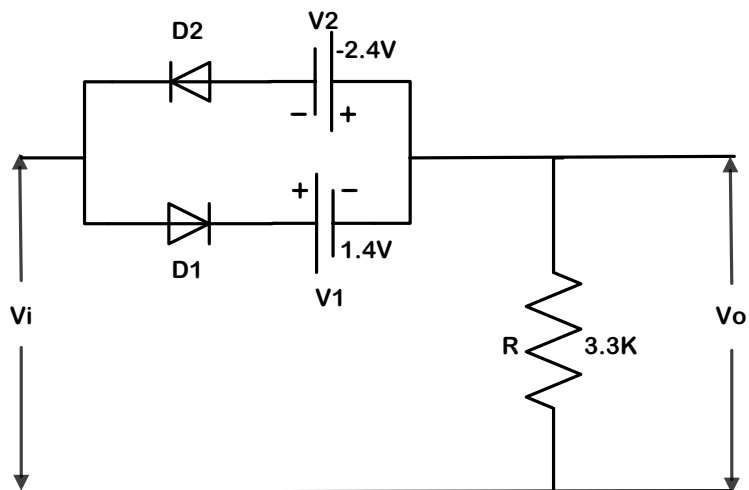

Transfer Characteristics:

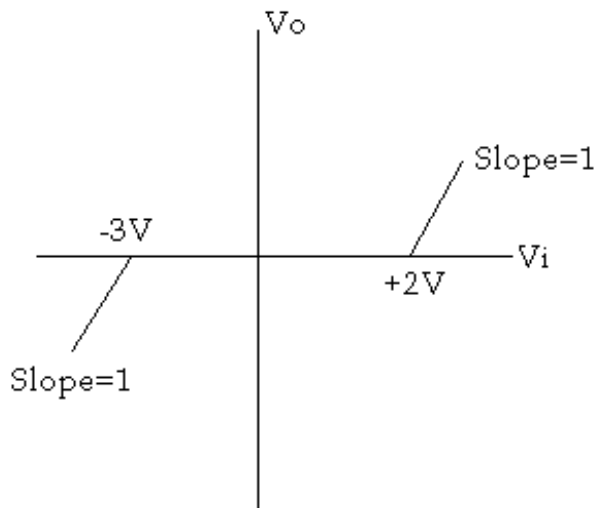

To Clip a sine wave between +2V and -3V level

$$V_o = V_1 + V_r$$

$$V_1 = V_o - V_r = 2 - 0.7$$

$$V_1 = 1.4V$$

$$V_o = V_2 - V_r$$

$$-3 = V_2 - 0.7$$

$$V_2 = -3 + 0.7$$

$$V_2 = -2.3V$$

CLAMPING CIRCUITS

Aim: Design and test positive and negative clamping circuit for a given reference voltage.

Components required:

- Power Supply
- CRO
- Signal Generator
- Diode BY 127
- Resistors
- Capacitor

Design:

R_f - Diode forward resistance = 100Ω

R_r - Diode Reverse resistance = $1M\Omega$

$$R = \sqrt{R_f R_r} = 10K\Omega$$


$RC \gg T$ let $T = 1ms$ $f(1KHz)$




Let $RC = 10T$

$RC = 10ms$

$C = 1\mu F$

$R = 10K\Omega$


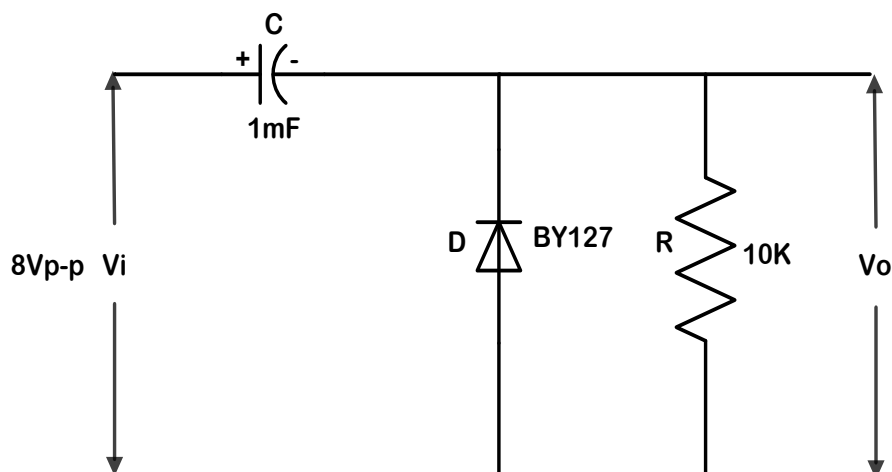
I) Positive Clamping Circuits:**Circuit Diagram:**

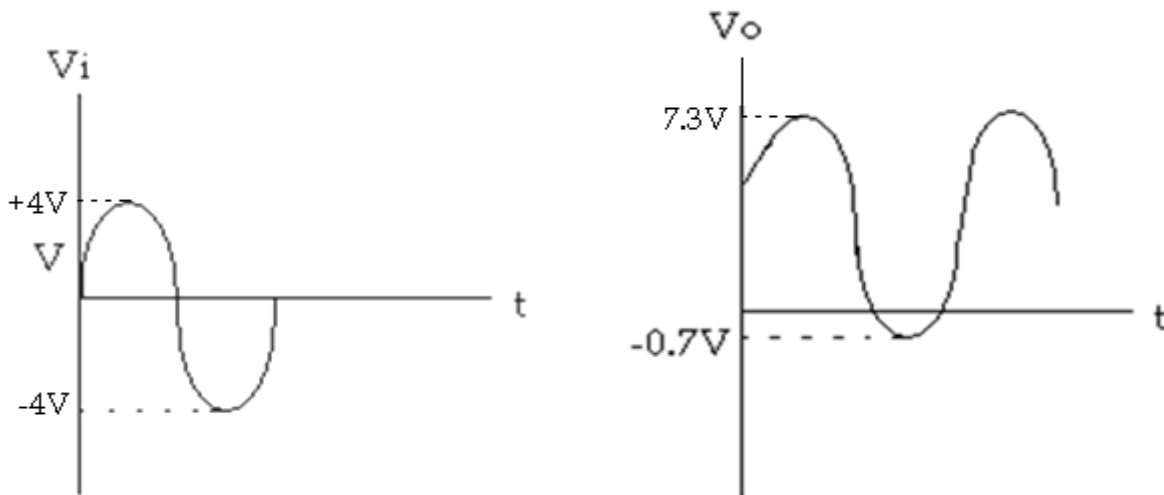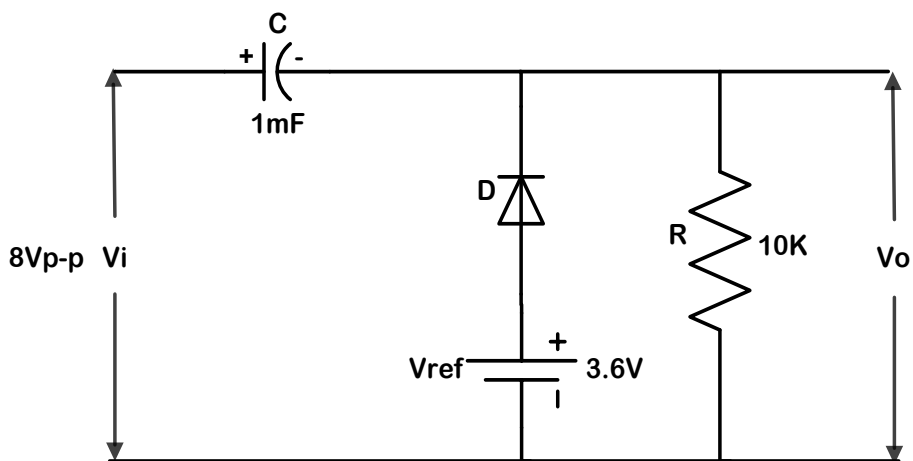
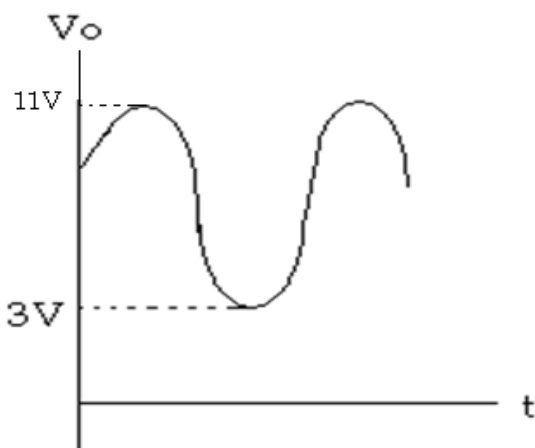
Waveforms:**II) Design a Clamping Circuit to Clamp Negative Peak at +3V:****Waveforms:**

$$V_o = V_{\theta} + V_{ref}$$

$$3 = -0.7 + V_{ref},$$

$$V_{ref} = 3.7$$

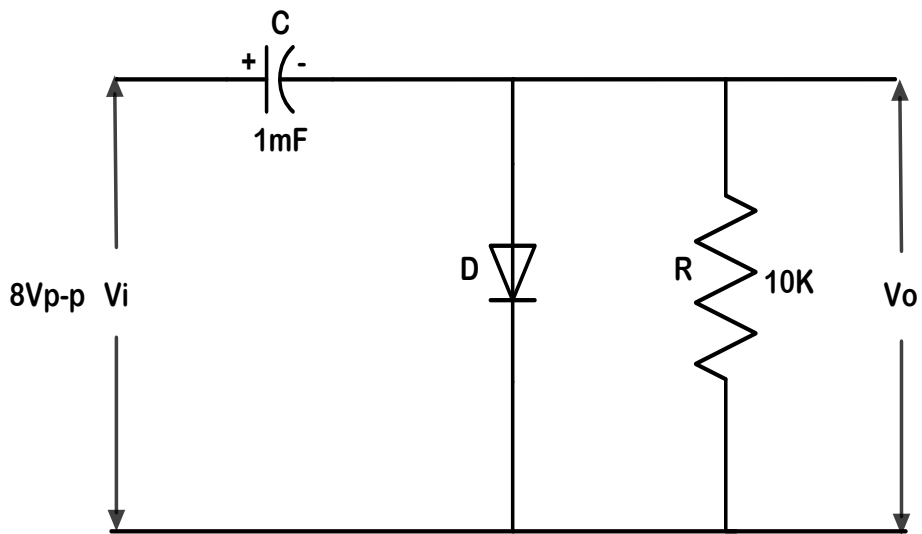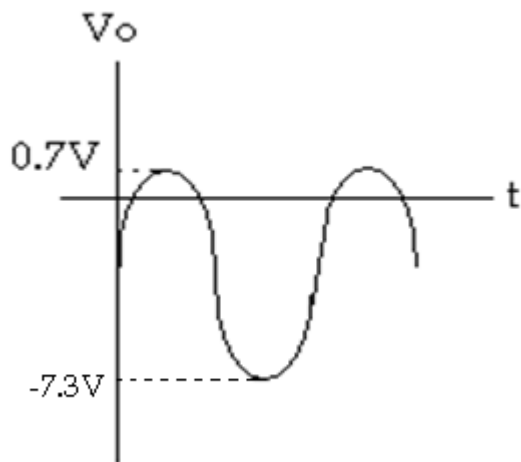III) Negative Clamping Circuit:Circuit Diagram:Waveforms:

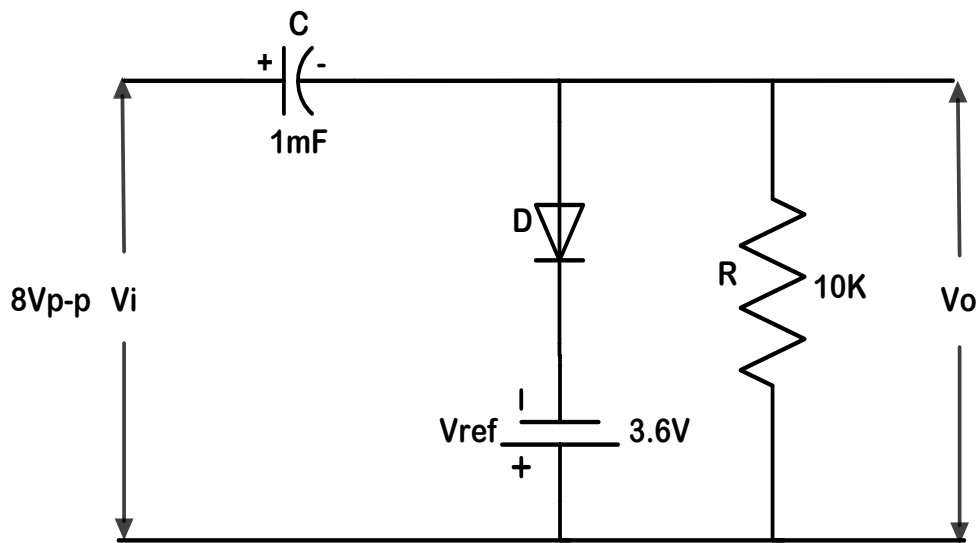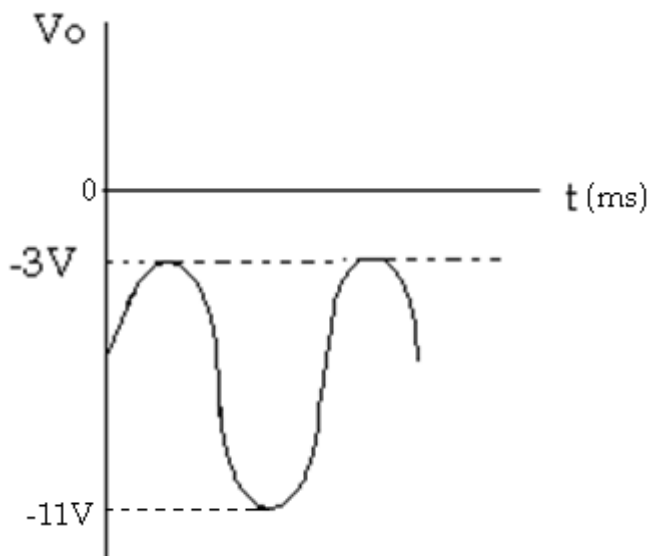IV) Design a Clamping Circuit to clamp Positive Peak at -3V:Circuit Diagram:Waveforms:

$$V_o = V_g - V_{ref}$$


$$V_{ref} = -V_o + V_g$$

$$= +3 + 0.7$$


$$V_{ref} = 3.7$$

V) Design a Clamping Circuit to Clamp Negative Peak at -3V:

Circuit Diagram:

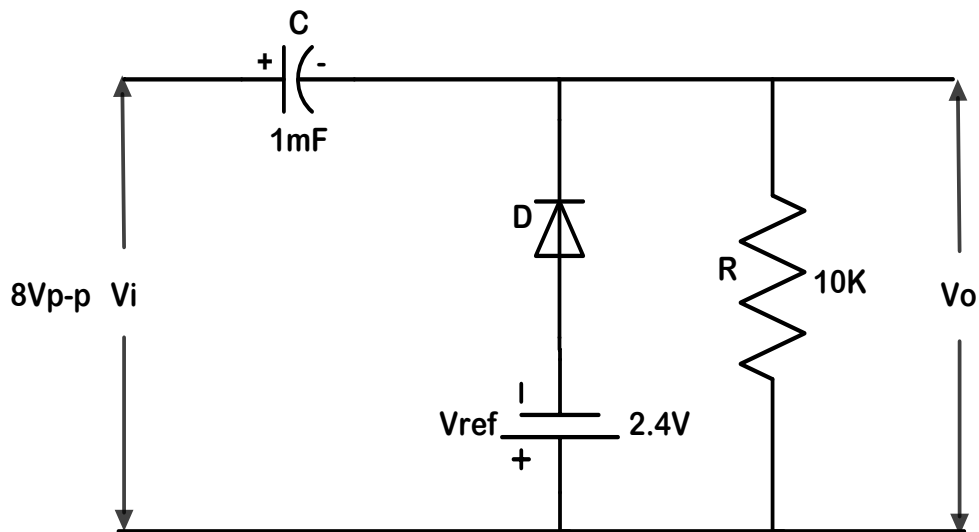

Waveforms:

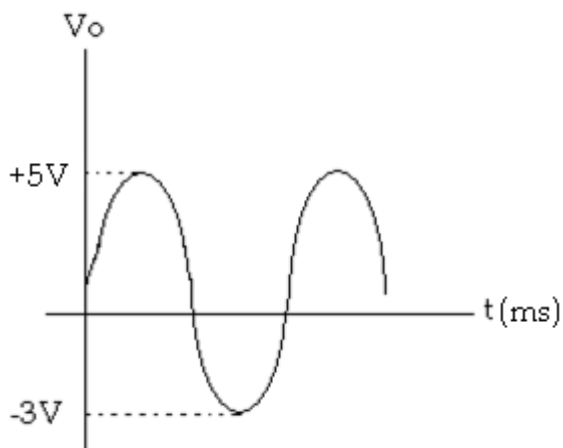

$$V_o = - (V_{\theta} + V_{ref})$$


$$V_{ref} = -V_o - V_{\theta}$$

$$= -0.7 - (-3)$$


$$V_{ref} = +2.3V$$

VI) Design a Clamping Circuit to clamp Positive Peak at +3V:

Circuit Diagram:

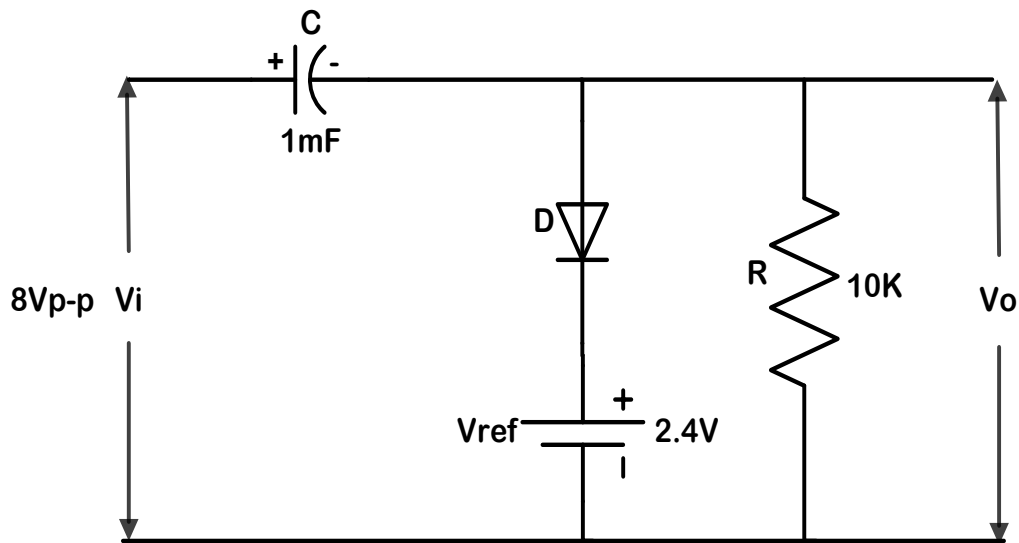

Waveforms:

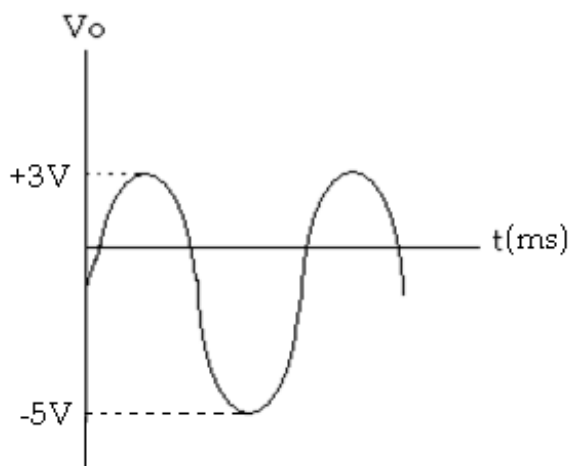

$$V_o = V_{\theta} + V_{ref}$$

$$V_{ref} = V_o - V_{\theta}$$

$$= 3 - 0.7$$

$$V_{ref} = 2.7V$$

Procedure:

- Rig up the circuit.
- Apply sinusoidal input signal of 8V P-P from signal generator.
- Observe the output waveform in the CRO.
- Note down the readings from the CRO and compare it with the expected values.

RECTIFIER CIRCUITS

Aim: To design and test Half wave, Full wave, Bridge Rectifier circuits with & without capacitor filter and determine the Ripple factor, Regulation & Efficiency.

Components required:

- Resistors
- Diodes
- 12-0-12V Transformer
- Capacitor

Calculations:

Assume $R_L = 4.7K\Omega$, $C = 220\mu F$

I) Half wave Rectifier:

1. Ripple Factor without Filter (Theoretical) = 1.21

2. Percentage Regulation = $\frac{R_f}{R_L} \times 100$ (R_f = Diode forward resistance)

3. Rectifier Efficiency $\eta = \frac{0.406}{1 + \frac{R_f}{R_L}} \simeq 40.6 \%$

4. Ripple Factor without Filter $Y = \frac{1}{2\sqrt{3} f R_L C}$ (f = frequency = 50Hz)

II) Full wave Rectifier:

1. Ripple Factor without Filter = 0.48

2. Percentage Regulation = $\frac{R_f}{R_L} \times 100$

3. Rectifier Efficiency $\eta = \frac{0.81}{1 + \frac{R_f}{R_L}} = 81 \%$

4. Ripple Factor without Filter $Y = \frac{1}{4\sqrt{3} f C R_L}$

III) Bridge Rectifier:

1. Ripple Factor without Filter = 0.48


2. Percentage Regulation = $\frac{R_f}{R_L} \times 100$

3. Rectifier Efficiency $\eta = \frac{0.81}{1 + \frac{R_f}{R_L}} = 81 \%$



4. Ripple Factor without Filter $Y = \frac{1}{4\sqrt{3} fR_L C}$

I) Half wave Rectifier without Filter:

Circuit Diagram:

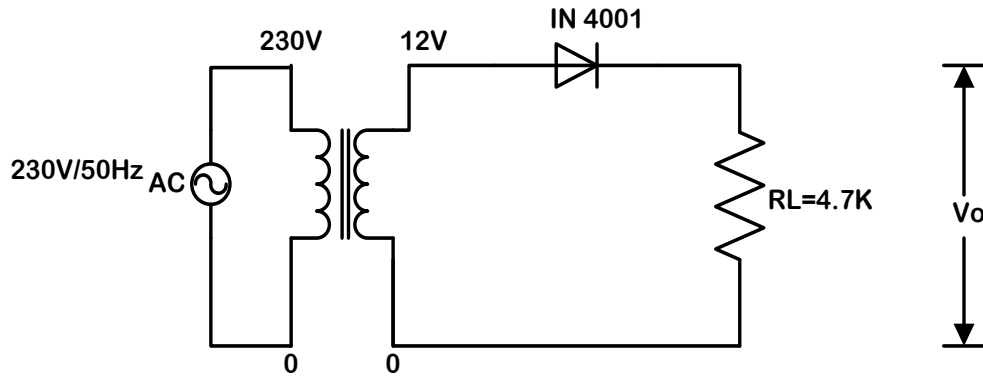

Waveforms:

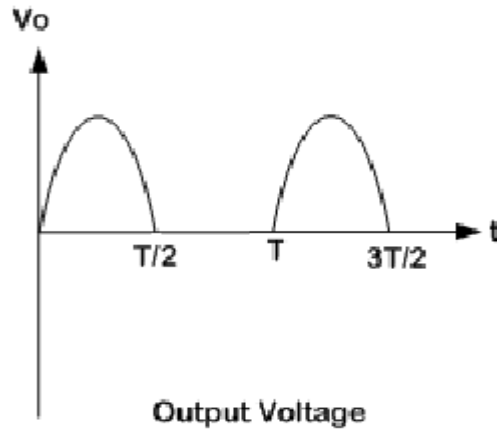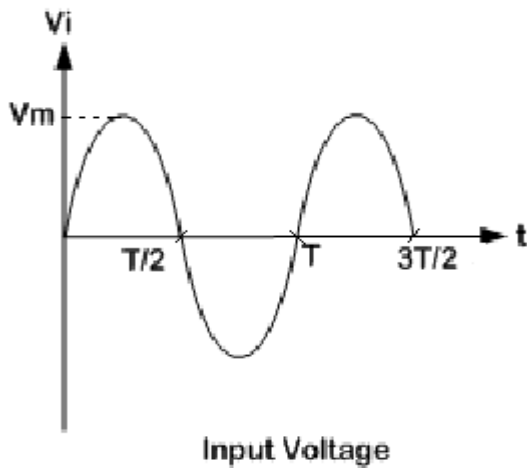

Peak output voltage $V_m =$

$$V_{dc} = \frac{V_m}{\pi} =$$

$$V_{rms} = \frac{V_m}{2} =$$


$$V_{ac} = \sqrt{V_{rms}^2 - V_{dc}^2} =$$

$$\text{Ripple Factor } Y = \frac{V_{ac}}{V_{dc}} =$$


$$\text{Rectifier efficiency } \eta = \frac{P_{dc}}{P_{ac}} = \frac{V_{dc}^2}{V_{rms}^2} =$$

$$\% \text{ Regulation} = \frac{V_{dc(NL)} - V_{dc(FL)}}{V_{dc(FL)}} \times 100 =$$

II) Half wave Rectifier with Filter:

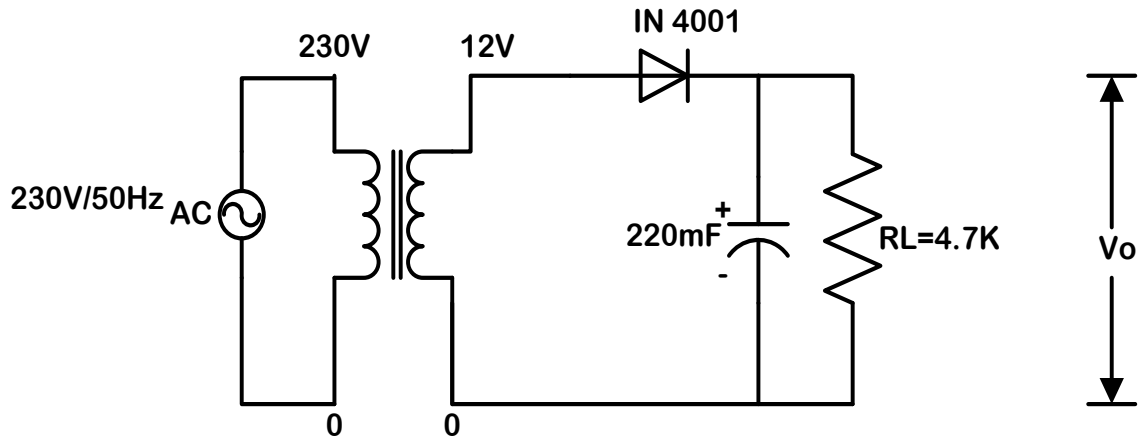

Waveforms:

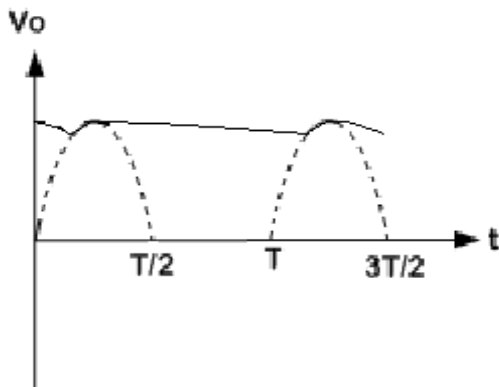

Peak output Voltage $V_m =$

$$\text{Ripple Factor} = \frac{V_{ac}}{V_{dc}} =$$

$$V_{dc} = \frac{V_m}{1 + \frac{1}{2fR_L C}} =$$

$$V_{ac} = \frac{V_{rp-p}}{2} =$$


$$V_{rms} = \sqrt{V_{dc}^2 + V_{ac}^2} =$$

$$\text{Rectifier efficiency } \eta = \frac{P_{dc}}{P_{ac}} = \left[\frac{V_{dc}}{V_{rms}} \right]^2 =$$


$$\% \text{ Regulation} = \frac{V_{dc(NL)} - V_{dc(FL)}}{V_{dc(FL)}} \times 100 =$$

III) Full wave Rectifier without Filter:

Circuit Diagram:

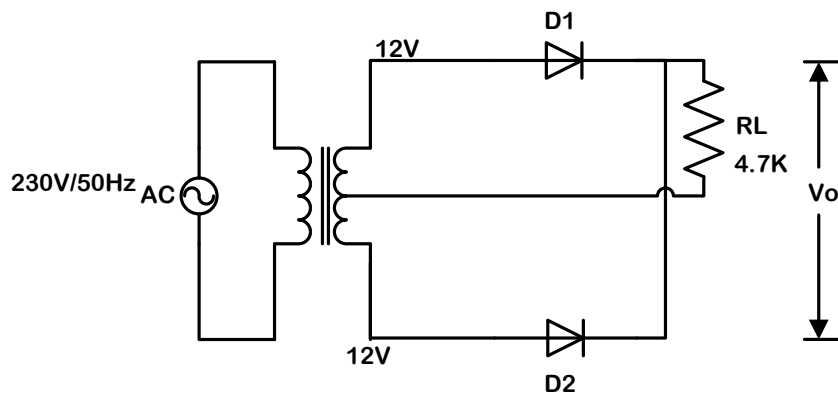

Waveforms:

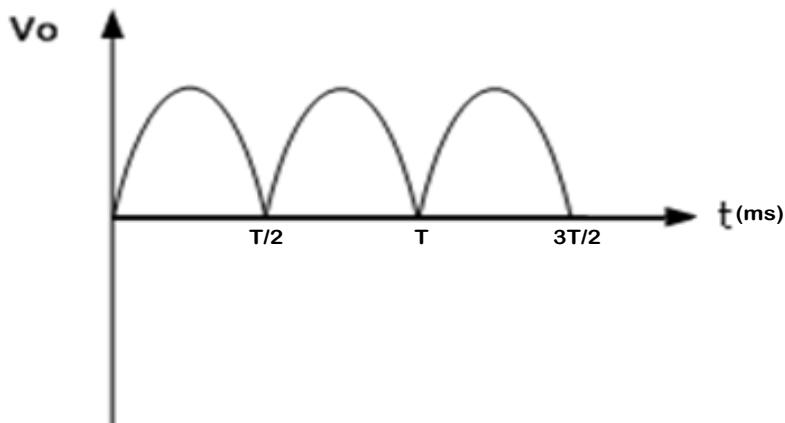

$$V_{dc} = \frac{2V_m}{\pi} =$$

$$V_{rms} = \frac{V_m}{\sqrt{2}} =$$

$$V_{ac} = \sqrt{V_{rms}^2 - V_{dc}^2} =$$


$$\gamma = \frac{V_{ac}}{V_{dc}} =$$

$$\eta = \frac{P_{dc}}{P_{ac}} = \left[\frac{V_{dc}}{V_{rms}} \right]^2 =$$


$$\% \text{ Regulation} = \frac{V_{dc(NL)} - V_{dc(FL)}}{V_{dc(FL)}} \times 100 =$$

IV) Full wave Rectifier with Filter:

Circuit Diagram:

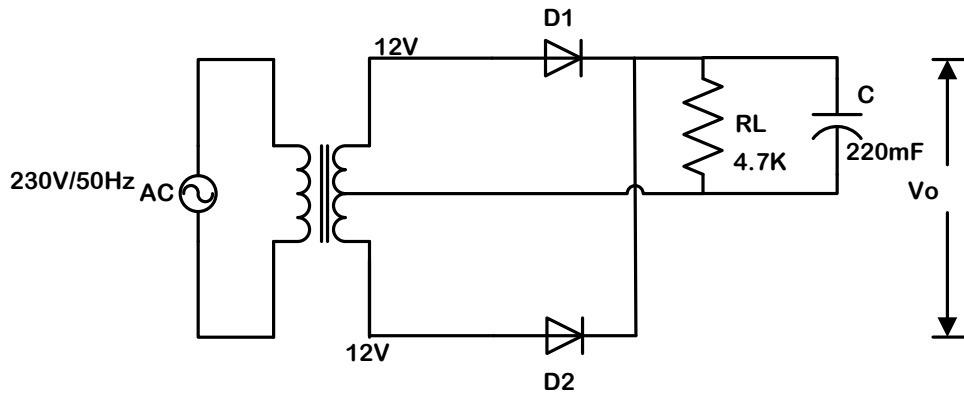

Waveforms:

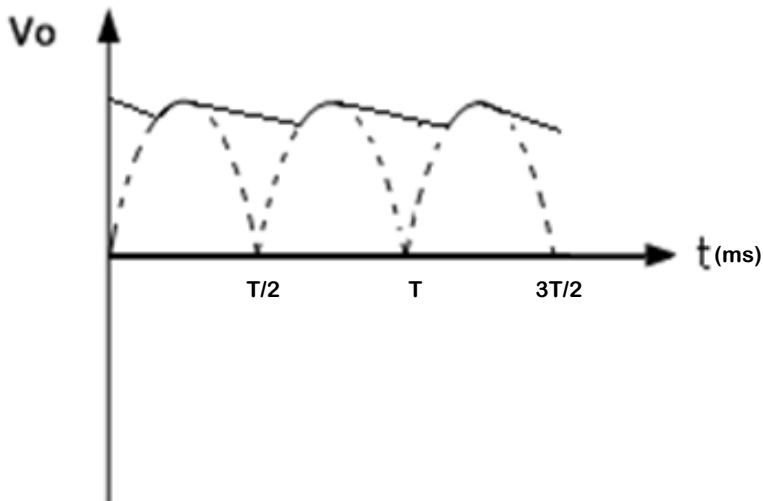

$$V_{dc} = \frac{V_m}{1 + \frac{1}{4fR_L C}} =$$

$$V_{ac} = \frac{V_r - (p-p)}{2\sqrt{3}} =$$


$$\gamma = \frac{V_{ac}}{V_{dc}} =$$

$$V_{rms} = \sqrt{V_{dc}^2 + V_{ac}^2} =$$


$$\eta = \frac{P_{dc}}{P_{ac}} = \left[\frac{V_{dc}}{V_{rms}} \right]^2 =$$

V) Bridge Rectifier without Filter:

Circuit Diagram:

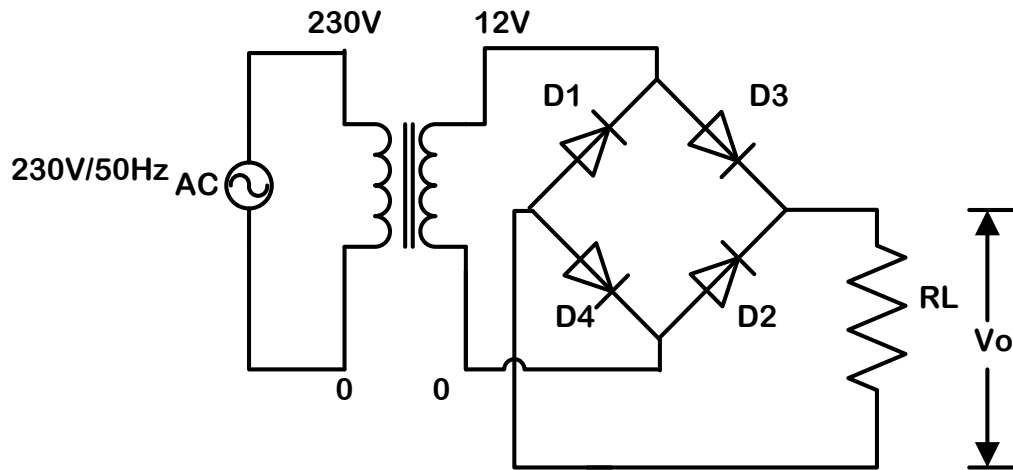

Waveforms:

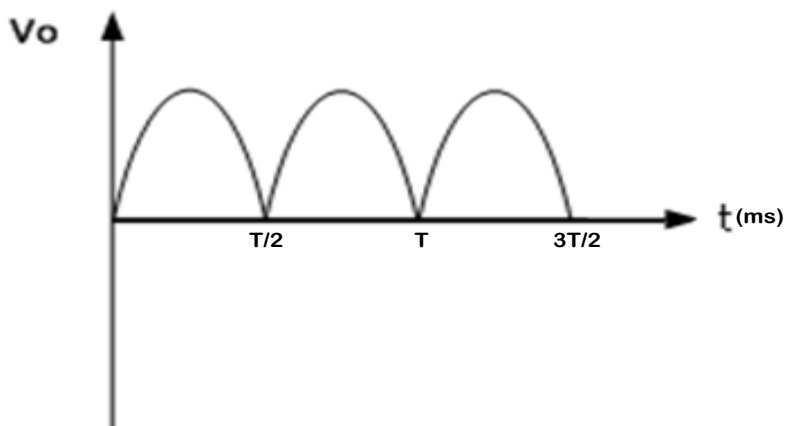

$$V_{dc} = \frac{2V_m}{\pi} =$$

$$V_{rms} = \frac{V_m}{\sqrt{2}} =$$

$$V_{ac} = \sqrt{V_{rms}^2 - V_{dc}^2} =$$


$$\gamma = \frac{V_{ac}}{V_{dc}} =$$

$$\eta = \frac{P_{dc}}{P_{ac}} = \left[\frac{V_{dc}}{V_{rms}} \right]^2 =$$


$$\% \text{ Regulation} = \frac{V_{dc(NL)} - V_{dc(FL)}}{V_{dc(FL)}} \times 100 =$$

VI) Bridge Rectifier with Filter:

Circuit Diagram:

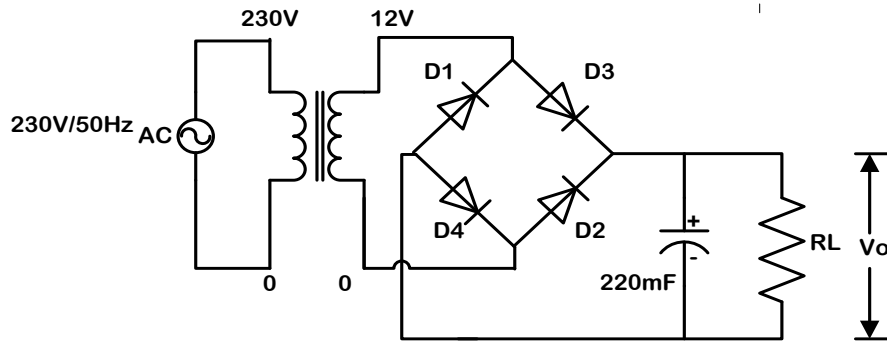

Waveforms:

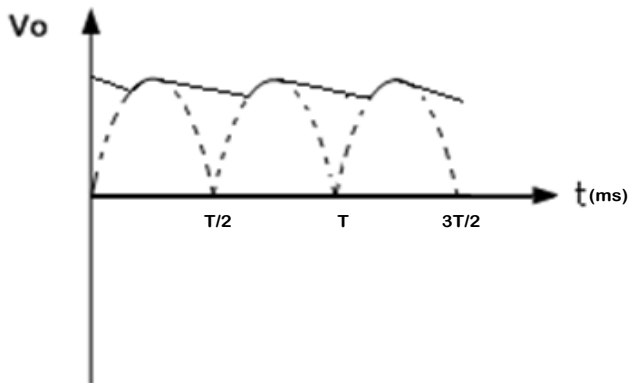

$$V_{dc} = \frac{V_m}{1 + \frac{1}{4fR_L C}} =$$

$$V_{ac} = \frac{V_r - (p-p)}{2\sqrt{3}} =$$

$$\gamma = \frac{V_{ac}}{V_{dc}} =$$

$$V_{rms} = \sqrt{V_{dc}^2 + V_{ac}^2} =$$

$$\eta = \frac{P_{dc}}{P_{ac}} = \left[\frac{V_{dc}}{V_{rms}} \right]^2 =$$

Procedure:

- Make the Connections as shown in the circuit diagram
- Apply 230V AC supply from the power mains to the primary of the transformer
- Observe the voltage across secondary to get V_m , the peak value in CRO
- Use relevant formula to find V_{dc} and V_{rms} of both Full wave and Half wave rectifier & draw the waveforms
- Find out the Ripple factor, Regulation and Efficiency by using the formula.

Conclusions:

RC-COUPLED AMPLIFIER

Aim: To design and setup an RC Coupled amplifier using BJT & to find the input and output impedance of the RC-Coupled amplifier.

Components Required:

- Transistor
- Capacitor
- Resistors
- Signal Generator
- CRO

Design:

Let $V_{CC} = 10V$

$I_C = 5mA$

$\beta = 100$

To find R_E :

$$V_{RE} = \frac{V_{CC}}{10} = \frac{10}{10} = 1V$$

i.e. $I_E R_E = 1V$

$$R_E = \frac{1V}{I_E} = \frac{1V}{I_C} = \frac{1V}{5mA} = 200\Omega$$

Select $R_E = 220\Omega$

To find R_C :

$$V_{CE} = \frac{V_{CC}}{2} = \frac{10}{2} = 5V$$

Apply KVL to CE loop,

$$V_{CC} - I_C R_C - V_{CE} - V_{BE} = 0$$

$$10 - 5mR_C - 5 - 1 = 0$$

$$R_C = 800\Omega$$

Select R_C as 820Ω

To find R_1 :

From the above biasing circuit,

$$V_B = V_{BE} + V_{RE} = 0.7 + 1 = 1.7V$$

$$I_C = \beta I_B \text{ or } I_B = \frac{I_C}{\beta} = \frac{5m}{100} = 0.05mA$$

Assume 10 I_B flows through R_1

$$\therefore R_1 = \frac{V_{CC} - V_B}{10 I_B} = \frac{10 - 1.7}{10 \times 0.050}$$

$$R_1 = 16.6K\Omega$$

Select R_1 as 18K Ω

Assume 9 I_B flows through R_2

$$\therefore R_2 = \frac{V_B}{9 I_B} = \frac{1.7}{9 \times 0.050m} = 3.7K\Omega$$

Select R_2 as 3.9K Ω

Bypass capacitor C_E and coupling Capacitor C_{C1} and C_{C2}

$$\text{Let } X_{CE} = \frac{1}{10} R_E \text{ at } f = 100\text{Hz}$$

$$\text{i.e. } \frac{1}{2\pi f C_E} = \frac{R_E}{10}$$

$$\therefore C_E = \frac{10}{2\pi \times 100 \times 220} = 72.3\mu F$$


Select C_E as 100 μF

Also use $C_{C1} = C_{C2} = 0.47 \mu F$


Procedure:

- Rig up the circuit
- Apply the sinusoidal input of 50m(P-P) and observe the input and output waveforms simultaneously on the CRO screen
- By varying the frequency of the input from Hz to maximum value and note down the output voltages
- Plot the frequency response (gain in dB vs log f) and determine the bandwidth from the graph

Circuit Diagram:

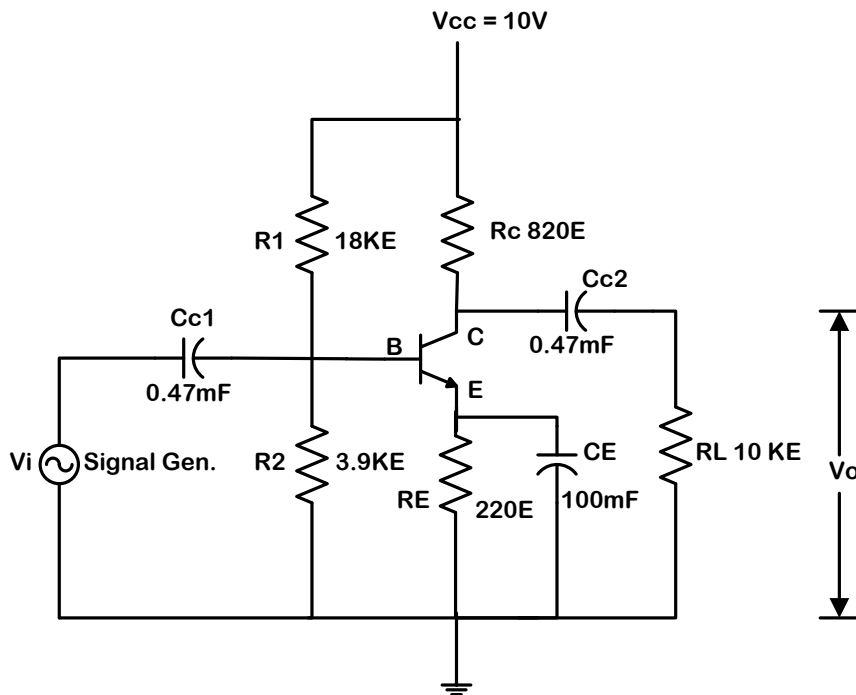

Waveforms:

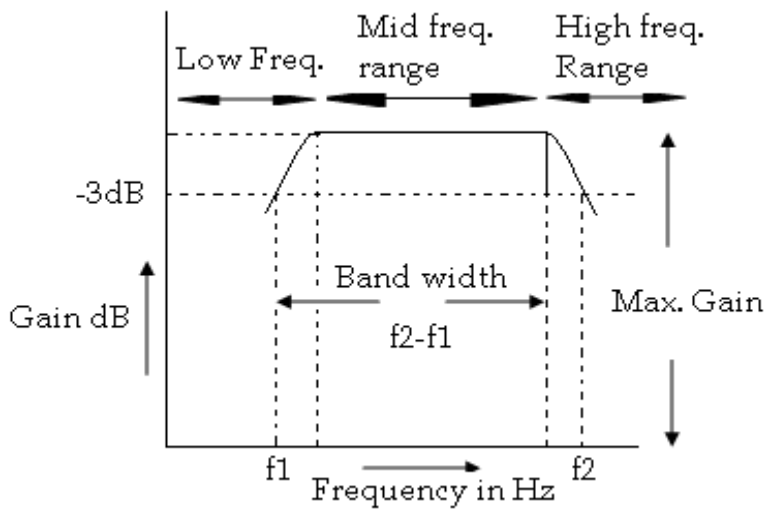

Tabular Column:

Freq. in Hz	$V_{o\ P-P}$	$A_v = \frac{V_o}{V_i}$	Gain in dB $= 20 \log_{10} A_v$
50 Hz			
100 Hz			
200 Hz			
300 Hz			
500 Hz			
1KHz			


1.2 KHz			
.			
.			
2 KHz			
3 KHz			
4 KHz			
.			
200KHz			
300KHz			
.			
2 MHz			

To measure input impedance and output impedance:

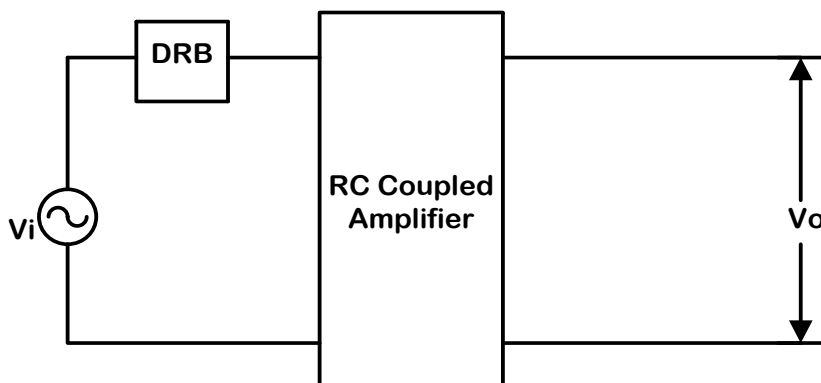I) Input impedance (R_i):

Procedure:


- Connect the circuit as shown
- Set the DRB to a minimum value
- Set the output to a convenient level and note down the output voltage
- Increase the DRB value till V_O becomes half of the maximum amplitude
- The corresponding DRB value gives input impedance



II) Output impedance (R_o):

Procedure:

- Connect the circuit as shown
- Set the DRB to a maximum value
- Set the output to a convenient level and note down the output voltage
- Increase the DRB value till V_O becomes half of the maximum amplitude
- The corresponding DRB value gives input impedance

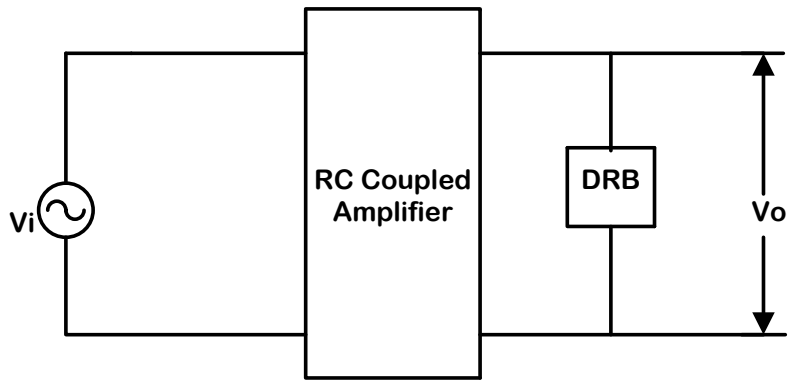**Result:**

Bandwidth: _____ Hz


Input Impedance: _____ Ω Output Impedance: _____ Ω

DARLINGTON EMITTER FOLLOWER

Aim: To determine a BJT Darlington Emitter Follower and determine the Gain, Input and Output impedances.

Components required:

- Transistor (SL100)
- Resistors
- Signal Generator
- CRO
- Capacitors

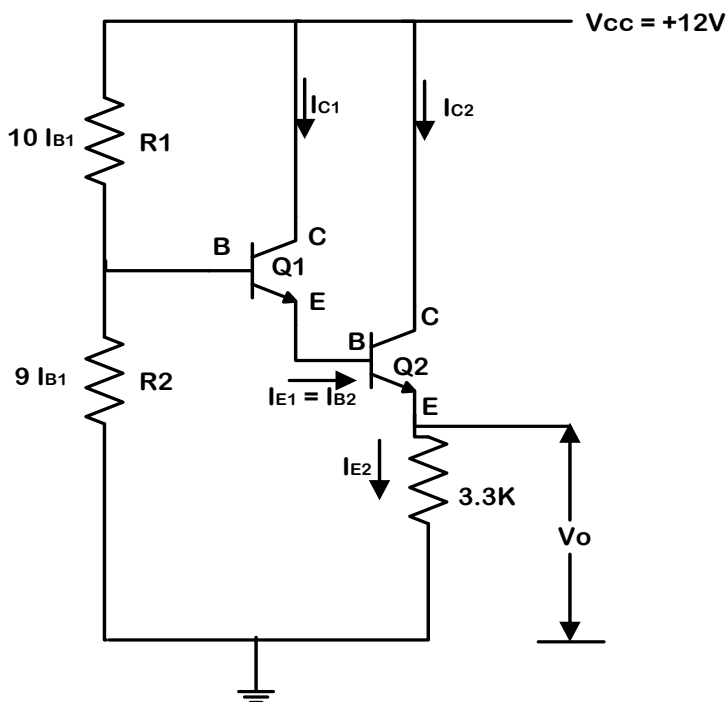Biasing Circuit:**Design:**

$$\text{Let } V_{cc} = 12\text{V}$$

$$I_{c2} = 2\text{mA}$$

$$\beta = 100$$

From Biasing Circuit,

$$V_{B1} = 2V_{BE} + V_{RE}$$

$$V_{B1} = 1.4 + 6$$

$$V_{B1} = 7.4\text{V}$$

$$\text{Let } V_{B2} = \frac{V_{CC}}{2} = \frac{12}{2} = 6\text{V}$$

$$I_{E2}R_E = 6\text{V}$$

$$R_E = \frac{6}{2_m} = 3\text{K}\Omega$$

Select $R_E = 3.3\text{K}\Omega$

$$I_{B2} = \frac{I_{C2}}{\beta} = \frac{2_m}{100} = 0.02\text{mA}$$

$$I_{B1} = \frac{I_{C1}}{\beta} = \frac{I_{B2}}{\beta} = \frac{0.02_m}{100} = 0.0002\text{mA}$$

Assume $10 I_B$ flows through R_1

$$R_1 = \frac{V_{CC} - V_{B1}}{10 I_{B1}} = \frac{12 - 7.4}{10 \times 0.0002_m} = \frac{4.6}{2 \times 10^{-3} \times 10^{-3}} = 2.3\text{M}\Omega$$

Assume $9 I_B$ flows through R_2


$$R_2 = \frac{V_B}{9 I_B} = \frac{7.4}{9 \times 0.0002_m} = \frac{7.4}{1.8 \times 10^{-2} \times 10^{-3}} = 4.1\text{M}\Omega$$

Choose the coupling capacitor C_{C1} and C_{C2} as $0.47\mu\text{F}$

Procedure:

- Connect the circuit as shown in the circuit diagram.
- Set the Signal generator amplitude as 1V peak to peak and observe the input and output waveforms simultaneously on the CRO.
- By varying the frequency of the input from Hz range to MHz range and note the frequency range of the signal and corresponding voltage.
- The output voltage remains constant in mid frequency range.
- Tabulate the readings in tabular column.
- Plot the graph with frequency along X-axis and gain in dB along Y-axis.
- From the graph determine the bandwidth.

Circuit Diagram:

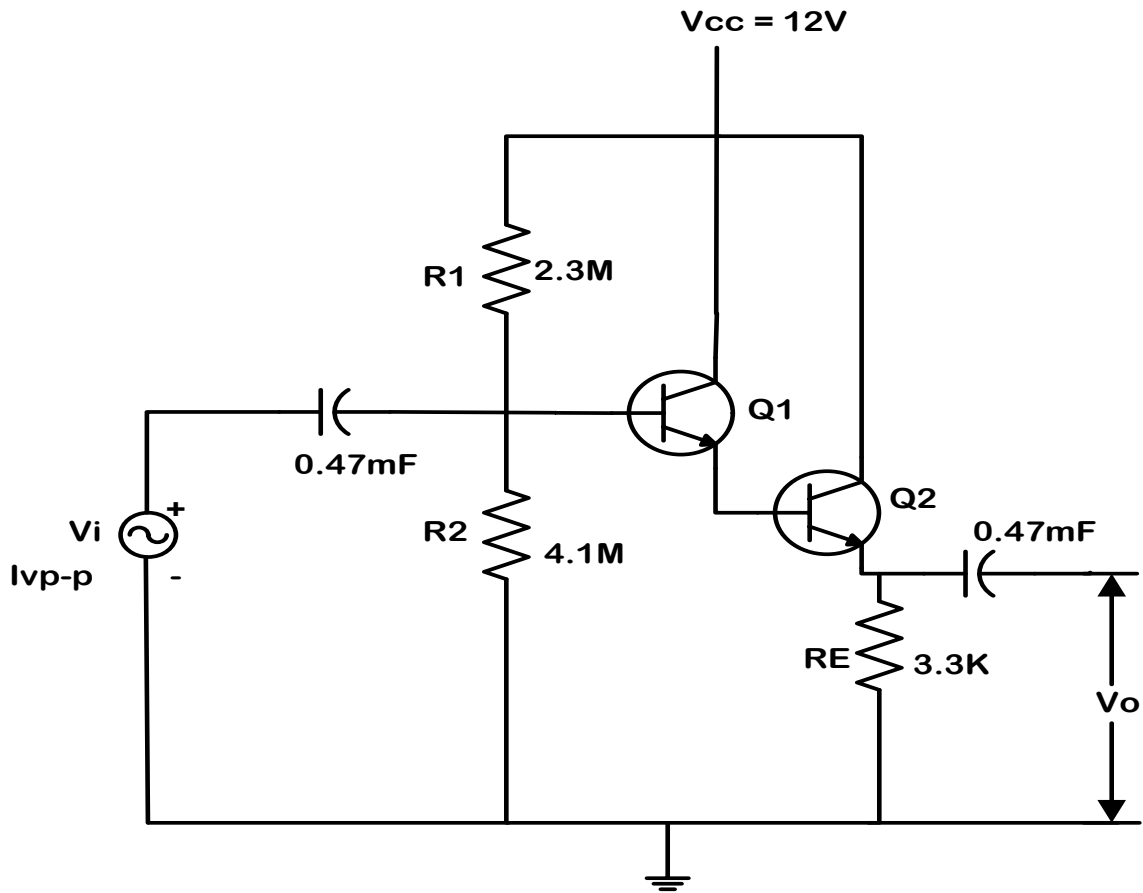


Tabular Column:


Freq. in Hz	V_o P-P	$A_V = \frac{V_o}{V_i}$	Gain in dB $= 20 \log_{10} A_V$
50 Hz			
100 Hz			
200 Hz			
500 Hz			
1kHz			
2Khz			
3Khz			
4Khz			
200Khz			
300Khz			
.			
.			
3 MHz			

To measure input impedance and output impedance:**I) Input impedance (R_i):****Procedure:**

- Connect the circuit as shown
- Set the DRB to a minimum value
- Set the output to a convenient level and note down the output voltage
- Increase the DRB value till V_o becomes half of the maximum amplitude
- The corresponding DRB value gives input impedance

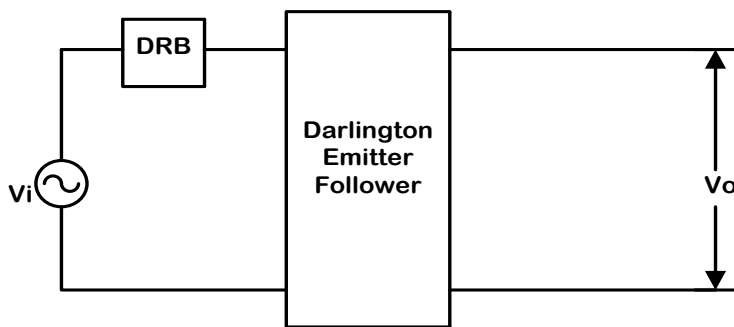**II) Output impedance (R_o):****Procedure:**

- Connect the circuit as shown
- Set the DRB to a maximum value
- Set the output to a convenient level and note down the output voltage
- Increase the DRB value till V_o becomes half of the maximum amplitude
- The corresponding DRB value gives input impedance

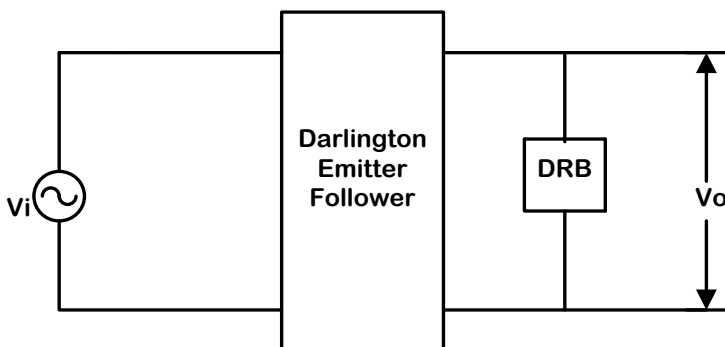**Result:**

Bandwidth: _____ Hz

Input Impedance: _____ Ω Output Impedance: _____ Ω

R.C.PHASE SHIFT OSCILLATOR

Aim: To design and test the RC Phase shift Oscillator for the frequency of 1KHz.

Components required:

- Transistor (BC 107)
- Resistors
- CRO
- Capacitors

Design:

$$V_{CC} = 12V$$

$$I_C = 2mA$$

$$V_{RC} = 40\% V_{CC} = 4.8V$$

$$V_{RE} = 10\% V_{CC} = 1.2V$$

$$V_{CE} = 50\% V_{CC} = 6V$$

To find R_C , R_1 , R_E & R_2

We Have,

$$V_{RC} = I_C R_C = 4.8V$$

$$R_C = 2.4K\Omega$$

$$\text{Choose } R_C = 2.2K\Omega$$

$$V_{RE} = I_E R_E = 1.2V$$

$$R_E = 600\Omega$$

$$\text{Choose } R_E = 680\Omega$$

$$h_{fe} = 100 \text{ (For BC 107)}$$

$$I_B = \frac{I_C}{h_{fe}} = 20mA$$

Assume current through $R_1 = 10 I_B$ & through $R_2 = 9 I_B$

$$V_{R1} = V_{CC} - V_{R2}$$

$$= 10V$$

$$\text{Also, } V_{R1} = 10 I_B \quad R_1 = 10.1V$$

$$R_1 = 50\text{K}\Omega$$

Choose $R_1 = 47\text{K}\Omega$

$$V_{R_2} = V_{BE} + V_{RE}$$

$$= 0.7 + 1.2$$

$$= 1.9\text{V}$$

Also, $V_{R_2} = I_B R_2 = 1.9\text{V}$

$$R_2 = 10.6\text{K}\Omega$$

Choose $R_1 = 12\text{K}\Omega$

To find C_C & C_E

$$X_{C_E} = \frac{1}{2\pi C_E} = \frac{1}{10} R_E = \frac{680}{10} = 68\Omega$$

For $\omega = 20\text{Hz}$

$$C_E = 117\mu\text{F}$$

Choose $C_E = 220\mu\text{F}$

$$X_{C_C} = \frac{1}{2\pi C_C} = \frac{R_C}{10} = 220\Omega$$

For $\omega = 20\text{Hz}$

Choose $C_C = 47\mu\text{F}$

Design of ω Selective Circuit:

Required ω of oscillations $f = 1\text{KHz}$

$$f = \frac{1}{2\pi R C \sqrt{6 + \frac{4R_C}{R}}}$$


Take $R = 4.7\text{K}\Omega$ & $C = 0.01\mu\text{F}$

Procedure:

- Rig up the circuit as shown in the figure
- Observe the sinusoidal output voltage.

- Measure the frequency and compare with the theoretical values.

Circuit Diagram:

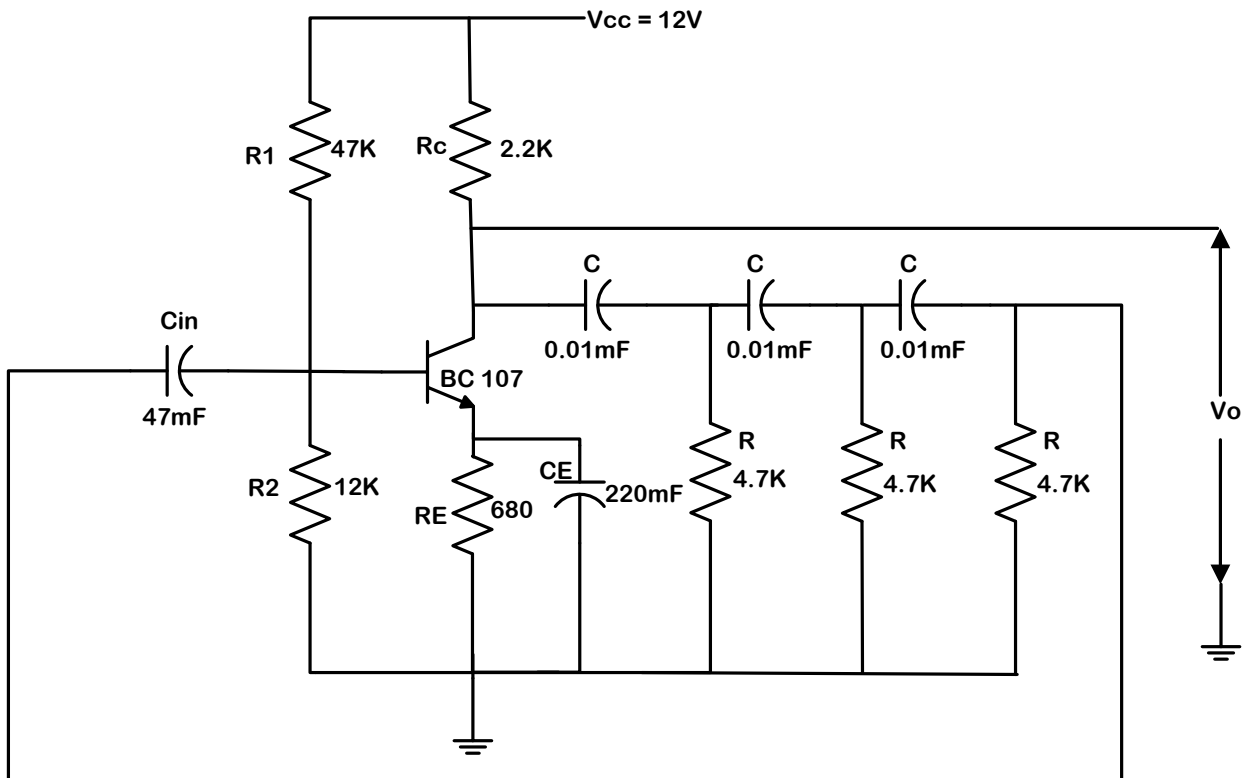

Result:

Frequency

Theoretical: 1KHz

Practical: _____

VERIFICATION OF NETWORK THEOREMS

Aim: To verify Thevenin's & Maximum power transfer theorem for DC Circuits.


Components Required:

- Resistor
- DRB
- Ammeter (DC)
- Multimeter


1) Thevenin's Theorem:

Circuit Diagram:


a) Given Resistor Network:

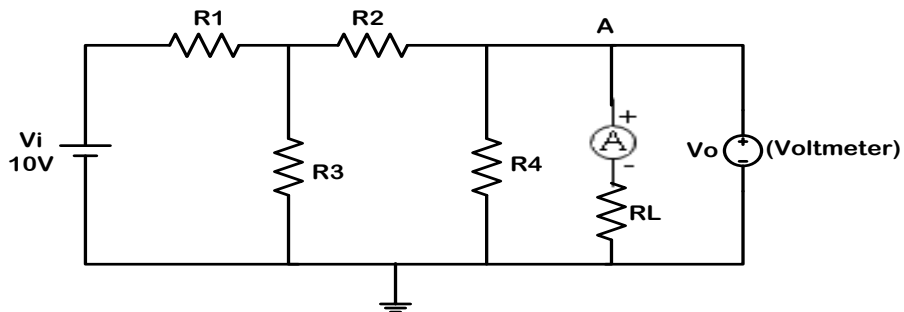


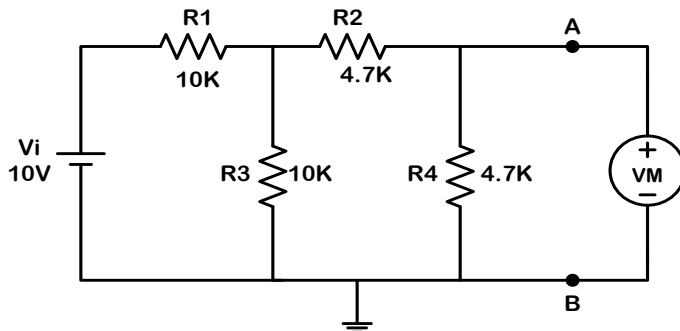b) Thevenin's Voltage - Experimental Setup:



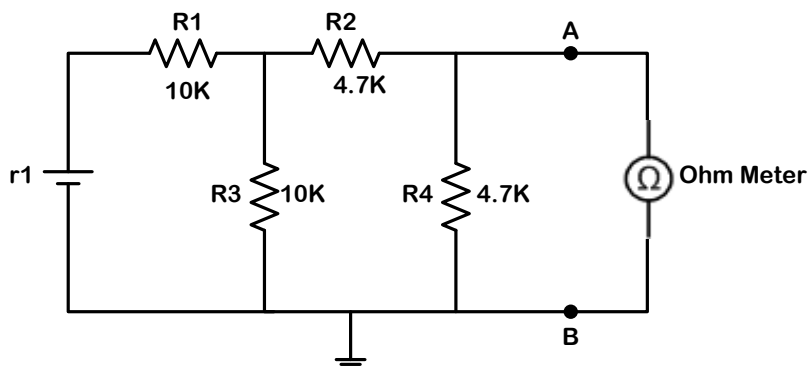c) Thevenin's Resistance - Experimental Setup:



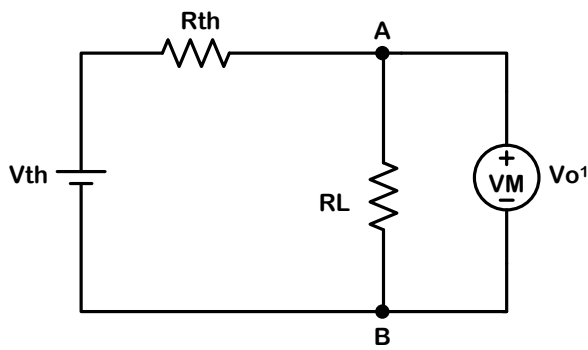

Calculations:

Assume $V_i = 10V$, $R_1 = 10K\Omega$, $R_2 = 4.7K\Omega$, $R_3 = 10K\Omega$, $R_4 = 4.7K\Omega$, $R_L = 10K\Omega$

At node 1:

$$\frac{V_1 - 10}{10K} + \frac{V_1 - V_2}{4.7K} + \frac{V_1}{10K} = 0$$

$$V_1 \left[\frac{1}{10K} + \frac{1}{4.7K} + \frac{1}{10K} \right] - \frac{V_2}{4.7K} = \frac{1}{1K}$$

$$4.128 \times 10^{-4} V_1 - 2.128 \times 10^{-4} V_2 = 1m \text{ -----(1)}$$

At node 2:

$$\frac{V_2 - V_1}{4.7K} + \frac{V_2}{4.7K} = 0$$

$$4.26 \times 10^{-4} V_2 - 2.128 \times 10^{-4} V_1 = 0 \text{ -----(2)}$$

From (1) & (2)

$$V_1 = 3.27V$$

$$V_2 = V_{th} = V_m = 1.635V$$

$$R_{th} = [(10 \parallel 10) + 4.7] \parallel 4.7 K$$

$$= \left(\left(\frac{10 \times 10}{20} \right) \times 4.7 \parallel 4.7 \right) K$$

$$= ((5 + 4.7) \parallel 4.7) K$$

$$= (9.7 \parallel 4.7) K$$

$$R_{th} = 3.16K\Omega$$

$$I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{1.63}{3.16K + 10K} = 0.124mA$$

$$I_L = 0.124mA$$

$$V_{O^1} = I_L \times R_L$$

$$= 0.1238\text{m} \times 10\text{K} = 1.24\text{V}$$

$$V_{O^1} = 1.24\text{V}$$

Procedure:

- Rig up the circuit as shown in the Fig I(a), measure the voltage across load R_L using DC Voltmeter. Note voltage as V_O .
- Connect the circuit as in Fig I(b), measure the voltage across terminals AB. Note down the voltage reading as V_{OC} .
- Rig up the circuit as shown in the Fig I(c), switch of the DC voltage source. The resistance ' r ', represents internal resistance of the voltage source.
- Measure resistance across terminals AB using multimeter. Note down the resistance value as R_O .
- Now rig up the circuit as shown in the Fig I(d), switch on the power supply and measure the voltage drop across the load resistance R_L using the multimeter, note down voltage as V_{O^1} .
- Compare the voltages V_O and V_{O^1} , they must agree each other, which verifies Thevenins theorem.

Observations:


Voltage across load R_L in the circuit Fig I(a), $V_O =$

Current through load R_L in the circuit Fig I(a), $I_O =$

Thevenins Voltage in Fig I(b), $V_{OC} =$

Thevenins Resistance in Fig I(c), $R_O =$

Voltage across load R_L in Thevenins equivalent circuit in Fig I(d), $V_{O^1} =$

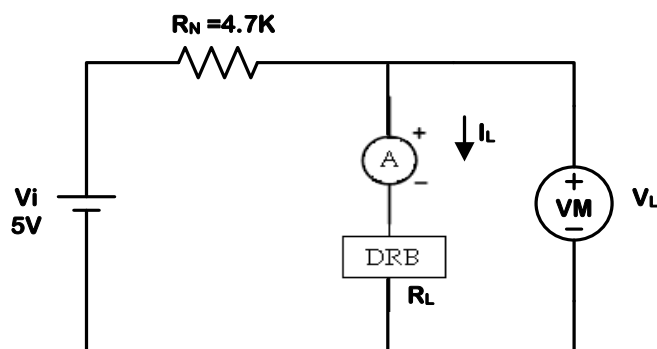II) Maximum Power Transfer Theorem:**Circuit Diagrams:**

Calculations:

Choose $R_N = 4.7K\Omega$

$$-5 + 4.7K I_L + R_L I_L = 0$$

$$9.4K I_L = 5$$

$$I_L = 0.53mA$$

Maximum Power:

$$P = I_L^2 R_L$$


$$= 1.32mw$$

Procedure:

- Rig up the circuit as shown in the Fig II
- Set the input Dc voltage $V_i = 5V$
- Vary the resistance R_L using DRB in regular steps and note down the corresponding voltmeter and ammeter readings.
- Plot the graph of power Vs Resistance R_L .
- Determine the resistance R_L at which power is maximum (From the Graph)

Tabular Column:

$R_L (\Omega)$	$I_L (mA)$	$V_L (volts)$	$P_L = V_L I_L (watts)$
1 K			
2 K			
3 K			
4 K			
4.1 K			
4.2 K			
.			
.			
5 K			
6 K			
10 K			

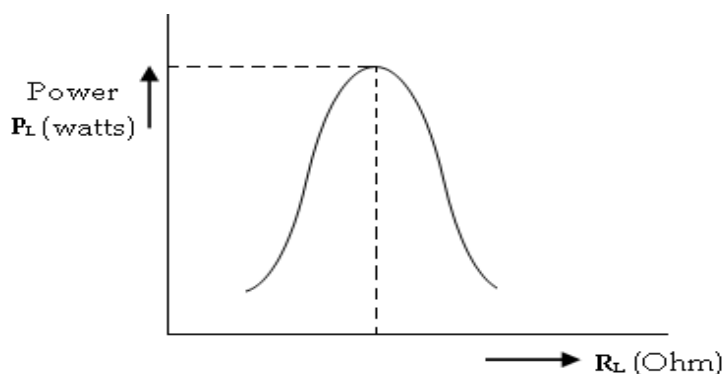Specimen Graph:

SERIES AND PARALLEL RESONANCE CIRCUITS


Aim: To test and verify the working/functioning of Series and Parallel resonance circuits and plots its response

Components Required:

- Resistor, Decade Resistance Box
- Decade Capacitance Box
- Decade Inductance Box
- Function Generator
- AC Voltmeter, Ammeter

I) Series Resonance:

Circuit Diagram:

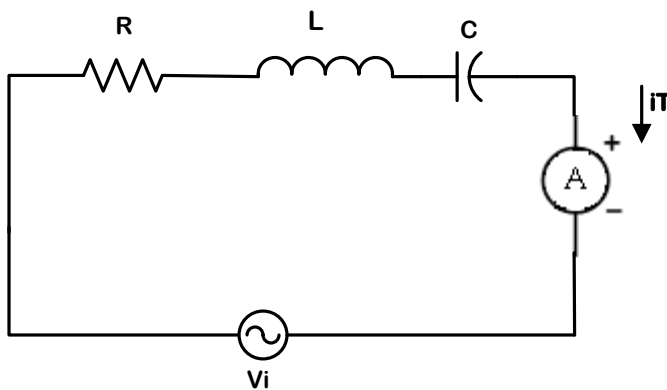

Procedure:

- Set up the circuit as in Fig
- Set input voltage $V_m = 5\text{v}$ using signal generator and vary the frequency from 100Hz to 1MHz in regular steps.
- Note down the corresponding voltage and current.
- Plot the graph of Frequency Vs Current
- Find Resonance Frequency, Quality Factor and Bandwidth from the graph obtained and compare with the theoretical values.

Calculations:

Take $R = 100\Omega$, $L = 10\text{mH}$, $C = 0.1\mu\text{F}$

$$\text{Resonance Frequency } f_o = \frac{1}{2\pi\sqrt{LC}} =$$



$$\text{Quality factor of Series Resonance Circuit } Q_o = \frac{W_o L}{R} = \frac{1}{W_o C R} =$$

$$\text{Bandwidth } B_W = \frac{W_o}{Q_o} =$$

Observations:

Frequency (Hz)	Total Current i_T (mA)	X_C (Ω)	X_L (Ω)	$Z = \frac{v}{i_T}$ (Ω)	$Z = \sqrt{R^2 + (X_L - X_C)^2}$ (Ω)
1 KHz					
2 KHz					
3 KHz					
4 KHz					
.					
.					
.					
10 KHz					


Model Graph:

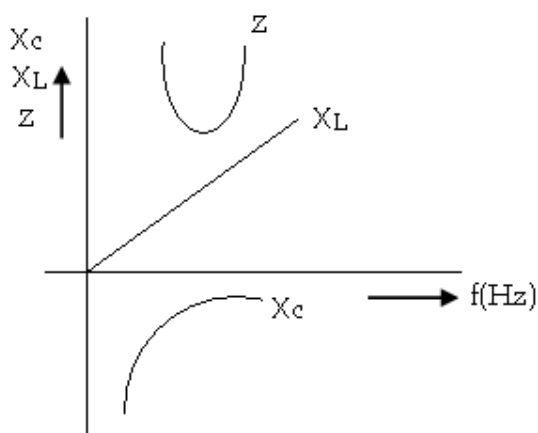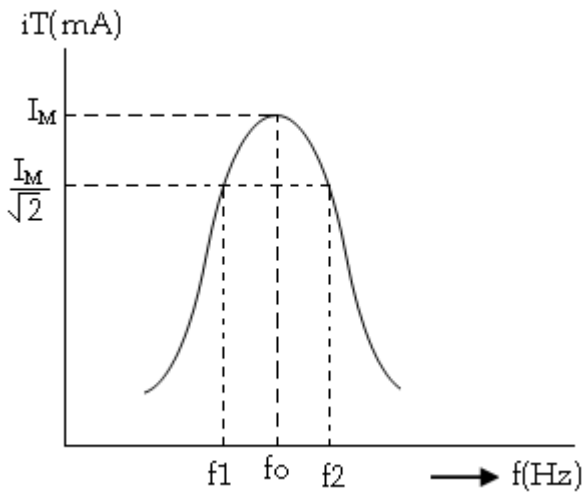

From the Graph,

Resonance Frequency $f_o =$

Bandwidth $BW = f_2 - f_1 =$

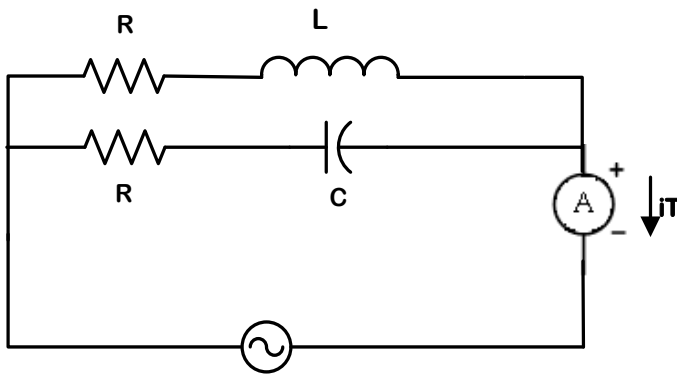II) Parallel Resonance:**Circuit Diagram:****Procedure:**

- Set up the circuit as in Fig
- Set input voltage $V_m = 5\text{v}$ using signal generator and vary the frequency from 100Hz to 1MHz in regular steps.
- Note down the corresponding voltage and current readings and calculate impedance $Z = \frac{V_T}{I_T}$
- Plot the graph of Frequency Vs Impedance.
- Find Resonance Frequency, Quality Factor and Bandwidth from the graph obtained and compare with the theoretical values.

Calculations:

Take $R_L = 4.7\text{K}\Omega$, $R_C = 4.7\text{K}\Omega$, $L = 10\text{mH}$, $C = 0.1\mu\text{F}$

Resonance Frequency $f_0 = \frac{1}{2\pi\sqrt{LC}}$, if $R_L = R_C$

Quality factor of Series Resonance Circuit $Q_0 = \frac{R}{\omega_0 L} = \omega_0 RC =$



Bandwidth $B_W =$

Observations:

$V_m = 5\text{V}$

Frequency (Hz)	Total Current $i_T(\text{mA})$	$X_C (\Omega)$	$X_L (\Omega)$	$Z = \frac{v}{i_T} (\Omega)$
1 KHz				
2 KHz				
3 KHz				
4 KHz				
.				
.				
10 KHz				

Specimen Graph:

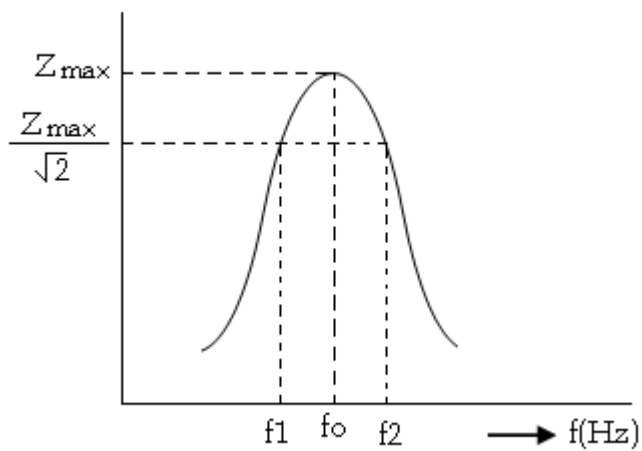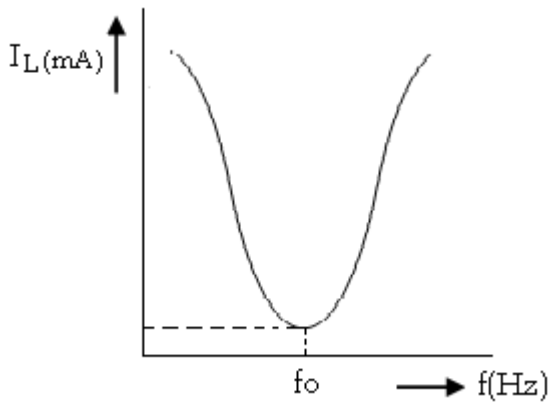

From the Graph,

Resonance Frequency $f_0 =$

Bandwidth $BW = f_2 - f_1 =$

Results:

Parameters		Series Resonance	Parallel Resonance
Resonance Frequency	Theoretical		
	Observed		
Bandwidth	Theoretical		
	Observed		
Quality Factor	Theoretical		
	Observed		


VOLTAGE SERIES FEEDBACK AMPLIFIER

Aim: Design of a FET Voltage series feedback amplifier and determine the gain, frequency response, input and output impedances with and without feedback.

Components required:

- Power supply
- Multimeter
- CRO
- Function Generator
- AC mill voltmeters
- FET BW 10/11
- Resistors
- Capacitors

Circuit Diagram:

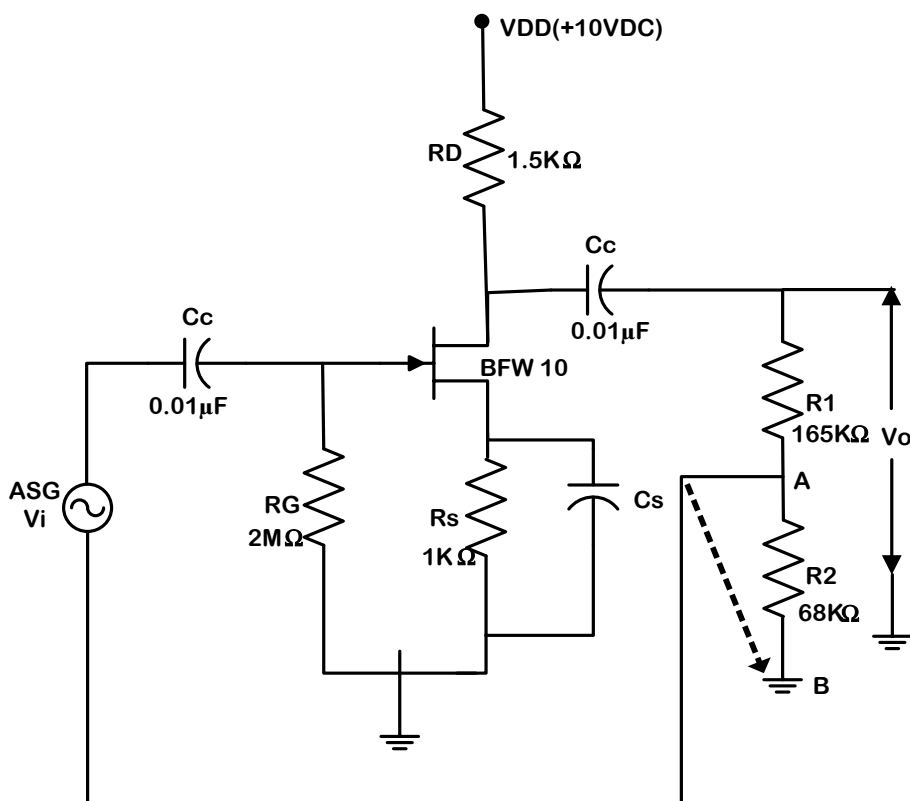

Design:

$$I_{DSS} = 10\text{mA}$$

$$V_P = -3\text{V (From Data Sheet)}$$

$$\text{Given, Q condition is } I_D = 2\text{mA}, V_{DS} = 5\text{V} = \frac{V_{DD}}{2}$$

$$I_D = I_{DSS} \left[1 - \left(\frac{V_{GS}}{V_P} \right) \right]^2$$

We Know that,

$$\left[\frac{I_D}{I_{DSS}}\right]^{1/2} = 1 - \left(\frac{V_{GS}}{V_P}\right)$$

$$1 - 0.44 = \frac{V_{GS}}{3}$$

R_S: $V_{GS} = -0.55 \times 3 = -1.65V$

$$I_D R_S = |V_{GS}|$$

Choose R_S = 1KΩ

R_D: $V_{DD} = V_{DS} + I_D (R_S + R_D)$

$$5 = 2 \times 10^3 [1K + R_D]$$

Choose R_D = 1.5 KΩ

R_G: $I_{gs} = 1000nA$ (From Data Sheet)

Before conduction, minority carriers have to be drained out, for this R_G would be usually very large. Further input impedance of the amplifier would be equal to R_G itself.

Thus, $I_{gs} R_G = V_{gs}$

$$R_G = \frac{V_{gs}}{I_{gs}} = 1.65M\Omega$$

Choose R_G = 2 MΩ

C_S: Should act as a short circuit at lowest frequency of interest

$$X_{C_S} = \frac{1}{100} R_S = 10\Omega \text{ at } 500\text{Hz (say)}$$

$$\therefore C_S = \frac{1}{2\pi f X_{C_S}} \Rightarrow C_S = 33\mu\text{F}$$

Choose C_S = 33 or 47μF

Theoretically gain A_V without feedback is calculated as

$$A_V = -g_m R_D$$

For the above circuit,

g_m is computed as bellow,

$$\text{We have, } I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

Differentiating with respect to V_{GS}

$$\left| \frac{\partial I_D}{\partial V_{GS}} \right| = 2I_{DSS} \left(1 + \frac{V_{GS}}{V_P}\right) \left(\frac{1}{V_P}\right)$$

$$\frac{\partial I_D}{\partial V_{GS}} = g_m \quad \therefore g_m = 2(10) \left(1 + \frac{1.65}{3}\right) \left(\frac{1}{3}\right)$$

$$g_m = 10 \text{ mA/V}$$

$$\therefore |A_V| = g_m \times R_D = 10 \times 1.5 = 15$$

To Design feedback circuit (R_1 , R_2)

Let us Assume gain with feedback desired is 2

$$\text{i.e. } A_{Vf} = 2$$

$$\text{Then } A_{Vf} = \frac{A_V}{1 + A_V \beta} \text{ where } \beta = \frac{R_2}{R_1 + R_2}$$

(Practically we may not get $A_V = 15$;

It is better to measure A_V practically & design R_1 & R_2)

E.g: Say $A_V = 4.8$ (Practical Value)

$$\therefore A_{Vf} = \frac{A_V}{1 + A_V \beta}$$


$$\frac{2}{4.8} = \frac{1}{1 + 4.8 \beta}$$

$$R_1 = 2.4 R_2$$

Choose $R_2 = 68\text{K}\Omega$, $R_1 = 165\text{K}\Omega$ ($150\text{K}\Omega + 15\text{K}\Omega$)

Procedure:


- Rig up the circuit as shown in the circuit diagram.
- Check Q conditions i.e., measure V_{DS} and V_{GS} .
- Set $V_i = 1\text{V}$ or 2V at 10KHz on Audio signal Generator and measure gain A_V without feedback.
- Disconnect short of Green and Black terminal of signal generator to avoid grounding problem or isolate ground of signal generator.
- Measure V_O with feedback & find A_{Vf} the gain with feedback. Note A_{Vf} is less than A_V
- To plot freq response, note output voltage with and without feedback from 100Hz to 10MHz

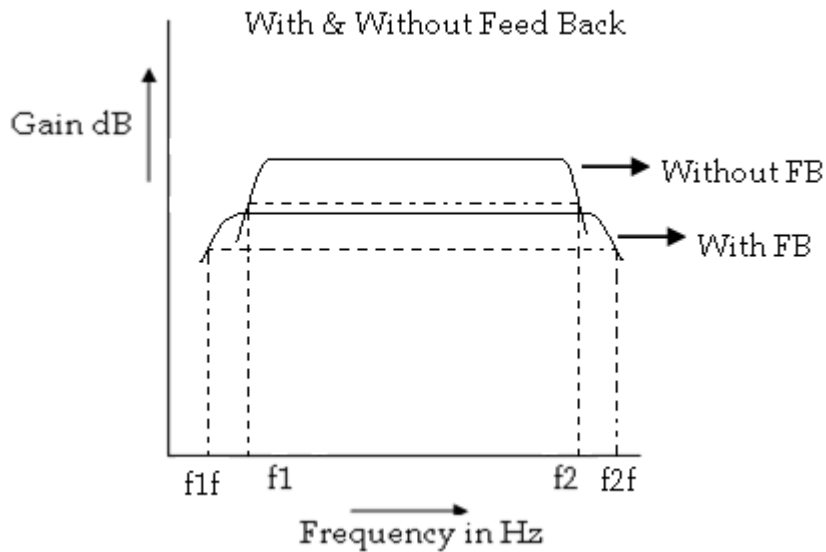Frequency response:

Here one can observe that effect of feedback is gain decreases but Bandwidth increases.

To measure input impedance and output impedance:**I) Input impedance (Zi):****Procedure:**

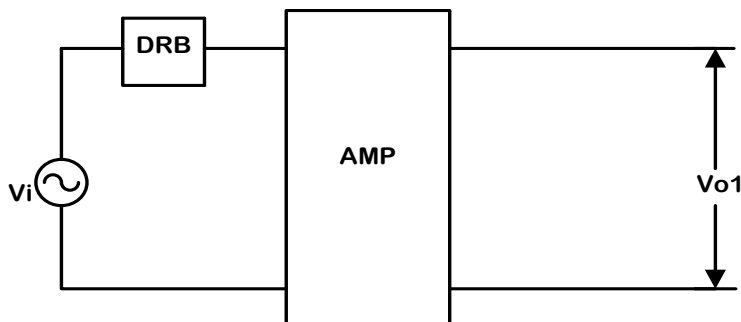
- Connect the circuit as shown
- Set all knobs of DRB to 0Ω
- Apply input sinusoidal wave (20 to 40 mV_{p-p})
- Fix input frequency in mid freq range (say 15 KHz) and measure output voltage V_O .
- Increase resistance on DRB, till V_O reduces to half the value this gives $V_{O1} = \frac{V_O}{2}$. The DRB values now gives input impedance Z_i of amplifier.



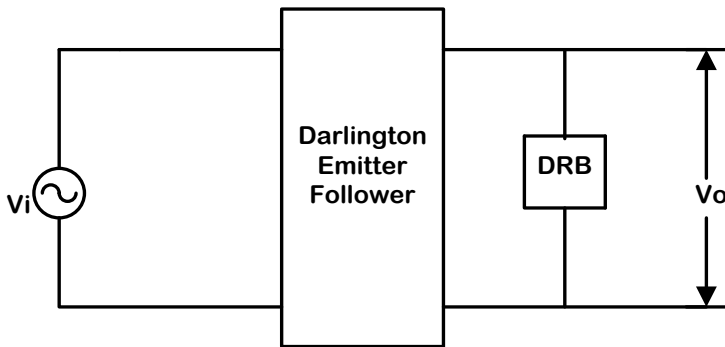II) Output impedance (R_O):

Procedure:

- Connect the circuit as shown
- Set all knobs of DRB to maximum value.
- Apply input sinusoidal wave (20 to 40 mV)
- Fix input frequency 15 KHz and measure output voltage.
- Decrease resistance on DRB, till output voltage reduces to half the value of V_O. Now $V_{O2} = \frac{V_O}{2}$. The DRB values now gives output impedance Z_O of amplifier.



Observation:

Gain with feedback : _____
 Gain without feedback : _____

Frequency	V _O	A _V	A _{VF}	Z _i	Z _O
100 Hz					
200 Hz					
.					
.					
1kHz					
2KHz					
.					
.					
100 KHz					


CLASS 'B' PUSH-PULL AMPLIFIER

Aim: To design and test the performance of transformer less Class 'B' Push-Pull Amplifier and to determine its conversion efficiency.

Components Required:

- Diodes IN 4001
- Transistor SL100, SK100
- Resistors
- Capacitors

Circuit Diagram:

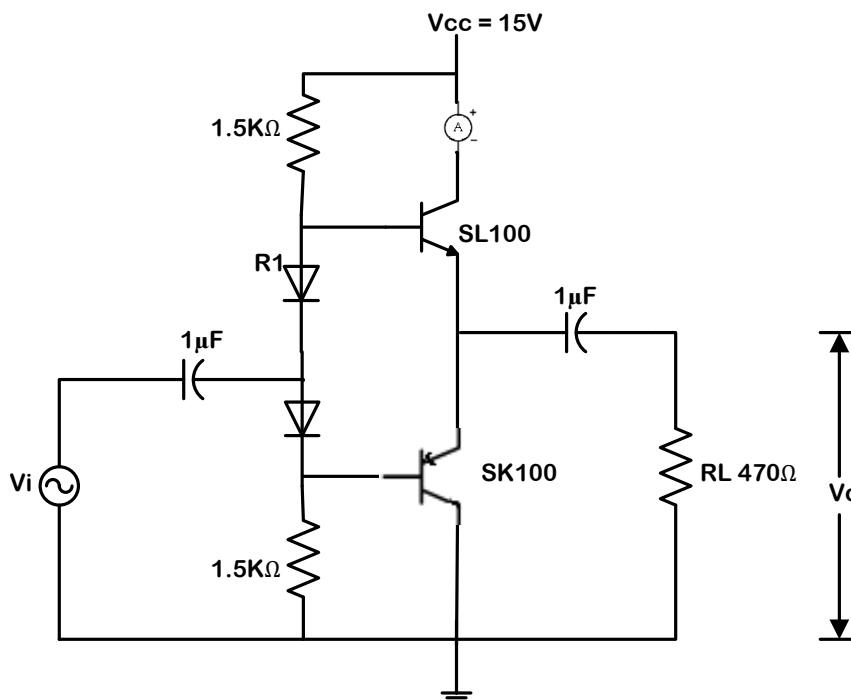

Design:

Given $V_{CC} = 15V$, $R_L = 470\Omega$

$$V_{CE1} = V_{CE2} = \frac{V_{CC}}{2} = 7.5V$$

$$V_{B1} = V_{CE2} + V_{BE1} = 7.5 + 0.7 = 8.2V$$

Assume $I_1 = 5mA$

$$R_1 = \frac{V_{CC} - V_{B1}}{I_1} = 1.36K\Omega$$

$$R_2 = \frac{V_{R2}}{I_1} = \frac{V_{B1} - V_{D1} - V_{D2}}{I_1} = 1.36K\Omega$$

Choose $R_1 = R_2 = 1.5K\Omega$

Choose $C_1 = C_2 = 1\mu\text{F}$

$$P_i(\text{dc}) = V_{CC} I_{dc}$$

$$P_o(\text{ac}) = \frac{V_m^2}{2R_L}$$

$$\text{Efficiency } \eta = \frac{P_o(\text{ac})}{P_i(\text{dc})}$$

Procedure:

- Connect the circuit as shown in the circuit diagram.
- Apply the input voltage $V_i = 5\text{V}$
- Keeping the voltage constant, vary the frequency from 100Hz to 1MHz in regular steps and note down the output voltage in each case.
- Plot the gain Vs Frequency graph.
- Note down the dc current I_{dc}
- Calculate the efficiency.

Observations:

$$V_i = 5\text{V}$$

Freq. in Hz	V_o	Gain = V_o/V_i	Gain in dB = $20 \log V_o/V_i$
50 Hz			
100 Hz			
200 Hz			
500 Hz			
1 KHz			
2 KHz			
3 KHz			
5 KHz			
10 KHz			
.			
.			
.			
.			
1MHz			
2 MHz			

Result:

Efficiency $\eta =$


CRYSTAL OSCILLATOR

Aim: To design and test the performance of BJT - Crystal Oscillator for $f_o > 100$ KHz.

Components Required:

- Crystal 2MHz
- Transistor SL100
- Resistors
- Capacitors

Circuit Diagram:

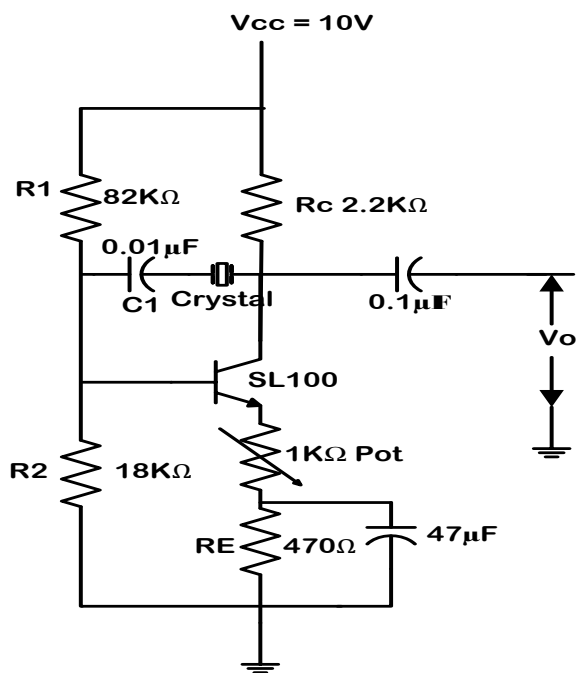

Design:

Given $V_{CC} = 10V$, $\beta = 200$, $I_C = 2mA$

To find R_E :

$$V_{RE} = \frac{V_{CC}}{10} = \frac{10}{10} = 1V$$

$$I_E R_E = 1, I_E \approx I_C$$

$$R_E = \frac{V_{RE}}{I_C} = \frac{V_{RE}}{I_C} = \frac{1}{2 \times 10^{-3}} = 500\Omega$$

Choose $R_E = 470\Omega$

To find R_C :

Applying KVL

$$V_{CC} - I_C R_C - V_{CE} - V_{RE} = 0 \quad [V_{CE} = \frac{V_{CC}}{2}]$$

$$10 - 2 \times 10^{-3} R_C - 5 - 1 = 0$$

$$4 - 2 \times 10^{-3} R_C = 0$$

$$R_C = 2K\Omega$$

Choose $R_C = 2.2K\Omega$

From the biasing circuit

$$V_B = V_{BE} + V_{RE}$$

$$= 0.7 + 1$$

$$= 1.7V$$

To find I_B :

$$I_B = \frac{I_C}{\beta} = \frac{2 \times 10^{-3}}{200} = 0.01mA$$

Assume 10 I_B flows through R_1

$$R_1 = \frac{V_{CC} - V_B}{10 I_B} = \frac{10 - 1.7}{10 \times 0.01m} = 83K\Omega$$

Choose $R_1 = 82K\Omega$

Assume 9 I_B flows through R_2

$$R_2 = \frac{V_B}{9 I_B} = \frac{1.7}{9 \times 0.01m} = 18 K\Omega$$

Choose $R_2 = 18K\Omega$

Assume coupling capacitor C_{C1} and C_{C2} as $0.47\mu F$

Procedue:

- Make the connections as shown in circuit diagram.
- Vary $1K\Omega$ potentiometer so as to get an undistorted sine wave at the output.
- Note down the frequency of the output wave and compare it with the theoretical frequency of oscillation.

Result:

Frequency : Theoretical: 2MHz

Practical:


FET HARTLEY & COLPITTS OSCILLATOR

Aim: To design Hartley & Colpitts Oscillator for given frequency using FET.

Components Required:

- FET (BFW11)
- Resistors
- Capacitors
- CRO

Biasing Circuit:

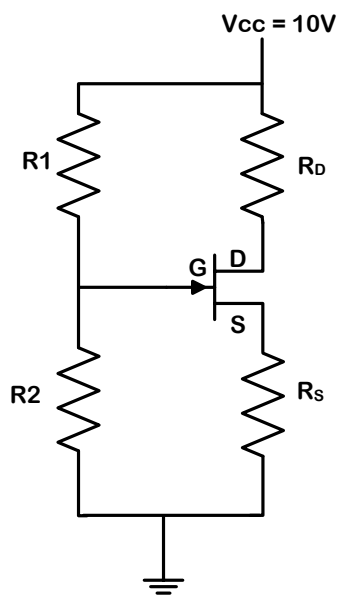

Design:

$$V_{DD} = 10V, V_{DS} = \frac{V_{DD}}{2} = 5V$$

$$\text{For } \vartheta \text{ FET, } I_{DSS} = 11.5\text{mA}$$

$$V_P = -3V$$

$$V_{GS} = -1.7V$$

$$I_D = I_{DSS} \left[1 - \frac{V_{GS}}{V_P} \right]^2$$

$$I_D = 11.5 \times 10^{-3} \left[1 - \frac{1.7}{3} \right]^2$$

$$I_D = 2\text{mA}$$

Applying KVL to the outer loop

$$V_{DD} = I_D(R_D + R_S) + V_{DS}$$

$$R_D + R_S = \frac{V_{DD} - V_{DS}}{I_D} = \frac{10 - 5}{2\text{m}} = 2.1\text{K}\Omega$$

$$\text{Let } R_D = 1\text{K}\Omega \text{ \& } R_S = 1.5\text{K}\Omega$$

Use 1K pot in series with 1.5K Ω for R_S

$$\frac{V_{DD}R_2}{R_1 + R_2} = V_{GS} + V_{RS}$$

$$\frac{R_2}{R_1 + R_2} = \frac{V_{GS} + I_D R_S}{V_{DD}} = \frac{-1.7 + (2 \times 10^{-3}) \times 1.5\text{K}}{10}$$

$$\frac{R_2}{R_1 + R_2} = 0.13$$

$$R_2 = 0.13R_1 + 0.13R_2$$

$$0.87R_2 = 0.13R_1$$

$$\frac{R_2}{R_1} = \frac{0.13}{0.87} = 0.149$$

$$R_1 = 1\text{M}\Omega$$

$$R_2 = 0.149 R_1$$

$$R_2 = 150\text{K}\Omega \text{ (Choose } R_2 \text{ as } 82\text{K}\Omega)$$

Hartley Oscillator:

Tank Circuit Design:

$$f_O = \frac{1}{2\pi\sqrt{LC}} \text{ Where } L = L_1 + L_2$$

$$f_O = 100\text{KHz}$$


$$L = \frac{1}{4\pi^2 f_O^2 C} \text{ let } C = 330\text{pF}$$

$$L = \frac{1}{4 \times (3.14)^2 (100 \times 10^3)^2 \times 330 \times 10^{-12}}$$

$$L = 7.68\text{mH}$$

$$L_1 = 5\text{mH}$$

$$L_2 = 2.6\text{mH}$$

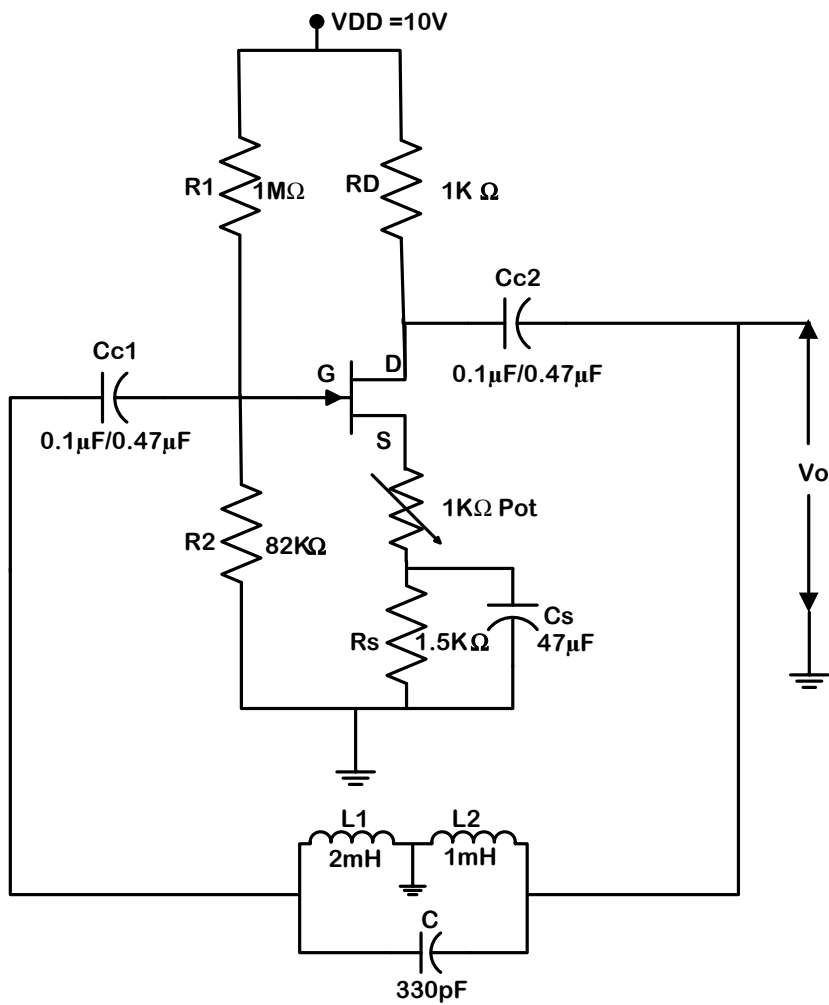Circuit Diagram:**Colpitts Oscillator:**

$$f_o = \frac{1}{2\pi\sqrt{LC_{eq}}} \quad C = \frac{C_1 C_2}{C_1 + C_2}$$

$$f_o = 100\text{KHz}$$


$$C = \frac{1000 \times 2200 \times 10^{-24}}{(1000 + 2200) \times 10^{-12}}$$

$$C = 687.5\text{pF}$$

$$L = \frac{1}{4\pi^2 f_o^2 C} = \frac{1}{4 \times (3.14)^2 (100 \times 10^3)^2 \times 687.5 \times 10^{-12}}$$

$$L = 3.6\text{mH}$$

Circuit Diagram:

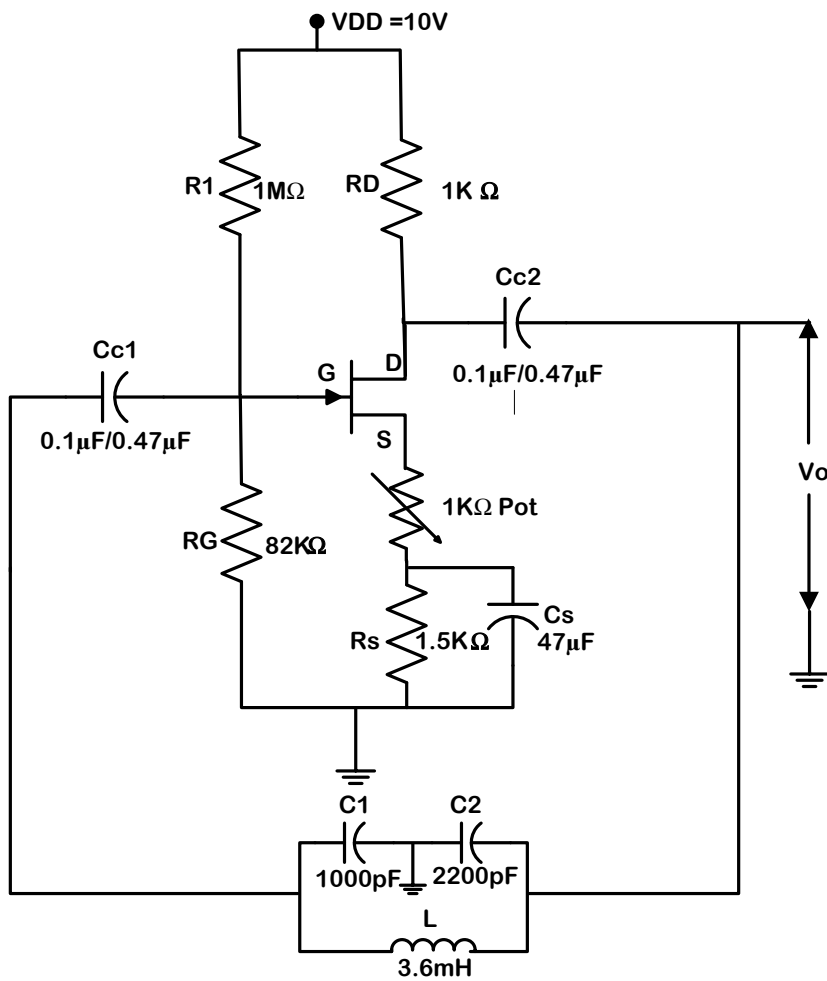

Procedue:

- Make the connections as shown in circuit diagram.
- Observe the sinusoidal output voltage.
- Measure the frequency and compare with the theoretical values.

Result:

Hartley Oscillator:

Theoretical Frequency : 100KHz

Practical Frequency :

Amplitude of the sine wave :

Colpitts Oscillator:

Theoretical Frequency : 100KHz

Practical Frequency :

Amplitude of the sine wave :

VIVA-VOCE QUESTIONS

- [1] What are conductors, insulators, and semi-conductors? Give examples.
- [2] Name different types of semiconductors.
- [3] What are intrinsic semiconductors and extrinsic semiconductors?
- [4] How do you get P-type and N-type semiconductors?
- [5] What is doping? Name different levels of doping.
- [6] Name different types of Dopants. .
- [7] What do you understand by Donor and acceptor atoms?
- [8] What is the other name for p-type and N-type semiconductors?
- [9] What are majority carriers and minority carriers?
- [10] What is the effect of temperature on semiconductors?
- [11] What is drift current?.
- [12] What is depletion region or space charge region?
- [13] What is junction potential or potential barrier in PN junction?
- [14] What is a diode? Name different types of diodes and name its applications
- [15] What is biasing? Name different types w.r.t. Diode biasing
- [16] How does a diode behave in its forward and reverse biased conditions?
- [17] What is static and dynamic resistance of diode?
- [18] Why the current in the forward biased diode takes exponential path?
- [19] What do you understand 1?y Avalanche breakdown and zener breakdown?
- [20] Why diode is called unidirectional device.
- [21] What is PIV of a diode
- [22] What is knee voltage or cut-in voltage?
- [23] What do you mean by transition capacitance or space charge capacitor?
- [24] What do you mean by diffusion capacitance or storage capacitance?
- [25] What is a transistor? Why is it called so? .
- [26] Name different types, of transistors?
- [27] Name different configurations in which the transistor is operated
- [28] Mention the applications of transistor. Explain how transistor is used as switch
- [29] What is transistor biasing? Why is it necessary?
- [30] What are the three different regions in which the transistor works?
- [31] Why transistor is called current controlled device?
- [32] What is FET? Why it is called *so*?
- [33] What are the parameters of FET?
- [34] What are the characteristics of FET?
- [35] Why FET is known as voltage controlled device?
- [36] What are the differences between BJT and FET?
- [37] Mention applications of FET. What is pinch off voltage.
- [38] What is an amplifier? What is the need for an amplifier circuit?
- [39] How do you classify amplifiers? ,
- [40] What is faithful amplification? How do you achieve this?
- [41] What is coupling? Name different types of coupling
- [42] What is operating point or quiescent point?
- [43] What do you mean by frequency response of an amplifier?

- [44] What are gain, Bandwidth, lower cutoff frequency and upper cutoff frequency?
- [45] What is the figure of merit of an amplifier circuit?
- [46] What are the advantages of RC coupled amplifier?
- [47] Why a 3db point is taken to calculate Bandwidth?
- [48] What is semi-log graph sheet? Why it is used to plot frequency response?
- [49] How do you test a diode, transistor, FET?
- [50] How do you identify the terminals of Diode, Transistor& FET?
- [51] Mention the type number of the devices used in your lab.
- [52] Describe the operation of NPN transistor. Define reverse saturation current.
- [51] Explain Doping w.r.t. Three regions of transistor
- [52] Explain the terms h_{ie}/h_{ib} , h_{oe}/h_{ob} , h_{re}/h_{rb} , h_{re}/h_{fb} .
- [53] Explain thermal runaway. How it can be prevented.
- [54] Define FET parameters and write the relation between them.
- [55] What are Drain Characteristics and transfer characteristics?
- [56] Explain the construction and working of FET
- [57] What is feedback? Name different types.
- [58] What is the effect of negative feedback on the characteristics of an amplifier?
- [59] Why common collector amplifier is known as emitter follower circuit?
- [60] What is the application of emitter follower ckt?
- [61] What is cascading and cascoding? Why do you cascade the amplifier ckts.?
- [62] How do you determine the value of capacitor?
- [63] Write down the diode current equation.
- [64] Write symbols of various passive and active components
- [65] How do you determine the value of resistor by color code method?
- [66] What is tolerance and power rating of resistor?
- [67] Name different types of resistors.
- [68] How do you classify resistors?
- [69] Name different types of capacitors.
- [70] What are clipping circuits? Classify them.
- [71] Mention the application of clipping circuits.
- [72] What are clamping circuits? Classify them
- [73] What is the other name of clamping circuits?
- [74] Mention the applications of clamping circuits.
- [75] What is Darlington emitter follower circuit?
- [76] Can we increase the number of transistors in Darlington emitter follower circuit?
- [77] Name different types of Emitter follower circuits.
- [78] What is an Oscillator? Classify them.
- [79] What are damped & Un-damped Oscillations?
- [80] What are Barkhausen's criteria?
- [81] What type of oscillator has got more frequency stability?
- [82] What is the disadvantage of Hartley & Colpit's Oscillator?
- [83] Why RC tank Circuit Oscillator is used for AF range?
- [84] Why LC tank Circuit Oscillator is used for RF range?
- [85] What type of feedback is used in Oscillator circuit?
- [86] In a Transistor type No. SL 100 and in Diode BY 127, what does SL and BY stands for?
- [87] Classify Amplifiers based on: operating point selection.

- [88] What is the efficiency of Class B push pull amplifier?
- [89] What is the drawback of Class B Push pull Amplifier? How it is eliminated.
- [90] What is the advantage of having complimentary symmetry push pull amplifier?
- [91] What is Bootstrapping? What is the advantage of bootstrapping?
- [92] State Thevenin's Theorem and Maximum power transfer theorem.
- [93] What is the figure of merit of resonance circuit?
- [94] What is the application of resonant circuit?
- [95] What is a rectifier? Classify.
- [96] What is the efficiency of half wave and full wave rectifier?
- [97] What is the advantage of Bridge rectifier of Centre tapped type FWR.
- [98] What is the different between Darlington emitter follower circuit & Voltage follower circuit using Op-Amp. Which is better.

For more information and queries visit:

www.ajaybolar.weebly.com

BIBLIOGRAPHY

- [1] “Electronic devices and circuit theory”, Robert L. Boylestad and Louis Nashelsky.
- [2] “Integrated electronics”, Jacob Millman and Christos C Halkias.
- [3] “Electronic devices and circuits”, David A. Bell.
- [4] “Electronic devices and circuits”, G.K.Mittal.

For more information and queries visit:

www.ajaybolar.weebly.com