

Capacitance and Dielectrics

Capacitors

Device for storing electrical energy which can then be released in a controlled manner

Consists of two conductors, carrying charges of q and $-q$, that are separated, usually by a nonconducting material - an insulator


Symbol in circuits is 

It takes work, which is then stored as potential energy in the electric field that is set up between the two plates, to place charges on the conducting plates of the capacitor


Since there is an electric field between the plates there is also a potential difference between the plates

Capacitors

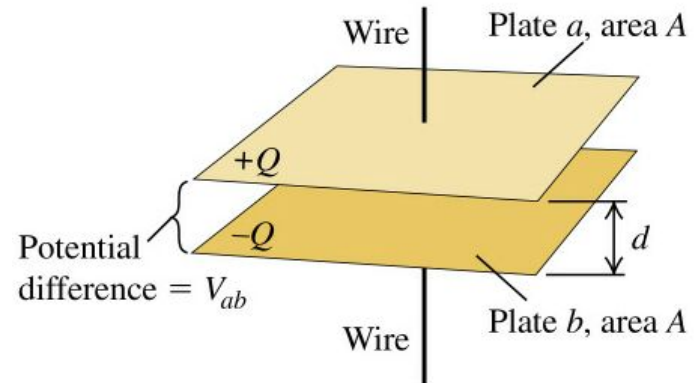We usually talk about capacitors in terms of parallel conducting plates



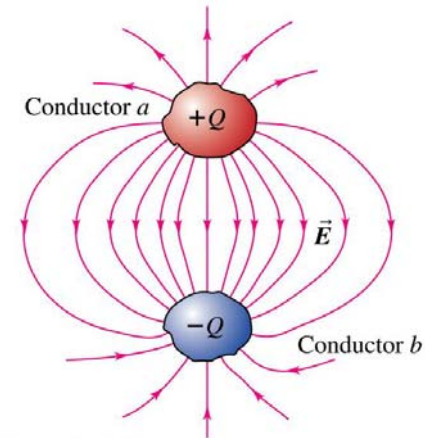They in fact can be any two conducting objects



Copyright © 2004 Pearson Education, Inc., publishing as Addison Wesley.

Capacitance

The capacitance is defined to be the ratio of the amount of charge that is on the capacitor to the potential difference between the plates at this point

$$C = \frac{Q}{V_{ab}}$$

Units are

$$1 \text{ farad} = \frac{1 \text{ Coulomb}}{1 \text{ Volt}}$$


Calculating the Capacitance

We start with the simplest form – two parallel conducting plates separated by vacuum

Let the conducting plates have area A and be separated by a distance d

The magnitude of the electric field between the two plates is given by

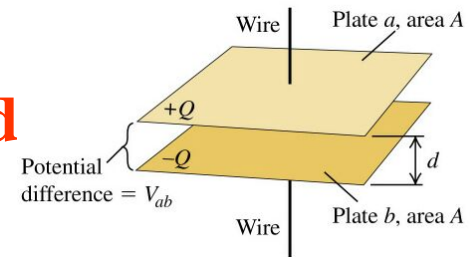We treat the field as being uniform allowing us to write



$$E = \frac{\sigma}{\epsilon_0} = \frac{Q}{\epsilon_0 A}$$

$$V_{ab} = Ed = \frac{Qd}{\epsilon_0 A}$$

Calculating the Capacitance

Putting this all together, we have for the capacitance

$$C = \frac{Q}{V_{ab}} = \epsilon_0 \frac{A}{d}$$

The capacitance is only dependent upon the geometry of the capacitor

1 farad Capacitor

Given a 1 farad parallel plate capacitor having a plate separation of 1mm. What is the area of the plates?

We start with $C = \epsilon_0 \frac{A}{d}$

And rearrange to solve for A , giving


$$A = \frac{C d}{\epsilon_0} = \frac{(1.0F)(1.0 \times 10^{-3}m)}{8.85 \times 10^{-12} F / m}$$
$$= 1.1 \times 10^8 m^2$$

This corresponds to a square about 10km on a side!

Series or Parallel Capacitors


Sometimes in order to obtain needed values of capacitance, capacitors are combined in either

Series

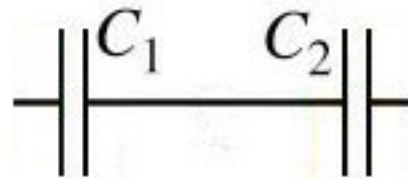

or


Parallel

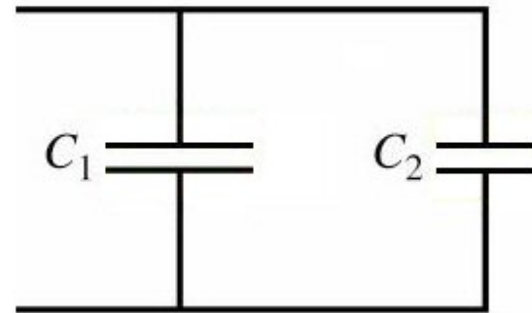


Capacitors in Series

Capacitors are often combined in series and the question then becomes what is the equivalent capacitance?


Given

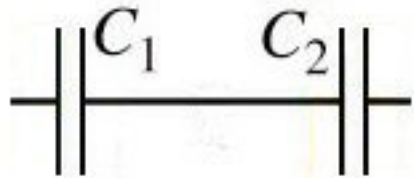


what is

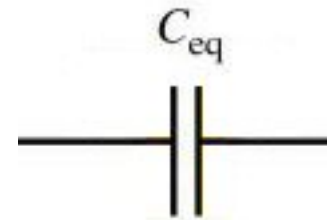

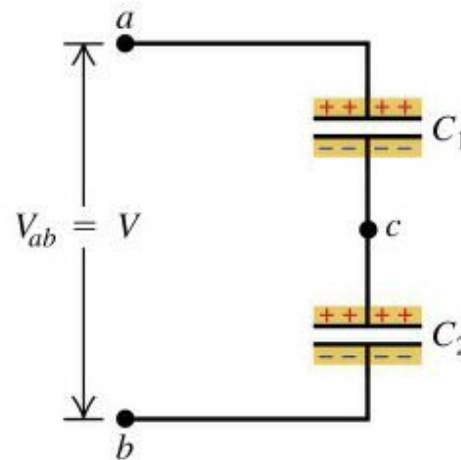We start by putting a voltage, V_{ab} , across the capacitors



Capacitors in Series

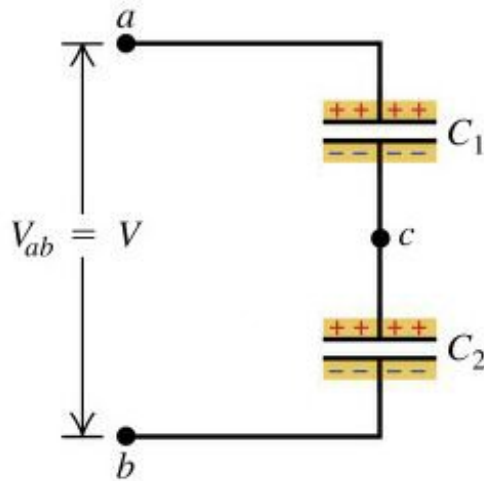

Capacitors become charged because of V_{ab}

If upper plate of C_1 gets a charge of $+Q$,

Then the lower plate of C_1 gets a charge of $-Q$

What happens with C_2 ?

Since there is no source of charge at point c , and we have effectively put a charge of $-Q$ on the lower plate of C_1 , the upper plate of C_2 gets a charge of $+Q$

Charge Conservation

This then means that lower plate of C_2 has a charge of $-Q$

Capacitors in Series

We also have to have that the potential across C_1 plus the potential across C_2 should equal the potential drop across the two capacitors

$$V_{ab} = V_{ac} + V_{cb} = V_1 + V_2$$

We have $V_1 = \frac{Q}{C_1}$ and $V_2 = \frac{Q}{C_2}$

Then $V_{ab} = \frac{Q}{C_1} + \frac{Q}{C_2}$

Dividing through by Q , we have $\frac{V_{ab}}{Q} = \frac{1}{C_1} + \frac{1}{C_2}$

Capacitors in Series

The equivalent capacitor will also have the same voltage across it

$$\frac{V_{ab}}{Q} = \frac{1}{C_1} + \frac{1}{C_2}$$

The left hand side is the inverse of the definition of capacitance

$$\frac{1}{C} = \frac{V}{Q}$$

So we then have for the equivalent capacitance

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$


If there are more than two capacitors in series, the resultant capacitance is given by

$$\frac{1}{C_{eq}} = \sum_i \frac{1}{C_i}$$

Capacitors in Parallel

Capacitors can also be connected in parallel


Given

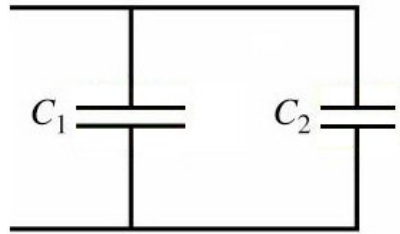


what is



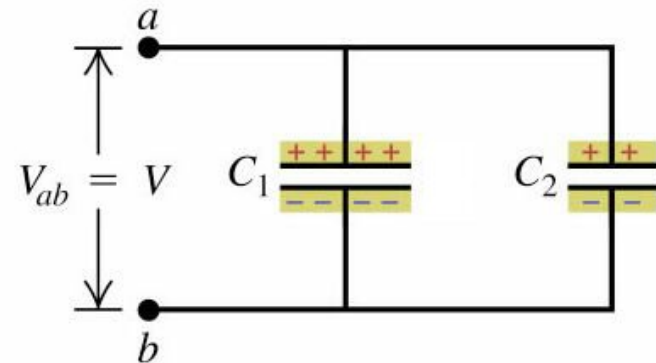Again we start by putting a voltage across a and b



Capacitors in Parallel

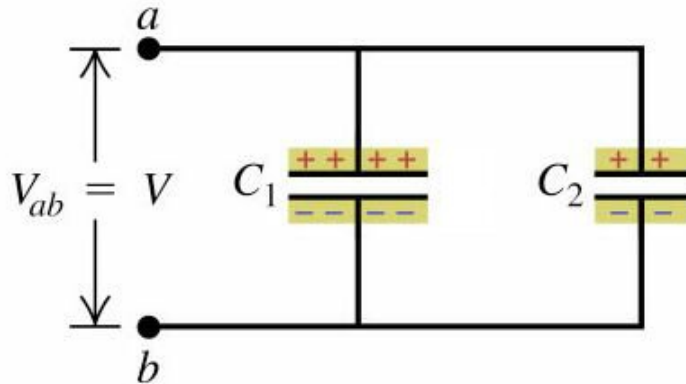

The upper plates of both capacitors are at the same potential

Likewise for the bottom plates

We have that $V_1 = V_2 = V_{ab}$

Now $V_1 = \frac{Q_1}{C_1}$ and $V_2 = \frac{Q_2}{C_2}$

or

$Q_1 = C_1 V$ and $Q_2 = C_2 V$

Capacitors in Parallel

The equivalent capacitor will have the same voltage across it, as do the capacitors in parallel

But what about the charge on the equivalent capacitor?

The equivalent capacitor will have the same total charge

$$Q = Q_1 + Q_2$$

Using this we then have

$$Q = Q_1 + Q_2$$

$$C_{eq}V = C_1V + C_2V$$

or

$$C_{eq} = C_1 + C_2$$


Capacitors in Parallel

The equivalent capacitance is just the sum of the two capacitors

If we have more than two, the resultant capacitance is just the sum of the individual capacitances

$$C_{eq} = \sum_i C_i$$

Example 1

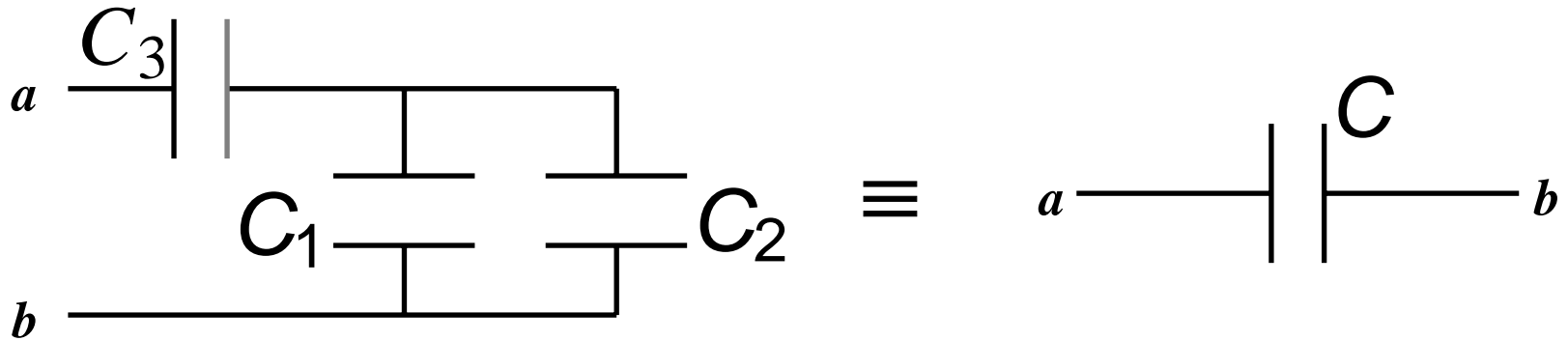

Where do we start?


Recognize that C_1 and C_2 are parallel with each other and combine these to get C_{12}

This C_{12} is then in series with with C_3


The resultant capacitance is then given by

$$\frac{1}{C} = \frac{1}{C_3} + \frac{1}{C_1 + C_2} \quad \Rightarrow \quad C = \frac{C_3(C_1 + C_2)}{C_1 + C_2 + C_3}$$


Example 2

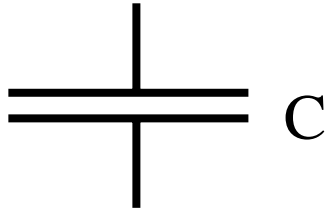

Configuration A

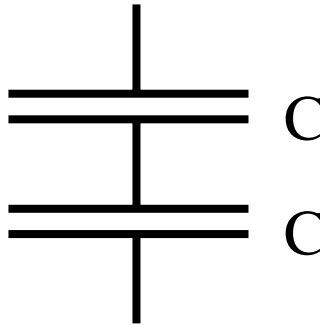

Configuration B

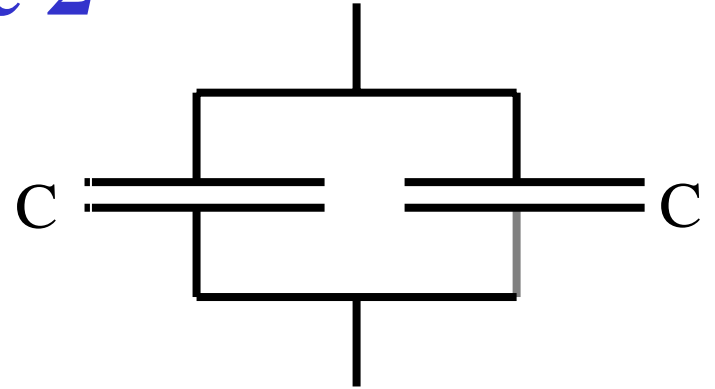

Configuration C

Three configurations are constructed using identical capacitors
Which of these configurations has the lowest overall capacitance?

a) Configuration A

b) Configuration B

c) Configuration C

The net capacitance for A is just C

In B, the caps
are in series and
the resultant is
given by

$$\frac{1}{C_{net}} = \frac{1}{C} + \frac{1}{C} = \frac{2}{C} \Rightarrow C_{net} = \frac{C}{2}$$


In C, the caps are in parallel and
the resultant is given by

$$C_{net} = C + C = 2C$$

Example 3

A circuit consists of three unequal capacitors C_1 , C_2 , and C_3 which are connected to a battery of emf E . The capacitors obtain charges Q_1 , Q_2 , Q_3 , and have voltages across their plates V_1 , V_2 , and V_3 . C_{eq} is the equivalent capacitance of the circuit.

Check all of the following that apply:

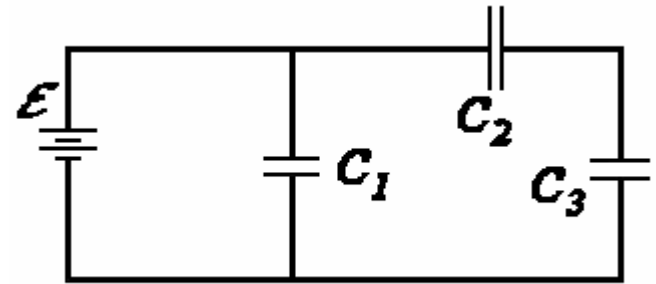

a) $Q_1 = Q_2$

b) $Q_2 = Q_3$

c) $V_2 = V_3$

d) $E = V_1$


e) $V_1 < V_2$

f) $C_{eq} > C_1$

A detailed worksheet is available detailing the answers

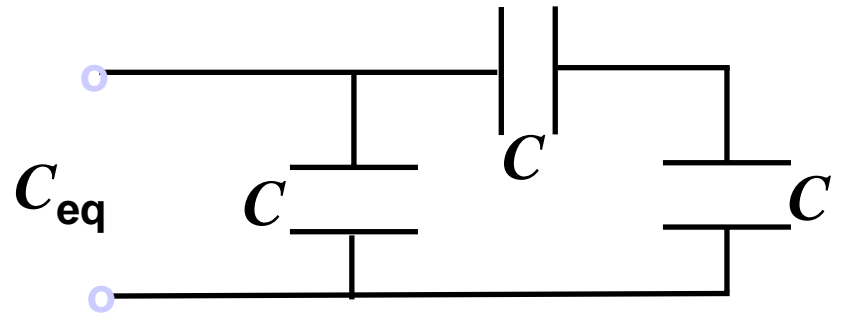Example 4


What is the equivalent capacitance, C_{eq} , of the combination shown?



(a) $C_{eq} = (3/2)C$

(b) $C_{eq} = (2/3)C$

(c) $C_{eq} = 3C$

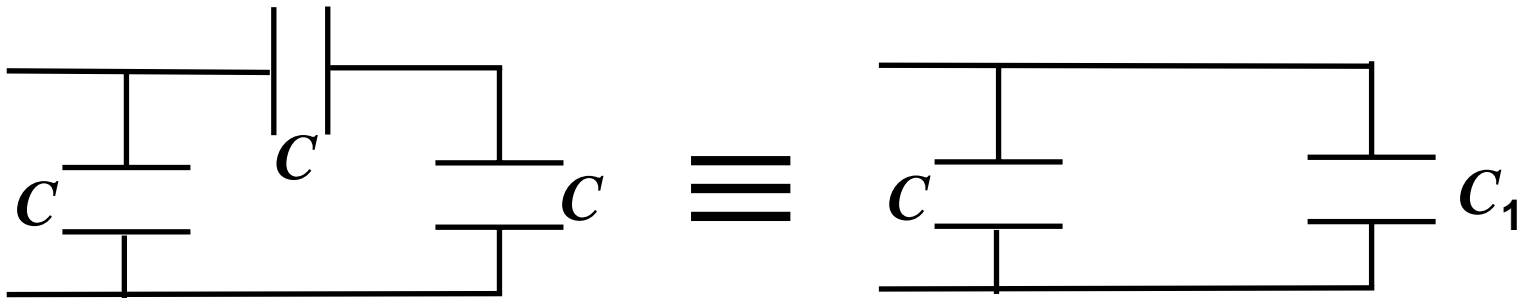

$$\frac{1}{C_1} = \frac{1}{C} + \frac{1}{C} \Rightarrow C_1 = \frac{C}{2} \Rightarrow C_{eq} = C + \frac{C}{2} = \frac{3}{2}C$$

Energy Stored in a Capacitor

Electrical Potential energy is stored in a capacitor

The energy comes from the work that is done in charging the capacitor

Let q and v be the intermediate charge and potential on the capacitor

The incremental work done in bringing an incremental charge, dq , to the capacitor is then given by

$$dW = v dq = \frac{q dq}{C}$$

Energy Stored in a Capacitor

The total work done is just the integral of this equation from 0 to Q

$$W = \frac{1}{C} \int_0^Q q \, dq = \frac{Q^2}{2C}$$

Using the relationship between capacitance, voltage and charge we also obtain


$$U = \frac{Q^2}{2C} = \frac{1}{2} C V^2 = \frac{1}{2} Q V$$

where U is the stored potential energy

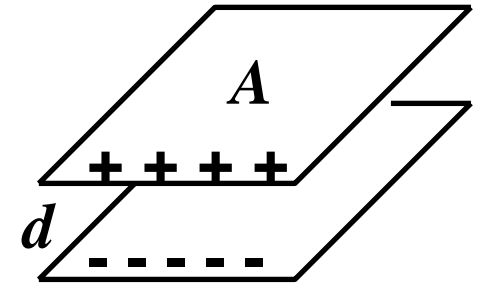Example 5

Suppose the capacitor shown here is charged to Q and then the battery is *disconnected*

Now suppose you pull the plates further apart so that the final separation is d_1



Which of the quantities Q , C , V , U , E change?

Q: Charge on the capacitor does not change

C: Capacitance Decreases

V: Voltage Increases

U: Potential Energy Increases

E: Electric Field does not change

How do these quantities change?

Answers:


$$C_1 = \frac{d}{d_1} C$$

$$V_1 = \frac{d_1}{d} V$$

$$U_1 = \frac{d_1}{d} U$$

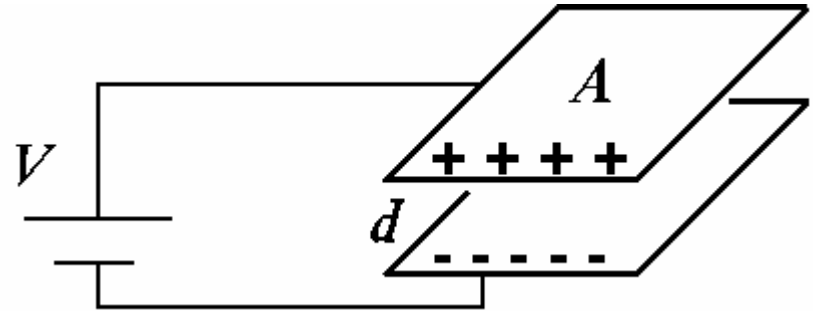Example 6

Suppose the battery (V) is kept attached to the capacitor



Again pull the plates apart from d to d_1

Now which quantities, if any, change?

Q: Charge Decreases

C: Capacitance Decreases

V: Voltage on capacitor does not change

U: Potential Energy Decreases

E: Electric Field Decreases

How much do these quantities change?

Answers:

$$Q_1 = \frac{d}{d_1} Q$$

$$C_1 = \frac{d}{d_1} C$$

$$U_1 = \frac{d}{d_1} U$$

$$E_1 = \frac{d}{d_1} E$$

Electric Field Energy Density

The potential energy that is stored in the capacitor can be thought of as being stored in the electric field that is in the region between the two plates of the capacitor

The quantity that is of interest is in fact the *energy density*

$$\text{Energy Density} = u = \frac{\frac{1}{2}CV^2}{Ad}$$

where A and d are the area of the capacitor plates and their separation, respectively

Electric Field Energy Density

Using $C = \epsilon_0 \frac{A}{d}$ and $V = E d$ we then have

$$u = \frac{1}{2} \epsilon_0 E^2$$

Even though we used the relationship for a parallel capacitor, this result holds for *all* capacitors regardless of configuration

This represents the energy density of the electric field in general

Dielectrics

Most capacitors have a nonconducting material between their plates

This nonconducting material, *a dielectric*, accomplishes three things

- 1) Solves mechanical problem of keeping the plates separated**
- 2) Increases the maximum potential difference allowed between the plates**
- 3) Increases the capacitance of a given capacitor over what it would be without the dielectric**

Dielectrics

Suppose we have a capacitor of value C_0 that is charged to a potential difference of V_0 and then removed from the charging source

We would then find that it has a charge of $Q = C_0 V_0$

We now insert the dielectric material into the capacitor

We find that the potential difference *decreases* by a factor K

$$V = \frac{V_0}{K}$$


Or equivalently the capacitance has *increased* by a factor of K

$$C = K C_0$$

This constant K is known as the dielectric constant and is dependent upon the material used and is a number greater than 1

Polarization

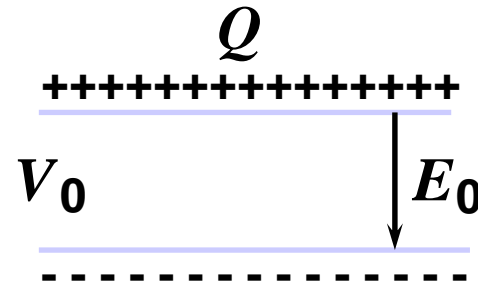
Without the dielectric in the capacitor, we have



The electric field points undiminished from the positive to the negative plate




With the dielectric in place we have

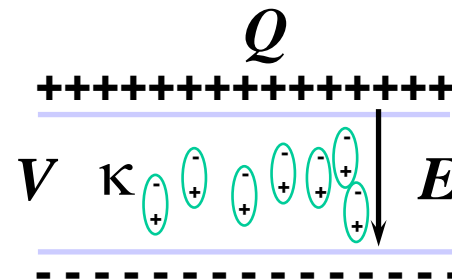

The electric field between the plates of the capacitor is reduced because some of the material within the dielectric rearranges so that their negative charges are oriented towards the positive plate

Polarization

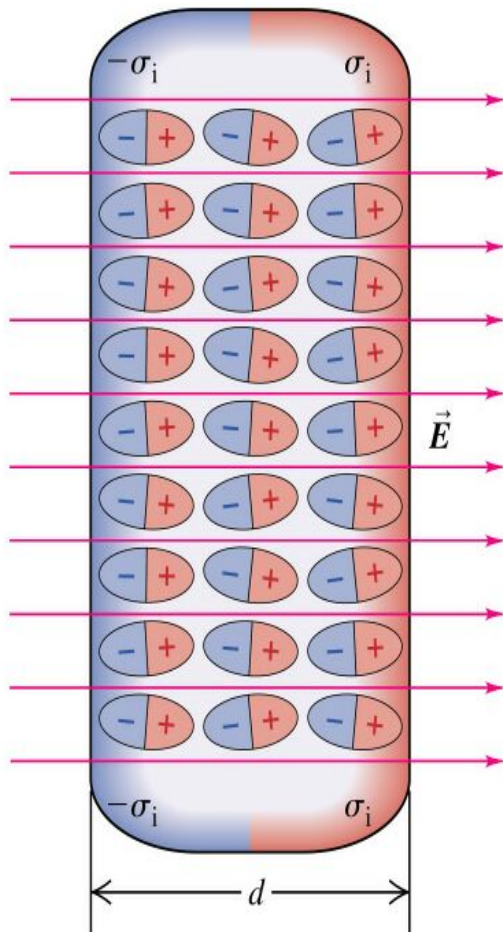

These rearranged charges set up an internal electric field that opposes the electric field due to the charges on the plates

The net electric field is given by

$$\mathbf{E} = \frac{\mathbf{E}_0}{K}$$

Redefinitions

We now redefine several quantities using the dielectric constant

We define the permittivity of the dielectric as being

$$\boldsymbol{\varepsilon} = \boldsymbol{K} \boldsymbol{\varepsilon}_0$$


Capacitance:
$$C = \boldsymbol{K} C_0 = \boldsymbol{K} \boldsymbol{\varepsilon}_0 \frac{A}{d} = \boldsymbol{\varepsilon} \frac{A}{d}$$

with the last two relationships holding for a parallel plate capacitor

Energy Density
$$u = \frac{1}{2} \boldsymbol{K} \boldsymbol{\varepsilon}_0 \boldsymbol{E}^2 = \frac{1}{2} \boldsymbol{\varepsilon} \boldsymbol{E}^2$$

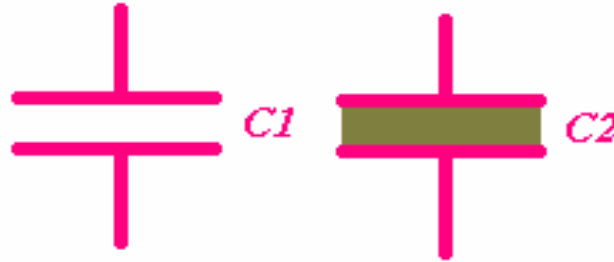Example 7

Two identical parallel plate capacitors are given the same charge Q , after which they are disconnected from the battery. After C_2 has been charged and disconnected it is filled with a dielectric.



Compare the voltages of the two capacitors.

a) $V_1 > V_2$

b) $V_1 = V_2$

c) $V_1 < V_2$

We have that $Q_1 = Q_2$ and that $C_2 = KC_1$

We also have that $C = Q/V$ or $V = Q/C$

Then $V_1 = \frac{Q_1}{C_1}$ and $V_2 = \frac{Q_2}{C_2} = \frac{Q_1}{KC_1} = \frac{1}{K}V_1$