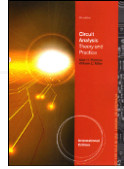


Chapter 07

Series-Parallel Circuits

Source: Circuit Analysis: Theory and Practice ©Delmar Cengage Learning




The Series-Parallel Network

- Complex circuits
 - May be separated both series and/or parallel elements
 - Combinations which are neither series nor parallel
- To analyze a circuit
 - Identify elements in series and elements in parallel

For example:

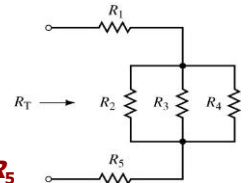$R_2, R_3,$ and R_4 are in parallel,
Series with R_1 and R_5



$$R_T = R_1 + (R_2 // R_3 // R_4) + R_5$$


C-C Tsai

The Series-Parallel Network


In this circuit:

- R_3 and R_4 are in parallel
- Combination is in series with R_2
- Entire combination is in parallel with R_1

$$R_T = R_1 // [R_2 + (R_3 // R_4)]$$

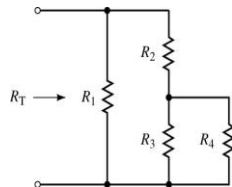

Another example:

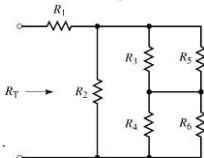

C-C

Analysis of Series-Parallel Circuits

Rules for analyzing series and parallel circuits apply:

- Same current occurs through all series elements**
- Same voltage occurs across all parallel elements**
- KVL and KCL apply for all circuits**


Steps to simplify a circuit:

- Redraw complicated circuits **showing the source at the left-hand side** and then label all nodes
- Simplify recognizable combinations of components
- Determine **equivalent resistance R_T** and solve for the total current
- Label polarities of voltage drops on all components
- Calculate how currents and voltages split between elements** in a circuit
- Verify your answer by taking a different approach

C-C Tsai

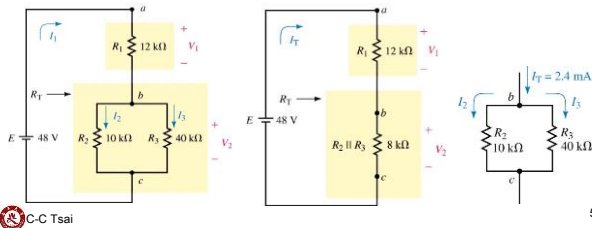Example: Analysis of Series-Parallel Circuits

- Combining R_2 and R_3 in parallel
- Circuit reduces to a series circuit
- Use **Voltage Divider Rule** to determine V_{ab} and V_{bc}
- Note that $V_{bc} = V_2$ is the voltage across R_2 and R_3
- Calculate all currents from **Ohm's Law**.




C-C Tsai

5

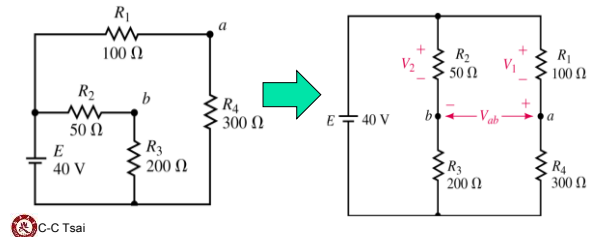Example: Analysis of Series-Parallel Circuits

Find the voltage V_{ab}

- Redraw circuit in simple form
- Determined by combination of voltages across R_1 and R_2 , or R_3 and R_4 (use voltage divider rule)




C-C Tsai

6

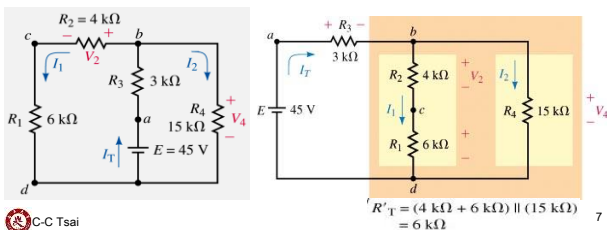Example: Analysis of Series-Parallel Circuits

Find currents in the circuit

- First redraw the circuit and move source branch all the way to left and reduce circuit to a series circuit
- Voltages: Use Ohm's Law or Voltage Divider Rule**
- Currents: Use Ohm's Law or Current Divider Rule**




C-C Tsai

7

Example: Analysis of Series-Parallel Circuits

Find V_{ab}

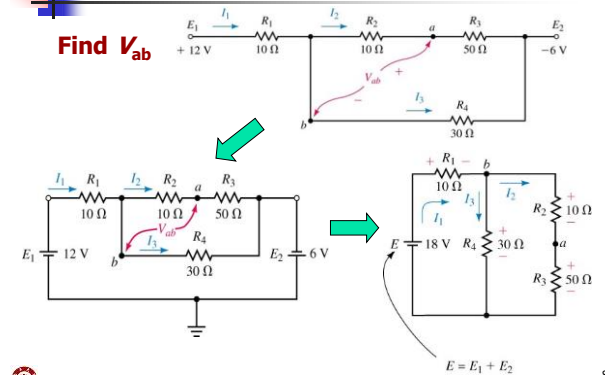


C-C Tsai

8

Example: Analysis of Series-Parallel Circuits

Find V_{ab}

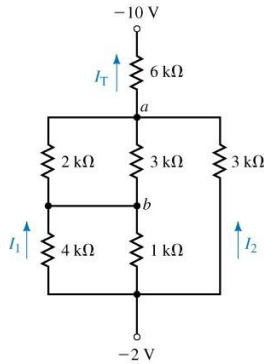

C-C Tsai


9

Example: Bridge Circuit

Determine V_{ab} and I if R_x is a short circuit (0Ω)

$$V_{ab} = V_a - V_b = 8V - 0V = 8V$$
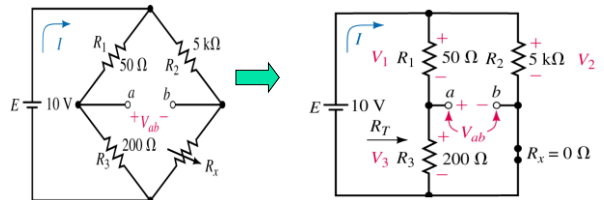
$$I = 10 / [(50+200) // 5k] = 10 / 238 = 42.2mA$$



C-C Tsai


10

Example: Bridge Circuit

Determine V_{ab} and I if circuit has $R_x = 15 k\Omega$

$$V_{ab} = V_a - V_b = 8V - 7.5V = 0.5V$$
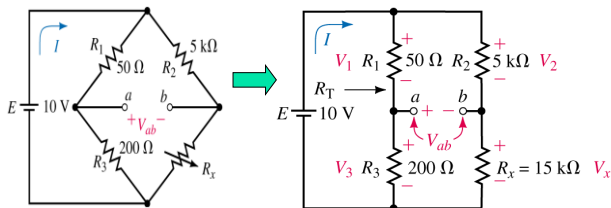
$$I = 10 / [(50+200) // (5k+15k)] = 10/247 = 40.5mA$$



C-C Tsai


11

Bridge Circuit

Determine V_{ab} and I if R_x is open

$$V_{ab} = V_a - V_b = 8V - 10V = -2V$$

$$I = 10 / (50+200) = 10 / 250 = 40mA$$

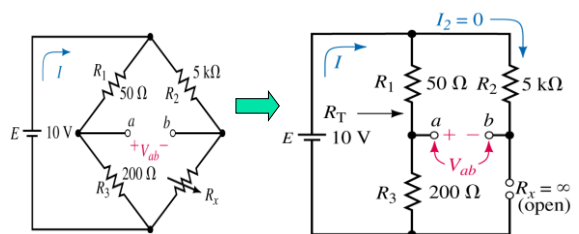

C-C Tsai

12


*Transistor Circuit

Transistor is a device that amplifies a signal

- Operating point of a transistor circuit is determined by a dc voltage source

Determine some dc voltages and currents

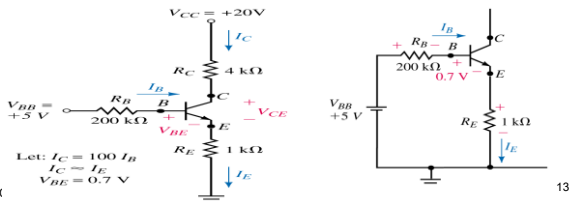
- Apply KVL: $V_{BB} = R_B I_B + V_{BE} + R_E I_E$
- Using $I_E = 100 I_B$ we find $I_B = 14.3 \mu\text{A}$.



13

Potentiometers

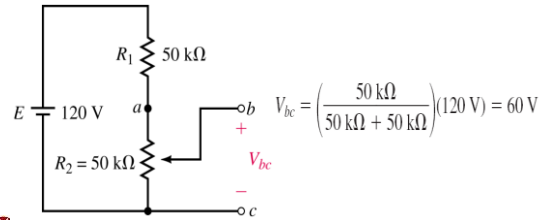- Example of variable resistor used as potentiometer
- Moveable terminal is **at uppermost position**
 then $V_{bc} = 60 \text{ V}$
- At the lowermost position**
 then $V_{bc} = 0 \text{ V}$




C-C Tsai

14

Potentiometers

V_{bc} changes

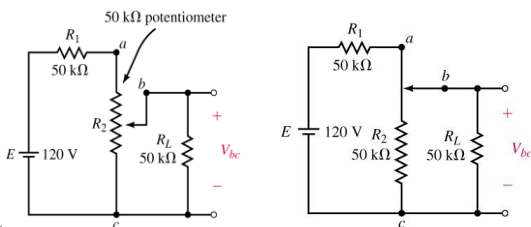- If load is added to circuit **at upper position**
 then $V_{bc} = 40 \text{ V}$
- At the lower position**
 then $V_{bc} = 0 \text{ V}$



15

Load Effects of Instruments

Actual value


$$V_{R1} = 27 \text{ V} * \frac{5 \text{ M}\Omega}{(5 \text{ M}\Omega + 10 \text{ M}\Omega)} = 9 \text{ V}$$

Reading value

$$V_{R1} = 27 \text{ V} * \frac{3.3 \text{ M}\Omega}{(3.3 \text{ M}\Omega + 10 \text{ M}\Omega)} = 6.75 \text{ V}$$

Loading effect

$$= (9 - 6.75) / 9 = 25\%$$

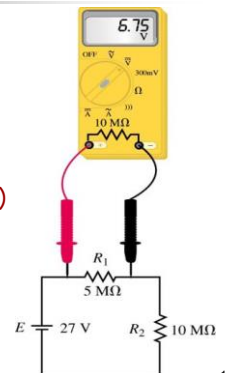

C-C Tsai

16

Example: Load Effects of Instruments

Actual value


$$V_{R_2} = 27V * \frac{10M}{(5M+10M)} = 18V$$

Reading value

$$V_{R_2} = 27V * \frac{5M}{(5M+5M)} = 13.5V$$

Loading effect


$$= (18 - 13.5) / 18 = 25\%$$

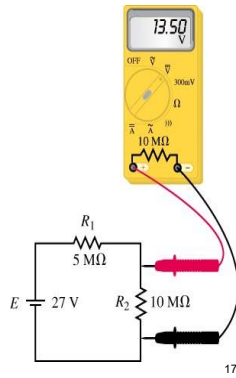

C-C Tsai

17

Example: Load Effects of Instruments

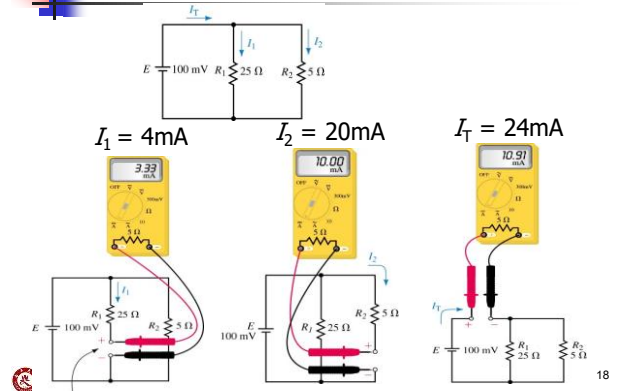


C-C Tsai

18

Circuit Analysis Using Multisim

Use Multisim to find the following quantities for the circuit shown

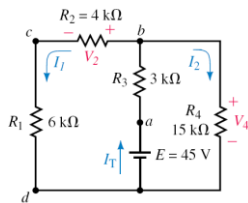- Total resistance, R_T**
- Voltages V_2 and V_4**
- Currents I_T , I_1 , and I_2**




C-C Tsai

19

Get R_T Using Multisim

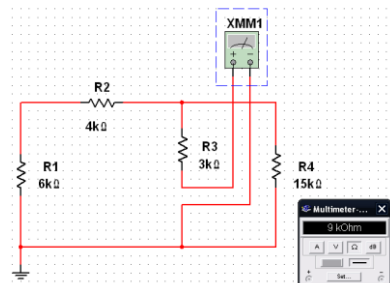
- Construct the circuit for determining the total resistance R_T



C-C Tsai

20


Get Voltages and currents Using Multisim

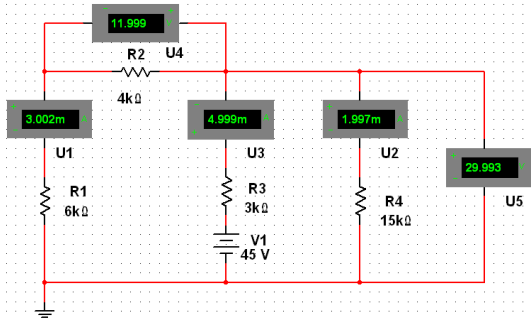


Kernel abilities

1. Can recognize which parts are in series or parallel for a series-parallel circuit.
2. Can compute the total resistance R_t of resistors $R_1 \sim R_n$ in series-parallel.
3. Can recognize KVL and KCL for applying a series-parallel circuit.
4. Can recognize the voltage divider and current divider for applying a series-parallel circuit.
5. Can recognize the loading effect for measuring voltage and current.

Problem 10: Find R_{ab} and R_{bc}

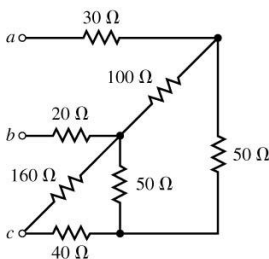

Problem 35: Find E

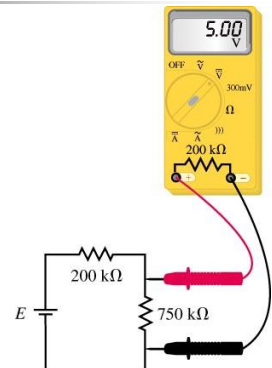

Problem 37: Find the reading of ammeter

