
Logic and Computer Design Fundamentals

Chapter 2 – Combinational Logic Circuits

Part 1 – Gate Circuits and Boolean Equations

Charles Kime & Thomas Kaminski

© 2008 Pearson Education, Inc.

(Hyperlinks are active in View Show mode)

Updated by Dr. Waleed Dweik

Combinational Logic Circuits

- Digital (logic) circuits are hardware components that manipulate binary information.
- Integrated circuits: transistors and interconnections.
 - Basic circuits is referred to as *logic gates*
 - The outputs of gates are applied to the inputs of other gates to form a digital circuit
- Combinational? Later...

Overview

- **Part 1 – Gate Circuits and Boolean Equations**
 - Binary Logic and Gates
 - Boolean Algebra
 - Standard Forms

- **Part 2 – Circuit Optimization**
 - Two-Level Optimization
 - Map Manipulation
 - Practical Optimization (Espresso)
 - Multi-Level Circuit Optimization

- **Part 3 – Additional Gates and Circuits**
 - Other Gate Types
 - Exclusive-OR Operator and Gates
 - High-Impedance Outputs

Binary Logic and Gates

- **Binary variables** take on one of two values
- **Logical operators** operate on binary values and binary variables
- Basic logical operators are the logic functions **AND**, **OR** and **NOT**
- **Logic gates** implement logic functions
- **Boolean Algebra**: a useful mathematical system for specifying and transforming logic functions
- We study Boolean algebra as a foundation for designing and analyzing digital systems!

Binary Variables

- Recall that the two binary values have different names:
 - True/False
 - On/Off
 - Yes/No
 - 1/0

- We use 1 and 0 to denote the two values

- Variable identifier examples:
 - A, B, y, z, or X_1 for now
 - RESET, START_IT, or ADD1 later

Logical Operations

- The three basic logical operations are:
 - AND
 - OR
 - NOT
- AND is denoted by a dot (\cdot) or (\wedge)
- OR is denoted by a plus ($+$) or (\vee)
- NOT is denoted by an over-bar ($\bar{\quad}$), a single quote mark ($'$) after, or (\sim) before the variable

Notation Examples

- Examples:
 - $Z = X \cdot Y = XY = X \wedge Y$: is read “Z is equal to X AND Y”
 - $Z = 1$ if and only if $X = 1$ and $Y = 1$; otherwise, $Z = 0$

 - $Z = X + Y = X \vee Y$: is read “Z is equal to X OR Y”
 - $Z = 1$ if (only $X = 1$) or if (only $Y = 1$) or if ($X = 1$ and $Y = 1$)

 - $Z = \bar{X} = X' = \sim X$: is read “Z is equal to NOT X”
 - $Z = 1$ if $X = 0$; otherwise, $Z = 0$

- Notice the difference between arithmetic addition and logical OR:

- The statement:

$1 + 1 = 2$ (read “one plus one equals two”)

is not the same as

$1 + 1 = 1$ (read “1 or 1 equals 1”)

Operator Definitions

- Operations are defined on the values "0" and "1" for each operator:

AND
$0 \cdot 0 = 0$
$0 \cdot 1 = 0$
$1 \cdot 0 = 0$
$1 \cdot 1 = 1$

OR
$0 + 0 = 0$
$0 + 1 = 1$
$1 + 0 = 1$
$1 + 1 = 1$

NOT
$\bar{0} = 1$
$\bar{1} = 0$

Truth Tables

- **Truth table** - a tabular listing of the values of a function for all possible combinations of values on its arguments
- Example: Truth tables for the basic logic operations:

AND		
Inputs		Output
X	Y	$Z = X \cdot Y$
0	0	0
0	1	0
1	0	0
1	1	1

OR		
Inputs		Output
X	Y	$Z = X + Y$
0	0	0
0	1	1
1	0	1
1	1	1


NOT	
Inputs	Output
X	$Z = \bar{X}$
0	1
1	0

Logic Function Implementation


■ Using Switches

- For inputs:
 - logic 1 is switch closed
 - logic 0 is switch open
- For outputs:
 - logic 1 is light on
 - logic 0 is light off
- NOT uses a switch such that:
 - logic 1 is switch open
 - logic 0 is switch closed


Switches in parallel => OR

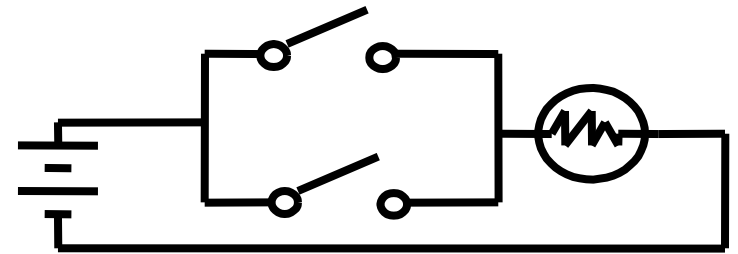

Switches in series => AND

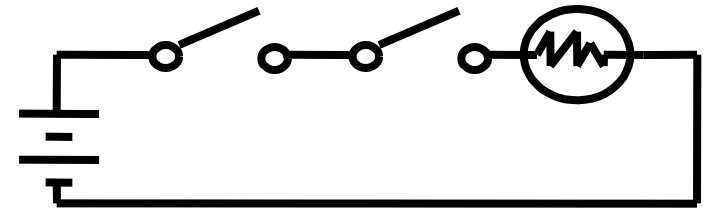


Normally-closed switch => NOT

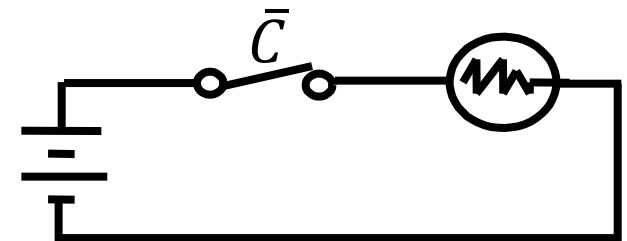

Logic Function Implementation (Continued)

- Example: Logic Using Switches

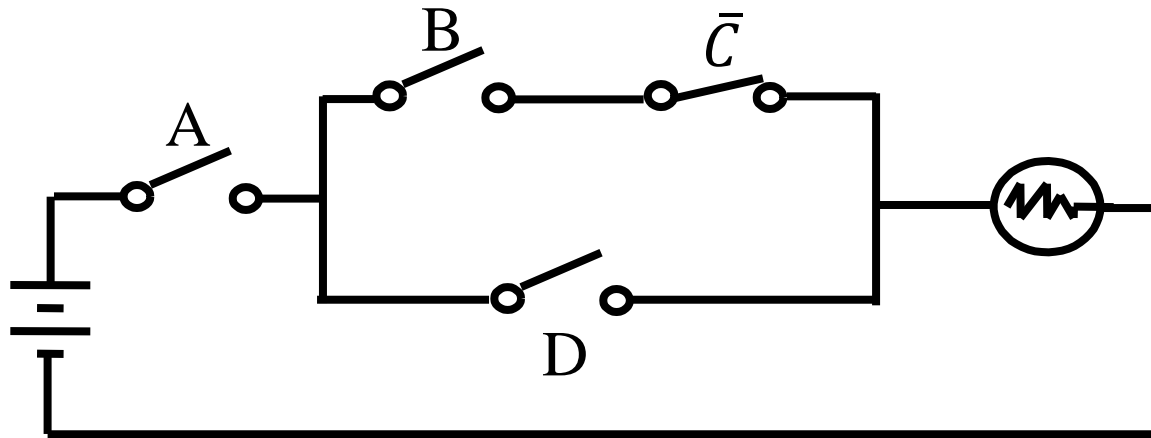




- Light is **ON** ($L = 1$) for $L(A, B, C, D) = A \cdot (B\bar{C} + D) = AB\bar{C} + AD$ and **OFF** ($L = 0$), otherwise.
- Useful model for relay circuits and for CMOS gate circuits, the foundation of current digital logic technology

Logic Gates

- In the earliest computers, switches were opened and closed by magnetic fields produced by energizing coils in *relays*. The switches in turn opened and closed the current paths
- Later, *vacuum tubes* that open and close current paths electronically replaced relays
- Today, *transistors* are used as electronic switches that open and close current paths
- Optional: Chapter 6 – Part 1: The Design Space


Logic Gate Symbols and Behavior

- Logic gates have special symbols:

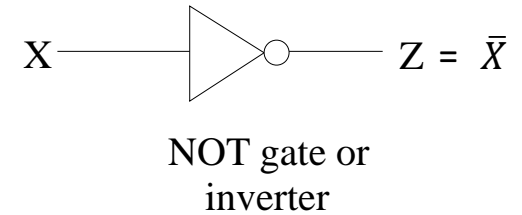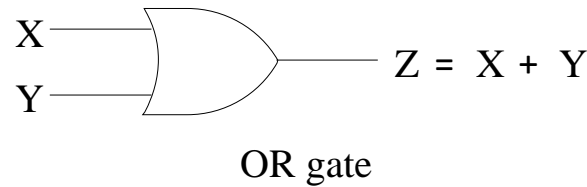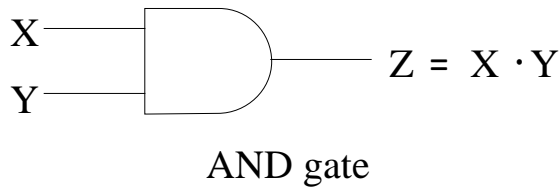

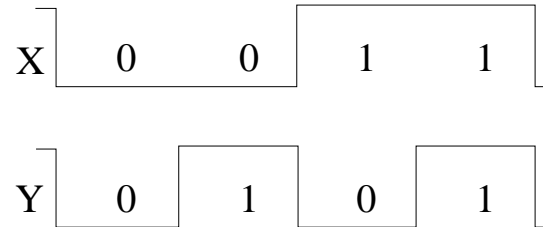(a) Graphic symbols


- And waveform behavior in time as follows:



(b) Timing diagram


Logic Gate Symbols and Behavior

- Logic gates have special symbols:

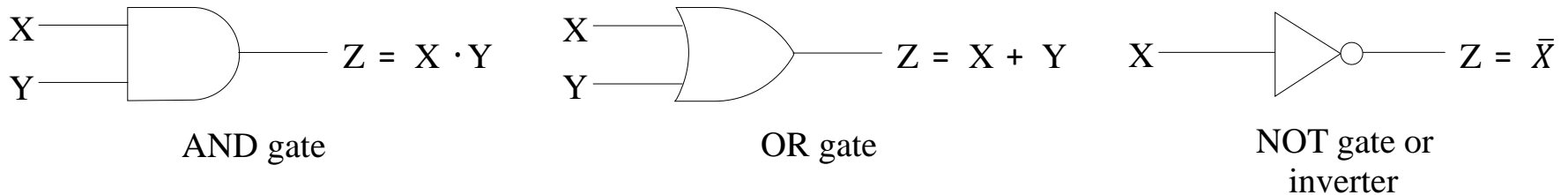

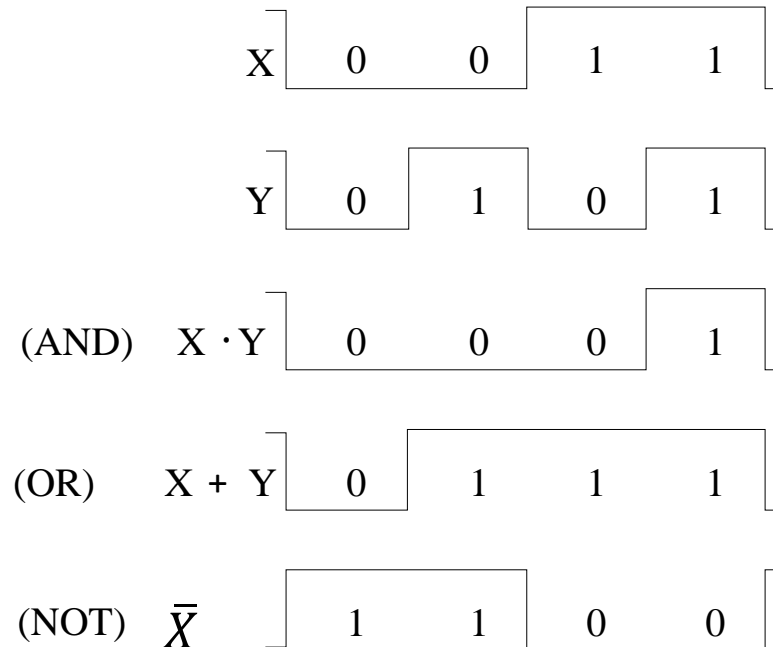(a) Graphic symbols


- And waveform behavior in time as follows:



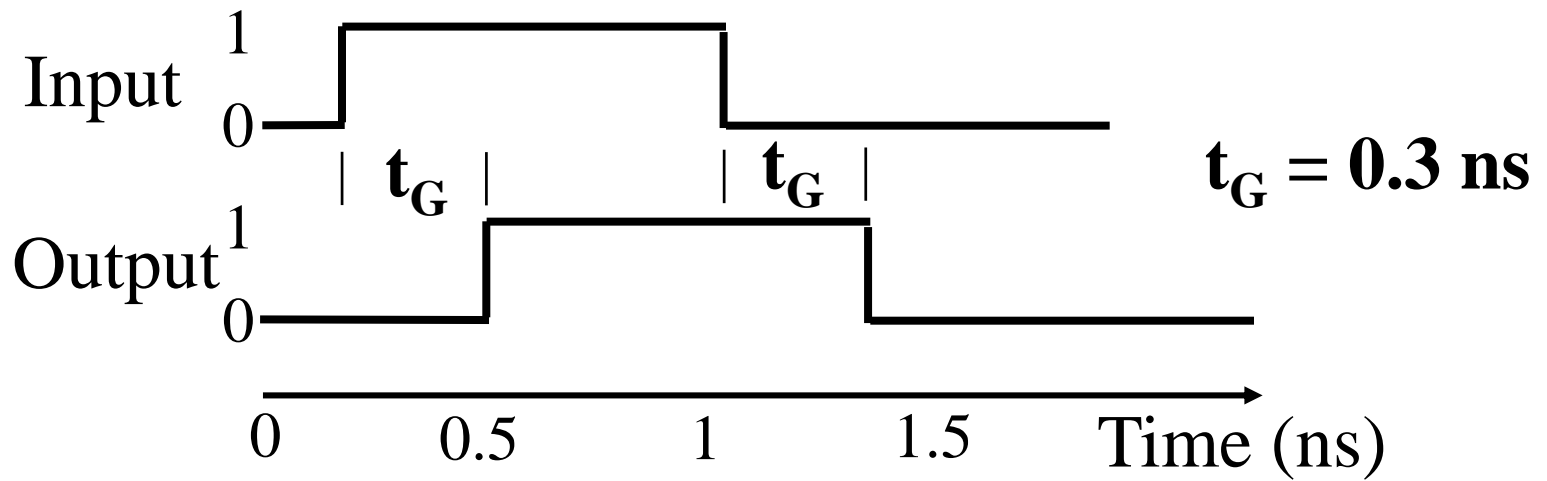(b) Timing diagram



Gate Delay

- In actual physical gates, if one or more input changes causes the output to change, the output change does not occur instantaneously
- The delay between an input change(s) and the resulting output change is the *gate delay* denoted by t_G :



Logic Gates: Inputs and Outputs

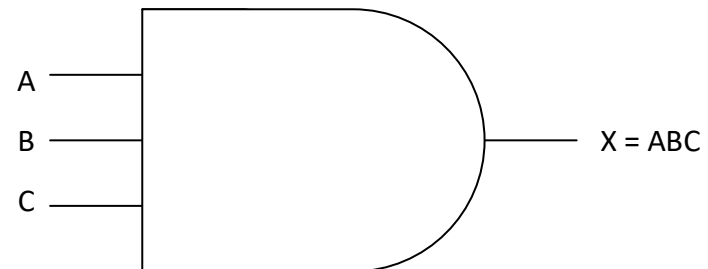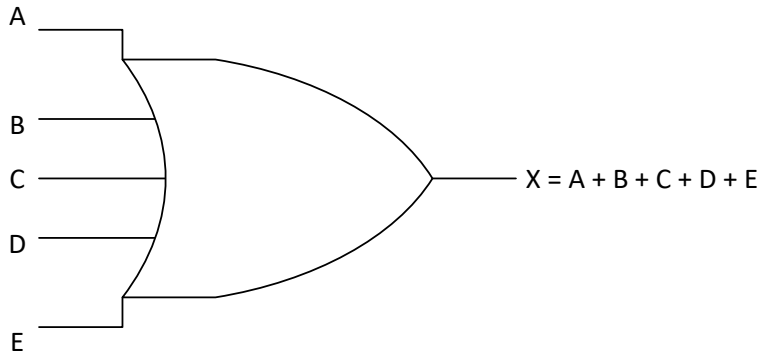- NOT (inverter)
 - Always one input and one output
- AND and OR gates
 - Always one output
 - Two or more inputs



Boolean Algebra

- An algebra dealing with binary variables and logic operations
 - Variables are designated by letters of the alphabet
 - Basic logic operations: AND, OR, and NOT
- ***A Boolean expression*** is an algebraic expression formed by using **binary variables, constants 0 and 1, the logic operation symbols, and parentheses**
 - E.g.: $X \cdot 1$, $A + B + C$, $(A + B)(C + D)$
- ***A Boolean function*** consists of a binary variable identifying the function followed by equals sign and a Boolean expression
 - E.g.: $F = A + B + C$, $L(D, X, A) = DX + \bar{A}$


Logic Diagrams and Expressions

1. Equation: $F = X + \bar{Y}Z$
2. Logic Diagram:
3. Truth Table:

Logic Diagrams and Expressions

1. Equation: $F = X + \bar{Y}Z$

2. Logic Diagram:

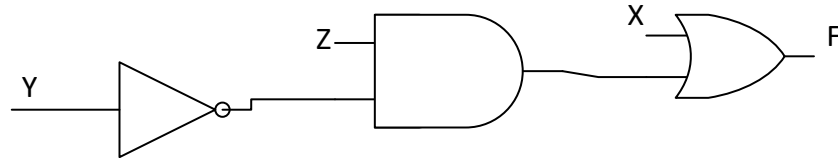

3. Truth Table:

- Boolean equations, truth tables and logic diagrams describe the same function!
- Truth tables are unique; expressions and logic diagrams are not. This gives flexibility in implementing functions.

X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Logic Diagrams and Expressions

1. Equation: $F = X + \bar{Y}Z$

2. Logic Diagram:

3. Truth Table:

- Boolean equations, truth tables and logic diagrams describe the same function!
- Truth tables are unique; expressions and logic diagrams are not. This gives flexibility in implementing functions.

X	Y	Z	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Example

- Draw the logic diagram and the truth table of the following Boolean function: $F(W, X, Y) = XY + W\bar{Y}$

- Logic Diagram:

- Truth Table:

W	X	Y	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

- This example represents a ***Single Output Function***


Example

- Draw the logic diagram and the truth table of the following Boolean function: $F(W, X, Y) = XY + W\bar{Y}$

- Logic Diagram:

- Truth Table:

W	X	Y	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

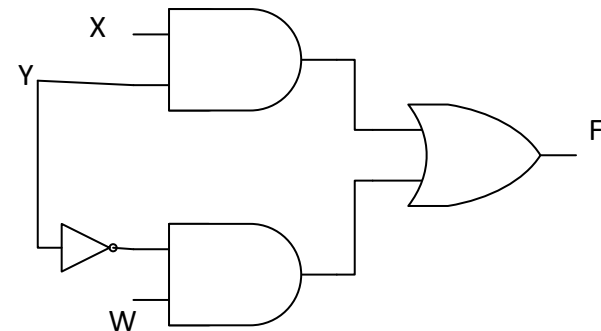

- This example represents a ***Single Output Function***

Example

- Draw the logic diagram and the truth table of the following Boolean functions: $F(W, X) = \bar{W}\bar{X} + W$, $G(W, X) = W + \bar{X}$
- Logic Diagram:
- Truth Table:

W	X	F	G
0	0		
0	1		
1	0		
1	1		


Example

- Draw the logic diagram and the truth table of the following Boolean functions: $F(W, X) = \bar{W}\bar{X} + W$, $G(W, X) = W + \bar{X}$

- Logic Diagram:

- Truth Table:


W	X	F	G
0	0	1	1
0	1	0	0
1	0	1	1
1	1	1	1

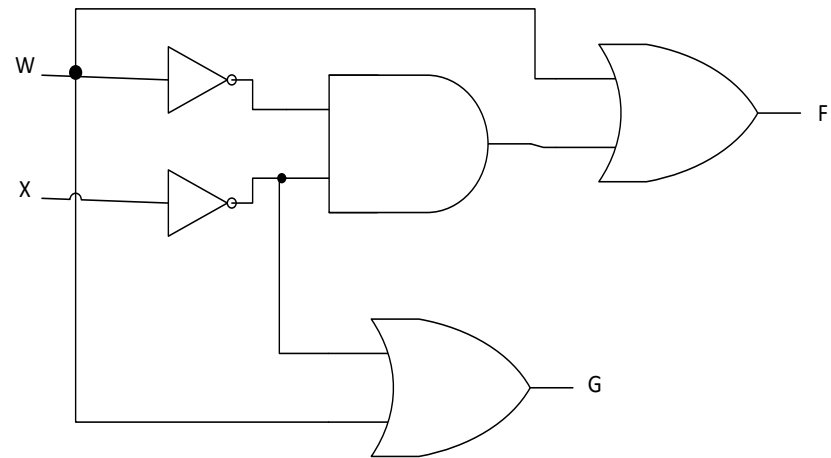

- This example represents a ***Multiple Output Function***

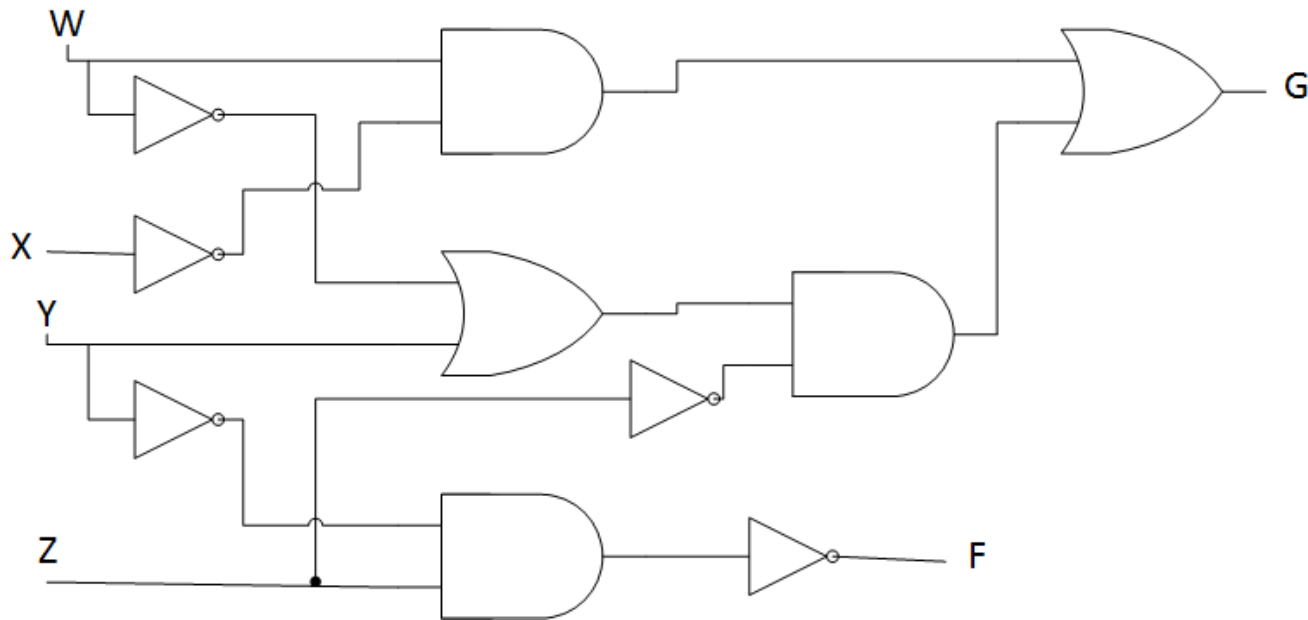Example:


- Given the following logic diagram, write the corresponding Boolean equation:



- Logic circuits of this type are called combinational logic circuits since the variables are combined by logical operations

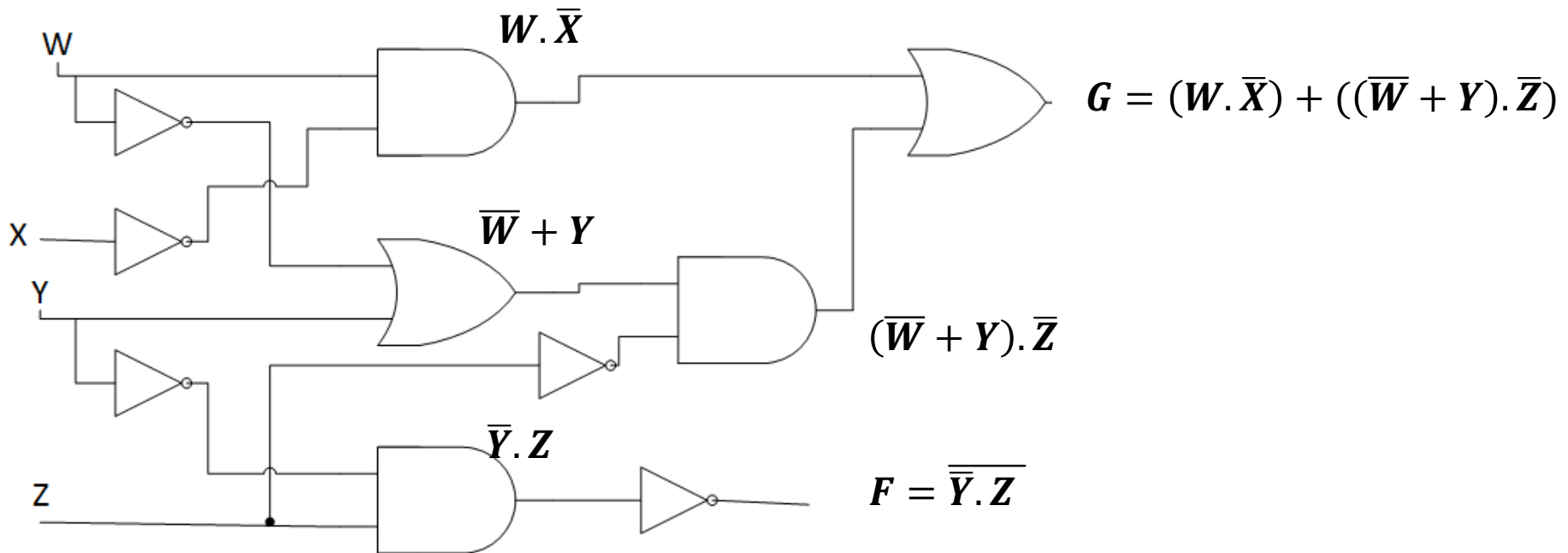Example:

- Given the following logic diagram, write the corresponding Boolean equation:



- Logic circuits of this type are called combinational logic circuits since the variables are combined by logical operations

Basic Identities of Boolean Algebra

1. $X + 0 = X$	2. $X \cdot 1 = X$	<i>Existence of 0 and 1</i>
3. $X + 1 = 1$	4. $X \cdot 0 = 0$	
5. $X + X = X$	6. $X \cdot X = X$	<i>Idempotence</i>
7. $X + \bar{X} = 1$	8. $X \cdot \bar{X} = 0$	<i>Existence of complement</i>
9. $\bar{\bar{X}} = X$		<i>Involution</i>
10. $X + Y = Y + X$	11. $XY = YX$	<i>Commutative Laws</i>
12. $(X + Y) + Z = X + (Y + Z)$	13. $(XY)Z = X(YZ)$	<i>Associative Laws</i>
14. $X(Y + Z) = XY + XZ$	15. $X + YZ = (X + Y)(X + Z)$	<i>Distributive Laws</i>
16. $\overline{\bar{X} + \bar{Y}} = \bar{X} \cdot \bar{Y}$	17. $\overline{\bar{X} \cdot \bar{Y}} = \bar{X} + \bar{Y}$	<i>DeMorgan's Laws</i>

Some Properties of Identities & the Algebra

- If the meaning is unambiguous, we leave out the symbol “.”
- The identities above are organized into pairs
 - The *dual* of an algebraic expression is obtained by interchanging (+) and (\cdot) and interchanging 0's and 1's
 - The identities appear in *dual* pairs. When there is only one identity on a line the identity is *self-dual*, i. e., the dual expression = the original expression.

Some Properties of Identities & the Algebra (Continued)

- Unless it happens to be self-dual, the dual of an expression does not equal the expression itself
- Examples:
 - $F = (A + \bar{C}) \cdot B + 0$
 - *Dual F =*
 - $G = XY + \overline{(W + Z)}$
 - *Dual G =*
 - $H = AB + AC + BC$
 - *Dual H =*
- Are any of these functions self-dual?
 - Yes, H is self-dual

Some Properties of Identities & the Algebra (Continued)

- Unless it happens to be self-dual, the dual of an expression does not equal the expression itself
- Examples:
 - $F = (A + \bar{C}) \cdot B + 0$
 - $Dual\ F = (A \cdot \bar{C}) + B \cdot 1 = A \cdot \bar{C} + B$ (Not Accurate)
 - $Dual\ F = ((A \cdot \bar{C}) + B) \cdot 1 = A \cdot \bar{C} + B$ (Accurate)
 - $G = XY + \overline{(W + Z)}$
 - $Dual\ G = (X + Y) \cdot \overline{WZ} = (X + Y) \cdot (\bar{W} + \bar{Z})$
 - $H = AB + AC + BC$
 - $Dual\ H = (A + B)(A + C)(B + C) = (A + BC)(B + C)$
 $= AB + AC + BC$
- Are any of these functions self-dual?

Boolean Operator Precedence

- The order of evaluation in a Boolean expression is:
 1. Parentheses
 2. NOT
 3. AND
 4. OR

- Consequence: Parentheses appear around OR expressions

- Examples:
 - $F = A(B + C)(C + \bar{D})$
 - $F = \sim AB = \bar{A}B$
 - $F = AB + C$
 - $F = A(B + C)$

Useful Boolean Theorems

<i>Theorem</i>	<i>Dual</i>	<i>Name</i>
$x \cdot y + \bar{x} \cdot y = y$	$(x + y)(\bar{x} + y) = y$	Minimization
$x + x \cdot y = x$	$x \cdot (x + y) = x$	Absorption
$x + \bar{x} \cdot y = x + y$	$x \cdot (\bar{x} + y) = x \cdot y$	Simplification
$x \cdot y + \bar{x} \cdot z + y \cdot z = x \cdot y + \bar{x} \cdot z$		Consensus
$(x + y)(\bar{x} + z)(y + z) = (x + y)(\bar{x} + z)$		

Example 1: Boolean Algebraic Proof

- $A + A \cdot B = A$ (Absorption Theorem)

Proof Steps	Justification (identity or theorem)
$A + A \cdot B$	
$= A \cdot 1 + A \cdot B$	$X = X \cdot 1$
$= A \cdot (1 + B)$	<i>Distributive Law</i>
$= A \cdot 1$	$1 + X = 1$
$= A$	$X \cdot 1 = X$

- Our primary reason for doing proofs is to learn:
 - Careful and efficient use of the identities and theorems of Boolean algebra
 - How to choose the appropriate identity or theorem to apply to make forward progress, irrespective of the application

Example 2: Boolean Algebraic Proofs

- $AB + \bar{A}C + BC = AB + \bar{A}C$ (Consensus Theorem)

Proof Steps	Justification (identity or theorem)
$AB + \bar{A}C + BC$	
$= AB + \bar{A}C + 1 \cdot BC$	$1 \cdot X = X$
$= AB + \bar{A}C + (A + \bar{A}) \cdot BC$	$X + \bar{X} = 1$
$= AB + \bar{A}C + ABC + \bar{A}BC$	<i>Distributive Law</i>
$= AB + ABC + \bar{A}C + \bar{A}BC$	<i>Commutative Law</i>
$= AB \cdot 1 + AB \cdot C + \bar{A}C \cdot 1 + \bar{A}C \cdot B$	$X \cdot 1 = X$ and <i>Commutative Law</i>
$= AB(1 + C) + \bar{A}C(1 + B)$	<i>Distributive Law</i>
$= AB \cdot 1 + \bar{A}C \cdot 1$	$1 + X = 1$
$= AB + \bar{A}C$	$X \cdot 1 = X$

Proof of Simplification

- $A + \bar{A}.B = A + B$ (Simplification Theorem)

Proof Steps	Justification (identity or theorem)
$A + \bar{A}.B$	
$= (A + \bar{A})(A + B)$	<i>Distributive law</i>
$= 1.(A + B)$	<i>Factor B out (Distributive Laws)</i>
$= (A + B)$	$X + \bar{X} = 1$

- $A.(\bar{A} + B) = AB$ (Simplification Theorem)

Proof Steps	Justification (identity or theorem)
$A.(\bar{A} + B)$	
$= (A.\bar{A}) + (A.B)$	<i>Distributive Law</i>
$= 0 + AB$	$X.\bar{X} = 0$
$= AB$	$X + 0 = X$

Proof of Minimization

- $A.B + \bar{A}.B = B$ (Minimization Theorem)

Proof Steps	Justification (identity or theorem)
$A.B + \bar{A}.B$	
$= B(A + \bar{A})$	<i>Distributive Law</i>
$= B.1$	$X + \bar{X} = 1$
$= B$	$X.1 = X$

- $(A + B)(\bar{A} + B) = B$ (Minimization Theorem)

Proof Steps	Justification (identity or theorem)
$(A + B)(\bar{A} + B)$	
$= B + (A.\bar{A})$	<i>Distributive Law</i>
$= B + 0$	$X.\bar{X} = 0$
$= B$	$X + 0 = X$

Proof of DeMorgan's Laws (1)

- $\overline{X + Y} = \bar{X} \cdot \bar{Y}$ (DeMorgan's Law)
 - We will show that, $\bar{X} \cdot \bar{Y}$, satisfies the definition of the complement of $(X + Y)$, defined as $\overline{X + Y}$ by DeMorgan's Law.
 - To show this, we need to show that $A + A' = 1$ and $A \cdot A' = 0$ with $A = X + Y$ and $A' = X' \cdot Y'$. This proves that $X' \cdot Y' = \overline{X + Y}$.
- Part 1: Show $X + Y + X' \cdot Y' = 1$

Proof of DeMorgan's Laws (1)

- $\overline{X + Y} = \bar{X} \cdot \bar{Y}$ (DeMorgan's Law)
 - We will show that, $\bar{X} \cdot \bar{Y}$, satisfies the definition of the complement of $(X + Y)$, defined as $\overline{X + Y}$ by DeMorgan's Law.
 - To show this, we need to show that $A + A' = 1$ and $A \cdot A' = 0$ with $A = X + Y$ and $A' = X' \cdot Y'$. This proves that $X' \cdot Y' = \overline{X + Y}$.
- Part 1: Show $X + Y + X' \cdot Y' = 1$

Proof Steps	Justification (identity or theorem)
$(X + Y) + X' \cdot Y'$	
$= (X + Y + X')(X + Y + Y')$	<i>Distributive Law</i>
$= (1 + Y)(X + 1)$	$X + \bar{X} = 1$
$= 1 \cdot 1$	$X + 1 = 1$
$= 1$	$X \cdot 1 = X$

Proof of DeMorgan's Laws (2)

- Part 2: Show $(X + Y).X'.Y' = 0$

- Based on the above two parts, $X'.Y' = \overline{X + Y}$
- The second DeMorgan's law is proved by duality
- Note that DeMorgan's law, given as an identity is not an axiom in the sense that it can be proved using the other identities.

Example 3: Boolean Algebraic Proofs

- $\overline{(X + Y)}Z + X\bar{Y} = \bar{Y}(X + Z)$

Example 3: Boolean Algebraic Proofs

- $\overline{(X + Y)}Z + X\bar{Y} = \bar{Y}(X + Z)$

Proof Steps	Justification (identity or theorem)
$\overline{(X + Y)}Z + X\bar{Y}$	
$= X'Y'Z + X.Y'$	<i>DeMorgan's law</i>
$= Y'(X'Z + X)$	<i>Distributive law</i>
$= Y'(X + X'Z)$	<i>Commutative law</i>
$= Y'(X + Z)$	<i>Simplification Theorem</i>

Boolean Function Evaluation

- $F_1 = xy\bar{z}$
- $F_2 = x + \bar{y}z$
- $F_3 = \bar{x}\bar{y}\bar{z} + \bar{x}yz + x\bar{y}$
- $F_4 = x\bar{y} + \bar{x}z$

x	y	z	F_1	F_2	F_3	F_4
0	0	0	0	0	1	0
0	0	1	0	1	0	1
0	1	0	0	0	0	0
0	1	1	0	0	1	1
1	0	0	0	1	1	1
1	0	1	0	1	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	0

Expression Simplification

- An application of Boolean algebra
- Simplify to contain the smallest number of literals (complemented and uncomplemented variables)
- Example: Simplify the following Boolean expression
 - $AB + A'CD + A'BD + A'CD' + ABCD$

Simplification Steps	Justification (identity or theorem)
$AB + A'CD + A'BD + A'CD' + ABCD$	
$= AB + ABCD + A'CD + A'CD' + A'BD$	<i>Commutative law</i>
$= AB(1 + CD) + A'C(D + D') + A'BD$	<i>Distributive law</i>
$= AB.1 + A'C.1 + A'BD$	$1 + X = 1$ and $X + X' = 1$
$= AB + A'C + A'BD$	$X.1 = X$
$= AB + A'BD + A'C$	<i>Commutative law</i>
$= B(A + A'D) + A'C$	<i>Distributive law</i>
$= B(A + D) + A'C \rightarrow 5 \text{ Literals}$	<i>Simplification Theorem</i>

Complementing Functions

- Use DeMorgan's Theorem to complement a function:
 1. Interchange AND and OR operators
 2. Complement each constant value and literal

- Example: Complement $F = x'yz' + xy'z'$

$$F' = (x + y' + z)(x' + y + z)$$

- Example: Complement $G = (a' + bc)d' + e$


$$G' = (a(b' + c') + d).e'$$

Example

- Simplify the following:
 - $F = X'YZ + X'YZ' + XZ$


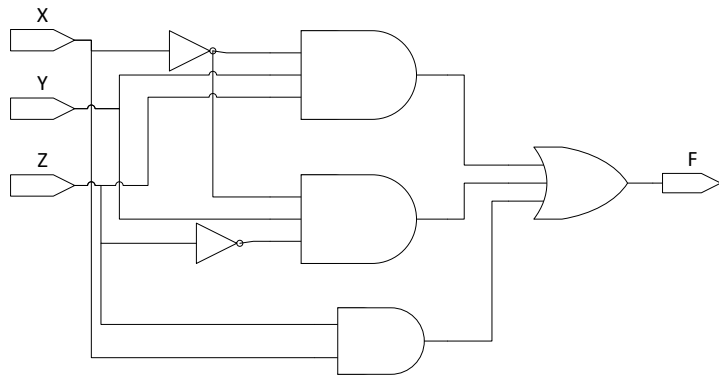
Example

- Simplify the following:
 - $F = X'YZ + X'YZ' + XZ$



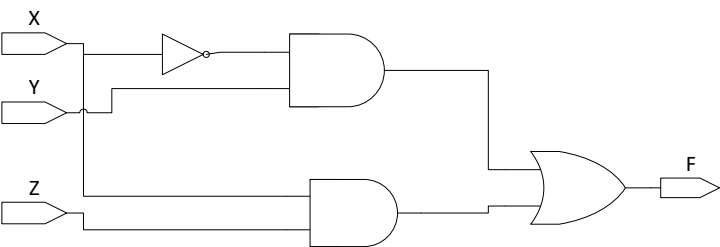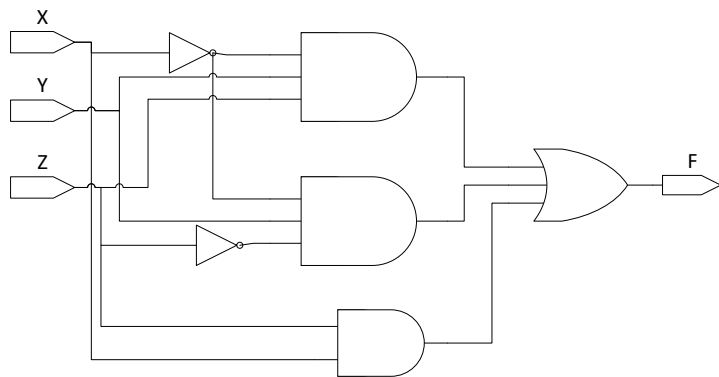Example

- Simplify the following:
 - $F = X'YZ + X'YZ' + XZ$



Simplification Steps	(identity or theorem)
$X'YZ + X'YZ' + XZ$	
$= X'Y(Z + Z') + XZ$	<i>Distributive law</i>
$= X'Y.1 + XZ$	$X + X' = 1$
$= X'Y + XZ$	$X.1 = X$

x	y	z	$X'YZ + X'YZ' + XZ$	$X'Y + XZ$
0	0	0	0	0
0	0	1	0	0
0	1	0	1	1
0	1	1	1	1
1	0	0	0	0
1	0	1	1	1
1	1	0	0	0
1	1	1	1	1
			3 terms and 8 literals	2 terms and 4 literals

Example

- Show that $F = x'y' + xy' + x'y + xy = 1$

- Solution1: Truth Table

x	y	F
0	0	1
0	1	1
1	0	1
1	1	1

- Solution2: Boolean Algebra

Proof Steps	(identity or theorem)
$x'y' + xy' + x'y + xy$	
$= y'(x' + x) + y(x' + x)$	<i>Distributive law</i>
$= y'.1 + y.1$	$X + X' = 1$
$= y' + y$	$X.1 = X$
$= 1$	$X + X' = 1$

Examples

- Show that $ABC + A'C' + AC' = AB + C'$ using Boolean algebra.


Proof Steps	(identity or theorem)
$ABC + A'C' + AC'$	
$= ABC + C'(A' + A)$	<i>Distributive law</i>
$= ABC + C'.1$	$X + X' = 1$
$= ABC + C'$	$X.1 = X$
$= (AB + C')(C + C')$	<i>Distributive law</i>
$= (AB + C').1$	$X + X' = 1$
$= AB + C'$	$X.1 = X$

- Find the dual and the complement of $f = wx + y'z.0 + w'z$
 - $Dual(f) = (w + x)(y' + z + 1)(w' + z)$
 - $f' = (w' + x')(y + z' + 1)(w + z')$

Overview – Canonical Forms

- What are Canonical Forms?
- Minterms and Maxterms
- Index Representation of Minterms and Maxterms
- Sum-of-Minterm (SOM) Representations
- Product-of-Maxterm (POM) Representations
- Representation of Complements of Functions
- Conversions between Representations

Boolean Representation Forms

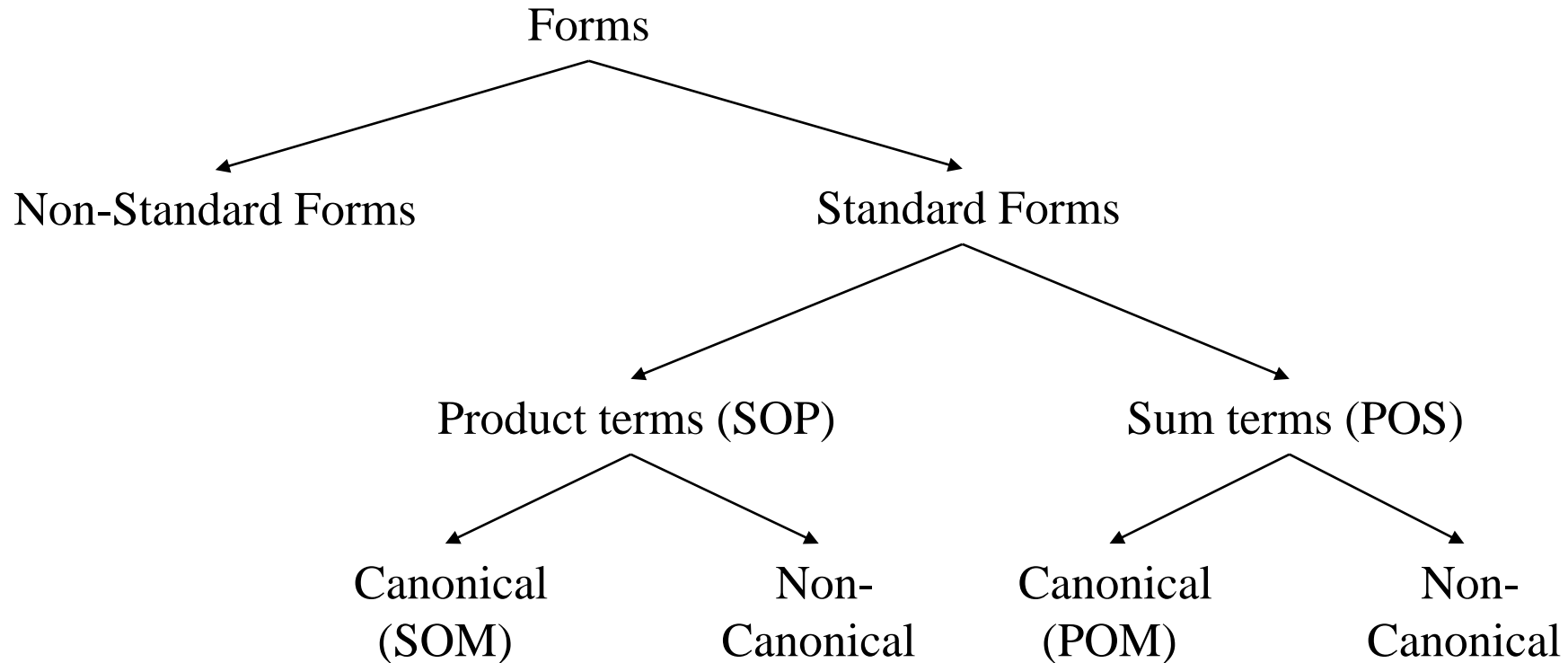

Canonical Forms

- It is useful to specify Boolean functions in a form that:
 - Allows comparison for equality
 - Has a correspondence to the truth tables
 - Facilitates simplification
- Canonical Forms in common usage:
 - Sum of Minterms (SOM)
 - Product of Maxterms (POM)

Minterms

- ***Minterms*** are AND terms with ***every variable*** present in either true or complemented form
- Given that each binary variable may appear normal (e.g., x) or complemented (e.g., \bar{x}), there are 2^n minterms for n variables
- Example: Two variables (X and Y) produce $2^2 = 4$ combinations:
 - XY (both normal)
 - $X\bar{Y}$ (X normal, Y complemented)
 - $\bar{X}Y$ (X complemented, Y normal)
 - $\bar{X}\bar{Y}$ (both complemented)
- Thus there are ***four minterms*** of two variables

Maxterms

- **Maxterms** are OR terms with *every variable* in true or complemented form
- Given that each binary variable may appear normal (e.g., x) or complemented (e.g., \bar{x}), there are 2^n maxterms for n variables
- Example: Two variables (X and Y) produce $2^2 = 4$ combinations:

$X + Y$ (both normal)

$X + \bar{Y}$ (X normal, Y complemented)

$\bar{X} + Y$ (X complemented, Y normal)

$\bar{X} + \bar{Y}$ (both complemented)

Maxterms and Minterms

- Examples: Three variable (X, Y, Z) minterms and maxterms

Index	X,Y,Z	Minterm (m)	Maxterm (M)
0	000	$\bar{X}\bar{Y}\bar{Z}$	$X + Y + Z$
1	001	$\bar{X}\bar{Y}Z$	$X + Y + \bar{Z}$
2	010	$\bar{X}Y\bar{Z}$	$X + \bar{Y} + Z$
3	011	$\bar{X}YZ$	$X + \bar{Y} + \bar{Z}$
4	100	$X\bar{Y}\bar{Z}$	$\bar{X} + Y + Z$
5	101	$X\bar{Y}Z$	$\bar{X} + Y + \bar{Z}$
6	110	$XY\bar{Z}$	$\bar{X} + \bar{Y} + Z$
7	111	XYZ	$\bar{X} + \bar{Y} + \bar{Z}$

- The *index* above is important for describing which variables in the terms are true and which are complemented

Standard Order

- Minterms and maxterms are designated with a subscript
- The subscript is a number, corresponding to a binary pattern
- The bits in the pattern represent the complemented or normal state of each variable listed in a standard order
- All variables will be present in a minterm or maxterm and will be listed in the *same order (usually alphabetically)*
- **Example: For variables a, b, c:**
 - **Maxterms:** $(a + b + \bar{c})$, $(a + b + c)$
 - **Terms:** $(b + a + c)$, $a\bar{c}b$, and $(c + b + a)$ are **NOT** in standard order.
 - **Minterms:** $a\bar{b}c$, abc , $\bar{a}\bar{b}c$
 - **Terms:** $(a + c)$, $\bar{b}c$, and $(\bar{a} + b)$ do not contain all variables

Purpose of the Index

- The *index* for the minterm or maxterm, expressed as a binary number, is used to determine whether the variable is shown in the true form or complemented form
- **For Minterms:**
 - “0” means the variable is “Complemented”
 - “1” means the variable is “Not Complemented”
- **For Maxterms:**
 - “0” means the variable is “Not Complemented”
 - “1” means the variable is “Complemented”

Index Example: Three Variables

Index (Decimal)	Index (Binary) n = 3 Variables	Minterm (m)	Maxterm (M)
0	000	$m_0 = \bar{X}\bar{Y}\bar{Z}$	$M_0 = X + Y + Z$
1	001	$m_1 = \bar{X}\bar{Y}Z$	$M_1 = X + Y + \bar{Z}$
2	010	$m_2 = \bar{X}Y\bar{Z}$	$M_2 = X + \bar{Y} + Z$
3	011	$m_3 = \bar{X}YZ$	$M_3 = X + \bar{Y} + \bar{Z}$
4	100	$m_4 = X\bar{Y}\bar{Z}$	$M_4 = \bar{X} + Y + Z$
5	101	$m_5 = X\bar{Y}Z$	$M_5 = \bar{X} + Y + \bar{Z}$
6	110	$m_6 = XY\bar{Z}$	$M_6 = \bar{X} + \bar{Y} + Z$
7	111	$m_7 = XYZ$	$M_7 = \bar{X} + \bar{Y} + \bar{Z}$

Index Example: Four Variables

i (Decimal)	i (Binary) n = 4 Variables	m_i	M_i
0	0000	$\bar{a}\bar{b}\bar{c}\bar{d}$	$a + b + c + d$
1	0001	$\bar{a}\bar{b}\bar{c}d$	$a + b + c + \bar{d}$
3	0011	$\bar{a}\bar{b}cd$	$a + b + \bar{c} + \bar{d}$
5	0101	$\bar{a}b\bar{c}d$	$a + \bar{b} + c + \bar{d}$
7	0111	$\bar{a}bcd$	$a + \bar{b} + \bar{c} + \bar{d}$
10	1010	$a\bar{b}\bar{c}\bar{d}$	$\bar{a} + b + \bar{c} + d$
13	1101	$ab\bar{c}d$	$\bar{a} + \bar{b} + c + \bar{d}$
15	1111	$abcd$	$\bar{a} + \bar{b} + \bar{c} + \bar{d}$

Minterm and Maxterm Relationship

- Review: DeMorgan's Theorem
 - $\overline{x \cdot y} = \bar{x} + \bar{y}$ and $\overline{\bar{x} + \bar{y}} = x \cdot y$
- Two-variable example:
 - $M_2 = \bar{x} + y$ and $m_2 = x \cdot \bar{y}$
 - Using DeMorgan's Theorem $\rightarrow \overline{\bar{x} + \bar{y}} = \bar{\bar{x}} \cdot \bar{\bar{y}} = x \cdot y$
 - Using DeMorgan's Theorem $\rightarrow \overline{x \cdot \bar{y}} = \bar{x} + \bar{\bar{y}} = \bar{x} + y$
 - Thus, M_2 is the complement of m_2 and vice-versa
- Since DeMorgan's Theorem holds for n variables, the above holds for terms of n variables:

$$M_i = \overline{m_i} \text{ and } m_i = \overline{M_i}$$

- Thus, M_i is the complement of m_i and vice-versa

Function Tables for Both

- Minterms of 2 variables:

xy	m_0	m_1	m_2	m_3
00	1	0	0	0
01	0	1	0	0
10	0	0	1	0
11	0	0	0	1

- Maxterms of 2 variables:

xy	M_0	M_1	M_2	M_3
00	0	1	1	1
01	1	0	1	1
10	1	1	0	1
11	1	1	1	0

- Each column in the maxterm function table is the complement of the column in the minterm function table since M_i is the complement of m_i .

Observations

- In the function tables:
 - Each *minterm* has one and only one 1 present in the 2^n terms (a minimum of 1s). All other entries are 0.
 - Each *maxterm* has one and only one 0 present in the 2^n terms. All other entries are 1 (a maximum of 1s).
- We can implement any function by
 - "ORing" the minterms corresponding to "1" entries in the function table. These are called the minterms of the function.
 - "ANDing" the maxterms corresponding to "0" entries in the function table. These are called the maxterms of the function.
- This gives us two canonical forms for stating any Boolean function:
 - *Sum of Minterms (SOM)*
 - *Product of Maxterms (POM)*

Minterm Function Example

- Example: Find $F_1 = m_1 + m_4 + m_7$
- $F_1 = x'y'z + xy'z' + xyz$

xyz	Index	$m_1 + m_4 + m_7 = F_1$
000	0	$0 + 0 + 0 = 0$
001	1	$1 + 0 + 0 = 1$
010	2	$0 + 0 + 0 = 0$
011	3	$0 + 0 + 0 = 0$
100	4	$0 + 1 + 0 = 1$
101	5	$0 + 0 + 0 = 0$
110	6	$0 + 0 + 0 = 0$
111	7	$0 + 0 + 1 = 1$

Minterm Function Example

- $F(A, B, C, D, E) = m_2 + m_9 + m_{17} + m_{23}$
- $F(A, B, C, D, E) = A'B'C'DE' + A'BC'D'E + AB'C'D'E + AB'CDE$

Maxterm Function Example

- **Example: Implement F1 in maxterms:**
- $F_1 = M_0 \cdot M_2 \cdot M_3 \cdot M_5 \cdot M_6$
- $F_1 = (x + y + z) \cdot (x + y' + z) \cdot (x + y' + z') \cdot (x' + y + z') \cdot (x' + y' + z)$

xyz	Index	$M_0 \cdot M_2 \cdot M_3 \cdot M_5 \cdot M_6 = F_1$
000	0	0 . 1 . 1 . 1 . 1 = 0
001	1	1 . 1 . 1 . 1 . 1 = 1
010	2	1 . 0 . 1 . 1 . 1 = 0
011	3	1 . 1 . 0 . 1 . 1 = 0
100	4	1 . 1 . 1 . 1 . 1 = 1
101	5	1 . 1 . 1 . 0 . 1 = 0
110	6	1 . 1 . 1 . 1 . 0 = 0
111	7	1 . 1 . 1 . 1 . 1 = 1

Maxterm Function Example

- $F(A, B, C, D) = M_3 \cdot M_8 \cdot M_{11} \cdot M_{14}$
- $F(A, B, C, D) = (A + B + C' + D') \cdot (A' + B + C + D) \cdot (A' + B + C' + D') \cdot (A' + B' + C' + D)$

Canonical Sum of Minterms

- Any Boolean function can be expressed as a Sum of Minterms (SOM):
 - For the function table, the minterms used are the terms corresponding to the 1's
 - For expressions, expand all terms first to explicitly list all minterms. Do this by “ANDing” any term missing a variable v with a term $(v + \bar{v})$
- Example: Implement $f = x + \bar{x}\bar{y}$ as a SOM?
 1. Expand terms $\rightarrow f = x(y + \bar{y}) + \bar{x}\bar{y}$
 2. Distributive law $\rightarrow f = xy + x\bar{y} + \bar{x}\bar{y}$
 3. Express as SOM $\rightarrow f = m_3 + m_2 + m_0 = m_0 + m_2 + m_3$

Another SOM Example

- Example: $F = A + \bar{B}C$
- There are three variables: A, B, and C which we take to be the standard order
- Expanding the terms with missing variables:
 - $F = A(B + \bar{B})(C + \bar{C}) + (A + \bar{A})\bar{B}C$
- Distributive law:
 - $F = ABC + A\bar{B}C + AB\bar{C} + A\bar{B}\bar{C} + \bar{A}BC + \bar{A}\bar{B}C$
- Collect terms (removing all but one of duplicate terms):
 - $F = ABC + AB\bar{C} + A\bar{B}C + A\bar{B}\bar{C} + \bar{A}\bar{B}C$
- Express as SOM:
 - $F = m_7 + m_6 + m_5 + m_4 + m_1$
 - $F = m_1 + m_4 + m_5 + m_6 + m_7$

Shorthand SOM Form

- From the previous example, we started with:
 - $F = A + \bar{B}C$
- We ended up with:
 - $F = m_1 + m_4 + m_5 + m_6 + m_7$
- This can be denoted in the *formal shorthand*:
 - $F(A, B, C) = \sum_m(1,4,5,6,7)$
- Note that we explicitly show the standard variables in order and drop the “m” designators.

Canonical Product of Maxterms

- Any Boolean Function can be expressed as a Product of Maxterms (POM):
 - For the function table, the maxterms used are the terms corresponding to the 0's
 - For an expression, expand all terms first to explicitly list all maxterms. Do this by first applying the second distributive law, “ORing” terms missing variable v with $(v \cdot \bar{v})$ and then applying the distributive law again
- Example: Convert $f(x, y, z) = x + \bar{x}\bar{y}$ to POM?
 - Distributive law $\rightarrow f = (x + \bar{x}) \cdot (x + \bar{y}) = x + \bar{y}$
 - ORing with missing variable (z) $\rightarrow f = x + \bar{y} + z \cdot \bar{z}$
 - Distributive law $\rightarrow f = (x + \bar{y} + z) \cdot (x + \bar{y} + \bar{z})$
 - Express as POS $\rightarrow f = M_2 \cdot M_3$

Another POM Example

- Convert $f(A, B, C) = AC' + BC + A'B'$ to POM?
- Use $x + yz = (x + y) \cdot (x + z)$, assuming $x = AC' + BC$ and $y = A'$ and $z = B'$
 - $f(A, B, C) = (AC' + BC + A') \cdot (AC' + BC + B')$
- Use Simplification theorem to get:
 - $f(A, B, C) = (BC + A' + C') \cdot (AC' + B' + C)$
- Use Simplification theorem again to get:
 - $f(A, B, C) = (A' + B + C') \cdot (A + B' + C) = M_5 \cdot M_2$
 - $f(A, B, C) = M_2 \cdot M_5 = \prod_M(2,5) \rightarrow$ ***Shorthand POM form***

Function Complements

- The complement of a function expressed as a sum of minterms is constructed by selecting the minterms missing in the sum-of-minterms canonical forms.
- Alternatively, the complement of a function expressed by a sum of minterms form is simply the Product of Maxterms with the same indices.
- Example: Given $F(x, y, z) = \sum_m(1,3,5,7)$, find complement F as SOM and POM?
 - $\bar{F}(x, y, z) = \sum_m(0,2,4,6)$
 - $\bar{F}(x, y, z) = \prod_M(1,3,5,7)$

Conversion Between Forms

- To convert between sum-of-minterms and product-of-maxterms form (or vice-versa) we follow these steps:
 - Find the function complement by swapping terms in the list with terms not in the list.
 - Change from products to sums, or vice versa.
- **Example:** Given F as before: $F(x, y, z) = \sum_m(1,3,5,7)$
 - Form the Complement:
$$\bar{F}(x, y, z) = \sum_m(0,2,4,6)$$
 - Then use the other form with the same indices – this forms the complement again, giving the other form of the original function:
$$F(x, y, z) = \prod_M(0,2,4,6)$$

Important Properties of Minterms

- Maxterms are seldom used directly to express Boolean functions
- Minterms properties:
 - For n Boolean variables, there are 2^n minterms (0 to $2^n - 1$)
 - Any Boolean function can be represented as a logical sum of minterms (SOM)
 - The complement of a function contains those minterms not included in the original function
 - A function that include all the 2^n minterms is equal to 1

Standard Forms

- Standard Sum-of-Products (SOP) form: equations are written as an OR of AND terms
- Standard Product-of-Sums (POS) form: equations are written as an AND of OR terms
- **Examples:**
 - SOP: $ABC + \bar{A}\bar{B}C + B$
 - POS: $(A + B) \cdot (A + \bar{B} + \bar{C}) \cdot C$
- **These “mixed” forms are neither SOP nor POS**
 - $(AB + C)(A + C)$
 - $AB\bar{C} + AC(A + B)$

Standard Sum-of-Products (SOP)

- A sum of minterms form for n variables can be written down directly from a truth table
- Implementation of this form is a two-level network of gates such that:
 - The first level consists of n -input AND gates, and
 - The second level is a single OR gate (with fewer than 2^n inputs)
- This form often can be simplified so that the corresponding circuit is simpler

Standard Sum-of-Products (SOP)



- A Simplification Example: $F(A, B, C) = \sum_m(1,4,5,6,7)$
- Writing the minterm expression:
 - $F(A, B, C) = A'B'C + AB'C' + AB'C + ABC' + ABC$
- Simplifying using boolean Algebra:

Simplification Steps	(identity or theorem)
$A'B'C + AB'C' + AB'C + ABC' + ABC$	
$= A'B'C + AB'(C' + C) + AB(C' + C)$	<i>Distributive law</i>
$= A'B'C + AB' + AB$	$X + X' = 1$
$= A'B'C + A(B' + B)$	<i>Distributive law</i>
$= A'B'C + A$	<i>Simplification Theorem</i>
$= A + B'C$	

- Simplified F contains 3 literals compared to 15 in minterm F

AND/OR Two-level Implementation of SOP Expression

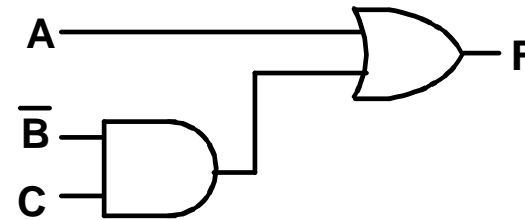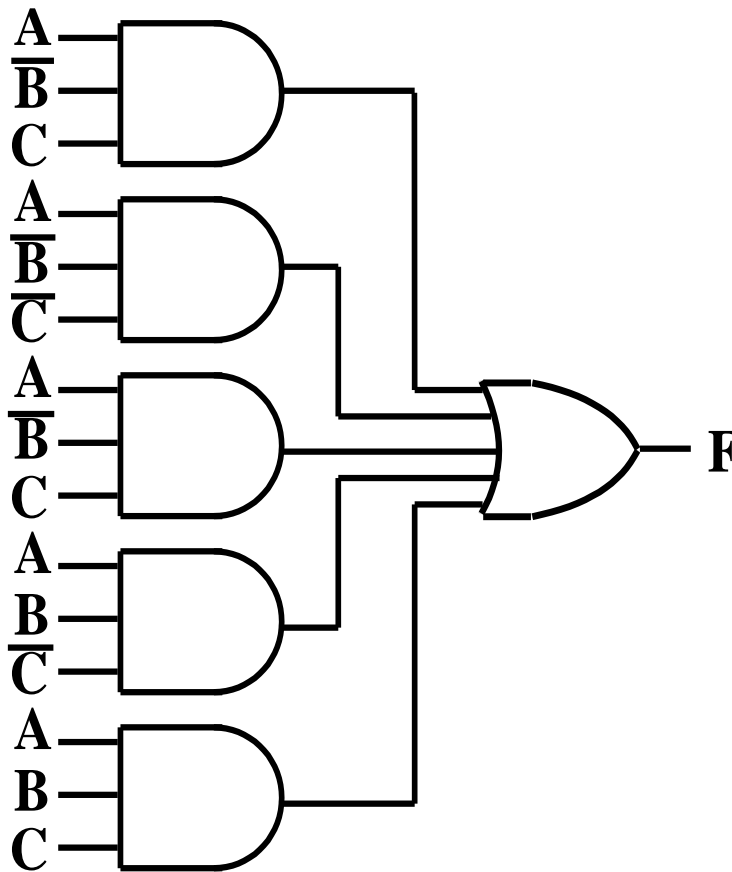- The two implementations for F are shown below – it is quite apparent which is simpler!



Two-level Implementation


- Draw the logic diagram of the following boolean function:
 - $f = AB + C(D + E)$

- Represent the function using two-level implementation:
 - $f = AB + CD + CE \rightarrow \text{SOP}$

Two-level Implementation


- Draw the logic diagram of the following boolean function:

- $f = AB + C(D + E)$

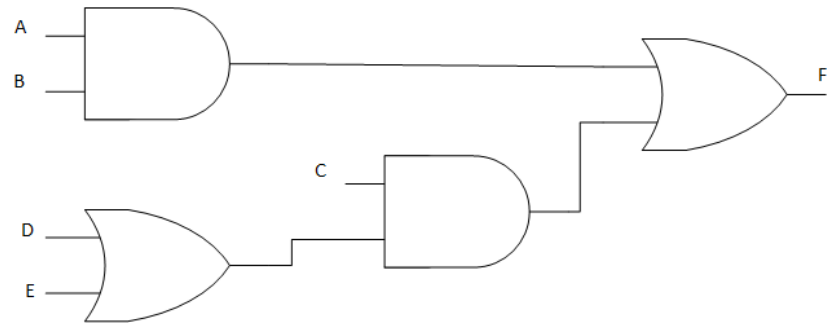

- Represent the function using two-level implementation:

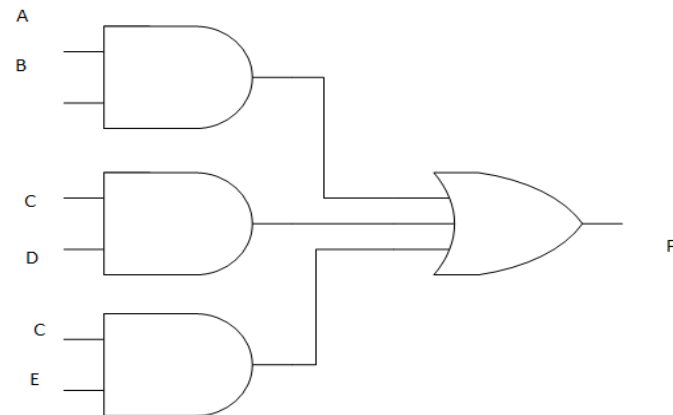- $f = AB + CD + CE \rightarrow \text{SOP}$



SOP and POS Observations

- **The previous examples show that:**
 - **Canonical Forms (Sum-of-minterms, Product-of-Maxterms), or other standard forms (SOP, POS) differ in complexity**
 - **Boolean algebra can be used to manipulate equations into simpler forms.**
 - **Simpler equations lead to simpler two-level implementations**
- **Questions:**
 - **How can we attain a “simplest” expression?**
 - **Is there only one minimum cost circuit?**
 - **The next part will deal with these issues.**