

Chapter #3: Diodes

from **Microelectronic Circuits** Text

by Sedra and Smith

Oxford Publishing

Introduction

■ IN THIS CHAPTER WE WILL LEARN

- the **characteristics of the ideal diode** and how to analyze and design circuits containing multiple ideal diodes together with resistors and dc sources to realize useful and interesting nonlinear function
- the **details of the i-v characteristic** of the junction diode (which was derived in Chapter 1) and how to use it to analyze diode circuits operating in the various bias regions: forward, reverse, and breakdown
- a simple but effective model of the diode i-v characteristic in the forward direction: the **constant-voltage-drop model**

Introduction

- a powerful technique for the application and modeling of the diode (and in later chapters, transistors): dc-biasing the diode and modeling its operation for small signals around the dc-operating point by means of the **small-signal model**
- the use of a string of forward-biased diodes and of diodes operating in the breakdown region (zener diodes), to provide constant dc voltages (**voltage regulators**)
- application of the diode in the design of **rectifier circuits**, which convert ac voltages to dc as needed for powering electronic equipment
- a number of other practical and important applications

3.1.1. Current-Voltage Characteristic of the Ideal Diode

- **ideal diode** – most fundamental nonlinear circuit element
 - two terminal device
 - **circuit symbol** shown to right
 - operates in **two modes**
 - on and off

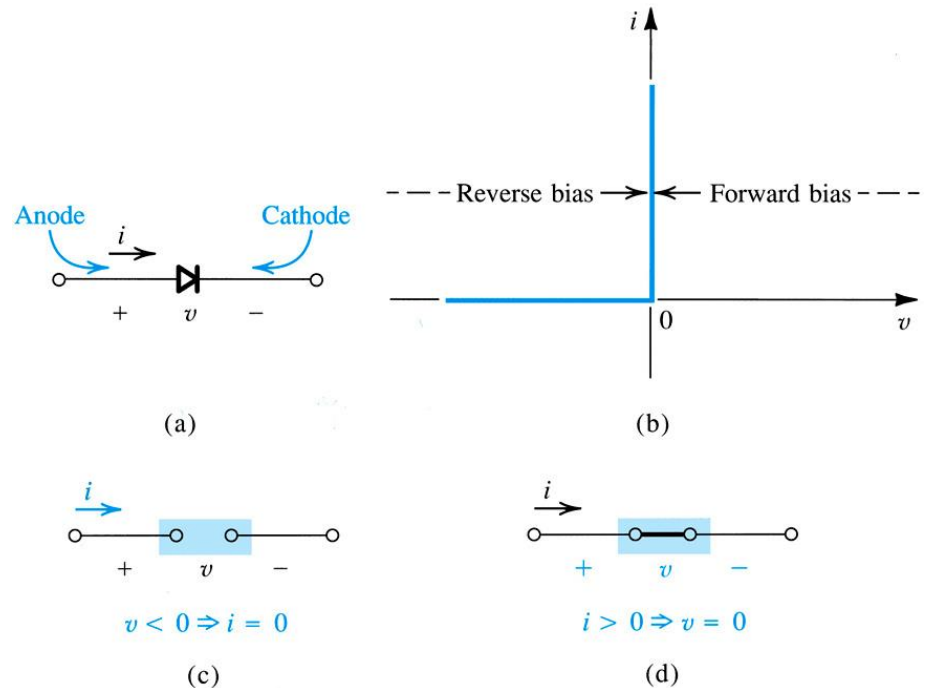


Figure 3.1: Diode characteristics


3.1.1. Current-Voltage Characteristic

- **cathode** – negative terminal, **from** which current flows
- **anode** – positive terminal of diode, **into** which current flows
- voltage-current (V/I) behavior is:
 - **piecewise linear** for rated values
 - **nonlinear** beyond this range


mode #2: reverse bias = open ckt.

mode #1: forward bias = short ckt


device symbol with two nodes

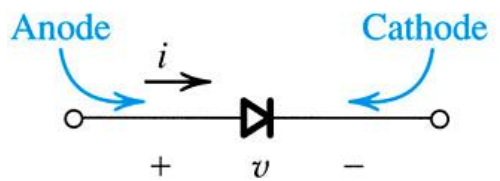

(a)

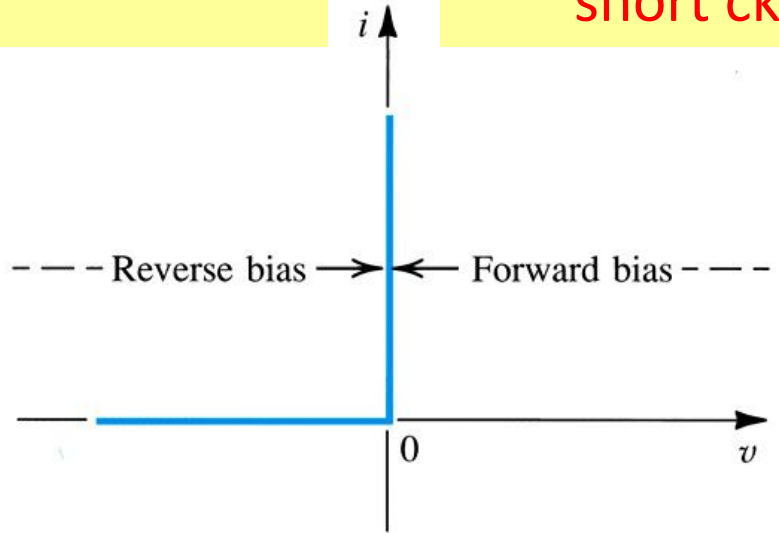


(b)

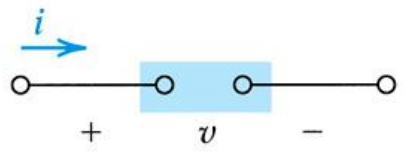

$v < 0 \Rightarrow i = 0$

(c)

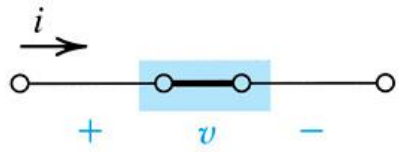

$i > 0 \Rightarrow v = 0$

(d)

3.1.1. Current-Voltage Characteristic

- External circuit should be designed to limit...
 - **current flow** across conducting diode
 - **voltage across** blocking diode
- Examples are shown to right...

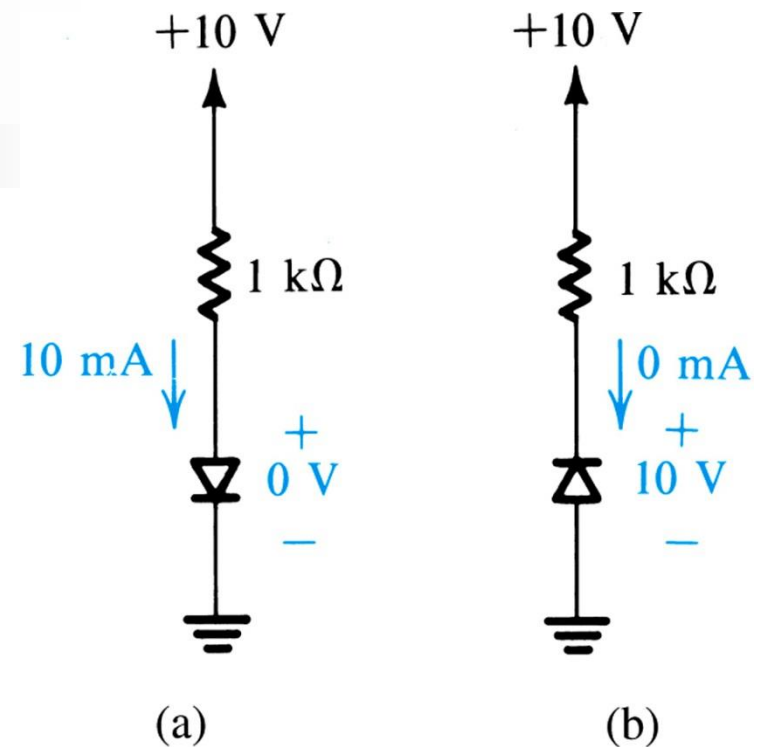


Figure 3.2: The two modes of operation of ideal diodes and the use of an external circuit to limit (a) the forward current and (b) the reverse voltage.

3.1.2: A Simple Application – The Rectifier

- One **fundamental application** of this piecewise linear behavior is the rectifier.
- **Q:** What is a **rectifier**?
 - **A:** Circuit which **converts AC waves in to DC**...ideally with no loss.

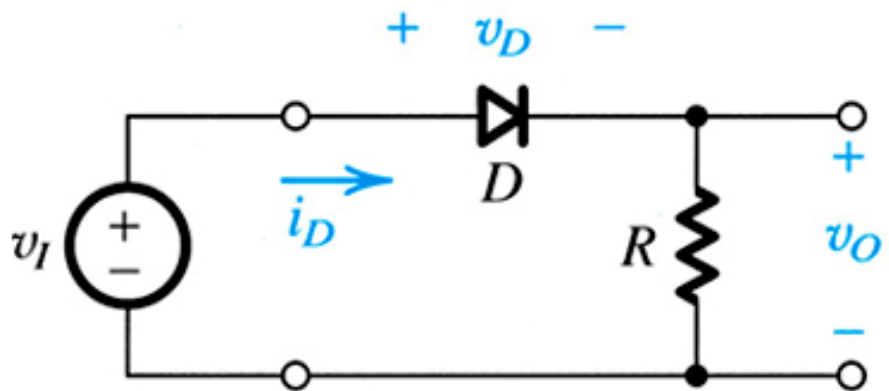


Figure 3.3(a): Rectifier Circuit

3.1.2: A Simple Application – The Rectifier

- This circuit is composed of diode and series resistor.
- **Q:** How does this circuit operate?
 - **A:** The diode blocks reverse current flow, preventing negative voltage across R .

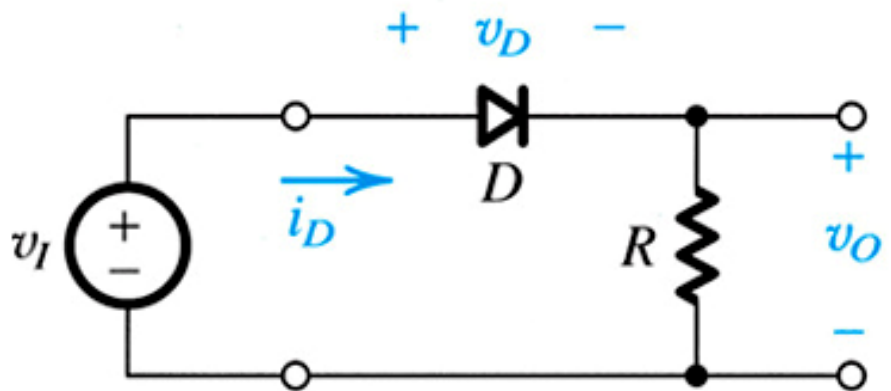


Figure 3.3(a): Rectifier Circuit

3.1.3. Another Application, Diode Logic Gates

- **Q:** How many diodes be used to create logic gates?
- **A:** Examples of **AND / OR gates** are shown right.
 - Refer to next slide.


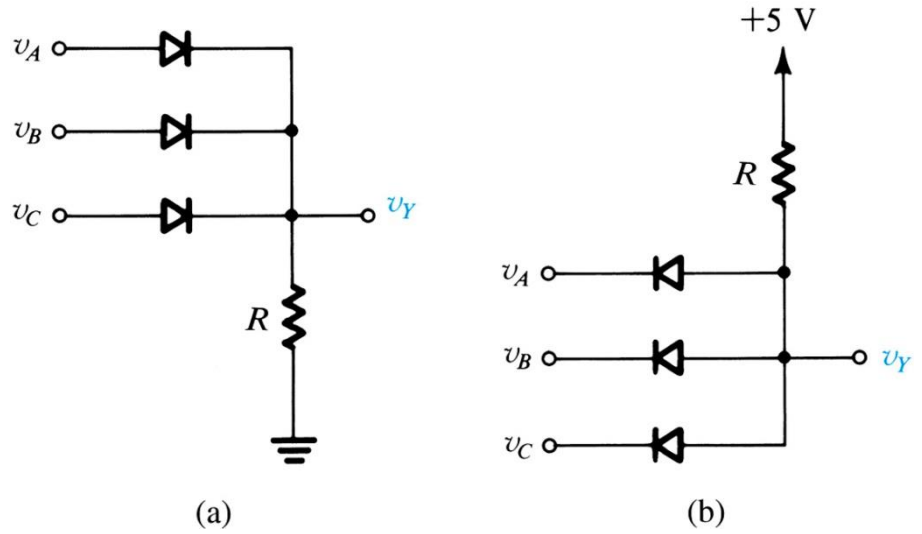


Figure 3.5: Diode logic gates: **(a)** OR gate; **(b)** AND gate (in a positive-logic system).

OR GATE

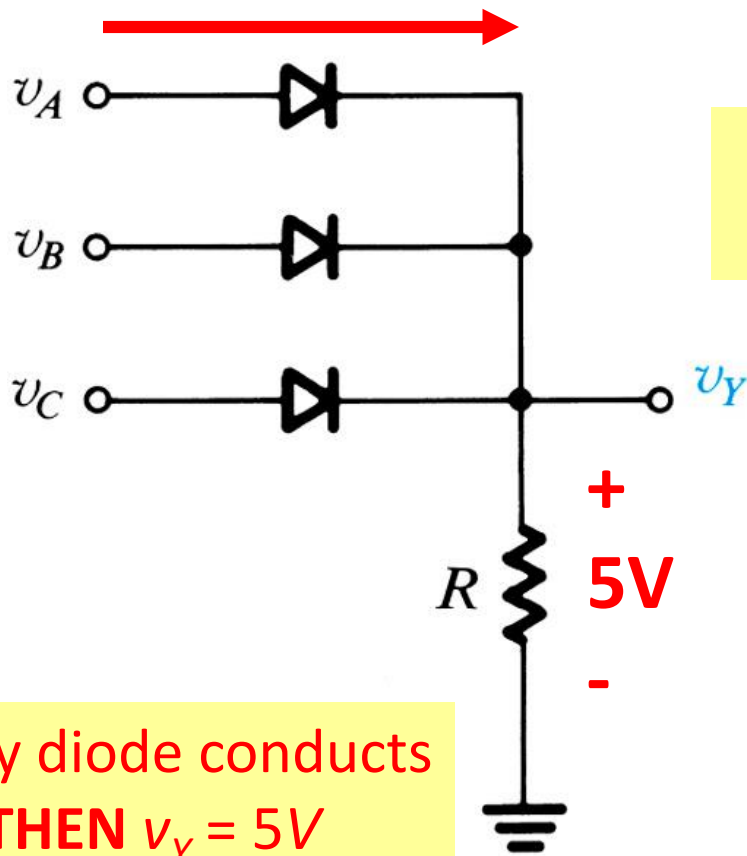IF $v_A = 5V$ THEN diode_A will conduct AND $v_Y = v_A = 5V$




IF any diode conducts THEN $v_Y = 5V$

(a)

AND GATE

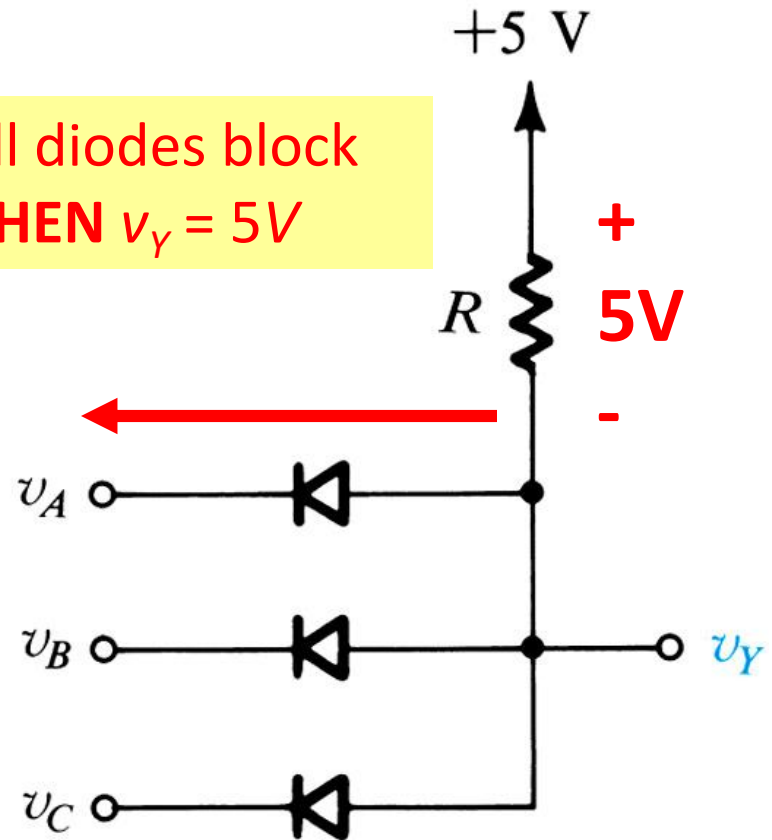IF $v_A = 0V$ THEN diode_A will conduct AND $v_Y = v_A = 0V$




IF all diodes block THEN $v_Y = 5V$

(b)

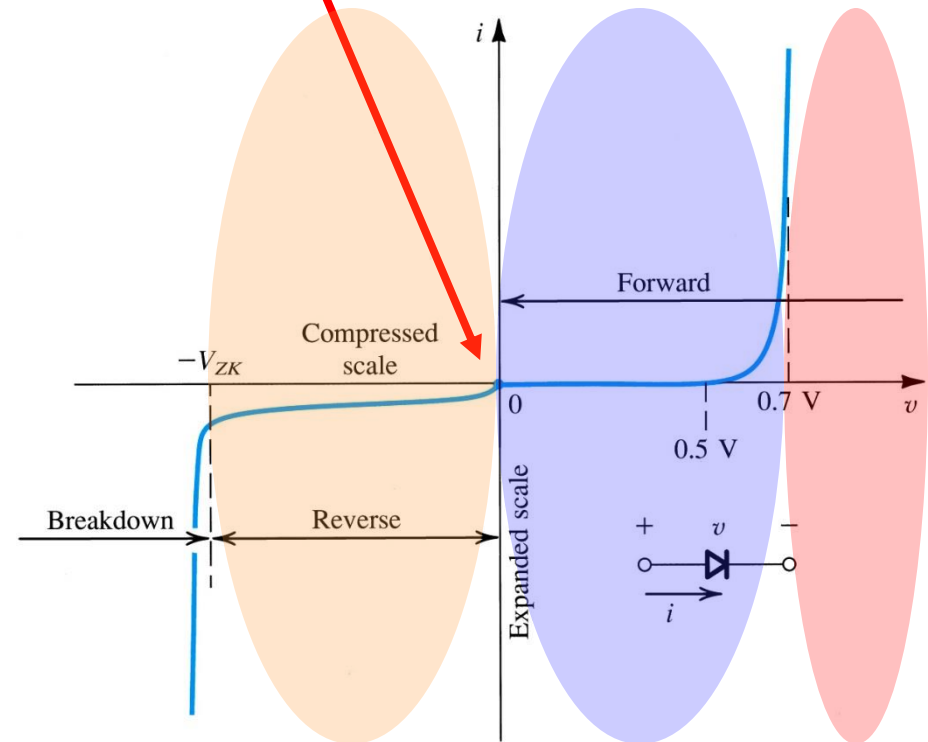3.2. Terminal Characteristics of Junction Diodes

- Most common implementation of a diode utilizes pn junction.
- I - V curve consists of **three characteristic regions**
 - forward bias: $v > 0$
 - reverse bias: $v < 0$
 - breakdown: $v \ll 0$

discontinuity caused by differences in scale



3.2.1. The Forward-Bias Region

- The **forward-bias region** of operation is entered when $v > 0$.
- **I - V relationship** is closely approximated by equations to right.

(3.3) is a simplification suitable for large v

$I_s =$ constant for diode at given temperature (aka. saturation current)

$$(Eq3.1) \quad i = I_s (e^{v/V_T} - 1)$$

$V_T =$ thermal voltage

$k =$ Boltzmann's constant (8.62E-5 eV/K)

$q =$ magnitude of electron charge (1.6E-19 C)

$$(Eq3.2) \quad V_T = \frac{kT}{q} = 25.8mV$$

at room temperature

$I_s =$ constant for diode at given temperature (aka. saturation current)

$$(Eq3.3) \quad i = I_s e^{v/V_T}$$

3.2.1. The Forward-Bias Region

- Equation (3.3) may be **reversed** to yield (3.4).
- This relationship applies over as many as **seven decades of current**.

$I_S =$ constant for diode at given temperature (aka. saturation current)

$$\text{(Eq3.4) } v = V_T \ln \left(\frac{i}{I_S} \right)$$

3.2.1. The Forward-Bias Region

- **Q:** What is the relative effect of current flow (i) on forward biasing voltage (v)?
- **A:** Very small.
 - 10x change in i , effects 60mV change in v .

step #1: consider two cases (#1 and #2)

$$I_1 = I_S e^{V_1/V_T} \quad \text{and} \quad I_2 = I_S e^{V_2/V_T}$$

step #2: divide I_2 by I_1

$$\frac{I_2}{I_1} = \frac{I_S e^{V_2/V_T}}{I_S e^{V_1/V_T}}$$

step #3: combine two exponentials

$$\frac{I_2}{I_1} = e^{(V_2 - V_1)/V_T}$$

step #4: invert this expression

$$V_2 - V_1 = V_T \ln(I_2 / I_1)$$


step #5: convert to log base 10

$$V_2 - V_1 = 2.3V_T \log(I_2 / I_1)$$

$60mV \approx 2.3V_T \log(10/1)$

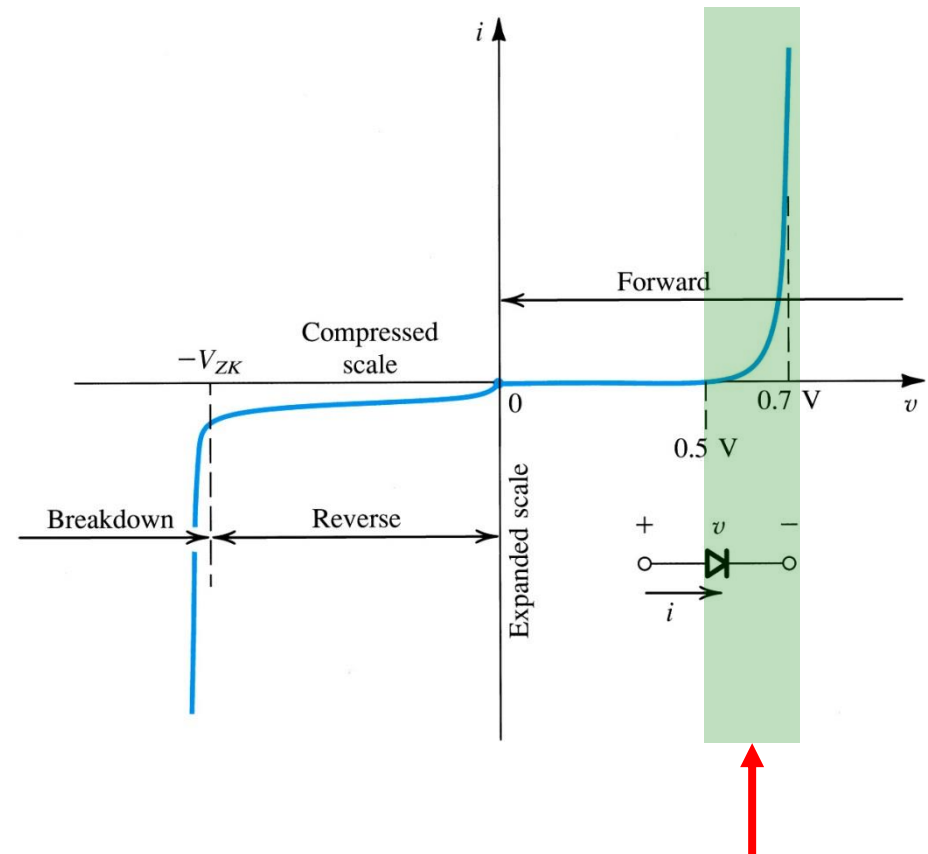3.2.1: The Forward-Bias Region

- **cut-in voltage** – is voltage, below which, **minimal current** flows
 - approximately 0.5V
- **fully conducting region** – is region in which R_{diode} is approximately equal 0
 - between **0.6 and 0.8V**



fully conducting region

3.2.2. The Reverse-Bias Region

- The **reverse-bias region of operation** is entered when $v < 0$.
- **I - V relationship**, for negative voltages with $|v| > V_T$ (25 **mV**), is closely approximated by equations to right.

this expression applies for negative voltages

$$i = -I_S e^{-|v|/V_T}$$

action: invert exponential

$$i = -I_S \left(\frac{1}{e^{|v|/V_T}} \right)$$

≈ 0 for larger voltage magnitudes


$$i = -I_S$$

3.2.2. The Reverse-Bias Region

- A “real” diode exhibits reverse-bias current, although small, **much larger than I_S** .
 - 10^{-9} vs. 10^{-14} ***Amps***
- A large part of this reverse current is attributed to **leakage effects**.

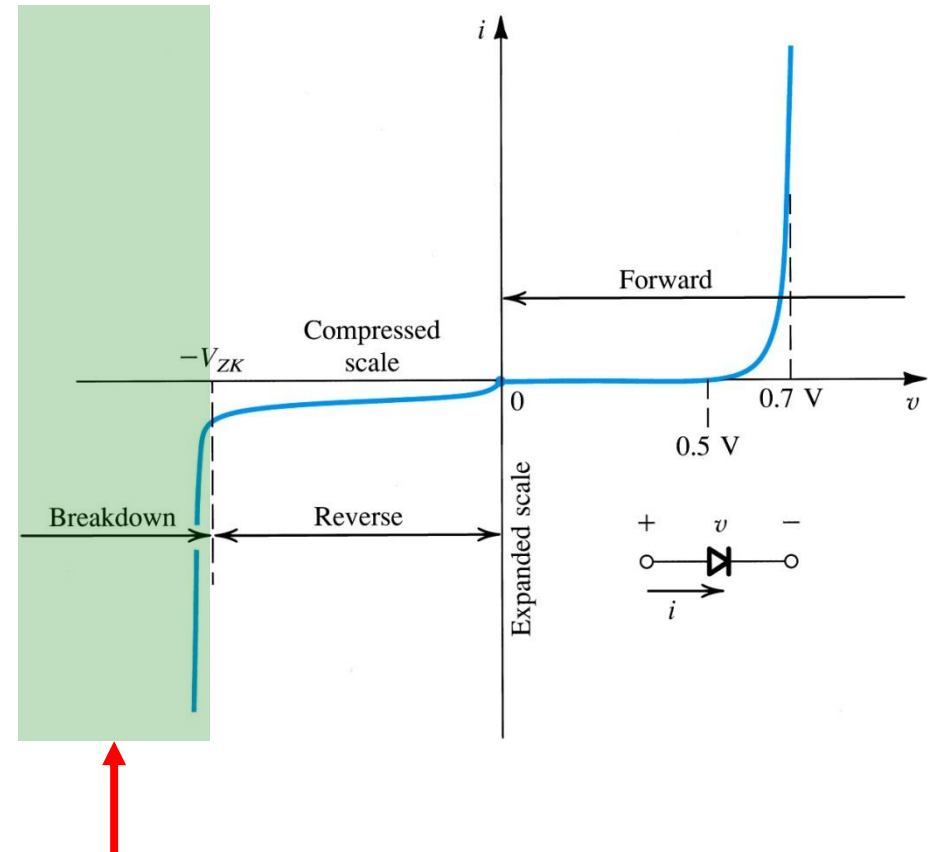3.2.3. The Breakdown Region

- The **breakdown region** of operation is entered when $v < V_{ZK}$.
 - **Zener-Knee Voltage (V_{ZK})**
- This is normally **non-destructive**.



breakdown region

$$i = I_s (e^{v/V_T} - 1)$$

