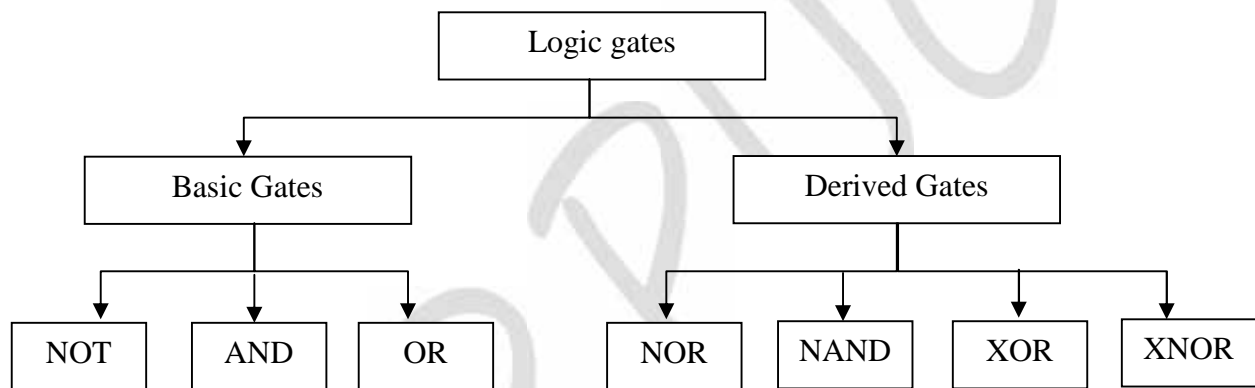


Chapter-3

LOGIC GATES

➤ Introduction:


- **Gate:** A Gate is a simply an electronic circuit which operates on one or more input signals and always produces an output signal.
- Gates are digital (two state) circuits because the input and output signals are either low voltage (0) or high voltage (1).
- Gates are often called logic circuits because they can be analyzed with Boolean algebra.
- Gates are classified into two types:



➤ Basic Gates:

➤ NOT Gate:

 
- A NOT gate has only one input and one output.
- The output state is always the opposite of the input state.
- A NOT Gate is also called as **Inverter** gate, because the output is not same as the input.
- The output is sometimes called the complement (opposite) of the input.
- The logical symbol and the truth table of NOT gate are given below.



X	\bar{X}
0	1
1	0

➤ OR Gate:

 
- A OR gate has two or more input signal but only one output signal.
- If any of the input signals is 1 (high), then the output is 1 (high).
- The logical symbol for two-input OR gate and the truth table is given below.



X	Y	F = X+Y
0	0	0
0	1	1
1	0	1
1	1	1

➤ **AND Gate:**

 
- A AND gate has two or more input signal but only one output signal.
- When all the input signals are 1 (high), the output is 1 (high), otherwise the output is 0.
- The logical symbol for two-input AND gate and the truth table is given below.




X	Y	F = X.Y
0	0	0
0	1	0
1	0	0
1	1	1

➤ **NOR Gate:**

- A NOR gate has two or more input signal but only one output signal.
- The NOR gate is a complemented of OR gate.
- The output of NOR gate will be 1 only when all inputs are 0 and output will be 0 if any input represents a 1.
- NOR is short form of NOT-OR.
- The symbol \downarrow is used to represent a NOR operation. So $\overline{X+Y}$ can be written as X NOR Y or X \downarrow Y.
- The logical structure shows an OR gate and NOT gate. For input X and Y, the output of the OR gate will be X+Y which is fed as input to the NOT gate. So the output of NOR gate is given by $\overline{X+Y}$ which is equal to $\bar{X} . \bar{Y}$.

 

 - The logical symbol for two-input NOR gate and the truth table is given below.




X	Y	F = $\overline{X+Y}$
0	0	1
0	1	0
1	0	0
1	1	0


X	Y	Z	F = $\overline{X+Y}$
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

➤ **NAND Gate:**

- A NAND gate has two or more input signal but only one output signal.
- The NAND gate is a complemented of AND gate.
- The output of NAND gate will be 0 only when all inputs are 1 and output will be 0 if any input represents a 0.
- NAND is short form of NOT-AND.
- The symbol ↑ is used to represent a NOR operation. So $\overline{X \cdot Y}$ can be written as X NAND Y or X ↑ Y.
- The logical structure shows an AND gate and NOT gate. For input X and Y, the output of the OR gate will be X . Y which is fed as input to the NOT gate. So the output of NAND gate is given by $\overline{X \cdot Y}$ which is equal to $\bar{X} + \bar{Y}$

 

 - The logical symbol for two-input NAND gate and the truth table is given below.



X	Y	F = $\overline{X \cdot Y}$
0	0	1
0	1	1
1	0	1
1	1	0

X	Y	Z	F = $\overline{X \cdot Y}$
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0


➤ **XOR (Exclusive-OR) Gate:**

- An exclusive-OR has two or more input signal but only one output signal.
- Exclusive-OR gate is different form of OR gate.
- Exclusive-OR gate produces output 1 for only those input combinations that have odd number of 1's.
- The output is 0 if there are even number of 1's in the input.
- The output is 1 if there are odd number of 1's in the input.
- In Boolean algebra, Θ sign stands for XOR operation. Thus X XOR Y can be written as $X \Theta Y$
- If the output is given by:

$$F = X \Theta Y$$

$$F = X \bar{Y} + \bar{X} Y$$

 - The XOR gate has a symbol similar to OR gate, except the additional curved line of the input side.



- The following truth table illustrates XOR operation for 2 and 3 inputs.

Number Of 1's	Input		Output
	X	Y	F = X ⊕ Y
EVEN	0	0	0
ODD	0	1	1
ODD	1	0	1
EVEN	1	1	0

Number of 1's	X	Y	Z	F = X ⊕ Y ⊕ Z
EVEN	0	0	0	0
ODD	0	0	1	1
ODD	0	1	0	1
EVEN	0	1	1	0
ODD	1	0	0	1
EVEN	1	0	1	0
EVEN	1	1	0	0
ODD	1	1	1	1


➤ **XNOR (Exclusive-NOR) Gate:**

- The XNOR gate is complement of XOR gate.
- The output of XNOR is 1 only when the logic values of both X and Y is same i.e. either both are equal to 1 or both are 0.
- Its output is 0 when its inputs are different.
- In Boolean algebra, \oplus sign stands for XNOR operation. Thus X XNOR Y can be written as $X \oplus Y$
- If the output is given by:

$$F = X \oplus Y$$

$$F = XY + \bar{X}\bar{Y}$$

 - The XNOR gate has a symbol similar to NOR gate, except the additional curved line of the input side.



- The following truth table illustrates XOR operation for 2 and 3 inputs.

Number Of 1's	Input		Output
	X	Y	F = X ⊙ Y
EVEN	0	0	1
ODD	0	1	0
ODD	1	0	0
EVEN	1	1	1

Number of 1's	X	Y	Z	F = X ⊙ Y ⊙ Z
EVEN	0	0	0	1
ODD	0	0	1	0
ODD	0	1	0	0
EVEN	0	1	1	1
ODD	1	0	0	0
EVEN	1	0	1	1
EVEN	1	1	0	1
ODD	1	1	1	0


➤ **Universal Gate (NAND & NOR):**

- *Universal gate is a gate using which all the basic gates can be designed.*
- NAND and NOR gate re called as Universal Gates, because all the Boolean functions can also be implemented using these two gates.
- NAND and NOR gates are more popular as these are less expensive and easier to design.

➤ **Realization of all basic gates using NAND gate:**

➤ **NAND to NOT:**

 - In the figure we have two input NAND gate whose inputs are purposely connected together so that the same input is applied to both.



- From the diagram $X \text{ NAND } X = \overline{X \cdot X}$
 $= \overline{X} + \overline{X}$ // DeMorgan's 2nd Theorem
 $= \overline{X}$ $\overline{X} + \overline{X} = \overline{X}$
 $= \text{Inverted Input} = \text{NOT gate}$

➤ **NAND to AND:**


- In the figure we have two NAND gates connected so that the AND operation is performed.
- NAND gate 2 is used as a NOT gate.



- From the diagram $X \text{ NAND } Y = F1 = \overline{X \cdot Y}$
 $F2 = \overline{F1 \cdot F1}$
 $= \overline{\overline{X \cdot Y} \cdot \overline{X \cdot Y}}$ // DeMorgan's 2nd Theorem
 $= \overline{\overline{X \cdot Y}}$ $\overline{\overline{X \cdot Y}} = X \cdot Y$
 $F2 = X \cdot Y$
 $= \text{AND gate}$

➤ **NAND to OR:**

 - The OR operation can be implemented using NAND gates connected as shown in figure.
- NAND gate 1 and NAND gate 2 are used as NOT to invert the inputs.




- From the diagram X NAND Y

$$\begin{aligned}
 F_1 &= \overline{X \cdot Y} \\
 F_2 &= \overline{X} + \overline{Y} \\
 F_3 &= \overline{F_1 \cdot F_2} \\
 &= \overline{\overline{X} + \overline{Y}} \quad // \text{DeMorgan's 2nd Theorem} \\
 &= \overline{\overline{X}} \cdot \overline{\overline{Y}} \quad \overline{\overline{X}} = X \text{ and } \overline{\overline{Y}} = Y \\
 F_3 &= X \cdot Y \\
 &= \text{OR gate}
 \end{aligned}$$

➤ Realization of all basic gates using NOR gate:

➤ NOR to NOT:

 - Figure shows that NOR gate with its inputs connected together behaves as a NOT gate.




- From the diagram X NOR X

$$\begin{aligned}
 &= \overline{X + X} \\
 &= \overline{X \cdot X} \quad // \text{DeMorgan's 1st Theorem} \\
 &= \overline{X} \quad \overline{X \cdot X} = \overline{X} \\
 &= \text{Inverted Input} = \text{NOT gate}
 \end{aligned}$$

➤ NOR to AND:

 - The AND operation can be implemented with NOR gate as shown in figure. Here NOR gate 1 and NOR gate 2 are used as NOT gate to invert inputs.




- From the diagram X NOR Y

$$\begin{aligned}
 F_1 &= \overline{X \cdot X} \\
 F_2 &= \overline{Y \cdot Y} \\
 F_3 &= \overline{F_1 + F_2} \\
 &= \overline{\overline{X} \cdot \overline{Y}} \quad // \text{DeMorgan's 1st Theorem} \\
 &= \overline{\overline{X}} \cdot \overline{\overline{Y}} \quad \overline{\overline{X}} = X \text{ and } \overline{\overline{Y}} = Y \\
 F_3 &= X \cdot Y \\
 &= \text{AND gate}
 \end{aligned}$$

➤ **NAND to OR:**

 - In the figure two NOR gates are arranged so that the OR operation is performed.
- NOR gate 2 is used as NOT gate.



- From the diagram X NOR Y

$$\begin{aligned}
 F_1 &= (X+Y)' \\
 F_2 &= ((X+Y)')' \\
 F_2 &= (X+Y) \quad // \text{DeMorgan's 1}^{st} \text{ Theorem} \\
 &= X+Y \\
 F_2 &= \overline{\overline{X+Y}} \\
 &= X+Y \quad \overline{\overline{X}} = X \\
 F_2 &= X+Y \\
 &= \text{OR gate}
 \end{aligned}$$

➤ **Designing of Logic Circuit using all basic gates :**

➤ **Designing of Logic Circuit using NAND and NOR gates:**

CHAPTER – LOGIC GATES BLUE PRINT			
VSA (1 marks)	LA (3 Marks)	-	Total
01 Question	01 Question	-	02 Questions
Question No 1	Question No 20	-	04 Marks