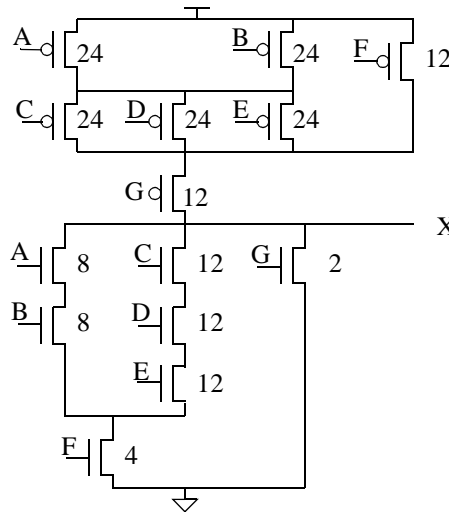


Chapter 6 PROBLEMS

1. [E, None, 4.2] Implement the equation $X = ((\bar{A} + \bar{B})(\bar{C} + \bar{D} + \bar{E}) + \bar{F})\bar{G}$ using complementary CMOS. Size the devices so that the output resistance is the same as that of an inverter with an NMOS $W/L = 2$ and PMOS $W/L = 6$. Which input pattern(s) would give the worst and best equivalent pull-up or pull-down resistance?

Solution

Rewriting the output expression in the form $X = ((\bar{A} + \bar{B})(\bar{C} + \bar{D} + \bar{E}) + \bar{F})\bar{G} = \overline{((AB + CDE)F) + G}$ allows us to build the pulldown network by inspection (parallel devices implement an OR, and series devices implement an AND). The pullup network is the dual of the pulldown network.



The plot shows sizes that meet the requirement - in the worst case, the output resistance of the circuit matches the output resistance of an inverter with NMOS $W/L=2$ and PMOS $W/L=6$.

The worst case pull-up resistance occurs whenever a single path exists from the output node to Vdd. Examples of vectors for the worst case are ABCDEFG=1111100 and 0101110. The best case pull-up resistance occurs when ABCDEFG=0000000.

The worst case pull-down resistance occurs whenever a single path exists from the output node to GND. Examples of vectors for the worst case are ABCDEFG=0000001 and 0011110.


The best case pull-down resistance occurs when ABCDEFG=1111111.

2. Implement the following expression in a full static CMOS logic fashion using no more than 10 transistors:

$$\bar{Y} = (A \cdot B) + (A \cdot C \cdot E) + (D \cdot E) + (D \cdot C \cdot B)$$

Solution

The circuit is given in the next figure.

 

3. Consider the circuit of Figure 6.1.

 


Figure 6.1 CMOS combinational logic gate.

- a. What is the logic function implemented by the CMOS transistor network? Size the NMOS and PMOS devices so that the output resistance is the same as that of an inverter with an NMOS $W/L = 4$ and PMOS $W/L = 8$.

Solution

The logic function is : $Y = \overline{(A + B)CD}$. The transistor sizes are given in the figure above.

- b. What are the input patterns that give the worst case t_{pHL} and t_{pLH} . State clearly what are the initial input patterns and which input(s) has to make a transition in order to achieve this maximum propagation delay. Consider the effect of the capacitances at the internal nodes.

Solution

The worst case t_{pHL} happens when the internal node capacitances ($Cx2$ and $Cx3$) are charged before the high to low transition. The initial states that can cause this are: $ABCD = [1010, 1110, 0110]$. The final state is one of: $ABCD = [1011, 0111]$.

The worst case t_{pLH} happens when C_{x1} is charged before the low to high transition. The input pattern that can cause this is: ABCD=[0111] =>[0011].

c. Verify part (b) with SPICE. Assume all transistors have minimum gate length (0.25 μ m).

Solution

The two cases are shown below.

 


Figure 6.2 Best and worst t_{pHL} .

 


Figure 6.3 Best and worst t_{pLH} .

d. If $P(A=1)=0.5$, $P(B=1)=0.2$, $P(C=1)=0.3$ and $P(D=1)=1$, determine the power dissipation in the logic gate. Assume $V_{DD}=2.5V$, $C_{out}=30fF$ and $f_{clk}=250MHz$.

Solution

Since D is always 1, the circuit implements the following function $Y = \overline{(A + B)C}$.

$$P_{(A+B)=1} = P_{A=0} \cdot P_{B=0} = 0.5 \cdot (1-0.2) = 0.4,$$

$$P_{(A+B)=0} = 1 - 0.4 = 0.6,$$

$$P_{Y=0} = P_{(A+B)=1} \cdot P_C = 1 = 0.6 \cdot 0.3 = 0.18$$

$$P_{Y=1} = 1 - 0.18 = 0.82$$

$$P_{Y=0 \Rightarrow 1} = 0.18 \cdot 0.82 = 0.1476$$

$$\text{So } P_{dyn} = P_{Y=0 \Rightarrow 1} C_{out} V_{DD}^2 f_{clk} = (0.1476)(30 \cdot 10^{-15})(2.5^2)(250 \cdot 10^6) = 6.92 \mu W.$$

4. [M, None, 4.2] CMOS Logic

a. Do the following two circuits (Figure 6.4) implement the same logic function? If yes, what is that logic function? If no, give Boolean expressions for both circuits.

Solution

Yes, they implement the same logic function :

$$F = (ABCD + E) = (A + B + C + D).E$$

- b. Will these two circuits' output resistances always be equal to each other?

Solution

No

- c. Will these two circuits' rise and fall times always be equal to each other? Why or why not?

Solution

No. Circuit B appears optimized for the case where the transistor with input E is on the critical path since it is closer to the output node than in circuit A. Therefore, if input E arrives later, circuit B will be faster than circuit A since the internal node will already be charged and only the output capacitance needs to be switched. Even if we assume, all inputs arrive at the same time, however, the two circuits rise and fall times will not be equal to each other. Consider an input combination where E,A,B,C,D are all low. Circuit A has only one body-affected device while circuit B has four. Since the associated rise in V_t and fall in output resistance affects only one resistor in circuit A, but four parallel resistors in circuit B, we expect a difference in the timing waveforms.

 


Figure 6.4 Two static CMOS gates.

5. [E, None, 4.2] The transistors in the circuits of the preceding problem have been sized to give an output resistance of $13 \text{ k}\Omega$ for the worst-case input pattern. This output resistance can vary, however, if other patterns are applied.
- a. What input patterns (A–E) give the lowest output resistance when the output is low? What is the value of that resistance?

Solution

The lowest output resistance is obtained when all inputs (A, B, C, D and E) are equal to 1. In that case, the output resistance is the parallel of the resistance of a nMOS of width 1, with a series of four equal nMOS of width 4. Both combinations have the same resistance, equal to the worst-case output resistance, $13 \text{ k}\Omega$. Then the output resistance, in this case, is half this value, $6.5 \text{ k}\Omega$.

- b. What input patterns (A–E) give the lowest output resistance when the output is high? What is the value of that resistance?

Solution

The lowest output resistance is obtained when all inputs are equal to zero. Each of the pMOS have the same width, so all of them have the same resistance. The worst case resistance happens when only one of the inputs (A, B, C or D) is equal to 0 while all the rest are equal to 1. The output resistance in that case is the series of the resistance of two of the pMOS and it is equal to $13\text{ k}\Omega$. Then, each of the pMOS has an output resistance equal to $6.5\text{ k}\Omega$. The output resistance is equal to the series of one of these resistance with the parallel of four of the same resistances. Then, the minimum output resistance is $6.5\text{ k}\Omega + 6.5\text{ k}\Omega / 4 = 8.125\text{ k}\Omega$.

6. [E, None, 4.2] What is the logic function of circuits A and B in Figure 6.5? Which one is a dual network and which one is not? Is the nondual network still a valid static logic gate? Explain. List any advantages of one configuration over the other.

 


Figure 6.5 Two logic functions.

Solution

Both circuits A and B implement the XOR logic function. Circuit A is a dual network because the pull up network is dual with the pull down network.

However, circuit B is still a valid static logic gate, because for any combination of the inputs, there is either a low resistance path from V_{DD} or ground to the output. Circuit B has an extra advantage. The internal node capacitances are less compared to Circuit A, which make it faster than Circuit A.

7. [E, None, 4.2] Compute the following for the pseudo-NMOS inverter shown in Figure 6.6:
 a. V_{OL} and V_{OH}

Solution

To find V_{OH} , set V_{in} to 0, because V_{OL} is likely to be below V_{T0} for the NMOS. If $V_{in}=0$, then M_1 is off, so the PMOS pulls the output all the way to the rail. So, $V_{OH}=V_{DD}=2.5\text{V}$.

To find V_{OL} , set $V_{in} = V_{OH} = 2.5\text{V}$. The NMOS is all the way on, but so is the PMOS. To find V_{OL} , we can write a current balancing equation at the output node: $I_{DP}+I_{DN}=0$. First, we must determine the region of operation for each device. We can assume that $V_{DS} = V_{OL}$ for the NMOS is less than V_{DSAT} , so the NMOS is in the linear region. V_{DS} for the PMOS will be more negative than V_{DSAT} , and $V_{GTP} = -2.1$, so the PMOS is velocity saturated. The equation is therefore:

$$k'_p \cdot \frac{W}{L} \cdot V_{DSAT} \cdot (V_{GT} - 0.5V_{DSAT}) \cdot (1 + \lambda V_{DS}) + k'_n \cdot \frac{W}{L} \cdot V_o \cdot (V_{GT} - 0.5V_o) \cdot (1 + \lambda V_o) = 0$$

Plugging in numbers (process parameters such as V_{DSAT} appear in tables in previous chapters) gives:

$$-30 \cdot 2 \cdot -1 \cdot (-1.6) \cdot (1 - 0.1(V_o - 2.5)) + 115(16) \cdot V_o \cdot (2.07 - 0.5V_o) \cdot (1 + 0.06V_o) = 0$$

Solving for V_o gives $V_{OL} = 31.6\text{mV}$.

b. NM_L and NM_H

Solution

Rather than calculating the derivative of the current, we will estimate V_{IL} and V_{IH} from the simulated VTC. This approach estimates that the noise margin low is about 0.47V and the noise margin high is about 1.67V .

c. The power dissipation: (1) for V_{in} low, and (2) for V_{in} high

Solution

For V_{in} low, the NMOS is off, so the power dissipation is 0W . For V_{in} high, $P = VI = 2.5 \cdot I_{DP}$. We saw in part a) the equation for I_{DP} . Plugging in the value for V_{OL} , we get $P = VI = 2.5 \cdot 120 \mu\text{A} = 300 \mu\text{W}$.

d. For an output load of 1pF , calculate t_{pLH} , t_{pHL} , and t_p . Are the rising and falling delays equal? Why or why not?

 


Figure 6.6 Pseudo-NMOS inverter.

Solution

We cannot use the estimate of resistance from the I-V curve for the HL transition because the PMOS is still on. Therefore, we will use the average current method for estimating delay. The average current for the HL transition through the PMOS is $0.5(I_{V_{DD}=2.5} + I_{V_{DD}=1.25})$. $I_{V_{DD}=2.5} = 0$. $I_{V_{DD}=1.25} = -30(2)(-1)(-2.1+0.5) \cdot (1+0.1(1.25)) = 108\mu\text{A}$. Thus, I_{avg} for the PMOS is $54\mu\text{A}$.

For the NMOS, $I_{V_{DD}=2.5} = 115(16)(0.63)(2.07 - .63/2)(1+0.06 \cdot 2.5) = 2.4\text{mA}$ and $I_{V_{DD}=1.25} = 115(16)(0.63) \cdot (2.07 - .63/2)(1+0.06 \cdot 1.25) = 2.2\text{mA}$. So, I_{avg} for the NMOS is 2.3mA . The average current discharging the capacitor is then $2.3\text{mA} - 54\mu\text{A} = 2.25\text{mA}$. Then $t_{pHL} = C \cdot \Delta V / I_{avg} = 556\text{ps}$.

For t_{pLH} , the NMOS is off, so we can use equivalent resistance to find the transition time. From the table of resistances in the text, we can calculate $R_{EQ} = 31\text{k}\Omega / (W/L_p) = 15.5\text{k}\Omega$. Then $t_{pLH} = 0.69 \cdot C \cdot R_{EQ}$. So $t_{pLH} = 10.7\text{ns}$.

$t_p = (t_{pLH} + t_{pHL}) / 2 = 5.6\text{ns}$. The rising delay is much longer because the PMOS is very weak relative to the NMOS.

8. [M, SPICE, 4.2] Consider the circuit of Figure 6.7.

a. What is the output voltage if only one input is high? If all four inputs are high?

Solution

$$I_D = k' \cdot \frac{W}{L} \cdot \left(V_{GT} \cdot V_{min} - \frac{V_{min}^2}{2} \right) \cdot (1 + \lambda \cdot V_{DS})$$

Consider a case when one input is high: $A = V_{DD}$ and $B = C = D = 0$ V. Assume that V_{out} is small enough that $V_{min} = V_{DSAT}$ for the PMOS device, and $V_{min} = V_{DS} = V_{out}$ for the NMOS devices. Solve for V_{out} by setting the drain currents in the PMOS and NMOS equal to each other, $|I_{DP}| = |I_{DN}|$, where the drain currents are functions of V_{out} , V_{DD} , and the device parameters.

$V_{out} = 102$ mV, and $I_D = 35.7$ μ A.

Now verify that the assumptions for V_{min} are correct. For the PMOS: $V_{DS} = -2.34$ V, $V_{DSAT} = -1$ V, $V_{GT} = -2.1$ V, therefore $V_{min} = V_{DSAT}$. For the NMOS: $V_{DS} = 102$ mV, $V_{DSAT} = 630$ mV, $V_{GT} = 2.07$ V, therefore $V_{min} = V_{DS}$.

Consider the case when all inputs are high: $A = B = C = D = V_{DD}$. For these hand calculations, this is numerically equivalent to a circuit with a single NMOS device with $W/L = 4 \cdot 1.5$ and its gate tied to V_{DD} . Now, the analysis used above for the case when one device is on can be reused, replacing W/L of the NMOS with 6, and using the same assumptions for V_{min} . $V_{out} = 25$ mV, and $I_D = 35.9$ μ A. The assumptions for V_{min} are correct.

b. What is the average static power consumption if, at any time, each input turns on with an (independent) probability of 0.5? 0.1?

Solution

Notice in part a) that the drain current in the PMOS is 35.7 μ A with one NMOS on and 35.9 μ A with four NMOS devices on. The current in the PMOS can be approximated as 35.8 μ A when any number of NMOS devices are on and 0 μ A when all four are off. The probability that all four NMOS devices are off is $(1-\rho)^4$ where ρ is the probability an input is high. Therefore,

$$P_{AVG} = P_{OFF} \cdot (1 - \rho)^4 + P_{ON} \cdot [1 - (1 - \rho)^4]$$

where $P_{OFF} = 0$ W, and $P_{ON} = 89.5$ μ W. $P_{AVG} = 83.9$ μ W when $\rho = 0.5$ and $P_{AVG} = 30.7$ μ W when $\rho = 0.1$.

c. Compare your analytically obtained results to a SPICE simulation.

Solution

From SPICE: $V_{out} = 98.7$ mV, and $I_D = 38.2$ μ A with one NMOS device on and $V_{out} = 23.5$ mV, and $I_D = 38.3$ μ A with all NMOS devices on.

 
 


Figure 6.7 Pseudo-NMOS gate.

9. [M, None, 4.2] Implement $F = \overline{ABC} + \overline{ACD}$ (and \overline{F}) in DCVSL. Assume A, B, C, D , and their complements are available as inputs. Use the minimum number of transistors.

Solution

10. [E, Layout, 4.2] A complex logic gate is shown in Figure 6.8.
- a. Write the Boolean equations for outputs F and G . What function does this circuit implement?

Solution

$$G = A(\text{XOR})B$$

$$F = A(\text{XNOR})B$$

- b. What logic family does this circuit belong to?

Solution

It belongs to the DCVSL logic family.

- c. Assuming $W/L = 0.5\mu/0.25\mu$ for all *nmos* transistors and $W/L = 2\mu/0.25\mu$ for the *pmos* transistors, produce a layout of the gate using Magic. Your layout should conform to the following datapath style: (1) Inputs should enter the layout from the left in polysilicon; (2) The outputs should exit the layout at the right in polysilicon (since the outputs would probably be driving transistor gate inputs of the next cell to the right); (3) Power and ground lines should run vertically in metal 1.

 


Figure 6.8 Two-input complex logic gate.

- d. Extract and netlist the layout. Load both outputs (F,G) with a 30fF capacitance and simulate the circuit. Does the gate function properly? If not, explain why and resize the transistors so that it does. Change the sizes (and areas and perimeters) in the HSPICE netlist.

Solution

The gate doesn't function properly, because the PMOS devices are strong and the NMOS pull down network can not switch the output nodes .

If you decrease the PMOS sizes to $W=0.5\mu\text{m}$, then the logic gate will function properly.

- Design and simulate a circuit that generates an optimal differential signal as shown in Figure 6.9. Make sure the rise and fall times are equal.


 


Figure 6.9 Differential Buffer.

Solution

The circuit is shown below.

 

If the inverters are sized for equal rise and fall times then you can achieve equal rise and fall times on the differential outputs, as long as the other FETs are sized symmetrically.

- What is the function of the circuit in Figure 6.10?

 


Figure 6.10 Gate.


Solution

The circuit implements an S-R latch. Set is A and Reset is B. The invalid state is when both A and B are 0.

- Implement the function $S = ABC + \overline{ABC} + \overline{ABC} + \overline{ABC}$, which gives the sum of two inputs with a carry bit, using NMOS pass transistor logic. Design a DCVSL gate which implements the same function. Assume A, B, C, and their complements are available as inputs.

Solution

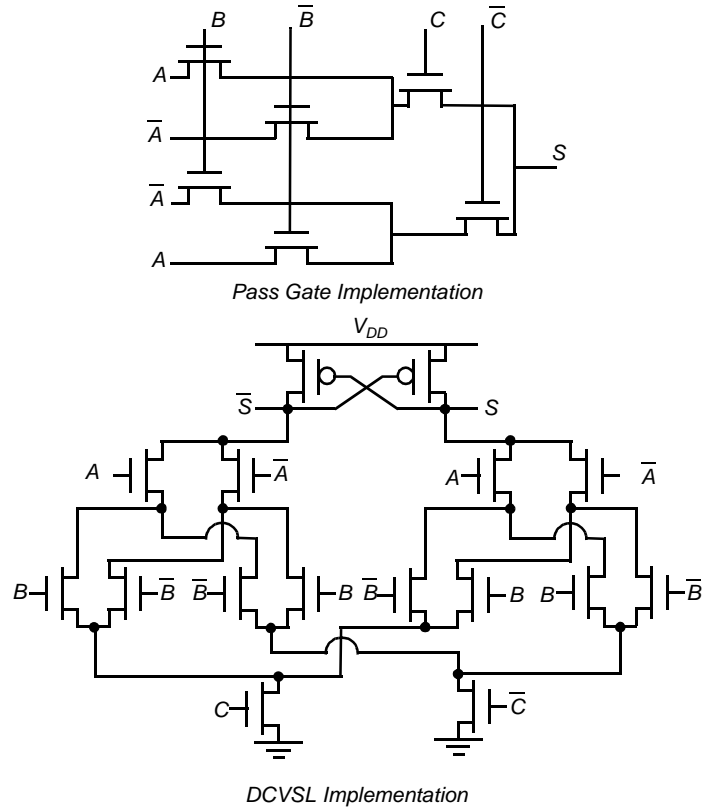The two cases are shown in the figure below.



14. Describe the logic function computed by the circuit in Figure 6.11. Note that all transistors (except for the middle inverters) are NMOS. Size and simulate the circuit so that it achieves a 100 ps delay (50-50) using 0.25 μ m devices, while driving a 100 fF load on both differential outputs. ($V_{DD} = 2.5V$). Assume A, B and their complements are available as inputs.

 


Figure 6.11 Cascoded Logic Styles.

For the drain and source perimeters and areas you can use the following approximations: $AS=AD=W \cdot 0.625u$ and $PS=PD=W+1.25u$.

15.

Solution

The circuit implements an XOR. The sizes of the transistors are M1: $28u/0.25u$, M2: $28u/0.25u$, M3: $10u/0.25u$, M4: $10u/0.25u$. $M_{pinv}: 4u/0.25$, $M_{Ninv}: 0.375u/10u$

16. [M, None. 4.2] Figure 6.12 contains a pass-gate logic network.

a. Determine the truth table for the circuit. What logic function does it implement?

Solution

The truth table is shown below

AB	Out
00	1
01	0
10	0
11	1

The circuit implements an XNOR.

b. Assuming 0 and 2.5 V inputs, size the PMOS transistor to achieve a $V_{OL} = 0.3$ V.

Solution

The PMOS device will be velocity saturated and the NMOS passgate will be in the linear region. $I_{DN}+I_{DP}=0$, so

$$k'_p \cdot \frac{W}{L} \cdot v_{DSAT} \cdot (V_{GT} - 0.5V_{DSAT}) \cdot (1 + \lambda V_{DS}) + k'_n \cdot \frac{W}{L} \cdot V_o \cdot (V_{GT} - 0.5V_o) \cdot (1 + \lambda V_o) = 0$$

We know that $V_o=0.3V$, so we can plug in numbers and solve for W/L for the PMOS is 7. Let the PMOS be $1.75/0.25$.

c. If the PMOS were removed, would the circuit still function correctly? Does the PMOS transistor serve any useful purpose?

 


Figure 6.12 Pass-gate network.

Solution

No. If the PMOS were removed, the output node could remain low when $AB=00$ because it would be floating. The PMOS device pulls the output node high when it would otherwise be in a high impedance state.

17. [M, None, 4.2] This problem considers the effects of process scaling on pass-gate logic.

- a. If a process has a t_{buf} of 0.4 ns, R_{eq} of 8 k Ω , and C of 12 fF, what is the optimal number of stages between buffers in a pass-gate chain?

Solution

$$m_{opt} = 1.7 \sqrt{t_p / (R_{eq} \cdot C)} = 3.47 \approx 3 \text{ gates between buffers.}$$

- b. Suppose that, if the dimension of this process are shrunk by a factor S , R_{eq} scales as $1/S^2$, C scales as $1/S$, and t_{buf} scales as $1/S^2$. What is the expression for the optimal number of buffers as a function of S ? What is this value if $S = 2$?

Solution

$$m_{opt} = 1.7 \sqrt{\frac{t_p / S^2}{R_{eq} / S^2 \cdot C / S}} = 1.7 \sqrt{\frac{S \cdot t_p}{R_{eq} \cdot C}} = 4.9 \approx 5 \text{ gates between buffers.}$$

18. [C, None, 4.2] Consider the circuit of Figure 6.13. Let $C_x = 50$ fF, M_r has $W/L = 0.375/0.375$, M_n has $W/L_{eff} = 0.375/0.25$. Assume the output inverter doesn't switch until its input equals $V_{DD}/2$.

- a. How long will it take M_n to pull down node x from 2.5 V to 1.25 V if I_n is at 0 V and B is at 2.5V?

Solution

To determine the time required for these transitions, we will find the average currents in the FETs M_r and M_n . The equivalent resistance method will not suffice since it does not account for both devices being on.

For M_r , $I_{V_{DD}=2.5} = 0$ since $V_{DS} = 0$. For the other case, the PMOS device is velocity saturated, so:

$I_{V_{DD}=1.25} = (-30)(1)(-1)(-2.1+0.5)(1+0.1*1.25) = -54\mu\text{A}$. The average current in the PMOS is $-27\mu\text{A}$.

M_n is in the velocity saturation region for both endpoints of the transition. The two currents are therefore:

$$I_{V_{DD}=2.5} = (115)(1.5)(0.63)(2.07-0.63/2)(1+0.06*2.5) = 219\mu\text{A}.$$

$$I_{V_{DD}=1.25} = (115)(1.5)(0.63)(2.07-0.63/2)(1+0.06*2.5) = 205\mu\text{A}.$$

And the average current in the NMOS is $212\mu\text{A}$.

The total current DISCHARGING the capacitor is $211\mu\text{A} - 27\mu\text{A} = 185\mu\text{A}$.

The time for the transition is then

$$t = \frac{C \times DV}{I_{avg}} = \frac{50\text{fF} \times 1.25\text{V}}{185\mu\text{A}} = 338\text{ps}.$$

- b. How long will it take M_n to pull up node x from 0 V to 1.25 V if V_{in} is 2.5 V and V_B is 2.5 V?

Solution

For the LH transition, the PMOS "keeper" is off. The NMOS M_n is the only FET that is on for this transition. We present both methods for finding the pull-up time.

Equivalent Resistance: We need to perform a different sweep for this measurement than the regular I_D vs V_{DS} sweep. In this case, V_{DS} is changing because the *source node* of the FET is rising. Since the source voltage is changing, V_{GS} also is reducing as node x rises. This effectively "turns down" the current the NMOS can sustain. Performing the appropriate sweep and measuring R_{EQ} gives $R_{EQ} = (11.3\text{k}\Omega + 34.7\text{k}\Omega) / 2 = 23\text{k}\Omega$. Thus,

$$t = 0.69 \cdot C \cdot R_{EQ} = 0.69 \cdot 50\text{fF} \cdot 23\text{k}\Omega = 794\text{ps}.$$

Average Current: When $x = 0$, the pass transistor has a $V_{GS} = 2.5$ and a $V_{DS} = 2.5$, so it is velocity saturated.

$$I_{x=0} = (115)(1.5)(0.63)(2.07-0.63/2)(1+0.06*2.5) = 219\mu\text{A}.$$

When $x = 1.25$, the pass transistor has $V_{DS} = 1.25$ and $V_{GS} = 1.25$. It is still velocity saturated, but notice that V_{GS} has decreased. Thus,

$$I_{x=1.25} = (115)(1.5)(0.63)(1.25-0.43-0.63/2)(1+0.06*1.25) = 59\mu\text{A}.$$

The average current is then $I_{avg} = 139\mu\text{A}$.

$$t = \frac{C \times DV}{I_{avg}} = \frac{50\text{fF} \times 1.25\text{V}}{139\mu\text{A}} = 450\text{ps}.$$

Clearly, the two solutions are not very close together. The actual **simulated transition time is about 644ps**. The I_{avg} approximation underestimates the solution because the true average current in this case is not close to the average of the endpoints. In a typical inverter (PMOS pullup and NMOS pulldown), V_{GS} doesn't change over the transition, so the current is reasonably linear with V_{DS} . For that case, the average current is close to the average of the endpoints. In this problem, the pinch-off of $V_{GS}-V_T$ in the pass transistor means the average is closer to the smaller value. Numerical calculation of the average current from an HSPICE sim gives $I_{avg} = 93\mu\text{A}$ which would give a transition time of $t = 672\text{ps}$, which is much closer to the actual value.

c. What is the minimum value of V_B necessary to pull down V_x to 1.25 V when $V_{in} = 0$ V?

Solution

In order for M_n to pull node x low, the current in M_r must equal or exceed the current that charges up the capacitor at every point in the transition. The maximum current in M_r occurs when $x = 1.25$ V, and it is (from part a) $I_{M_r} = -54\mu\text{A}$. We can write a current equation for M_n at this point in the transition and solve for V_B :

Note that M_n is velocity saturated at this point: $54 = 115(1.5)(0.63)(V_B-0.43-0.63/2)(1+0.06*1.25)$.

Solving gives $V_B = 1.207\text{V}$.

 


Figure 6.13 Level restorer.

19. Pass Transistor Logic

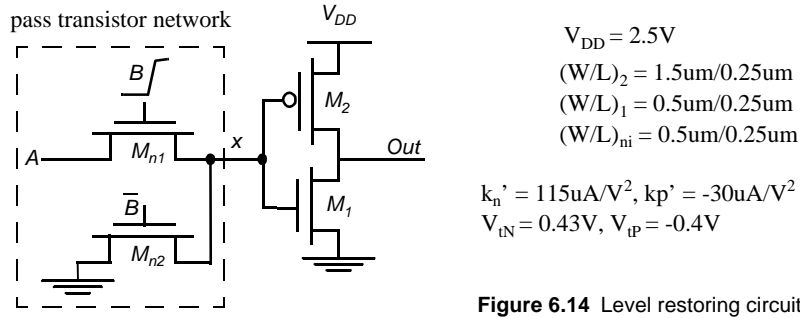


Figure 6.14 Level restoring circuit.

Consider the circuit of Figure 6.14. Assume the inverter switches ideally at $V_{DD}/2$, neglect body effect, channel length modulation and all parasitic capacitance throughout this problem.

a. What is the logic function performed by this circuit?

Solution

The circuit is a NAND gate.

b. Explain why this circuit has non-zero static dissipation.


Solution

When $A=B=V_{DD}$, the voltage at node x is $V_x = V_{DD} - V_{tN}$. This causes static power dissipation at the inverter the pass transistor network is driving.

 c. Using only just 1 transistor, design a fix so that there will not be any static power dissipation. Explain how you chose the size of the transistor.

Solution

The modified circuit is shown in the next figure.




The size of M_r should be chosen so that when one of the inputs A or B equals 0, either M_{n1} or M_{n2} , would be able to pull node X to $V_{DD}/2$ or less.

d. Implement the same circuit using transmission gates.

Solution


The circuit is shown below.

 

- e. Replace the pass-transistor network in Figure 6.14 with a pass transistor network that computes the following function: $x = ABC$ at the node x . Assume you have the true and complementary versions of the three inputs A, B and C .

Solution

One possible implementation is shown.

 

20. [M, None, 4.3] Sketch the waveforms at x , y , and z for the given inputs (Figure 6.15). You may approximate the time scale, but be sure to compute the voltage levels. Assume that $V_T = 0.5$ V when body effect is a factor.
21. [E, None, 4.3] Consider the circuit of Figure 6.16.
- a. Give the logic function of x and y in terms of A , B , and C . Sketch the waveforms at x and y for the given inputs. Do x and y evaluate to the values you expected from their logic functions? Explain.

Solution

$$x = \overline{AB} \text{ and } y = ABC$$

The circuit does not correctly implement the desired logic function. This stems from the fact that x is pre-charged high, and thus node y is discharged as soon as the evaluation phase starts. Although x is eventually discharged by the first stage, y cannot be charged high again since it is a dynamic node with no low-impedance path to V_{dd} (during evaluate). Common solutions to this problem are to either place an inverter between the two stages (thus allowing only 0-to-1 transitions on the inputs to each stage during evaluate) as in Domino logic or employing np -CMOS. The latter is presented in (b).

- b. Redesign the gates using np -CMOS to eliminate any race conditions. Sketch the waveforms at x and y for your new circuit.

Solution

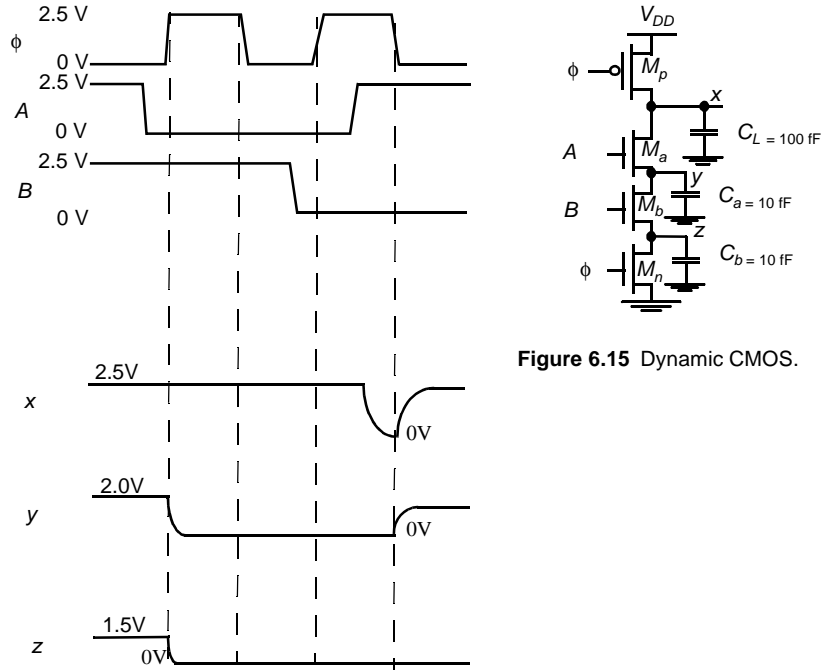


Figure 6.15 Dynamic CMOS.


The modified circuit using np-CMOS is shown below together with the waveforms at x and y. The desired logic function is now correctly implemented

22. [M, None, 4.3] Suppose we wish to implement the two logic functions given by $F = A + B + C$ and $G = A + B + C + D$. Assume both true and complementary signals are available.

 - a. Implement these functions in dynamic CMOS as cascaded ϕ stages so as to minimize the total transistor count.

Solution

Dynamic gates with NMOS pull-down networks cannot be directly cascaded. This solution uses a domino logic approach.



- b. Design an np-CMOS implementation of the same logic functions.

Solution



 
 


Figure 6.16 Cascaded dynamic gates.

 

The circuit is shown below

 

23. Consider a conventional 4-stage Domino logic circuit as shown in Figure 6.17 in which all precharge and evaluate devices are clocked using a common clock ϕ . For this entire problem, assume that the pulldown network is simply a single NMOS device, so that each Domino stage consists of a dynamic inverter followed by a static inverter. Assume that the precharge

time, evaluate time, and propagation delay of the static inverter are all $T/2$. Assume that the transitions are ideal (zero rise/fall times).


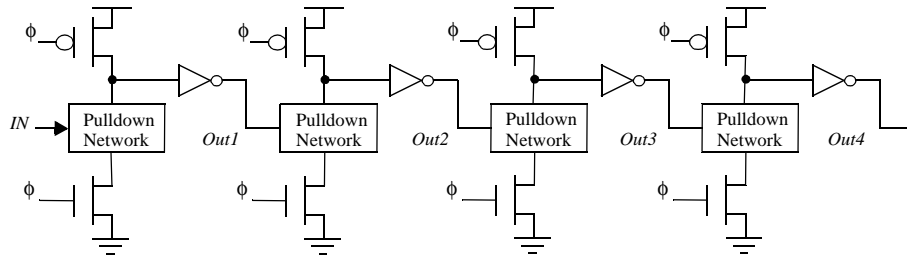


Figure 6.17 Conventional DOMINO Dynamic Logic.

- a. Complete the timing diagram for signals Out_1 , Out_2 , Out_3 and Out_4 , when the IN signal goes high before the rising edge of the clock ϕ . Assume that the clock period is $10 T$ time units.

Solution

The timing diagram is shown below.

 

- b. Suppose that there are no evaluate switches at the 3 latter stages. Assume that the clock ϕ is initially in the precharge state ($\phi=0$ with all nodes settled to the correct precharge states), and the block enters the evaluate period ($\phi=1$). Is there a problem during the evaluate period, or is there a benefit? Explain.

Solution

There is no problem during the evaluate stage. The precharged nodes remain charged until a signal propagates through the logic, activating the pull-down network and discharging the node. In fact, this topology improves the circuit's robustness in terms of charge sharing affecting the output for any generic pull-down network, and reduces the body effect in the pull-down network.

- c. Assume that the clock ϕ is initially in the evaluate state ($\phi=1$), and the block enters the precharge state ($\phi = 0$). Is there a problem, or is there any benefit, if the last three evaluate switches are removed? Explain.

Solution

There is a problem during the precharge stage. If all precharged nodes are discharged during the evaluate stage, when the precharge FETs simultaneously turn on, the pull-down

networks will initially remain on, creating a short circuit. This continues in each gate until the previous gate charges, disabling its pull-down network.

24. [C, Spice, 4.3] Figure 6.18 shows a dynamic CMOS circuit in Domino logic. In determining source and drain areas and perimeters, you may use the following approximations: $AD = AS = W \times 0.625\mu\text{m}$ and $PD = PS = W + 1.25\mu\text{m}$. Assume 0.1 ns rise/fall times for all inputs, including the clock. Furthermore, you may assume that all the inputs and their complements are available, and that all inputs change during the precharge phase of the clock cycle.

- a. What Boolean functions are implemented at outputs F and G ? If A and B are interpreted as two-bit binary words, $A = A_1A_0$ and $B = B_1B_0$, then what interpretation can be applied to output G ?

Solution

$$F = A_0B_0 + \bar{A}_1\bar{B}_1, G = F(A_0B_0 + \bar{A}_1\bar{B}_1)$$

If A and B are interpreted as two-bit binary words, output G is high if $A = B$: a comparator

- b. Which gate (1 or 2) has the highest potential for harmful charge sharing and why? What sequence of inputs (spanning two clock cycles) results in the worst-case charge-sharing scenario? Using SPICE, determine the extent to which charge sharing affects the circuit for this worst case.

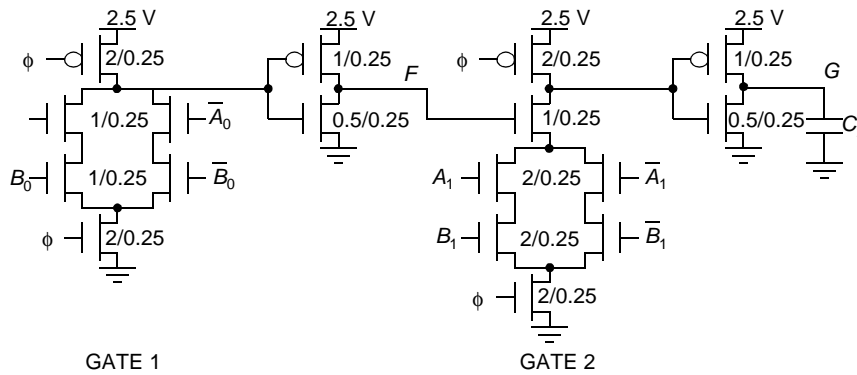



Figure 6.18 DOMINO logic circuit.

Solution

Gate 2 has the higher potential for harmful charge sharing because the capacitance that contributes to charge sharing is larger than in gate 1.

The sequence of inputs resulting in the worst-case charge sharing is $A_0 = B_0$ and $A_1 = B_1$ for the first cycle. Then $A_0 = B_0$ and $A_1 \neq B_1$ for the second cycle such that A_1/\bar{A}_1 transistor that is on during the second cycle is the same as in the first cycle. For example, $A_0 = B_0 = A_1 = B_1 = V_{DD}$ in cycle 1 and $A_0 = B_0 = A_1 = V_{DD}, B_1 = 0$ V in cycle 2. This

 
will cause the charge at the output of gate 2 to be shared with the total parasitic capacitance at the drains of the A_1 , \bar{A}_1 , and B_1 transistors.



 25. [M, Spice, 4.3] In this problem you will consider methods for eliminating charge sharing in the circuit of Figure 6.18. You will then determine the performance of the resulting circuit.
- a. In problem 24 you determined which gate (1 or 2) suffers the most from charge sharing. Add a single 2/0.25 PMOS precharge transistor (with its gate driven by the clock ϕ and its source connected to V_{DD}) to one of the nodes in that gate to maximally reduce the charge-sharing effect. What effect (if any) will this addition have on the gate delay? Use SPICE to demonstrate that the additional transistor has eliminated charge sharing for the previously determined worst-case sequence of inputs.

Solution

The additional precharge transistor should charge the node that is shared by the A_1 and \bar{A}_1 transistor drains and the F transistor source. Assuming the gate delay is dominated by the precharge stage, this will reduce the gate delay by briefly aiding the precharging of gate 2. SPICE output with additional precharge transistor.



- b. For the new circuit (including additional precharge transistor), find the sequence of inputs (spanning two clock cycles) that results in the worst-case delay through the circuit. Remember that precharging is another factor that limits the maximum clocking frequency of the circuit, so your input sequence should address the worst-case precharging delay.


Solution

The worst-case delay results from $A = B$ for two consecutive cycles. This results in the maximum charging and discharging of the internal nodes

- c. Using SPICE on the new circuit and applying the sequence of inputs found in part (b), find the maximum clock frequency for correct operation of the circuit. Remember that the precharge cycle must be long enough to allow all precharged nodes to reach ~90% of their final values before evaluation begins. Also, recall that the inputs (A , B and their complements) should not begin changing until the clock signal has reached 0 V (precharge phase), and they should reach their final values before the circuit enters the evaluation phase.


Solution

The maximum clock frequency is ~4.4 GHz.

 

26. [C, None, 4.2–3] For this problem, refer to the layout of Figure 6.19.
 a. Draw the schematic corresponding to the layout. Include transistor sizes.

Solution

 

- b. What logic function does the circuit implement? To which logic family does the circuit belong?

Solution

The circuit implements $\text{Out} = \overline{A+BC}$. It is in the pseudo NMOS family.

- c. Does the circuit have any advantages over fully complementary CMOS?

Solution

The circuit uses less area than a fully complementary CMOS implementation.

- d. Calculate the worst-case V_{OL} and V_{OH} .

Solution

$V_{OH} = V_{DD} = 2.5V$. To find V_{OL} , assume that we can combine M_B and M_C into one NMOS with $W/L = 0.75/0.25$. Then the worst case V_{OL} occurs when $A=0$ and the combined BC NMOS is on. Assume that V_{OL} is less than V_{DSATn} . Then the NMOS device is in the linear region. The PMOS device will be velocity saturated. Equating the currents at the output gives:

$$k'_p \cdot \frac{W}{L} \cdot V_{DSAT} \cdot (V_{GT} - 0.5V_{DSAT}) \cdot (1 + \lambda V_{DS}) + k'_n \cdot \frac{W}{L} \cdot V_o \cdot (V_{GT} - 0.5V_o) \cdot (1 + \lambda V_o) = 0$$

The only unknown in this 3rd order polynomial is V_o . Solving for V_o gives $V_{OL} = 51.2\text{mV}$

- e. Write the expressions for the area and perimeter of the drain and source for all of the FETs in terms of λ . Assume that the capacitance of shared diffusions divides evenly between the sharing devices. Copy the layout into Magic, extract and simulate to find the worst-case t_{pHL} time. For what input transition(s) does this occur? Name all of the parasitic capacitances that you would need to know to calculate this delay by hand (you do not need to perform the calculation).

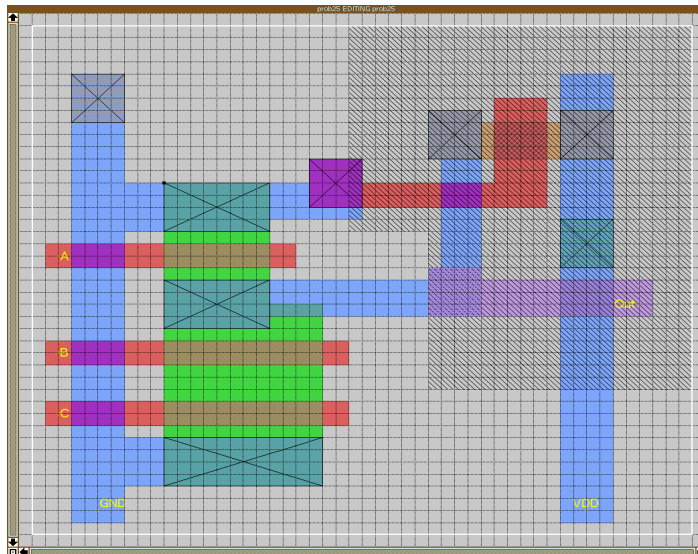


Figure 6.19 Layout of complex gate.

Solution

Call the PMOS device P, and name the other devices by their input signal.

$$AD_P = AS_P = 19\lambda^2. PD_P = PS_P = 15\lambda.$$

$$AS_A = 40\lambda^2. PS_A = 18\lambda.$$

$$AD_A = (3 \times 8 + 3 \times 12) \lambda^2 / 2 = 30 \lambda^2. PD_A = 16 \lambda / 2 = 8 \lambda .$$

$$AD_B = AD_A. PD_B = PD_A.$$

$$AS_B = 36 \lambda^2 / 2 = 18 \lambda^2. PS_B = 6 \lambda / 2 = 3 \lambda .$$

$$AD_C = AS_B. PD_C = PS_C.$$

$$AS_C = 60 \lambda^2. PS_C = 22 \lambda .$$

We can narrow the number of transitions to look at for determining the worst case t_{pHL} . The worst case capacitance occurs when the internal node between M_B and M_C is charged up to V_{DD} . Then the worst case delay will occur when either M_A or the M_B, M_C pair discharges this capacitance. If the series devices are doing the discharging, we need to consider the case where M_B is initially on and where M_B is initially off.

The simulation shows that the worst-case transition occurs over three cycles: ABC = 010 to 000 to 011 produces the worst-case t_{pHL} . This is worse than when MA discharges the node (ABC = 010 to 110) or when MB is initially on (ABC = 010 to 011).

We could calculate t_{pHL} using either the equivalent resistance method or the average current method. In either case, C_L would include the following parasitic capacitances:

$$C_{GDPMOS} + C_{DBPMOS} + C_{GDA}(\text{no Miller effect b/c input not changing}) + C_{DBA} + C_{GDB} + C_{DBB} + C_{GSB} + C_{GDC} + C_{DBC}.$$

27. [E, None, 4.4] Derive the truth table, state transition graph, and output transition probabilities for a three-input XOR gate with independent, identically distributed, uniform white-noise inputs.

Solution

The truth table of a three-input XOR gate is:

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Table 1: Truth table

As the inputs are independent, identically distribute, uniform white noise, each of the possible combinations of three input values, has a probability equal to 1/8. From the table, the probability of having the output equal to 0 is $p_0 = 0.5$. In the same way

28. [C, None, 4.4] Figure 6.20 shows a two-input multiplexer. For this problem, assume independent, identically-distributed uniform white noise inputs.
 a. Does this schematic contain reconvergent fan-out? Explain your answer.

Solution

This schematic has reconvergent fan-out because both inputs of the or gate depend on the value of S.

- b. Find the exact signal (P_1) and transition ($P_{0 \rightarrow 1}$) formulas for nodes X, Y, and Z for: (1) a static, fully complementary CMOS implementation, and (2) a dynamic CMOS implementation.

 


Figure 6.20 Two-input multiplexer

Solution

Assuming a fully complementary CMOS implementation:

X is the output of an AND gate with independent, identically-distributed uniform white noise inputs. As only when both inputs are equal to 1 the output is 1, $P_1 = 0.25$. On the other hand $P_{0 \rightarrow 1} = P_0 P_1 = 0.25(1 - 0.25) = 0.1875$.

Y is also the output of an AND gate with independent, identically distributed uniform white noise inputs. The analysis is the same as with X.

If we represent the truth table of the schematic we will see that $P_1 = 0.5$. Then $P_{0 \rightarrow 1} = P_0 P_1 = 0.5(1 - 0.5) = 0.25$.

Assuming a dynamic CMOS implementation:

In the same way as before, for X, $P_1 = 0.25$. In order to obtain the transition probability, an n-tree dynamic gate will be assumed. In this case: $P_{0 \rightarrow 1} = P_0 = 0.75$.

The analysis for Y is equal to the analysis for X.

For Z, using the truth table of the schematic we obtain, again, $P_1 = 0.5$. For the transition probability, it will be assumed that a np-CMOS structure is used. Then, Z is the output of a p-tree dynamic gate. Then: $P_{0 \rightarrow 1} = P_1 = 0.5$.

29. [M, None, 4.4] Compute the switching power consumed by the multiplexer of Figure 6.20, assuming that all significant capacitances have been lumped into the three capacitors shown in the figure, where $C = 0.3$ pF. Assume that $V_{DD} = 2.5$ V and independent, identically-distributed uniform white noise inputs, with events occurring at a frequency of 100 MHz. Perform this calculation for the following:

- a. A static, fully-complementary CMOS implementation

Solution

Switching power is:

$$P_{SW} = \alpha \cdot f \cdot C \cdot V_{DD}^2 = (\alpha_{X0 \rightarrow 1} + \alpha_{Y0 \rightarrow 1} + \alpha_{Z0 \rightarrow 1}) \cdot f \cdot C \cdot V_{DD}^2$$

We calculated in Problem 27 the probabilities of a 0->1 transition for each node: $P_{0 \rightarrow 1}$ for X and Y is 0.1875 and $P_{0 \rightarrow 1}$ for Z is 0.25.

Thus, $P_{SW} = (2 \cdot 0.1875 + 0.25) \cdot 100 \text{ MHz} \cdot 0.3 \text{ pF} \cdot 2.5^2 = 117.2 \text{ uW}$.

- b. A dynamic CMOS implementation

Solution

In Problem 27 for a dynamic np-CMOS gate, we calculated the probabilities: $P_{0 \rightarrow 1}$ for X and Y is 0.75 and $P_{0 \rightarrow 1}$ for Z is 0.5. Thus, $P_{SW} = (2*0.75+0.5)*100\text{MHz}*0.3\text{pF}*2.5^2 = 375\text{uW}$.

30. For the circuit shown Figure 6.21 ignore DIBL and $S=100\text{mV/decade}$.
- What is the logic function implemented by this circuit? Assume that all devices (M1-M6) are $0.5\mu\text{m}/0.25\mu\text{m}$.

Solution
 $\overline{A(B+C)}$

- Let the drain current for each device (NMOS and PMOS) be $1\mu\text{A}$ for NMOS at $V_{GS} = V_T$ and PMOS at $V_{SG} = V_T$. What input vectors cause the worst case leakage power for each output value? Explain (state all the vectors, but do not evaluate the leakage).

Solution

When the output is high, the worst-case leakage occurs when two transistors leak in parallel: $ABC = 100$. When the output is low, the worst-case leakage also occurs when two transistors leak in parallel: $ABC = 110$ or $ABC = 101$.

- Suppose the circuit is active for a fraction of time d and idle for $(1-d)$. When the circuit is active, the inputs arrive at 100 MHz and are uniformly distributed ($\Pr_{(A=1)} = 0.5$, $\Pr_{(B=1)} = 0.5$, $\Pr_{(C=1)} = 0.5$) and independent. When the circuit is in the idle mode, the inputs are fixed to one you chose in part (b). What is the duty cycle d for which the active power is equal to the leakage power?

 


Figure 6.21 CMOS logic gate.

Solution

$$d * P_{\text{active}} = (1-d) P_{\text{leakage}} \cdot P_{\text{active}} = \alpha_{0 \rightarrow 1} * f * C_L * V_{DD}^2 = (3/8 * 5/8) * (100 * 10^6) * (50 * 10^{-15}) * (2.5^2) = 7.3 \mu \text{ W}$$

$$P_{\text{leakage}} (ABC = 100) = V_{DD} * 2 * I_{\text{leakM1}} = 5 * I_o * 10^{\frac{-V_T}{S}} = 5 * 1 \mu \text{ A} * 10^{\frac{-0.43}{0.1}} = 251 \text{ pW}$$

Plugging the power numbers into the activity equation and solving for d gives $d = 3.4 * 10^{-8}$.

DESIGN PROJECT

Design, lay out, and simulate a CMOS four-input XOR gate in the standard 0.25 micron CMOS process. You can choose any logic circuit style, and you are free to choose how many stages of logic to use: you could use one large logic gate or a combination of smaller logic gates. The supply voltage is set at 2.5 V! Your circuit must drive an external 20 fF load in addition to whatever internal parasitics are present in your circuit.

The primary design objective is to minimize the propagation delay of the worst-case transition for your circuit. The secondary objective is to minimize the area of the layout. At the very worst, your design must have a propagation delay of no more than 0.5 ns and occupy an area of no more than 500 square microns, but the faster and smaller your circuit, the better. Be aware that, when using dynamic logic, the precharge time should be made part of the delay.

The design will be graded on the magnitude of $A \times t_p^2$, the product of the area of your design and the square of the delay for the worst-case transition.