

Digital Design

Chapter 7: Physical Implementation


Slides to accompany the textbook *Digital Design, with RTL Design, VHDL, and Verilog*, 2nd Edition,
by Frank Vahid, John Wiley and Sons Publishers, 2010.
<http://www.ddvahid.com>

Copyright © 2010 Frank Vahid

Instructors of courses requiring Vahid's *Digital Design* textbook (published by John Wiley and Sons) have permission to modify and use these slides for customary course-related activities, subject to keeping this copyright notice in place and unmodified. These slides may be posted as unanimated pdf versions on publicly-accessible course websites. PowerPoint source (or pdf with animations) may **not** be posted to publicly-accessible websites, but may be posted for students on internal protected sites or distributed directly to students by other electronic means. Instructors may make printouts of the slides available to students for a reasonable photocopying charge, without incurring royalties. Any other use requires explicit permission. Instructors may obtain PowerPoint source or obtain special use permissions from Wiley – see <http://www.ddvahid.com> for information.

Introduction

 - A digital circuit design is just an idea, perhaps drawn out
- Need to implement the circuit on a physical device
 - How do we get from *design* to *IC* (integrated circuit, aka chip)?



(a) Digital circuit design




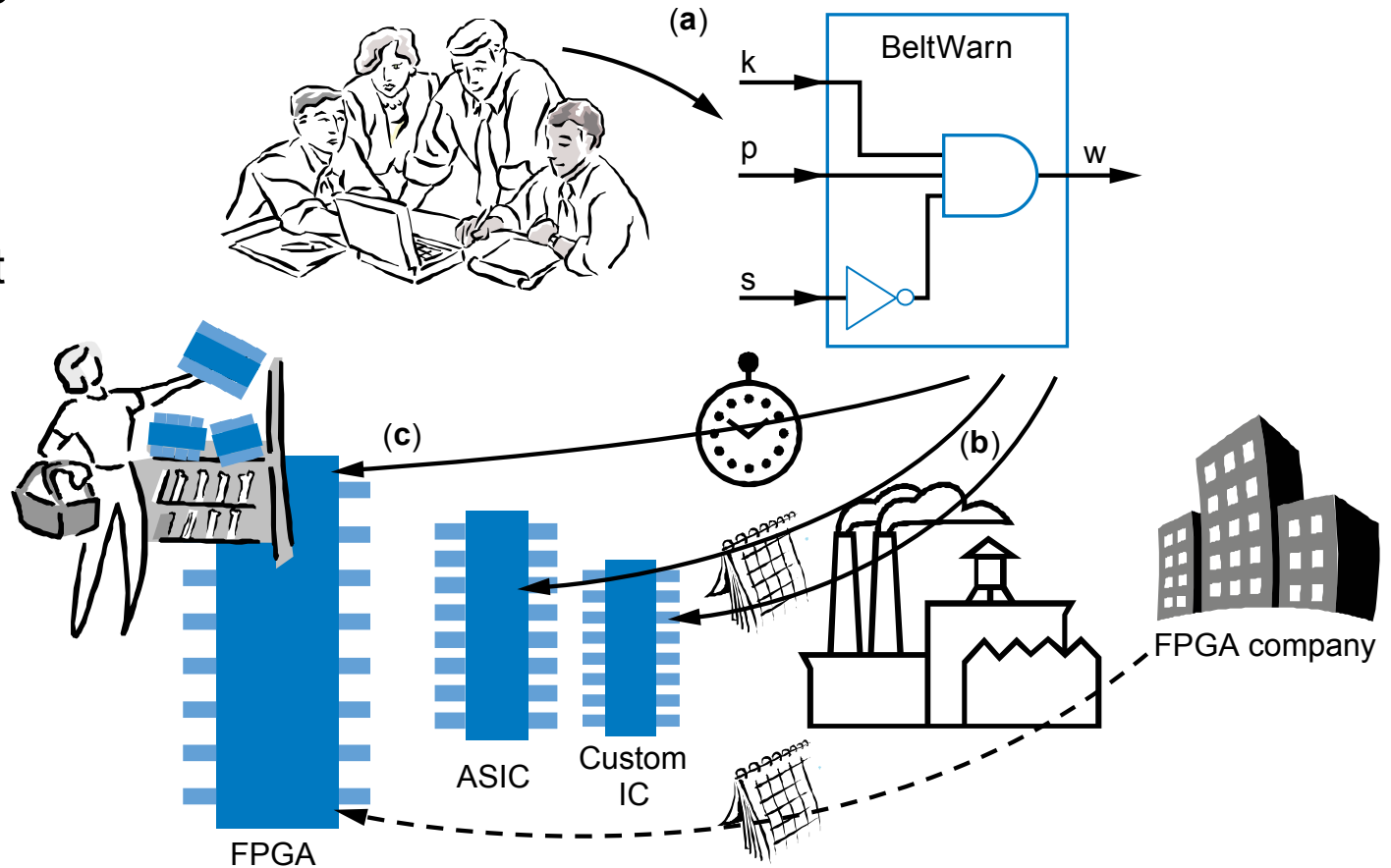(b) Physical implementation on an IC




IC Types, Design Flows

- Many *IC types*
 - Some fast but expensive
 - Others cheaper but slower
- Types also differ in *design flow*
 - Some long time
 - Others off-the-shelf
- Now discuss popular types




Manufactured IC Technologies

- Designer can manufacture a new IC
 - Months of time, millions of dollars
- (1) *Full-custom IC*
 - Convert design to *layout*: Describes location/size of every transistor on IC
 - Typically created by CAD tools
 - Send to fabrication plant (fab) to convert layout to actual IC
 - Photographic, laser, chemical equipment
 - Hard!
 - Fab setup costs ("non-recurring engineering", or *NRE*) high—millions of dollars
 - Long fab time (months)
 - Error prone (several "respins")
 - Uncommon
 - Only special ICs that demand the very best performance or the very smallest size/power

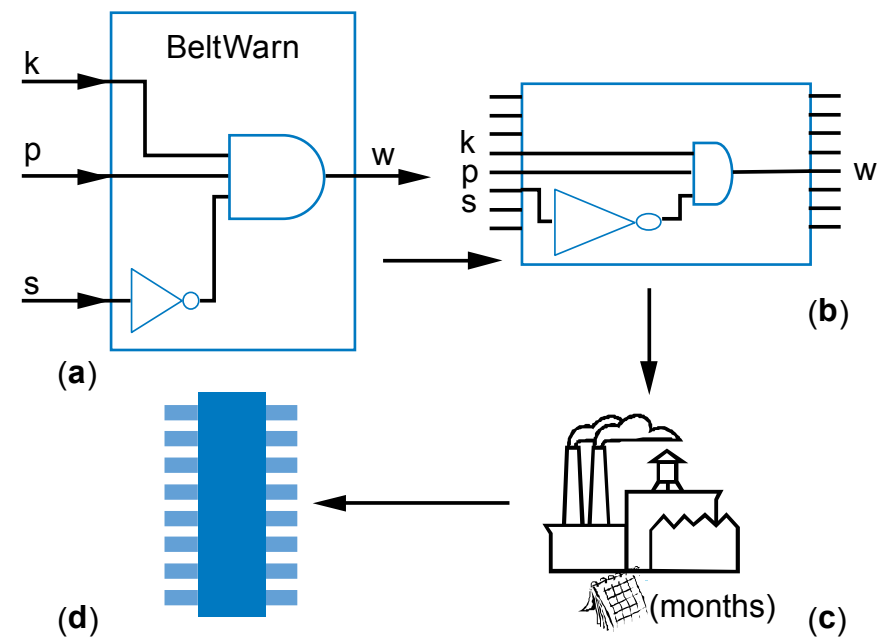


Manufactured IC Technologies—Standard Cell ASIC

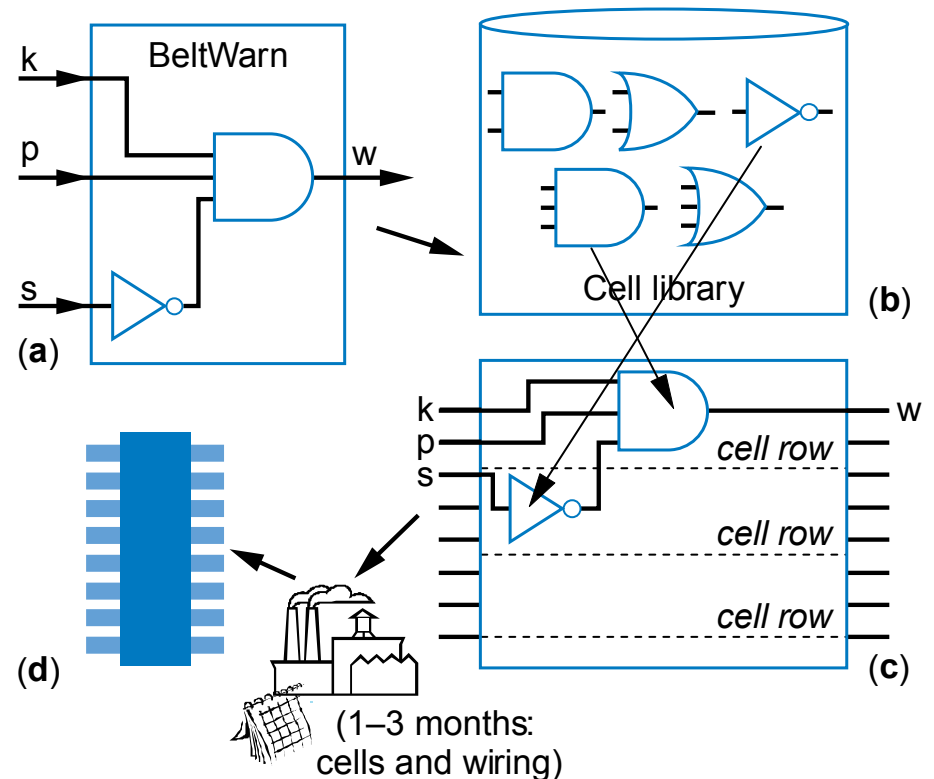- (2) Semicustom IC (ASIC)
 - "Application-specific" IC
 - (2a) Standard cell ASIC
 - Pre-layed-out standard-sized "cells" exist in library
 - Designer instantiates cells into pre-defined rows, and connects
 - Vs. full custom
 - Con: Bigger/slower circuit
 - Pro: Easier/faster to design/manufacture




Manufactured IC Technologies—Standard Cell ASIC

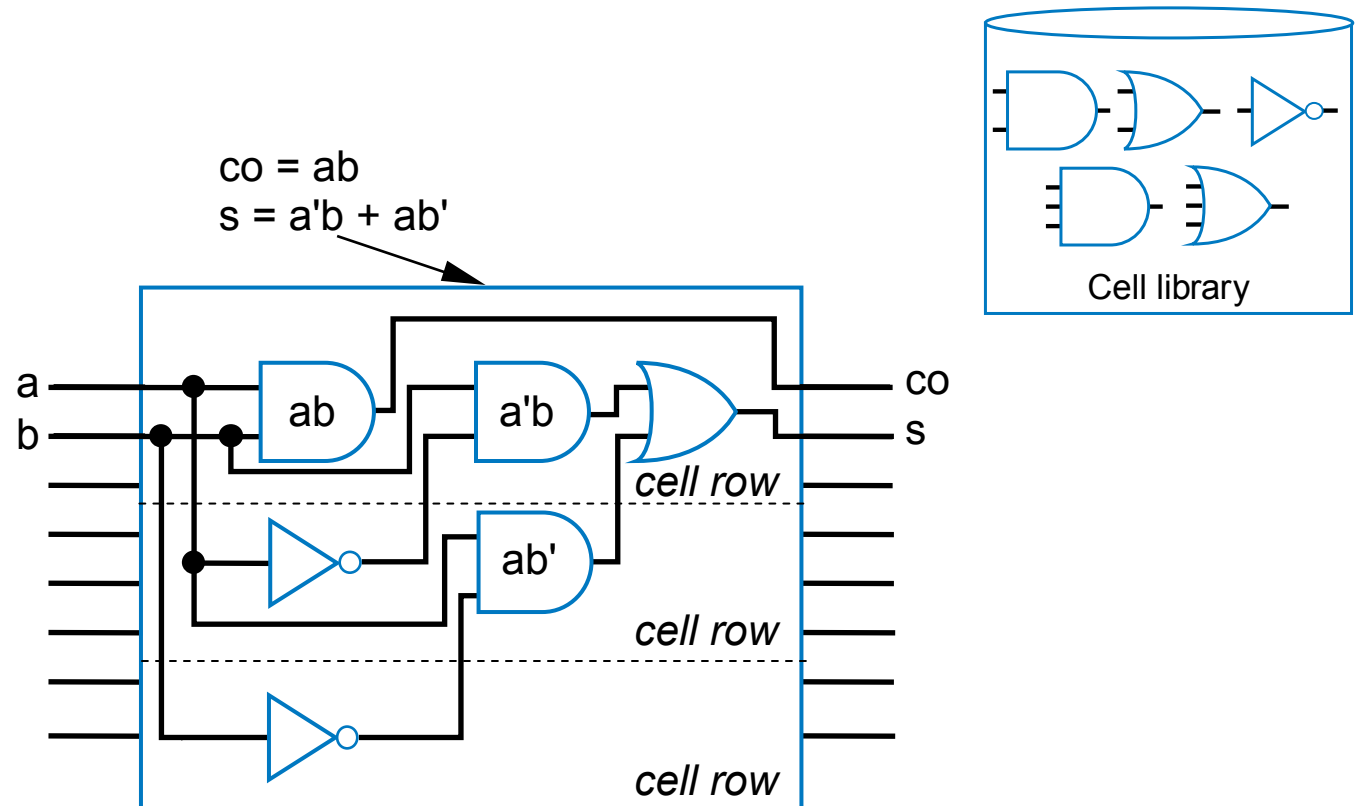- Example: Mapping half-adder to standard cell ASIC



Manufactured IC Technologies—Gate Array ASIC

 - (2b) Gate array ASIC
 - "Structured" ASIC
 - Array of gates already layed out on chip
 - Just need to wire them together
 - Vs. standard cell ASIC
 - Con: Even bigger/slower circuit
 - Pro: Even easier/faster to design/manufacture
 - Very popular




a





Manufactured IC Technologies—Gate Array ASIC

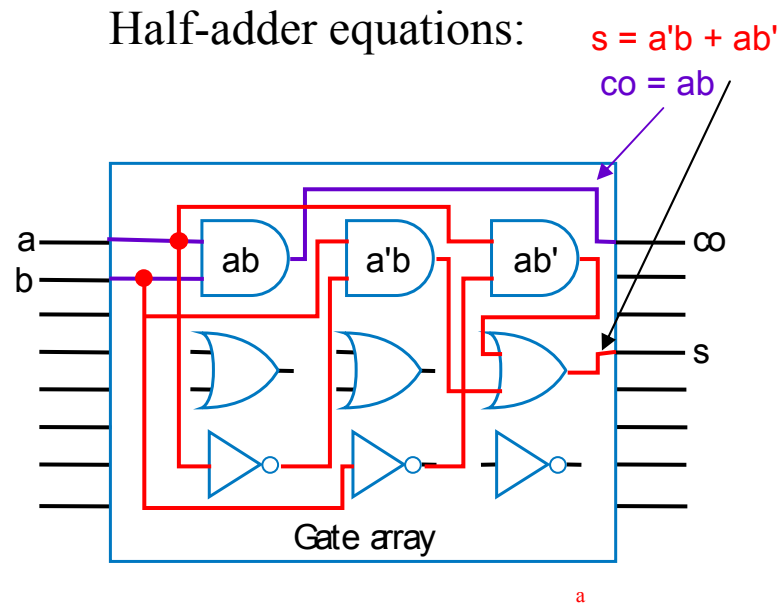- Example: Mapping a half-adder to a gate array ASIC




Implementing Circuits Using NAND Gates Only

  - Recall NAND/NOR more efficient than AND/OR
 - Gate array may have NANDs only
 - Std cell more efficient using NANDs
- NAND is a *universal gate*
 - Any circuit can be mapped to NANDs only
 - Each of AND, OR, and NOT can be converted to equivalent circuit of NANDs
- Convert AND/OR/NOT circuit to NAND-only circuit using mapping rules
 - After converting, remove double inversions




Inputs		Output		
x		a	b	F
0		0	0	1
1		1	1	0

a

 


a

 

a

Double inversion


 


a




Implementing Circuits Using NAND Gates Only


- Example: Half-adder

 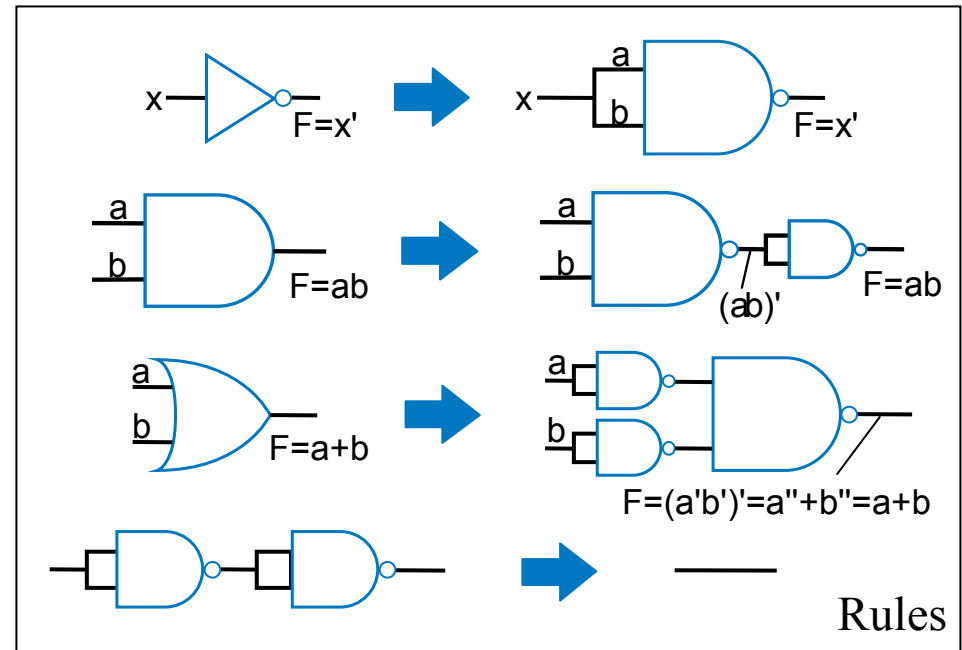

(a)

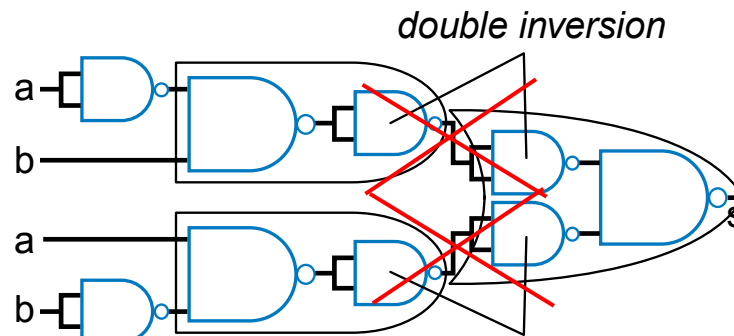

(b) double inversion

 


(c)




Implementing Circuits Using NAND Gates Only

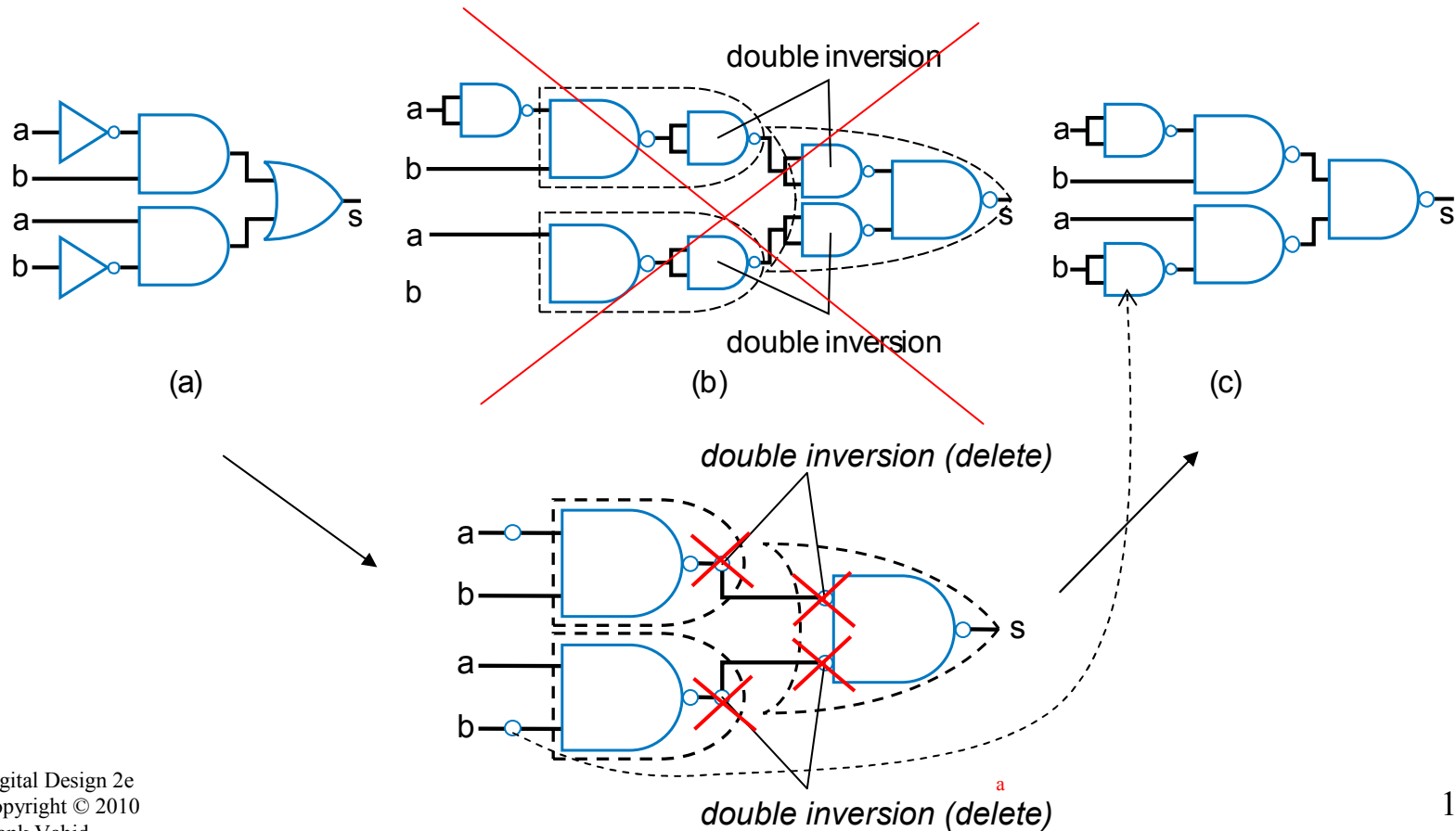- Shortcut when converting by hand
 - Use inversion bubbles rather than drawing inverters as 2-input NAND
 - Then remove double inversions as before




Implementing Circuits Using NOR Gates Only

 - NOR gate is also universal
- Converting AND/OR/NOT to NOR done using similar rules




Implementing Circuits Using NOR Gates Only

- Example: Half adder

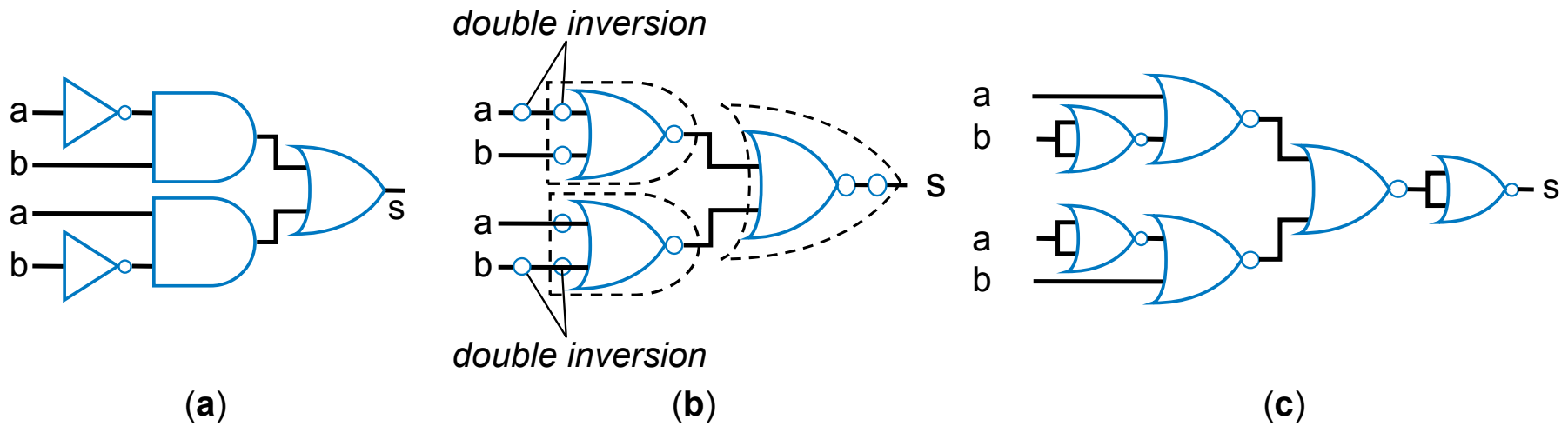



Implementing Circuits Using NOR Gates Only

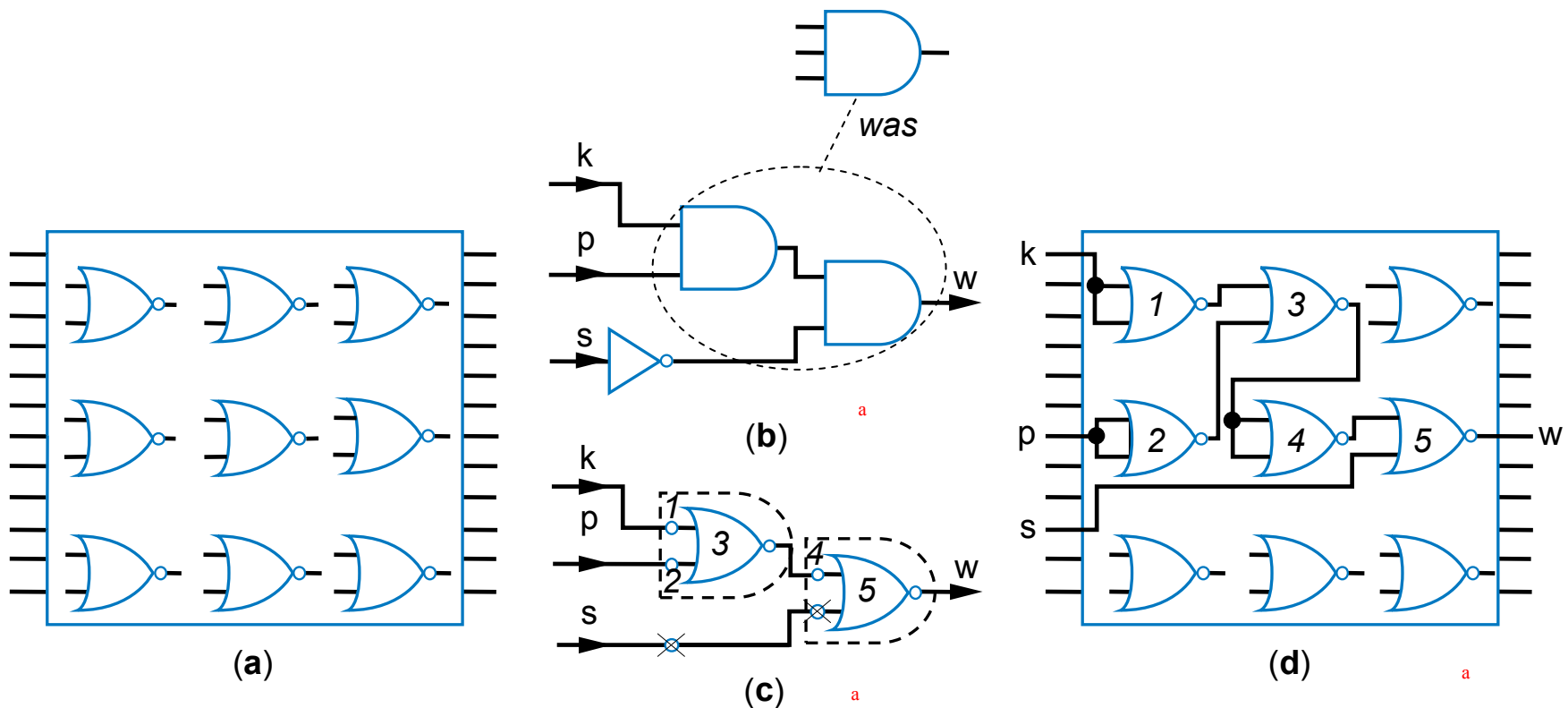- Example: Seat belt warning light on a NOR-based gate array
 - Note: if using 2-input NOR gates, first convert AND/OR gates to 2-inputs




Off-the-Shelf Programmable IC Type—FPGA

- Manufactured IC technologies require months to fabricate
 - Also large (million dollar) NRE costs
- *Programmable ICs* are pre-manufactured
 - User just downloads bits into device, in just seconds
 - Slower/bigger/more-power than manufactured ICs
 - But get it today, and no NRE costs
- Popular programmable IC—**FPGA**
 - "Field-programmable gate array"
 - Developed late 1980s
 - Though no "gate array" inside
 - Named when gate arrays were popular in 1980s
 - Programmable in the "field" (e.g, your lab) rather than requiring a fab

  


FPGA Internals: Lookup Tables (LUTs)

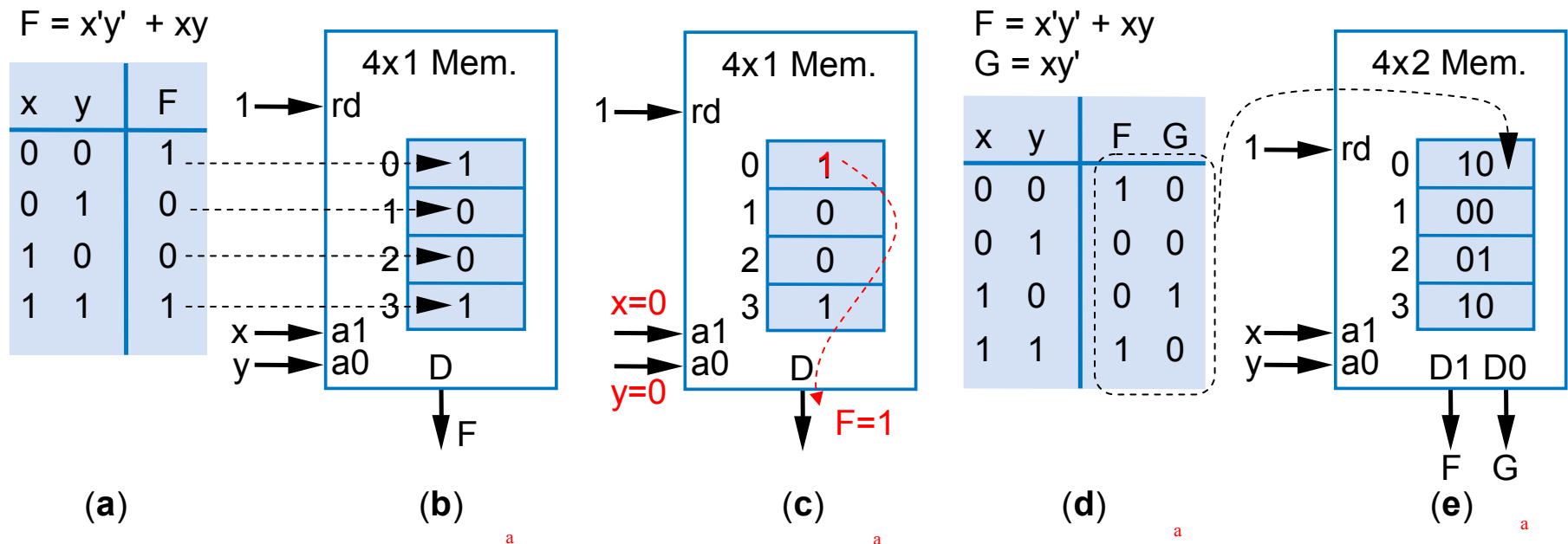- Basic idea: Memory can implement combinational logic
 - Ex: 2-address memory can implement 2-input logic
 - 1-bit wide memory – 1 function; 2-bits wide – 2 functions
- Such memory in FPGA known as *lookup table (LUT)*




Mapping a Combinational Circuit to a LUT

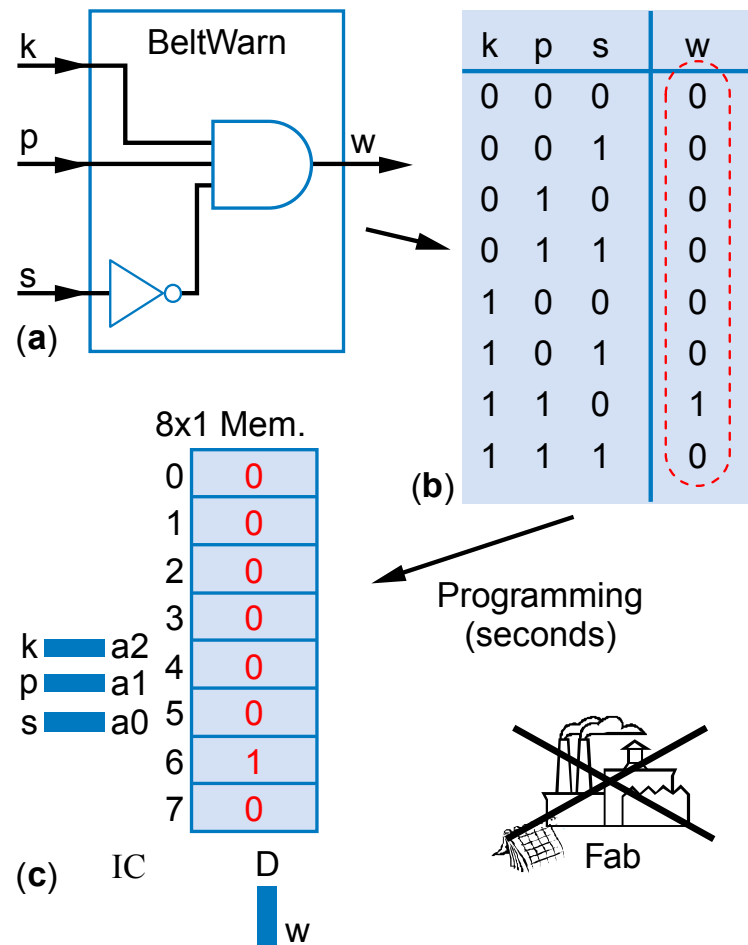- Example: Seat-belt warning light (again)



FPGAs More Efficient With Numerous Small LUTs

- Lookup tables become inefficient for more inputs
 - 3 inputs → only 8 words 8 inputs → 256 words 16 inputs → 65,536 words!
- FPGAs thus have numerous small (3, 4, 5, or even 6-input) LUTs
 - If circuit has more inputs, must partition circuit among LUTs
 - Ex: 9-input circuit more efficient on 8x1 mems rather than 512x1

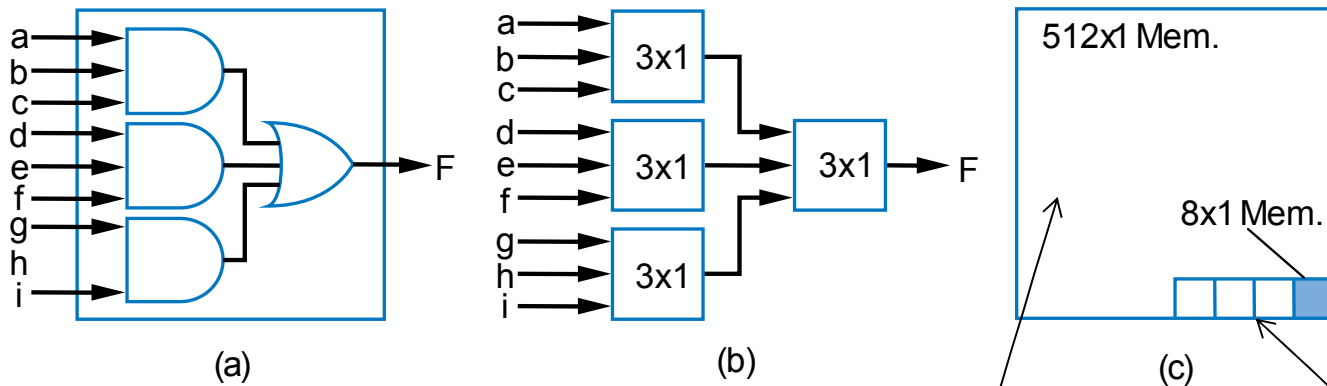

Original 9-input circuit


Partitioned among
3x1 LUTs

Requires only 4
3-input LUTs
(8x1 memories) –
much smaller than
a 9-input LUT
(512x1 memory)




Circuits Must be Partitioned among Small LUTs

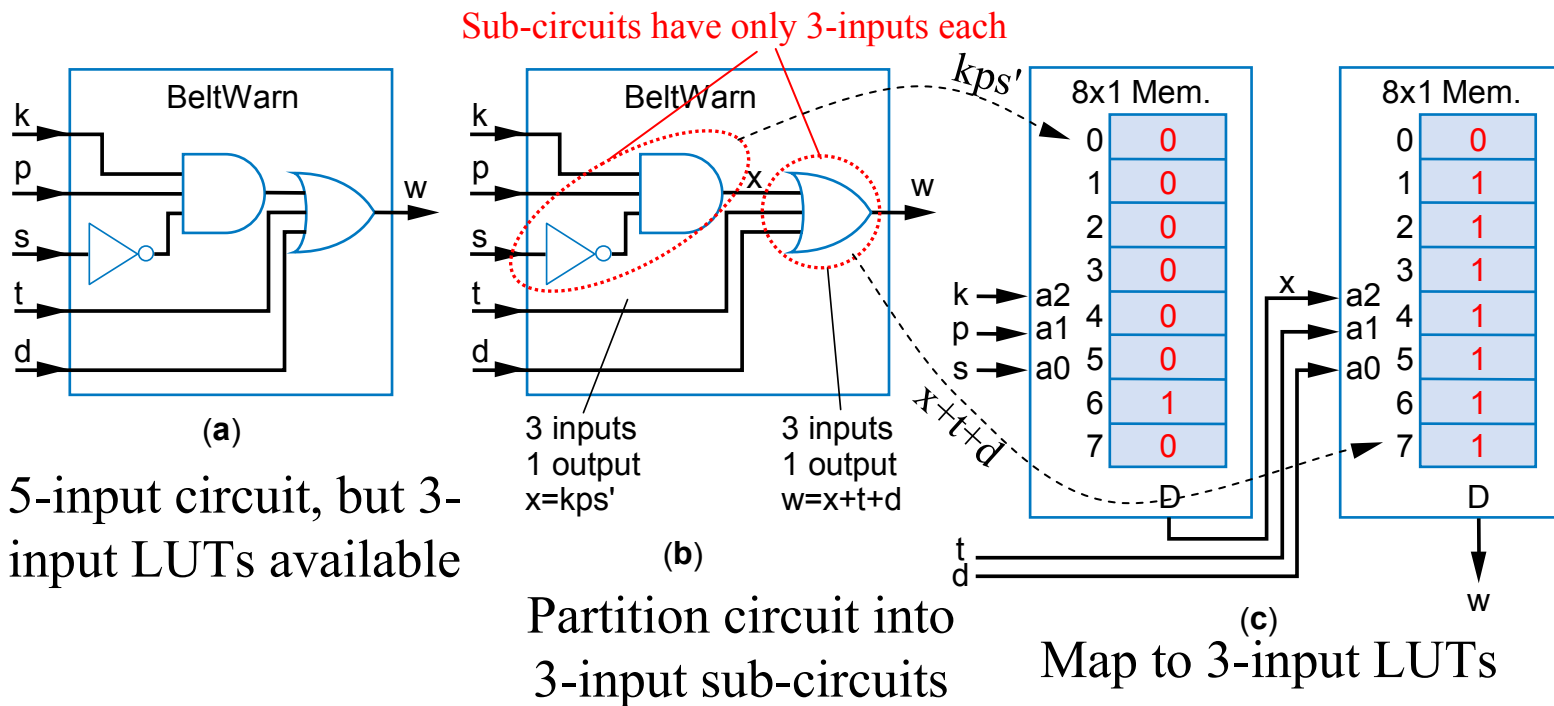- Example: Extended seat-belt warning light system
 - (Assume for now we can create any wires to/between LUTs)




Mapping a Circuit to 3x1 LUTs

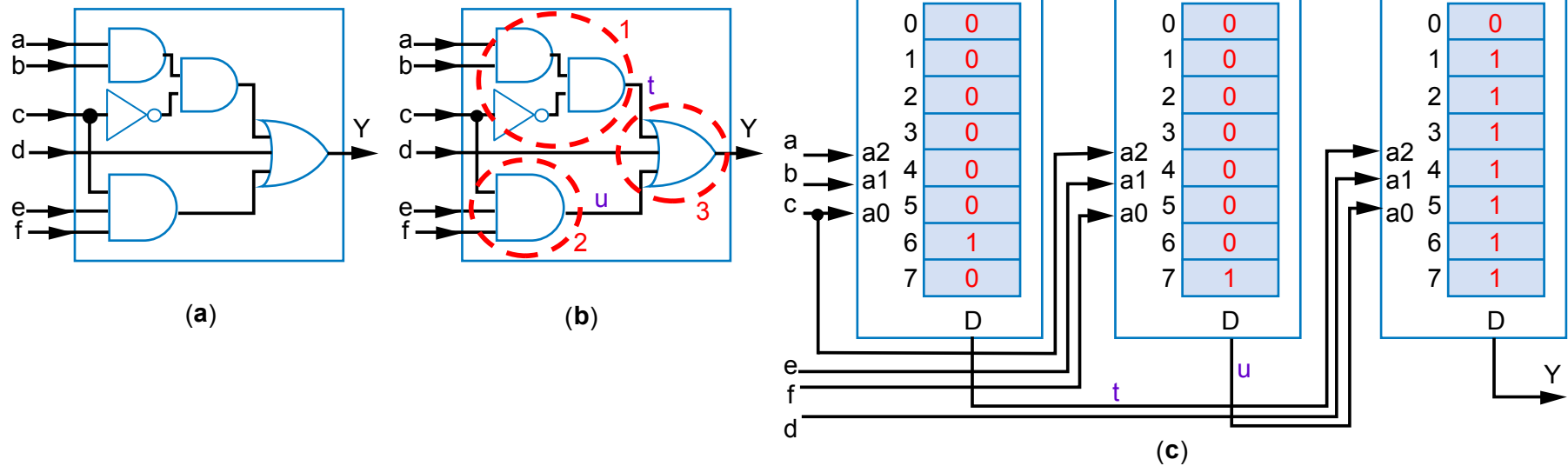


- Divide circuit into 3-input sub-circuits
- Map each sub-circuit to 3x1 LUT
- (Assume for now that we can create any wires to/between LUTs)



Underutilized LUTs are Common

 


(a)

 

(b)

Sub-circuit has only 2 inputs

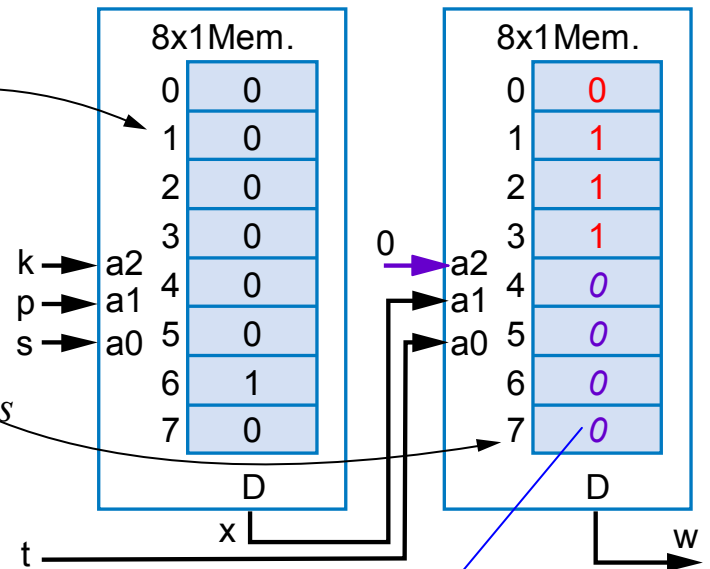


(c)

Italics: contents don't matter




Mapping to 3x2 LUTs

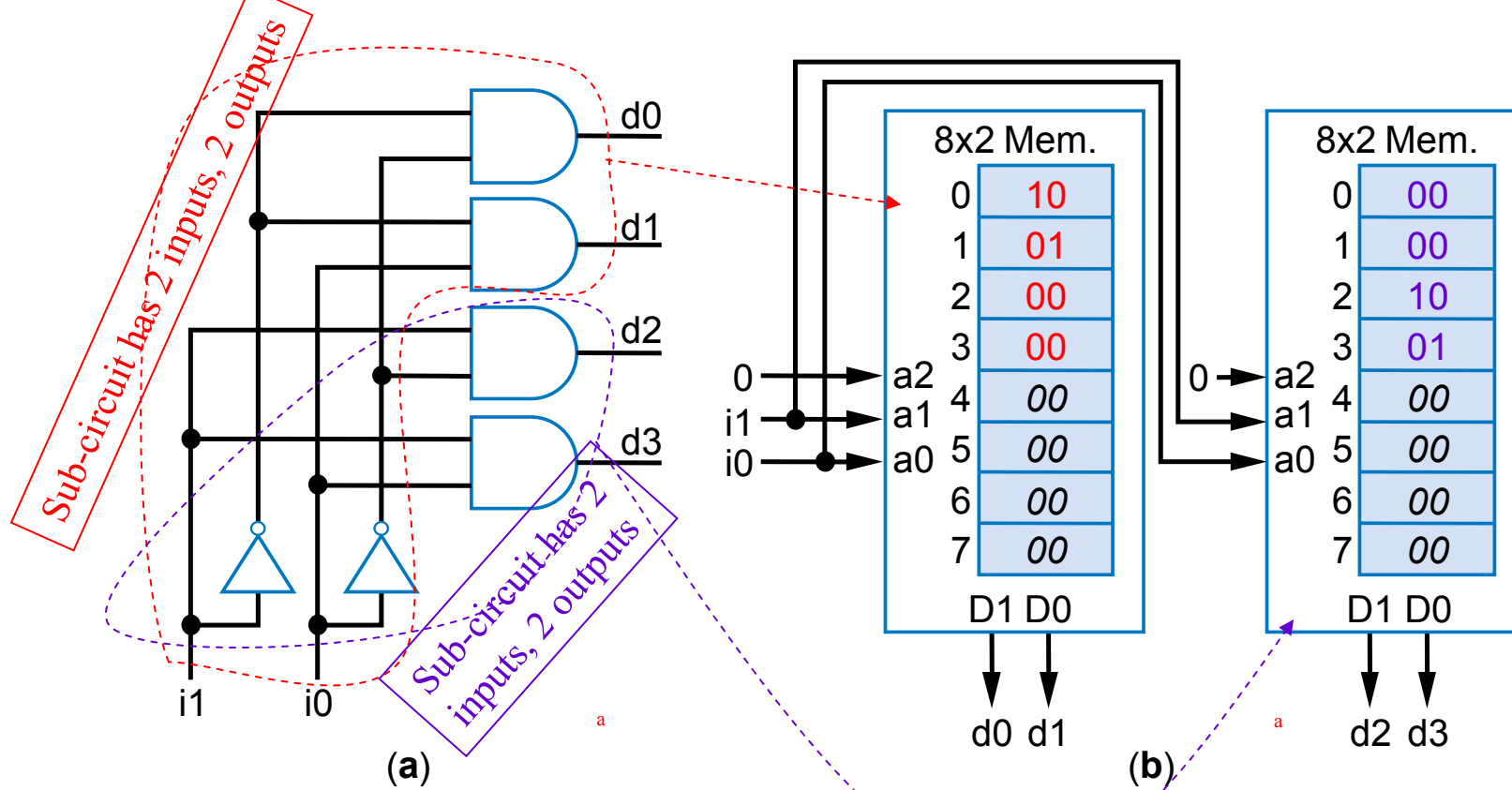- Example: Mapping a 2x4 decoder to 3-input 2-output LUTs



More Mapping Issues

 - Gate has more inputs than does LUT → Decompose gate first
- Sub-circuit has fewer outputs than LUT → Just don't use output



(Note: decomposed one 4-input AND into two smaller ANDs to enable partitioning into 3-input sub-circuits)


First column unused;
second column
implements AND

Second column unused;
first column implements
AND/OR sub-circuit




FPGA Internals: Switch Matrices

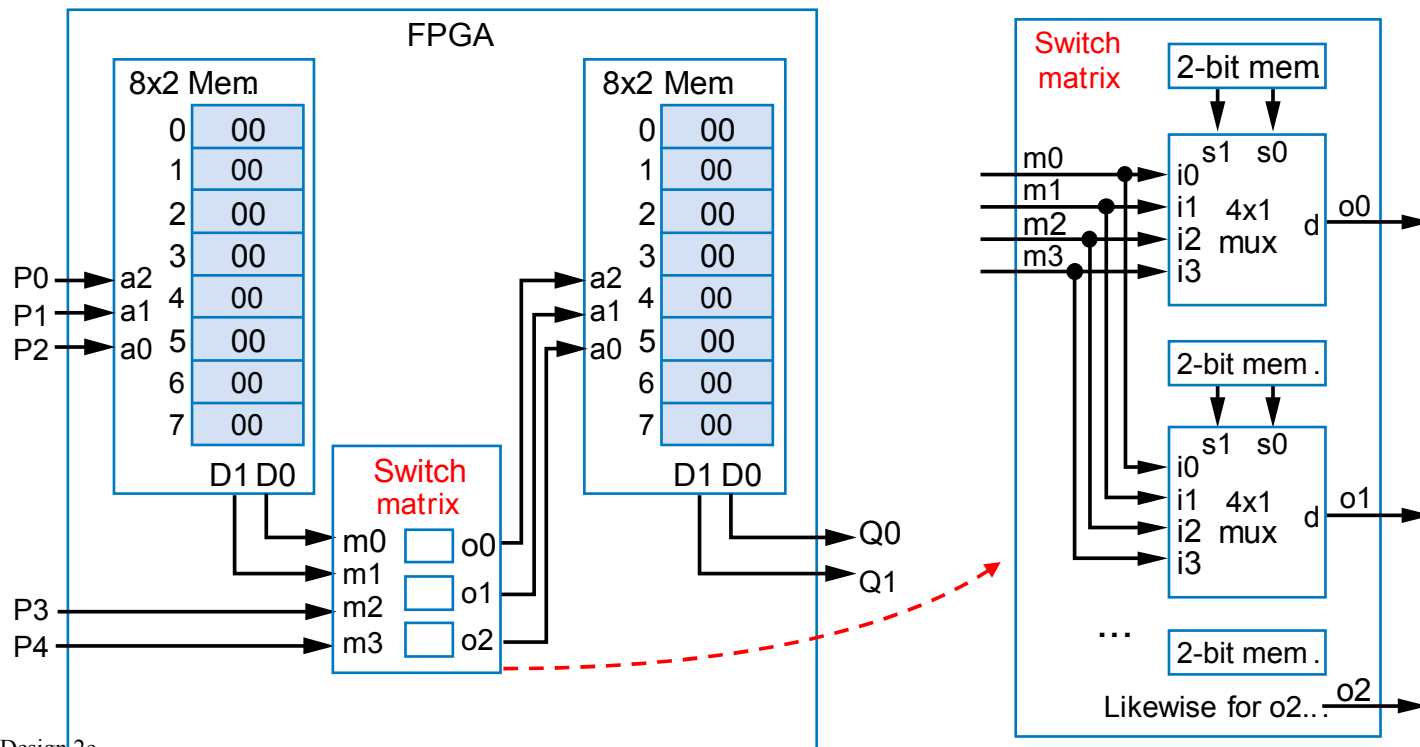- Previous slides had hardwired connections between LUTs
- Instead, want to program the connections too
- Use switch matrices (also known as programmable interconnect)
 - Simple mux-based version – each output can be set to any of the four inputs just by programming its 2-bit configuration memory




Ex: FPGA with Switch Matrix

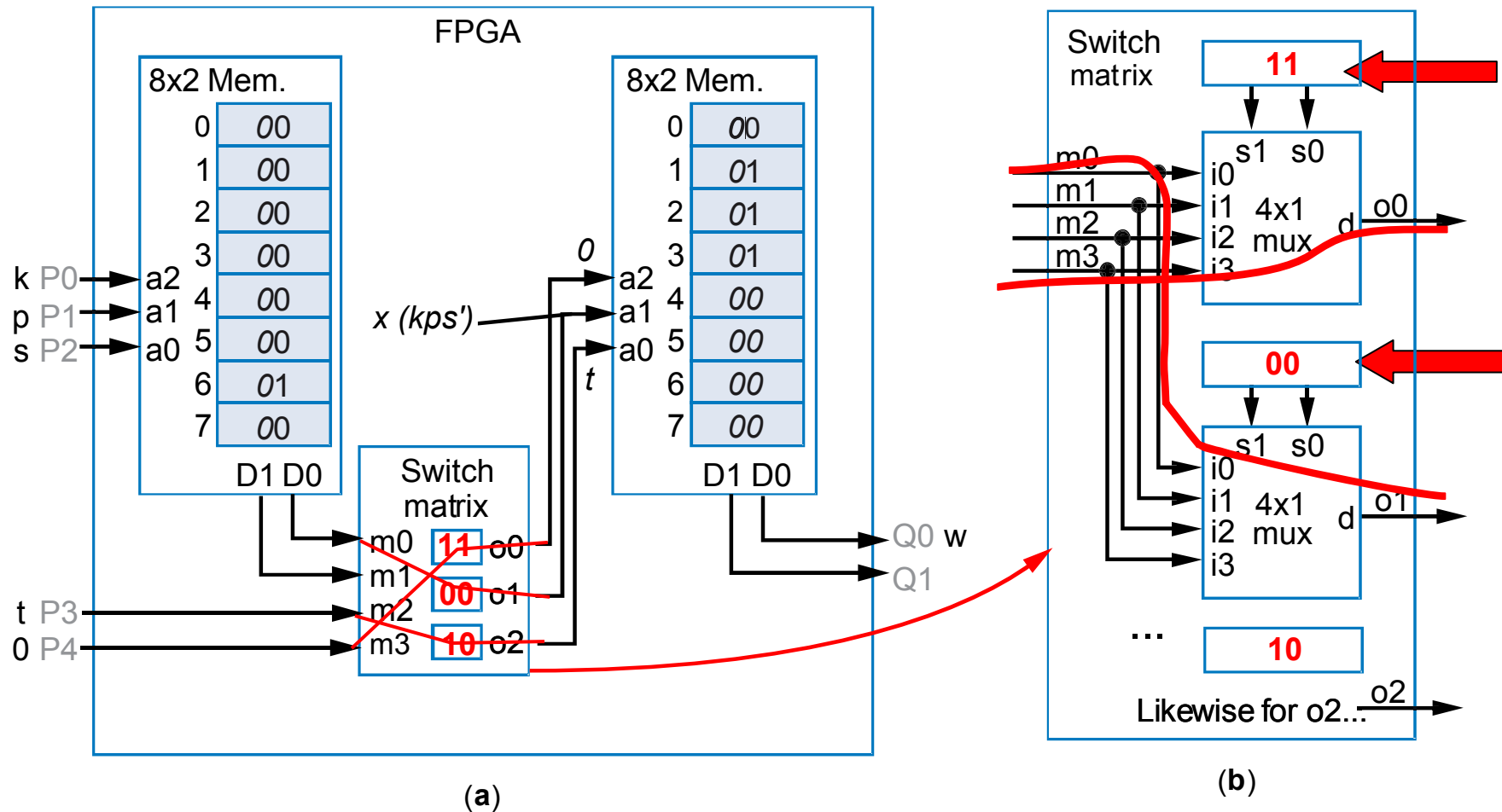- Mapping the extended seatbelt warning light circuit onto an FPGA with a switch matrix




Configurable Logic Blocks (CLBs)

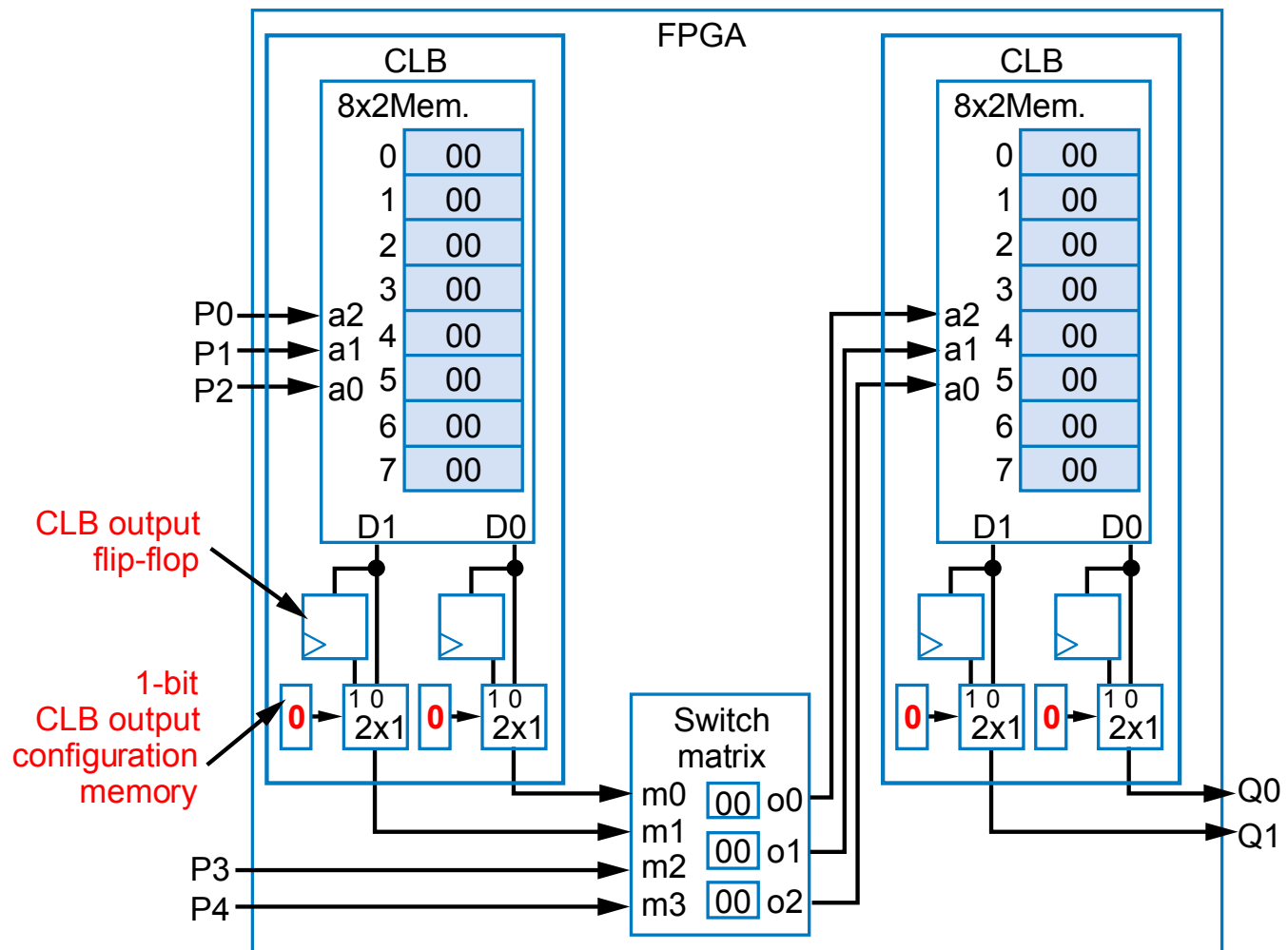- Include flip-flops to support sequential circuits
- Muxes programmed to output registered or non-registered LUT output




Sequential Circuited Mapped to FPGA

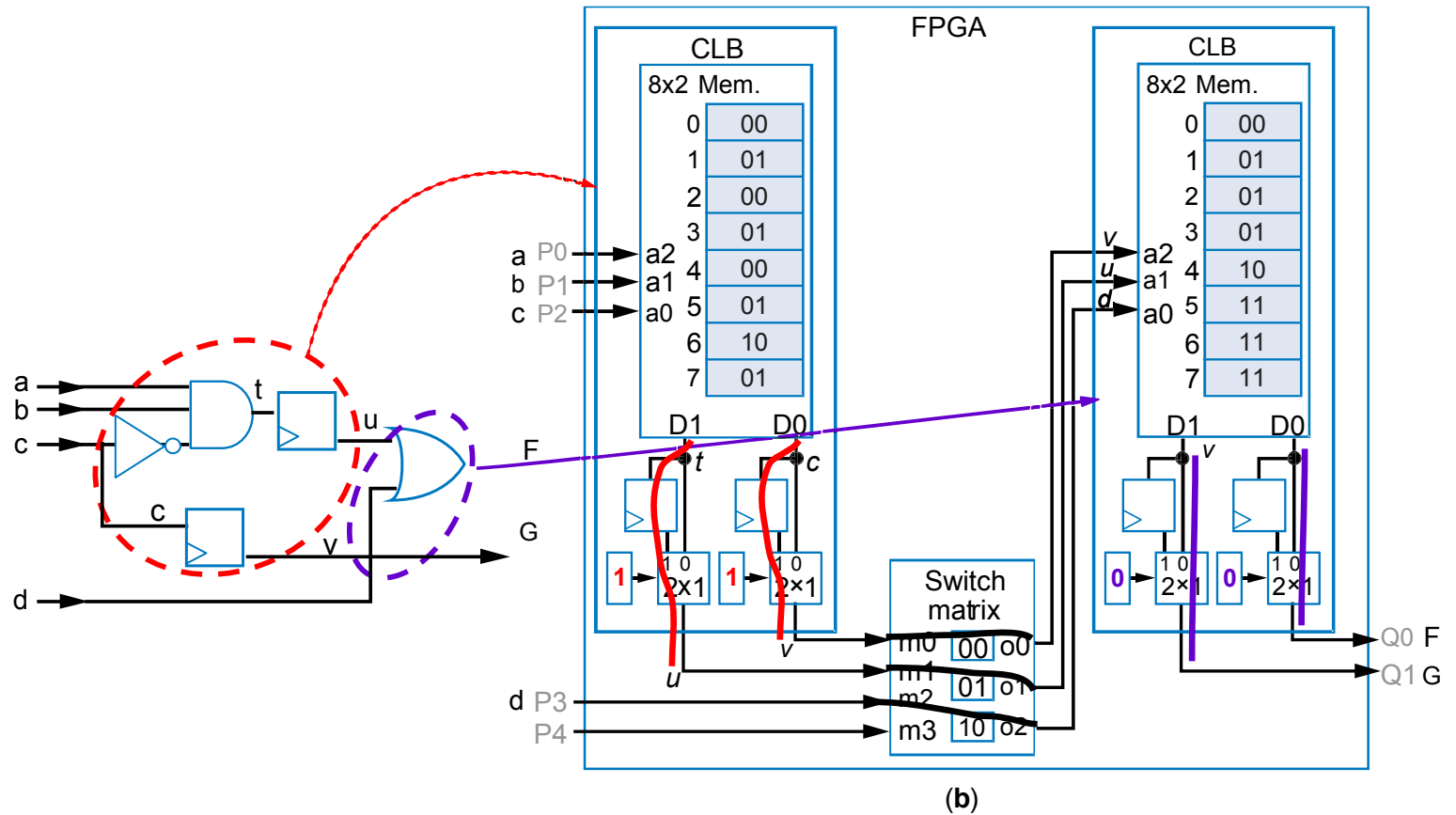

FPGA Internals: Overall Architecture

- Consists of hundreds or thousands of CLBs and switch matrices (SMs) arranged in regular pattern on a chip

*Represents channel with
tens of wires*

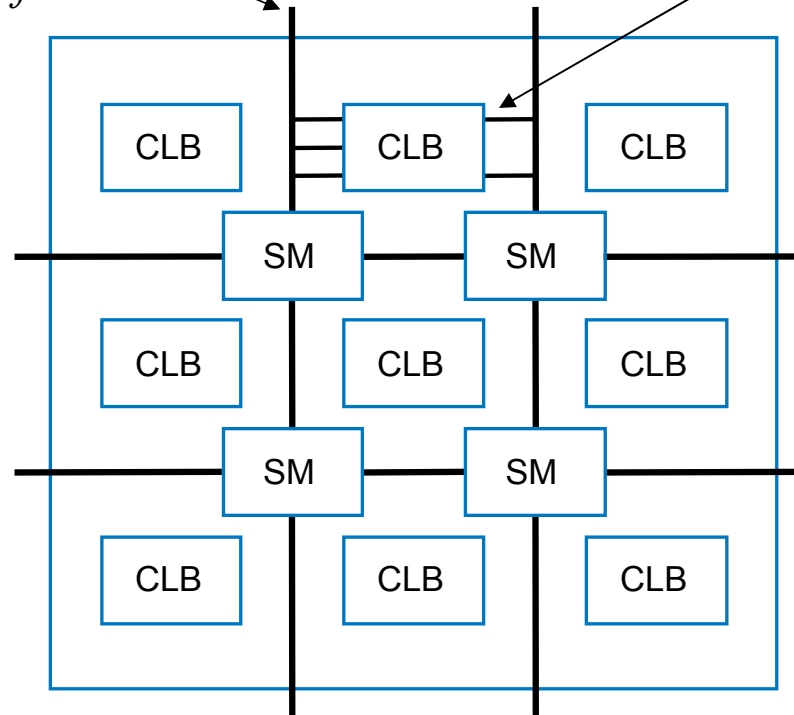


*Connections for just one
CLB shown, but all
CLBs are obviously
connected to channels*





Programming an FPGA

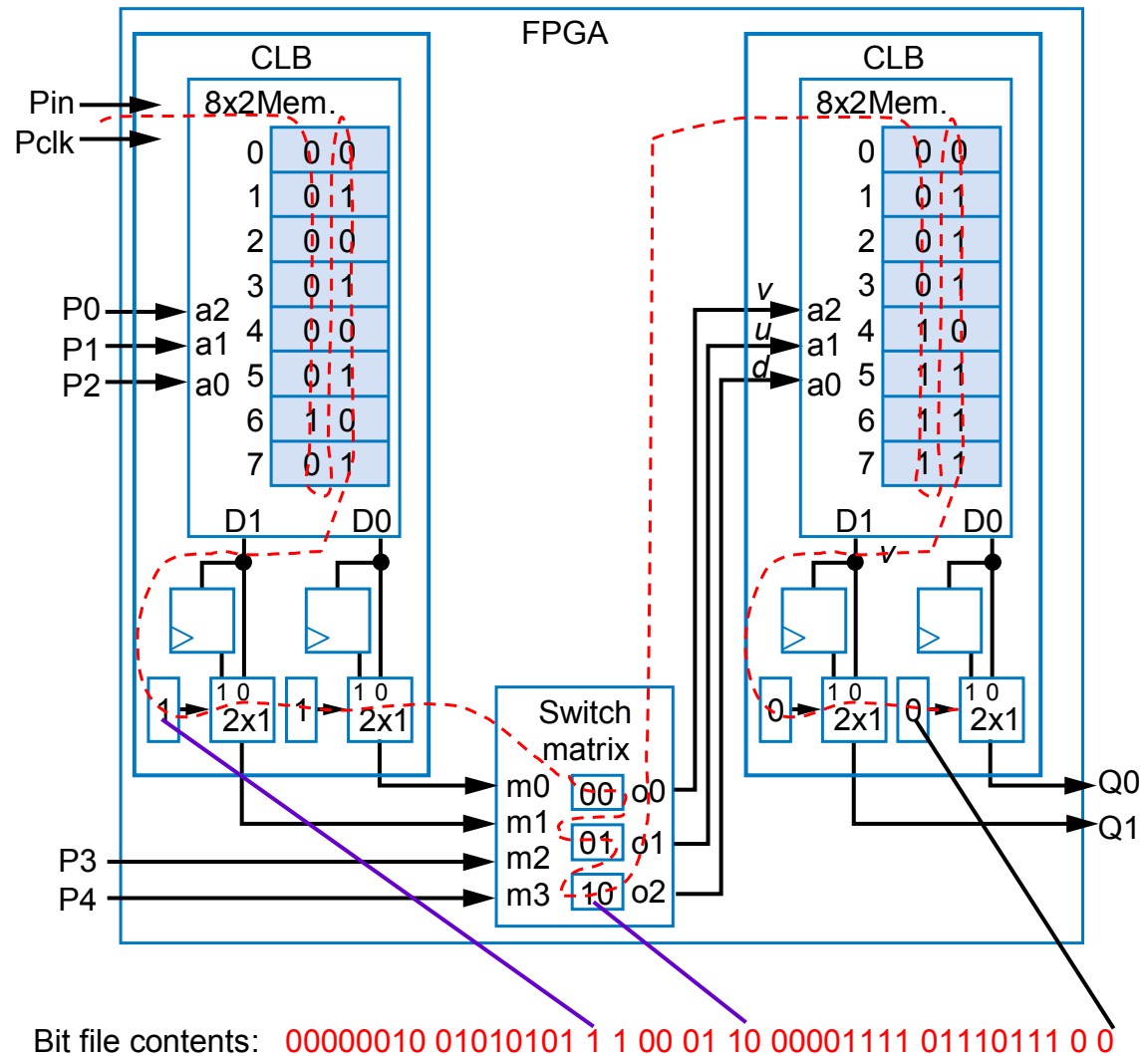- All configuration memory bits are connected as one big shift register
 - Known as *scan chain*
- Shift in the "*bit file*" of the desired circuit



Other Off-the-Shelf IC Types

  - Off-the-shelf logic (SSI) IC
 - Logic IC has a few gates, connected to IC's pins
 - Known as Small Scale Integration (SSI)
 - Popular logic IC series: 7400
 - Originally developed 1960s
 - Back then, each IC cost \$1000
 - Today, costs just tens of cents




7400-Series Logic ICs

TABLE 7.1: Commonly used 7400-series ICs.

Part	Description	Pins
74LS00	Four 2-input NAND	14
74LS02	Four 2-input NOR	14
74LS04	Six inverters	14
74LS08	Four 2-input AND	14
74LS10	Three 3-input NAND	14
74LS11	Three 3-input AND	14
74LS14	Six inverters (Schmitt trigger)	14
74LS20	Two 4-input NAND	14
74LS27	Three 3-input NOR	14
74LS30	One 8-input NAND	14
74LS32	Four 2-input OR	14
74LS74	Two D flip-flop, positive edge triggered, with preset and reset	14
74LS83	4-bit binary full-adder	16
74LS85	4-bit magnitude comparator	16

Source: www.digikey.com

 

Using Logic ICs


- Example: Seat belt warning light using off-the-shelf 7400 ICs
 - Option 1: Use one 74LS08 IC having 2-input AND gates, and one 74LS04 IC having inverters

TABLE 7.1: Commonly used 7400-series ICs.


Part	Description	Pins
74LS00	Four 2-input NAND	14
74LS02	Four 2-input NOR	14
74LS04	Six inverters	14
74LS08	Four 2-input AND	14
74LS10	Three 3-input NAND	14
74LS11	Three 3-input AND	14
74LS14	Six inverters (Schmitt trigger)	14
74LS20	Two 4-input NAND	14
74LS27	Three 3-input NOR	14
74LS30	One 8-input NAND	14
74LS32	Four 2-input OR	14
74LS74	Two D flip-flop, positive edge triggered, with preset and reset	14
74LS83	4-bit binary full-adder	16
74LS85	4-bit magnitude comparator	16

Source: www.digikey.com

(a) Desired circuit

 


(a)

 

(b)

(b) Decompose into 2-input AND gates

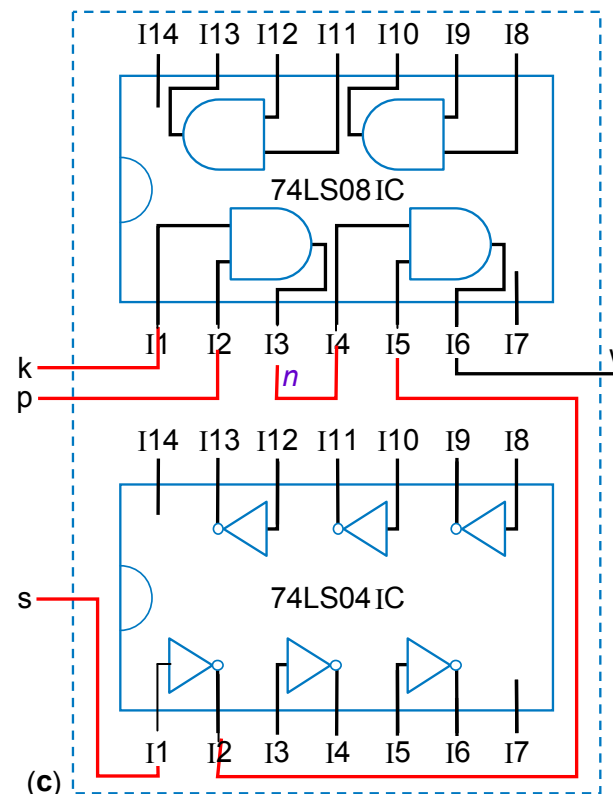

(c) Connect ICs to create desired circuit





Using Logic ICs

- Example: Seat belt warning light using off-the-shelf 7400 ICs
 - Option 2: Use a single 74LS27 IC having 3-input NOR gates


TABLE 7.1: Commonly used 7400-series ICs.

Part	Description	Pins
74LS00	Four 2-input NAND	14
74LS02	Four 2-input NOR	14
74LS04	Six inverters	14
74LS08	Four 2-input AND	14
74LS10	Three 3-input NAND	14
74LS11	Three 3-input AND	14
74LS14	Six inverters (Schmitt trigger)	14
74LS20	Two 4-input NAND	14
74LS27	Three 3-input NOR	14
74LS30	One 8-input NAND	14
74LS32	Four 2-input OR	14
74LS74	Two D flip-flop, positive edge triggered, with preset and reset	14
74LS83	4-bit binary full-adder	16
74LS85	4-bit magnitude comparator	16

Source: www.digikey.com

  

Converting to 3-input NOR gates

 


Connecting the pins to create the desired circuit






SPLD

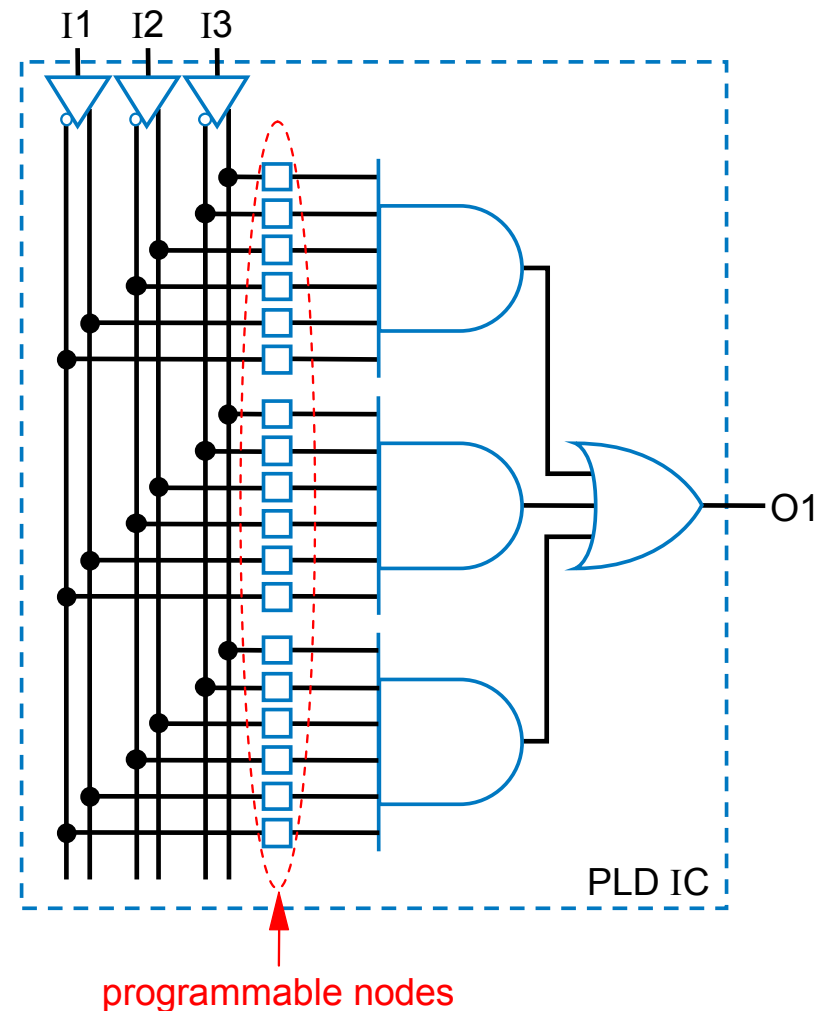- Simple Programmable Logic Devices (SPLDs)
 - Developed 1970s (thus, pre-dates FPGAs)
 - Prefabricated IC with large AND-OR structure
 - Connections can be "programmed" to create custom circuit
 - Programmable circuit shown can implement any 3-input function of up to 3 terms
 - e.g., $F = abc + a'c'$



Programmable Nodes in an SPLD

 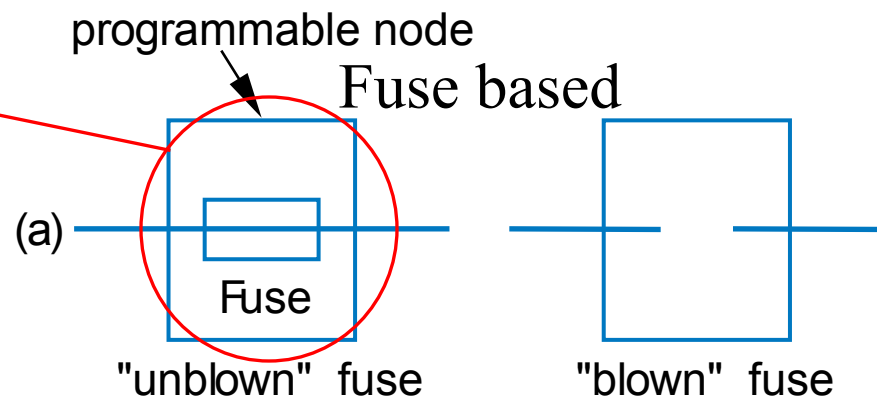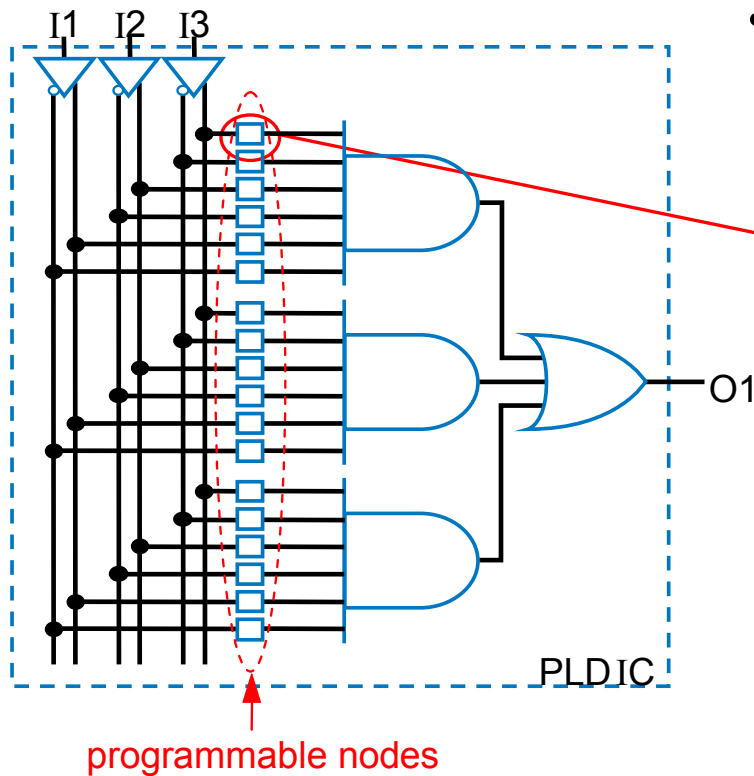
- Fuse based – "blown" fuse removes connection
- Memory based – 1 creates connection




PLD Drawings and PLD Implementation Example

- Common way of drawing PLD connections:

 - Uses one wire to represent all inputs of an AND
- Uses "x" to represent connection
 - Crossing wires are not connected unless "x" is present



 
- Example: Seat belt warning light using SPLD



Two ways to generate a 0 term




PLD Extensions

 

(a)

Two-output PLD

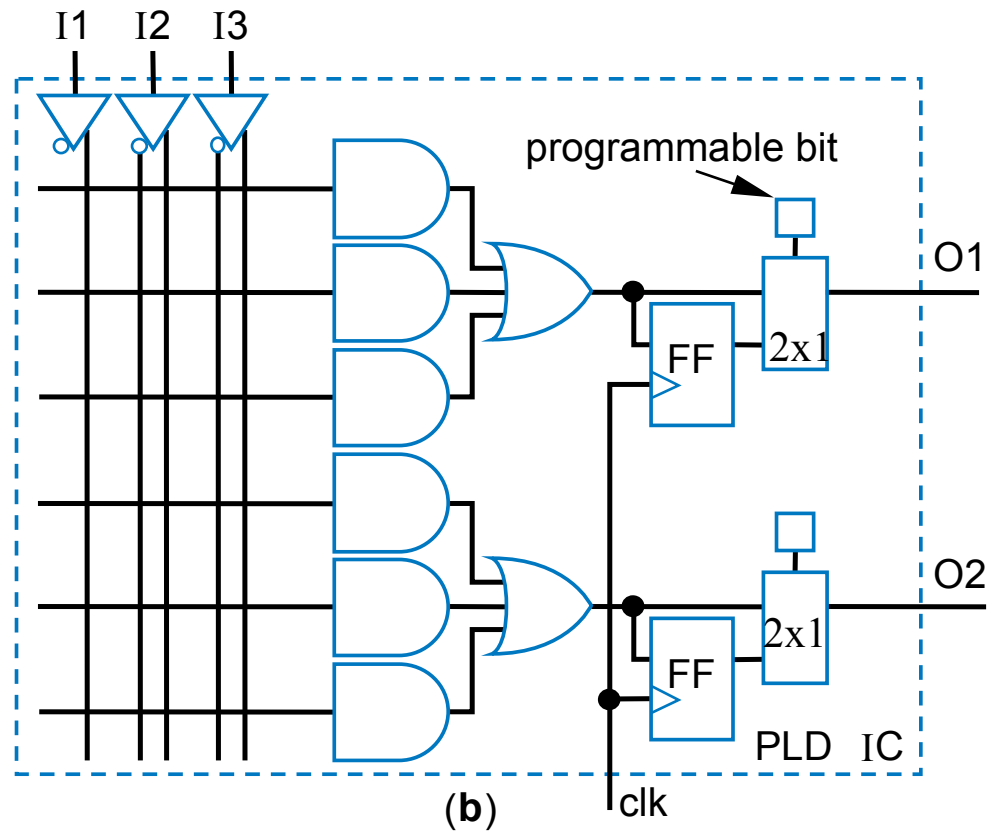

(b)

PLD with programmable registered outputs



More on PLDs

- Originally (1970s) known as Programmable Logic Array – *PLA*
 - Had programmable AND and OR arrays
- AMD created "Programmable Array Logic" – "*PAL*" (trademark)
 - Only AND array was programmable (fuse based)
- Lattice Semiconductor Corp. created "Generic Array Logic – "*GAL*" (trademark)
 - Memory based
- As IC capacities increased, companies put multiple PLD structures on one chip, interconnecting them
 - Became known as *Complex PLDs (CPLD)*, and older PLDs became known as Simple PLDs (SPLD)
- GENERALLY SPEAKING, difference of SPLDs vs. CPLDs vs. FPGAs:
 - SPLD: tens to hundreds of gates, and usually non-volatile (saves bits without power)
 - CPLD: thousands of gates, and usually non-volatile
 - FPGA: tens of thousands of gates and more, and usually volatile (but no reason why couldn't be non-volatile)




FPGA-to-Structured-ASIC

- FPGA sometimes used as ASIC prototype
 - Typical flow
 - (1) Implement user circuit on FPGA and test
 - (2) Implement user circuit on ASIC (large NRE cost)
 - FPGA-to-structured-ASIC flow
 - (1) Implement user circuit on FPGA and test
 - (2) Implement FPGA on ASIC
 - ASIC reflects FPGA structure, NOT the user's circuit structure
 - But remove programmability—LUTs and switch matrices are "hardwired"
 - ASICs lower layers prefabricated, only top layers remaining
 - Less chance of problems (ASIC is similar to FPGA, fewer changes)
 - Results in less NRE cost and less time to manufacture
 - But slower/bigger than if implement user circuit on ASIC directly



IC Tradeoffs, Trends, and Comparisons

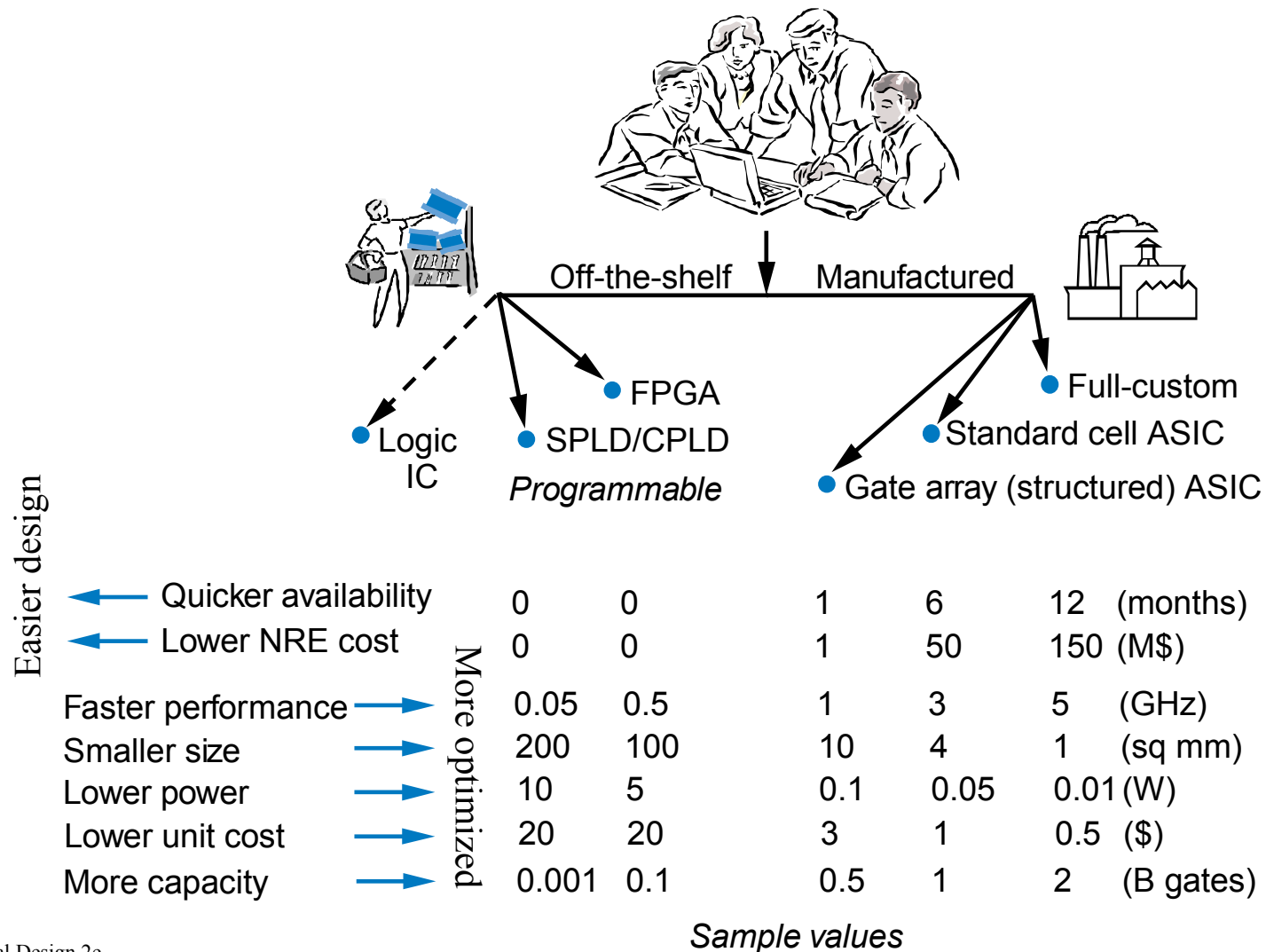

Choose an IC Type for Each Project


- Project A involves putting the circuit into 100 million mobile phones; encryption speed must be 2.5 GHz, and each chip can be priced up to \$5.
 - Only IC type with at least 2.5 GHz speed is standard cell ASIC. The \$50 million in NRE cost can be amortized over the 100 million chips by adding just \$0.50 to the price of each chip, which when added to the \$1 unit cost results in a price of \$1.50 per chip, much less than the limit of \$5.
 - → Use standard cell ASICs.
- Project B involves putting the circuit into 10,000 medical devices; encryption speed must be 1 MHz, and each chip can be priced up to \$50.
 - All three IC types meet speed requirement of 1 MHz. The \$50 million of NRE for a standard cell ASIC amortized over 10,000 chips would involve adding \$5,000 to the price of each chip, which clearly exceeds the limit of \$50 per chip. Even the \$1 million of NRE for a gate array ASIC would require adding \$100 to the price of each chip, which is still too much. Fortunately, the FPGA has no NRE cost, and a unit cost of \$20, which is less than the \$50 limit per chip.
 - → Use FPGAs.
- Project C involves putting the circuit into 100,000 automobiles; encryption speed must be 10 MHz, and each chip can be priced up to \$10.
 - All three IC types meet speed requirement of 10 MHz. Amortizing standard cell NRE would result in too high a chip price. Amortizing the gate array ASIC NRE of \$1 million over 100,000 chips would add \$10 per chip, which when added to the \$1 unit cost would result in \$11 per chip, slightly exceeding the \$10 per chip limit. However, the unit cost per FPGA chip is \$20. Thus, *none of the three IC types meets project C's price per chip requirement*, but the gate array IC type comes very close
 - → Use gate array.

(Choose from among standard cell ASIC, gate array ASIC, or FPGA IC types only, use metric values from previous slide.)




Key Trend in Implementation Technologies

 - Transistors per IC doubling every 18 months for past three decades
 - Known as "Moore's Law"
 - Tremendous implications – applications infeasible at one time due to outrageous processing requirements become feasible a few years later
 - Can Moore's Law continue?



Technology Comparisons

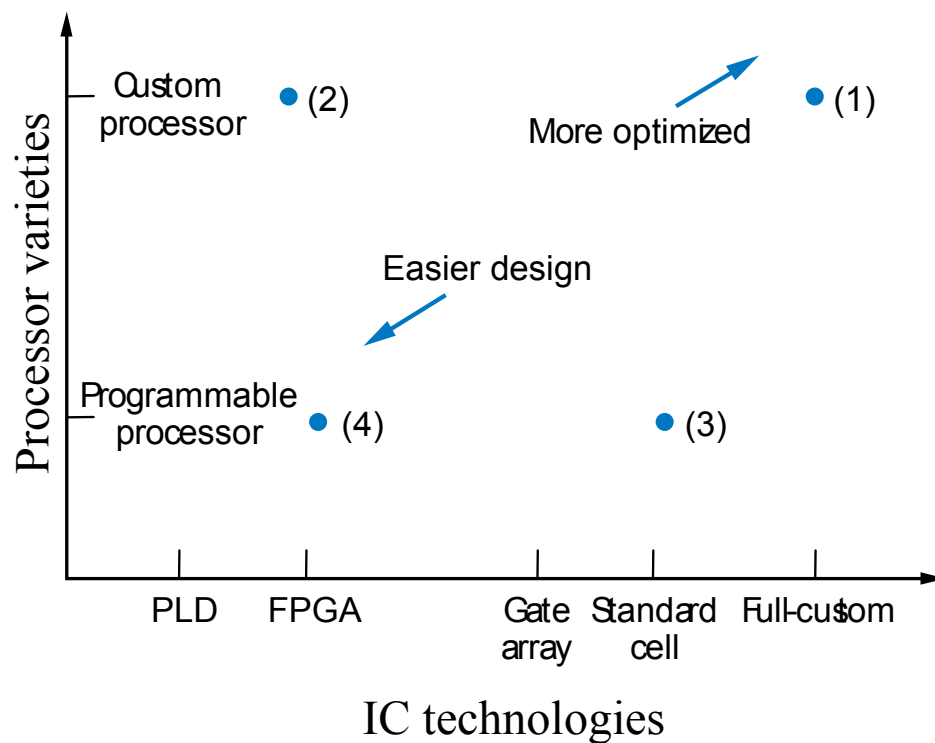

(1): Custom processor in full-custom IC
Highly optimized

(2): Custom processor in FPGA
Parallelized circuit, slower IC technology but programmable


(3): Programmable processor in standard cell IC
Program runs (mostly) sequentially on moderate-costing IC

 (4): Programmable processor in FPGA
Not only can processor be programmed, but FPGA can be programmed to implement multiple processors/coprocessors



Chapter Summary

- Many ways to get from design to physical implementation
 - Manufactured IC technologies
 - Full-custom IC
 - Decide on every transistor and wire
 - Semi-custom IC
 - Transistor details pre-designed
 - Gate array: Just wire existing gates
 - Standard cell: Place pre-designed cells and wire them
 - FPGAs
 - Fully programmable
 - Other technologies
 - Logic ICs, PLDs
 - Numerous tradeoffs among technologies, must choose best for given project
 - Trend towards programmable ICs



(a) Digital circuit design



(b) Physical implementation

