


CIS 501

Computer Organization and Design

Unit 4: Single-Cycle Datapath

Based on slides by Profs. Benedict Brown, C.J. Taylor,
Amir Roth & Milo Martin

This Unit: Single-Cycle Datapath

 


- Overview of ISAs
- Datapath storage elements
- MIPS Datapath
- MIPS Control

Readings

- P&H
 - Sections 4.1 – 4.4


Recall from CIS240...

240 Review: ISA

 

- App/OS are software ... execute on hardware
- HW/SW interface is **ISA (instruction set architecture)**
 - A **"contract"** between SW and HW
 - Encourages compatibility, allows SW/HW to evolve independently
 - **Functional definition** of HW storage locations & operations
 - Storage locations: registers, memory
 - Operations: add, multiply, branch, load, store, etc.
 - **Precise description** of how to invoke & access them
 - Instructions (bit-patterns hardware interprets as commands)

240 Review: LC4 ISA

 

- **LC4**: a toy ISA you know
 - 16-bit ISA (what does this mean?)
 - 16-bit insns
 - 8 registers (integer)
 - ~30 different insns
 - Simple OS support
- **Assembly language**
 - Human-readable ISA representation


```
.DATA
array .BLKW #100
sum .FILL #0

.CODE
.FALIGN

array_sum
CONST R5, #0
LEA R1, array
LEA R2, sum

array_sum_loop
LDR R3, R1, #0
LDR R4, R2, #0
ADD R4, R3, R4
STR R4, R2, #0
ADD R1, R1, #1
ADD R5, R5, #1
CMPI R5, #100
BRn array_sum_loop
```

371/501 Preview: A Real ISA

 


- **MIPS**: example of real ISA
 - 32/64-bit operations
 - 32-bit insns
 - 64 registers
 - 32 integer, 32 floating point
 - ~100 different insns
 - Full OS support

Example code is MIPS, but all ISAs are similar at some level

```
.data
array: .space 100
sum:   .word 0
.text

array_sum:
    li $5, 0
    la $1, array
    la $2, sum
array_sum_loop:
    lw $3, 0($1)
    lw $4, 0($2)
    add $4, $3, $4
    sw $4, 0($2)
    addi $1, $1, 1
    addi $5, $5, 1
    li $6, 100
    blt $5, $6, array_sum_loop
```


240 Review: Assembly Language

 


- **Assembly language**
 - Human-readable representation
- **Machine language**
 - Machine-readable representation
 - 1s and 0s (often displayed in “hex”)
- **Assembler**
 - Translates assembly to machine

| <u>Machine code</u> | <u>Assembly code</u> |
|---------------------|----------------------|
| x9A00 | CONST R5, #0 |
| x9200 | CONST R1, array |
| xD320 | HICONST R1, array |
| x9464 | CONST R2, sum |
| xD520 | HICONST R2, sum |
| x6640 | LDR R3, R1, #0 |
| x6880 | LDR R4, R2, #0 |
| x18C4 | ADD R4, R3, R4 |
| x7880 | STR R4, R2, #0 |
| x1261 | ADD R1, R1, #1 |
| x1BA1 | ADD R5, R5, #1 |
| x2B64 | CMPI R5, #100 |
| x03F8 | BRn array_sum_loop |

240 Review: Insn Execution Model

 

- The computer is just finite state machine
 - **Registers** (few of them, but fast)
 - **Memory** (lots of memory, but slower)
 - **Program counter** (next insn to execute)
 - Sometimes called “instruction pointer”
- A computer executes **instructions**
 - **Fetches** next instruction from memory
 - **Decodes** it (figure out what it does)
 - **Reads** its **inputs** (registers & memory)
 - **Executes** it (adds, multiply, etc.)
 - **Write** its **outputs** (registers & memory)
 - **Next insn** (adjust the program counter)
- **Program is just “data in memory”**
 - Makes computers programmable (“universal”)

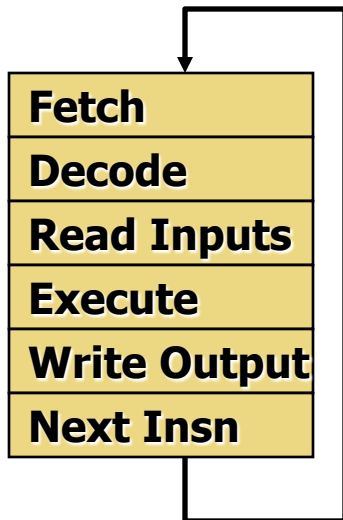

Instruction → **Insn**

What is an ISA?

What Is An ISA?

- **ISA (instruction set architecture)**
 - A well-defined hardware/software interface
 - The “**contract**” between software and hardware
 - **Functional definition** of storage locations & operations
 - Storage locations: registers, memory
 - Operations: add, multiply, branch, load, store, etc
 - **Precise description** of how to invoke & access them
- Not in the “contract”: non-functional aspects
 - How operations are implemented
 - Which operations are fast and which are slow and when
 - Which operations take more power and which take less
- Instructions
 - Bit-patterns hardware interprets as commands
 - Instruction → Insn (instruction is too long to write in slides)

A Language Analogy for ISAs

- Communication
 - Person-to-person → software-to-hardware
- Similar structure
 - Narrative → program
 - Sentence → insn
 - Verb → operation (add, multiply, load, branch)
 - Noun → data item (immediate, register value, memory value)
 - Adjective → addressing mode
- Many different languages, many different ISAs
 - Similar basic structure, details differ (sometimes greatly)
- Key differences between languages and ISAs
 - Languages evolve organically, many ambiguities, inconsistencies
 - ISAs are explicitly engineered and extended, unambiguous

LC4 vs Real ISAs

- LC4 has the basic features of a real-world ISAs
 - ± LC4 lacks a good bit of realism
 - Address size is only 16 bits
 - Only one data type (16-bit signed integer)
 - Little support for system software, none for multiprocessing (later)
- Many real-world ISAs to choose from:
 - Intel x86 (laptops, desktop, and servers)
 - MIPS (used throughout in book)
 - ARM (in all your mobile phones)
 - PowerPC (servers & game consoles)
 - SPARC (servers)
 - Intel's Itanium
 - Historical: IBM 370, VAX, Alpha, PA-RISC, 68k, ...


Some Key Attributes of ISAs

- Instruction encoding
 - Fixed length (16-bit for LC4, 32-bit for MIPS & ARM)
 - Variable length (1 byte to 16 bytes, average of ~ 3 bytes)
- Number and type of registers
 - LC-4 has 8 registers
 - MIPS has 32 “integer” registers and 32 “floating point” registers
 - ARM & x86 both have 16 “integer” regs and 16 “floating point” regs
- Address space
 - LC4: 16-bit addresses at 16-bit granularity (128KB total)
 - ARM: 32-bit addresses at 8-bit granularly (4GB total)
 - Modern x86 and ARM64: 64-bit addresses (16 exabytes!)
- Memory addressing modes
 - MIPS & LC4: address calculated by “reg+offset”
 - x86 and others have much more complicated addressing modes

Access Granularity & Alignment


- **Byte addressability**

 - An address points to a byte (8 bits) of data
- The ISA's minimum granularity to read or write memory
- ISAs also support wider load/stores
 - "Half" (2 bytes), "Longs" (4 bytes), "Quads" (8 bytes)



- Load.byte [6] -> r1
- Load.long [12] -> r2

 However, physical memory systems operate on **even larger chunks**



- Load.long [4] -> r1
- Load.long [11] -> r2
- "unaligned"

- **Access alignment:** if $\text{address} \% \text{size} \neq 0$, then it is "unaligned"
 - A single unaligned access may require multiple physical memory accesses

Handling Unaligned Accesses

- **Access alignment:** if $\text{address} \% \text{size} \neq 0$, then it is “unaligned”
 - A single unaligned access may require multiple physical memory accesses
- How to handle such unaligned accesses?
 1. Disallow (unaligned operations are considered illegal)
 - MIPS, ARMv5 and earlier took this route
 2. Support in hardware? (allow such operations)
 - x86, ARMv6+ allow regular loads/stores to be unaligned
 - Unaligned access still slower, adds significant hardware complexity
 3. Trap to software routine?
 - Simpler hardware, but high penalty when unaligned
 4. In software (compiler can use regular instructions when possibly unaligned)
 - Load, shift, load, shift, and (slow, needs help from compiler)

How big is this struct?

```
struct foo {  
    char c;  
    int i;  
}
```

Another Addressing Issue: Endian-ness

- **Endian-ness**: arrangement of bytes in a multi-byte number
 - Big-endian: sensible order (e.g., MIPS, PowerPC, ARM)
 - A 4-byte integer: "00000000 00000000 00000010 00000011" is 515
 - Little-endian: reverse order (e.g., x86)
 - A 4-byte integer: "00000011 00000010 00000000 00000000" is 515
 - Why little endian?

00000011 00000010 00000000 00000000

starting address

integer casts are free
on little-endian
architectures

ISA Code Examples

Array Sum Loop: LC4

```
.DATA
array .BLKW #100
sum   .FILL #0

.CODE
.FALIGN
array_sum
    CONST R5, #0
    LEA R1, array
    LEA R2, sum

L1
    LDR R3, R1, #0
    LDR R4, R2, #0
    ADD R4, R3, R4
    STR R4, R2, #0
    ADD R1, R1, #1
    ADD R5, R5, #1
    CMPI R5, #100
    BRn L1
```

```
int array[100];
int sum;
void array_sum() {
    for (int i=0; i<100;i++)
    {
        sum += array[i];
    }
}
```

Array Sum Loop: LC4 → MIPS

```
.DATA
array .BLKW #100
sum .FILL #0

.CODE
.FALIGN
array_sum
    CONST R5, #0
    LEA R1, array
    LEA R2, sum
L1
    LDR R3, R1, #0
    LDR R4, R2, #0
    ADD R4, R3, R4
    STR R4, R2, #0
    ADD R1, R1, #1
    ADD R5, R5, #1
    CMPI R5, #100
    BRn L1

.data
array: .space 100
sum: .word 0

.text
array_sum:
    li $5, 0
    la $1, array
    la $2, sum
L1:
    lw $3, 0($1)
    lw $4, 0($2)
    add $4, $3, $4
    sw $4, 0($2)
    addi $1, $1, 1
    addi $5, $5, 1
    li $6, 100
    blt $5, $6, L1
```

MIPS (right) similar to LC4

Syntactic differences:
register names begin with \$
immediates are un-prefixed

Only simple addressing modes
syntax: displacement(reg)

Left-most register is generally
destination register

Array Sum Loop: LC4 → x86

```
.DATA
array .BLKW #100
sum .FILL #0

.CODE
.FALIGN
array_sum
    CONST R5, #0
    LEA R1, array
    LEA R2, sum

L1
    LDR R3, R1, #0
    LDR R4, R2, #0
    ADD R4, R3, R4
    STR R4, R2, #0
    ADD R1, R1, #1
    ADD R5, R5, #1
    CMPI R5, #100
    BRn L1
```

```
.LFE2
.comm array,400,32
.comm sum,4,4

.globl array_sum
array_sum:
    movl $0, -4(%rbp)

.L1:
    movl -4(%rbp), %eax
    movl array(,%eax,4), %edx
    movl sum(%rip), %eax
    addl %edx, %eax
    movl %eax, sum(%rip)
    addl $1, -4(%rbp)
    cmpl $99, -4(%rbp)
    jle .L1
```

x86 (right) is different

Syntactic differences:
register names begin with %
immediates begin with \$

%rbp is base (frame) pointer

Many addressing modes

x86 Operand Model

.LFE2

```
.comm array,400,32
```

```
.comm sum,4,4
```

```
.globl array_sum
```

```
array_sum:
```

```
movl $0, -4(%rbp)
```

- x86 uses explicit accumulators
 - Both register and memory
 - Distinguished by addressing mode

Two operand insns
(right-most is typically source & destination)

.L1:

```
movl -4(%rbp), %eax
```

```
movl array(,%eax,4), %edx
```

```
movl sum(%rip), %eax
```

```
addl %edx, %eax
```

```
movl %eax, sum(%rip)
```

```
addl $1, -4(%rbp)
```

```
cmpl $99, -4(%rbp)
```

```
jle .L1
```

Register accumulator: $\%eax = \%eax + \%edx$

"L" insn suffix and "%e..." reg.
prefix mean "32-bit value"


Memory accumulator:
 $\text{Memory}[\%rbp-4] = \text{Memory}[\%rbp-4] + 1$

MOVUPS—Move Unaligned Packed Single-Precision Floating-Point Values

| Opcode/ Instruction | Op/ En | 64/32-bit Mode | CPUID Feature Flag | Description |
|--|-----------|-------------------|--------------------------|---|
| OF 10 /r MOVUPS <i>xmm1, xmm2/m128</i> | RM | V/V | SSE | Move packed single-precision floating-point values from <i>xmm2/m128</i> to <i>xmm1</i> . |
| VEX.128.OF.WIG 10 /r VMOVUPS <i>xmm1, xmm2/m128</i> | RM | V/V | AVX | Move unaligned packed single-precision floating-point from <i>xmm2/mem</i> to <i>xmm1</i> . |
| VEX.256.OF.WIG 10 /r VMOVUPS <i>ymm1, ymm2/m256</i> | RM | V/V | AVX | Move unaligned packed single-precision floating-point from <i>ymm2/mem</i> to <i>ymm1</i> . |
| OF 11 /r MOVUPS <i>xmm2/m128, xmm1</i> | MR | V/V | SSE | Move packed single-precision floating-point values from <i>xmm1</i> to <i>xmm2/m128</i> . |
| VEX.128.OF.WIG 11 /r VMOVUPS <i>xmm2/m128, xmm1</i> | MR | V/V | AVX | Move unaligned packed single-precision floating-point from <i>xmm1</i> to <i>xmm2/mem</i> . |
| VEX.256.OF.WIG 11 /r VMOVUPS <i>ymm2/m256, ymm1</i> | MR | V/V | AVX | Move unaligned packed single-precision floating-point from <i>ymm1</i> to <i>ymm2/mem</i> . |


Implementing an ISA

Implementing an ISA

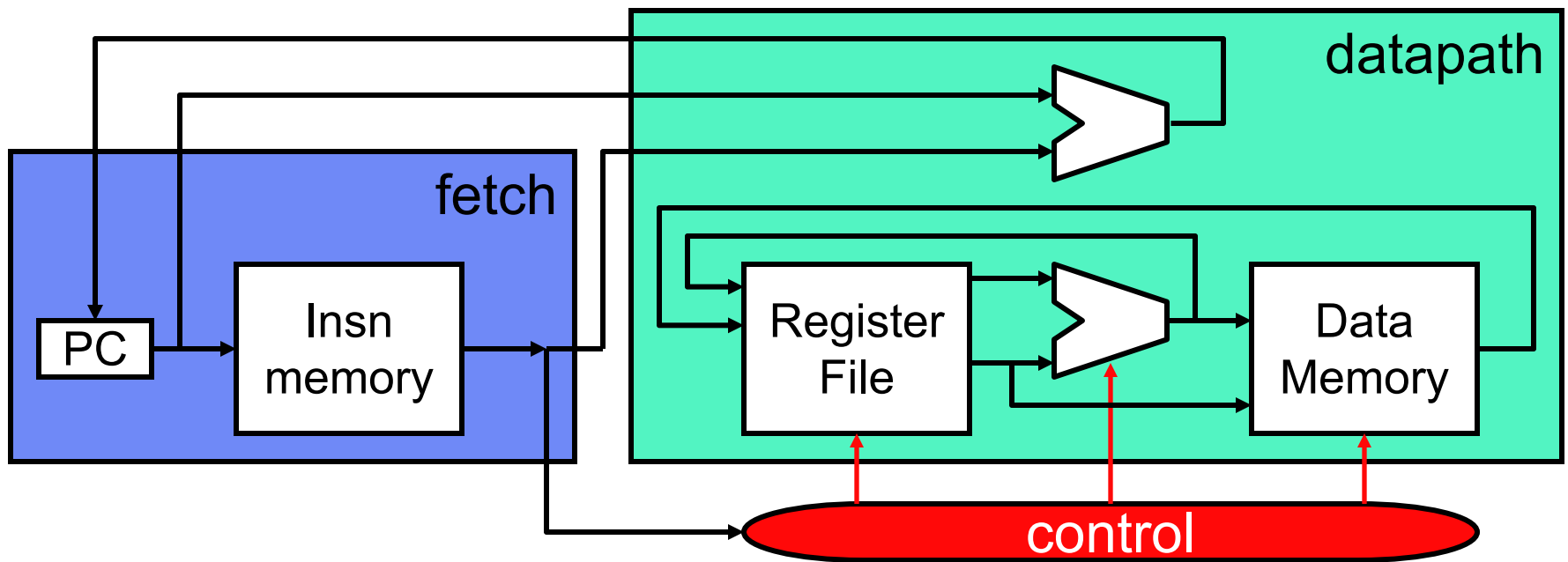


- **Datapath:** performs computation (registers, ALUs, etc.)
 - ISA specific: can implement every insn (single-cycle: in one pass!)
- **Control:** determines which computation is performed
 - Routes data through datapath (which regs, which ALU op)
- **Fetch:** get insn, translate opcode into control
- **Fetch** → **Decode** → **Execute** "cycle"

Two Types of Components

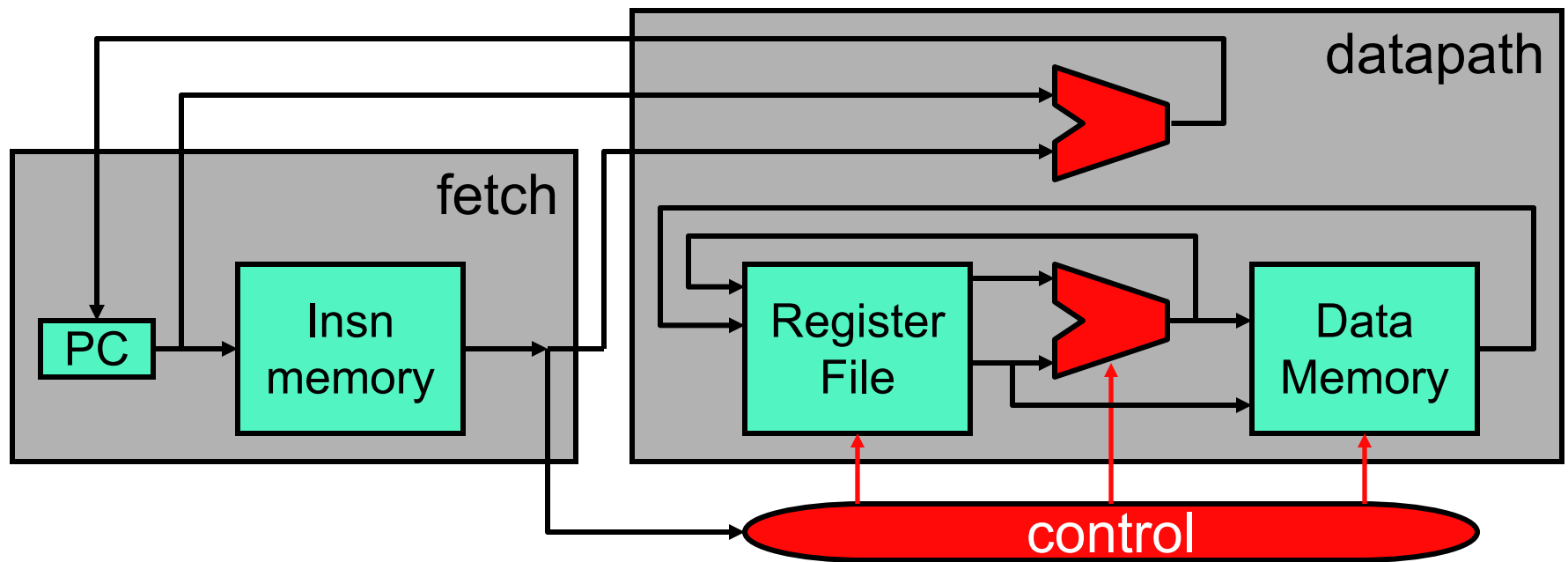


- **Purely combinational:** stateless computation
 - ALUs, muxes, control
 - Arbitrary Boolean functions
- **Combinational/sequential:** storage
 - PC, insn/data memories, register file
 - Internally contain some combinational components

Example Datapath

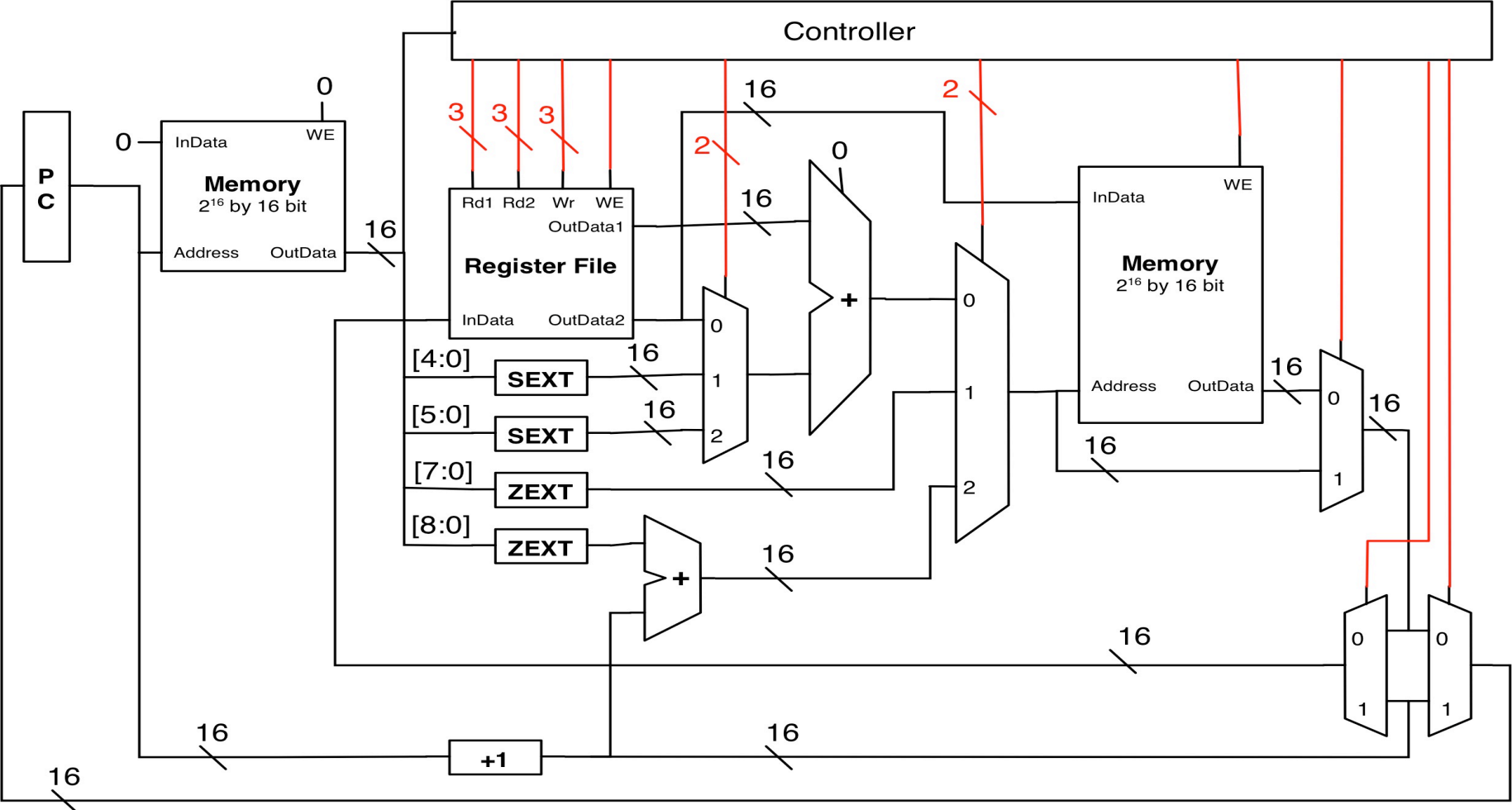


LC4 Datapath

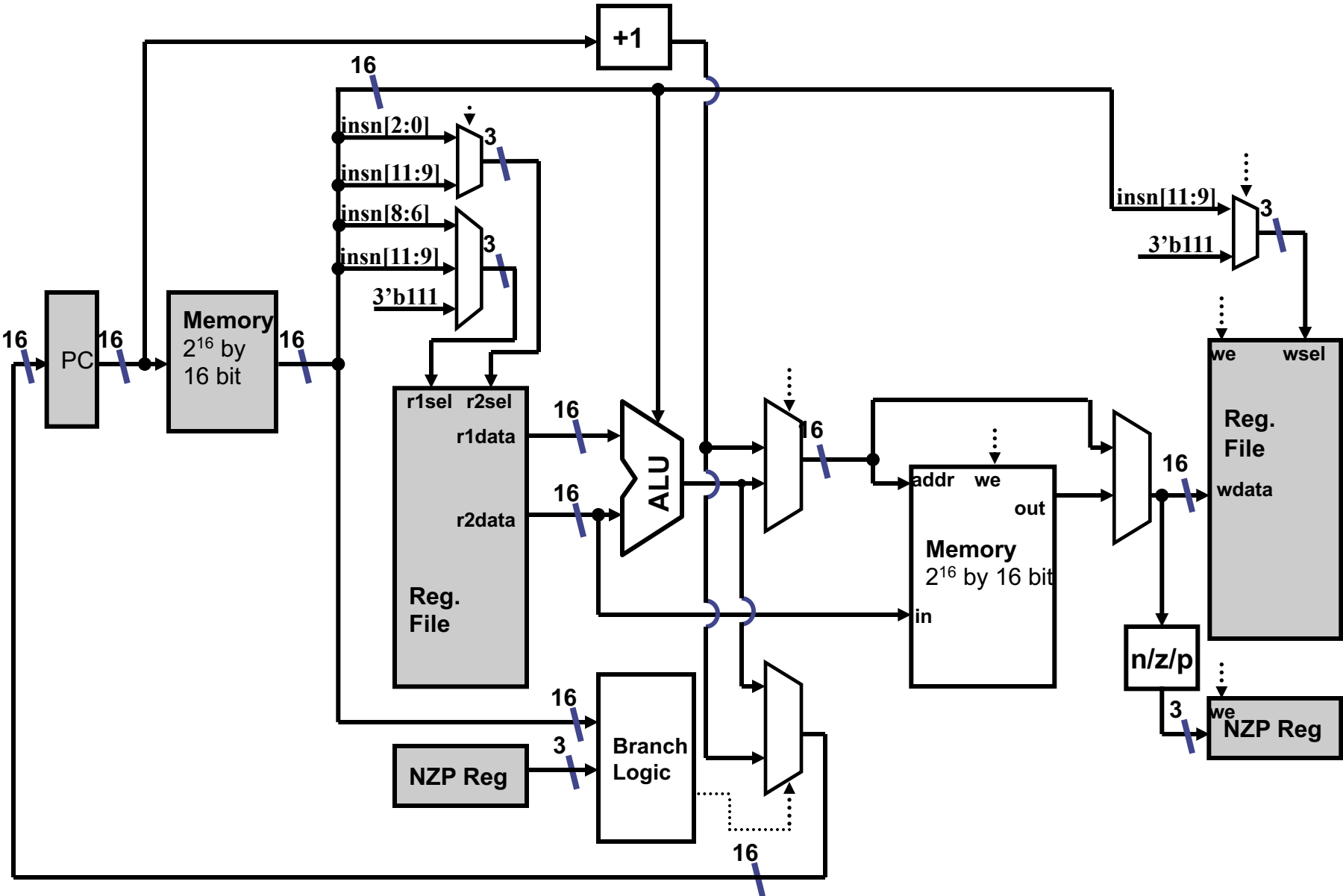

MIPS Datapath

Unified vs Split Memory Architecture

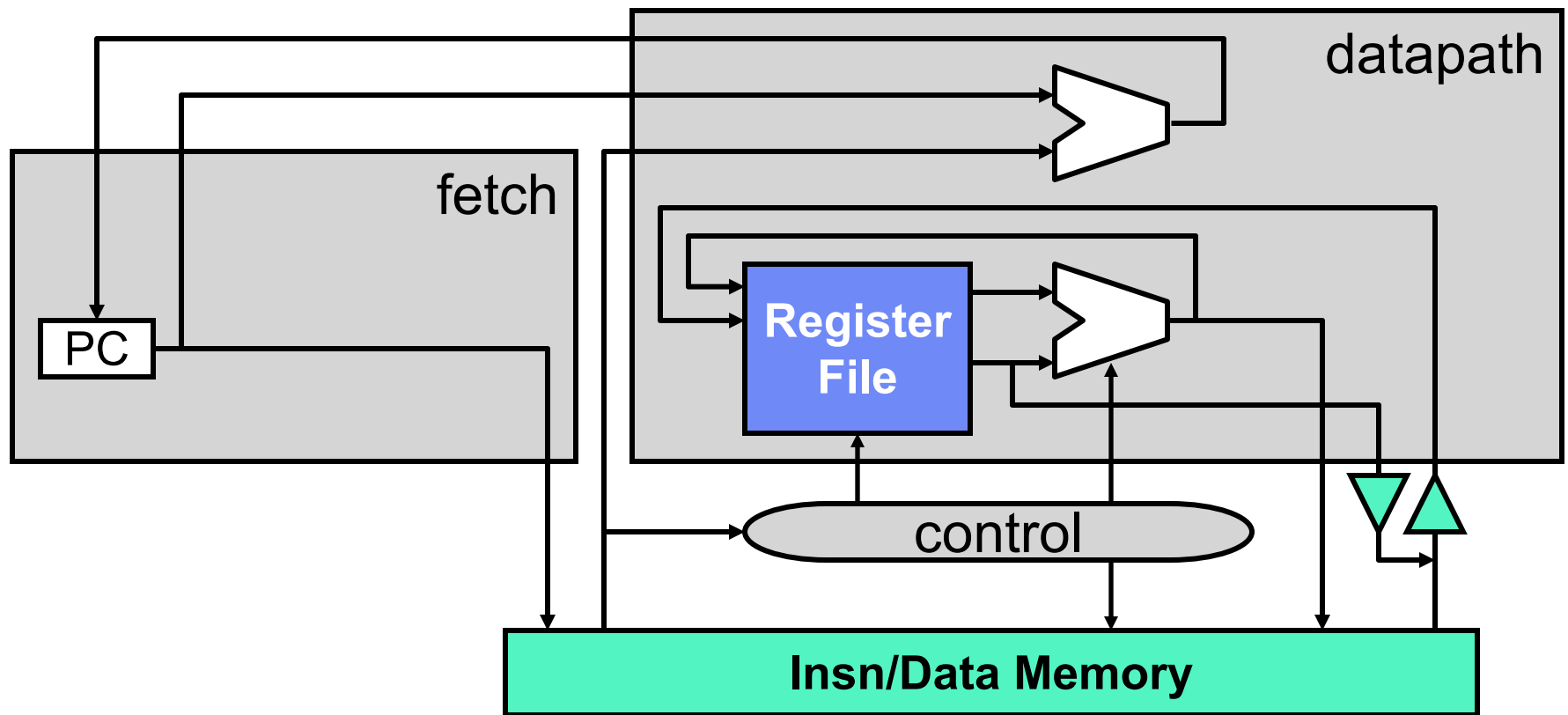

- **Unified architecture**: unified insn/data memory
- **“Harvard” architecture**: split insn/data memories

Datapath for MIPS ISA

- MIPS: 32-bit instructions, registers are \$0, \$2... \$31

- Consider only the following instructions

| | | |
|---|----------------------------------|----------------------|
| <code>add \$1,\$2,\$3</code> | <code>\$1 = \$2 + \$3</code> | (add) |
| <code>addi \$1,\$2,3</code> | <code>\$1 = \$2 + 3</code> | (add immed) |
| <code>lw \$1,4(\$3)</code> | <code>\$1 = Memory[4+\$3]</code> | (load) |
| <code>sw \$1,4(\$3)</code> | <code>Memory[4+\$3] = \$1</code> | (store) |
| <code>beq \$1,\$2,PC_relative_target</code> | | (branch equal) |
| <code>j absolute_target</code> | | (unconditional jump) |

- Why only these?

- Most other instructions are the same from datapath viewpoint
- The ones that aren't are left for you to figure out 😊


MIPS Instruction layout

MIPS machine language

| Name | Format | Example | | | | | | Comments |
|------------|--------|---------|--------|--------|---------|--------|--------|--|
| add | R | 0 | 18 | 19 | 17 | 0 | 32 | add \$s1,\$s2,\$s3 |
| sub | R | 0 | 18 | 19 | 17 | 0 | 34 | sub \$s1,\$s2,\$s3 |
| addi | I | 8 | 18 | 17 | 100 | | | addi \$s1,\$s2,100 |
| lw | I | 35 | 18 | 17 | 100 | | | lw \$s1,100(\$s2) |
| sw | I | 43 | 18 | 17 | 100 | | | sw \$s1,100(\$s2) |
| Field size | | 6 bits | 5 bits | 5 bits | 5 bits | 5 bits | 6 bits | All MIPS instructions are 32 bits long |
| R-format | R | op | rs | rt | rd | shamt | funct | Arithmetic instruction format |
| I-format | I | op | rs | rt | address | | | Data transfer format |


FIGURE 2.6 MIPS architecture revealed through Section 2.5. The two MIPS instruction formats so far are R and I. The first 16 bits are the same: both contain an *op* field, giving the base operation; an *rs* field, giving one of the sources; and the *rt* field, which specifies the other source operand, except for load word, where it specifies the destination register. R-format divides the last 16 bits into an *rd* field, specifying the destination register; the *shamt* field, which Section 2.6 explains; and the *funct* field, which specifies the specific operation of R-format instructions. I-format combines the last 16 bits into a single *address* field.

Start With Fetch

 

- PC and instruction memory (split insn/data architecture, for now)
- A +4 incrementer computes default next instruction PC
- How would Verilog for this look given insn memory as interface?

First Instruction: **add**

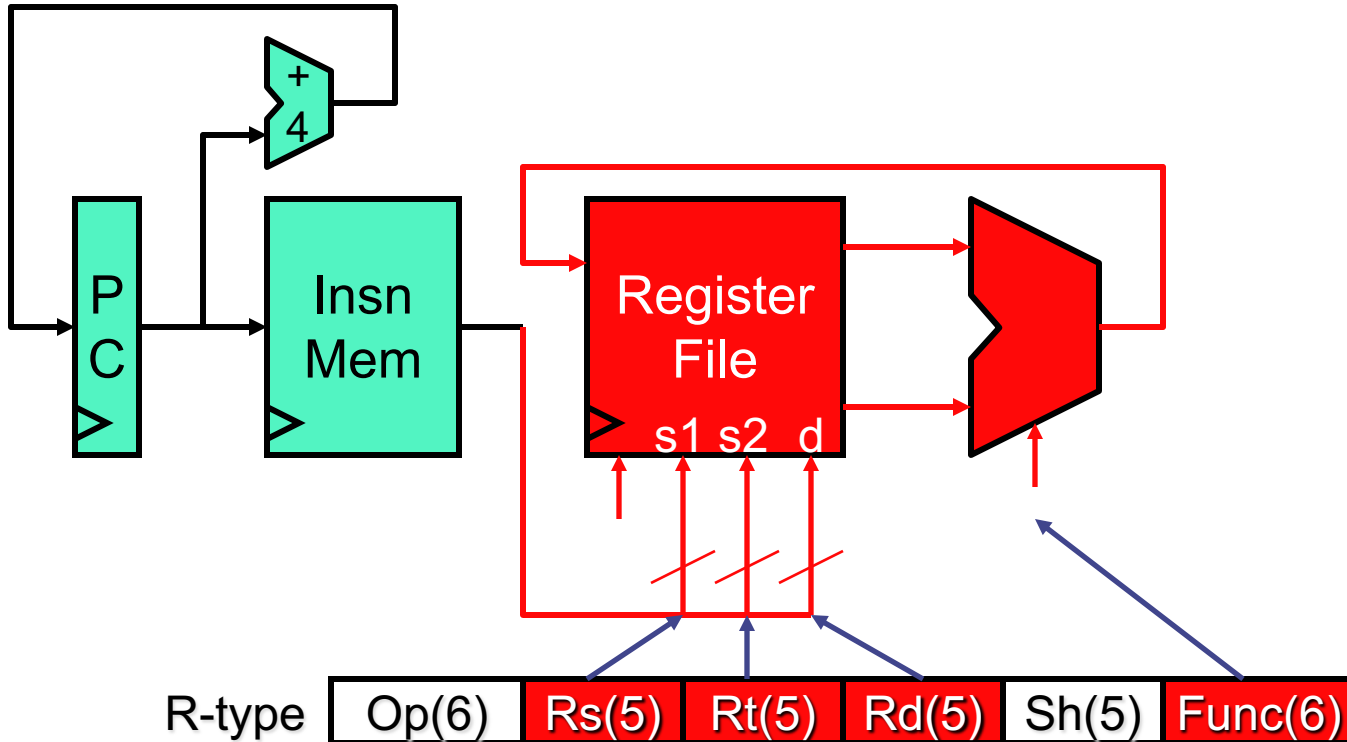

- Add register file
- Add arithmetic/logical unit (ALU)

Wire Select in Verilog


- How to rip out individual fields of an insn? **Wire select**

```
wire [31:0] insn;  
wire [5:0] op = insn[31:26];  
wire [4:0] rs = insn[25:21];  
wire [4:0] rt = insn[20:16];  
wire [4:0] rd = insn[15:11];  
wire [4:0] sh = insn[10:6];  
wire [5:0] func = insn[5:0];
```

R-type

| | | | | | |
|-------|-------|-------|-------|-------|---------|
| Op(6) | Rs(5) | Rt(5) | Rd(5) | Sh(5) | Func(6) |
|-------|-------|-------|-------|-------|---------|

Second Instruction: **addi**

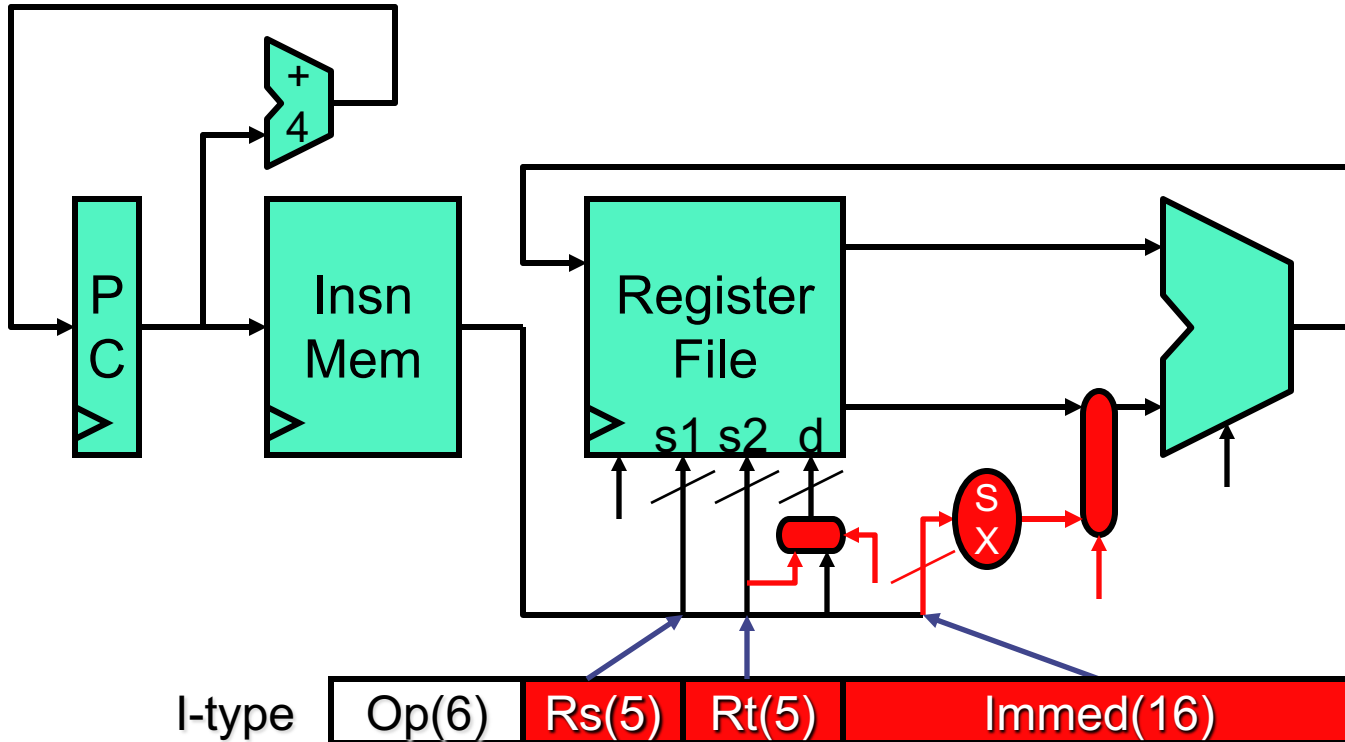

- Destination register can now be either Rd or Rt
- Add sign extension unit and mux into second ALU input


Verilog Wire Concatenation

- Recall two Verilog constructs
 - **Wire concatenation:** {bus0, bus1, ... , busn}
 - **Wire repeat:** {repeat_x_times{w0}}
- How do you specify sign extension? **Wire concatenation**

```
wire [31:0] insn;  
wire [15:0] imm16 = insn[15:0];  
wire [31:0] sximm16 = {{16{imm16[15]}}, imm16};
```




Third Instruction: **lw**

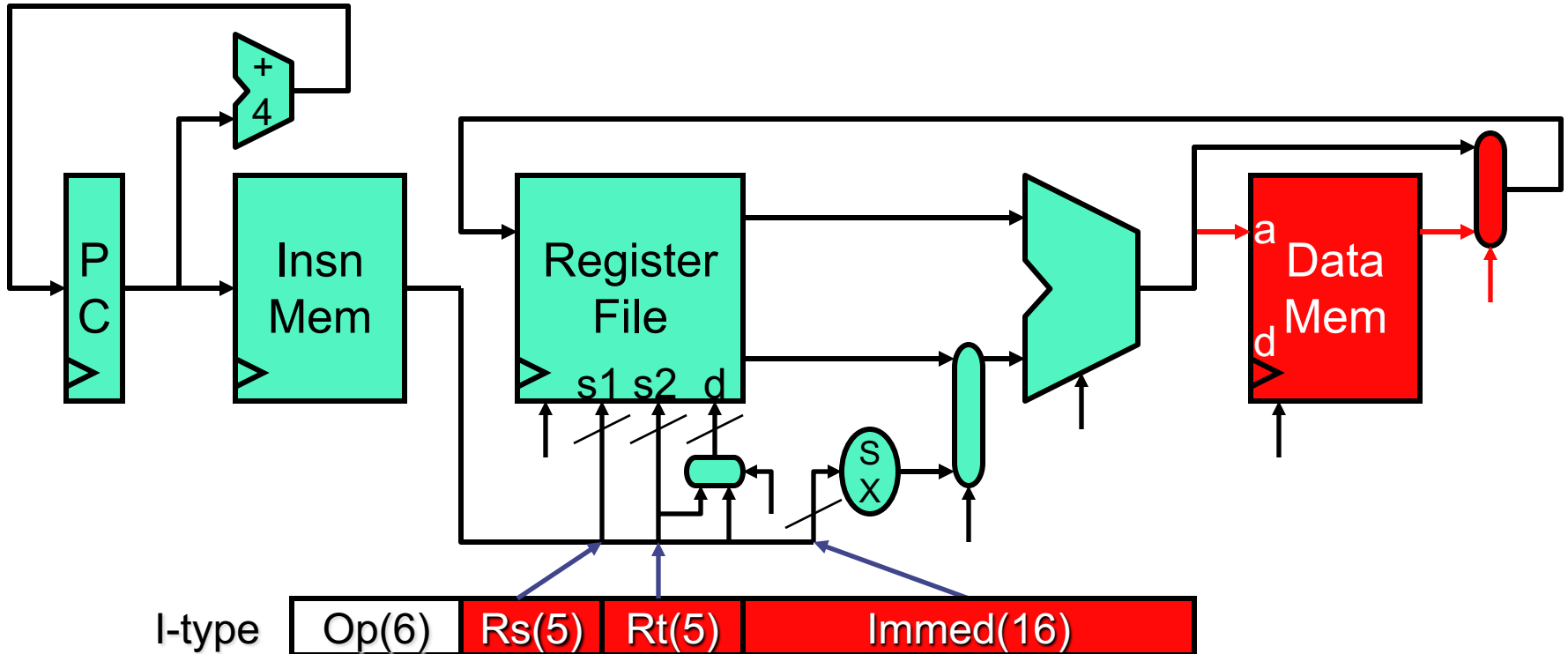


- Add data memory, address is ALU output
- Add register write data mux to select memory output or ALU output

Fourth Instruction: **SW**

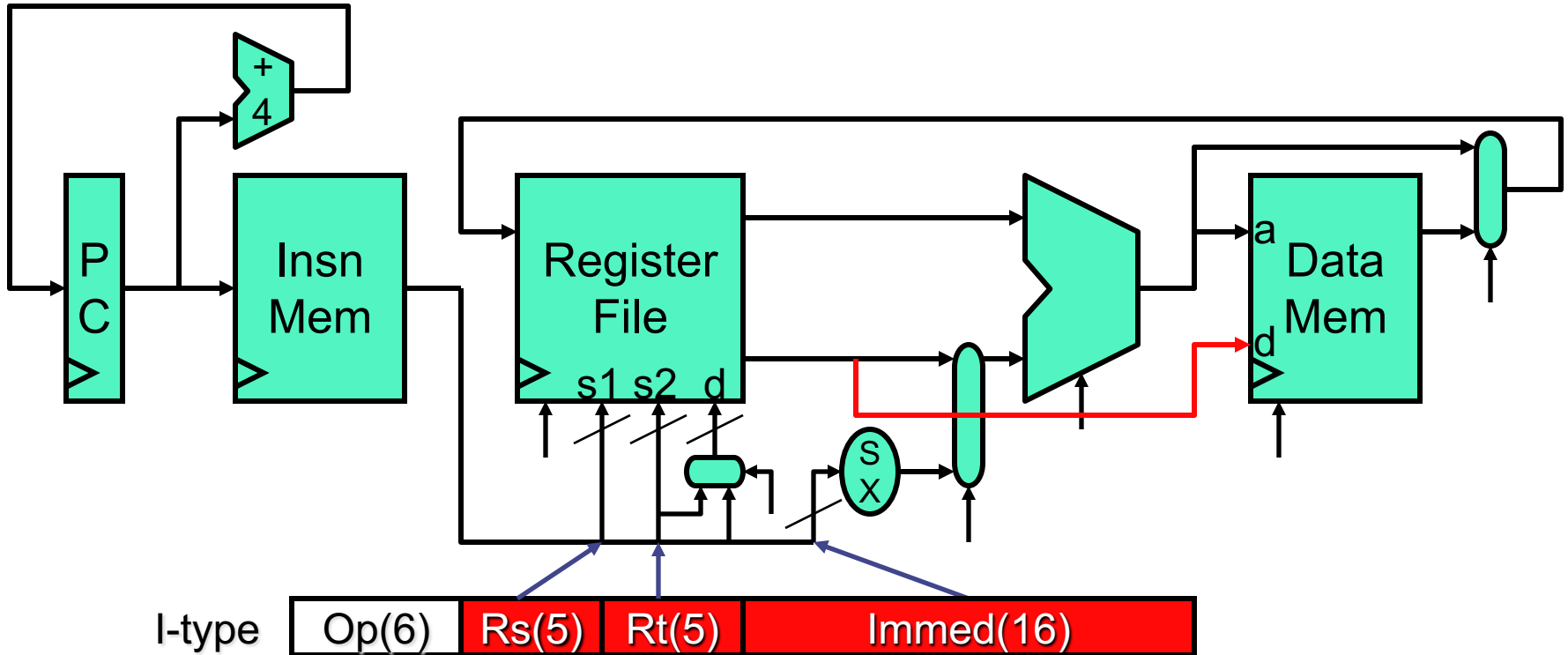

- Add path from second input register to data memory data input

Fifth Instruction: **beq**

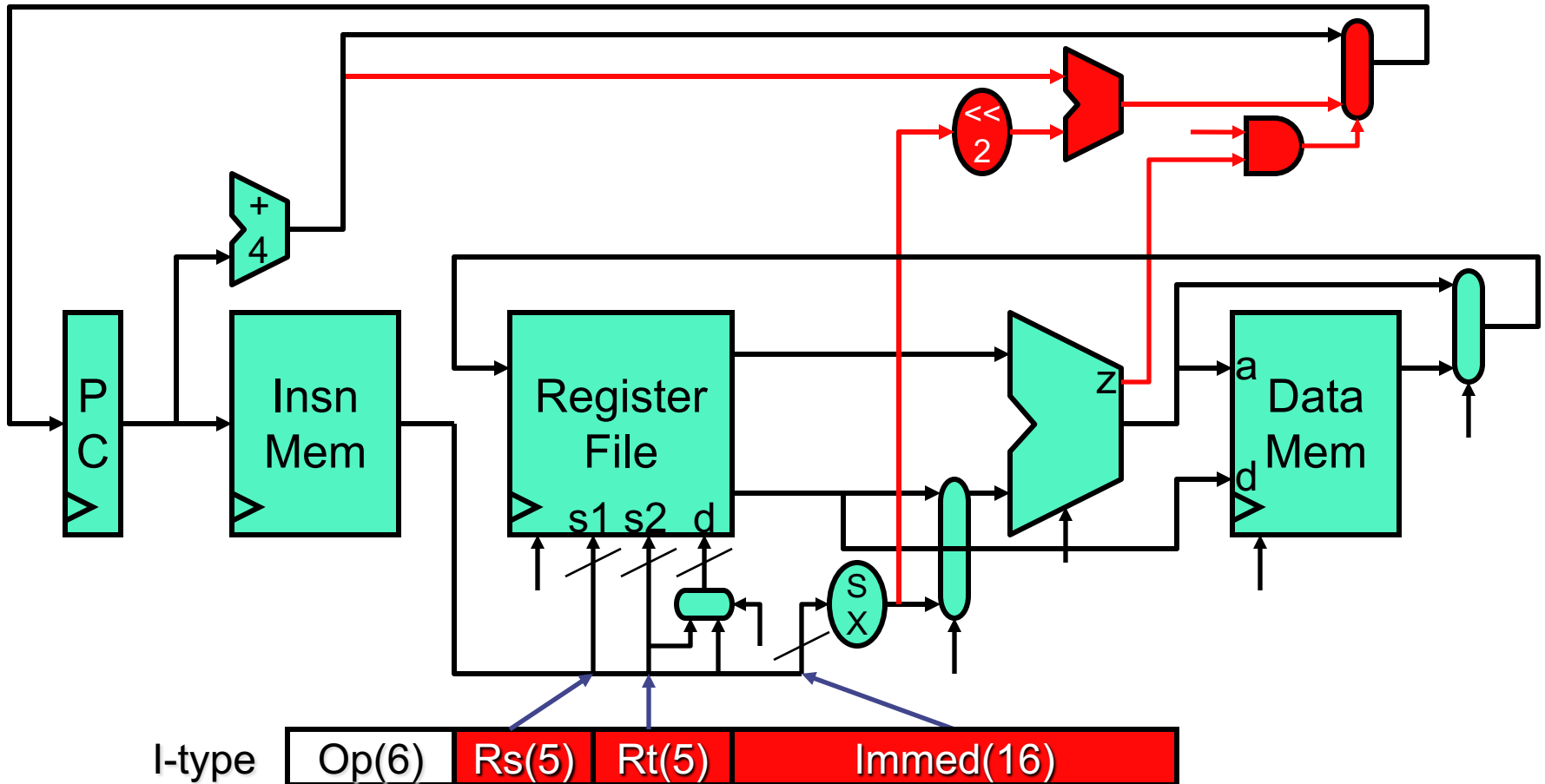

- Add left shift unit and adder to compute PC-relative branch target
- Add PC input mux to select PC+4 or branch target

Another Use of Wire Concatenation

- How do you do $\ll 2$? **Wire concatenation**


```
wire [31:0] insn;
```

```
wire [25:0] imm26 = insn[25:0]
```

```
wire [31:0] imm26_shifted_by_2 = {4'b0000, imm26, 2'b00};
```




Sixth Instruction: **j**

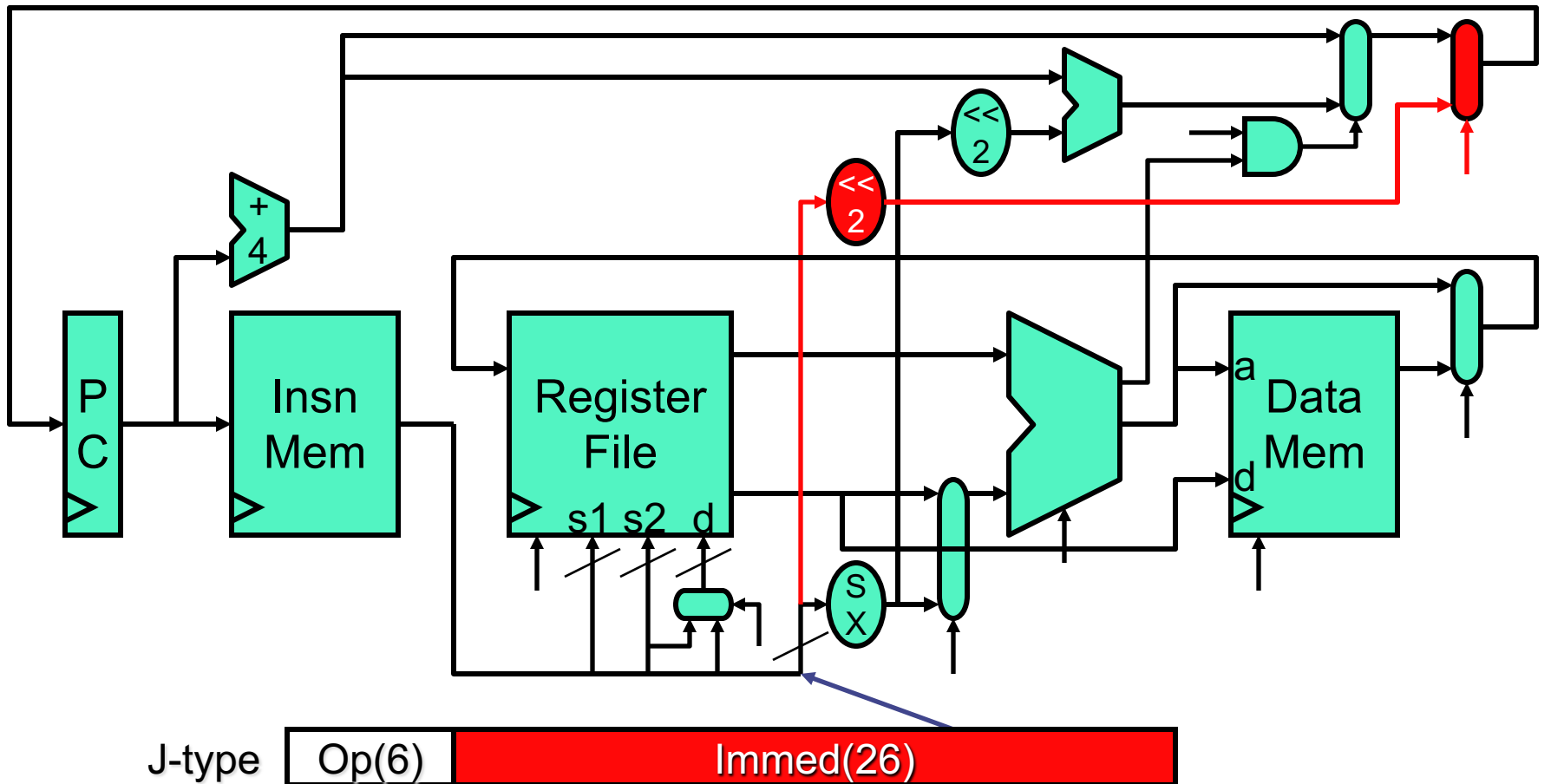

- Add shifter to compute left shift of 26-bit immediate
- Add additional PC input mux for jump target


MIPS Control

What Is Control?

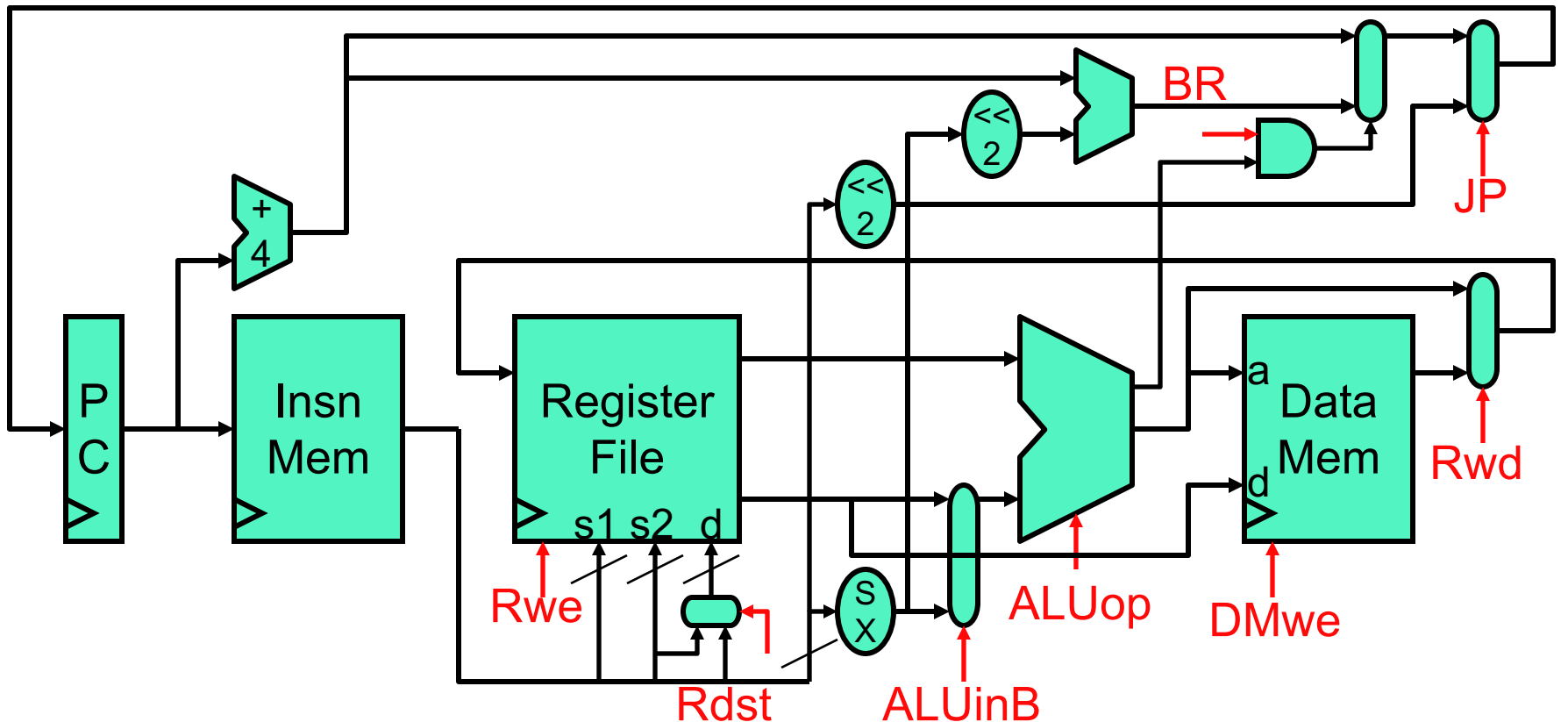


- 8 signals control flow of data through this datapath
 - MUX selectors, or register/memory write enable signals
 - A real datapath has 300-500 control signals

Example: Control for **add**

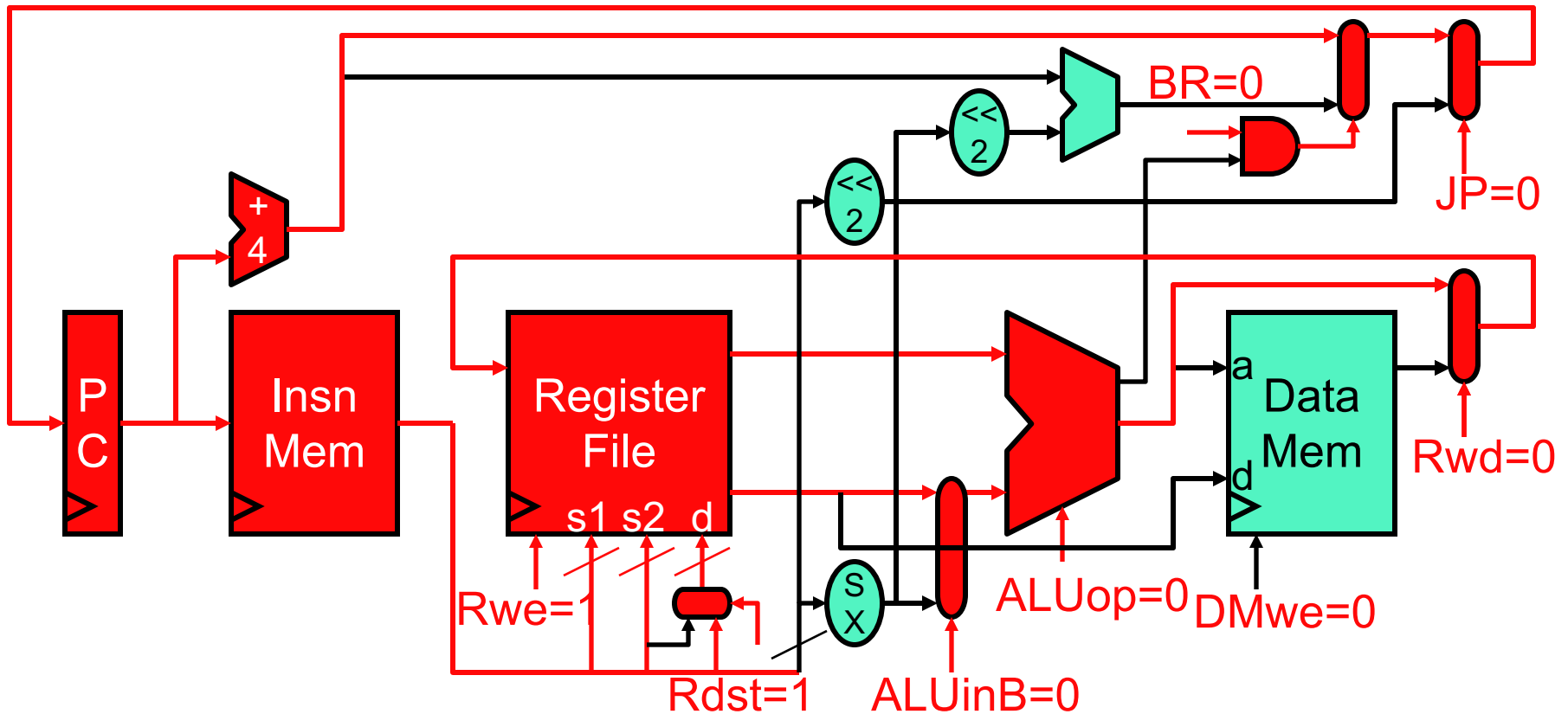


Example: Control for **sw**

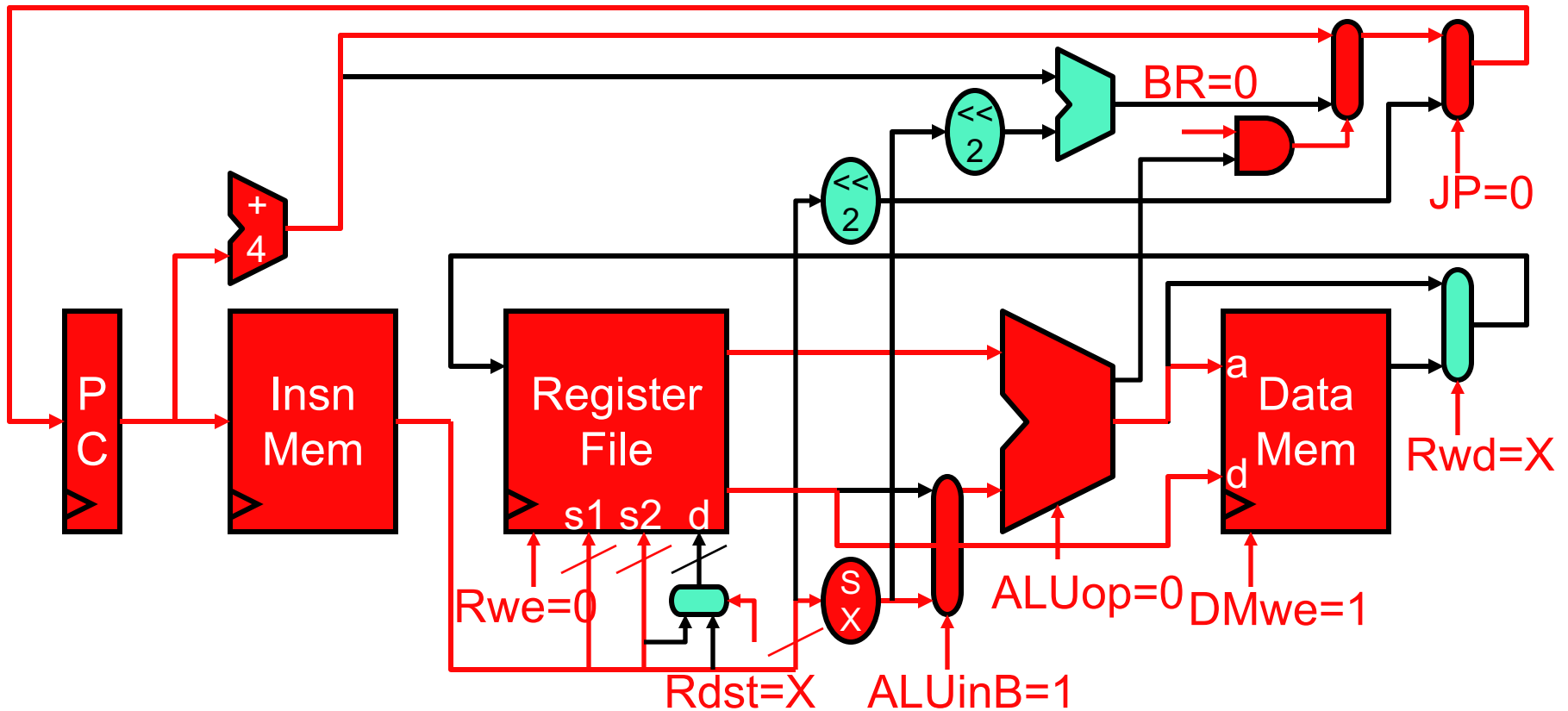


- Difference between **sw** and **add** is 5 signals
 - 3 if you don't count the X (don't care) signals

Example: Control for **beq**

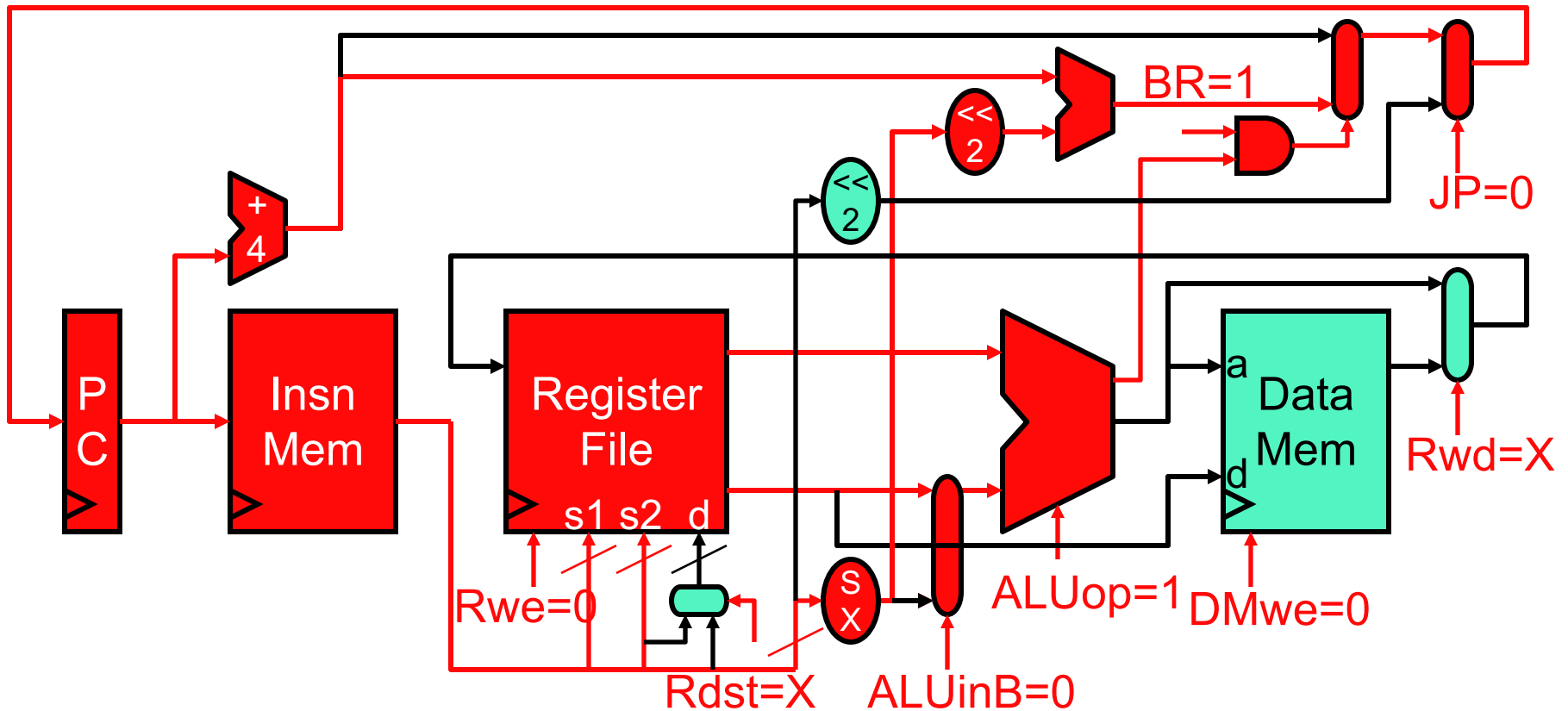

- Difference between **sw** and **beq** is only 4 signals

How Is Control Implemented?

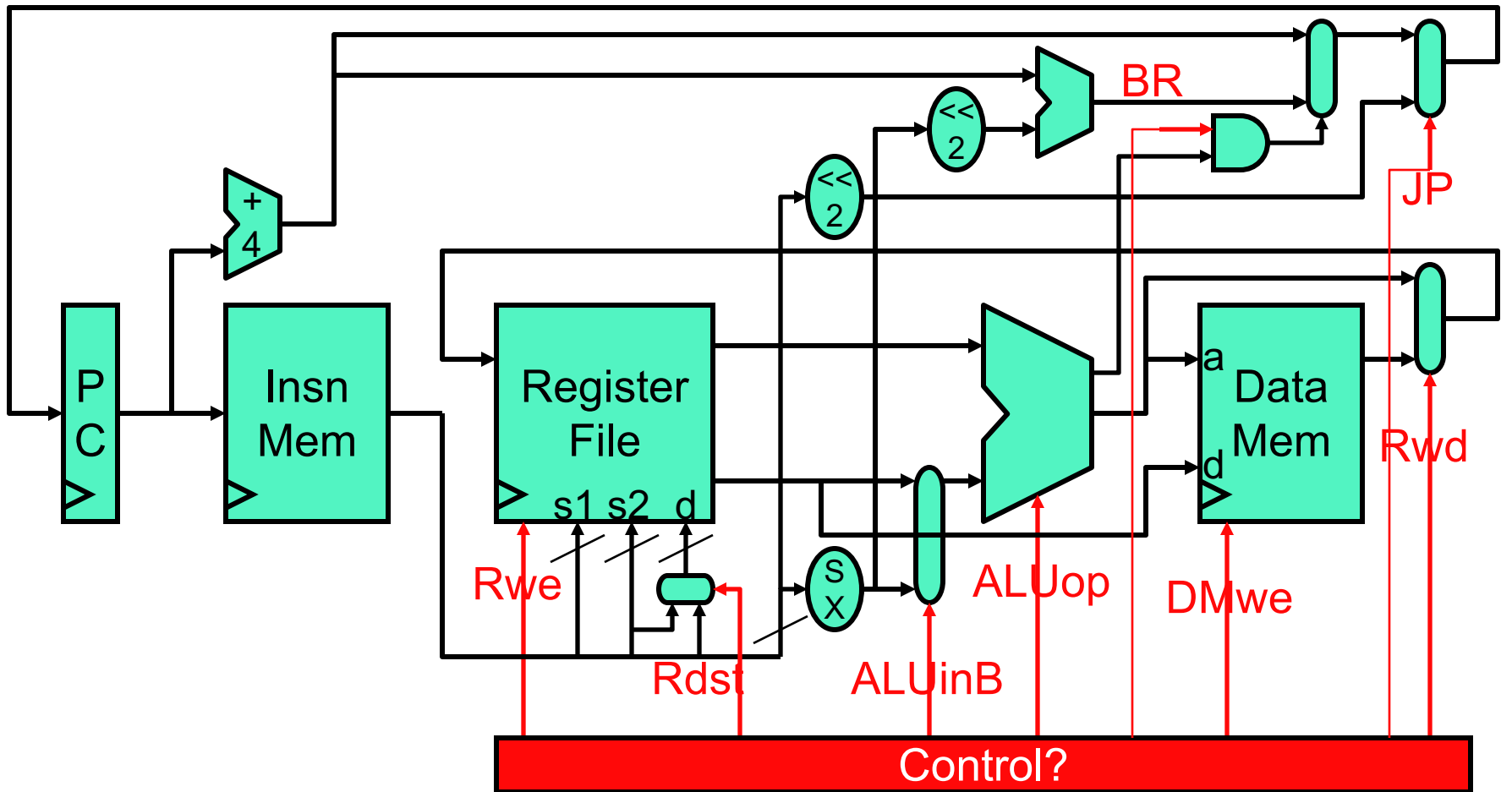


Implementing Control

- Each instruction has a unique set of control signals
 - Most are function of opcode
 - Some may be encoded in the instruction itself
 - E.g., the ALUop signal is some portion of the MIPS Func field
 - + Simplifies controller implementation
 - Requires careful ISA design

Control Implementation: ROM

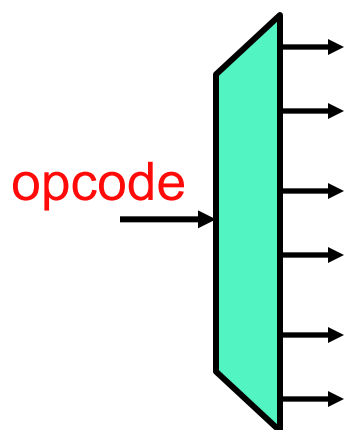
- **ROM (read only memory)**: like a RAM but unwritable
 - Bits in data words are control signals
 - Lines indexed by opcode
 - Example: ROM control for 6-insn MIPS datapath
 - X is “don’t care”



| | BR | JP | ALUinB | ALUop | DMwe | Rwe | Rdst | Rwd |
|------|----|----|--------|-------|------|-----|------|-----|
| add | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| addi | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 |
| lw | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 1 |
| sw | 0 | 0 | 1 | 0 | 1 | 0 | X | X |
| beq | 1 | 0 | 0 | 1 | 0 | 0 | X | X |
| j | 0 | 1 | 0 | 0 | 0 | 0 | X | X |


Control Implementation: Logic

 - Real machines have 100+ insns 300+ control signals
 - 30,000+ control bits (~4KB)
 - Not huge, but hard to make faster than datapath (important!)
- Alternative: **logic gates** or “random logic” (unstructured)
 - Exploits the observation: many signals have few 1s or few 0s
 - Example: random logic control for 6-insn MIPS datapath




Control Logic in Verilog

```
wire [31:0] insn;  
wire [5:0] func = insn[5:0]  
wire [5:0] opcode = insn[31:26];  
wire is_add = ((opcode == 6'h00) & (func == 6'h20));  
wire is_addi = (opcode == 6'h0F);  
wire is_lw = (opcode == 6'h23);  
wire is_sw = (opcode == 6'h2A);  
wire ALUinB = is_addi | is_lw | is_sw;  
wire Rwe = is_add | is_addi | is_lw;  
wire Rwd = is_lw;  
wire Rdst = ~is_add;  
wire DMwe = is_sw;
```

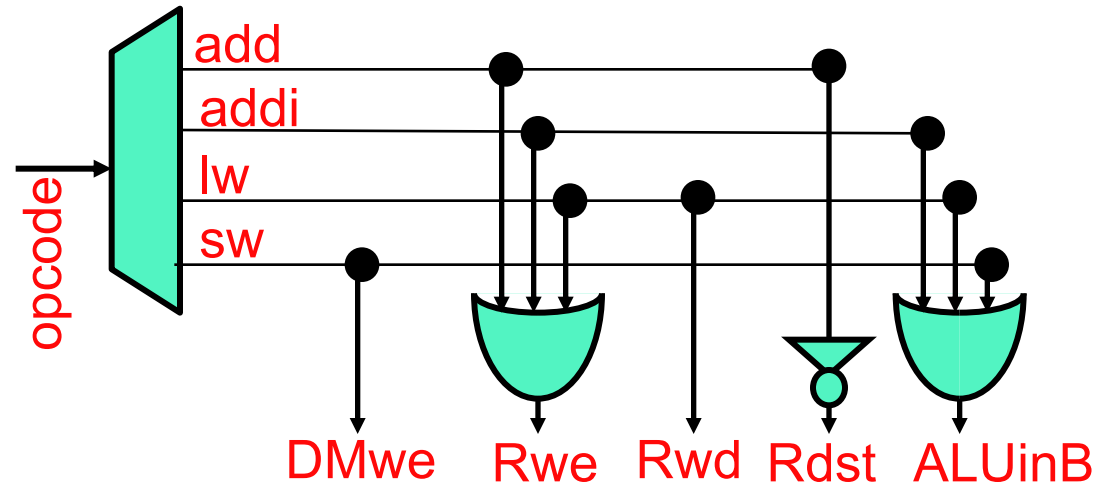

Datapath Storage Elements


Register File

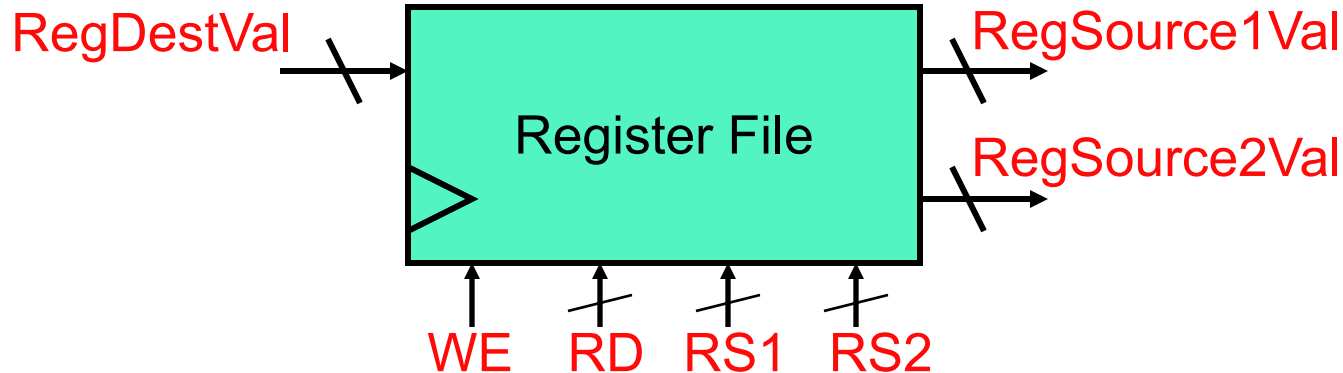

- **Register file**: M N-bit storage words
 - Multiplexed input/output: data buses write/read "random" word
- **"Port"**: set of buses for accessing a random word in array
 - Data bus (N-bits) + address bus ($\log_2 M$ -bits) + optional WE bit
 - P ports = P parallel and independent accesses
- MIPS integer register file
 - 32 32-bit words, two read ports + one write port (why?)

Decoder

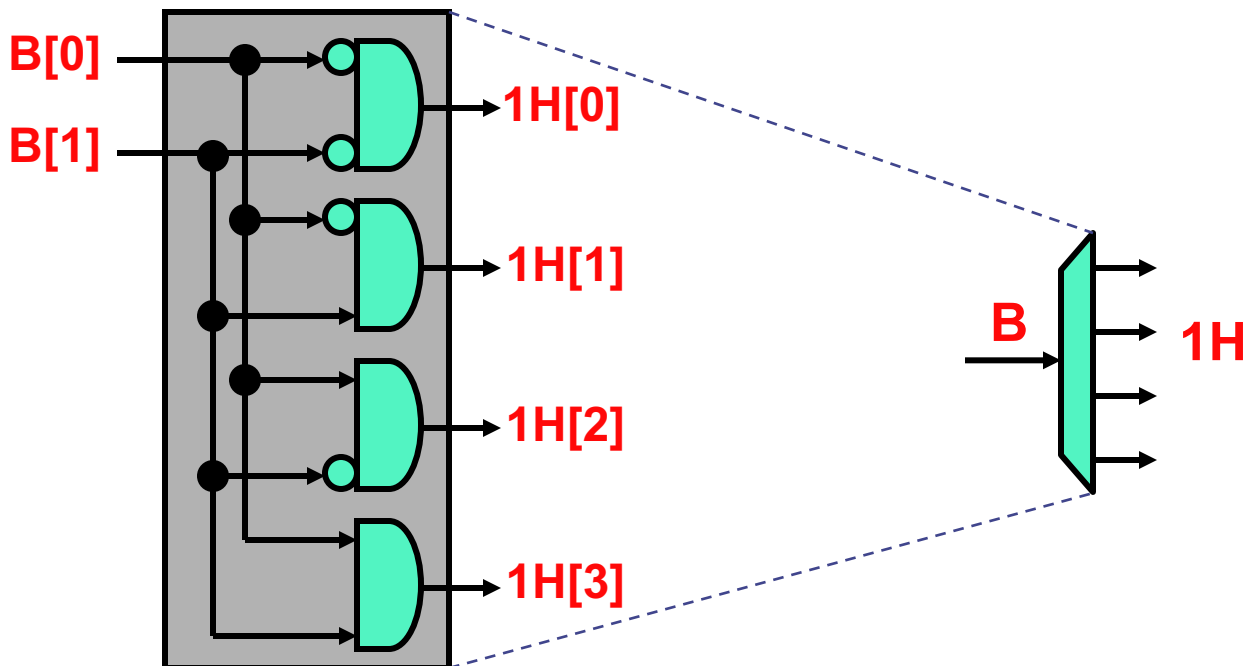- **Decoder**: converts binary integer to “1-hot” representation
 - Binary representation of $0 \dots 2^N - 1$: N bits
 - 1 hot representation of $0 \dots 2^N - 1$: 2^N bits
 - J represented as J^{th} bit 1, all other bits zero
 - Example below: 2-to-4 decoder



Decoder in Verilog (1 of 2)

```
module decoder_2_to_4 (binary_in, onehot_out);
    input [1:0] binary_in;
    output [3:0] onehot_out;
    assign onehot_out[0] = (~binary_in[0] & ~binary_in[1]);
    assign onehot_out[1] = (~binary_in[0] & binary_in[1]);
    assign onehot_out[2] = (binary_in[0] & ~binary_in[1]);
    assign onehot_out[3] = (binary_in[0] & binary_in[1]);
endmodule
```

- Is there a simpler way?

Decoder in Verilog (2 of 2)

```
module decoder_2_to_4 (binary_in, onehot_out);
    input [1:0] binary_in;
    output [3:0] onehot_out;
    assign onehot_out[0] = (binary_in == 2'd0);
    assign onehot_out[1] = (binary_in == 2'd1);
    assign onehot_out[2] = (binary_in == 2'd2);
    assign onehot_out[3] = (binary_in == 2'd3);
endmodule
```


- How is "a == b" implemented for vectors?
 - $\sim|(a \wedge b)$ (this is a "nor" reduction of bitwise "a xor b")
 - When one of the inputs to "==" is a constant
 - Simplifies to simpler inverter on bits with "one" in constant
 - Exactly what was on previous slide! (apply DeMorgan's law)

Register File Interface




- **Inputs:**
 - RS1, RS2 (reg. sources to read), RD (reg. destination to write)
 - WE (write enable), RDestVal (value to write)
- **Outputs:** RSrc1Val, RSrc2Val (value of RS1 & RS2 registers)

Register File: Four Registers

 


- Register file with four registers

Add a Read Port

 


- Output of each register into 4to1 mux (RSrc1Val)
 - RS1 is select input of RSrc1Val mux

Add Another Read Port

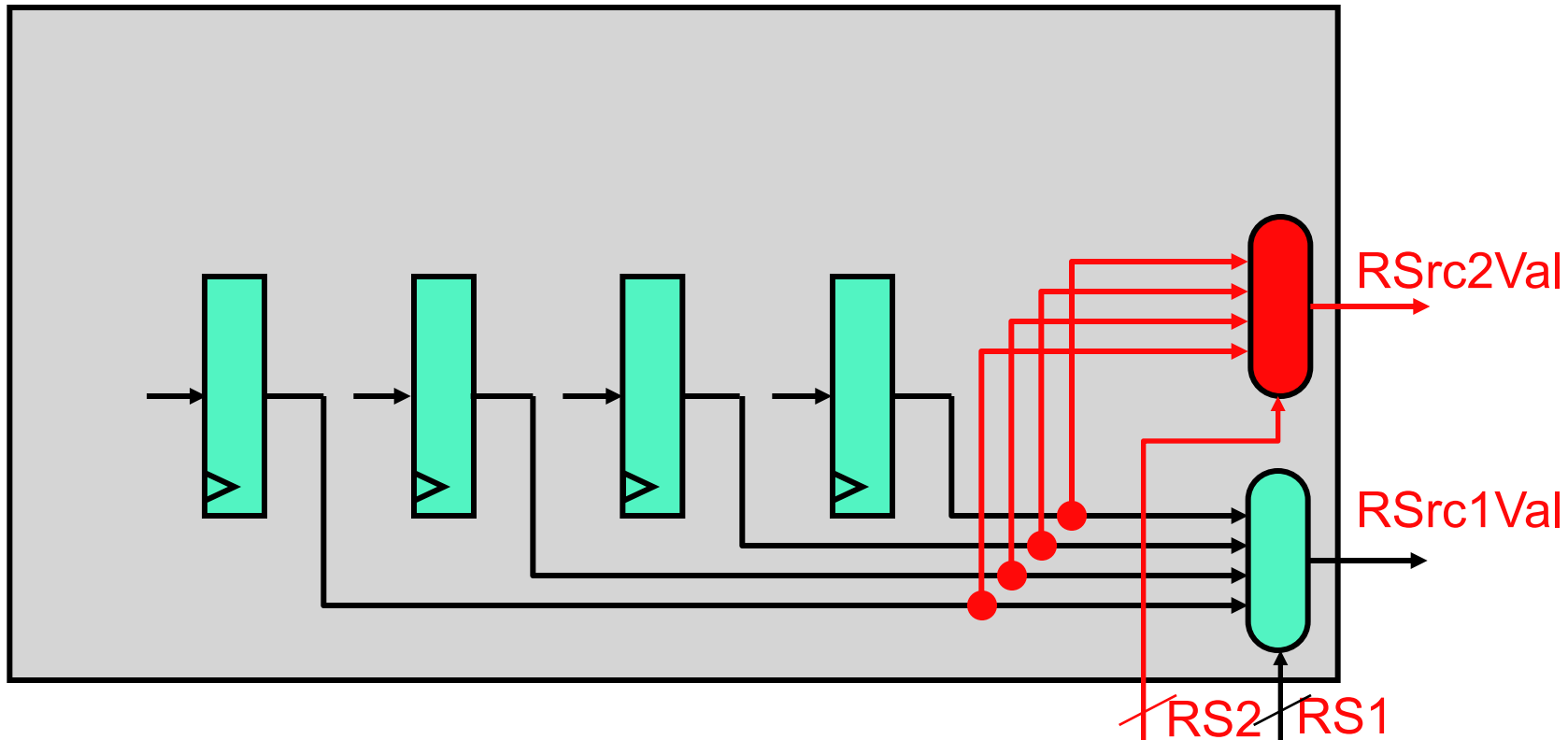

- Output of each register into another 4to1 mux (RSrc2Val)
 - RS2 is select input of RSrc2Val mux

Add a Write Port

 

- Input **RegDestVal** into each register
 - Enable only one register's **WE**: (Decoded **RD**) & (**WE**)
- What if we needed two write ports?

Register File Interface (Verilog)

```
module regfile4(rs1, rs1val, rs2, rs2val, rd, rdval, we, rst, clk);
    parameter n = 1;
    input [1:0] rs1, rs2, rd;
    input we, rst, clk;
    input [n-1:0] rdval;
    output [n-1:0] rs1val, rs2val;
    ...
endmodule
```

- Building block modules:
 - module **register** (out, in, wen, rst, clk);
 - module **decoder_2_to_4** (binary_in, onehot_out)
 - module **Nbit_mux4to1** (sel, a, b, c, d, out);

Register File Interface (Verilog)

```
module regfile4(rs1, rs1val, rs2, rs2val, rd, rdval, we, rst, clk);  
    input [1:0] rs1, rs2, rd;  
    input we, rst, clk;  
    input [15:0] rdval;  
    output [15:0] rs1val, rs2val;
```

endmodule

- Warning: this code not tested, may contain typos, do not blindly trust!

Register File Interface (Verilog)

```
module regfile4(rs1, rs1val, rs2, rs2val, rd, rdval, we, rst, clk);
    parameter n = 1;
    input [1:0] rs1, rs2, rd;
    input we, rst, clk;
    input [n-1:0] rdval;
    output [n-1:0] rs1val, rs2val;
```

endmodule

- Warning: this code not tested, may contain typos, do not blindly trust!

Register File: Four Registers (Verilog)

```
module regfile4(rs1, rs1val, rs2, rs2val, rd, rdval, we, rst, clk);
  parameter n = 1;
  input [1:0] rs1, rs2, rd;
  input we, rst, clk;
  input [n-1:0] rdval;
  output [n-1:0] rs1val, rs2val;
  wire [n-1:0] r0v, r1v, r2v, r3v;

  Nbit_reg #(n) r0 (r0v, , , rst, clk);
  Nbit_reg #(n) r1 (r1v, , , rst, clk);
  Nbit_reg #(n) r2 (r2v, , , rst, clk);
  Nbit_reg #(n) r3 (r3v, , , rst, clk);

endmodule
```

- Warning: this code not tested, may contain typos, do not blindly trust!

Add a Read Port (Verilog)

```
module regfile4(rs1, rs1val, rs2, rs2val, rd, rdval, we, rst, clk);
    parameter n = 1;
    input [1:0] rs1, rs2, rd;
    input we, rst, clk;
    input [n-1:0] rdval;
    output [n-1:0] rs1val, rs2val;
    wire [n-1:0] r0v, r1v, r2v, r3v;

    Nbit_reg #(n) r0 (r0v, , , rst, clk);
    Nbit_reg #(n) r1 (r1v, , , rst, clk);
    Nbit_reg #(n) r2 (r2v, , , rst, clk);
    Nbit_reg #(n) r3 (r3v, , , rst, clk);
    Nbit_mux4to1 #(n) mux1 (rs1, r0v, r1v, r2v, r3v, rs1val);

endmodule
```

- Warning: this code not tested, may contain typos, do not blindly trust!

Add Another Read Port (Verilog)

```
module regfile4(rs1, rs1val, rs2, rs2val, rd, rdval, we, rst, clk);
    parameter n = 1;
    input [1:0] rs1, rs2, rd;
    input we, rst, clk;
    input [n-1:0] rdval;
    output [n-1:0] rs1val, rs2val;
    wire [n-1:0] r0v, r1v, r2v, r3v;

    Nbit_reg #(n) r0 (r0v,          ,          , rst, clk);
    Nbit_reg #(n) r1 (r1v,          ,          , rst, clk);
    Nbit_reg #(n) r2 (r2v,          ,          , rst, clk);
    Nbit_reg #(n) r3 (r3v,          ,          , rst, clk);
    Nbit_mux4to1 #(n) mux1 (rs1, r0v, r1v, r2v, r3v, rs1val);
    Nbit_mux4to1 #(n) mux2 (rs2, r0v, r1v, r2v, r3v, rs2val);
endmodule
```

- Warning: this code not tested, may contain typos, do not blindly trust!

Add a Write Port (Verilog)

```
module regfile4(rs1, rs1val, rs2, rs2val, rd, rdval, we, rst, clk);
    parameter n = 1;
    input [1:0] rs1, rs2, rd;
    input we, rst, clk;
    input [n-1:0] rdval;
    output [n-1:0] rs1val, rs2val;
    wire [n-1:0] r0v, r1v, r2v, r3v;
    wire [3:0] rd_select;
    decoder_2_to_4 dec (rd, rd_select);
    Nbit_reg #(n) r0 (r0v, rdval, rd_select[0] & we, rst, clk);
    Nbit_reg #(n) r1 (r1v, rdval, rd_select[1] & we, rst, clk);
    Nbit_reg #(n) r2 (r2v, rdval, rd_select[2] & we, rst, clk);
    Nbit_reg #(n) r3 (r3v, rdval, rd_select[3] & we, rst, clk);
    Nbit_mux4to1 #(n) mux1 (rs1, r0v, r1v, r2v, r3v, rs1val);
    Nbit_mux4to1 #(n) mux2 (rs2, r0v, r1v, r2v, r3v, rs2val);
endmodule
```

- Warning: this code not tested, may contain typos, do not blindly trust!


Final Register File (Verilog)

```
module regfile4(rs1, rs1val, rs2, rs2val, rd, rdval, we, rst, clk);
    parameter n = 1;
    input [1:0] rs1, rs2, rd;
    input we, rst, clk;
    input [n-1:0] rdval;
    output [n-1:0] rs1val, rs2val;
    wire [n-1:0] r0v, r1v, r2v, r3v;

    Nbit_reg #(n) r0 (r0v, rdval, (rd == 2'd0) & we, rst, clk);
    Nbit_reg #(n) r1 (r1v, rdval, (rd == 2'd1) & we, rst, clk);
    Nbit_reg #(n) r2 (r2v, rdval, (rd == 2'd2) & we, rst, clk);
    Nbit_reg #(n) r3 (r3v, rdval, (rd == 2'd3) & we, rst, clk);
    Nbit_mux4to1 #(n) mux1 (rs1, r0v, r1v, r2v, r3v, rs1val);
    Nbit_mux4to1 #(n) mux2 (rs2, r0v, r1v, r2v, r3v, rs2val);
endmodule
```

- Warning: this code not tested, may contain typos, do not blindly trust!


Another Useful Component: Memory

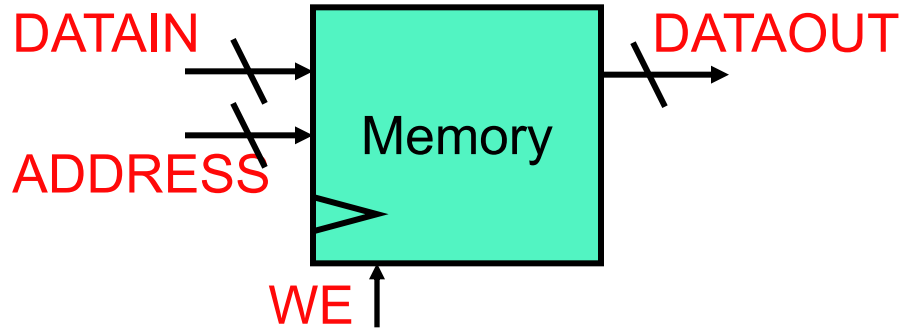

- Register file: M N-bit storage words
 - Few words (< 256), many ports, dedicated read and write ports
- **Memory**: M N-bit storage words, yet not a register file
 - Many words (> 1024), few ports (1, 2), shared read/write ports
- Leads to different implementation choices
 - Lots of circuit tricks and such
 - Larger memories typically only 6 transistors per bit
- In Verilog? We'll give you the code for large memories


Single-Cycle Performance

Single-Cycle Datapath Performance

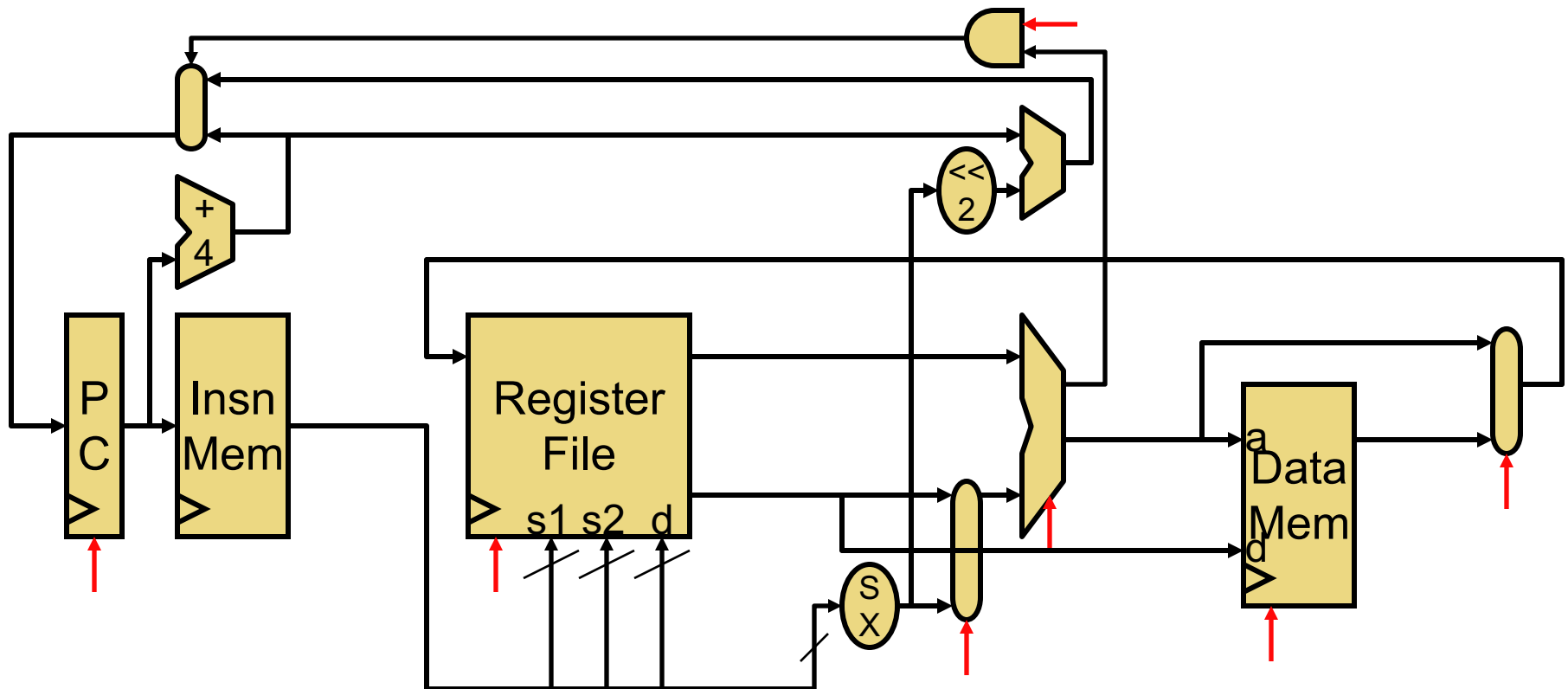


- One cycle per instruction (CPI)
- **Clock cycle time proportional to worst-case logic delay**
 - In this datapath: insn fetch, decode, register read, ALU, data memory access, write register
 - Can we do better?

Foreshadowing: Pipelined Datapath

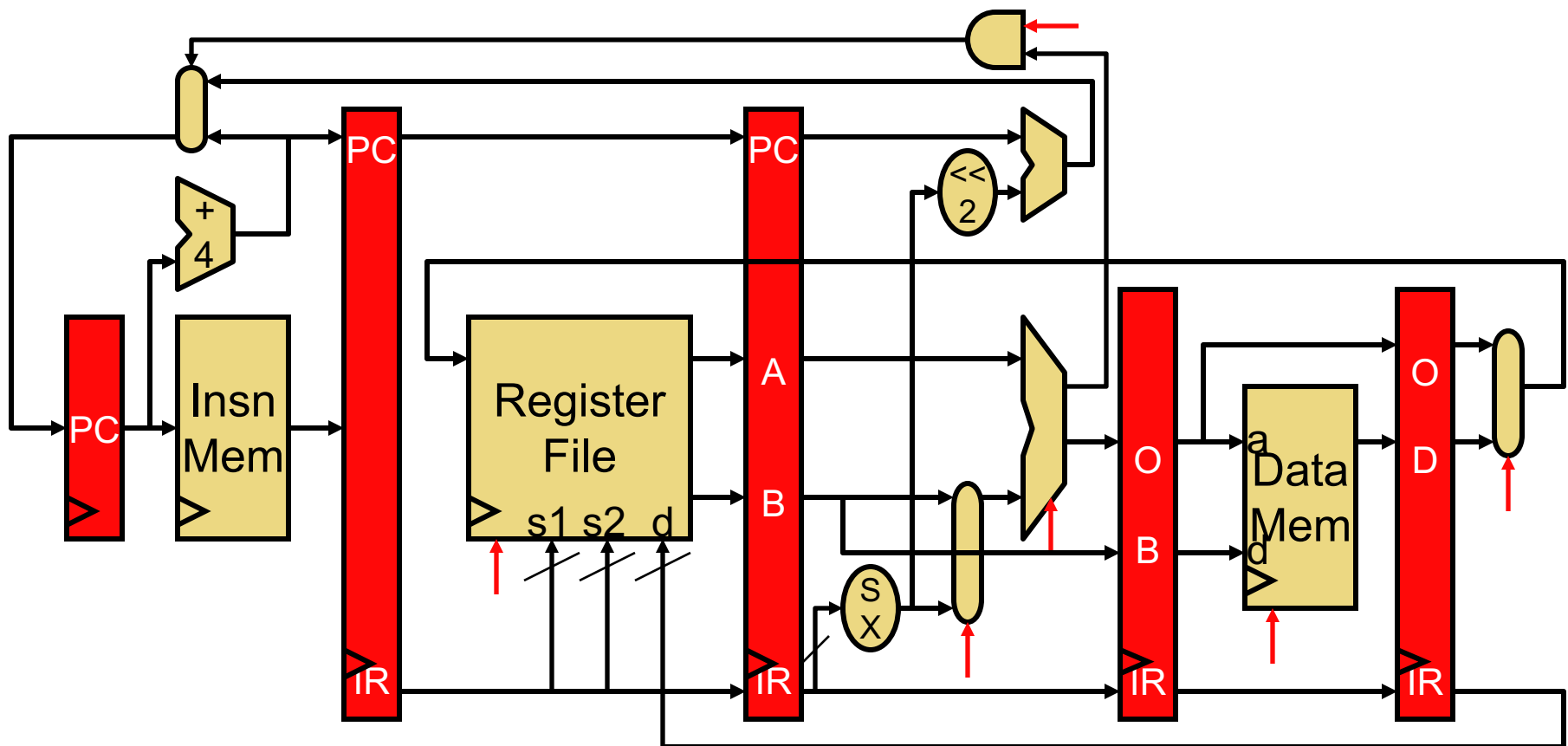

- Split datapath into multiple stages
 - Assembly line analogy
 - 5 stages results in up to 5x clock & performance improvement

Summary

 

- Overview of ISAs
- Datapath storage elements
- MIPS Datapath
- MIPS Control