

CMOS Analog Integrated Circuits: Models, Analysis, & Design

Dr. John Choma, Jr.
Professor of Electrical Engineering

University of Southern California
Department of Electrical Engineering-Electrophysics
University Park; Mail Code: 0271
Los Angeles, California 90089-0271

213-740-4692 [OFF]
626-915-7503 [HOME]
626-915-0944 [FAX]
johnc@almaak.usc.edu (E-MAIL)

EE448



MOS Circuit Level Models

Fall 2001

Lecture Overview

- Static Model
 - Cutoff Region
 - Ohmic (Triode) Region Model
 - Saturation Region Model
 - Subthreshold Model
- Short Channel Effects In Saturation
 - Channel Length Modulation
 - Substrate/Bulk Phenomena
 - Mobility Degradation
 - Carrier Velocity Saturation
- Small Signal Model In Saturation
 - Forward Transconductance
 - Bulk Transconductance
 - Capacitances
- Sample Circuit Analysis (Inverter)
 - Gain
 - Bandwidth

N-Channel MOSFET

  

$$I_s = I_d + I_g + I_b$$



$$I_g \approx 0$$

$$I_b \approx 0, \text{ for } V_{bs} < 0$$

$$I_s \approx I_d$$

$$V_{ds} = V_{gs} - V_{gd}$$

P-Channel MOSFET

  

$$I_s = I_d + I_g + I_b$$

$$I_g \approx 0$$

$$I_b \approx 0, \text{ for } V_{sb} < 0$$

$$I_s \approx I_d$$

$$V_{sd} = V_{sg} - V_{dg}$$

Characteristic Curves: Cutoff And Ohmic Regimes

- **Cutoff Regime:** $V_{gs} < V_{hn}$
 - $I_d = 0$
 - $V_{hn} \rightarrow$ Threshold Voltage, Function Of Bulk–Source Voltage

 - **Ohmic Regime:** $V_{gs} \geq V_{hn}$ and $V_{ds} < V_{gs} - V_{hn}$
 - $I_d = K_n \left(\frac{W}{L} \right) V_{ds} \left(V_{gs} - V_{hn} - \frac{V_{ds}}{2} \right)$
 - $K_n = \mu_n C_{ox} = \frac{\mu_n \epsilon_{ox}}{T_{ox}}$ (Hundreds Of $\mu\text{mhos/Volt}$)

 - **Comments**
 - W/L Is Gate–Channel Aspect Ratio, A Designable Parameter
 - $V_{ds} = V_{gs} - V_{gd} < V_{gs} - V_{hn}$ Implies $V_{gd} > V_{hn}$
 - Temperature Effects (Holes And Electrons): $\mu(T) \approx \mu(T_o) \left(\frac{T_o}{T} \right)^{3/2}$
 - Resistance For Small Drain–Source Voltage:
- $$\frac{\partial I_d}{\partial V_{ds}} \triangleq \frac{1}{R_{ds}} = K_n \left(\frac{W}{L} \right) \left(V_{gs} - V_{hn} - V_{ds} \right) = \frac{I_d}{V_{ds}} \left(\frac{V_{gs} - V_{hn} - V_{ds}}{V_{gs} - V_{hn} - \frac{V_{ds}}{2}} \right) \approx \frac{I_d}{V_{ds}}$$

Characteristic Curves: Saturated Regime

- **Saturation Regime:** $V_{gs} \geq V_{th} \quad \& \quad V_{ds} \geq V_{gs} - V_{th}$

- $I_d = \frac{K_n}{2} \left(\frac{W}{L} \right) (V_{gs} - V_{th})^2$

- $V_{dss} \triangleq V_{gs} - V_{th} \rightarrow$ Drain Saturation Voltage

- $I_{dss} = \frac{K_n}{2} \left(\frac{W}{L} \right) V_{dss}^2 \rightarrow$ Drain Saturation Current

- **Comments**


- Square Law Voltage–Controlled Current Source
- Drain Current Shows Negative Temperature Coefficient Because Of Its Proportionality To Mobility
- Differential Current Of Two Matched Devices Is Linear With Differential Gate–Source Voltage (V_{DM}) Provided Common Mode Gate–Source Voltage (V_{CM}) Is A Constant

$$I_{d1} - I_{d2} = \frac{K_n}{2} \left(\frac{W}{L} \right) \left[(V_{gs1} - V_{th})^2 - (V_{gs2} - V_{th})^2 \right]$$

$$I_{d1} - I_{d2} = K_n \left(\frac{W}{L} \right) \left(\frac{V_{gs1} + V_{gs2}}{2} - V_{th} \right) (V_{gs1} - V_{gs2})$$

$$I_{d1} - I_{d2} = K_n \left(\frac{W}{L} \right) (V_{CM} - V_{th}) V_{DM}$$

Simple Differential Pair

 

● Inputs

$$V_{gs1} = V_{CM} + \frac{V_{DM}}{2}$$

$$V_{gs2} = V_{CM} - \frac{V_{DM}}{2}$$

$$V_{gs1} + V_{gs2} = 2V_{CM}$$

$$V_{gs1} - V_{gs2} = V_{DM}$$

● Response

$$I_{d1} - I_{d2} = K_n \left(\frac{W}{L} \right) (V_{CM} - V_{th}) V_{DM}$$

$$V_o = R (I_{d1} - I_{d2}) = K_n R \left(\frac{W}{L} \right) (V_{CM} - V_{th}) V_{DM}$$

- Note Differential Output Current And Voltage Are Linear With Respect To Differential Input Voltage Without Invoking Small Signal Approximation

Characteristic Curves: Subthreshold Regime

- Subthreshold Regime: $V_{gs} < V_{th} + 2nV_T$ & $V_{ds} \leq 3V_T$

- ◆ $V_T = \frac{kT}{q} = 26 \text{ mV @ } 27^\circ\text{C}$


- ◆ $1.2 < n < 2.0$

- ◆
$$I_d = 2K_n \left(\frac{W}{L} \right) \left(\frac{nV_T}{\epsilon} \right)^2 e^{(V_{gs} - V_{th})/nV_T}$$

- Comments

- ◆ Bipolar Type I–V Action Indigenous To Subthreshold Regime
- ◆ Subthreshold Operation Corresponds To Gate–Channel Interface Potentials Lying Between One And Two Fermi Potentials
- ◆ Useful Only For Low Speed, Low Power Applications

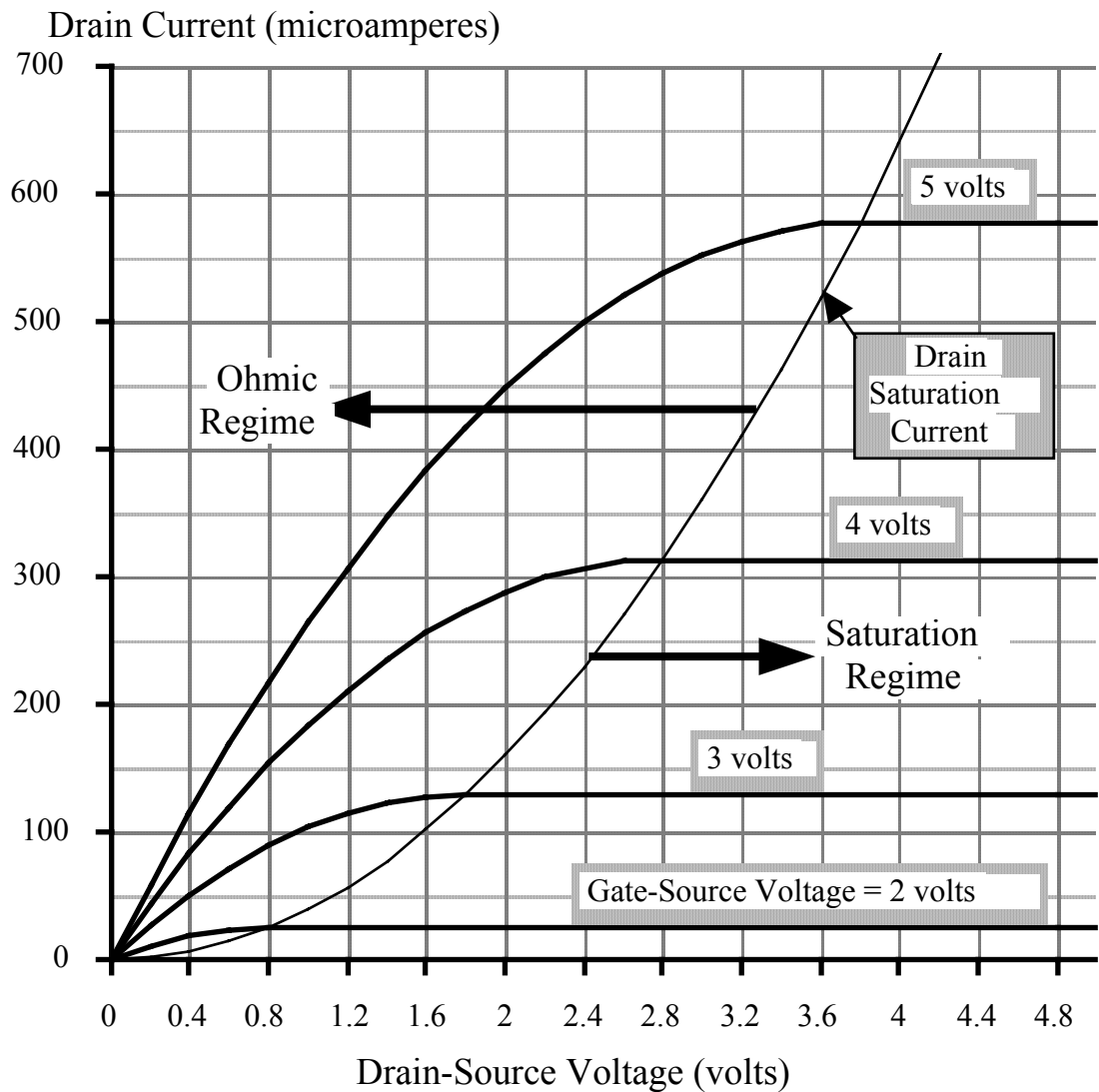
Sample Simplified MOS Static Characteristics



$$K_n \left(\frac{W}{L} \right) = 80 \mu\text{mho/volt}$$

$$V_{th} = 1.2 \text{ volts}$$

Cutoff Regime

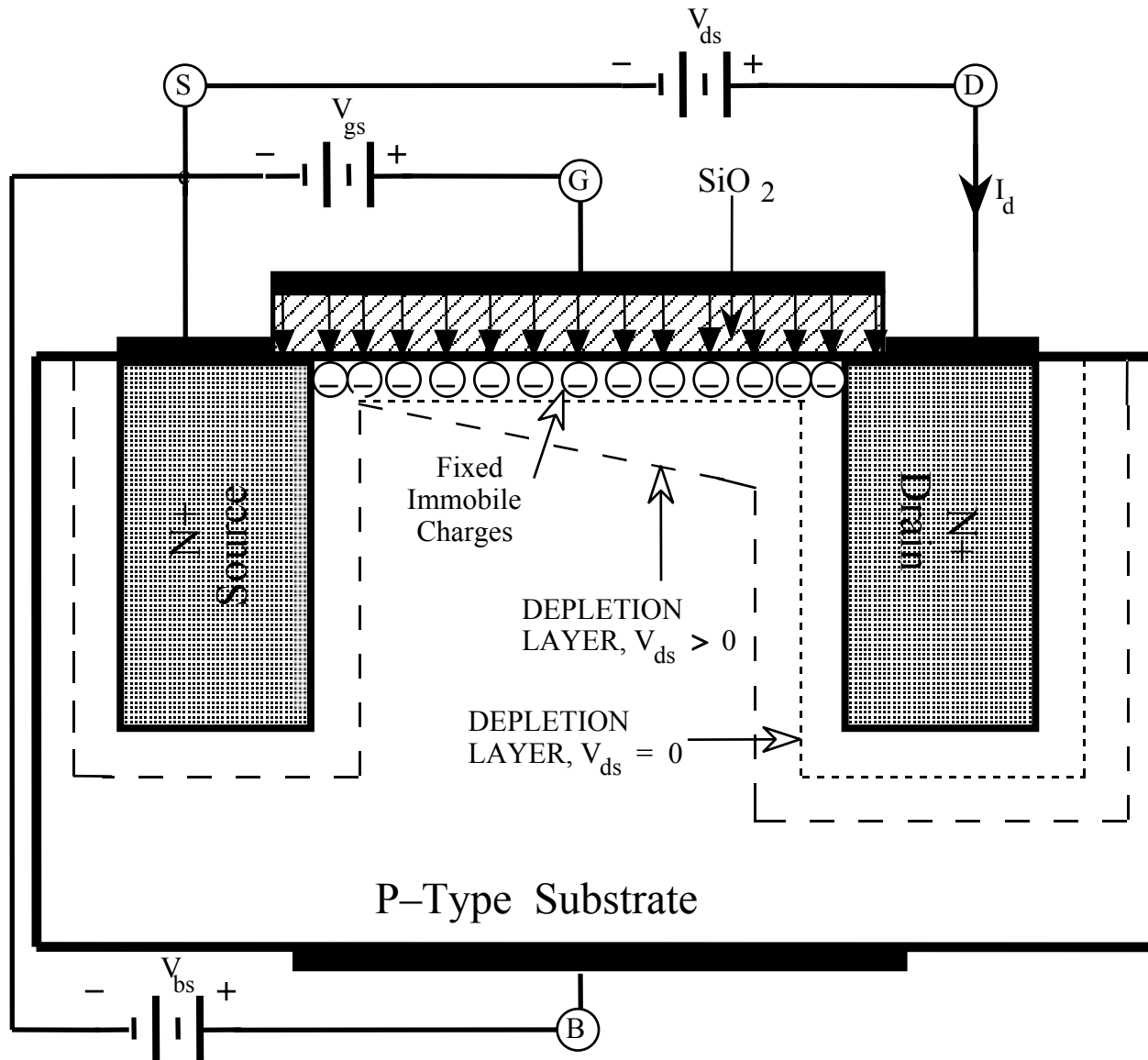

- Depletion

$$V_{ds} \geq 0$$

$$0 < V_{gs} < V_{th}$$

$$V_{bs} \leq 0$$


- Zero Current

- $V_{gs} = V_{ox} + V_y$

- $V_{ox} \rightarrow$ Voltage Across Oxide


- $V_y \rightarrow$ Interface Potential

Channel Inversion: Ohmic Regime

 

$$V_{gs} > V_{hn}$$

$$V_{ds} = 0$$

 


$$V_{gs} > V_{hn}$$

$$0 \leq V_{ds} \leq V_{gs} - V_{hn}$$

$$V_{gd} > V_{hn}$$

 Metal or Polysilicon	 Inversion Layer
 Silicon Dioxide	 Depletion

Channel Inversion: Saturation Regime

 

$$V_{gs} > V_{hn}$$

$$0 \leq V_{ds} = V_{gs} - V_{hn}$$

$$V_{gd} \leq V_{hn}$$


$$V_{gs} > V_{hn}$$

$$0 \leq V_{ds} > V_{gs} - V_{hn}$$

$$V_{gd} < V_{hn}$$

- Metal or Polysilicon
- Inversion Layer
- Silicon Dioxide
- Depletion

Channel Length Modulation

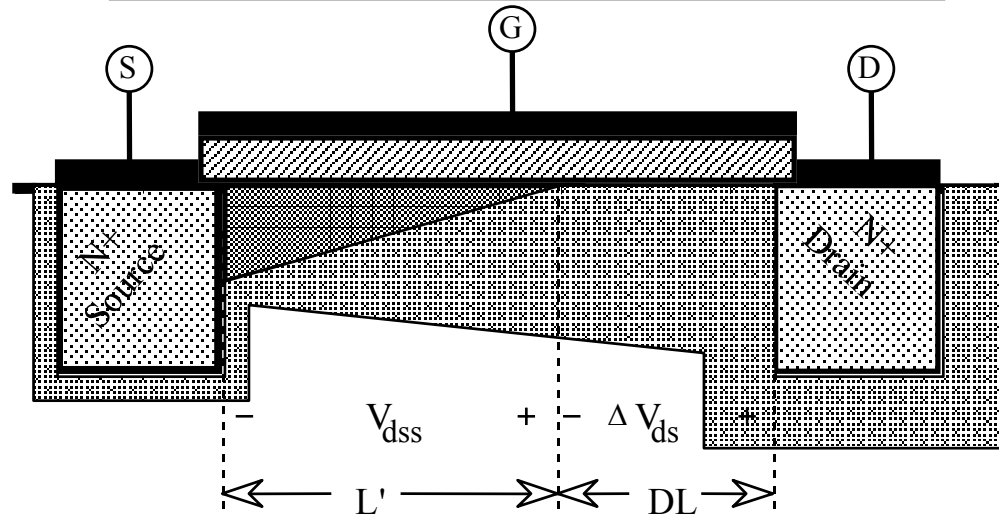

- Modified Saturation Regime Current

$$I_d \Big|_{V_{ds} > V_{dss}} = I_{dss} \left(\frac{L}{L - \Delta L} \right) = \frac{K_n}{2} \left(\frac{W}{L} \right) (V_{gs} - V_{th})^2 \left(1 + \frac{V_{ds} - V_{dss}}{V_\lambda} \right)$$

- Channel Modulation Voltage

$$V_\lambda = L \sqrt{\left(\frac{2qN_A}{\epsilon_s} \right) (V_{ds} - V_{dss} + V_j)}$$

$$V_{dss} = V_{gs} - V_{th}$$

$$V_j = \frac{kT}{q} \ln \frac{N_D N_A}{N_{iB}^2}$$

(Typically Under 20 Volts And As Small As 1/3 Volt For Deep Submicron MOSFETs)

Channel Length Modulation Parameters

● Modified Saturation Regime Current

$$I_d \Big|_{V_{ds} > V_{dss}} = I_{dss} \left(\frac{L}{L - \Delta L} \right) = \frac{K_n}{2} \left(\frac{W}{L} \right) (V_{gs} - V_{th})^2 \left(1 + \frac{V_{ds} - V_{dss}}{V_\lambda} \right)$$

$$V_{dss} = V_{gs} - V_{th}$$

$$V_j = \frac{kT}{q} \ln \frac{N_D N_A}{N_{iB}^2} \quad V_\lambda = L \sqrt{\left(\frac{2q N_A}{\epsilon_s} \right) (V_{ds} - V_{dss} + V_j)}$$

● Parameters

- N_A → Average Substrate Impurity Concentration
- ϵ_s → Dielectric Constant Of Silicon (1.05 pF/cm)
- q → Electronic Charge Magnitude
- V_1 → Channel Length Modulation Voltage
- V_j → Built In Substrate–Drain/Source Junction Potential

● Note

- Large Channel Length Reduces Channel Modulation
- Small Substrate Concentration Increases Channel Modulation

Substrate/Bulk Phenomena

● Effect On Threshold Voltage

$$\blacksquare I_d = \frac{K_n}{2} \left(\frac{W}{L} \right) (V_{gs} - V_{hnc})^2 \left(1 + \frac{V_{ds} - V_{dss}}{V_\lambda} \right)$$

$$\blacksquare V_h = V_{ho} + 2 \sqrt{V_\theta (V_F - V_T)} \left[\sqrt{\left(1 - \frac{V_{bs}}{2(V_F - V_T)} \right)} - 1 \right]$$

$$\blacksquare V_\theta = \frac{q N_A \epsilon_s}{C_{ox}^2} = q N_A \epsilon_s \left(\frac{T_{ox}}{\epsilon_{ox}} \right)^2 \quad (\text{High Hundreds Of } \mu\text{Volts})$$

$$\blacksquare V_F = V_T \ln \left(\frac{N_A}{N_{iB}} \right) \quad (\text{Few Tenths Of Volts})$$


● Parameters

- V_F → Fermi Potential; Renders Channel Surface Intrinsic
- N_{iB} → Intrinsic Carrier Concentration In Substrate
- ϵ_{ox} → Dielectric Constant Of Silicon Dioxide (345 fF/cm)

● Note

- Small Oxide Thickness Reduces Threshold Modulation
- Small Substrate Concentration Reduces Threshold Modulation

Threshold Voltage Modulation

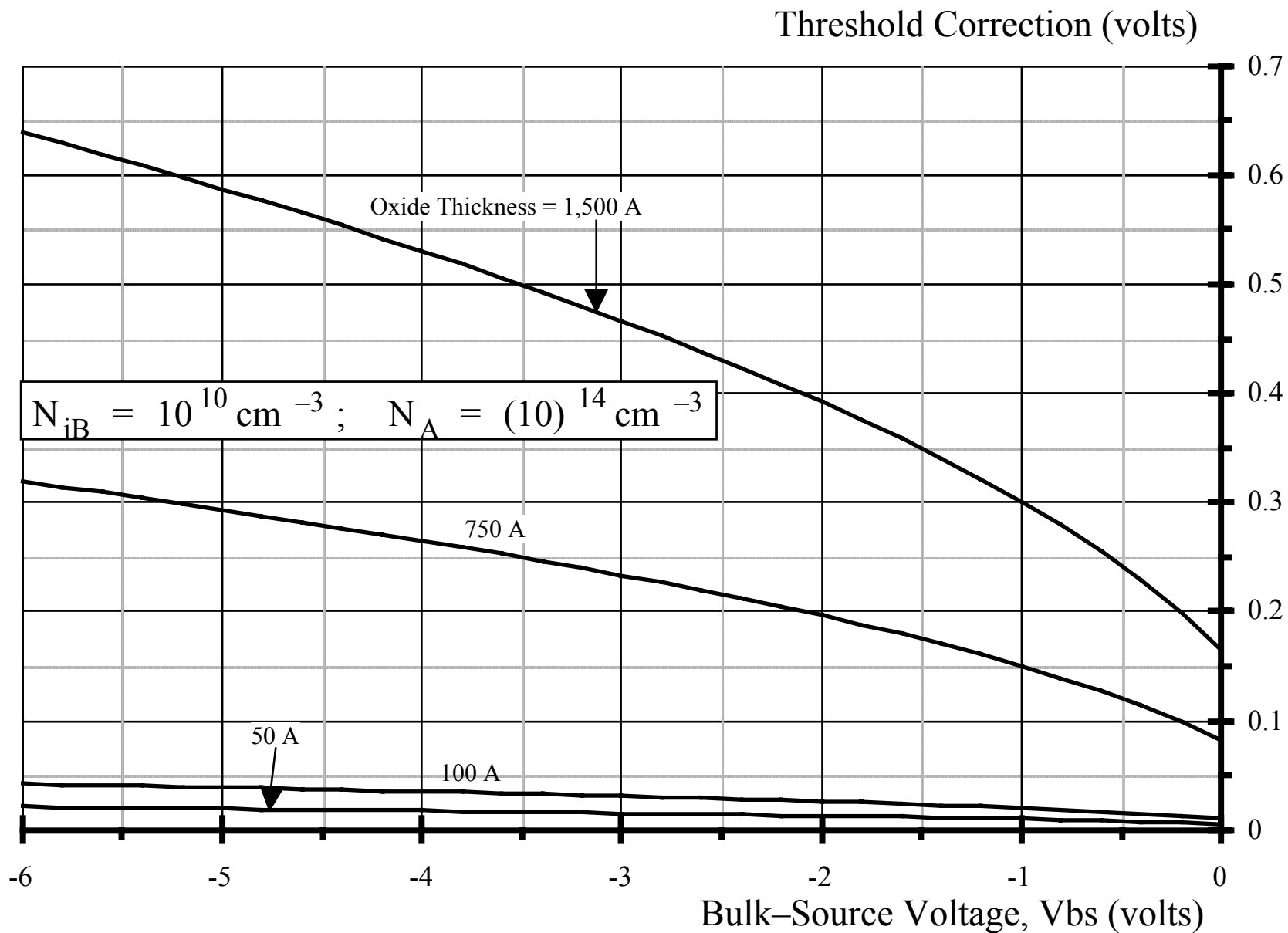

Mobility Degradation Due To Vertical Field

- Electric Field Problems

- Thin Oxide Layers Conduce Large Gate -To- Channel Fields For Even Small -To- Moderate Gate-Source Voltages
- These Enhanced Fields Impart Increasing Energies To Carriers, Thereby Causing More Carrier Collisions And Degraded Mobilities

- Mobility:
$$\mu_{\text{neff}} \approx \frac{\mu_n}{1 + \frac{V_{\text{gs}} - V_{\text{hnc}}}{V_E}}$$

$$V_E \approx (500)(10^6) T_{\text{ox}} \quad (\text{Low Hundreds Of Volts})$$

- Parameters

- μ_{neff} → Effective Carrier Mobility In Channel
- V_E → Vertical Field Degradation Voltage Parameter
- Crude One Dimension Approximation To Two Dimensional Problem
- T_{ox} in MKS Units Yields V_E In Volts

Impact Of Mobility Degradation

● Static Drain Current

- $K_n = \mu_n C_{ox} \rightarrow K_{neff} = \mu_{neff} C_{ox}$

- $$I_d = \frac{K_n}{2} \left(\frac{W}{L} \right) \left[\frac{\left(V_{gs} - V_{hnc} \right)^2 \left(1 + \frac{V_{ds} - V_{dss}}{V_\lambda} \right)}{\left(1 + \frac{V_{gs} - V_{hnc}}{V_E} \right)} \right]$$

● Other Effects

- Reduced Bandwidth And Increased Carrier Transit Time
- Smaller Current For Given Gate–Source Bias
- Reduced Forward Transconductance

Mobility Degradation Due To Lateral Field

● Electric Field Problems

- Short Channels Conduce Large Drain -To- Source Fields For Even Small -To- Moderate Drain–Source Voltages
- These Enhanced Fields Impart Increasing Energies To Carriers, Thereby Causing More Carrier Collisions And Degraded Mobilities
- At Very Large Horizontal Fields, Carrier Velocities Ultimately Saturate To A Value Of v_{sat} , Which Is About $0.1 \mu\text{m/pSEC}$
- Saturation Occurs When Horizontal Field, E_h , Equals Or Exceeds A Critical Value, E_c , Which Is About $5 \text{ V}/\mu\text{m}$

● Mobility And Field


- $$\mu_{\text{ne}} \approx \frac{\mu_n}{1 + \frac{E_h}{E_c}} = \frac{v_{\text{sat}}}{E_c + E_h}$$

- $$v_{\text{sat}} = \mu_n E_c$$

- $$v = \mu_{\text{ne}} E_h \approx \frac{\mu_n E_h}{1 + \frac{E_h}{E_c}}$$

- $$E_h \approx \frac{V_{\text{gs}} - V_{\text{hn}}}{L}$$

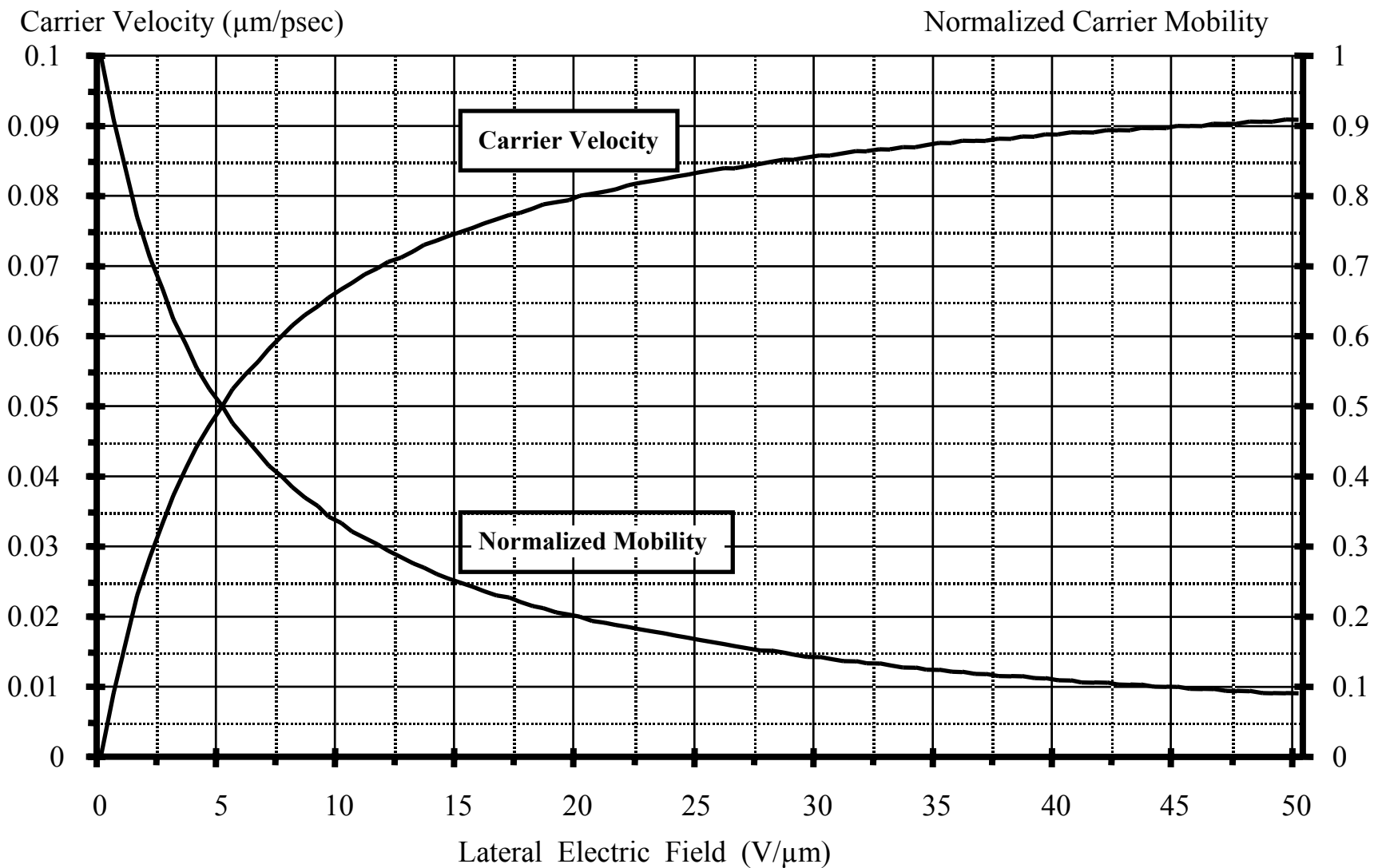Velocity – Mobility – Field Relationships



Mobility And Lateral Field

● Mobility And Field

$$\mu_{ne} \approx \frac{\mu_n}{1 + \frac{E_h}{E_c}} \approx \frac{\mu_n}{1 + \frac{V_{gs} - V_{hnc}}{L E_c}} = \frac{\mu_n}{1 + \frac{V_{dss}}{L E_c}}$$

$$E_h \approx \frac{V_{gs} - V_{hnc}}{L} = \frac{V_{dss}}{L}$$

● Electric Field Problems

- Crude Approximation For Horizontal Field, E_h
- Free Carriers Exist Only Over Channel Where Voltage With Respect To The Source Is At Most $V_{dss} = (V_{gs} - V_{hnc})$
- Channel Length, L , Should Be Effective Channel Length, L' , But This Shrinkage Is Already Accounted For By Channel Length Modulation Voltage Parameter, V_{λ}
- $L E_c$ Is About 1.75 Volts For $L = 0.35 \mu\text{m}$

Volt–Ampere Impact Of High Lateral Field

- Static Drain Current

- $K_n = \mu_n C_{ox} \rightarrow K_{neff} = \mu_{neff} C_{ox}$

- $$I_d = \frac{K_n}{2} \left(\frac{W}{L} \right) \frac{(V_{gs} - V_{hnc})^2 \left(1 + \frac{V_{ds} - V_{dss}}{V_\lambda} \right)}{1 + \frac{V_{gs} - V_{hnc}}{L E_c}}$$

- Very High Fields


- $V_{gs} - V_{hnc} \gg L E_c$

- $$I_d \approx \left(\frac{W C_{ox} v_{sat}}{2} \right) (V_{gs} - V_{hnc}) \left(1 + \frac{V_{ds} - V_{dss}}{V_1} \right)$$

- Comments

- Drain Current Scales Approximately With W, As Opposed To W/L
 - Drain Current Almost Linear W/R To Gate–Source Voltage


MOS Large Signal Model

 

DBD → Bulk-Drain Diode
DBS → Bulk-Source Diode

- C_{gd} → Gate-Drain Capacitance
- C_{gs} → Gate-Source Capacitance
- C_{db} → Drain-Bulk Capacitance
- C_{sb} → Source-Bulk Capacitance
- C_{old} → Drain Overlap Capacitance
- C_{ols} → Source Overlap Capacitance
- r_{dd} → Drain Ohmic Resistance
- r_{ss} → Source Ohmic Resistance
- r_{bb} → Bulk Ohmic Resistance
- r_{sb} → Bulk Spreading Resistance
- r_{db} → Bulk Spreading Resistance

Device Capacitances In Saturation

 

- C_{db} → Large (Hundreds Of fF)
- C_{sb} → Large (Hundreds Of fF)
- C_{gs} → Moderate (High Tens Of fF)
- C_{gd}, C_{old}, C_{ols} → Small (Tens Of fF)

$$C_{gd} + C_{old} \approx C_{old} = W L_d C_{ox}$$

$$C_{gs} = W L C_{ox} \left(\frac{2}{3} + \frac{L_d}{L} \right)$$

$$C_{db} = \frac{A_d C_{j0}}{\sqrt{1 - \frac{V_{bd}}{V_j}}}$$

$$C_{sb} = \frac{(A_s + W L) C_{j0}}{\sqrt{1 - \frac{V_{bs}}{V_j}}}$$


$$C_{ols} = W L_d C_{ox}$$

A_d → Drain-Bulk Junction Area

A_s → Source-Bulk Junction Area

C_{j0} → Zero Bias Depletion
Capacitance Density

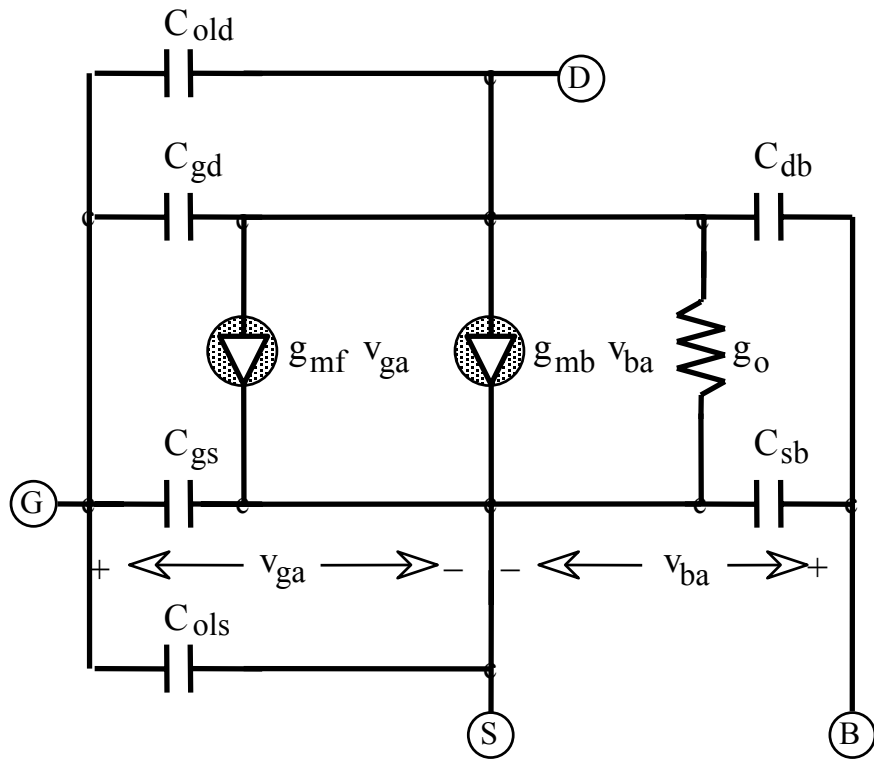Approximate (Long Channel) Small Signal Model



$$g_{mf} \triangleq \left. \frac{\partial I_d}{\partial V_{gs}} \right|_Q \approx \sqrt{2 K_n \left(\frac{W}{L} \right) I_{dQ}}$$

$$g_{mb} \triangleq \left. \frac{\partial I_d}{\partial V_{bs}} \right|_Q = \lambda_b g_{mf}$$

$$\lambda_b = \sqrt{\frac{V_{\theta}/2}{2(V_F - V_T) - V_{bsQ}}}$$

$$g_o \triangleq \left. \frac{\partial I_d}{\partial V_{ds}} \right|_Q \approx \frac{I_{dQ}}{V_{\lambda} + V_{ds} - V_{dss}}$$

● Assumptions

- All Series Ohmic Resistances Are Negligible
- Transistor Operates In Saturation Regime
- "Long Channel" Approximation Invoked For Static Drain Current
- Model To Be Used As A Precursor To Computer-Based Studies

Short Channel Small Signal Model

- Drain Current:
$$I_d = \frac{K_n}{2} \left(\frac{W}{L} \right) \frac{(V_{gs} - V_{hnc})^2 \left(1 + \frac{V_{ds} - V_{dss}}{V_\lambda} \right)}{1 + \frac{V_{gs} - V_{hnc}}{L E_c}}$$
- Intermediate Parameters:
$$f_\lambda = \frac{V_{ds} - V_{dss}}{V_\lambda} \quad f_c = \frac{V_{dss}}{L E_c}$$

$$g_{mf} = \sqrt{2 K_n \left(\frac{W}{L} \right) I_{dQ}}$$

$$\lambda_b = \sqrt{\frac{V_\theta / 2}{2(V_F - V_T) - V_{bsQ}}}$$
- Forward Transconductance:
$$g_{mfs} = g_{mf} \sqrt{\frac{1 + f_\lambda}{1 + f_c}} \left(1 - \frac{V_{dss} / 2 V_\lambda}{1 + f_\lambda} - \frac{f_c / 2}{1 + f_c} \right)$$
- Bulk Transconductance:
$$g_{mbs} = \lambda_b g_{mfs}$$
- Output Conductance:
$$g_o = \frac{I_{dQ}}{V_\lambda + V_{ds} - V_{dss}}$$

Hypothetical Device

- Physical Parameters

$$N_A = 5 (10)^{14} \text{ cm}^{-3}$$

$$N_D = 5 (10)^{20} \text{ cm}^{-3}$$

$$N_{iB} = (10)^{10} \text{ cm}^{-3}$$

$$\epsilon_s = 1.05 \text{ pF/cm}$$

$$\epsilon_{ox} = 345 \text{ fF/cm}$$

$$\mu_n = 400 \text{ cm}^2 / \text{ volt-sec}$$

$$E_c = 4 \text{ volts} / \mu\text{m}$$

- Device Parameters

$$T_{ox} = 50 \text{ Angstroms}$$

$$L = 0.35 \mu\text{m}$$

$$V_{hn} = 0.65 \text{ volts}$$

$$T = 300 \text{ } \mathcal{K}$$

$$W / L = 5$$

- Circuit Parameters

$$V_{ds} = 2 \text{ volts}$$

$$V_{gs} = 1.2 \text{ volts}$$

$$V_{bs} = -3 \text{ volts}$$

Static Performance

● Peripheral Calculations

$$V_F = 280.0 \text{ mV} \quad (\text{Fermi Potential})$$

$$V_j = 917.4 \text{ mV} \quad (\text{Junction Potential})$$

$$V_u = 176.4 \text{ } \mu\text{V} \quad (\text{Body Effect Potential})$$

$$V_{\text{hnc}} = 685.2 \text{ mV} \quad (\text{Compensated Threshold}) \quad \rightarrow \quad \Delta V_{\text{hn}} = 35.2 \text{ mV}$$

$$V_{\text{dss}} = 514.8 \text{ mV} \quad (\text{Drain Saturation Voltage})$$

$$V_{\lambda} = 669.7 \text{ mV} \quad (\text{Channel Length Voltage})$$

$$L E_c = 1.4 \text{ volts} \quad (\text{Lateral Field Voltage})$$

$$K_n = 276.0 \text{ } \mu\text{mho} / \text{volt} \quad (\text{Transconductance Parameter})$$

$$f_{\lambda} = 2.218 \quad (\text{Channel Length Parameter})$$

$$f_c = 0.368 \quad (\text{Lateral Field Parameter})$$

● Static Drain Current

- $I_d = 182.9 \text{ } \mu\text{A}$ (Long Channel Drain Current)


- $I_d = 430.2 \text{ } \mu\text{A}$ (Short Channel Drain Current)

- Note Short Channel -To- Long Channel Ratio of 2.35; Ratio Is Generally Between 1.5 And 3.0

Small Signal Parameters

- **Forward Transconductance**
 - $g_{mf} = 1.09 \text{ mmho}$ (Ignoring Short Channel Effects)
 - $g_{mf} = 1.25 \text{ mmho}$ (Incorporating Short Channel Effects)
 - Note Short Channel -To- Long Channel Ratio of 1.14; Ratio Is Generally Between 0.5 And 2.0
- **Bulk Transconductance**
 - $\lambda_b = 5.0 \times 10^{-10}$ (Bulk Parameter)
 - $g_{mb} = 6.25 \text{ } \mu\text{mho}$ (Incorporating Short Channel Effects)
 - Note Bulk Transconductance Is About 200 Times Smaller Than Forward Transconductance
- **Drain–Source Conductance**
 - $g_o = 199.7 \text{ } \mu\text{mho}$ (Incorporating Short Channel Effects)
 - Corresponds To Shunt Output Resistance Of About 5 K Ω
 - Mandates Conductance Enhancement Strategies When Designing High Performance Transconductors

Device Unity Gain Frequency

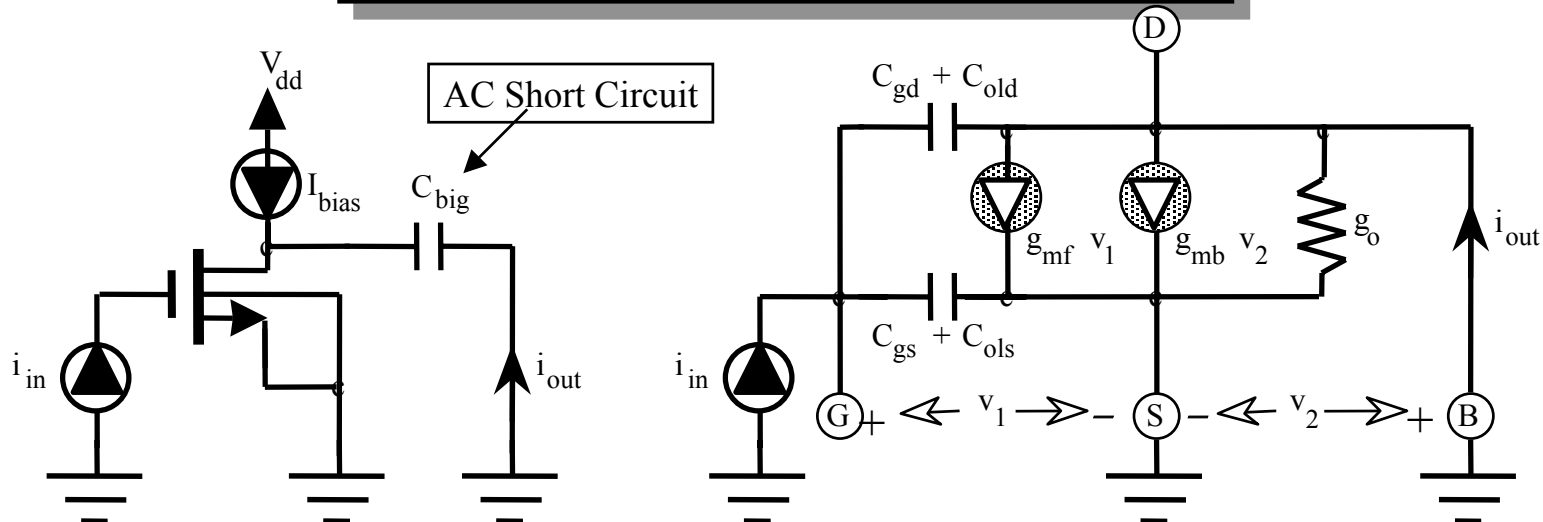


- $$\frac{i_{out}}{i_{in}} = \frac{g_{mf} - s(C_{gd} + C_{old})}{s(C_{gs} + C_{ols} + C_{gd} + C_{old})}$$

- $$\omega_T \approx \frac{g_{mf}}{C_{gs} + C_{ols} + C_{gd} + C_{old}} \approx \frac{\mu_n (V_{gs} - V_{thn})}{L^2 \left(\frac{2}{3} + \frac{3L_d}{L} \right)}$$

- ## Comments

- Unity Gain Frequency Is Good Device Figure Of Merit;
Crude Circuit Performance Figure Of Merit
 - Result Assumes $\omega_T C_{gd} \ll g_{mf}$


Common Source Inverter

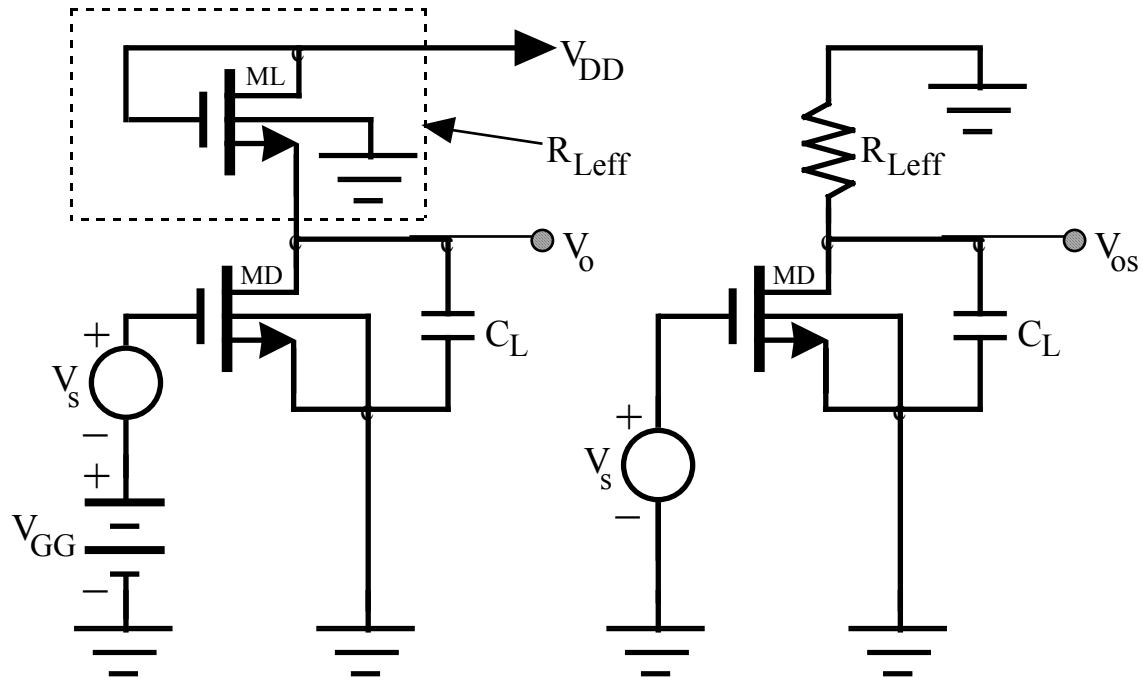

Schematic Diagram

AC Schematic Diagram

Inverter Load Resistance Calculations

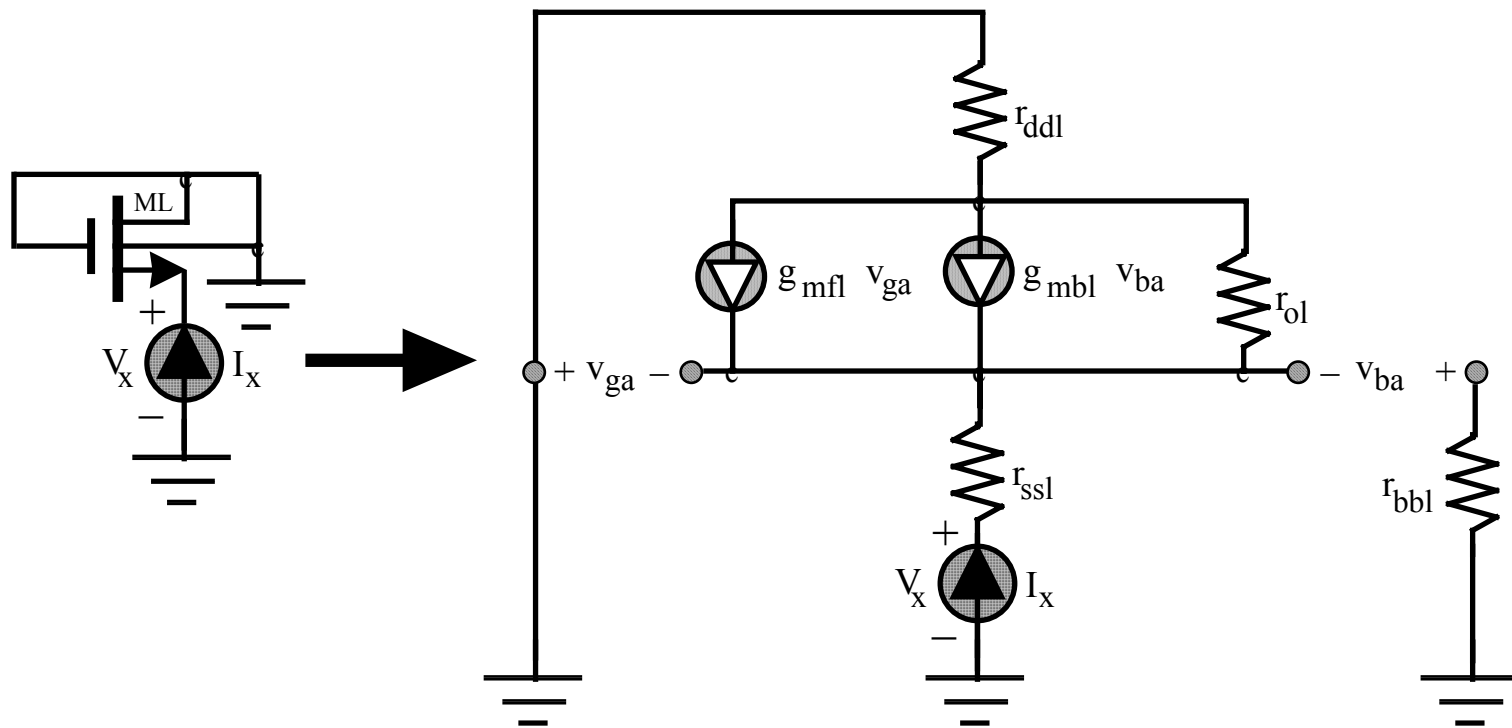


$$v_{ga} = v_{ba} = -V_x + r_{ssl} I_x$$

$$V_x = (r_{ssl} + r_{ddl}) I_x + r_{ol} (I_x + g_{mfl} v_{ga} + g_{mbl} v_{ba})$$

$$R_{Leff} \triangleq \frac{V_x}{I_x} = r_{ssl} + \frac{r_{ddl} + r_{ol}}{1 + (1 + \lambda_{bl}) g_{mfl} r_{ol}} \approx \frac{1}{(1 + \lambda_{bl}) g_{mfl}}$$


Inverter Gain Calculations

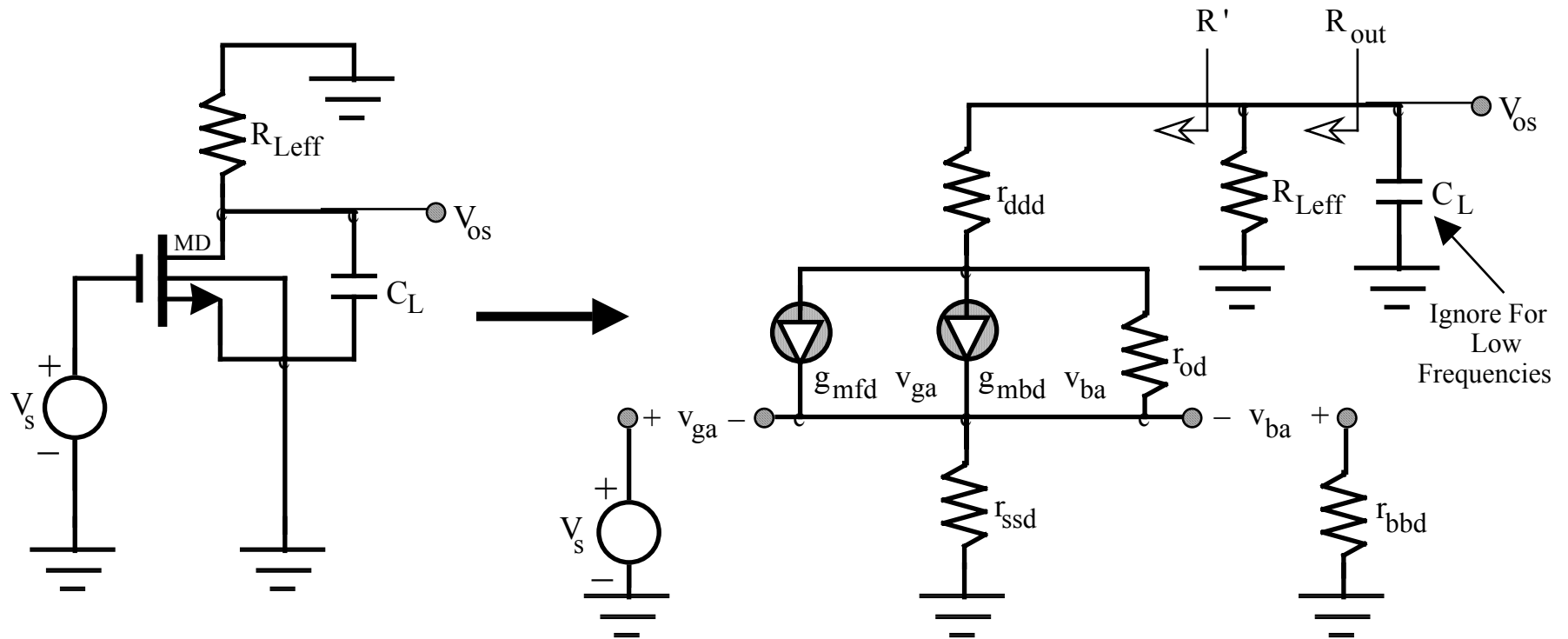

$$A_v = \frac{V_{os}}{V_s} = - \frac{g_{mfd} R_{Leff}}{1 + (1 + \lambda_{bd}) g_{mfd} r_{ssd} + \frac{R_{Leff} + r_{ddd} + r_{ssd}}{r_{od}}} \approx - g_{mfd} R_{Leff} \approx - \frac{g_{mfd}}{(1 + \lambda_{bl}) g_{mfl}}$$

$$A_v \approx - \left(\frac{1}{1 + \lambda_{bl}} \right) \sqrt{\frac{W_d/L}{W_1/L}}$$

Inverter Bandwidth Calculations

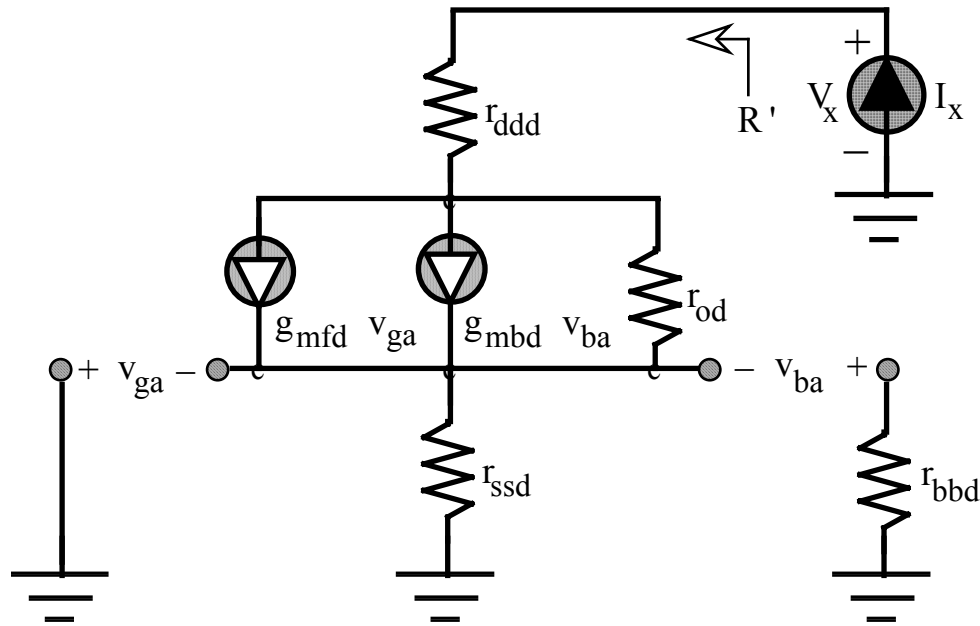

$$B_{3dB} = \frac{1}{R_{out} C_L} = \frac{1}{(R' \parallel R_{Leff}) C_L} \approx \frac{1}{R_{Leff} C_L}$$

$$R' = \frac{V_x}{I_x} = r_{ddd} + r_{ssd} + [1 + (1 + \lambda_{bl}) g_{mfd} r_{ssd}] r_{od}$$

$$B_{3dB} \approx \frac{1}{R_{Leff} C_L} \approx \frac{(1 + \lambda_{bl}) g_{mfl}}{C_L}$$

$$GBP \triangleq |A_v B_{3dB}| = \frac{g_{mfd}}{C_L}$$