

# Combinational Circuit Design

EE 200

Digital Logic Circuit Design

Dr. Muhamed Mudawar

King Fahd University of Petroleum and Minerals

# Presentation Outline

- ❖ How to Design a Combinational Circuit
- ❖ Designing a BCD to Excess-3 Code Converter
- ❖ Designing a BCD to 7-Segment Decoder
- ❖ Hierarchical Design
- ❖ Iterative Design

# Combinational Circuit

❖ A combinational circuit is a block of logic gates having:


$n$  inputs:  $x_1, x_2, \dots, x_n$

$m$  outputs:  $f_1, f_2, \dots, f_m$

❖ Each output is a function of the input variables

❖ Each output is determined from **present combination** of inputs

 ❖ Combination circuit performs operation specified by logic gates



# How to Design a Combinational Circuit

## 1. Specification

- ✧ Specify the inputs, outputs, and what the circuit should do

## 2. Formulation

- ✧ Convert the specification into truth tables or logic expressions for outputs

## 3. Logic Minimization

- ✧ Minimize the output functions using K-map or Boolean algebra

## 4. Technology Mapping

- ✧ Draw a logic diagram using ANDs, ORs, and inverters
- ✧ Map the logic diagram into the selected technology
- ✧ Considerations: cost, delays, fan-in, fan-out

## 5. Verification

- ✧ Verify the correctness of the design, either manually or using simulation

# Designing a BCD to Excess-3 Code Converter

## 1. Specification

- ✧ Convert BCD code to Excess-3 code
- ✧ Input: BCD code for decimal digits 0 to 9
- ✧ Output: Excess-3 code for digits 0 to 9

## 2. Formulation

- ✧ Done easily with a truth table
- ✧ BCD input:  $a, b, c, d$
- ✧ Excess-3 output:  $w, x, y, z$
- ✧ Output is don't care for 1010 to 1111

BCD				Excess-3			
a	b	c	d	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1010 to 1111				X	X	X	X

# Designing a BCD to Excess-3 Code Converter

## 3. Logic Minimization using K-maps

		K-map for w				K-map for x				K-map for y				K-map for z			
		00	01	11	10	00	01	11	10	00	01	11	10	00	01	11	10
ab	cd																
	00						1	1	1	1		1		1			1
01			1	1	1	1				1		1		1			1
11		X	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X
10		1	1	X	X		1	X	X	1		X	X	1		X	X

Minimal Sum-of-Product expressions:

$$w = a + bc + bd, \quad x = b'c + b'd + bc'd', \quad y = cd + c'd', \quad z = d'$$

Additional 3-Level Optimizations: extract common term  $(c + d)$


$$w = a + b(c + d), \quad x = b'(c + d) + b(c + d)', \quad y = cd + (c + d)'$$

# Designing a BCD to Excess-3 Code Converter
 
## 4. Technology Mapping

Draw a logic diagram using ANDs, ORs, and inverters


Other gates can be used, such as NAND, NOR, and XOR


 
### Using XOR gates

$$x = b'(c + d) + b(c + d)' = b \oplus (c + d)$$

$$y = cd + c'd' = (c \oplus d)' = c \oplus d'$$



# Designing a BCD to Excess-3 Code Converter

## 5. Verification

Can be done manually


Extract output functions from circuit diagram

Find the truth table of the circuit diagram

Match it against the specification truth table

Verification process can be automated

Using a simulator for complex designs

 

Truth Table of the  
Circuit Diagram



BCD				c+d	b(c+d)	Excess-3			
a	b	c	d			w	x	y	z
0	0	0	0	0	0	0	0	1	1
0	0	0	1	1	0	0	0	1	0
0	0	1	0	1	0	0	0	1	0
0	0	1	1	1	0	0	0	1	0
0	1	0	0	0	0	0	0	1	1
0	1	0	1	1	1	1	0	0	0
0	1	1	0	1	1	1	0	0	1
0	1	1	1	1	1	1	0	1	0
1	0	0	0	0	0	0	1	0	1
1	0	0	1	1	0	0	1	1	0



# BCD to 7-Segment Decoder

  
## ❖ Seven-Segment Display:

- ❖ Made of Seven segments: light-emitting diodes (LED)
- ❖ Found in electronic devices: such as clocks, calculators, etc.


 
## ❖ BCD to 7-Segment Decoder

- ❖ Accepts as input a BCD decimal digit (0 to 9)
- ❖ Generates output to the seven LED segments to display the BCD digit
- ❖ Each segment can be turned on or off separately




# Designing a BCD to 7-Segment Decoder

## 1. Specification:

- ✧ Input: 4-bit BCD ( $A, B, C, D$ )
- ✧ Output: 7-bit ( $a, b, c, d, e, f, g$ )
- ✧ Display should be OFF for Non-BCD input codes
 
## 2. Formulation

- ✧ Done with a truth table
- ✧ Output is zero for 1010 to 1111



## Truth Table

BCD input				7-Segment decoder						
A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1010 to 1111				0	0	0	0	0	0	0

# Designing a BCD to 7-Segment Decoder

## 3. Logic Minimization Using K-Maps

K-map for  $a$

CD \ AB	00	01	11	10
00	1		1	1
01		1	1	1
11				
10	1	1		

K-map for  $b$

CD \ AB	00	01	11	10
00	1	1	1	1
01	1		1	
11				
10	1	1		

K-map for  $c$

CD \ AB	00	01	11	10
00	1	1	1	
01	1	1	1	1
11				
10	1	1		

$$a = A'C + A'BD + AB'C' + B'C'D'$$

$$b = A'B' + B'C' + A'C'D' + A'CD$$

$$c = A'B + B'C' + A'D$$

Extracting common terms

$$\text{Let } T_1 = A'B, T_2 = B'C', T_3 = A'D$$

Optimized Logic Expressions

$$a = A'C + T_1 D + T_2 A + T_2 D'$$

$$b = A'B' + T_2 + A'C'D' + T_3 C$$

$$c = T_1 + T_2 + T_3$$

$T_1, T_2, T_3$  are shared gates

# Designing a BCD to 7-Segment Decoder

## 3. Logic Minimization Using K-Maps

K-map for  $d$

$CD \backslash AB$	00	01	11	10
00	1		1	1
01		1		1
11				
10	1	1		

K-map for  $e$

$CD \backslash AB$	00	01	11	10
00	1			1
01				1
11				
10	1			

K-map for  $f$

$CD \backslash AB$	00	01	11	10
00	1			
01	1	1		1
11				
10	1	1		

K-map for  $g$

$CD \backslash AB$	00	01	11	10
00			1	1
01	1	1		1
11				
10	1	1		

Common AND Terms

→ Shared Gates

$$T_4 = AB'C', T_5 = B'C'D'$$

$$T_6 = A'B'C, T_7 = A'CD'$$

$$T_8 = A'BC', T_9 = A'BD'$$

Optimized Logic Expressions

$$d = T_4 + T_5 + T_6 + T_7 + T_8 D$$

$$e = T_5 + T_7$$

$$f = T_4 + T_5 + T_8 + T_9$$

$$g = T_4 + T_6 + T_8 + T_9$$

# Designing a BCD to 7-Segment Decoder

## 4. Technology Mapping

Many Common AND terms:  $T_0$  thru  $T_9$

$$T_0 = A'C, T_1 = A'B, T_2 = B'C'$$

$$T_3 = A'D, T_4 = AB'C', T_5 = B'C'D'$$

$$T_6 = A'B'C, T_7 = A'CD'$$

$$T_8 = A'BC', T_9 = A'BD'$$

Optimized Logic Expressions

$$a = T_0 + T_1 D + T_4 + T_5$$

$$b = A'B' + T_2 + A'C'D' + T_3 C$$


$$c = T_1 + T_2 + T_3$$

$$d = T_4 + T_5 + T_6 + T_7 + T_8 D$$

$$e = T_5 + T_7$$

$$f = T_4 + T_5 + T_8 + T_9$$

$$g = T_4 + T_6 + T_8 + T_9$$

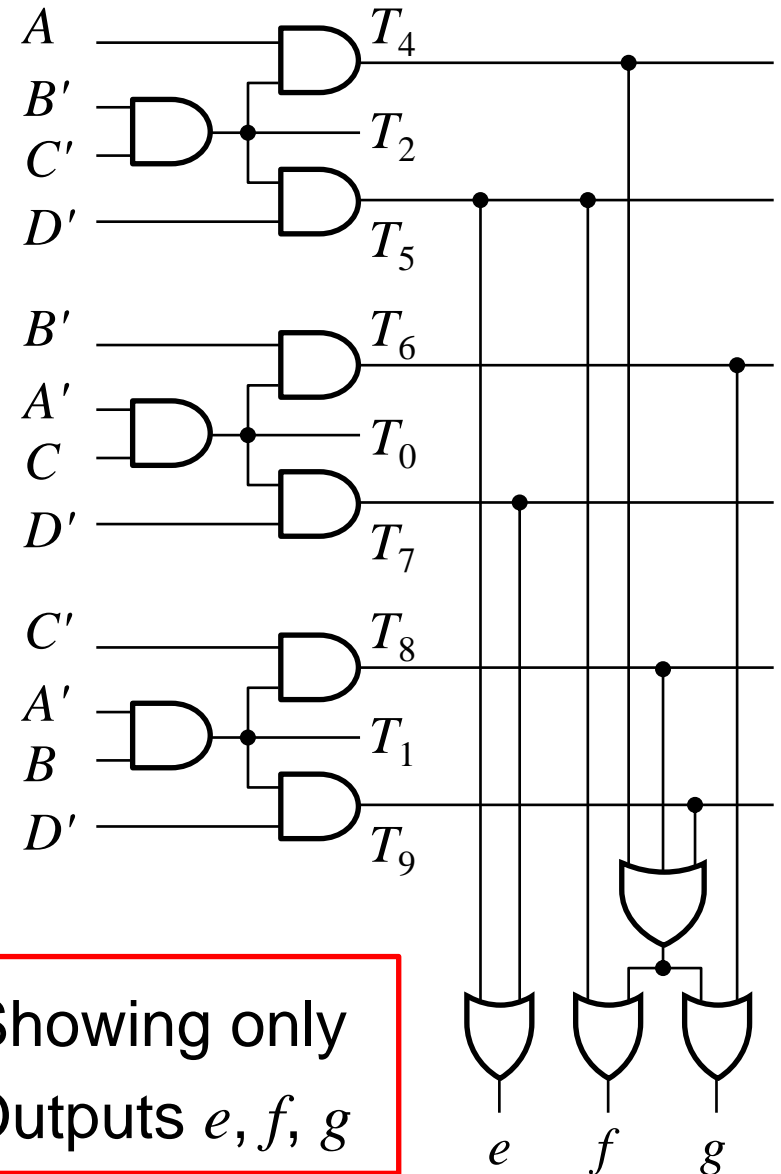

Showing only  
Outputs  $e, f, g$

# Verification Methods

## ❖ Manual Logic Analysis

- ✧ Find the logic expressions and truth table of the final circuit
- ✧ Compare the final circuit truth table against the specified truth table
- ✧ Compare the circuit output expressions against the specified expressions
- ✧ Tedious for large designs + Human Errors

## ❖ Simulation

- ✧ Simulate the final circuit, possibly written in HDL (such as Verilog)
- ✧ Write a test bench that automates the verification process
- ✧ Generate test cases for ALL possible inputs (exhaustive testing)
- ✧ Verify the output correctness for ALL input test cases
- ✧ Exhaustive testing can be very time consuming for many inputs

# Hierarchical Design

## ❖ Why Hierarchical Design?

To simplify the implementation of a complex circuit

## ❖ What is Hierarchical Design?

Decompose a complex circuit into smaller pieces called blocks

Decompose each block into even smaller blocks

Repeat as necessary until the blocks are small enough

Any block not decomposed is called a primitive block


The hierarchy is a tree of blocks at different levels

## ❖ The blocks are verified and well-document

## ❖ They are placed in a library for future use
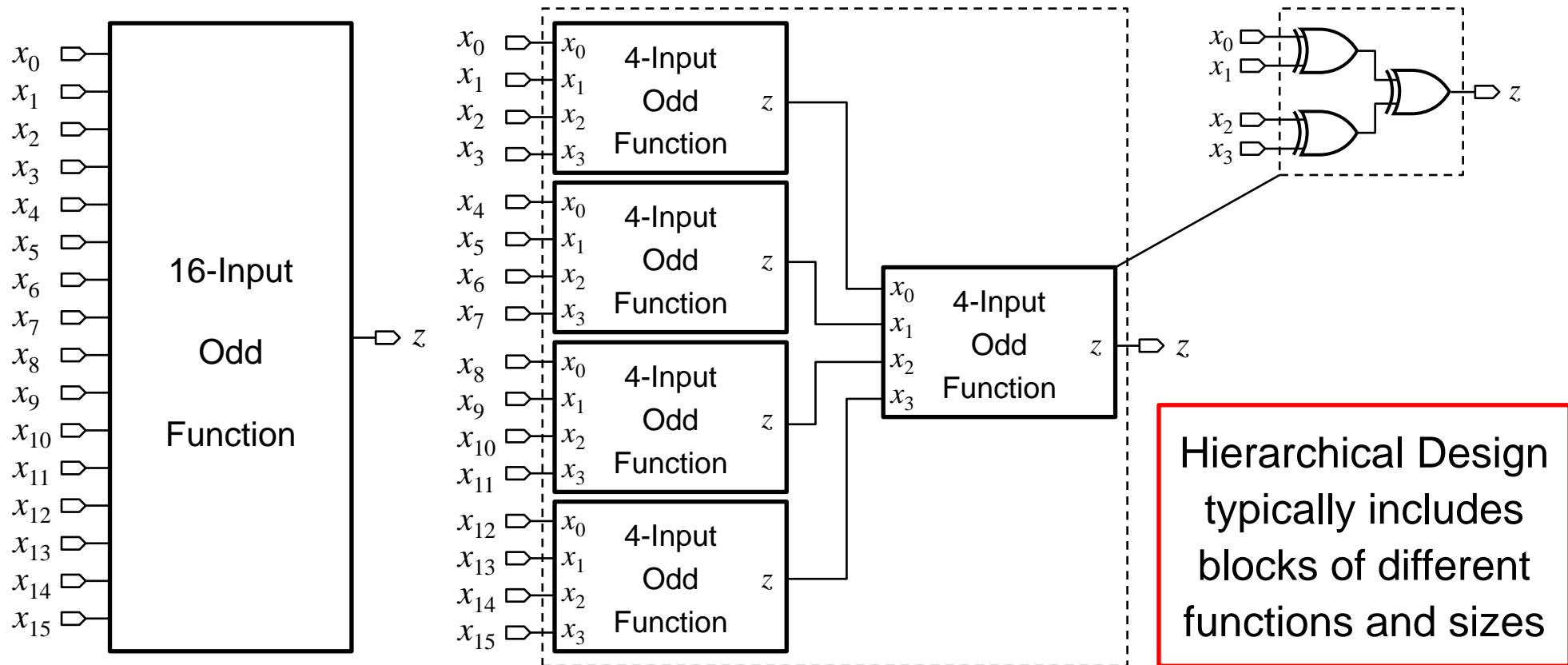
# Example of Hierarchical Design

- ❖ Top Level: 16-input odd function: 16 inputs, one output
  - ✧ Implemented using Five 4-input odd functions
- ❖ Second Level: 4-input odd function that uses three XOR gates



Hierarchical Design typically includes blocks of different functions and sizes




# Top-Down versus Bottom-Up Design

- ❖ A **top-down design** proceeds from a high-level specification to a more and more detailed design by decomposition and successive refinement
- ❖ A **bottom-up design** starts with detailed primitive blocks and combines them into larger and more complex functional blocks
- ❖ Design usually proceeds top-down to a known set of building blocks, ranging from complete processors to primitive logic gates
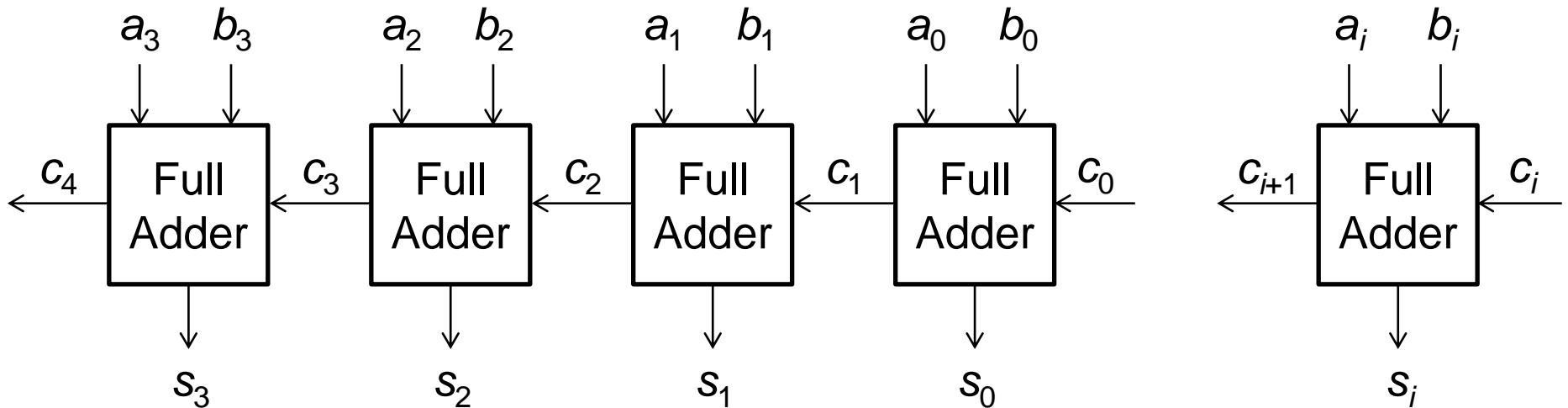
# Iterative Design

- ❖ Using **identical copies** of a smaller circuit to build a large circuit
- ❖ Example: Building a 4-bit adder using 4 copies of a full-adder
- ❖ The **cell** (iterative block) is a **full adder**  
Adds 3 bits:  $a_i, b_i, c_i$ , Computes: Sum  $s_i$  and Carry-out  $c_{i+1}$
- ❖ Carry-out of cell  $i$  becomes carry-in to cell  $(i+1)$



# Full Adder

❖ Full adder adds 3 bits: **a**, **b**, and **c**

❖ Two output bits:

1. Carry bit: **cout**

2. Sum bit: **sum**

❖ Sum bit is 1 if the number of 1's in the input is odd (odd function)

$$\text{sum} = (a \oplus b) \oplus c$$

❖ Carry bit is 1 if the number of 1's in the input is 2 or 3

$$\text{cout} = a \cdot b + (a \oplus b) \cdot c$$

**Truth Table**

a	b	c	cout	sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1