

---

# Combinational Logic Design with Verilog

---

ECE 152A – Winter 2012

# Reading Assignment

- Brown and Vranesic
  - 2 Introduction to Logic Circuits
    - 2.10 Introduction to Verilog
      - 2.10.1 Structural Specification of Logic Circuits
      - 2.10.2 Behavioral Specification of Logic Circuits
      - 2.10.3 How *Not* to Write Verilog Code

# Reading Assignment

- Brown and Vranesic (cont) *1<sup>st</sup> edition only!*
  - 4 Optimized Implementation of Logic Functions
    - 4.12 CAD Tools
      - 4.12.1 Logic Synthesis and Optimization
      - 4.12.2 Physical Design
      - 4.12.3 Timing Simulation
      - 4.12.4 Summary of Design Flow
      - 4.12.5 Examples of Circuits Synthesized from Verilog Code

# Programmable Logic

- Provides low cost and flexibility in a design
  - Replace multiple discrete gates with single device
  - Logical design can be changed by reprogramming the device
    - No change in board design
  - Logical design can be changed even after the part has been soldered onto the circuit board in modern, In-system programmable device
  - Inventory can focus on one part
    - Multiple uses of same device

# Programmable Logic

- Evolution of Programmable Logic
  - Both in time and complexity
  - ROM's and RAM's
    - Not strictly programmable logic, but useful in implementing combinational logic and state machines
  - PAL's
    - PAL's – Programmable Array Logic
    - PLA's – Programmable Logic Array
    - GAL's – Generic Logic Array

# Programmable Logic

- ❑ PLD's
  - Programmable Logic Device
    - ❑ PLDs are (in general) advanced PALs
- ❑ CPLD's
  - Complex Programmable Logic Device
    - ❑ Multiple PLDs on a single chip
- ❑ FPGA's
  - Field Programmable Gate Array

# Design Entry

- ❑ In previous examples, design entry is schematic based
  - TTL implementation using standard, discrete integrated circuits
  - PLD implementation using library of primitive elements
- ❑ Code based design entry uses a hardware description language (HDL) for design entry
  - Code is synthesized and implemented on a PLD

# Verilog Design

- Structural Verilog
  - Looks like the gate level implementation
    - Specify gates and interconnection
  - Text form of schematic
    - Referred to as “netlist”
  - Allows for “bottom – up” design
    - Begin with primitives, instantiate in larger blocks




# Verilog Design

- RTL (Register Transfer Level) Verilog
  - Allows for “top – down” design
  - No gate structure or interconnection specified
  - Synthesizable code (by definition)
    - Emphasis on synthesis, not simulation
      - vs. high level behavioral code and test benches
    - No timing specified in code
    - No initialization specified in code
      - Timing, stimulus, initialization, etc. generated in testbench (later)
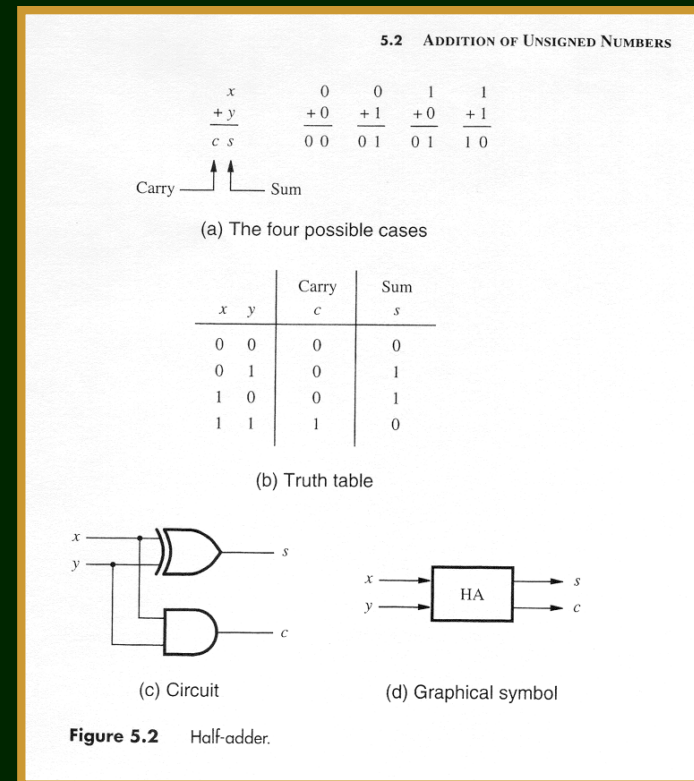
# Half Adder - Structural Verilog Design

- Recall Half Adder description from schematic based design example
  - Operation
  - Truth table
  - Circuit
  - Graphical symbol



# Verilog Syntax

- Modules are the basic unit of Verilog models
  - Functional Description
    - Unambiguously describes module's operation
      - Functional, i.e., without timing information
  - Input, Output and Bidirectional ports for interfaces
  - May include instantiations of other modules
    - Allows building of hierarchy

# Verilog Syntax

- Module declaration

- module ADD\_HALF (s,c,x,y);
  - Parameter list is I/O Ports

- Port declaration

- Can be input, output or inout (bidirectional)
  - output s,c;
  - input x,y;

# Verilog Syntax

- Declare nodes as wires or reg
  - Wires assigned to declaratively
  - Reg assigned to procedurally
    - More on this later
  - In a combinational circuit, all nodes can, but don't have to be, declared wires
    - Depends on how code is written
    - Node defaults to wire if not declared otherwise
    - wire s,c,x,y;

# Verilog Syntax

- Gates and interconnection
  - xor G1(s,x,y);
  - and G2(c,x,y);
    - Verilog gate level primitive
      - Gate name
    - Internal (local) name
      - Instance name
    - Parameter list
      - Output port, input port, input port...

# Gate Instantiation

- Verilog Gates
  - Note: *notif* and *bufif* are tri-state gates

Table A.2 Verilog gates.

Name	Description	Usage
and	$f = (a \cdot b \cdot \dots)$	<b>and</b> ( <i>f</i> , <i>a</i> , <i>b</i> , ...)
nand	$f = \overline{(a \cdot b \cdot \dots)}$	<b>nand</b> ( <i>f</i> , <i>a</i> , <i>b</i> , ...)
or	$f = (a + b + \dots)$	<b>or</b> ( <i>f</i> , <i>a</i> , <i>b</i> , ...)
nor	$f = \overline{(a + b + \dots)}$	<b>nor</b> ( <i>f</i> , <i>a</i> , <i>b</i> , ...)
xor	$f = (a \oplus b \oplus \dots)$	<b>xor</b> ( <i>f</i> , <i>a</i> , <i>b</i> , ...)
xnor	$f = (a \odot b \odot \dots)$	<b>xnor</b> ( <i>f</i> , <i>a</i> , <i>b</i> , ...)
not	$f = \bar{a}$	<b>not</b> ( <i>f</i> , <i>a</i> )
buf	$f = a$	<b>buf</b> ( <i>f</i> , <i>a</i> )
notif0	$f = (!e ? \bar{a} : 'bz)$	<b>notif0</b> ( <i>f</i> , <i>a</i> , <i>e</i> )
notif1	$f = (e ? \bar{a} : 'bz)$	<b>notif1</b> ( <i>f</i> , <i>a</i> , <i>e</i> )
bufif0	$f = (!e ? a : 'bz)$	<b>bufif0</b> ( <i>f</i> , <i>a</i> , <i>e</i> )
bufif1	$f = (e ? a : 'bz)$	<b>bufif1</b> ( <i>f</i> , <i>a</i> , <i>e</i> )

# Verilog Syntax

- Close the module definition with
  - endmodule
- Comments begin with //




# Half Adder - Structural Verilog Design

```
module ADD_HALF (s,c,x,y);  
  
    output s,c;  
    input x,y;  
  
    wire s,c,x,y;  
        // this line is optional since nodes default to wires  
  
    xor G1 (s,x,y); // instantiation of XOR gate  
    and G2 (c,x,y); // instantiation of AND gate  
  
endmodule
```


# Half Adder – PLD Implementation

## ■ Functional Simulation

 

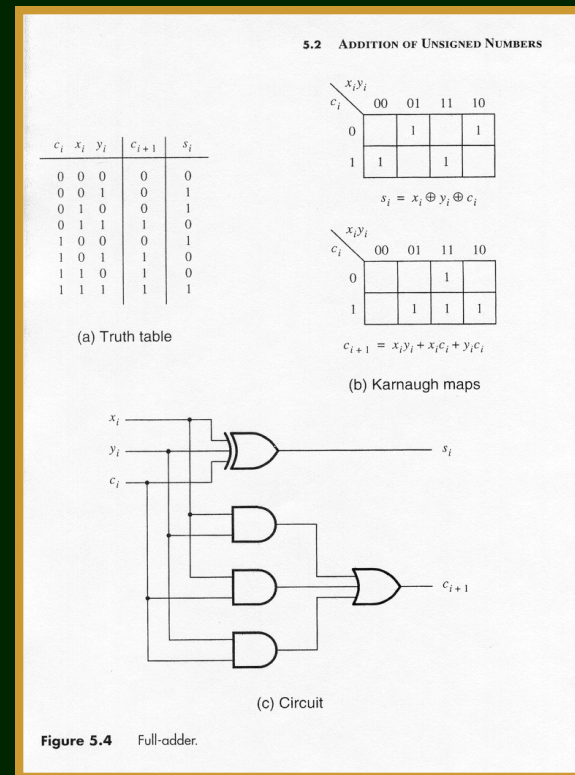
# Full Adder – Structural Verilog Design


- Recall Full Adder description from schematic based design example
  - Truth table
  - Karnaugh maps
  - Circuit



# Full Adder from 2 Half Adders

 

(a) Block diagram

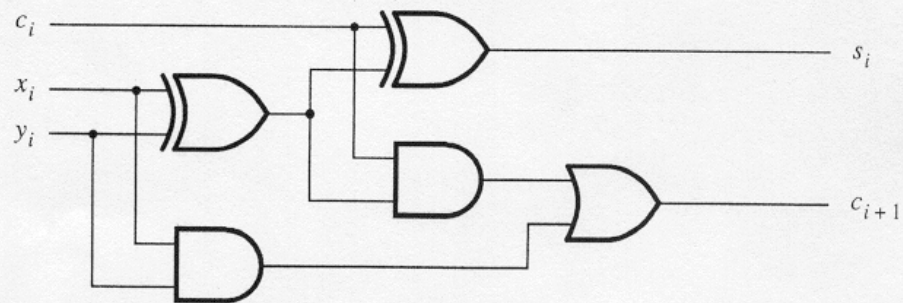

(b) Detailed diagram


**Figure 5.5** A decomposed implementation of the full-adder circuit.

# Full Adder – Structural Verilog Design

```
module ADD_FULL (s,cout,x,y,cin);  
  
    output s,cout;  
    input x,y,cin;  
  
    //internal nodes also declared as wires  
    wire cin,x,y,s,cout,s1,c1,c2;  
  
    ADD_HALF HA1(s1,c1,x,y);  
    ADD_HALF HA2(s,c2,cin,s1);  
    or (cout,c1,c2);  
  
endmodule
```

# Full Adder – PLD Implementation

## ■ Functional Simulation

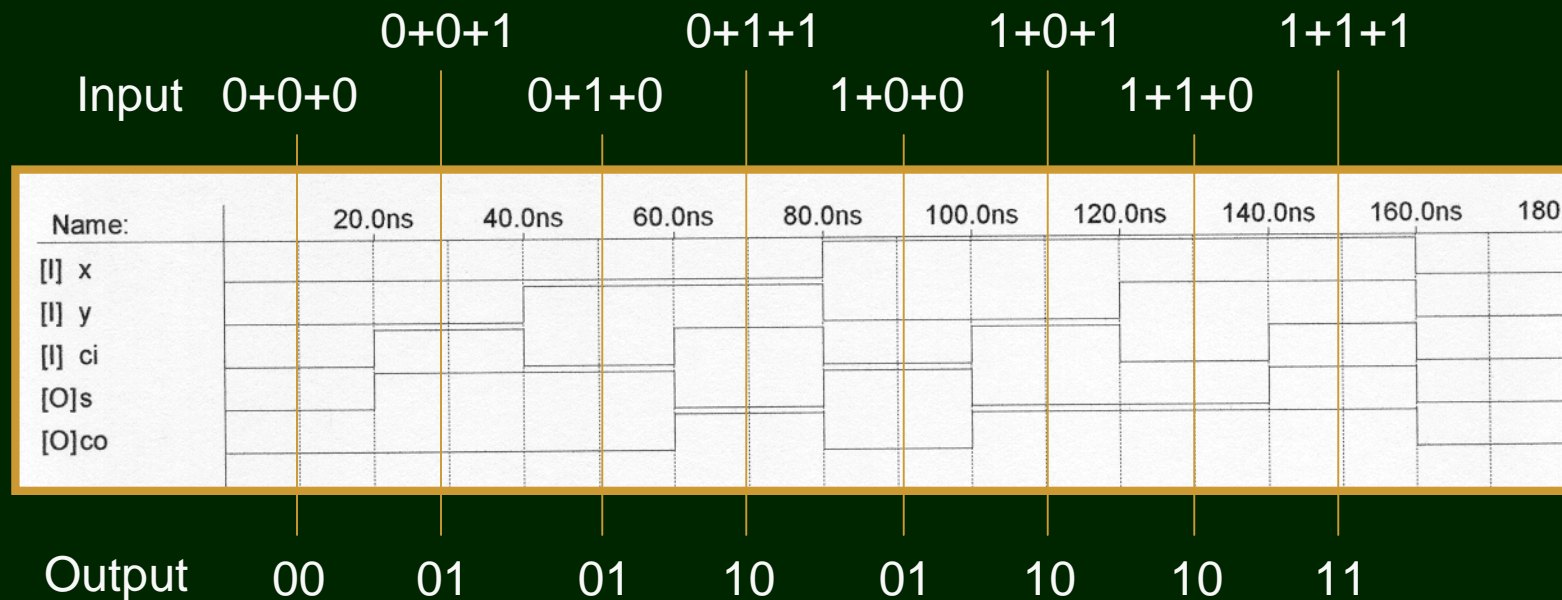

# Verilog Operators

- The Verilog language includes a large number of logical and arithmetic operators
  - Bit length column indicates width of result

**Table A.1** Verilog operators and bit lengths.

Category	Examples	Bit Length
Bitwise	$\sim A$ , $+A$ , $-A$ $A \& B$ , $A   B$ , $A \sim^{\wedge} B$ , $A \sim^{\sim} B$	$L(A)$ $\text{MAX}(L(A), L(B))$
Logical	$!A$ , $A \&\&B$ , $A    B$	1 bit
Reduction	$\&A$ , $\sim \&A$ , $ A$ , $\sim  A$ , $\sim^{\wedge} A$ , $\sim^{\sim} A$	1 bit
Relational	$A == B$ , $A != B$ , $A > B$ , $A < B$ $A >= B$ , $A <= B$ $A === B$ , $A! == B$	1 bit
Arithmetic	$A + B$ , $A - B$ , $A * B$ , $A / B$ $A \% B$	$\text{MAX}(L(A), L(B))$
Shift	$A << B$ , $A >> B$	$L(A)$
Concatenate	$\{A, \dots, B\}$	$L(A) + \dots + L(B)$
Replication	$\{B\{A\}\}$	$B * L(A)$
Condition	$A ? B : C$	$\text{MAX}(L(B), L(C))$

# Behavioral Specification of Logic Circuits

- Continuous Assignment Operator
  - assign sum = a ^ b;
    - “Assign” to a wire (generated declaratively)
    - Equivalent to
      - xor (sum,a,b);
  - Continuous and concurrent with other wire assignment operations
    - If a or b changes, sum changes accordingly
    - All wire assignment operations occur concurrently
      - Order not specified (or possible)



# Full Adder from Logical Operations

```
module ADD_FULL_RTL (sum,cout,x,y,cin);  
  
    output sum,cout;  
    input x,y,cin;  
  
    //declaration for continuous assignment  
    wire cin,x,y,sum,cout;  
  
    //logical assignment  
    assign sum = x ^ y ^ cin;  
    assign cout = x & y | x & cin | y & cin;  
  
endmodule
```

# Full Adder from Arithmetic Operations

```
module ADD_FULL_RTL (sum,cout,x,y,cin);
```

```
    output sum,cout;
```

```
    input x,y,cin;
```

```
    //declaration for continuous assignment
```

```
    wire cin,x,y,sum,cout;
```

```
    // concatenation operator and addition
```

```
    assign {cout, sum} = x + y + cin;
```

```
endmodule
```

# Procedural Verilog Statements

- Recall:
  - Wires assigned to declaratively
    - Continuous / concurrent assignment
  - Reg “variables” assigned to procedurally
    - Value is “registered” until next procedural assignment
      - Continuous assignment (wires) occurs immediately on input change
    - Enables clocked (synchronous) timing

# Procedural Verilog Statements

- The “always” block
  - Syntax is “always at the occurrence (@) of any event on the *sensitivity list*, execute the statements inside the block (in order)”

```
always @ (x or y or cin)  
{cout, sum} = x + y + cin;
```

# RTL Design of Full Adder


```
module ADD_FULL_RTL (sum,cout,x,y,cin);  
  
    output sum,cout;  
    input x,y,cin;  
  
    //declaration for behavioral model  
    wire cin,x,y;  
    reg sum,cout;  
  
    // behavioral specification  
    always @ (x or y or cin)  
        {cout, sum} = x + y + cin;  
  
endmodule
```

# Two-bit, Ripple Carry Adder – Structural Verilog

```
module TWO_BIT_ADD (S,X,Y,cin,cout);  
  
    input cin;  
    input [1:0]X,Y; // vectored input  
    output [1:0]S; // and output signals  
    output cout;  
  
    wire cinternal;  
  
    ADD_FULL AF0(S[0],cinternal,X[0],Y[0],cin);  
    ADD_FULL AF1(S[1],cout,X[1],Y[1],cinternal);  
  
endmodule
```
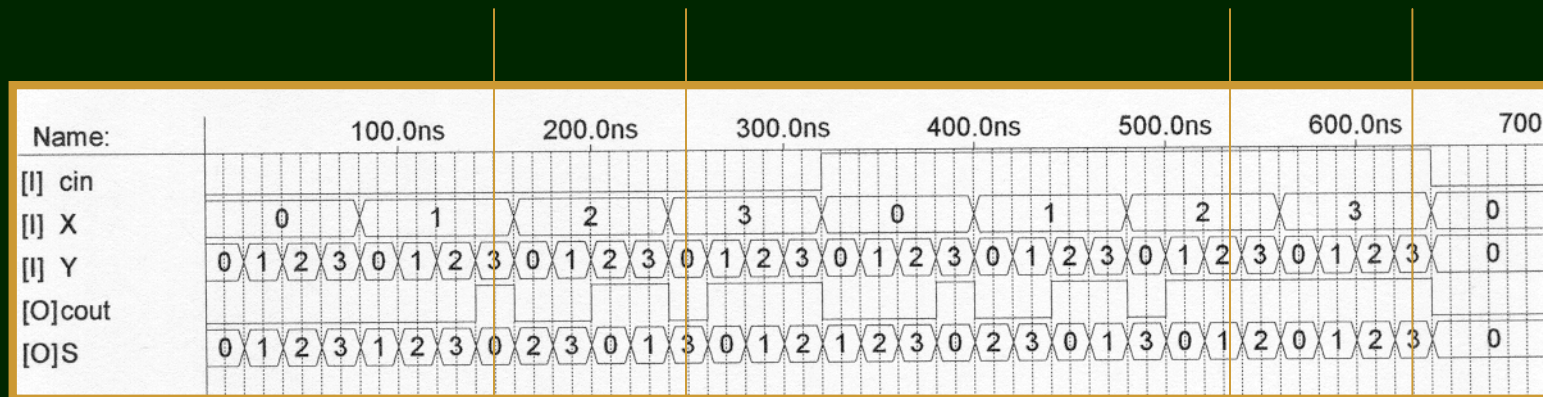
# Two-bit, Ripple Carry Adder – PLD Implementation

- Functional Simulation
  - Base-4 Bus Representation of X, Y and Sum



$$0+1+3 = 4 = 10_4 \rightarrow$$

$$1+2+2 = 5 = 11_4 \rightarrow$$

$$0+3+0 = 3 = 03_4 \rightarrow$$

$$1+3+3 = 7 = 13_4 \rightarrow$$

# Verilog Test Bench

- ❑ Device Under Test (DUT)
  - Circuit being designed/developed
    - ❑ Full adder for this example
- ❑ Testbench
  - Provides stimulus to DUT
    - ❑ Like test equipment on a bench
- ❑ Instantiate DUT in testbench
  - Generate all signals in testbench
  - No I/O (parameter list) in testbench



# Full Adder Testbench Example

```
module ADDFULL_TB;

    reg a,b,ci;
    wire sum,co;

    initial begin
        a = 0;
        b = 0;
        ci = 0;
    end

    always begin
        #5 a = ~a;
    end

    always begin
        #10 b = ~b;
    end

    always begin
        #20 ci = ~ci;
    end

    ADD_FULL AF1(sum,co,a,b,ci);

endmodule
```