

# Physics 1022

Fall 2011, Ch 31, 32

## Chapter 31. Current and Resistance

### Topics:

- Conductivity and Resistivity
- Resistance and Ohm's Law

## Chapter 32. Simple circuits

- Capacitors in series and parallel
- Resistors in series and parallel
- Kirchhoff's Rules

## ConceptTest 1


## Electric Current

Compare the currents  $I_1$  and  $I_2$ .

1.  $I_1 > I_2$


2.  $I_1 = I_2$

3.  $I_1 < I_2$

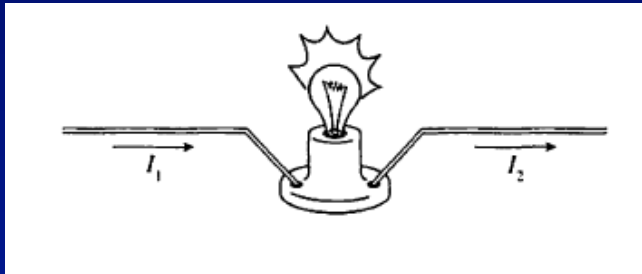

PHYS 1022: Chap. 31-32, Pg 3

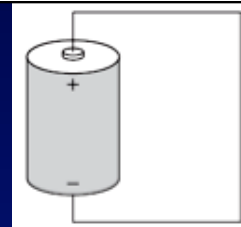Consider a battery with a wire connecting its terminals.



- In which direction (CW or CCW) does an electron travel through the wire?
- In which direction (CW or CCW) does an electron travel through the wire?
- How does an electron's potential energy change as it moves through the wire?
- What happened to that energy? Where did it come from, or where did it go?

PHYS 1022: Chap. 31-32, Pg 4

# Resistance and Resistivity

*New Topic*

PHYS 1022: Chap. 31-32, Pg 5

## Resistivity

- The electric field is directly proportional to the current density in the wire.
- $\rho$  is called **resistivity**, R is the **resistance**
  - a measure of how hard a charge can move in a material
- SI unit:  $V \cdot m / A = \Omega \cdot m$

$$\vec{E} = \rho \vec{J}$$

$$V = RI$$

Table 25.1 Resistivities at Room Temperature (20°C)

	Substance	$\rho (\Omega \cdot m)$	Substance	$\rho (\Omega \cdot m)$
<i>Conductors</i>	<i>Semiconductors</i>			
	Metals:		Pure carbon (graphite)	$3.5 \times 10^{-5}$
	Silver	$1.47 \times 10^{-8}$	Pure germanium	0.60
	Copper	$1.72 \times 10^{-8}$	Pure silicon	2300
	Gold	$2.44 \times 10^{-8}$	<i>Insulators</i>	
	Aluminum	$2.75 \times 10^{-8}$	Amber	$5 \times 10^{14}$
	Tungsten	$5.25 \times 10^{-8}$	Glass	$10^{10} - 10^{14}$
	Steel	$20 \times 10^{-8}$	Lucite	$> 10^{13}$
	Lead	$22 \times 10^{-8}$	Mica	$10^{11} - 10^{15}$
	Mercury	$95 \times 10^{-8}$	Quartz (fused)	$75 \times 10^{16}$
Alloys:	Manganin (Cu 84%, Mn 12%, Ni 4%)	$44 \times 10^{-8}$	Sulfur	$10^{15}$
	Constantan (Cu 60%, Ni 40%)	$49 \times 10^{-8}$	Teflon	$> 10^{13}$
	Nichrome	$100 \times 10^{-8}$	Wood	$10^8 - 10^{11}$

Copyright © 2004 Pearson Education, Inc., publishing as Addison Wesley.

- A perfect conductor has zero resistivity. A perfect insulator has infinite resistivity
  - The reciprocal of resistivity ( $1/\rho$ ) is called conductivity

$$\sigma \vec{E} = \vec{J}$$

PHYS 1022: Chap. 31-32, Pg 6

## Temperature dependence of Resistivity

- The resistivity of a material depends on *temperature*.


*Metal near room temperature:*

$$\rho(T) = \rho_0 [1 + \alpha(T - T_0)]$$

Table 25.2 Temperature Coefficients of Resistivity  
(Approximate Values Near Room Temperature)

Material	$\alpha [(\text{°C})^{-1}]$	Material	$\alpha [(\text{°C})^{-1}]$
Aluminum	0.0039	Lead	0.0043
Brass	0.0020	Manganin	0.00000
Carbon (graphite)	-0.0005	Mercury	0.00088
Constantan	0.00001	Nichrome	0.0004
Copper	0.00393	Silver	0.0038
Iron	0.0050	Tungsten	0.0045

Copyright © 2004 Pearson Education, Inc., publishing as Addison Wesley.

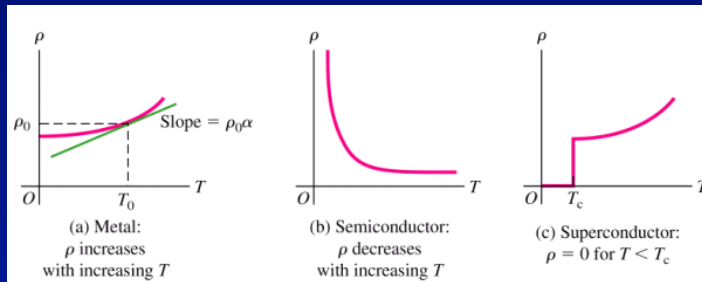

Chap. 31-32, Pg 7

### ConceptTest 3

### Conductivity

If a metal is heated, what happens to its conductivity?

- increases
- does not change
- decreases

- Are collisions with positive ions more frequent?
- How does that affect the drift speed?
- Does this make a better or worse conductor?


PHYS 1022: Chap. 31-32, Pg 8

### ConceptTest 2 (Post) Ohm's Law

What is the value of R?

Draw the graph for the case where the length of the resistor is doubled.

1. 0.25  $\Omega$
2. 0.5  $\Omega$
3. 1.0  $\Omega$
4. 2.0  $\Omega$
5. 4.0  $\Omega$


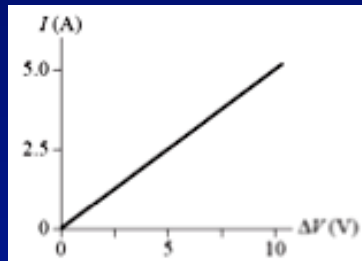


PHYS 1022: Chap. 31-32, Pg 9

### ConceptTest 3 (Post) Ohm's Law


Rank the currents in the resistors shown below.

1.  $I_3 > (I_1 = I_4) > I_2$
2.  $(I_1 = I_3) > (I_2 = I_4)$
3.  $(I_1 = I_2) > (I_3 = I_4)$
4.  $I_1 > (I_2 = I_3) > I_4$
5.  $I_3 > I_1 > (I_2 = I_4)$

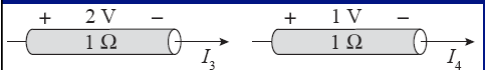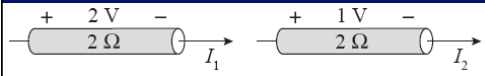


PHYS 1022: Chap. 31-32, Pg 10

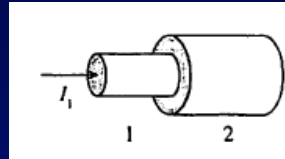A wire consists of two segments of different diameters of the same material.




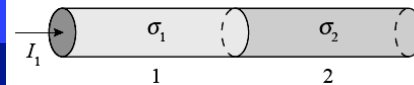- (a) Compare the currents  $I_1$  and  $I_2$ .
- (b) Compare the current densities  $J_1$  and  $J_2$ .
- (c) Compare the electric field strengths  $E_1$  and  $E_2$ .
- (d) Compare the electron drift speeds  $v_1$  and  $v_2$ .


A wire consists of two segments with equal diameters, but their conductivities and electron densities differ ( $\sigma_2 > \sigma_1$  and  $n_2 > n_1$ ).



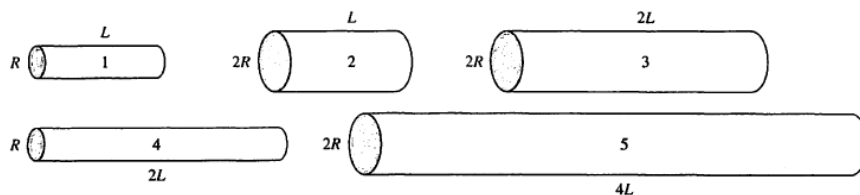Rank these resistances, from largest to smallest.



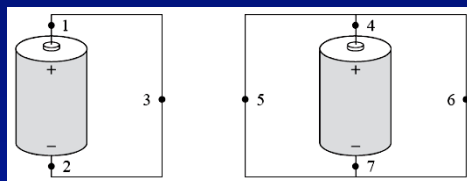Rank the currents at 1-7, from largest to smallest. Both batteries are identical.



## Chapter 31. Current and Resistance

### Topics:

- Conductivity and Resistivity
- Resistance and Ohm's Law

## Chapter 32. Simple circuits

- Capacitors in series and parallel
- Resistors in series and parallel
- Kirchhoff's Rules

PHYS 1022: Chap. 31-32, Pg 13

## Combinations of Capacitors

*New Topic*

PHYS 1022: Chap. 31-32, Pg 14

## Capacitors in parallel

- Potential difference between points **a** and **b** is the **same** for all 3 capacitors


$$\triangleright V_1 = V_2 = V_3 = V$$

- However, charges add:

$$\blacktriangleright Q_1 + Q_2 + Q_3 = Q$$

- Since  $Q = CV$ , we have
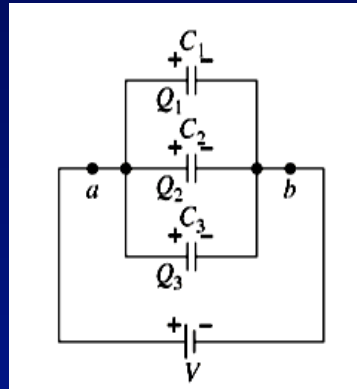
$$\blacktriangleright C_1V + C_2V + C_3V = CV$$



$$C = C_1 + C_2 + C_3$$

**C is called an equivalent capacitor.**

PHYS 1022: Chap. 31-32, Pg 15

## Capacitors in series

- Each capacitor has to hold the **same charge**:

$$\triangleright Q_1 = Q_2 = Q_3 = Q$$


- However, voltages add:

$$\blacktriangleright V_1 + V_2 + V_3 = V$$

- Since  $V = Q/C$ , we have

$$\blacktriangleright Q/C_1 + Q/C_2 + Q/C_3 = Q/C$$

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

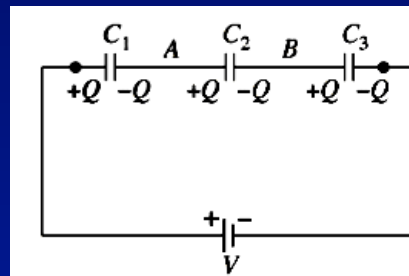


PHYS 1022: Chap. 31-32, Pg 16



### ConcepTest 4 capacitors

What is the equivalent capacitance of the combination shown ?

- 1)  $3C/2$
- 2)  $2C/3$
- 3)  $3C$
- 4)  $2C$
- 5)  $C/2$

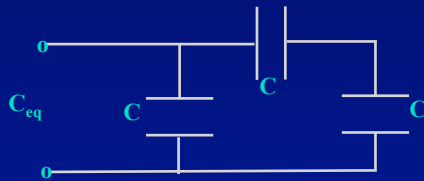


PHYS 1022: Chap. 31-32, Pg 17

### ConcepTest 5 capacitors

How does the voltage  $V_1$  across the  $C_1$  compare to the voltage  $V_2$  across  $C_2$ ?

- 1)  $V_1 = V_2$
- 2)  $V_1 > V_2$
- 3)  $V_1 < V_2$
- 4) all voltages are zero

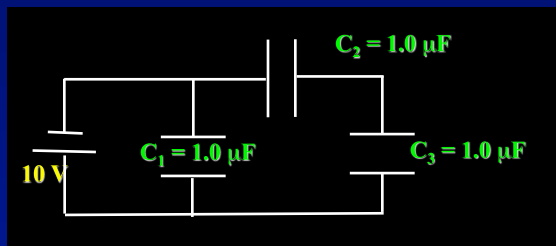


PHYS 1022: Chap. 31-32, Pg 18

### ConcepTest 6 capacitors


How does the charge  $Q_1$  across  $C_1$  compare to the charge  $Q_2$  across  $C_2$ ?

- 1)  $Q_1 = Q_2$
- 2)  $Q_1 < Q_2$
- 3)  $Q_1 > Q_2$
- 4) all charges are zero

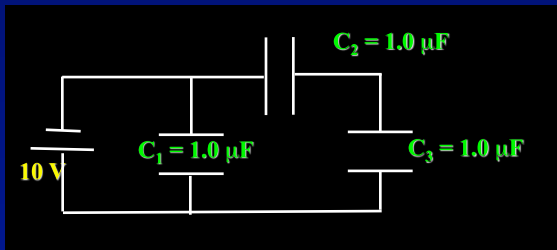

PHYS 1022: Chap. 31-32, Pg 19


Each capacitor in the circuits below has capacitance  $C$ . What is the equivalent capacitance of the group of capacitors?

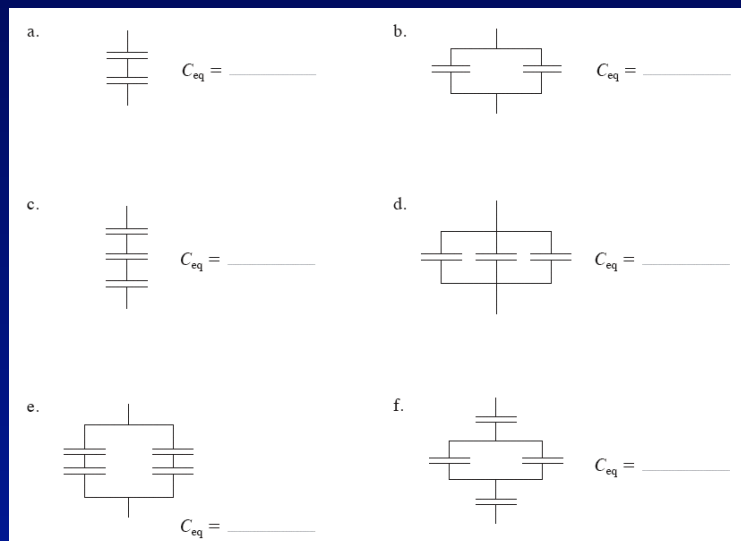

PHYS 1022: Chap. 31-32, Pg 20

## Capacitor calculations

- Find the charge, potential difference, and energy stored in each capacitor.

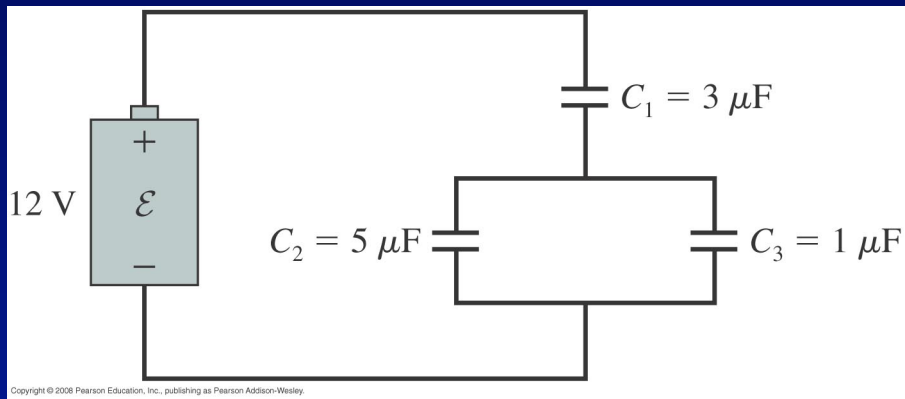

PHYS 1022: Chap. 31-32, Pg 21

## Combination of Resistors

*New Topic*

PHYS 1022: Chap. 31-32, Pg 22

## Resistors in series

- Same charge has to flow through all the resistors

same current:  $I_1 = I_2 = I_3 = I$


- Total work done by battery must equal sum of energy lost as charge moves through resistors

voltages add:  $V = V_1 + V_2 + V_3$

- Ohm's Law,  $V = I R$ , gives:

$$I R_{eq} = I R_1 + I R_2 + I R_3$$

$$R_{eq} = R_1 + R_2 + R_3$$

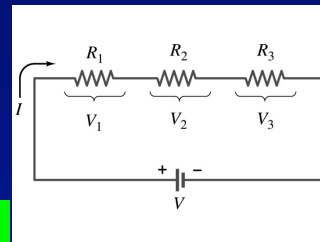

PHYS 1022: Chap. 31-32, Pg 23

## Resistors in parallel

- Current splits up into several branches. However, total current must be conserved!

➤ currents add:  $I = I_1 + I_2 + I_3$


- But the voltage is the same across each resistor

⚡  $V = V_1 = V_2 = V_3$

- From Ohm's Law,  $V = I R$ , we find:

$$\frac{V}{R_{eq}} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$
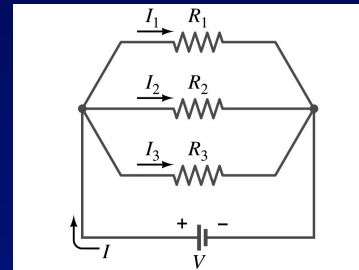
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$



$R_{eq}$  is the reciprocal of the sum of the reciprocals.

PHYS 1022: Chap. 31-32, Pg 24

# Kirchhoff's Rules

*New Topic*


PHYS 1022: Chap. 31-32, Pg 25

## Kirchhoff's Junction Rule

- At any junction point, the sum of all currents entering the junction must equal the sum of all currents leaving.

(or: what goes in has to come out!)


$$I_3 = I_1 + I_2$$

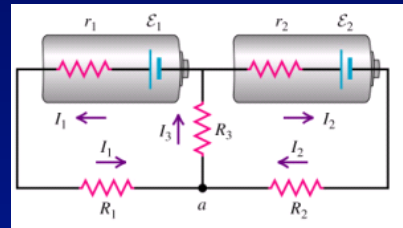

This rule follows from *conservation of charge* !

PHYS 1022: Chap. 31-32, Pg 26

# Kirchhoff's Loop Rule

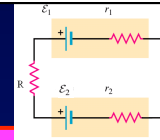

● “The sum of voltage drops and gains around any closed circuit loop must be zero”

$$\Delta V_1 + \Delta V_2 + \Delta V_3 + \Delta V_4 + \dots = 0$$


● This rule follows from *conservation of energy*

**Sign convention:**

– sign for voltage drop **and** + sign voltage gain.

It depends on several factors:


1. emf or resistor
2. direction of current
3. direction of loop travel

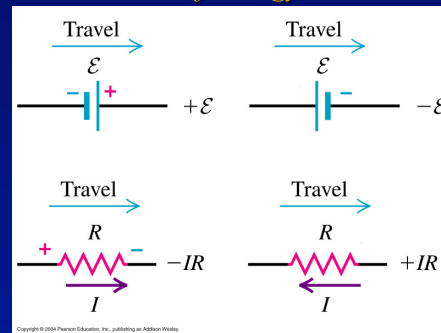

PHYS 1022: Chap. 31-32, Pg 27

# ConceptTest 7 Junction Rule

What is the current at point P?

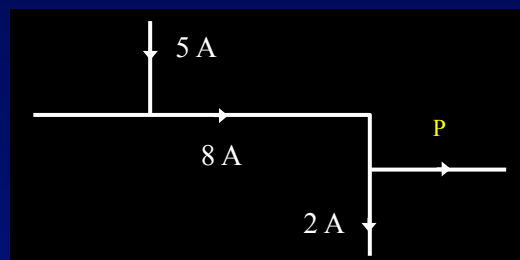


- 1) 2 A
- 2) 5 A
- 3) 6 A
- 4) 10 A

PHYS 1022: Chap. 31-32, Pg 28

### ConceptTest 8 (Post) Parallel Resistors

What fraction of the current goes through the  $3\ \Omega$  resistor?

1. 100% (all of it)
2. 75%
3. 50%
4. 33%
5. 0%

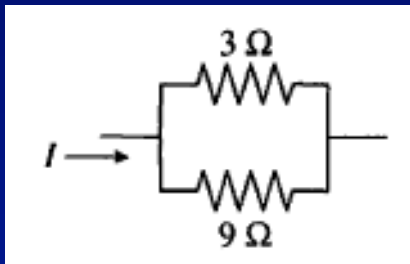


PHYS 1022: Chap. 31-32, Pg 29

### ConceptTest 9 (Post) Kirchhoff's Laws

Rank the resistors in the part of the circuit below.

1.  $R_1 > R_2 > R_3$
2.  $R_2 > R_1 > R_3$
3.  $R_3 > (R_2 = R_1)$
4.  $R_3 > R_1 > R_2$
5.  $R_1 = R_2 = R_3$

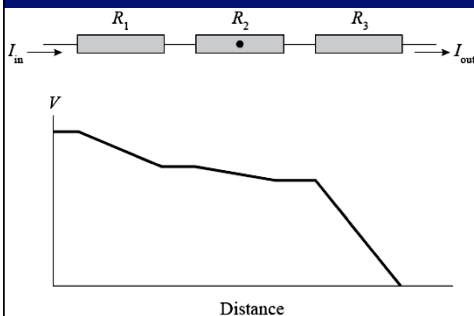


PHYS 1022: Chap. 31-32, Pg 30

### ConceptTest 10 (Post) Kirchhoff's Laws

Rank the currents shown in the circuit below.

1.  $I_3 > I_2 > I_1$
2.  $I_2 > I_1 > I_3$
3.  $I_1 > (I_2 = I_3)$
4.  $I_1 > I_3 > I_2$
5.  $I_1 > I_2 > I_3$

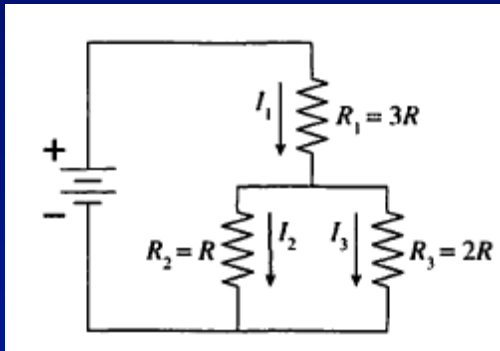


PHYS 1022: Chap. 31-32, Pg 31

### ConceptTest 11 (Post) Real Batteries

If the resistor  $R$  increases, what happens to the terminal voltage  $\Delta V_{\text{bat}}$  of the battery?

1. increases
2. decreases
3. stays the same
4. goes to zero

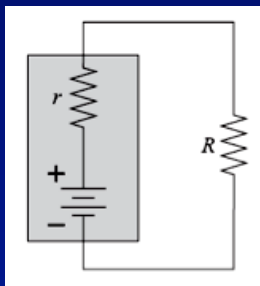

PHYS 1022: Chap. 31-32, Pg 32




### ConcepTest 12 (Post) Parallel Resistors

Which resistor dissipates the greater power, if  $R_1 > R_2$  ?

$$P = V^2/R$$

1.  $P_1 > P_2$
2.  $P_2 > P_1$
3. both the same

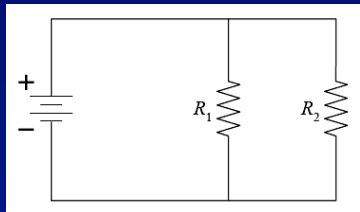


PHYS 1022: Chap. 31-32, Pg 33

### ConcepTest 13 (Post) Light Bulbs

Which bulb glows brighter?


For a 100W bulb,  $P = V^2/R$ , where  $V = 110V$ .

1. 60 W is brighter
2. 100 W is brighter
3. both equally bright

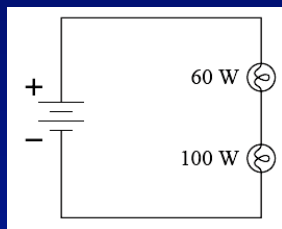

PHYS 1022: Chap. 31-32, Pg 34

## Loop Rule Example (with numbers)

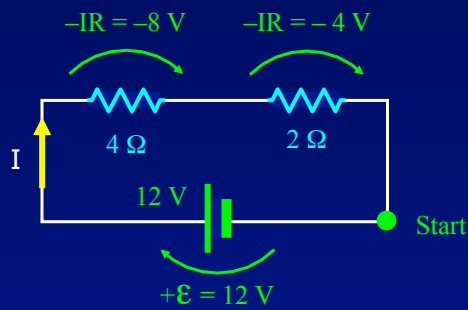

Current in each resistor?

Total resistance =  $6 \Omega$

$$\begin{aligned} \text{Ohm's Law: } I &= V / R \\ &= 12 \text{ V} / 6 \Omega \\ &= 2 \text{ A} \end{aligned}$$


Voltage drop across resistor?

$$V = I R$$

$$\Delta V = +12 \text{ V} - 8 \text{ V} - 4 \text{ V} = 0 \quad \checkmark$$

PHYS 1022: Chap. 31-32, Pg 35

## Loop Rule Example (without numbers)

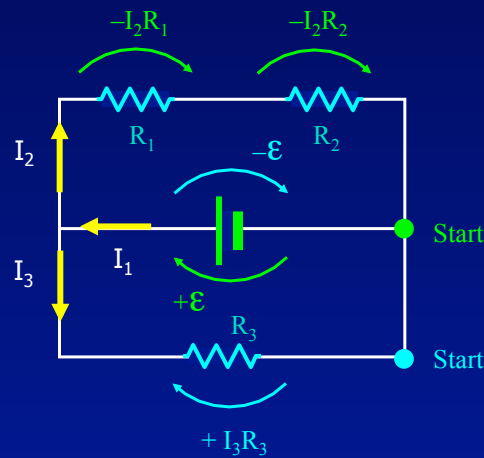

The first thing we have to do is?  
Define currents!

Next: Define travel direction:  
top loop (CW)  
bottom loop (CW)

Now apply Loop rule to each loop

$$\Delta V = +\epsilon - I_2 R_1 - I_2 R_2 = 0$$


$$\Delta V = +I_3 R_3 - \epsilon = 0$$

PHYS 1022: Chap. 31-32, Pg 36

In the circuits below, the two batteries are identical and all of the resistors have the same value.




(a) Compare  $\Delta V_{ab}$  and  $\Delta V_{cd}$ .

(b) Rank the currents (from high to low).

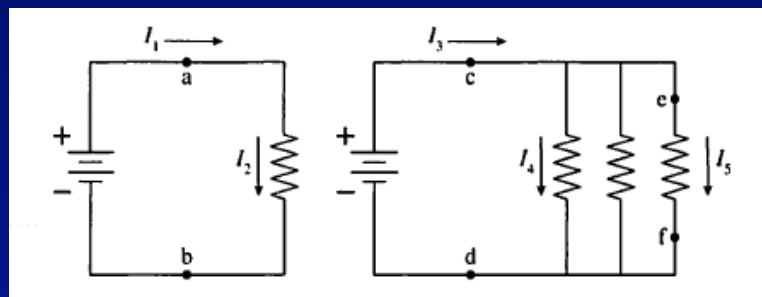


PHYS 1022: Chap. 31-32, Pg 37

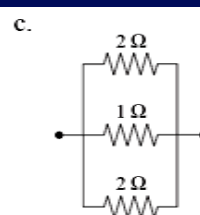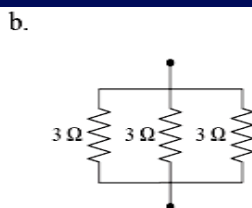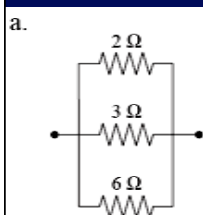Find the equivalent resistance of each resistor network.




Rank the equivalent resistances (large to small).

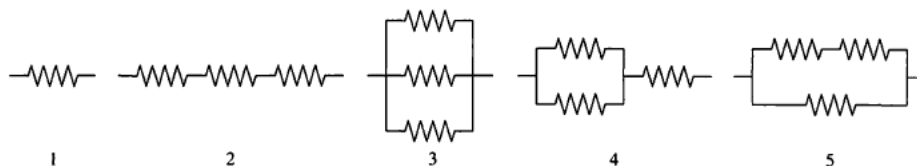

PHYS 1022: Chap. 31-32, Pg 38

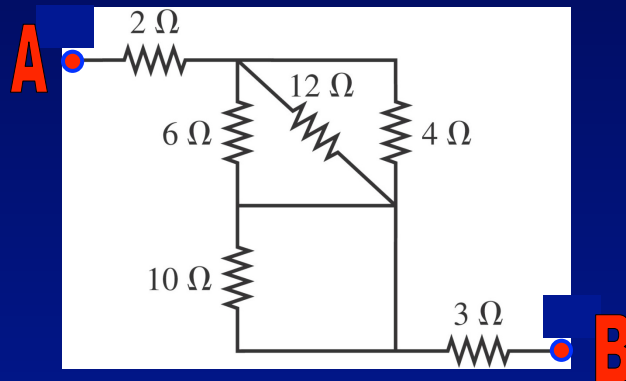
What is the equivalent resistance between points A and B in the network below?



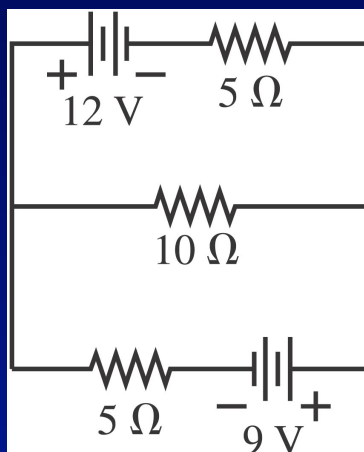**3+2=5**

PHYS 1022: Chap. 31-32, Pg 39

Find the current through each resistor in the circuit.



**3+2=5**

PHYS 1022: Chap. 31-32, Pg 40