

CS:APP3e Web Aside ARCH:VLOG

Verilog Implementation of a Pipelined Y86-64 Processor*

Randal E. Bryant
David R. O'Hallaron

December 29, 2014

Notice

The material in this document is supplementary material to the book Computer Systems, A Programmer's Perspective, Third Edition, by Randal E. Bryant and David R. O'Hallaron, published by Prentice-Hall and copyrighted 2016. In this document, all references beginning with "CS:APP3e " are to this book. More information about the book is available at csapp.cs.cmu.edu.

This document is being made available to the public, subject to copyright provisions. You are free to copy and distribute it, but you must give attribution for any use of this material.

1 Introduction

Modern logic design involves writing a textual representation of a hardware design in a *hardware description language*. The design can then be tested by both simulation and by a variety of formal verification tools. Once we have confidence in the design, we can use *logic synthesis* tools to translate the design into actual logic circuits.

In this document, we describe an implementation of the PIPE processor in the Verilog hardware description language. This design combines modules implementing the basic building blocks of the processor, with control logic generated directly from the HCL description developed in CS:APP2eChapter 4 and presented in Web Aside ARCH:HCL. We have been able to synthesize this design, download the logic circuit description onto field-programmable gate array (FPGA) hardware, and have the processor execute Y86-64 programs.

Aside: A Brief History of Verilog

Many different hardware description languages (HDLs) have been developed over the years, but Verilog was the first to achieve widespread success. It was developed originally by Philip Moorby, working at a company started in 1983 by Prabhu Goel to produce software that would assist hardware designers in designing and testing digital hardware.

*Copyright © 2015, R. E. Bryant, D. R. O'Hallaron. All rights reserved.

They gave their company what seemed at the time like a clever name: Automated Integrated Design Systems, or “AIDS.” When that acronym became better known to stand for Acquired Immune Deficiency Syndrome, they renamed their company Gateway Design Automation in 1985. Gateway was acquired by Cadence Design Systems in 1990, which remains one of the major companies in Electronic Design Automation (EDA). Cadence transferred the Verilog language into the public domain, and it became IEEE Standard 1364-1995. Since then it has undergone several revisions, as well.

Verilog was originally conceived as a language for writing simulation models for hardware. The task of designing actual hardware was still done by more manual means of drawing logic schematics, with some assistance provided by software for drawing circuits on a computer.

Starting in the 1980s, researchers developed efficient means of automatically synthesizing logic circuits from more abstract descriptions. Given the popularity of Verilog for writing simulation models, it was natural to use this language as the basis for synthesis tools. The first, and still most widely used such tool is the Design Compiler, marked by Synopsys, Inc., another major EDA company. **End Aside.**

Since Verilog was originally designed to create simulation models, it has many features that cannot be synthesized into hardware. For example, it is possible to describe the detailed timing of different events, whereas this would depend greatly on the hardware technology for which the design is synthesized. As a result, there is a recognized *synthesizable subset* of the Verilog language, and hardware designers must restrict how they write Verilog descriptions to ensure they can be synthesized. Our Verilog stays well within the bounds of the synthesizable subset.

This document is not intended to be a complete description of Verilog, but just to convey enough about it to see how we can readily translate our Y86-64 processor designs into actual hardware. A comprehensive description of Verilog is provided by Thomas and Moorby’s book [1]

A complete Verilog implementation of PIPE suitable for logic synthesis is given in Appendix A of this document. We will go through some parts of this description, using the fetch stage of the PIPE processor as our main source of examples. For reference, a diagram of this stage is shown in Figure 1.

2 Combinational Logic

The basic data type for Verilog is the *bit vector*, a collection of bits having a range of indices. The standard notation for bit vectors is to specify the indices as a range of the form $[hi:lo]$, where integers *hi* and *lo* give the index values of the most and least significant bits, respectively. Here are some examples of signal declarations:

```
wire [63:0] aluA;
wire [ 3:0] alufun;
wire      stall;
```

These declarations specify that the signals are of type `wire`, indicating that they serve as connections in a combinational circuit, rather than storing any information. We see that signals `aluA` and `alufun` are vectors of 64 and 4 bits, respectively, and that `stall` is a single bit (indicated when no index range is given.)

The operations on Verilog bit vectors are similar to those on C integers: arithmetic and bit-wise operations, shifting, and testing for equality or ordering relationships. In addition, it is possible to create new bit vectors by extracting ranges of bits from other vectors. For example, the expression `aluA[63:56]` creates an 8-bit wide vector equal to the most significant byte of `aluA`.

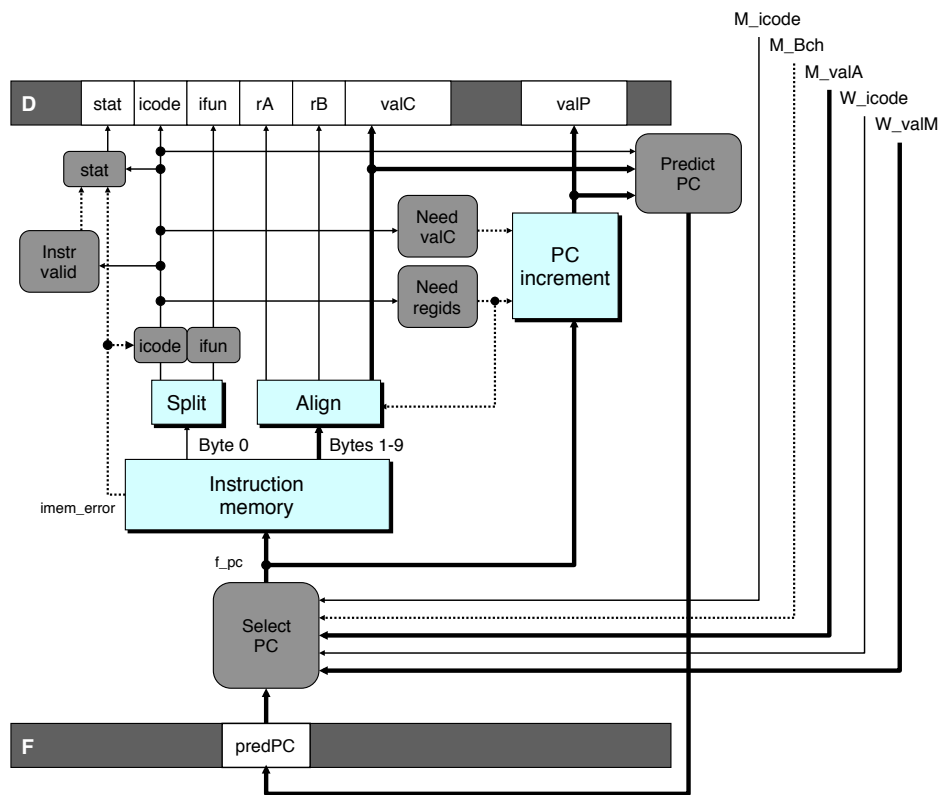


Figure 1: PIPE PC selection and fetch logic.

```

// Split instruction byte into icode and ifun fields
module split(itype, icode, ifun);
    input  [7:0] itype;
    output [3:0] icode;
    output [3:0] ifun;

    assign      icode = itype[7:4];
    assign      ifun  = itype[3:0];
endmodule

// Extract immediate word from 9 bytes of instruction
module align(itypes, need_regids, rA, rB, valC);
    input  [71:0] itypes;
    input          need_regids;
    output [ 3:0] rA;
    output [ 3:0] rB;
    output [63:0] valC;
    assign      rA = itypes[7:4];
    assign      rB = itypes[3:0];
    assign      valC = need_regids ? itypes[71:8] : itypes[63:0];
endmodule

// PC incrementer
module pc_increment(pc, need_regids, need_valC, valP);
    input  [63:0] pc;
    input          need_regids;
    input          need_valC;
    output [63:0] valP;
    assign      valP = pc + 1 + 8*need_valC + need_regids;
endmodule

```

Figure 2: **Hardware Units for Fetch Stage.** These illustrate the use of modules and bit vector operations in Verilog.

Verilog allows a system to be described as a hierarchy of *modules*. These modules are similar to procedures, except that they do not define an action to be performed when invoked, but rather they describe a portion of a system that can be *instantiated* as a block of hardware. Each module declares a set of interface signals—the inputs and outputs of the block—and a set of interconnected hardware components, consisting of either other module instantiations or primitive logic operations.

As an example of Verilog modules implementing simple combinational logic, Figure 2 shows Verilog descriptions of the hardware units required by the fetch stage of PIPE. For example, the module `split` serves to split the first byte of an instruction into the instruction code and function fields. We see that this module has a single eight-bit input `itype` and two four-bit outputs `icode` and `ifun`. Output `icode` is defined to be the high-order four bits of `itype`, while `ifun` is defined to be the low-order four bits.

Verilog has several different forms of *assignment* operators. An assignment starting with the keyword `assign` is known as a *continuous assignment*. It can be thought of as a way to connect two signals via

```

module alu(aluA, aluB, alufun, valE, new_cc);
    input  [63:0] aluA, aluB;    // Data inputs
    input  [ 3:0] alufun;       // ALU function
    output [63:0] valE;         // Data Output
    output [ 2:0] new_cc;       // New values for ZF, SF, OF

    parameter    ALUADD = 4'h0;
    parameter    ALUSUB = 4'h1;
    parameter    ALUAND = 4'h2;
    parameter    ALUXOR = 4'h3;

    assign       valE =
        alufun == ALUSUB ? aluB - aluA :
        alufun == ALUAND ? aluB & aluA :
        alufun == ALUXOR ? aluB ^ aluA :
        aluB + aluA;
    assign       new_cc[2] = (valE == 0); // ZF
    assign       new_cc[1] = valE[63];   // SF
    assign       new_cc[0] =
        alufun == ALUADD ?
            (aluA[63] == aluB[63]) & (aluA[63] != valE[63]) :
        alufun == ALUSUB ?
            (~aluA[63] == aluB[63]) & (aluB[63] != valE[63]) :
        0;
endmodule

```

Figure 3: **Verilog implementation of Y86-64 ALU.** This illustrates arithmetic and logical operations, as well as the Verilog notation for bit-vector constants.

simple wires, as when constructing combinational logic. Unlike an assignment in a programming language such as C, continuous assignment does not specify a single updating of a value, but rather it creates a permanent connection from the output of one block of logic to the input of another. So, for example, the description in the `split` module states that the two outputs are directly connected to the relevant fields of the input.

The `align` module describes how the processor extracts the remaining fields from an instruction, depending on whether or not the instruction has a register specifier byte. Again we see the use of continuous assignments and bit vector subranges. This module also includes a *conditional expression*, similar to the conditional expressions of C. In Verilog, however, this expression provides a way of creating a multiplexor—combinational logic that chooses between two data inputs based on a one-bit control signal.

The `pc_increment` module demonstrates some arithmetic operations in Verilog. These are similar to the arithmetic operations of C. Originally, Verilog only supported unsigned arithmetic on bit vectors. Two's complement arithmetic was introduced in the 2001 revision of the language. All operations in our description involve unsigned arithmetic.

As another example of combinational logic, Figure 3 shows an implementation of an ALU for the Y86-64 execute stage. We see that it has as inputs two 64-bit data words and a 4-bit function code. For outputs,

```

// Clocked register with enable signal and synchronous reset
// Default width is 8, but can be overridden
module cenrreg(out, in, enable, reset, resetval, clock);
    parameter width = 8;
    output [width-1:0] out;
    reg [width-1:0] out;
    input [width-1:0] in;
    input enable;
    input reset;
    input [width-1:0] resetval;
    input clock;

    always
        @(posedge clock)
        begin
            if (reset)
                out <= resetval;
            else if (enable)
                out <= in;
        end
endmodule

```

Figure 4: **Basic Clocked Register.**

it has a 64-bit data word and the three bits used to create condition codes. The `parameter` statement provides a way to give names to constant values, much as the way constants can be defined in C using `#define`. In Verilog, a bit-vector constant has a specific width, and a value given in either decimal (the default), hexadecimal (specified with ‘h’), or binary (specified with ‘b’) form. For example, the notation `4’h2` indicates a 4-bit wide vector having hexadecimal value `0x2`. The rest of the module describes the functionality of the ALU. We see that the data output will equal the sum, difference, bitwise EXCLUSIVE-OR, or bitwise AND of the two data inputs. The output conditions are computed using the values of the input and output data words, based on the properties of a two’s complement representation of the data (CS:APP3e Section 2.3.2.)

3 Registers

Thus far, we have considered only combinational logic, expressed using continuous assignments. Verilog has many different ways to express sequential behavior, event sequencing, and time-based waveforms. We will restrict our presentation to ways to express the simple clocking methods required by the Y86-64 processor.

Figure 4 shows a clocked register `cenrreg` (short for “conditionally-enabled, resettable register”) that we will use as a building block for the hardware registers in our processor. The idea is to have a register that can be loaded with the value on its input in response to a clock. Additionally, it is possible to *reset* the register, causing it to be set to a fixed constant value.

Some features of this module are worth highlighting. First, we see that the module is *parameterized* by a value `width`, indicating the number of bits comprising the input and output words. By default, the module has a width of 8 bits, but this can be overridden by instantiating the module with a different width.

We see that the register data output `out` is declared to be of type `reg` (short for “register”). That means that it will hold its value until it is explicitly updated. This contrasts to the signals of type `wire` that are used to implement combinational logic.

The statement beginning `always @(posedge clock)` describes a set of actions that will be triggered every time the clock signal goes for 0 to 1 (this is considered to be the positive edge of a clock signal.) Within this statement, we see that the output may be updated to be either its input or its reset value. The assignment operator `<=` is known as a *non-blocking* assignment. That means that the actual updating of the output will only take place when a new event is triggered, in this case the transition of the clock from 0 to 1. We can see that the output may be updated as the clock rises. Observe, however, that if neither the reset nor the enable signals are 1, then the output will remain at its current value.

The following module `preg` shows how we can use our basic register to construct a pipeline register:

```
// Pipeline register. Uses reset signal to inject bubble
// When bubbling, must specify value that will be loaded
module preg(out, in, stall, bubble, bubbleval, clock);
    parameter width = 8;
    output [width-1:0] out;
    input  [width-1:0] in;
    input                stall, bubble;
    input  [width-1:0] bubbleval;
    input                clock;

    cenreg #(width) r(out, in, ~stall, bubble, bubbleval, clock);
endmodule
```

We see that a pipeline register is created by instantiating a clocked register, but making the enable signal be the complement of the stall signal. We see here also the way modules are instantiated in Verilog. A module instantiation gives the name of the module, an optional list of parametric values, (in this case, we want the width of the register to be the width specified by the module’s parameter), an instance name (used when debugging a design by simulation), and a list of module parameters.

The register file is implemented using 15 clocked registers for the 15 program registers. Combinational logic is used to select which program register values are routed to the register file outputs, and which program registers to update by a write operation. The Verilog code for this is found in Appendix A, lines 135–271.

4 Memory

The memory module, illustrated in Figure 5, implements both the instruction and the data memory. The Verilog code for the module can be found in Appendix A, lines 273–977.

The module interface is defined as follows:

```
module bmemory(maddr, wenable, wdata, renable, rdata, m_ok,
```

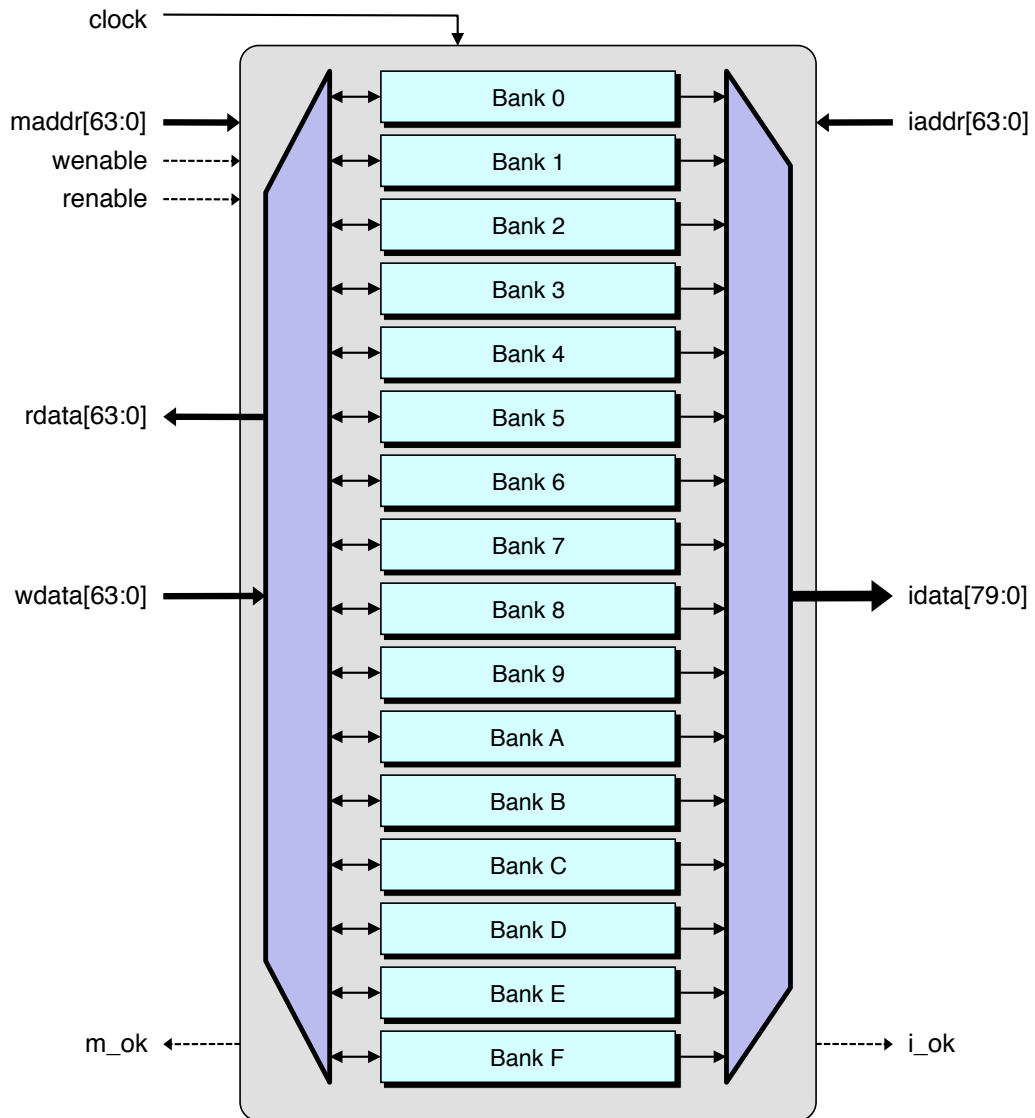


Figure 5: **Memory structure.** The memory consists of 16 banks, each performing single-byte reads and writes.


```

        iaddr, instr, i_ok, clock);
parameter memsize = 8192; // Number of bytes in memory
input  [63:0] maddr;      // Read/Write address
input          wenable;  // Write enable
input  [63:0] wdata;     // Write data
input          renable;  // Read enable
output [63:0] rdata;     // Read data
output          m_ok;    // Read & write addresses within range
input  [63:0] iaddr;     // Instruction address
output [79:0] instr;    // 10 bytes of instruction
output          i_ok;    // Instruction address within range
input          clock;

```

In Figure 5, we adopt the Verilog convention of indicating the index ranges for each of the multi-bit signals. The left-hand side of the figure shows the port used for reading and writing data. We see that it has an address input `maddr`, data output `rdata` and input `wdata`, and enable signals for reading and writing. The output signal `m_ok` indicates whether or not the address input is within the range of valid addresses for the memory.

The right-hand side of the figure shows the port used for fetching instructions. It has just an address input `iaddr`, an 80-byte wide data output `idata`, and a signal `i_ok` indicating whether or not the address is within the range of valid addresses.

We require a method for accessing groups of 8 or 10 successive bytes in the memory, and we cannot assume any particular alignment for the addresses. We therefore implement the memory with a set of 16 *banks*, each of which is a random-access memory that can be used to store, read, and write individual bytes. A byte with memory address i is stored in bank $i \bmod 16$, and the address of the byte within the bank is $\lfloor i/16 \rfloor$. Some advantages of this organization are:

- Any 10 successive bytes will be stored in separate banks. Thus, the processor can read all 10 instruction bytes using single-byte bank reads. Similarly, the processor can read or write all 8 data bytes using single-byte bank reads or writes.
- The bank number is given by the low-order 4 bits of the memory address.
- The address of a byte within the bank is given by the remaining bits of the memory address.

Figure 6 gives a Verilog description of a *combinational* RAM module suitable for implementing the memory banks. This RAM stores data in units of words, where we set the word size to be eight bits. We see that the module has three associated parametric values:

wordsize: The number of bits in each word of the memory. The default value is eight.

wordcount: The number of words stored in the memory. The default value of 512 creates a memory capable of storing $16 \cdot 512 = 8192$ bytes.

addrsiz: The number of bits in the address input. If the memory contains n words, this parameter must be at least $\log_2 n$.

```

1 // This module implements a dual-ported RAM.
2 // with clocked write and combinational read operations.
3 // This version matches the conceptual model presented in the CS:APP book,
4
5 module ram(clock, addrA, wEnA, wDatA, rEnA, rDatA,
6           addrB, wEnB, wDatB, rEnB, rDatB);
7
8     parameter wordsize = 8;    // Number of bits per word
9     parameter wordcount = 512; // Number of words in memory
10    // Number of address bits. Must be >= log wordcount
11    parameter addrsize = 9;
12
13    input    clock;           // Clock
14    // Port A
15    input [addrsize-1:0]  addrA; // Read/write address
16    input                wEnA;  // Write enable
17    input [wordsize-1:0] wDatA; // Write data
18    input                rEnA;  // Read enable
19    output [wordsize-1:0] rDatA; // Read data
20    // Port B
21    input [addrsize-1:0]  addrB; // Read/write address
22    input                wEnB;  // Write enable
23    input [wordsize-1:0] wDatB; // Write data
24    input                rEnB;  // Read enable
25    output [wordsize-1:0] rDatB; // Read data
26
27    // Actual storage
28    reg [wordsize-1:0] mem[wordcount-1:0];
29
30    always @(posedge clock)
31    begin
32        if (wEnA)
33        begin
34            mem[addrA] <= wDatA;
35        end
36    end
37    // Combinational reads
38    assign rDatA = mem[addrA];
39
40    always @(posedge clock)
41    begin
42        if (wEnB)
43        begin
44            mem[addrB] <= wDatB;
45        end
46    end
47    // Combinational reads
48    assign rDatB = mem[addrB];
49
50 endmodule

```

Figure 6: **Combinational RAM Module.** This module implements the memory banks, following the read/write model we have assumed for Y86-64.

 


Figure 7: **Timing of synchronous RAM.** By having the memory be read and written on the falling clock edge, the combinational logic can be active both before (A) and after (B) the memory operation.

This module implements the model we have assumed in Chapter 4: memory writes occur when the clock goes high, but memory reads operate as if the memory were a block of combinational logic.

Several features of the combinational RAM module are worth noting. We see the declaration of the actual memory array on line 28. It declares `mem` to be an array with elements numbered from 0 to the word count minus 1, where each array element is a bit vector with bits numbered from 0 to the word size minus 1. Furthermore, each bit is of type `reg`, and therefore acts as a storage element.

The combinational RAM has two ports, labeled “A” and “B,” that can be independently written on each cycle. We see the writes occurring within `always` blocks, and each involving a nonblocking assignment (lines 34 and 44.) The memory array is addressed using an array notation. We see also the two reads are expressed as continuous assignments (lines 38 and 48), meaning that these outputs will track the values of whatever memory elements are being addressed.

The combinational RAM is fine for running simulations of the processor using a Verilog simulator. In real life, however, most random-access memories require a clock to trigger a sequence of events that carries out a read operation (see CS:APP3e Section 6.1.1), and so we must modify our design slightly to work with a *synchronous* RAM, meaning that both read and write operations occur in response to a clock signal. Fortunately, a simple timing trick allows us to use a synchronous RAM module in the PIPE processor.

We design the RAM blocks used to implement the memory banks, such that the read and write operations are triggered by the *falling* edge of the clock, as it makes the transition for 1 to 0. This yields a timing illustrated in Figure 7. We see that the regular registers (including the pipeline registers, the condition code register, and the register file) are updated when the clock goes from 0 to 1. At this point, values propagate through combinational logic to the address, data, and control inputs of the memory. The clock transition from 1 to 0 causes the designated memory operations to take place. More combinational logic is then activated to propagate values to the register inputs, arriving there in time for the next clock transition.

With this timing, we can therefore classify each combinational logic block as being either in group I, meaning that it depends only on the values stored in registers, and group II, meaning that it depends on the values read from memory.

Practice Problem 1:

Determine which combination logic blocks in the fetch stage (Figure 1) are in group I, and which are in group II.

```

1 // This module implements a dual-ported RAM.
2 // with clocked write and read operations.
3
4 module ram(clock, addrA, wEnA, wDatA, rEnA, rDatA,
5           addrB, wEnB, wDatB, rEnB, rDatB);
6
7 parameter wordsize = 8;    // Number of bits per word
8 parameter wordcount = 512; // Number of words in memory
9 // Number of address bits. Must be >= log wordcount
10 parameter addrsize = 9;
11
12
13 input  clock;                // Clock
14 // Port A
15 input [addrsize-1:0] addrA;  // Read/write address
16 input  wEnA;                // Write enable
17 input [wordsize-1:0] wDatA;  // Write data
18 input  rEnA;                // Read enable
19 output [wordsize-1:0] rDatA; // Read data
20 reg [wordsize-1:0] rDatA;
21 // Port B
22 input [addrsize-1:0] addrB;  // Read/write address
23 input  wEnB;                // Write enable
24 input [wordsize-1:0] wDatB;  // Write data
25 input  rEnB;                // Read enable
26 output [wordsize-1:0] rDatB; // Read data
27 reg [wordsize-1:0] rDatB;
28
29 reg[wordsize-1:0] mem[wordcount-1:0]; // Actual storage
30
31 always @(negedge clock)
32 begin
33     if (wEnA)
34     begin
35         mem[addrA] <= wDatA;
36     end
37     if (rEnA)
38         rDatA <= mem[addrA];
39 end
40
41 always @(negedge clock)
42 begin
43     if (wEnB)
44     begin
45         mem[addrB] <= wDatB;
46     end
47     if (rEnB)
48         rDatB <= mem[addrB];
49 end
50 endmodule

```

Figure 8: **Synchronous RAM Module.** This module implements the memory banks using synchronous read operations.

 


Figure 9: **Processor interface.** Mechanisms are included to upload and download memory data and processor state, and to operate the processor in different modes.

```

module processor(mode, udaddr, idata, odata, stat, clock);
  input  [ 2:0] mode;    // Signal operating mode to processor
  input  [63:0] udaddr; // Upload/download address
  input  [63:0] idata;  // Download data word
  output [63:0] odata;  // Upload data word
  output [ 2:0] stat;   // Status
  input          clock; // Clock input

```

Figure 10: **Declaration of processor module.**

Figure 8 shows a synchronous RAM module that better reflects the random-access memories available to hardware designers. Comparing this module to the combinational RAM (Figure 6), we see two differences. First the data outputs `rDatA` and `rDatB` are both declared to be of type `reg`, meaning that they will hold the value assigned to them until they are explicitly updated (lines 20 and 27.) Second, the updating of these two outputs occur via nonblocking assignments within `always` blocks (lines 38 and 48).

The remaining portions of the memory module are implemented as combinational logic, and so changing the underlying bank memory design is the only modification required to shift the memory from having combinational read operations to having synchronous ones. This is the only modification required to our processor design to make it synthesizable as actual hardware.

5 Overall Processor Design

We have now created the basic building blocks for a Y86-64 processor. We are ready to assemble these pieces into an actual processor. Figure 9 shows the input and output connections we will design for our processor, allowing the processor to be operated by an external controller. The Verilog declaration for the processor module is shown in Figure 10. The `mode` input specifies what the processor should be doing. The possible values (declared as parameters in the Verilog code) are

RUN: Execute instructions in the normal manner.

RESET: All registers are set to their initial values, clearing the pipeline registers and setting the program

counter to 0.

DOWNLOAD: The processor memory can be loaded using the `udaddr` address input and the `idata` data input to specify addresses and values. By this means, we can load a program into the processor.

UPLOAD: Data can be extracted from the processor memory, using the address input `udaddr` to specify an address and the `odata` output to provide the data stored at that address.

STATUS: Similar to **UPLOAD** mode, except that the values of the program registers, and the condition codes can be extracted. Each program register and the condition codes have associated addresses for this operation.

The `stat` output is a copy of the `Stat` signal generated by the processor.

A typical operation of the processor involves the following sequence: 1) first, a program is downloaded into memory, downloading 8 bytes per cycle in **DOWNLOAD** mode. The processor is then put into **RESET** mode for one clock cycle. The processor is operated in **RUN** mode until the `stat` output indicates that some type of exception has occurred (normally when the processor executes a `halt` instruction.) The results are then read from the processor over multiple cycles using the **UPLOAD** and **STATUS** modes.

6 Implementation Highlights

The following are samples of the Verilog code for our implementation of PIPE, showing the implementation of the fetch stage.

The following are declarations of the internal signals of the fetch stage. They are all of type `wire`, meaning that they are simply connectors from one logic block to another.

```
wire [63:0] f_predPC, F_predPC, f_pc;
wire      f_ok;
wire      imem_error;
wire [ 2:0] f_stat;
wire [79:0] f_instr;
wire [ 3:0] imem_icode;
wire [ 3:0] imem_ifun;
wire [ 3:0] f_icode;
wire [ 3:0] f_ifun;
wire [ 3:0] f_rA;
wire [ 3:0] f_rB;
wire [63:0] f_valC;
wire [63:0] f_valP;
wire      need_regids;
wire      need_valC;
wire      instr_valid;
wire      F_stall, F_bubble;
```

The following signals must be included to allow pipeline registers F and D to be reset when either the processor is in **RESET** mode or the bubble signal is set for the pipeline register.

```

wire resetting = (mode == RESET_MODE);
wire F_reset = F_bubble | resetting;
wire D_reset = D_bubble | resetting;

```

The different elements of pipeline registers F and D are generated as instantiations of the `preg` register module. Observe how these are instantiated with different widths, according to the number of bits in each element:

```

// All pipeline registers are implemented with module
//   preg(out, in, stall, bubble, bubblelevel, clock)
// F Register
preg #(64) F_predPC_reg(F_predPC, f_predPC, F_stall, F_reset, 64'b0, clock);
// D Register
preg #(3) D_stat_reg(D_stat, f_stat, D_stall, D_reset, SBUB, clock);
preg #(64) D_pc_reg(D_pc, f_pc, D_stall, D_reset, 64'b0, clock);
preg #(4) D_icode_reg(D_icode, f_icode, D_stall, D_reset, INOP, clock);
preg #(4) D_ifun_reg(D_ifun, f_ifun, D_stall, D_reset, FNONE, clock);
preg #(4) D_rA_reg(D_rA, f_rA, D_stall, D_reset, RNONE, clock);
preg #(4) D_rB_reg(D_rB, f_rB, D_stall, D_reset, RNONE, clock);
preg #(64) D_valC_reg(D_valC, f_valC, D_stall, D_reset, 64'b0, clock);
preg #(64) D_valP_reg(D_valP, f_valP, D_stall, D_reset, 64'b0, clock);

```

We want to generate the Verilog descriptions of the control logic blocks directly from their HCL descriptions. For example, the following are HCL representations of blocks found in the fetch stage:

```

## What address should instruction be fetched at
word f_pc = [
    # Mispredicted branch. Fetch at incremented PC
    M_icode == IJXX && !M_Cnd : M_valA;
    # Completion of RET instruction
    W_icode == IRET : W_valM;
    # Default: Use predicted value of PC
    1 : F_predPC;
];

## Determine icode of fetched instruction
word f_icode = [
    imem_error : INOP;
    1: imem_icode;
];

# Determine ifun
word f_ifun = [
    imem_error : FNONE;
    1: imem_ifun;
];

# Is instruction valid?

```

```

bool instr_valid = f_icode in
    { INOP, IHALT, IRRMOVQ, IIRMOVQ, IRMMOVQ, IMRMOVQ,
      IOPQ, IJXX, ICALL, IRET, IPUSHQ, IPOPOPQ };

# Determine status code for fetched instruction
word f_stat = [
    imem_error: SADR;
    !instr_valid : SINS;
    f_icode == IHALT : SHLT;
    1 : SAOK;
];

# Does fetched instruction require a regid byte?
bool need_regids =
    f_icode in { IRRMOVQ, IOPQ, IPUSHQ, IPOPOPQ,
                IIRMOVQ, IRMMOVQ, IMRMOVQ };

# Does fetched instruction require a constant word?
bool need_valC =
    f_icode in { IIRMOVQ, IRMMOVQ, IMRMOVQ, IJXX, ICALL };

# Predict next value of PC
word f_predPC = [
    f_icode in { IJXX, ICALL } : f_valC;
    1 : f_valP;
];

```

We have implemented a program HCL2V (short for “HCL to Verilog”) to generate Verilog code from HCL expressions. The following are examples of code generated from the HCL descriptions of blocks found in the fetch stage. These are not formatted in a way that makes them easily readable, but it can be seen that the conversion from HCL to Verilog is fairly straightforward:

```

assign f_pc =
    ((M_icode == IJXX) & ~M_Cnd) ? M_valA : (W_icode == IRET) ? W_valM :
    F_predPC);

assign f_icode =
    (imem_error ? INOP : imem_icode);

assign f_ifun =
    (imem_error ? FNONE : imem_ifun);

assign instr_valid =
    (f_icode == INOP | f_icode == IHALT | f_icode == IRRMOVQ | f_icode ==
     IIRMOVQ | f_icode == IRMMOVQ | f_icode == IMRMOVQ | f_icode == IOPQ
     | f_icode == IJXX | f_icode == ICALL | f_icode == IRET | f_icode ==
     IPUSHQ | f_icode == IPOPOPQ);

assign f_stat =

```



```

(imem_error ? SADR : ~instr_valid ? SINS : (f_icode == IHALT) ? SHLT :
  SAOK);

assign need_regids =
  (f_icode == IRRMOVQ | f_icode == IOPQ | f_icode == IPUSHQ | f_icode ==
   IPOPOQ | f_icode == IIRMOVQ | f_icode == IRMMOVQ | f_icode == IMRMOVQ)
  ;

assign need_valC =
  (f_icode == IIRMOVQ | f_icode == IRMMOVQ | f_icode == IMRMOVQ | f_icode
   == IJXX | f_icode == ICALL);

assign f_predPC =
  ((f_icode == IJXX | f_icode == ICALL) ? f_valC : f_valP);

```

Finally, we must instantiate the different modules implementing the hardware units we examined earlier:

```

split split(f_instr[7:0], imem_icode, imem_ifun);
align align(f_instr[79:8], need_regids, f_rA, f_rB, f_valC);
pc_increment pci(f_pc, need_regids, need_valC, f_valP);

```

7 Summary

We have successfully generated a synthesizable Verilog description of a pipelined Y86-64 processor. We see from this exercise that the processor design we created in CS:APP3e Chapter 4 is sufficiently complete that it leads directly to a hardware realization. We have successfully run this Verilog through synthesis tools and mapped the design onto FPGA-based hardware.

Homework Problems

Homework Problem 2 ◆◆◆:

Generate a Verilog description of the SEQ processor suitable for simulation. You can use the same blocks as shown here for the PIPE processor, and you can generate the control logic from the HCL representation using the HCL2V program. Use the combinational RAM module (Figure 6) to implement the memory banks.

Homework Problem 3 ◆◆:

Suppose we wish to create a synthesizable version of the SEQ processor.

- A. Analyze what would happen if you were to use the synchronous RAM module (Figure 8) in an implementation of the SEQ processor (Problem 2.)
- B. Devise and implement (in Verilog) a clocking scheme for the registers and the memory banks that would enable the use of a synchronous RAM in an implementation of the SEQ processor.

Problem Solutions

Problem 1 Solution: [Pg. 11]

We see that only the PC selection block is in group I. All others depend, in part, on the value read from the instruction memory and therefore are in group II.

Acknowledgments

James Hoe of Carnegie Mellon University has been instrumental in the design of the Y86-64 processor, in helping us learn Verilog, and in using synthesis tools to generate a working microprocessor.

A Complete Verilog for PIPE

The following is a complete Verilog description of our implementation of PIPE. It was generated by combining a number of different module descriptions, and incorporating logic generated automatically from the HCL description. This model uses the synchronous RAM module suitable for both simulation and synthesis.

```

1 // -----
2 // Verilog representation of PIPE processor
3 // -----
4
5 // -----
6 // Memory module for implementing bank memories
7 // -----
8 // This module implements a dual-ported RAM.
9 // with clocked write and read operations.
10
11 module ram(clock, addrA, wEnA, wDatA, rEnA, rDatA,
12           addrB, wEnB, wDatB, rEnB, rDatB);
13
14 parameter wordsize = 8;    // Number of bits per word
15 parameter wordcount = 512; // Number of words in memory
16 // Number of address bits. Must be >= log wordcount
17 parameter addrsize = 9;
18
19
20 input  clock;                // Clock
21 // Port A
22 input [addrsize-1:0] addrA;  // Read/write address
23 input  wEnA;                // Write enable
24 input [wordsize-1:0] wDatA;  // Write data

```

```

25  input  rEnA;                // Read enable
26  output [wordsize-1:0] rDatA; // Read data
27  reg [wordsize-1:0] rDatA; // line:arch:synchram:rData
28  // Port B
29  input [addrsize-1:0] addrB; // Read/write address
30  input  wEnB;                // Write enable
31  input [wordsize-1:0] wDatB; // Write data
32  input  rEnB;                // Read enable
33  output [wordsize-1:0] rDatB; // Read data
34  reg [wordsize-1:0] rDatB; // line:arch:synchram:rDatB
35
36  reg[wordsize-1:0] mem[wordcount-1:0]; // Actual storage
37
38  // To make the pipeline processor work with synchronous reads, we
39  // operate the memory read operations on the negative
40  // edge of the clock. That makes the reading occur in the middle
41  // of the clock cycle---after the address inputs have been set
42  // and such that the results read from the memory can flow through
43  // more combinational logic before reaching the clocked registers
44
45  // For uniformity, we also make the memory write operation
46  // occur on the negative edge of the clock. That works OK
47  // in this design, because the write can occur as soon as the
48  // address & data inputs have been set.
49  always @(negedge clock)
50  begin
51      if (wEnA)
52      begin
53          mem[addrA] <= wDatA;
54      end
55      if (rEnA)
56          rDatA <= mem[addrA]; // line:arch:synchram:readA
57  end
58
59  always @(negedge clock)
60  begin
61      if (wEnB)
62      begin
63          mem[addrB] <= wDatB;
64      end
65      if (rEnB)
66          rDatB <= mem[addrB]; // line:arch:synchram:readB
67  end
68 endmodule
69
70 // -----
71 // Other building blocks
72 // -----
73
74 // Basic building blocks for constructing a Y86-64 processor.

```

```

75
76 // Different types of registers, all derivatives of module cenrreg
77
78 // Clocked register with enable signal and synchronous reset
79 // Default width is 8, but can be overridden
80 module cenrreg(out, in, enable, reset, resetval, clock);
81     parameter width = 8;
82     output [width-1:0] out;
83     reg     [width-1:0] out;
84     input  [width-1:0] in;
85     input                enable;
86     input                reset;
87     input  [width-1:0] resetval;
88     input                clock;
89
90     always
91         @(posedge clock)
92         begin
93             if (reset)
94                 out <= resetval;
95             else if (enable)
96                 out <= in;
97         end
98 endmodule
99
100 // Clocked register with enable signal.
101 // Default width is 8, but can be overridden
102 module cenreg(out, in, enable, clock);
103     parameter width = 8;
104     output [width-1:0] out;
105     input  [width-1:0] in;
106     input                enable;
107     input                clock;
108
109     cenrreg #(width) c(out, in, enable, 1'b0, 8'b0, clock);
110 endmodule
111
112 // Basic clocked register. Default width is 8.
113 module creg(out, in, clock);
114     parameter width = 8;
115     output [width-1:0] out;
116     input  [width-1:0] in;
117     input                clock;
118
119     cenreg #(width) r(out, in, 1'b1, clock);
120 endmodule
121
122 // Pipeline register. Uses reset signal to inject bubble
123 // When bubbling, must specify value that will be loaded
124 module preg(out, in, stall, bubble, bubbleval, clock);

```

```

125     parameter width = 8;
126     output [width-1:0] out;
127     input  [width-1:0] in;
128     input                stall, bubble;
129     input  [width-1:0] bubbleval;
130     input                clock;
131
132     cenrreg #(width) r(out, in, ~stall, bubble, bubbleval, clock);
133 endmodule
134
135 // Register file
136 module regfile(dstE, valE, dstM, valM, srcA, valA, srcB, valB, reset, clock,
137             rax, rcx, rdx, rbx, rsp, rbp, rsi, rdi,
138             r8, r9, r10, r11, r12, r13, r14);
139     input  [ 3:0] dstE;
140     input  [63:0] valE;
141     input  [ 3:0] dstM;
142     input  [63:0] valM;
143     input  [ 3:0] srcA;
144     output [63:0] valA;
145     input  [ 3:0] srcB;
146     output [63:0] valB;
147     input                reset; // Set registers to 0
148     input                clock;
149     // Make individual registers visible for debugging
150     output [63:0] rax, rcx, rdx, rbx, rsp, rbp, rsi, rdi,
151             r8, r9, r10, r11, r12, r13, r14;
152
153     // Define names for registers used in HCL code
154     parameter RRAX = 4'h0;
155     parameter RRCX = 4'h1;
156     parameter RRDY = 4'h2;
157     parameter RRBX = 4'h3;
158     parameter RRSP = 4'h4;
159     parameter RRBP = 4'h5;
160     parameter RRSI = 4'h6;
161     parameter RRDI = 4'h7;
162     parameter R8   = 4'h8;
163     parameter R9   = 4'h9;
164     parameter R10  = 4'ha;
165     parameter R11  = 4'hb;
166     parameter R12  = 4'hc;
167     parameter R13  = 4'hd;
168     parameter R14  = 4'he;
169     parameter RNONE = 4'hf;
170
171     // Input data for each register
172     wire [63:0] rax_dat, rcx_dat, rdx_dat, rbx_dat,
173             rsp_dat, rbp_dat, rsi_dat, rdi_dat,
174             r8_dat, r9_dat, r10_dat, r11_dat,

```

```

175         r12_dat, r13_dat, r14_dat;
176
177 // Input write controls for each register
178 wire      rax_wrt, rcx_wrt, rdx_wrt, rbx_wrt,
179          rsp_wrt, rbp_wrt, rsi_wrt, rdi_wrt,
180          r8_wrt, r9_wrt, r10_wrt, r11_wrt,
181          r12_wrt, r13_wrt, r14_wrt;
182
183
184 // Implement with clocked registers
185 cenrreg #(64) rax_reg(rax, rax_dat, rax_wrt, reset, 64'b0, clock);
186 cenrreg #(64) rcx_reg(rcx, rcx_dat, rcx_wrt, reset, 64'b0, clock);
187 cenrreg #(64) rdx_reg(rdx, rdx_dat, rdx_wrt, reset, 64'b0, clock);
188 cenrreg #(64) rbx_reg(rbx, rbx_dat, rbx_wrt, reset, 64'b0, clock);
189 cenrreg #(64) rsp_reg(rsp, rsp_dat, rsp_wrt, reset, 64'b0, clock);
190 cenrreg #(64) rbp_reg(rbp, rbp_dat, rbp_wrt, reset, 64'b0, clock);
191 cenrreg #(64) rsi_reg(rsi, rsi_dat, rsi_wrt, reset, 64'b0, clock);
192 cenrreg #(64) rdi_reg(rdi, rdi_dat, rdi_wrt, reset, 64'b0, clock);
193 cenrreg #(64) r8_reg(r8, r8_dat, r8_wrt, reset, 64'b0, clock);
194 cenrreg #(64) r9_reg(r9, r9_dat, r9_wrt, reset, 64'b0, clock);
195 cenrreg #(64) r10_reg(r10, r10_dat, r10_wrt, reset, 64'b0, clock);
196 cenrreg #(64) r11_reg(r11, r11_dat, r11_wrt, reset, 64'b0, clock);
197 cenrreg #(64) r12_reg(r12, r12_dat, r12_wrt, reset, 64'b0, clock);
198 cenrreg #(64) r13_reg(r13, r13_dat, r13_wrt, reset, 64'b0, clock);
199 cenrreg #(64) r14_reg(r14, r14_dat, r14_wrt, reset, 64'b0, clock);
200
201 // Reads occur like combinational logic
202 assign    valA =
203          srcA == RRAX ? rax :
204          srcA == RRCX ? rcx :
205          srcA == RRDY ? rdx :
206          srcA == RRBX ? rbx :
207          srcA == RRSP ? rsp :
208          srcA == RRBP ? rbp :
209          srcA == RRSI ? rsi :
210          srcA == RRDI ? rdi :
211          srcA == R8   ? r8  :
212          srcA == R9   ? r9  :
213          srcA == R10  ? r10 :
214          srcA == R11  ? r11 :
215          srcA == R12  ? r12 :
216          srcA == R13  ? r13 :
217          srcA == R14  ? r14 :
218          0;
219
220 assign    valB =
221          srcB == RRAX ? rax :
222          srcB == RRCX ? rcx :
223          srcB == RRDY ? rdx :
224          srcB == RRBX ? rbx :

```

```

225         srcB == RRSP ? rsp :
226         srcB == RRBP ? rbp :
227         srcB == RRSI ? rsi :
228         srcB == RRDI ? rdi :
229         srcB == R8   ? r8   :
230         srcB == R9   ? r9   :
231         srcB == R10  ? r10  :
232         srcB == R11  ? r11  :
233         srcB == R12  ? r12  :
234         srcB == R13  ? r13  :
235         srcB == R14  ? r14  :
236         0;
237
238     assign    rax_dat = dstM == RRAX ? valM : valE;
239     assign    rcx_dat = dstM == RRCX ? valM : valE;
240     assign    rdx_dat = dstM == RRDY ? valM : valE;
241     assign    rbx_dat = dstM == RRBX ? valM : valE;
242     assign    rsp_dat = dstM == RRSP ? valM : valE;
243     assign    rbp_dat = dstM == RRBP ? valM : valE;
244     assign    rsi_dat = dstM == RRSI ? valM : valE;
245     assign    rdi_dat = dstM == RRDI ? valM : valE;
246     assign    r8_dat  = dstM == R8   ? valM : valE;
247     assign    r9_dat  = dstM == R9   ? valM : valE;
248     assign    r10_dat = dstM == R10  ? valM : valE;
249     assign    r11_dat = dstM == R11  ? valM : valE;
250     assign    r12_dat = dstM == R12  ? valM : valE;
251     assign    r13_dat = dstM == R13  ? valM : valE;
252     assign    r14_dat = dstM == R14  ? valM : valE;
253
254     assign    rax_wrt = dstM == RRAX | dstE == RRAX;
255     assign    rcx_wrt = dstM == RRCX | dstE == RRCX;
256     assign    rdx_wrt = dstM == RRDY | dstE == RRDY;
257     assign    rbx_wrt = dstM == RRBX | dstE == RRBX;
258     assign    rsp_wrt = dstM == RRSP | dstE == RRSP;
259     assign    rbp_wrt = dstM == RRBP | dstE == RRBP;
260     assign    rsi_wrt = dstM == RRSI | dstE == RRSI;
261     assign    rdi_wrt = dstM == RRDI | dstE == RRDI;
262     assign    r8_wrt  = dstM == R8   | dstE == R8;
263     assign    r9_wrt  = dstM == R9   | dstE == R9;
264     assign    r10_wrt = dstM == R10  | dstE == R10;
265     assign    r11_wrt = dstM == R11  | dstE == R11;
266     assign    r12_wrt = dstM == R12  | dstE == R12;
267     assign    r13_wrt = dstM == R13  | dstE == R13;
268     assign    r14_wrt = dstM == R14  | dstE == R14;
269
270
271     endmodule
272
273 // Memory. This memory design uses 16 memory banks, each
274 // of which is one byte wide. Banking allows us to select an

```

```

275 // arbitrary set of 10 contiguous bytes for instruction reading
276 // and an arbitrary set of 8 contiguous bytes
277 // for data reading & writing.
278 // It uses an external RAM module from either the file
279 // combram.v (using combinational reads)
280 // or synchram.v (using clocked reads)
281 // The SEQ & SEQ+ processors only work with combram.v.
282 // PIPE works with either.
283
284 module bmemory(maddr, wenable, wdata, renable, rdata, m_ok,
285               iaddr, instr, i_ok, clock);
286     parameter memsize = 8192; // Number of bytes in memory
287     input  [63:0] maddr;      // Read/Write address
288     input          wenable;   // Write enable
289     input  [63:0] wdata;     // Write data
290     input          renable;   // Read enable
291     output [63:0] rdata;     // Read data
292     output          m_ok;    // Read & write addresses within range
293     input  [63:0] iaddr;     // Instruction address
294     output [79:0] instr;     // 10 bytes of instruction
295     output          i_ok;    // Instruction address within range
296     input          clock;
297
298     // Instruction bytes
299     wire [ 7:0]  ib0, ib1, ib2, ib3, ib4, ib5, ib6, ib7, ib8, ib9;
300 // Data bytes
301     wire [ 7:0]  db0, db1, db2, db3, db4, db5, db6, db7;
302
303     wire [ 3:0]  ibid  = iaddr[3:0]; // Instruction Bank ID
304     wire [59:0] iindex = iaddr[63:4]; // Address within bank
305     wire [59:0] iip1  = iindex+1;   // Next address within bank
306
307     wire [ 3:0]  mbid  = maddr[3:0]; // Data Bank ID
308     wire [59:0] mindex = maddr[63:4]; // Address within bank
309     wire [59:0] mip1  = mindex+1;   // Next address within bank
310
311     // Instruction addresses for each bank
312     wire [59:0]  addrI0, addrI1, addrI2, addrI3, addrI4, addrI5, addrI6, addrI7,
313                addrI8, addrI9, addrI10, addrI11, addrI12, addrI13, addrI14,
314                addrI15;
315     // Instruction data for each bank
316     wire [ 7:0]  outI0, outI1, outI2, outI3, outI4, outI5, outI6, outI7,
317                outI8, outI9, outI10, outI11, outI12, outI13, outI14, outI15;
318
319     // Data addresses for each bank
320     wire [59:0]  addrD0, addrD1, addrD2, addrD3, addrD4, addrD5, addrD6, addrD7,
321                addrD8, addrD9, addrD10, addrD11, addrD12, addrD13, addrD14,
322                addrD15;
323
324     // Data output for each bank

```



```

325 wire [ 7:0]   outD0, outD1, outD2, outD3, outD4, outD5, outD6, outD7,
326               outD8, outD9, outD10, outD11, outD12, outD13, outD14, outD15;
327
328 // Data input for each bank
329 wire [ 7:0]   inD0, inD1, inD2, inD3, inD4, inD5, inD6, inD7,
330               inD8, inD9, inD10, inD11, inD12, inD13, inD14, inD15;
331
332 // Data write enable signals for each bank
333 wire          dwEn0, dwEn1, dwEn2, dwEn3, dwEn4, dwEn5, dwEn6, dwEn7,
334               dwEn8, dwEn9, dwEn10, dwEn11, dwEn12, dwEn13, dwEn14, dwEn15;
335
336 // The bank memories
337 ram #(8, memsize/16, 60) bank0(clock,
338                               addrI0, 1'b0, 8'b0, 1'b1, outI0, // Instruction
339                               addrD0, dwEn0, inD0, renable, outD0); // Data
340
341 ram #(8, memsize/16, 60) bank1(clock,
342                               addrI1, 1'b0, 8'b0, 1'b1, outI1, // Instruction
343                               addrD1, dwEn1, inD1, renable, outD1); // Data
344
345 ram #(8, memsize/16, 60) bank2(clock,
346                               addrI2, 1'b0, 8'b0, 1'b1, outI2, // Instruction
347                               addrD2, dwEn2, inD2, renable, outD2); // Data
348
349 ram #(8, memsize/16, 60) bank3(clock,
350                               addrI3, 1'b0, 8'b0, 1'b1, outI3, // Instruction
351                               addrD3, dwEn3, inD3, renable, outD3); // Data
352
353 ram #(8, memsize/16, 60) bank4(clock,
354                               addrI4, 1'b0, 8'b0, 1'b1, outI4, // Instruction
355                               addrD4, dwEn4, inD4, renable, outD4); // Data
356
357 ram #(8, memsize/16, 60) bank5(clock,
358                               addrI5, 1'b0, 8'b0, 1'b1, outI5, // Instruction
359                               addrD5, dwEn5, inD5, renable, outD5); // Data
360
361 ram #(8, memsize/16, 60) bank6(clock,
362                               addrI6, 1'b0, 8'b0, 1'b1, outI6, // Instruction
363                               addrD6, dwEn6, inD6, renable, outD6); // Data
364
365 ram #(8, memsize/16, 60) bank7(clock,
366                               addrI7, 1'b0, 8'b0, 1'b1, outI7, // Instruction
367                               addrD7, dwEn7, inD7, renable, outD7); // Data
368
369 ram #(8, memsize/16, 60) bank8(clock,
370                               addrI8, 1'b0, 8'b0, 1'b1, outI8, // Instruction
371                               addrD8, dwEn8, inD8, renable, outD8); // Data
372
373 ram #(8, memsize/16, 60) bank9(clock,
374                               addrI9, 1'b0, 8'b0, 1'b1, outI9, // Instruction

```

```

375         addrD9, dwEn9, inD9, renable, outD9); // Data
376
377     ram #(8, memsize/16, 60) bank10(clock,
378         addrI10, 1'b0, 8'b0, 1'b1, outI10, // Instruction
379         addrD10, dwEn10, inD10, renable, outD10); // Data
380
381     ram #(8, memsize/16, 60) bank11(clock,
382         addrI11, 1'b0, 8'b0, 1'b1, outI11, // Instruction
383         addrD11, dwEn11, inD11, renable, outD11); // Data
384
385     ram #(8, memsize/16, 60) bank12(clock,
386         addrI12, 1'b0, 8'b0, 1'b1, outI12, // Instruction
387         addrD12, dwEn12, inD12, renable, outD12); // Data
388
389     ram #(8, memsize/16, 60) bank13(clock,
390         addrI13, 1'b0, 8'b0, 1'b1, outI13, // Instruction
391         addrD13, dwEn13, inD13, renable, outD13); // Data
392
393     ram #(8, memsize/16, 60) bank14(clock,
394         addrI14, 1'b0, 8'b0, 1'b1, outI14, // Instruction
395         addrD14, dwEn14, inD14, renable, outD14); // Data
396
397     ram #(8, memsize/16, 60) bank15(clock,
398         addrI15, 1'b0, 8'b0, 1'b1, outI15, // Instruction
399         addrD15, dwEn15, inD15, renable, outD15); // Data
400
401
402     // Determine the instruction addresses for the banks
403     assign     addrI0 = ibid >= 7 ? iip1 : iindex;
404     assign     addrI1 = ibid >= 8 ? iip1 : iindex;
405     assign     addrI2 = ibid >= 9 ? iip1 : iindex;
406     assign     addrI3 = ibid >= 10 ? iip1 : iindex;
407     assign     addrI4 = ibid >= 11 ? iip1 : iindex;
408     assign     addrI5 = ibid >= 12 ? iip1 : iindex;
409     assign     addrI6 = ibid >= 13 ? iip1 : iindex;
410     assign     addrI7 = ibid >= 14 ? iip1 : iindex;
411     assign     addrI8 = ibid >= 15 ? iip1 : iindex;
412     assign     addrI9 = iindex;
413     assign     addrI10 = iindex;
414     assign     addrI11 = iindex;
415     assign     addrI12 = iindex;
416     assign     addrI13 = iindex;
417     assign     addrI14 = iindex;
418     assign     addrI15 = iindex;
419
420
421     // Get the bytes of the instruction
422     assign     i_ok =
423         (iaddr + 9) < memsize;
424

```

```
425     assign      ib0 = !i_ok ? 0 :
426                ibid == 0 ? outI0 :
427                ibid == 1 ? outI1 :
428                ibid == 2 ? outI2 :
429                ibid == 3 ? outI3 :
430                ibid == 4 ? outI4 :
431                ibid == 5 ? outI5 :
432                ibid == 6 ? outI6 :
433                ibid == 7 ? outI7 :
434                ibid == 8 ? outI8 :
435                ibid == 9 ? outI9 :
436                ibid == 10 ? outI10 :
437                ibid == 11 ? outI11 :
438                ibid == 12 ? outI12 :
439                ibid == 13 ? outI13 :
440                ibid == 14 ? outI14 :
441                outI15;
442     assign      ib1 = !i_ok ? 0 :
443                ibid == 0 ? outI1 :
444                ibid == 1 ? outI2 :
445                ibid == 2 ? outI3 :
446                ibid == 3 ? outI4 :
447                ibid == 4 ? outI5 :
448                ibid == 5 ? outI6 :
449                ibid == 6 ? outI7 :
450                ibid == 7 ? outI8 :
451                ibid == 8 ? outI9 :
452                ibid == 9 ? outI10 :
453                ibid == 10 ? outI11 :
454                ibid == 11 ? outI12 :
455                ibid == 12 ? outI13 :
456                ibid == 13 ? outI14 :
457                ibid == 14 ? outI15 :
458                outI0;
459     assign      ib2 = !i_ok ? 0 :
460                ibid == 0 ? outI2 :
461                ibid == 1 ? outI3 :
462                ibid == 2 ? outI4 :
463                ibid == 3 ? outI5 :
464                ibid == 4 ? outI6 :
465                ibid == 5 ? outI7 :
466                ibid == 6 ? outI8 :
467                ibid == 7 ? outI9 :
468                ibid == 8 ? outI10 :
469                ibid == 9 ? outI11 :
470                ibid == 10 ? outI12 :
471                ibid == 11 ? outI13 :
472                ibid == 12 ? outI14 :
473                ibid == 13 ? outI15 :
474                ibid == 14 ? outI0 :
```

```

475         outI1;
476     assign    ib3 = !i_ok ? 0 :
477             ibid == 0 ? outI3 :
478             ibid == 1 ? outI4 :
479             ibid == 2 ? outI5 :
480             ibid == 3 ? outI6 :
481             ibid == 4 ? outI7 :
482             ibid == 5 ? outI8 :
483             ibid == 6 ? outI9 :
484             ibid == 7 ? outI10 :
485             ibid == 8 ? outI11 :
486             ibid == 9 ? outI12 :
487             ibid == 10 ? outI13 :
488             ibid == 11 ? outI14 :
489             ibid == 12 ? outI15 :
490             ibid == 13 ? outI0 :
491             ibid == 14 ? outI1 :
492         outI2;
493     assign    ib4 = !i_ok ? 0 :
494             ibid == 0 ? outI4 :
495             ibid == 1 ? outI5 :
496             ibid == 2 ? outI6 :
497             ibid == 3 ? outI7 :
498             ibid == 4 ? outI8 :
499             ibid == 5 ? outI9 :
500             ibid == 6 ? outI10 :
501             ibid == 7 ? outI11 :
502             ibid == 8 ? outI12 :
503             ibid == 9 ? outI13 :
504             ibid == 10 ? outI14 :
505             ibid == 11 ? outI15 :
506             ibid == 12 ? outI0 :
507             ibid == 13 ? outI1 :
508             ibid == 14 ? outI2 :
509         outI3;
510     assign    ib5 = !i_ok ? 0 :
511             ibid == 0 ? outI5 :
512             ibid == 1 ? outI6 :
513             ibid == 2 ? outI7 :
514             ibid == 3 ? outI8 :
515             ibid == 4 ? outI9 :
516             ibid == 5 ? outI10 :
517             ibid == 6 ? outI11 :
518             ibid == 7 ? outI12 :
519             ibid == 8 ? outI13 :
520             ibid == 9 ? outI14 :
521             ibid == 10 ? outI15 :
522             ibid == 11 ? outI0 :
523             ibid == 12 ? outI1 :
524             ibid == 13 ? outI2 :

```

```
525         ibid == 14 ? outI3 :
526         outI4;
527     assign    ib6 = !i_ok ? 0 :
528             ibid == 0 ? outI6 :
529             ibid == 1 ? outI7 :
530             ibid == 2 ? outI8 :
531             ibid == 3 ? outI9 :
532             ibid == 4 ? outI10 :
533             ibid == 5 ? outI11 :
534             ibid == 6 ? outI12 :
535             ibid == 7 ? outI13 :
536             ibid == 8 ? outI14 :
537             ibid == 9 ? outI15 :
538             ibid == 10 ? outI0 :
539             ibid == 11 ? outI1 :
540             ibid == 12 ? outI2 :
541             ibid == 13 ? outI3 :
542             ibid == 14 ? outI4 :
543         outI5;
544     assign    ib7 = !i_ok ? 0 :
545             ibid == 0 ? outI7 :
546             ibid == 1 ? outI8 :
547             ibid == 2 ? outI9 :
548             ibid == 3 ? outI10 :
549             ibid == 4 ? outI11 :
550             ibid == 5 ? outI12 :
551             ibid == 6 ? outI13 :
552             ibid == 7 ? outI14 :
553             ibid == 8 ? outI15 :
554             ibid == 9 ? outI0 :
555             ibid == 10 ? outI1 :
556             ibid == 11 ? outI2 :
557             ibid == 12 ? outI3 :
558             ibid == 13 ? outI4 :
559             ibid == 14 ? outI5 :
560         outI6;
561     assign    ib8 = !i_ok ? 0 :
562             ibid == 0 ? outI8 :
563             ibid == 1 ? outI9 :
564             ibid == 2 ? outI10 :
565             ibid == 3 ? outI11 :
566             ibid == 4 ? outI12 :
567             ibid == 5 ? outI13 :
568             ibid == 6 ? outI14 :
569             ibid == 7 ? outI15 :
570             ibid == 8 ? outI0 :
571             ibid == 9 ? outI1 :
572             ibid == 10 ? outI2 :
573             ibid == 11 ? outI3 :
574             ibid == 12 ? outI4 :
```

```

575         ibid == 13 ? outI5 :
576         ibid == 14 ? outI6 :
577         outI7;
578     assign    ib9 = !i_ok ? 0 :
579             ibid == 0 ? outI9 :
580             ibid == 1 ? outI10 :
581             ibid == 2 ? outI11 :
582             ibid == 3 ? outI12 :
583             ibid == 4 ? outI13 :
584             ibid == 5 ? outI14 :
585             ibid == 6 ? outI15 :
586             ibid == 7 ? outI0 :
587             ibid == 8 ? outI1 :
588             ibid == 9 ? outI2 :
589             ibid == 10 ? outI3 :
590             ibid == 11 ? outI4 :
591             ibid == 12 ? outI5 :
592             ibid == 13 ? outI6 :
593             ibid == 14 ? outI7 :
594             outI8;
595
596     assign    instr[ 7: 0] = ib0;
597     assign    instr[15: 8] = ib1;
598     assign    instr[23:16] = ib2;
599     assign    instr[31:24] = ib3;
600     assign    instr[39:32] = ib4;
601     assign    instr[47:40] = ib5;
602     assign    instr[55:48] = ib6;
603     assign    instr[63:56] = ib7;
604     assign    instr[71:64] = ib8;
605     assign    instr[79:72] = ib9;
606
607     assign    m_ok =
608             (!renable & !wenable | (maddr + 7) < memsize);
609
610     assign    addrD0 = mbid >= 9 ? mip1 : mindex;
611     assign    addrD1 = mbid >= 10 ? mip1 : mindex;
612     assign    addrD2 = mbid >= 11 ? mip1 : mindex;
613     assign    addrD3 = mbid >= 12 ? mip1 : mindex;
614     assign    addrD4 = mbid >= 13 ? mip1 : mindex;
615     assign    addrD5 = mbid >= 14 ? mip1 : mindex;
616     assign    addrD6 = mbid >= 15 ? mip1 : mindex;
617     assign    addrD7 = mindex;
618     assign    addrD8 = mindex;
619     assign    addrD9 = mindex;
620     assign    addrD10 = mindex;
621     assign    addrD11 = mindex;
622     assign    addrD12 = mindex;
623     assign    addrD13 = mindex;
624     assign    addrD14 = mindex;

```

```
625     assign          addrD15 = mindex;
626
627     // Get the bytes of data;
628     assign          db0 = !m_ok ? 0      :
629                   mbid == 0 ? outD0    :
630                   mbid == 1 ? outD1    :
631                   mbid == 2 ? outD2    :
632                   mbid == 3 ? outD3    :
633                   mbid == 4 ? outD4    :
634                   mbid == 5 ? outD5    :
635                   mbid == 6 ? outD6    :
636                   mbid == 7 ? outD7    :
637                   mbid == 8 ? outD8    :
638                   mbid == 9 ? outD9    :
639                   mbid == 10 ? outD10  :
640                   mbid == 11 ? outD11  :
641                   mbid == 12 ? outD12  :
642                   mbid == 13 ? outD13  :
643                   mbid == 14 ? outD14  :
644                   outD15;
645     assign          db1 = !m_ok ? 0      :
646                   mbid == 0 ? outD1    :
647                   mbid == 1 ? outD2    :
648                   mbid == 2 ? outD3    :
649                   mbid == 3 ? outD4    :
650                   mbid == 4 ? outD5    :
651                   mbid == 5 ? outD6    :
652                   mbid == 6 ? outD7    :
653                   mbid == 7 ? outD8    :
654                   mbid == 8 ? outD9    :
655                   mbid == 9 ? outD10  :
656                   mbid == 10 ? outD11  :
657                   mbid == 11 ? outD12  :
658                   mbid == 12 ? outD13  :
659                   mbid == 13 ? outD14  :
660                   mbid == 14 ? outD15  :
661                   outD0;
662     assign          db2 = !m_ok ? 0      :
663                   mbid == 0 ? outD2    :
664                   mbid == 1 ? outD3    :
665                   mbid == 2 ? outD4    :
666                   mbid == 3 ? outD5    :
667                   mbid == 4 ? outD6    :
668                   mbid == 5 ? outD7    :
669                   mbid == 6 ? outD8    :
670                   mbid == 7 ? outD9    :
671                   mbid == 8 ? outD10  :
672                   mbid == 9 ? outD11  :
673                   mbid == 10 ? outD12  :
674                   mbid == 11 ? outD13  :
```

```

675         mbid == 12 ? outD14 :
676         mbid == 13 ? outD15 :
677         mbid == 14 ? outD0  :
678         outD1;
679     assign    db3 = !m_ok ? 0      :
680         mbid == 0  ? outD3  :
681         mbid == 1  ? outD4  :
682         mbid == 2  ? outD5  :
683         mbid == 3  ? outD6  :
684         mbid == 4  ? outD7  :
685         mbid == 5  ? outD8  :
686         mbid == 6  ? outD9  :
687         mbid == 7  ? outD10 :
688         mbid == 8  ? outD11 :
689         mbid == 9  ? outD12 :
690         mbid == 10 ? outD13 :
691         mbid == 11 ? outD14 :
692         mbid == 12 ? outD15 :
693         mbid == 13 ? outD0  :
694         mbid == 14 ? outD1  :
695         outD2;
696     assign    db4 = !m_ok ? 0      :
697         mbid == 0  ? outD4  :
698         mbid == 1  ? outD5  :
699         mbid == 2  ? outD6  :
700         mbid == 3  ? outD7  :
701         mbid == 4  ? outD8  :
702         mbid == 5  ? outD9  :
703         mbid == 6  ? outD10 :
704         mbid == 7  ? outD11 :
705         mbid == 8  ? outD12 :
706         mbid == 9  ? outD13 :
707         mbid == 10 ? outD14 :
708         mbid == 11 ? outD15 :
709         mbid == 12 ? outD0  :
710         mbid == 13 ? outD1  :
711         mbid == 14 ? outD2  :
712         outD3;
713     assign    db5 = !m_ok ? 0 :
714         mbid == 0  ? outD5  :
715         mbid == 1  ? outD6  :
716         mbid == 2  ? outD7  :
717         mbid == 3  ? outD8  :
718         mbid == 4  ? outD9  :
719         mbid == 5  ? outD10 :
720         mbid == 6  ? outD11 :
721         mbid == 7  ? outD12 :
722         mbid == 8  ? outD13 :
723         mbid == 9  ? outD14 :
724         mbid == 10 ? outD15 :

```



```

725         mbid == 11 ? outD0 :
726         mbid == 12 ? outD1 :
727         mbid == 13 ? outD2 :
728         mbid == 14 ? outD3 :
729         outD4;
730     assign    db6 = !m_ok ? 0      :
731         mbid == 0  ? outD6 :
732         mbid == 1  ? outD7 :
733         mbid == 2  ? outD8 :
734         mbid == 3  ? outD9 :
735         mbid == 4  ? outD10 :
736         mbid == 5  ? outD11 :
737         mbid == 6  ? outD12 :
738         mbid == 7  ? outD13 :
739         mbid == 8  ? outD14 :
740         mbid == 9  ? outD15 :
741         mbid == 10 ? outD0 :
742         mbid == 11 ? outD1 :
743         mbid == 12 ? outD2 :
744         mbid == 13 ? outD3 :
745         mbid == 14 ? outD4 :
746         outD5;
747     assign    db7 = !m_ok ? 0      :
748         mbid == 0  ? outD7 :
749         mbid == 1  ? outD8 :
750         mbid == 2  ? outD9 :
751         mbid == 3  ? outD10 :
752         mbid == 4  ? outD11 :
753         mbid == 5  ? outD12 :
754         mbid == 6  ? outD13 :
755         mbid == 7  ? outD14 :
756         mbid == 8  ? outD15 :
757         mbid == 9  ? outD0 :
758         mbid == 10 ? outD1 :
759         mbid == 11 ? outD2 :
760         mbid == 12 ? outD3 :
761         mbid == 13 ? outD4 :
762         mbid == 14 ? outD5 :
763         outD6;
764
765     assign    rdata[ 7: 0] = db0;
766     assign    rdata[15: 8] = db1;
767     assign    rdata[23:16] = db2;
768     assign    rdata[31:24] = db3;
769     assign    rdata[39:32] = db4;
770     assign    rdata[47:40] = db5;
771     assign    rdata[55:48] = db6;
772     assign    rdata[63:56] = db7;
773
774     wire [7:0] wd0 = wdata[ 7: 0];

```

```
775 wire [7:0] wd1 = wdata[15: 8];
776 wire [7:0] wd2 = wdata[23:16];
777 wire [7:0] wd3 = wdata[31:24];
778 wire [7:0] wd4 = wdata[39:32];
779 wire [7:0] wd5 = wdata[47:40];
780 wire [7:0] wd6 = wdata[55:48];
781 wire [7:0] wd7 = wdata[63:56];
782
783 assign      inD0 =
784             mbid == 9 ? wd7 :
785             mbid == 10 ? wd6 :
786             mbid == 11 ? wd5 :
787             mbid == 12 ? wd4 :
788             mbid == 13 ? wd3 :
789             mbid == 14 ? wd2 :
790             mbid == 15 ? wd1 :
791             mbid == 0 ? wd0 :
792             0;
793
794 assign      inD1 =
795             mbid == 10 ? wd7 :
796             mbid == 11 ? wd6 :
797             mbid == 12 ? wd5 :
798             mbid == 13 ? wd4 :
799             mbid == 14 ? wd3 :
800             mbid == 15 ? wd2 :
801             mbid == 0 ? wd1 :
802             mbid == 1 ? wd0 :
803             0;
804
805 assign      inD2 =
806             mbid == 11 ? wd7 :
807             mbid == 12 ? wd6 :
808             mbid == 13 ? wd5 :
809             mbid == 14 ? wd4 :
810             mbid == 15 ? wd3 :
811             mbid == 0 ? wd2 :
812             mbid == 1 ? wd1 :
813             mbid == 2 ? wd0 :
814             0;
815
816 assign      inD3 =
817             mbid == 12 ? wd7 :
818             mbid == 13 ? wd6 :
819             mbid == 14 ? wd5 :
820             mbid == 15 ? wd4 :
821             mbid == 0 ? wd3 :
822             mbid == 1 ? wd2 :
823             mbid == 2 ? wd1 :
824             mbid == 3 ? wd0 :
```

```
825         0;
826
827     assign    inD4 =
828         mbid == 13 ? wd7 :
829         mbid == 14 ? wd6 :
830         mbid == 15 ? wd5 :
831         mbid == 0 ? wd4 :
832         mbid == 1 ? wd3 :
833         mbid == 2 ? wd2 :
834         mbid == 3 ? wd1 :
835         mbid == 4 ? wd0 :
836     0;
837
838     assign    inD5 =
839         mbid == 14 ? wd7 :
840         mbid == 15 ? wd6 :
841         mbid == 0 ? wd5 :
842         mbid == 1 ? wd4 :
843         mbid == 2 ? wd3 :
844         mbid == 3 ? wd2 :
845         mbid == 4 ? wd1 :
846         mbid == 5 ? wd0 :
847     0;
848
849     assign    inD6 =
850         mbid == 15 ? wd7 :
851         mbid == 0 ? wd6 :
852         mbid == 1 ? wd5 :
853         mbid == 2 ? wd4 :
854         mbid == 3 ? wd3 :
855         mbid == 4 ? wd2 :
856         mbid == 5 ? wd1 :
857         mbid == 6 ? wd0 :
858     0;
859
860     assign    inD7 =
861         mbid == 0 ? wd7 :
862         mbid == 1 ? wd6 :
863         mbid == 2 ? wd5 :
864         mbid == 3 ? wd4 :
865         mbid == 4 ? wd3 :
866         mbid == 5 ? wd2 :
867         mbid == 6 ? wd1 :
868         mbid == 7 ? wd0 :
869     0;
870
871     assign    inD8 =
872         mbid == 1 ? wd7 :
873         mbid == 2 ? wd6 :
874         mbid == 3 ? wd5 :
```

```
875         mbid == 4 ? wd4 :
876         mbid == 5 ? wd3 :
877         mbid == 6 ? wd2 :
878         mbid == 7 ? wd1 :
879         mbid == 8 ? wd0 :
880         0;
881
882     assign    inD9 =
883         mbid == 2 ? wd7 :
884         mbid == 3 ? wd6 :
885         mbid == 4 ? wd5 :
886         mbid == 5 ? wd4 :
887         mbid == 6 ? wd3 :
888         mbid == 7 ? wd2 :
889         mbid == 8 ? wd1 :
890         mbid == 9 ? wd0 :
891         0;
892
893     assign    inD10 =
894         mbid == 3 ? wd7 :
895         mbid == 4 ? wd6 :
896         mbid == 5 ? wd5 :
897         mbid == 6 ? wd4 :
898         mbid == 7 ? wd3 :
899         mbid == 8 ? wd2 :
900         mbid == 9 ? wd1 :
901         mbid == 10 ? wd0 :
902         0;
903
904     assign    inD11 =
905         mbid == 4 ? wd7 :
906         mbid == 5 ? wd6 :
907         mbid == 6 ? wd5 :
908         mbid == 7 ? wd4 :
909         mbid == 8 ? wd3 :
910         mbid == 9 ? wd2 :
911         mbid == 10 ? wd1 :
912         mbid == 11 ? wd0 :
913         0;
914
915     assign    inD12 =
916         mbid == 5 ? wd7 :
917         mbid == 6 ? wd6 :
918         mbid == 7 ? wd5 :
919         mbid == 8 ? wd4 :
920         mbid == 9 ? wd3 :
921         mbid == 10 ? wd2 :
922         mbid == 11 ? wd1 :
923         mbid == 12 ? wd0 :
924         0;
```

```

925
926     assign          inD13 =
927                     mbid == 6 ? wd7  :
928                     mbid == 7 ? wd6  :
929                     mbid == 8 ? wd5  :
930                     mbid == 9 ? wd4  :
931                     mbid == 10 ? wd3 :
932                     mbid == 11 ? wd2 :
933                     mbid == 12 ? wd1 :
934                     mbid == 13 ? wd0 :
935                     0;
936
937     assign          inD14 =
938                     mbid == 7 ? wd7  :
939                     mbid == 8 ? wd6  :
940                     mbid == 9 ? wd5  :
941                     mbid == 10 ? wd4 :
942                     mbid == 11 ? wd3 :
943                     mbid == 12 ? wd2 :
944                     mbid == 13 ? wd1 :
945                     mbid == 14 ? wd0 :
946                     0;
947
948     assign          inD15 =
949                     mbid == 8 ? wd7  :
950                     mbid == 9 ? wd6  :
951                     mbid == 10 ? wd5 :
952                     mbid == 11 ? wd4 :
953                     mbid == 12 ? wd3 :
954                     mbid == 13 ? wd2 :
955                     mbid == 14 ? wd1 :
956                     mbid == 15 ? wd0 :
957                     0;
958
959     // Which banks get written
960     assign          dwEn0 = wenable & (mbid <= 0 | mbid >= 9);
961     assign          dwEn1 = wenable & (mbid <= 1 | mbid >= 10);
962     assign          dwEn2 = wenable & (mbid <= 2 | mbid >= 11);
963     assign          dwEn3 = wenable & (mbid <= 3 | mbid >= 12);
964     assign          dwEn4 = wenable & (mbid <= 4 | mbid >= 13);
965     assign          dwEn5 = wenable & (mbid <= 5 | mbid >= 14);
966     assign          dwEn6 = wenable & (mbid <= 6 | mbid >= 15);
967     assign          dwEn7 = wenable & (mbid <= 7);
968     assign          dwEn8 = wenable & (mbid >= 1 & mbid <= 8);
969     assign          dwEn9 = wenable & (mbid >= 2 & mbid <= 9);
970     assign          dwEn10 = wenable & (mbid >= 3 & mbid <= 10);
971     assign          dwEn11 = wenable & (mbid >= 4 & mbid <= 11);
972     assign          dwEn12 = wenable & (mbid >= 5 & mbid <= 12);
973     assign          dwEn13 = wenable & (mbid >= 6 & mbid <= 13);
974     assign          dwEn14 = wenable & (mbid >= 7 & mbid <= 14);

```

```

975     assign          dwEn15 = wenable & (mbid >= 8);
976
977 endmodule
978
979
980 // Combinational blocks
981
982 // Fetch stage
983
984 // Split instruction byte into icode and ifun fields
985 module split(itype, icode, ifun);
986     input  [7:0] itype;
987     output [3:0] icode;
988     output [3:0] ifun;
989
990     assign          icode = itype[7:4];
991     assign          ifun  = itype[3:0];
992 endmodule
993
994 // Extract immediate word from 9 bytes of instruction
995 module align(itypes, need_regids, rA, rB, valC);
996     input  [71:0] itypes;
997     input          need_regids;
998     output [ 3:0] rA;
999     output [ 3:0] rB;
1000    output [63:0] valC;
1001    assign          rA = itypes[7:4];
1002    assign          rB = itypes[3:0];
1003    assign          valC = need_regids ? itypes[71:8] : itypes[63:0];
1004 endmodule
1005
1006 // PC incrementer
1007 module pc_increment(pc, need_regids, need_valC, valP);
1008     input  [63:0] pc;
1009     input          need_regids;
1010     input          need_valC;
1011     output [63:0] valP;
1012     assign          valP = pc + 1 + 8*need_valC + need_regids;
1013 endmodule
1014
1015 // Execute Stage
1016
1017 // ALU
1018 module alu(aluA, aluB, alufun, valE, new_cc);
1019     input  [63:0] aluA, aluB;    // Data inputs
1020     input  [ 3:0] alufun;        // ALU function
1021     output [63:0] valE;          // Data Output
1022     output [ 2:0] new_cc;        // New values for ZF, SF, OF
1023
1024     parameter      ALUADD = 4'h0;

```

```

1025 parameter    ALUSUB = 4'h1;
1026 parameter    ALUAND = 4'h2;
1027 parameter    ALUXOR = 4'h3;
1028
1029 assign        vale =
1030              alufun == ALUSUB ? aluB - aluA :
1031              alufun == ALUAND ? aluB & aluA :
1032              alufun == ALUXOR ? aluB ^ aluA :
1033              aluB + aluA;
1034 assign        new_cc[2] = (vale == 0); // ZF
1035 assign        new_cc[1] = vale[63]; // SF
1036 assign        new_cc[0] = // OF
1037              alufun == ALUADD ?
1038              (aluA[63] == aluB[63]) & (aluA[63] != vale[63]) :
1039              alufun == ALUSUB ?
1040              (~aluA[63] == aluB[63]) & (aluB[63] != vale[63]) :
1041              0;
1042 endmodule
1043
1044
1045 // Condition code register
1046 module cc(cc, new_cc, set_cc, reset, clock);
1047     output [2:0] cc;
1048     input  [2:0] new_cc;
1049     input          set_cc;
1050     input          reset;
1051     input          clock;
1052
1053     cenreg #(3) c(cc, new_cc, set_cc, reset, 3'b100, clock);
1054 endmodule
1055
1056 // branch condition logic
1057 module cond(ifun, cc, Cnd);
1058     input [3:0] ifun;
1059     input [2:0] cc;
1060     output      Cnd;
1061
1062     wire      zf = cc[2];
1063     wire      sf = cc[1];
1064     wire      of = cc[0];
1065
1066     // Jump & move conditions.
1067     parameter C_YES  = 4'h0;
1068     parameter C_LE   = 4'h1;
1069     parameter C_L    = 4'h2;
1070     parameter C_E    = 4'h3;
1071     parameter C_NE   = 4'h4;
1072     parameter C_GE   = 4'h5;
1073     parameter C_G    = 4'h6;
1074

```

```

1075     assign      Cnd =
1076                (ifun == C_YES) |           //
1077                (ifun == C_LE & ((sf^of)|zf)) | // <=
1078                (ifun == C_L  & (sf^of)) |   // <
1079                (ifun == C_E  & zf) |       // ==
1080                (ifun == C_NE & ~zf) |      // !=
1081                (ifun == C_GE & (~sf^of)) |  // >=
1082                (ifun == C_G  & (~sf^of)&~zf); // >
1083
1084 endmodule
1085
1086 // -----
1087 // Processor implementation
1088 // -----
1089
1090
1091 // The processor can run in 5 different modes:
1092 // RUN:      Normal operation
1093 // RESET:    Sets PC to 0, clears all pipe registers;
1094 //           Initializes condition codes
1095 // DOWNLOAD: Download bytes from controller into memory
1096 // UPLOAD:   Upload bytes from memory to controller
1097 // STATUS:   Upload other status information to controller
1098
1099 // Processor module
1100 module processor(mode, udaddr, idata, odata, stat, clock);
1101     input  [ 2:0] mode; // Signal operating mode to processor
1102     input  [63:0] udaddr; // Upload/download address
1103     input  [63:0] idata; // Download data word
1104     output [63:0] odata; // Upload data word
1105     output [ 2:0] stat; // Status
1106     input          clock; // Clock input
1107
1108 // Define modes
1109     parameter RUN_MODE = 0; // Normal operation
1110     parameter RESET_MODE = 1; // Resetting processor;
1111     parameter DOWNLOAD_MODE = 2; // Transferring to memory
1112     parameter UPLOAD_MODE = 3; // Reading from memory
1113     // Uploading register & other status information
1114     parameter STATUS_MODE = 4;
1115
1116 // Constant values
1117
1118 // Instruction codes
1119     parameter IHALT = 4'h0;
1120     parameter INOP = 4'h1;
1121     parameter IRRMOVQ = 4'h2;
1122     parameter IIRMOVQ = 4'h3;
1123     parameter IRMMOVQ = 4'h4;
1124     parameter IMRMVQ = 4'h5;

```



```

1125 parameter IOPQ      = 4'h6;
1126 parameter IJXX      = 4'h7;
1127 parameter ICALL      = 4'h8;
1128 parameter IRET       = 4'h9;
1129 parameter IPUSHQ     = 4'hA;
1130 parameter IPOPQ      = 4'hB;
1131 parameter IIADDQ     = 4'hC;
1132 parameter ILEAVE     = 4'hD;
1133 parameter IPOP2      = 4'hE;
1134
1135 // Function codes
1136 parameter FNONE      = 4'h0;
1137
1138 // Jump conditions
1139 parameter UNCOND     = 4'h0;
1140
1141 // Register IDs
1142 parameter RRSP       = 4'h4;
1143 parameter RRBP       = 4'h5;
1144 parameter RNONE      = 4'hF;
1145
1146 // ALU operations
1147 parameter ALUADD     = 4'h0;
1148
1149 // Status conditions
1150 parameter SBUB       = 3'h0;
1151 parameter SAOK       = 3'h1;
1152 parameter SHLT       = 3'h2;
1153 parameter SADR       = 3'h3;
1154 parameter SINS       = 3'h4;
1155 parameter SPIP       = 3'h5;
1156
1157 // Fetch stage signals
1158 wire [63:0] f_predPC, F_predPC, f_pc;
1159 wire      f_ok;
1160 wire      imem_error;
1161 wire [ 2:0] f_stat;
1162 wire [79:0] f_instr;
1163 wire [ 3:0] imem_icode;
1164 wire [ 3:0] imem_ifun;
1165 wire [ 3:0] f_icode;
1166 wire [ 3:0] f_ifun;
1167 wire [ 3:0] f_rA;
1168 wire [ 3:0] f_rB;
1169 wire [63:0] f_valC;
1170 wire [63:0] f_valP;
1171 wire      need_regids;
1172 wire      need_valC;
1173 wire      instr_valid;
1174 wire      F_stall, F_bubble;

```

```

1175
1176 // Decode stage signals
1177   wire [ 2:0] D_stat;
1178   wire [63:0] D_pc;
1179   wire [ 3:0] D_icode;
1180   wire [ 3:0] D_ifun;
1181   wire [ 3:0] D_rA;
1182   wire [ 3:0] D_rB;
1183   wire [63:0] D_valC;
1184   wire [63:0] D_valP;
1185
1186   wire [63:0] d_valA;
1187   wire [63:0] d_valB;
1188   wire [63:0] d_rvalA;
1189   wire [63:0] d_rvalB;
1190   wire [ 3:0] d_dstE;
1191   wire [ 3:0] d_dstM;
1192   wire [ 3:0] d_srcA;
1193   wire [ 3:0] d_srcB;
1194   wire          D_stall, D_bubble;
1195
1196 // Execute stage signals
1197   wire [ 2:0] E_stat;
1198   wire [63:0] E_pc;
1199   wire [ 3:0] E_icode;
1200   wire [ 3:0] E_ifun;
1201   wire [63:0] E_valC;
1202   wire [63:0] E_valA;
1203   wire [63:0] E_valB;
1204   wire [ 3:0] E_dstE;
1205   wire [ 3:0] E_dstM;
1206   wire [ 3:0] E_srcA;
1207   wire [ 3:0] E_srcB;
1208
1209   wire [63:0] aluA;
1210   wire [63:0] aluB;
1211   wire          set_cc;
1212   wire [ 2:0] cc;
1213   wire [ 2:0] new_cc;
1214   wire [ 3:0] alufun;
1215   wire          e_Cnd;
1216   wire [63:0] e_valE;
1217   wire [63:0] e_valA;
1218   wire [ 3:0] e_dstE;
1219   wire          E_stall, E_bubble;
1220
1221 // Memory stage
1222   wire [ 2:0] M_stat;
1223   wire [63:0] M_pc;
1224   wire [ 3:0] M_icode;

```

```

1225 wire [ 3:0] M_ifun;
1226 wire      M_Cnd;
1227 wire [63:0] M_valE;
1228 wire [63:0] M_valA;
1229 wire [ 3:0] M_dstE;
1230 wire [ 3:0] M_dstM;
1231
1232 wire [ 2:0] m_stat;
1233 wire [63:0] mem_addr;
1234 wire [63:0] mem_data;
1235 wire      mem_read;
1236 wire      mem_write;
1237 wire [63:0] m_valM;
1238 wire      M_stall, M_bubble;
1239 wire      m_ok;
1240
1241 // Write-back stage
1242 wire [ 2:0] W_stat;
1243 wire [63:0] W_pc;
1244 wire [ 3:0] W_icode;
1245 wire [63:0] W_valE;
1246 wire [63:0] W_valM;
1247 wire [ 3:0] W_dstE;
1248 wire [ 3:0] W_dstM;
1249 wire [63:0] w_valE;
1250 wire [63:0] w_valM;
1251 wire [ 3:0] w_dstE;
1252 wire [ 3:0] w_dstM;
1253 wire      W_stall, W_bubble;
1254
1255 // Global status
1256 wire [ 2:0] Stat;
1257
1258 // Debugging logic
1259 wire [63:0] rax, rcx, rdx, rbx, rsp, rbp, rsi, rdi,
1260           r8, r9, r10, r11, r12, r13, r14;
1261 wire zf = cc[2];
1262 wire sf = cc[1];
1263 wire of = cc[0];
1264
1265 // Control signals
1266 wire resetting = (mode == RESET_MODE);
1267 wire uploading = (mode == UPLOAD_MODE);
1268 wire downloading = (mode == DOWNLOAD_MODE);
1269 wire running = (mode == RUN_MODE);
1270 wire getting_info = (mode == STATUS_MODE);
1271 // Logic to control resetting of pipeline registers
1272 wire F_reset = F_bubble | resetting;
1273 wire D_reset = D_bubble | resetting;
1274 wire E_reset = E_bubble | resetting;

```

```

1275 wire M_reset = M_bubble | resetting;
1276 wire W_reset = W_bubble | resetting;
1277
1278 // Processor status
1279 assign stat = Stat;
1280 // Output data
1281 assign odata =
1282 // When getting status, get either register or special status value
1283 getting_info ?
1284 (udaddr == 0 ? rax :
1285  udaddr == 8 ? rcx :
1286  udaddr == 16 ? rdx :
1287  udaddr == 24 ? rbx :
1288  udaddr == 32 ? rsp :
1289  udaddr == 40 ? rbp :
1290  udaddr == 48 ? rsi :
1291  udaddr == 56 ? rdi :
1292  udaddr == 64 ? r8 :
1293  udaddr == 72 ? r9 :
1294  udaddr == 80 ? r10 :
1295  udaddr == 88 ? r11 :
1296  udaddr == 96 ? r12 :
1297  udaddr == 104 ? r13 :
1298  udaddr == 112 ? r14 :
1299  udaddr == 120 ? cc :
1300  udaddr == 128 ? W_pc : 0)
1301 : m_valM;
1302
1303 // Pipeline registers
1304
1305 // All pipeline registers are implemented with module
1306 // preg(out, in, stall, bubble, bubbleval, clock)
1307 // F Register
1308 preg #(64) F_predPC_reg(F_predPC, f_predPC, F_stall, F_reset, 64'b0, clock);
1309 // D Register
1310 preg #(3) D_stat_reg(D_stat, f_stat, D_stall, D_reset, SBUB, clock);
1311 preg #(64) D_pc_reg(D_pc, f_pc, D_stall, D_reset, 64'b0, clock);
1312 preg #(4) D_icode_reg(D_icode, f_icode, D_stall, D_reset, INOP, clock);
1313 preg #(4) D_ifun_reg(D_ifun, f_ifun, D_stall, D_reset, FNONE, clock);
1314 preg #(4) D_rA_reg(D_rA, f_rA, D_stall, D_reset, RNONE, clock);
1315 preg #(4) D_rB_reg(D_rB, f_rB, D_stall, D_reset, RNONE, clock);
1316 preg #(64) D_valC_reg(D_valC, f_valC, D_stall, D_reset, 64'b0, clock);
1317 preg #(64) D_valP_reg(D_valP, f_valP, D_stall, D_reset, 64'b0, clock);
1318 // E Register
1319 preg #(3) E_stat_reg(E_stat, D_stat, E_stall, E_reset, SBUB, clock);
1320 preg #(64) E_pc_reg(E_pc, D_pc, E_stall, E_reset, 64'b0, clock);
1321 preg #(4) E_icode_reg(E_icode, D_icode, E_stall, E_reset, INOP, clock);
1322 preg #(4) E_ifun_reg(E_ifun, D_ifun, E_stall, E_reset, FNONE, clock);
1323 preg #(64) E_valC_reg(E_valC, D_valC, E_stall, E_reset, 64'b0, clock);
1324 preg #(64) E_valA_reg(E_valA, d_valA, E_stall, E_reset, 64'b0, clock);

```

```

1325 preg #(64) E_valB_reg(E_valB, d_valB, E_stall, E_reset, 64'b0, clock);
1326 preg #(4) E_dstE_reg(E_dstE, d_dstE, E_stall, E_reset, RNONE, clock);
1327 preg #(4) E_dstM_reg(E_dstM, d_dstM, E_stall, E_reset, RNONE, clock);
1328 preg #(4) E_srcA_reg(E_srcA, d_srcA, E_stall, E_reset, RNONE, clock);
1329 preg #(4) E_srcB_reg(E_srcB, d_srcB, E_stall, E_reset, RNONE, clock);
1330 // M Register
1331 preg #(3) M_stat_reg(M_stat, E_stat, M_stall, M_reset, SBUB, clock);
1332 preg #(64) M_pc_reg(M_pc, E_pc, M_stall, M_reset, 64'b0, clock);
1333 preg #(4) M_icode_reg(M_icode, E_icode, M_stall, M_reset, INOP, clock);
1334 preg #(4) M_ifun_reg(M_ifun, E_ifun, M_stall, M_reset, FNONE, clock);
1335 preg #(1) M_Cnd_reg(M_Cnd, e_Cnd, M_stall, M_reset, 1'b0, clock);
1336 preg #(64) M_valE_reg(M_valE, e_valE, M_stall, M_reset, 64'b0, clock);
1337 preg #(64) M_valA_reg(M_valA, e_valA, M_stall, M_reset, 64'b0, clock);
1338 preg #(4) M_dstE_reg(M_dstE, e_dstE, M_stall, M_reset, RNONE, clock);
1339 preg #(4) M_dstM_reg(M_dstM, E_dstM, M_stall, M_reset, RNONE, clock);
1340 // W Register
1341 preg #(3) W_stat_reg(W_stat, m_stat, W_stall, W_reset, SBUB, clock);
1342 preg #(64) W_pc_reg(W_pc, M_pc, W_stall, W_reset, 64'b0, clock);
1343 preg #(4) W_icode_reg(W_icode, M_icode, W_stall, W_reset, INOP, clock);
1344 preg #(64) W_valE_reg(W_valE, M_valE, W_stall, W_reset, 64'b0, clock);
1345 preg #(64) W_valM_reg(W_valM, m_valM, W_stall, W_reset, 64'b0, clock);
1346 preg #(4) W_dstE_reg(W_dstE, M_dstE, W_stall, W_reset, RNONE, clock);
1347 preg #(4) W_dstM_reg(W_dstM, M_dstM, W_stall, W_reset, RNONE, clock);
1348
1349 // Fetch stage logic
1350 split split(f_instr[7:0], imem_icode, imem_ifun);
1351 align align(f_instr[79:8], need_regids, f_rA, f_rB, f_valC);
1352 pc_increment pci(f_pc, need_regids, need_valC, f_valP);
1353
1354 // Decode stage
1355 regfile regf(w_dstE, w_valE, w_dstM, w_valM,
1356             d_srcA, d_rvalA, d_srcB, d_rvalB, resetting, clock,
1357             rax, rcx, rdx, rbx, rsp, rbp, rsi, rdi,
1358             r8, r9, r10, r11, r12, r13, r14);
1359
1360
1361 // Execute stage
1362 alu alu(aluA, aluB, alufun, e_valE, new_cc);
1363 cc ccreg(cc, new_cc,
1364         // Only update CC when everything is running normally
1365         running & set_cc,
1366         resetting, clock);
1367 cond cond_check(E_ifun, cc, e_Cnd);
1368
1369 // Memory stage
1370 bmemory m(
1371     // Only update memory when everything is running normally
1372     // or when downloading
1373     (downloading | uploading) ? udaddr : mem_addr, // Read/Write address
1374     (running & mem_write) | downloading, // When to write to memory

```

```

1375     downloading ? idata : M_valA,           // Write data
1376     (running & mem_read) | uploading,      // When to read memory
1377     m_valM,                                 // Read data
1378     m_ok,
1379     f_pc, f_instr, f_ok, clock);           // Instruction memory access
1380
1381     assign imem_error = ~f_ok;
1382     assign dmem_error = ~m_ok;
1383
1384 // Write-back stage logic
1385
1386 // Control logic
1387 // -----
1388 // The following code is generated from the HCL description of the
1389 // pipeline control using the hcl2v program
1390 // -----
1391 assign f_pc =
1392     ((M_icode == IJXX) & ~M_Cnd) ? M_valA : (W_icode == IRET) ? W_valM :
1393     F_predPC);
1394
1395 assign f_icode =
1396     (imem_error ? INOP : imem_icode);
1397
1398 assign f_ifun =
1399     (imem_error ? FNONE : imem_ifun);
1400
1401 assign instr_valid =
1402     (f_icode == INOP | f_icode == IHALT | f_icode == IRRMOVQ | f_icode ==
1403     IIRMOVQ | f_icode == IRMMOVQ | f_icode == IMRMOVQ | f_icode == IOPQ
1404     | f_icode == IJXX | f_icode == ICALL | f_icode == IRET | f_icode ==
1405     IPUSHQ | f_icode == IPOPQ);
1406
1407 assign f_stat =
1408     (imem_error ? SADR : ~instr_valid ? SINS : (f_icode == IHALT) ? SHLT :
1409     SAOK);
1410
1411 assign need_regids =
1412     (f_icode == IRRMOVQ | f_icode == IOPQ | f_icode == IPUSHQ | f_icode ==
1413     IPOPQ | f_icode == IIRMOVQ | f_icode == IRMMOVQ | f_icode == IMRMOVQ)
1414     ;
1415
1416 assign need_valC =
1417     (f_icode == IIRMOVQ | f_icode == IRMMOVQ | f_icode == IMRMOVQ | f_icode
1418     == IJXX | f_icode == ICALL);
1419
1420 assign f_predPC =
1421     ((f_icode == IJXX | f_icode == ICALL) ? f_valC : f_valP);
1422
1423 assign d_srcA =
1424     ((D_icode == IRRMOVQ | D_icode == IRMMOVQ | D_icode == IOPQ | D_icode

```

```

1425         == IPUSHQ) ? D_rA : (D_icode == IPOPQ | D_icode == IRET) ? RRSP :
1426         RNONE);
1427
1428 assign d_srcB =
1429     ((D_icode == IOPQ | D_icode == IRMMOVQ | D_icode == IMRMOVQ) ? D_rB : (
1430         D_icode == IPUSHQ | D_icode == IPOPQ | D_icode == ICALL | D_icode
1431         == IRET) ? RRSP : RNONE);
1432
1433 assign d_dstE =
1434     ((D_icode == IRRMOVQ | D_icode == IIRMOVQ | D_icode == IOPQ) ? D_rB : (
1435         D_icode == IPUSHQ | D_icode == IPOPQ | D_icode == ICALL | D_icode
1436         == IRET) ? RRSP : RNONE);
1437
1438 assign d_dstM =
1439     ((D_icode == IMRMOVQ | D_icode == IPOPQ) ? D_rA : RNONE);
1440
1441 assign d_valA =
1442     ((D_icode == ICALL | D_icode == IJXX) ? D_valP : (d_srcA == e_dstE) ?
1443         e_vale : (d_srcA == M_dstM) ? m_valM : (d_srcA == M_dstE) ? M_vale :
1444         (d_srcA == W_dstM) ? W_valM : (d_srcA == W_dstE) ? W_vale : d_rvalA);
1445
1446 assign d_valB =
1447     ((d_srcB == e_dstE) ? e_vale : (d_srcB == M_dstM) ? m_valM : (d_srcB
1448         == M_dstE) ? M_vale : (d_srcB == W_dstM) ? W_valM : (d_srcB ==
1449         W_dstE) ? W_vale : d_rvalB);
1450
1451 assign aluA =
1452     ((E_icode == IRRMOVQ | E_icode == IOPQ) ? E_valA : (E_icode == IIRMOVQ
1453         | E_icode == IRMMOVQ | E_icode == IMRMOVQ) ? E_valC : (E_icode ==
1454         ICALL | E_icode == IPUSHQ) ? -8 : (E_icode == IRET | E_icode == IPOPQ
1455         ) ? 8 : 0);
1456
1457 assign aluB =
1458     ((E_icode == IRMMOVQ | E_icode == IMRMOVQ | E_icode == IOPQ | E_icode
1459         == ICALL | E_icode == IPUSHQ | E_icode == IRET | E_icode == IPOPQ)
1460         ? E_valB : (E_icode == IRRMOVQ | E_icode == IIRMOVQ) ? 0 : 0);
1461
1462 assign alufun =
1463     ((E_icode == IOPQ) ? E_ifun : ALUADD);
1464
1465 assign set_cc =
1466     (((E_icode == IOPQ) & ~(m_stat == SADR | m_stat == SINS | m_stat ==
1467         SHLT)) & ~(W_stat == SADR | W_stat == SINS | W_stat == SHLT));
1468
1469 assign e_valA =
1470     E_valA;
1471
1472 assign e_dstE =
1473     ((E_icode == IRRMOVQ) & ~e_Cnd) ? RNONE : E_dstE);
1474

```

```

1475 assign mem_addr =
1476     ((M_icode == IRMMOVQ | M_icode == IPUSHQ | M_icode == ICALL | M_icode
1477     == IMRMOVQ) ? M_valE : (M_icode == IPOPQ | M_icode == IRET) ?
1478     M_valA : 0);
1479
1480 assign mem_read =
1481     (M_icode == IMRMOVQ | M_icode == IPOPQ | M_icode == IRET);
1482
1483 assign mem_write =
1484     (M_icode == IRMMOVQ | M_icode == IPUSHQ | M_icode == ICALL);
1485
1486 assign m_stat =
1487     (dmem_error ? SADR : M_stat);
1488
1489 assign w_dstE =
1490     W_dstE;
1491
1492 assign w_valE =
1493     W_valE;
1494
1495 assign w_dstM =
1496     W_dstM;
1497
1498 assign w_valM =
1499     W_valM;
1500
1501 assign Stat =
1502     ((W_stat == SBUB) ? SAOK : W_stat);
1503
1504 assign F_bubble =
1505     0;
1506
1507 assign F_stall =
1508     (((E_icode == IMRMOVQ | E_icode == IPOPQ) & (E_dstM == d_srcA | E_dstM
1509     == d_srcB)) | (IRET == D_icode | IRET == E_icode | IRET ==
1510     M_icode));
1511
1512 assign D_stall =
1513     ((E_icode == IMRMOVQ | E_icode == IPOPQ) & (E_dstM == d_srcA | E_dstM
1514     == d_srcB));
1515
1516 assign D_bubble =
1517     (((E_icode == IJXX) & ~e_Cnd) | (~((E_icode == IMRMOVQ | E_icode ==
1518     IPOPQ) & (E_dstM == d_srcA | E_dstM == d_srcB)) & (IRET ==
1519     D_icode | IRET == E_icode | IRET == M_icode)));
1520
1521 assign E_stall =
1522     0;
1523
1524 assign E_bubble =

```



```
1525      ((E_icode == IJXX) & ~e_Cnd) | ((E_icode == IMRMOVQ | E_icode == IPOPOQ
1526          ) & (E_dstM == d_srcA | E_dstM == d_srcB));
1527
1528 assign M_stall =
1529     0;
1530
1531 assign M_bubble =
1532     ((m_stat == SADR | m_stat == SINS | m_stat == SHLT) | (W_stat == SADR
1533         | W_stat == SINS | W_stat == SHLT));
1534
1535 assign W_stall =
1536     (W_stat == SADR | W_stat == SINS | W_stat == SHLT);
1537
1538 assign W_bubble =
1539     0;
1540
1541 // -----
1542 // End of code generated by hcl2v
1543 // -----
1544 endmodule
1545
```

References

- [1] D. Thomas and P. Moorby. *The Verilog Hardware Description Language, Fifth Edition*. Springer, 2008.

Index

CS:APP3e , 1

conditional expression (Verilog), 5

continuous assignment (Verilog), 4

Design Compiler, 2

Goel, Prabhu, 1

memory bank, Y86-64 processor, 9

module, Verilog, 4

Moorby, Philip, 1

multiplexor, 5

non-blocking assignment, Verilog, 7

reg, Verilog state-holding signal, 7

Synopsys, Inc., 2

wire, Verilog combinational signal, 2, 7, 14