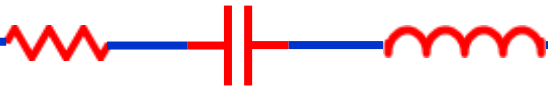


DC Circuits:


Circuit Theorems

Hasan Demirel



Circuit Theorems

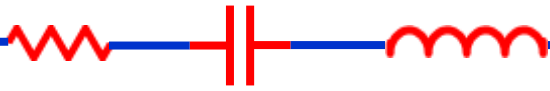- Introduction
- **Linearity Property**
- Superposition
- **Source Transformations**
- Thevenin's Theorem
- **Norton's Theorem**
- Maximum Power Transfer



Introduction

**A large
complex circuits**




**Simplify
circuit analysis**



Circuit Theorems

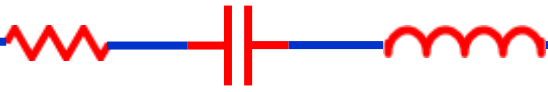- Thevenin's theorem
- Circuit linearity
- Source transformation
- Norton theorem
- Superposition
- Max. power transfer



Linearity Property

- **Homogeneity property (Scaling)**

$$i \rightarrow v = iR$$


$$ki \rightarrow kv = kiR$$

- **Additivity property**

$$i_1 \rightarrow v_1 = i_1R$$


$$i_2 \rightarrow v_2 = i_2R$$

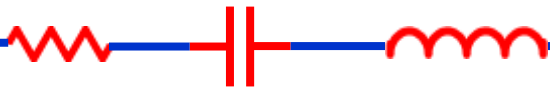
$$i_1 + i_2 \rightarrow (i_1 + i_2)R = i_1R + i_2R = v_1 + v_2$$



Linearity Property

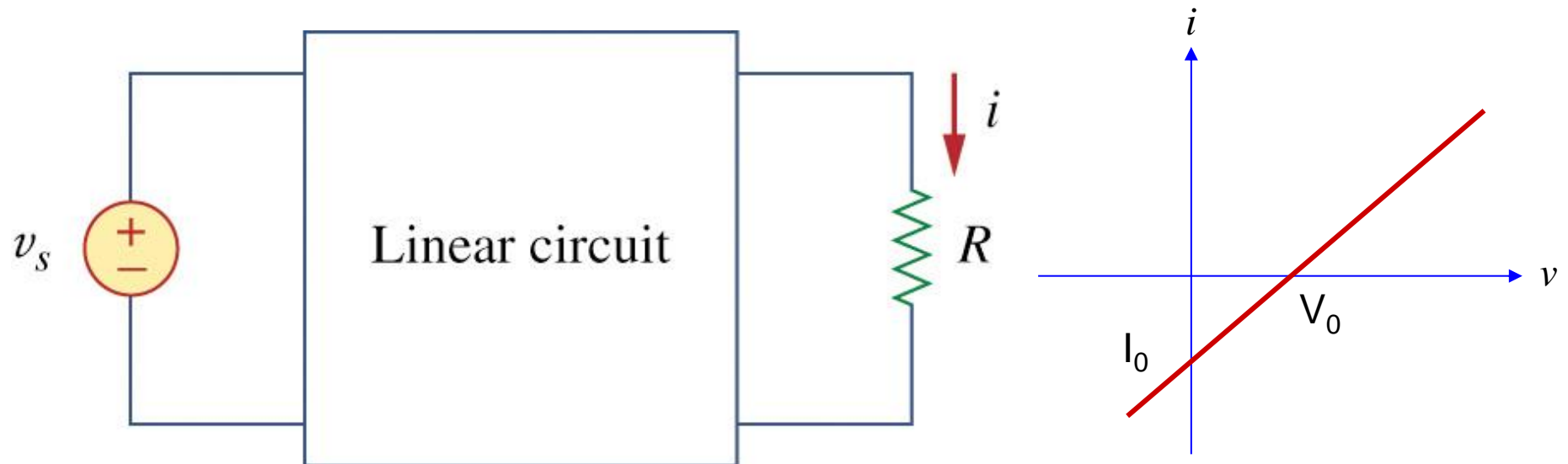- A **linear circuit** is one whose output is linearly related (directly proportional) to its input.



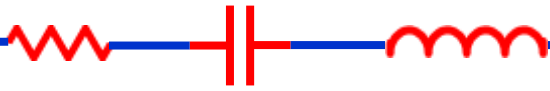

Linearity Property


- A **linear circuit** consist of :
 - linear elements (i.e. $R=5\ \Omega$)
 - linear dependent sources (i.e. $v_s=6I_o\ \text{V}$)
 - independent sources (i.e. $v_s=12\ \text{V}$)

$$v_s = 10\text{V} \rightarrow i = 2\text{A}$$

$$v_s = 1\text{V} \rightarrow i = 0.2\text{A}$$


$$v_s = 5\text{mV} \leftarrow i = 1\text{mA}$$

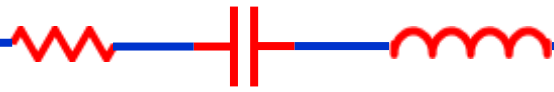
$$p = i^2 R = \frac{v^2}{R} : \textit{nonlinear}$$



Linearity Property

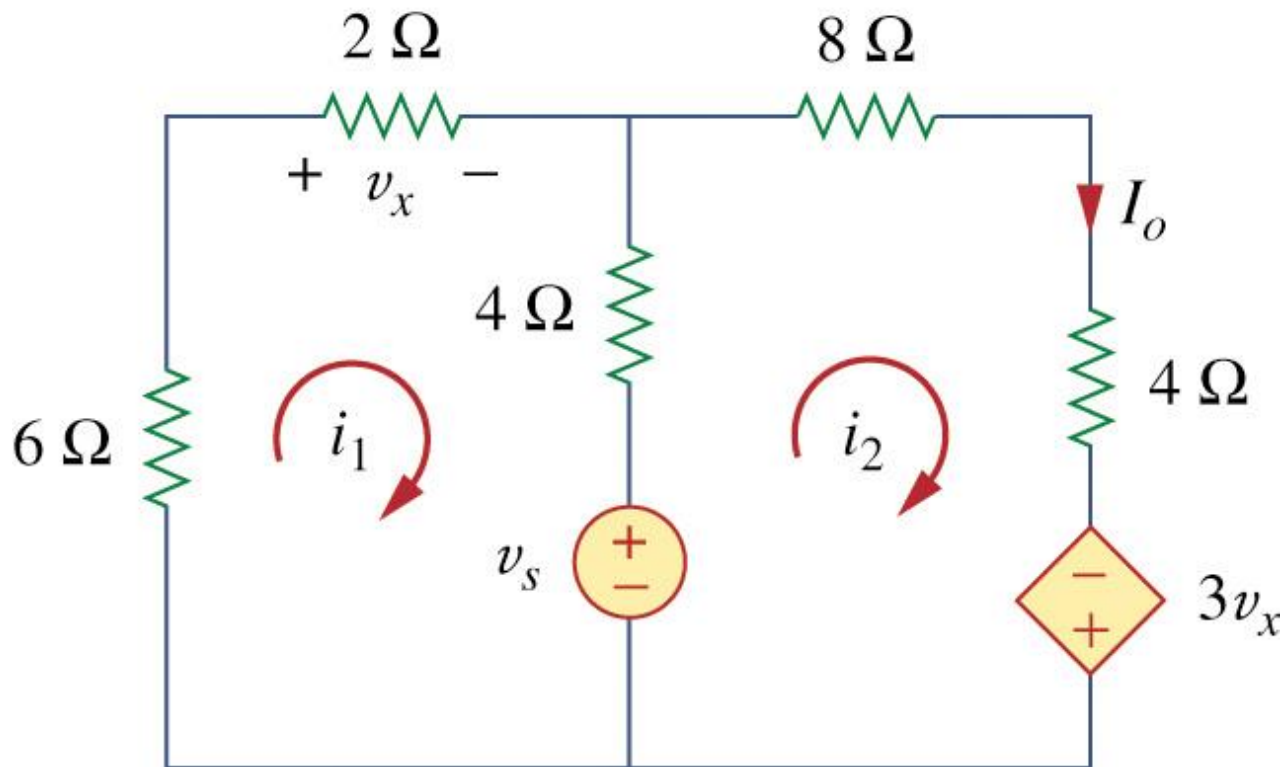Example 4.1: For the circuit in below find I_o when $v_s=12\text{V}$ and $v_s=24\text{V}$.



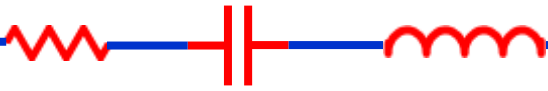

Linearity Property

Example 4.1: For the circuit in below find I_o when $v_s=12\text{V}$ and $v_s=24\text{V}$.

KVL

$$12i_1 - 4i_2 + v_s = 0 \quad (1)$$

$$-4i_1 + 16i_2 - 3v_x - v_s = 0 \quad (2)$$


$$v_x = 2i_1$$

Eq(2) becomes

$$-10i_1 + 16i_2 - v_s = 0 \quad (3)$$

Using **Eqs(1)** and **(3)** we get
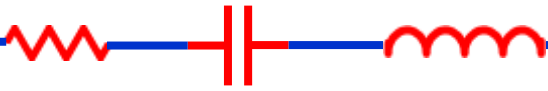
$$2i_1 + 12i_2 = 0 \rightarrow i_1 = -6i_2$$



Linearity Property

Example 4.1: For the circuit in below find I_o when $v_s=12\text{V}$ and $v_s=24\text{V}$.

From Eq(1) we get: $-76i_2 + v_s = 0 \Rightarrow i_2 = \frac{v_s}{76}$


when $v_s = 12\text{V}$

$$I_o = i_2 = \frac{12}{76} \text{A}$$

when $v_s = 24\text{V}$


$$I_o = i_2 = \frac{24}{76} \text{A}$$

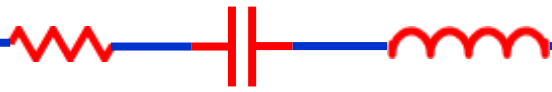
Showing that when the **source value is doubled, I_o doubles.**



Linearity Property

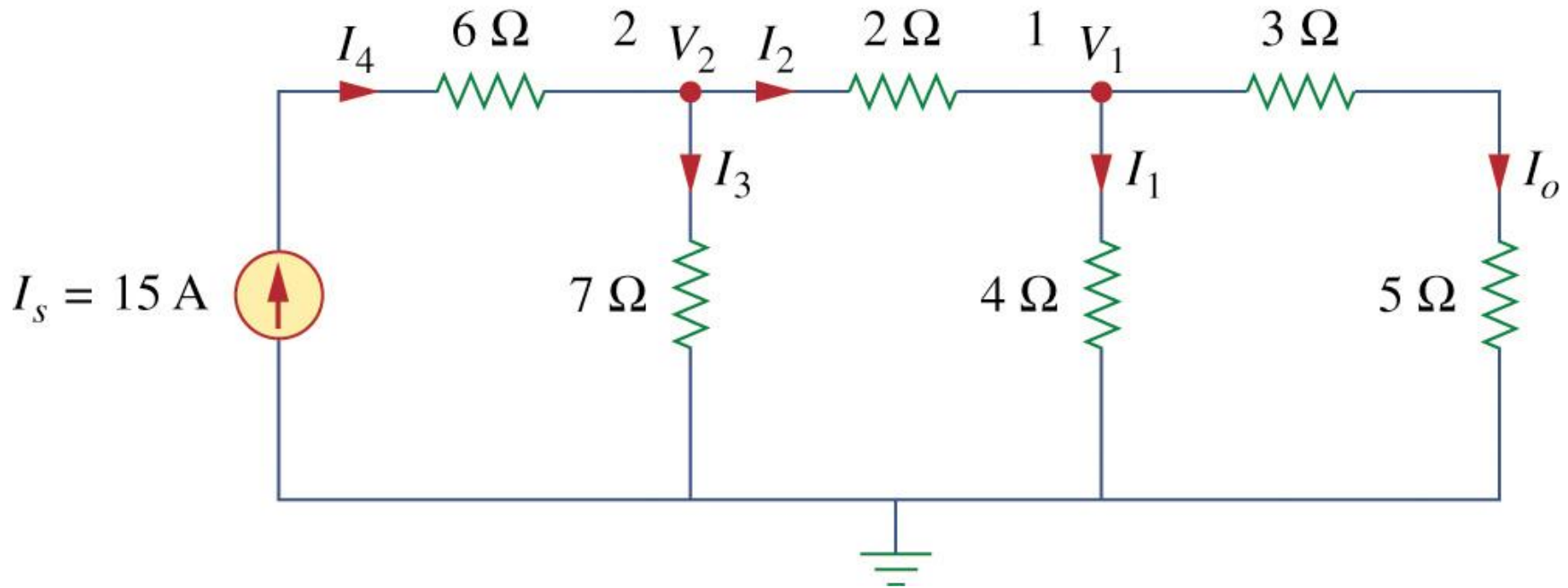Example 4.2: Assume $I_o = 1\text{ A}$ and use linearity to find the actual value of I_o in the following circuit.



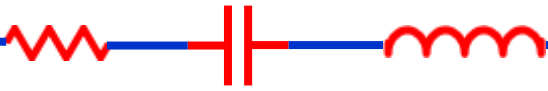

Linearity Property

Example 4.2: Assume $I_o = 1\text{A}$ and use linearity to find the actual value of I_o in the following circuit.

$$\text{If } I_o = 1\text{A, then } v_1 = (3 + 5)I_o = 8\text{V}$$


$$I_1 = v_1 / 4 = 2\text{A}, \quad I_2 = I_1 + I_o = 3\text{A}$$

$$V_2 = V_1 + 2I_2 = 8 + 6 = 14\text{V}, \quad I_3 = \frac{V_2}{7} = 2\text{A}$$

$$I_4 = I_3 + I_2 = 5\text{A} \Rightarrow I_s = 5\text{A}$$


$$I_o = 1\text{A} \rightarrow I_s = 5\text{A}$$
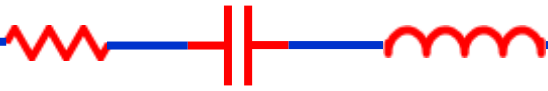
$$I_o = 3\text{A} \leftarrow I_s = 15\text{A}$$



Superposition


- The **superposition principle** states that the voltage across (or current through) an element in a linear circuit is the algebraic sum of the voltages across (or currents through) that element due to each **independent** source acting alone.
- **Turn off, kill, inactive source(s):**
 - independent voltage source: **0 V (short circuit)**
 - independent current source: **0 A (open circuit)**
- **Dependent sources are left intact.**

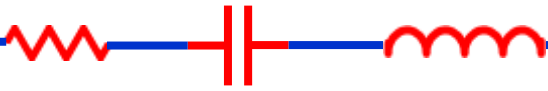

Superposition


- **Steps to apply superposition principle:**

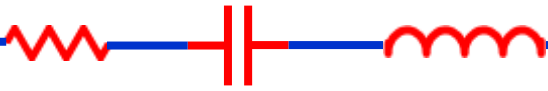1. **Turn off** all **independent sources** except **one source**. Find the output (voltage or current) due to that active source using nodal or mesh analysis.
2. **Repeat** step 1 for each of the other independent sources.
3. Find the total contribution by adding algebraically all the contributions due to the independent sources.




Superposition

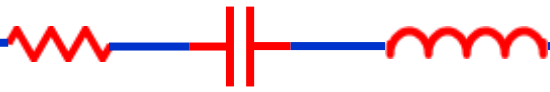
- **How to turn off independent sources:**
 - **Turn off voltage sources = short voltage sources; make it equal to zero voltage**
 - **Turn off current sources = open current sources; make it equal to zero current**
- **Superposition** involves **more work** but **simpler circuits**.
- **Superposition** is **not applicable** to the effect on **power**.



Superposition

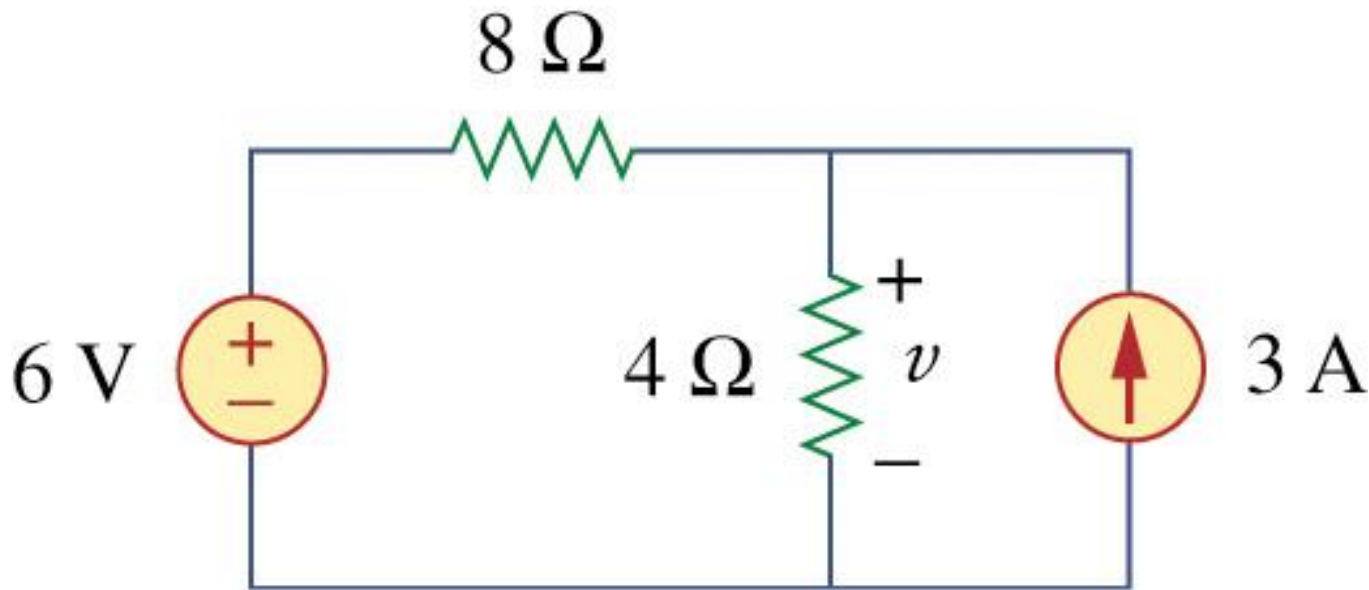- Example 4.3:** Use the superposition theorem to find v in the circuit below.



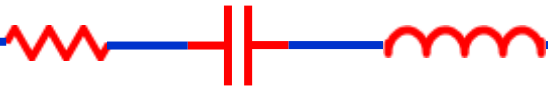

Superposition

- Example 4.3:** Use the superposition theorem to find v in the circuit below.

Since there are two sources,

Let $v = v_1 + v_2$

Voltage division to get



$$v_1 = \frac{4}{4+8}(6) = 2V$$


Current division, to get

$$i_3 = \frac{8}{4+8}(3) = 2A$$

Hence $v_2 = 4i_3 = 8V$

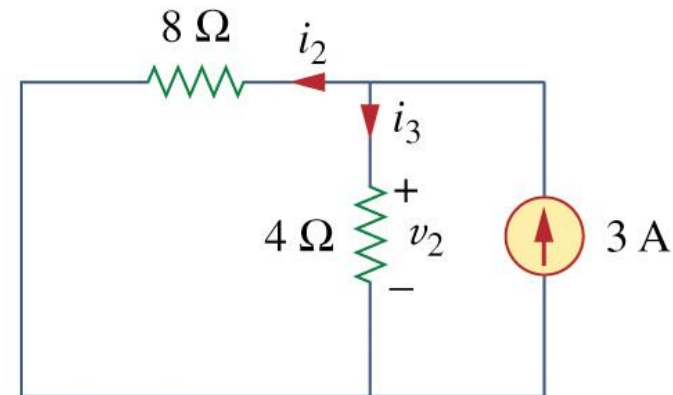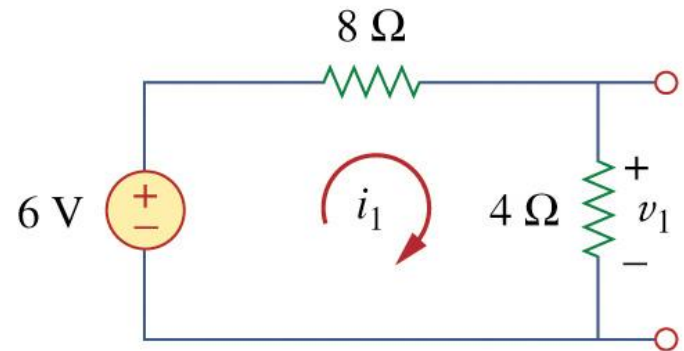
And we find $v = v_1 + v_2 = 2 + 8 = 10V$




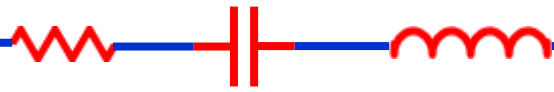

Superposition

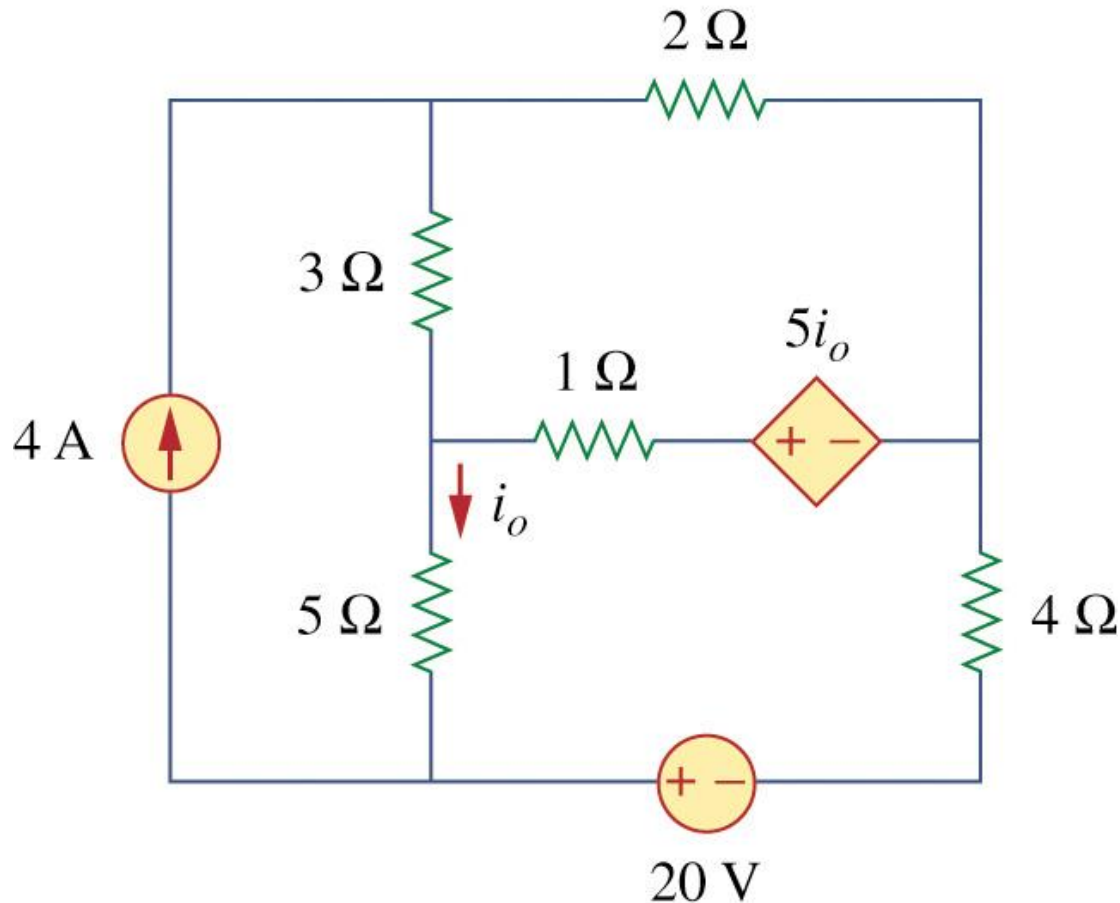- Example 4.4:** Find I_o in the circuit below using superposition.




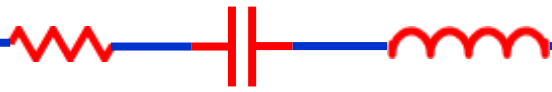


Superposition

- Example 4.4:** Find I_o in the circuit below using superposition.

Turn off 20V voltage source:

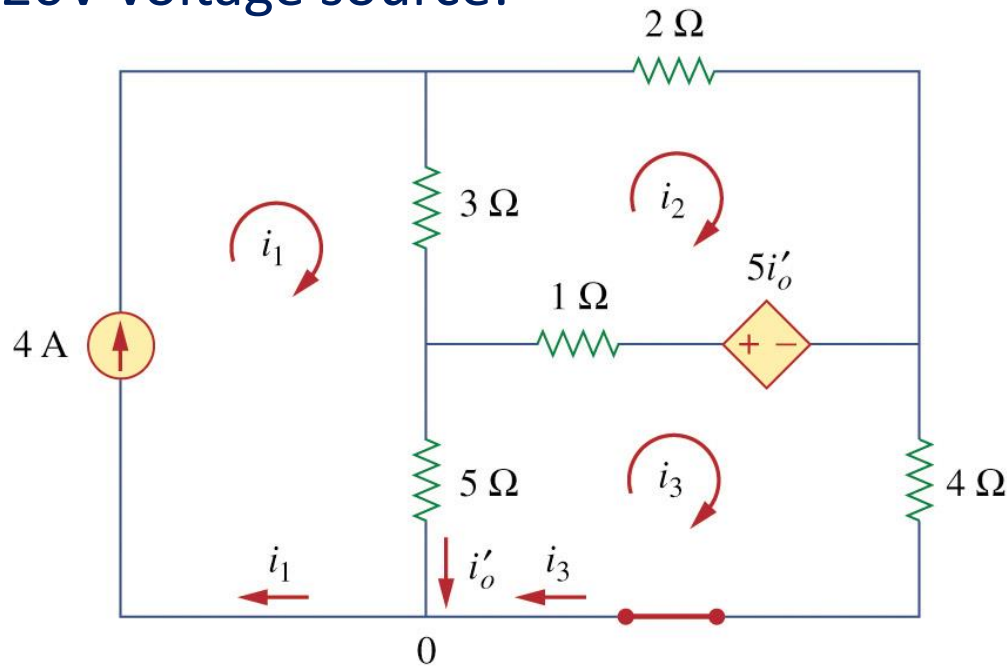


(a)

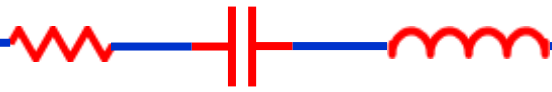


Superposition

- Example 4.4:** Find I_o in the circuit below using superposition.

Turn off 4A current source:

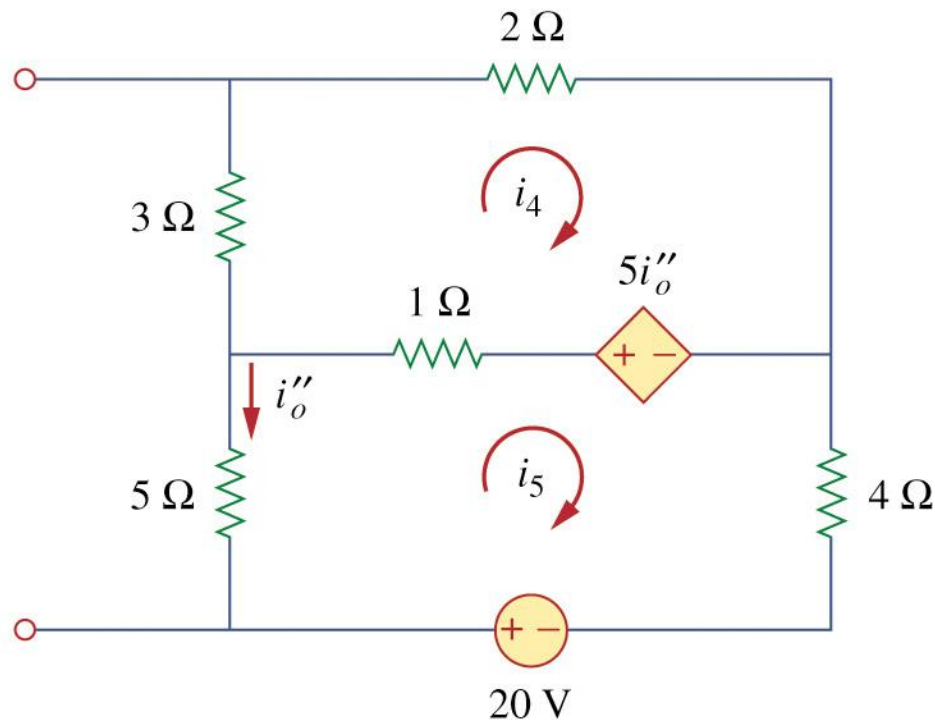


(b)

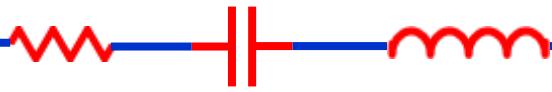

Source Transformation

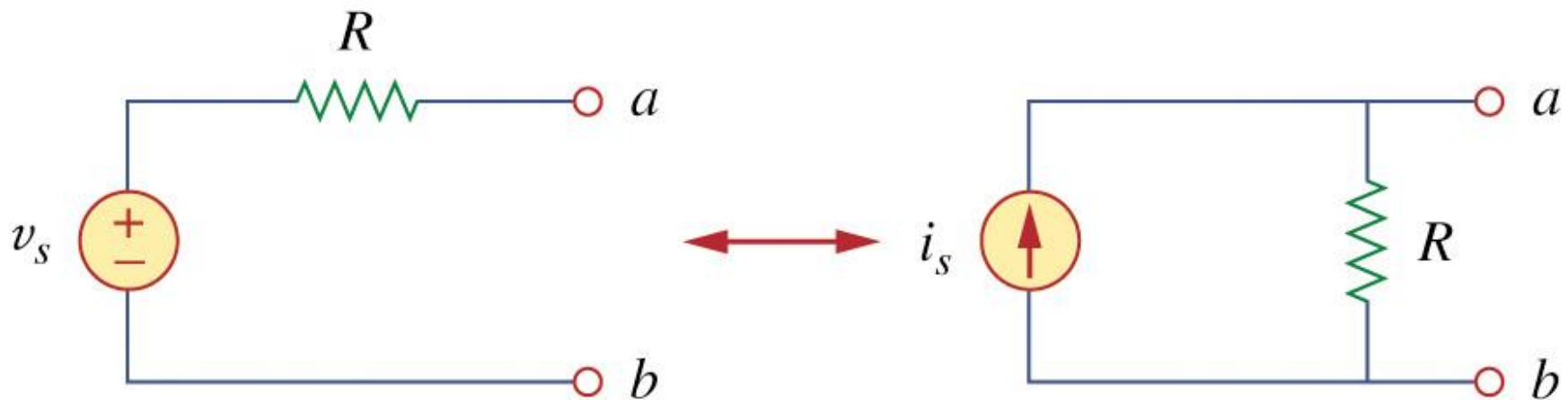- A **source transformation** is the process of replacing a **voltage source v_s in series with a resistor R** by a **current source i_s in parallel with a resistor R** , or vice versa






$$v_s = i_s R \quad \text{or} \quad i_s = \frac{v_s}{R}$$



Source Transformation


- Equivalent Circuits:

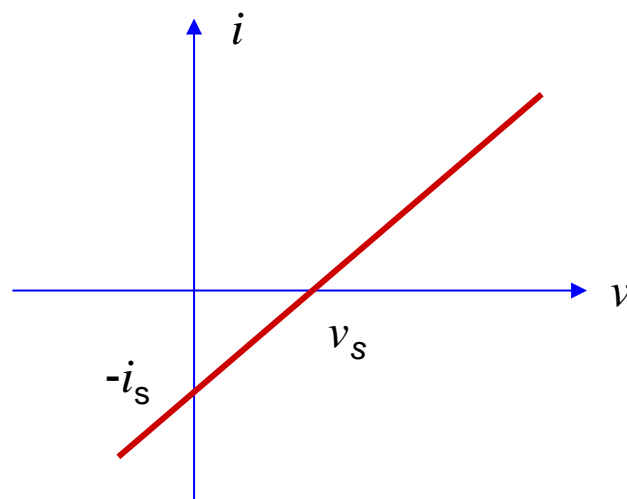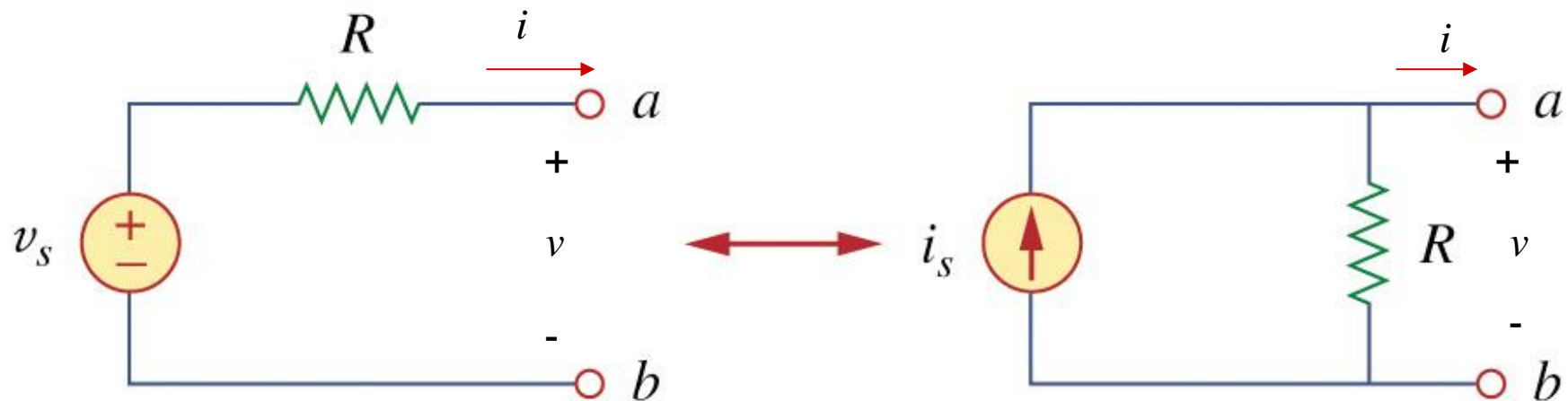

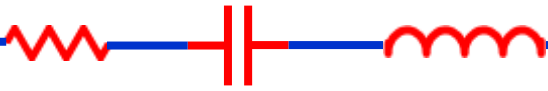


Source Transformation

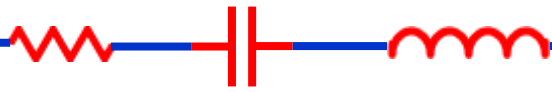
- **Source transformation:** Important points
 1. Arrow of the current source is directed toward the positive terminal of the voltage source.
 2. Transformation is not possible when:
 - ◆ ideal voltage source ($R = 0$)
 - ◆ ideal current source ($R = \infty$)



Source Transformation

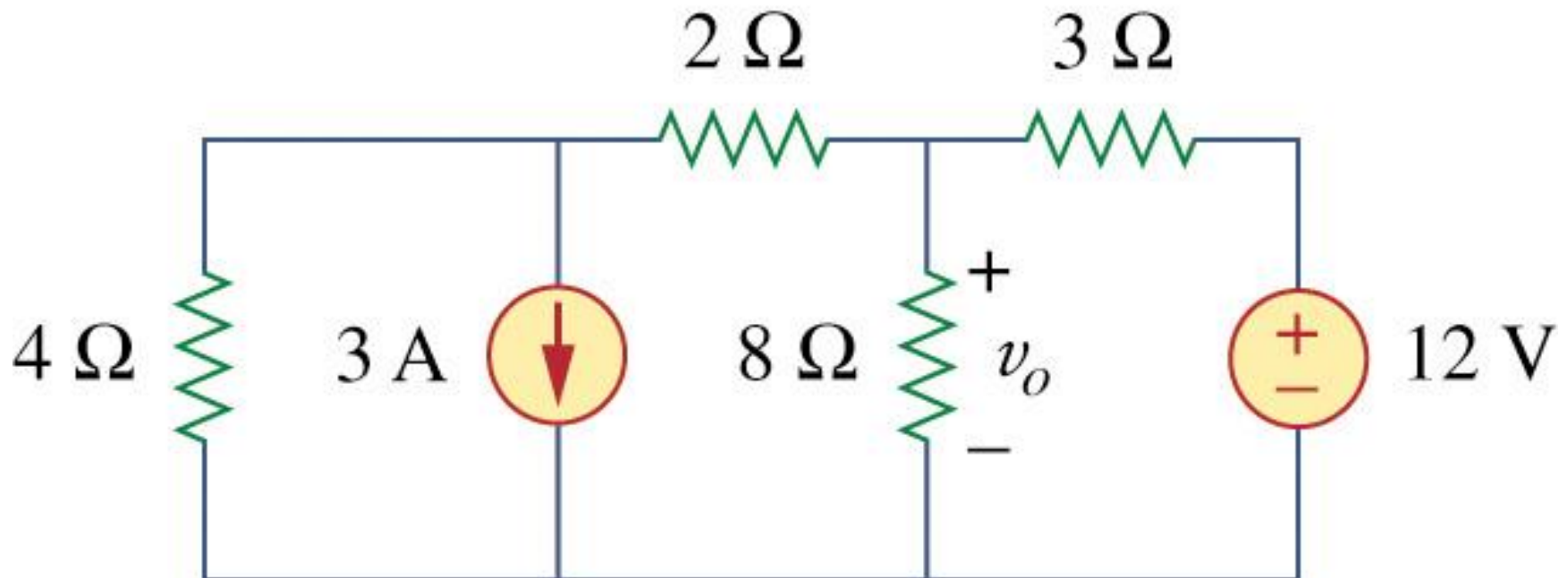
- Example 4.6:** Use source transformation to find v_o in the circuit below.



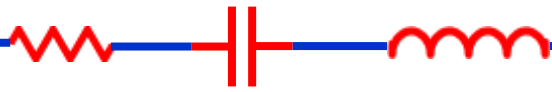


Source Transformation

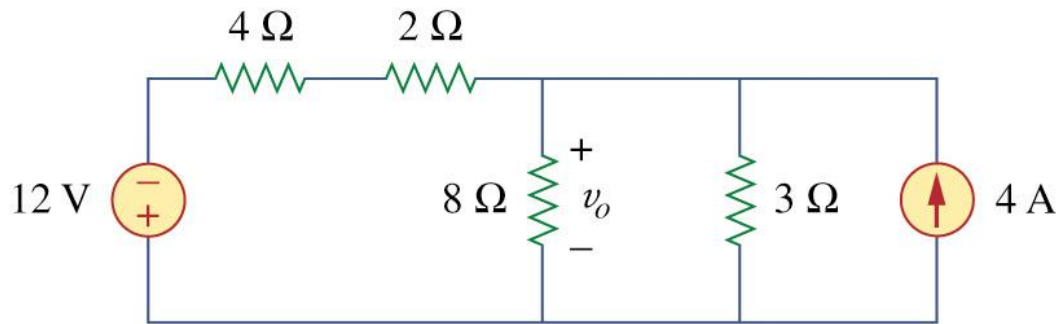
- Example 4.6:** Use source transformation to find v_o in the circuit below.



(a)

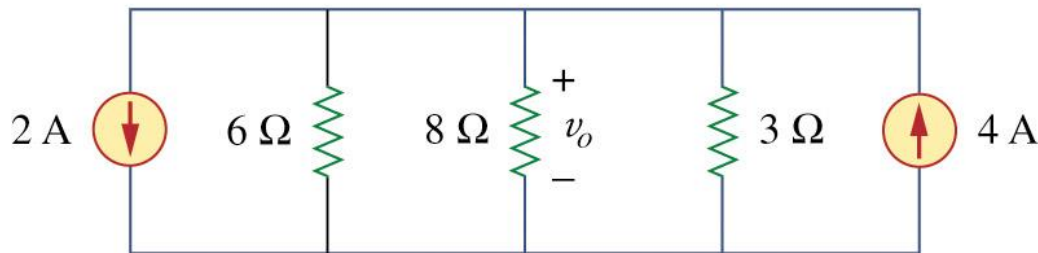


(b)

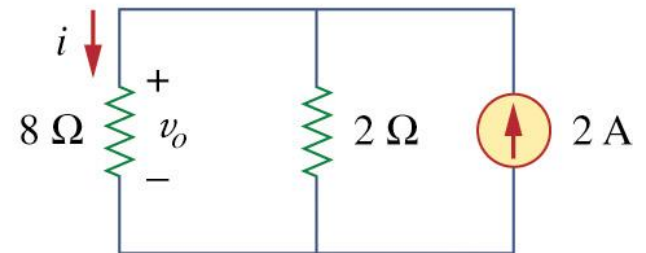

(c)

Fig.4.18

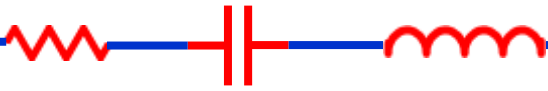

Source Transformation


- **Example 4.6:** Use source transformation to find v_o in the circuit below.

we use current division in Fig.4.18(c) to get

$$i = \frac{2}{2+8}(2) = 0.4\text{A}$$


and


$$v_o = 8i = 8(0.4) = 3.2\text{V}$$

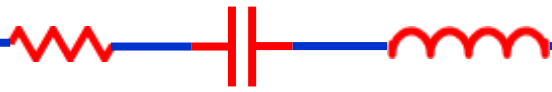

Source Transformation

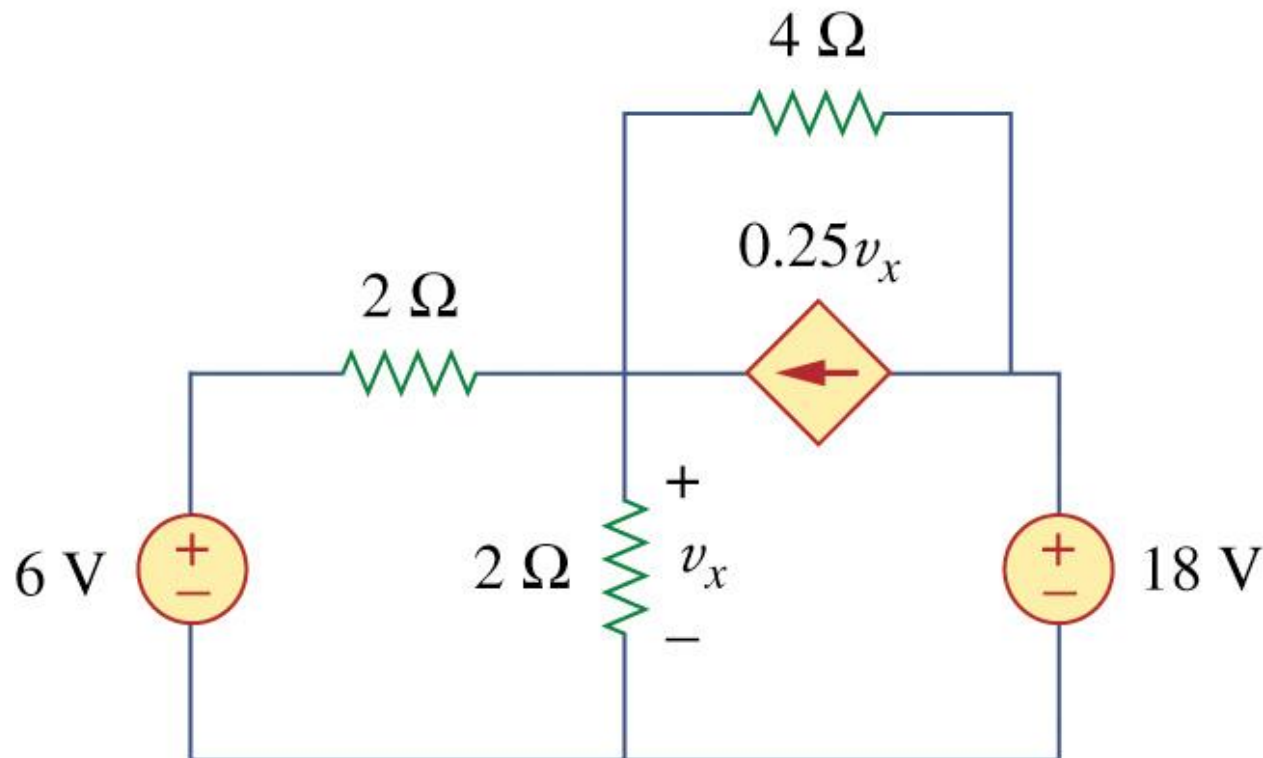
- Example 4.7:** Find v_x in the circuit below using source transformation.



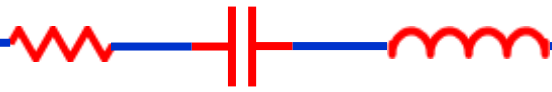


Source Transformation

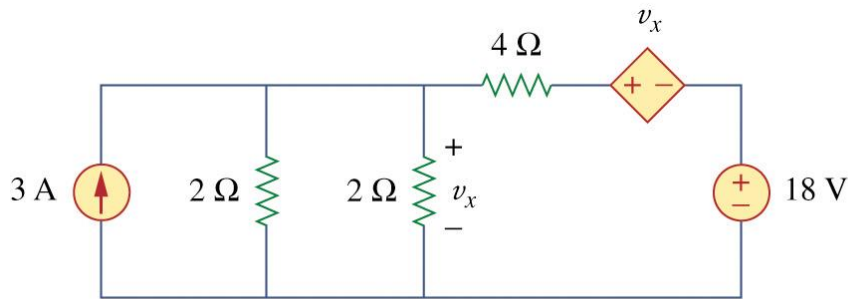- Example 4.7:** Find v_x in the circuit below using source transformation.



(a)

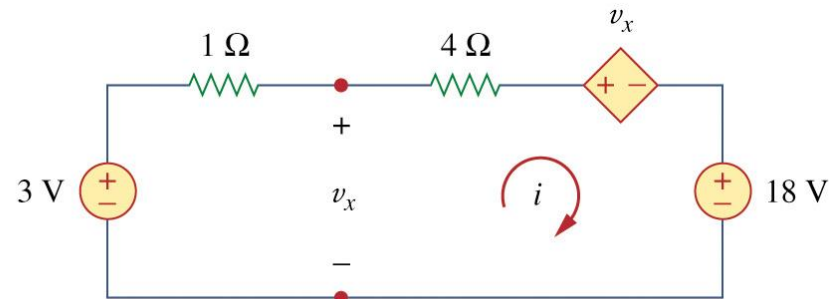


(b)

KVL around the loop in Fig (b)

$$-3 + 5i + v_x + 18 = 0 \quad (1)$$

Applying KVL to the loop containing only the 3V voltage source, the 1Ω resistor, and v_x yields:
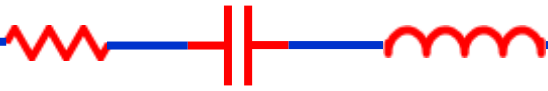
$$-3 + 1i + v_x = 0 \Rightarrow v_x = 3 - i \quad (2)$$



Source Transformation

- Example 4.7:** Find v_x in the circuit below using source transformation.

Substituting Eq.(2) into Eq.(1), we obtain


$$15 + 5i + 3 = 0 \Rightarrow i = -4.5A$$

Alternatively

$$-v_x + 4i + v_x + 18 = 0 \Rightarrow i = -4.5A$$


thus

$$v_x = 3 - i = 7.5V$$

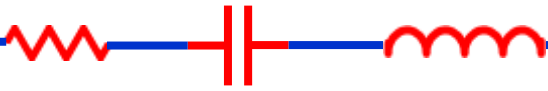



Thevenin's Theorem

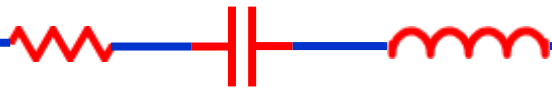
- **Thevenin's theorem** states that a linear two-terminal circuit can be replaced by an equivalent circuit consisting of a **voltage source V_{Th} in series with a resistor R_{Th}** where V_{Th} is the open circuit voltage at the terminals and R_{Th} is the input or equivalent resistance at the terminals when the **independent sources are turned off**.



Thevenin's Theorem


- Property of Linear Circuits

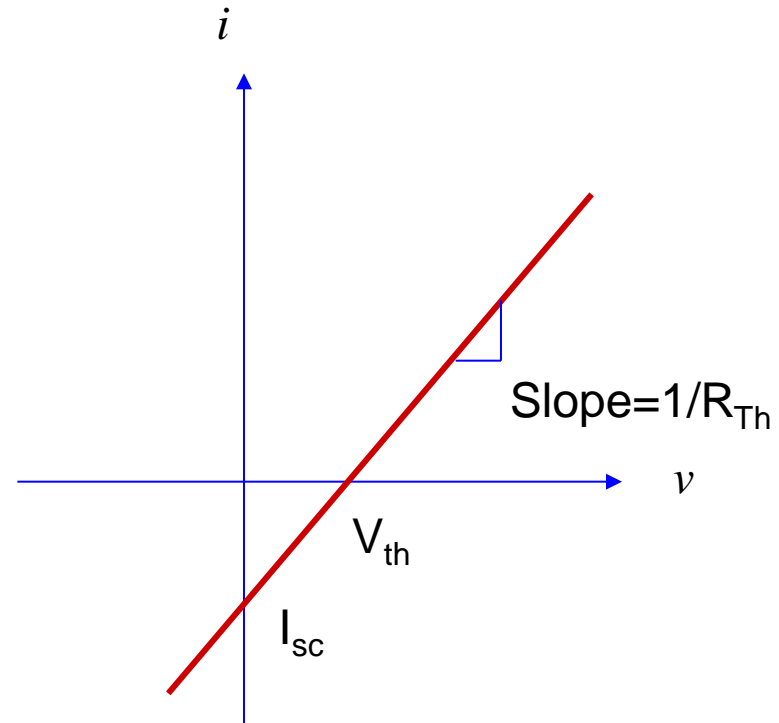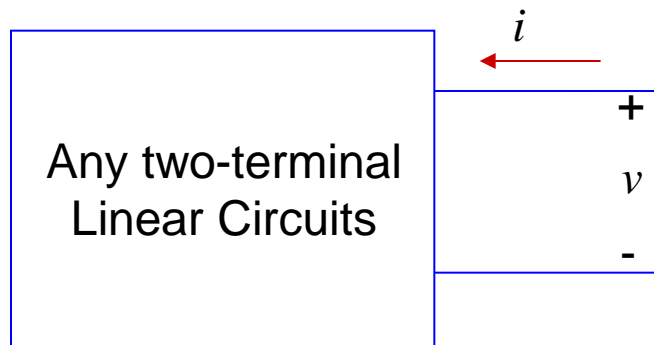

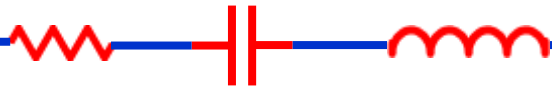


Thevenin's Theorem

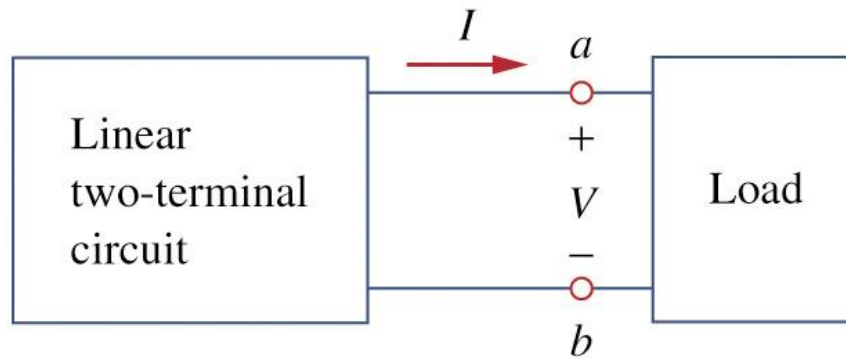
- Replacing a **linear two-terminal circuit (a)** by its **Thevenin equivalent circuit (b)**.



(a)

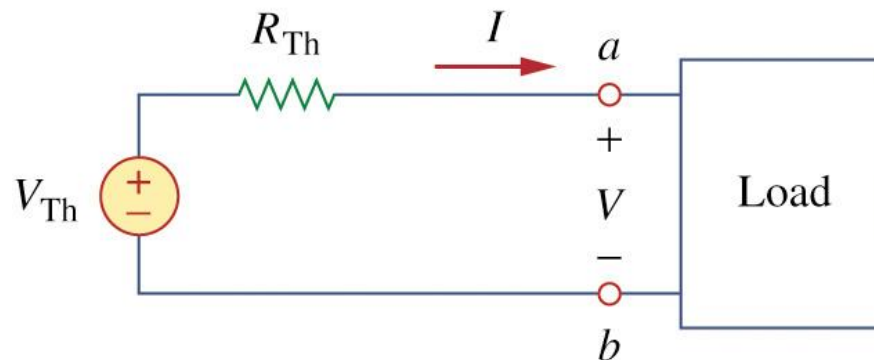


(b)

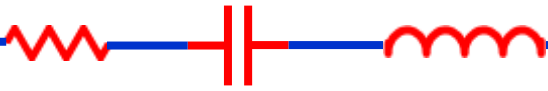


Thevenin's Theorem

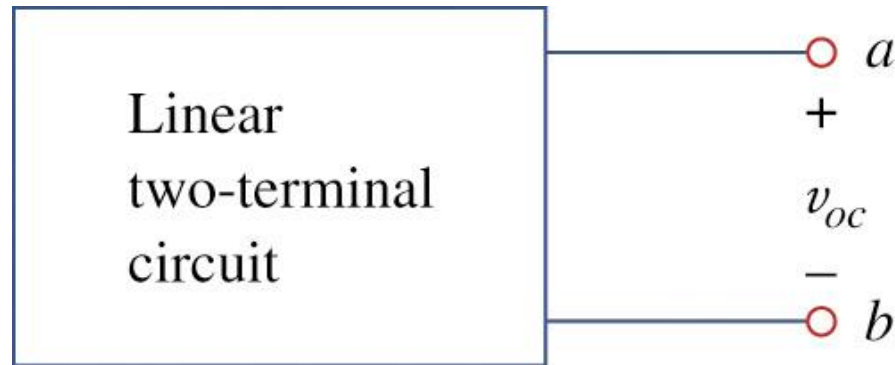- **How to find Thevenin Voltage?**
 - Equivalent circuit: same voltage-current relation at the terminals.
 - $V_{Th} = v_{oc}$: open circuit voltage at $a - b$



$$V_{Th} = v_{oc}$$

(a)

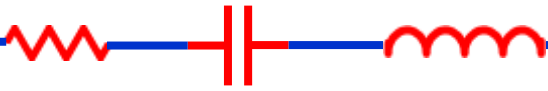


Thevenin's Theorem

• How to find Thevenin Resistance?


$R_{Th} = R_{in}$: input – resistance of the dead circuit at $a - b$.

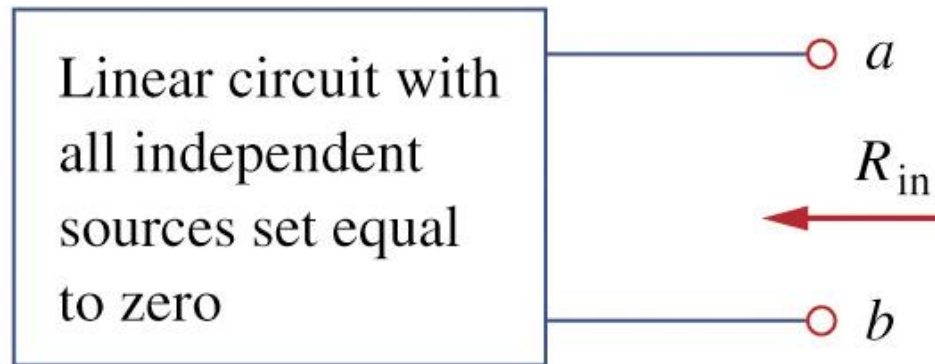- $a - b$ open circuited
- Turn off all independent sources



$$R_{Th} = R_{in}$$

(b)

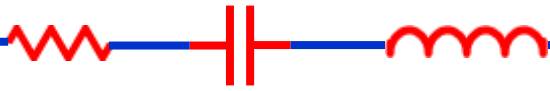


Thevenin's Theorem

- How to find Thevenin Resistance?
 - There are **two cases** in finding Thevenin Resistance R_{Th} .

CASE 1

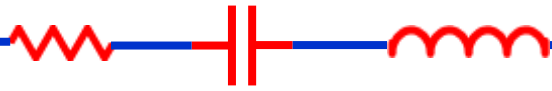- If the network has **no dependent sources**:
 - Turn off all independent sources.
 - R_{Th} : can be obtained via simplification of either parallel or series connection seen from a-b



Thevenin's Theorem

• How to find Thevenin Resistance?

- There are **two cases** in finding Thevenin Resistance R_{Th} .

CASE 2

- If the network has **dependent sources**:



- Turn off all independent sources.
- Apply a **voltage source** v_o at $a-b$


$$R_{Th} = \frac{v_o}{i_o}$$

- Alternatively, apply a **current source** i_o

at $a-b$


$$R_{Th} = \frac{v_o}{i_o}$$

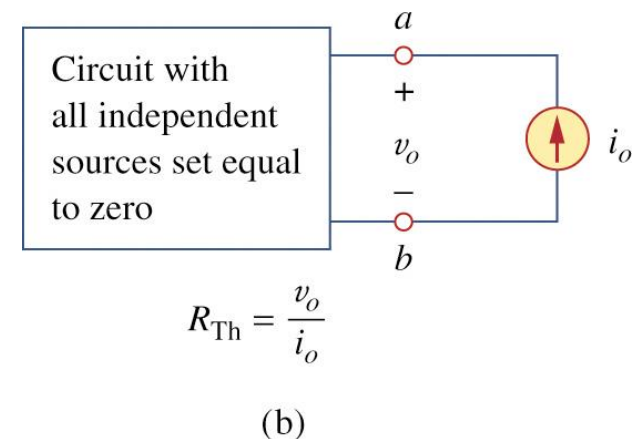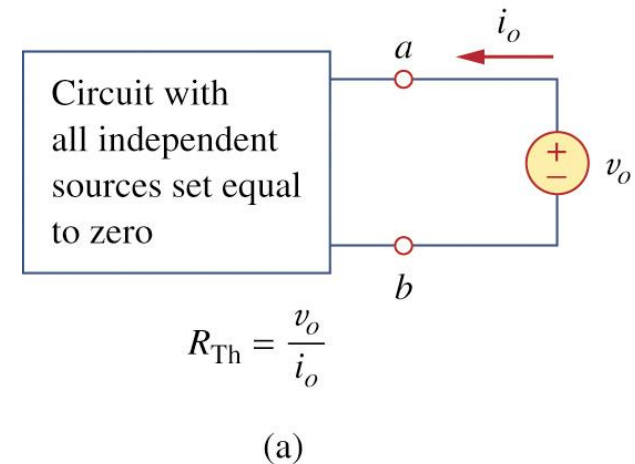

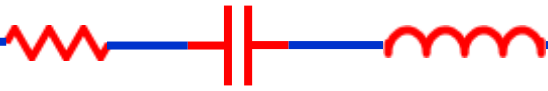

Thevenin's Theorem

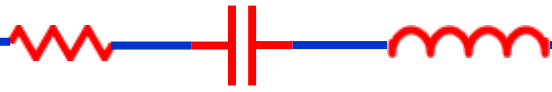- **How to find Thevenin Resistance?**
 - The Thevenin resistance, R_{Th} , may be negative, indicating that the circuit has ability providing (supplying) power.



Thevenin's Theorem


- After the **Thevenin Equivalent** is obtained, **the simplified circuit** can be used to calculate I_L and V_L easily.

Simplified circuit


$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

$$V_L = R_L I_L = \frac{R_L}{R_{Th} + R_L} V_{Th}$$


Voltage divider

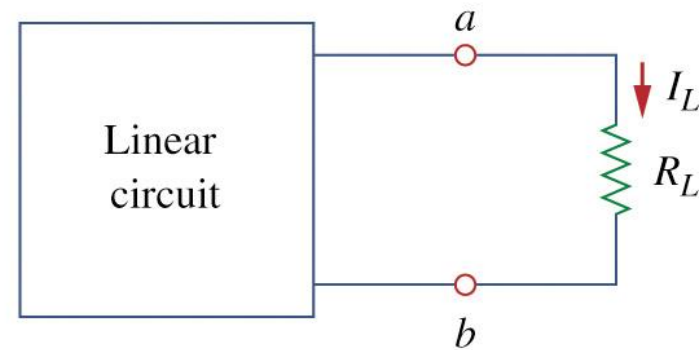

(a)

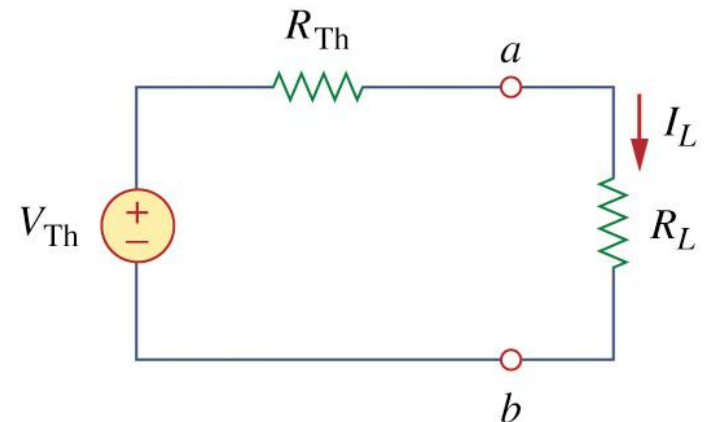



(b)

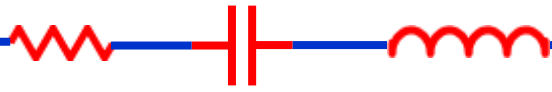

Thevenin's Theorem

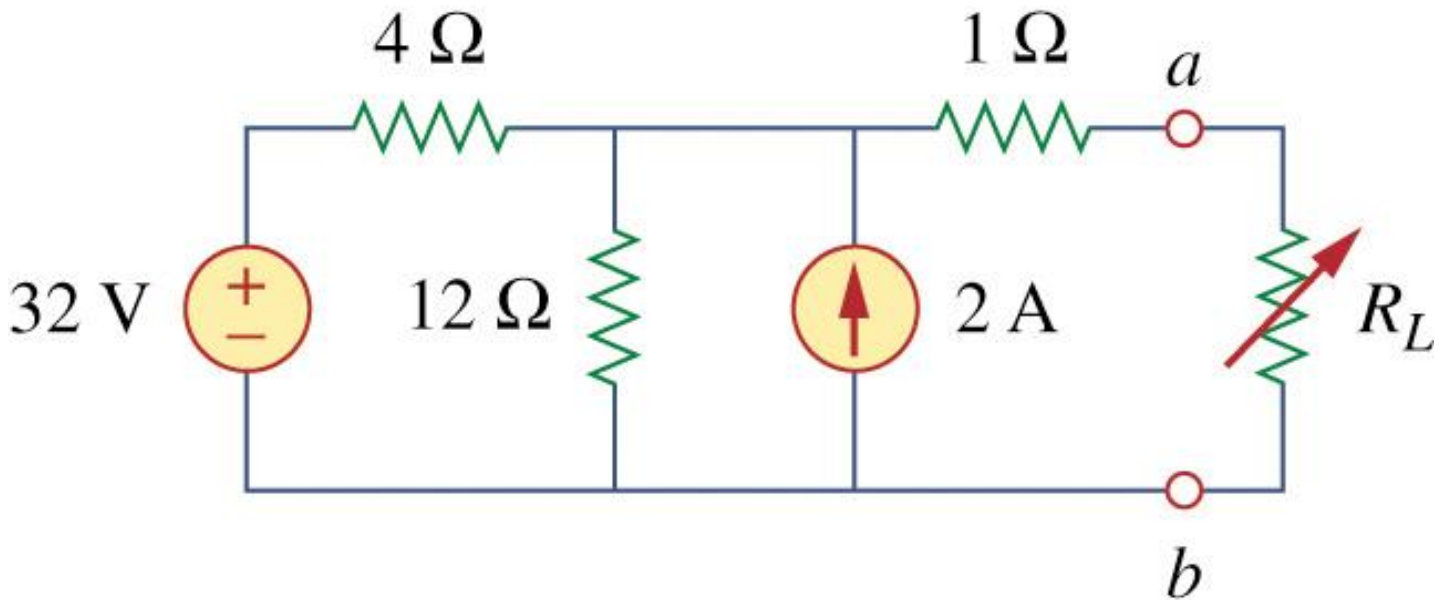- Example 4.8:** Find the Thevenin equivalent circuit of the circuit shown below, to the left of the terminals a - b . Then find the current through $R_L = 6, 16, \text{ and } 36 \Omega$.



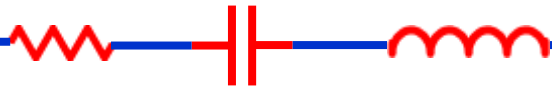



Thevenin's Theorem


- Example 4.8:** Find the Thevenin equivalent circuit of the circuit shown below, to the left of the terminals a - b . Then find the current through $R_L = 6, 16, \text{ and } 36 \Omega$.

Find R_{Th} :

R_{Th} : 32V voltage source \rightarrow short
 2A current source \rightarrow open
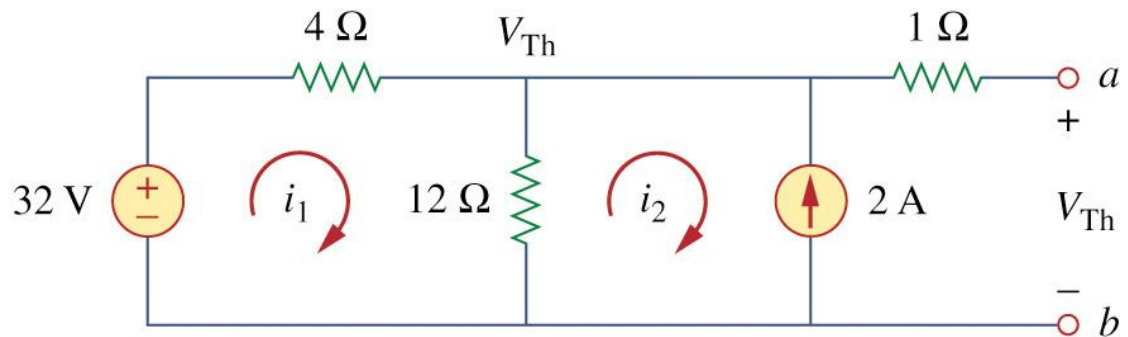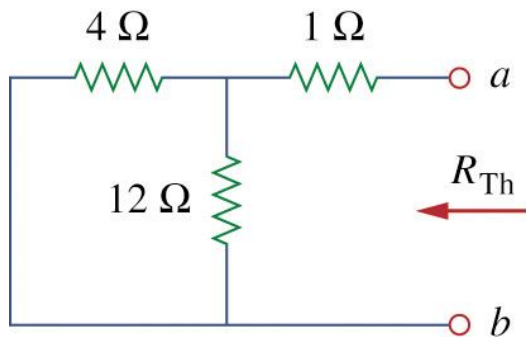
$$R_{Th} = 4 \parallel 12 + 1 = \frac{4 \times 12}{16} + 1 = 4 \Omega$$



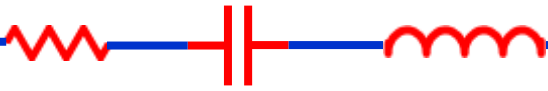

Thevenin's Theorem

- Example 4.8:** Find the Thevenin equivalent circuit of the circuit shown below, to the left of the terminals $a-b$. Then find the current through $R_L = 6, 16, \text{ and } 36 \Omega$.

Find V_{Th} : V_{Th} :

(1) Mesh analysis

$$-32 + 4i_1 + 12(i_1 - i_2) = 0, \quad i_2 = -2A$$


$$\therefore i_1 = 0.5A$$

$$V_{Th} = 12(i_1 - i_2) = 12(0.5 + 2.0) = 30V$$

(2) Alternatively, Nodal Analysis

$$(32 - V_{Th}) / 4 + 2 = V_{Th} / 12$$

$$\boxed{\therefore V_{Th} = 30V}$$

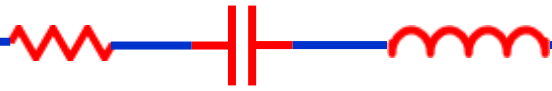

Thevenin's Theorem


- Example 4.8:** Find the Thevenin equivalent circuit of the circuit shown below, to the left of the terminals $a-b$. Then find the current through $R_L = 6, 16, \text{ and } 36 \Omega$.


Find V_{TH} : (3) Alternatively, source transform

$$\frac{32 - V_{TH}}{4} + 2 = \frac{V_{TH}}{12}$$

$$96 - 3V_{TH} + 24 = V_{TH} \Rightarrow V_{TH} = 30V$$

Thevenin Equivalent circuit:

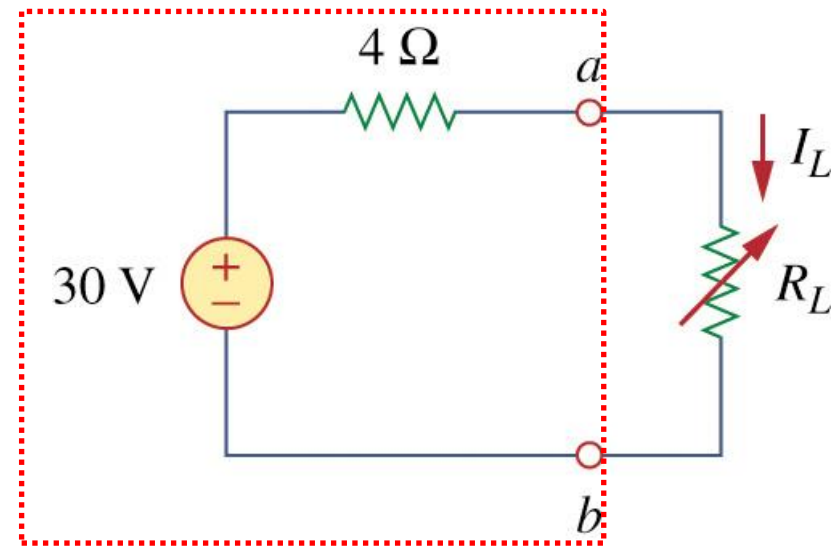

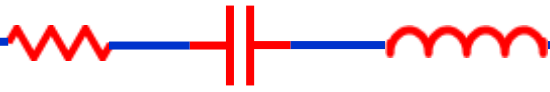

Thevenin's Theorem

- Example 4.8:** Find the Thevenin equivalent circuit of the circuit shown below, to the left of the terminals a - b . Then find the current through $R_L = 6, 16, \text{ and } 36 \Omega$.


Calculate I_L :


$$i_L = \frac{V_{Th}}{R_{Th} + R_L} = \frac{30}{4 + R_L}$$

$$R_L = 6 \rightarrow I_L = 30/10 = 3A$$

$$R_L = 16 \rightarrow I_L = 30/20 = 1.5A$$

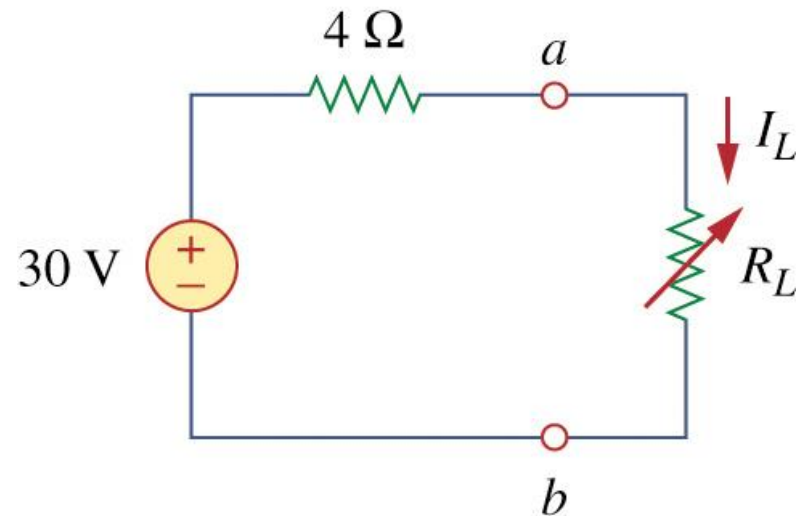
$$R_L = 36 \rightarrow I_L = 30/40 = 0.75A$$




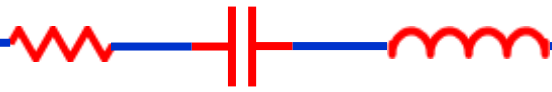

Thevenin's Theorem

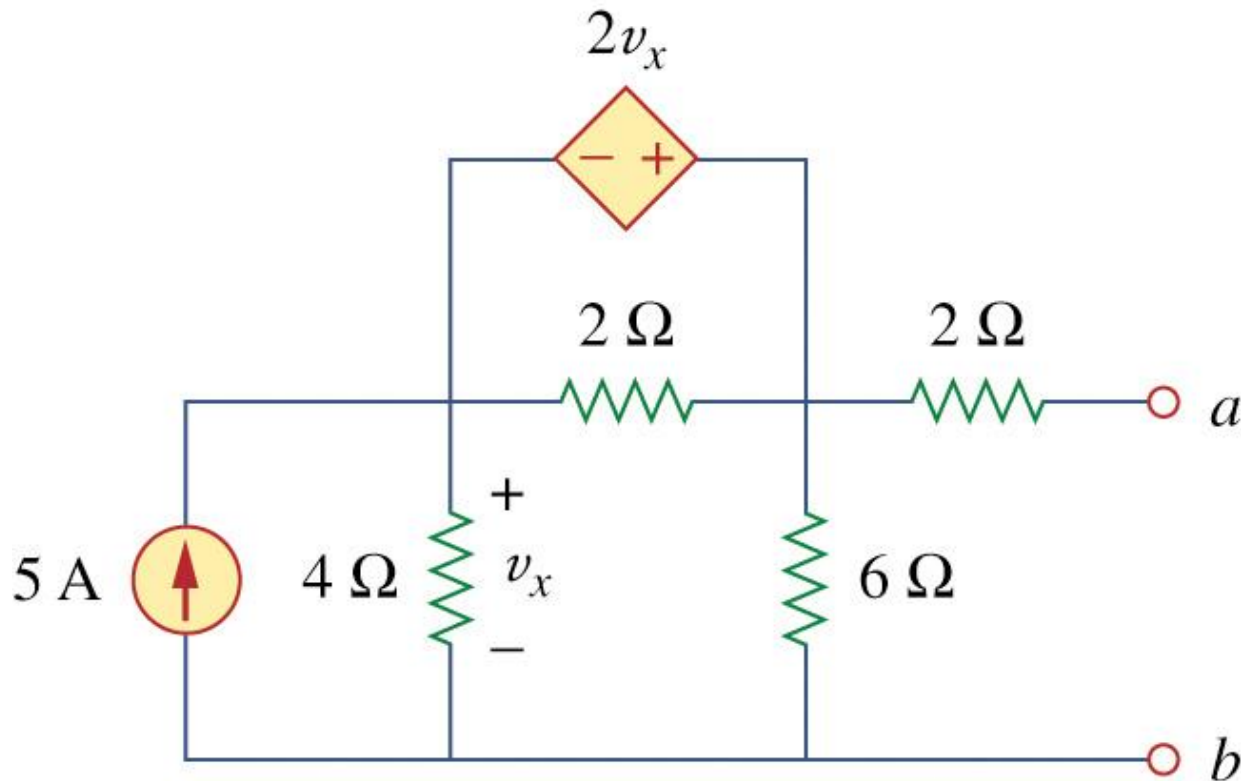- Example 4.9:** Find the Thevenin equivalent of the circuit below at terminals a - b .



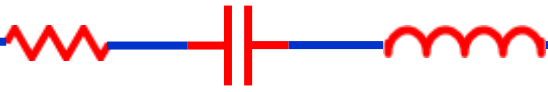


Thevenin's Theorem

- **Example 4.9:** Find the Thevenin equivalent of the circuit below at terminals a - b .
- **(independent + dependent sources case)**


Find R_{Th} : Use Fig (a):

independent source $\rightarrow 0$
 dependent source \rightarrow intact
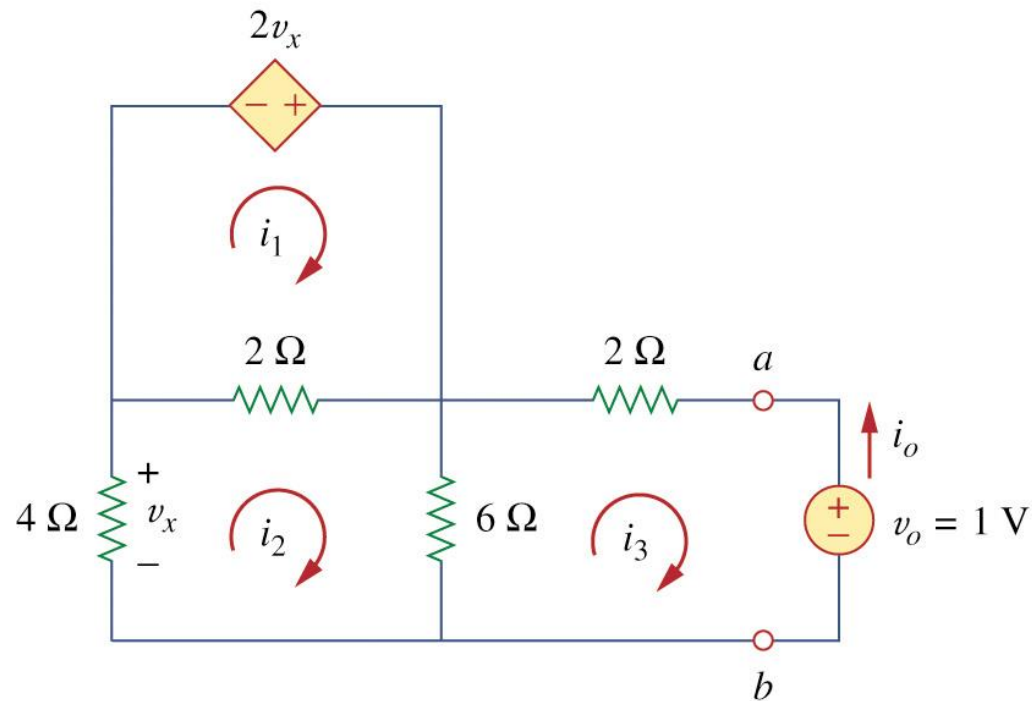
$$v_o = 1V, \quad R_{Th} = \frac{v_o}{i_o} = \frac{1}{i_o}$$



(a)

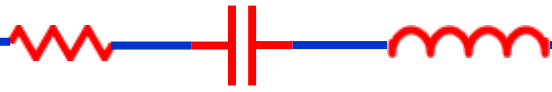

Thevenin's Theorem


- Example 4.9:** Find the Thevenin equivalent of the circuit below at terminals a - b .

Find R_{Th} : For Loop 1:


$$-2v_x + 2(i_1 - i_2) = 0 \quad \text{or} \quad v_x = i_1 - i_2$$

$$\text{But } v_x = -4i_2 = i_1 - i_2$$

$$\therefore i_1 = -3i_2$$

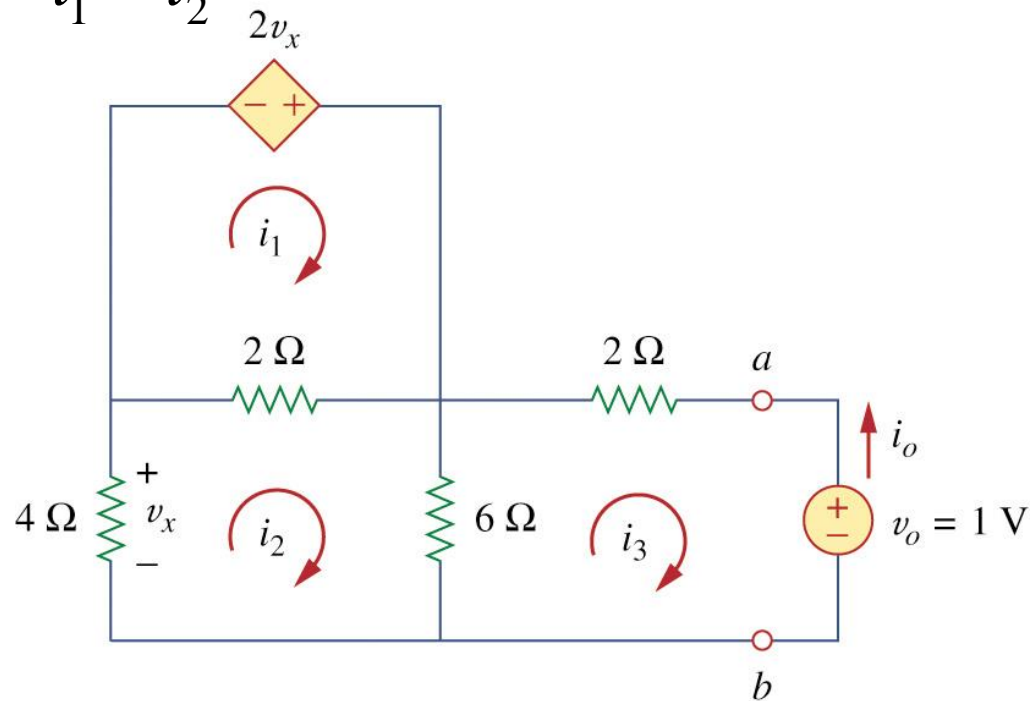

(a)

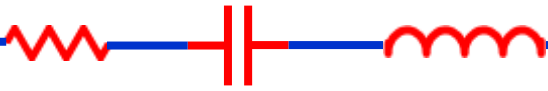

Thevenin's Theorem

- Example 4.9:** Find the Thevenin equivalent of the circuit below at terminals a - b .

Find R_{Th} : For Loops 2 and 3:

$$4i_2 + 2(i_2 - i_1) + 6(i_2 - i_3) = 0$$


$$6(i_3 - i_2) + 2i_3 + 1 = 0$$

Solving these equations gives

$$i_3 = -1/6 \text{ A.}$$

$$\text{But } i_o = -i_3 = \frac{1}{6} \text{ A}$$
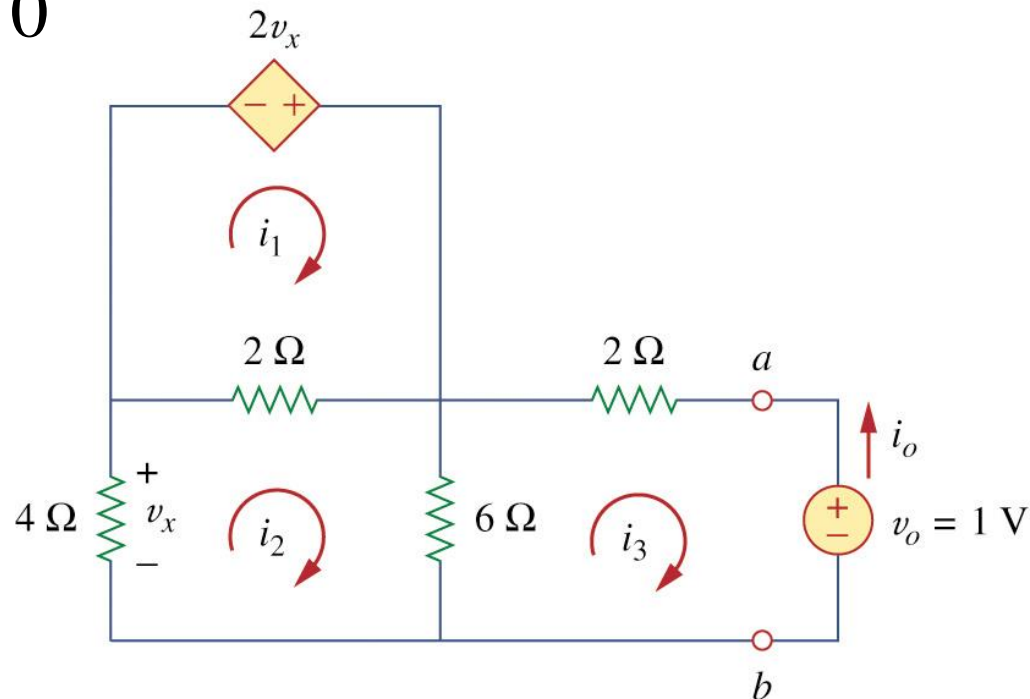
$$\therefore R_{Th} = \frac{1V}{i_o} = 6\Omega$$



Thevenin's Theorem

- Example 4.9:** Find the Thevenin equivalent of the circuit below at terminals a - b .

Find V_{Th} : Use Fig (b) : Mesh analysis

Loop 1: $i_1 = 5 \text{ A}$

Loop 2: $4(i_2 - i_1) + 2(i_2 - i_3) + 6i_2 = 0$


$$12i_2 - 2i_3 = 20$$

Loop 3: $-2v_x + 2(i_3 - i_2) = 0$

$$-2(4(i_1 - i_2)) + 2(i_3 - i_2) = 0$$


$$6i_2 + 2i_3 = 40$$

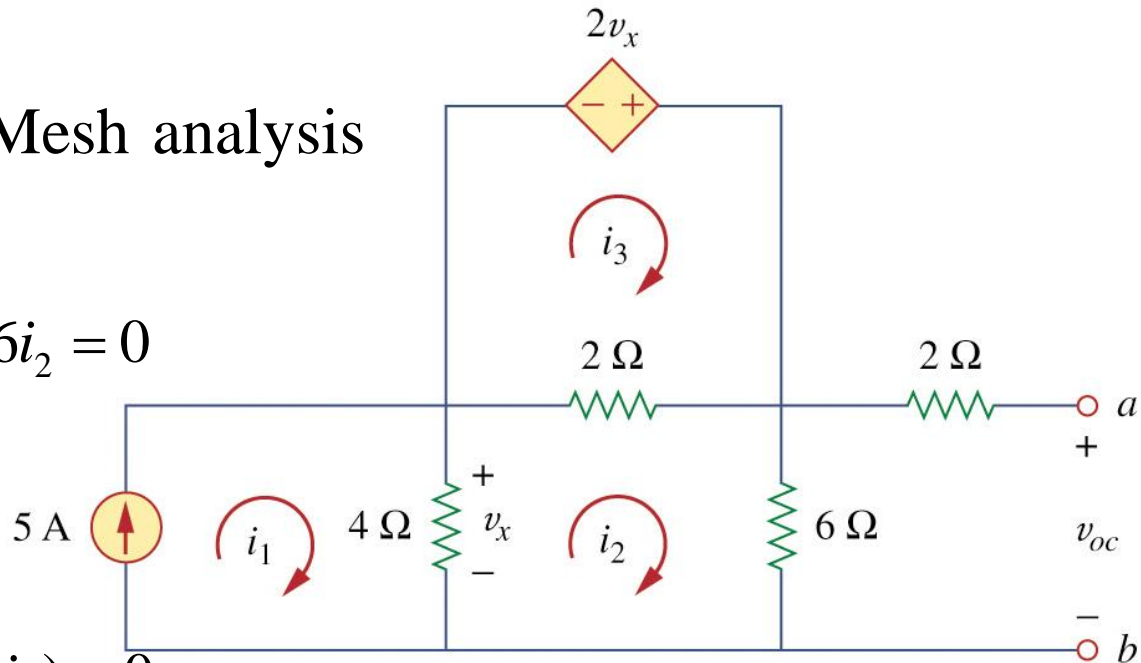
$$V_{Th} = v_{oc} = 6i_2 = 20 \text{ V}$$



$$\therefore i_2 = 60/18$$

Thevenin Equivalent circuit:

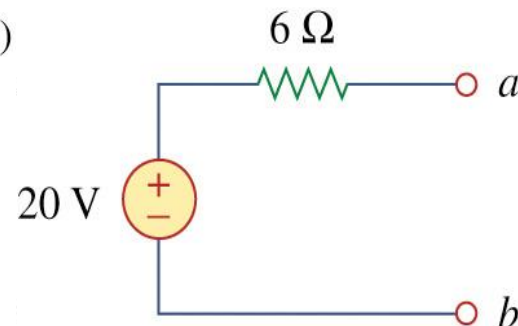

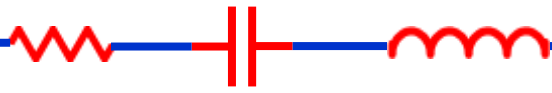

Thevenin's Theorem

- Example 4.10:** Determine the Thevenin equivalent circuit in Fig (a).

Find V_{Th} : $V_{Th} = 0$

Find R_{Th} : Use Fig (b):


(dependent source only case)

Apply a **current source** i_o at $a-b$


$$R_{Th} = \frac{v_o}{i_o}$$

Nodal analysis :


$$i_o + i_x = 2i_x + v_o / 4$$

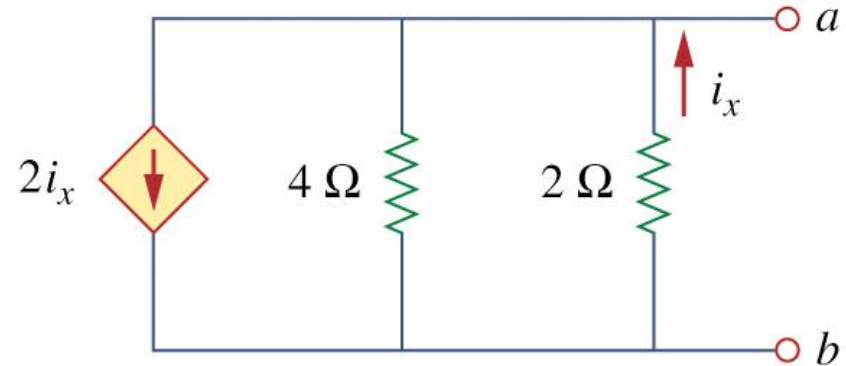

(a)

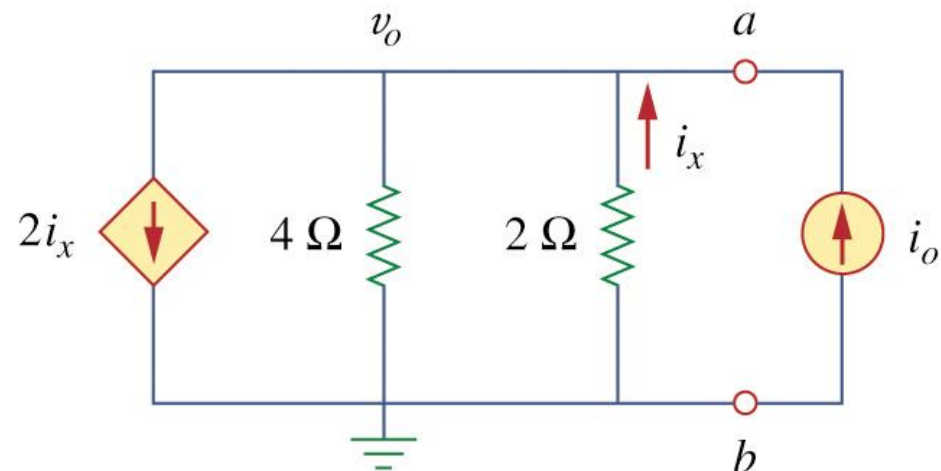

(b)

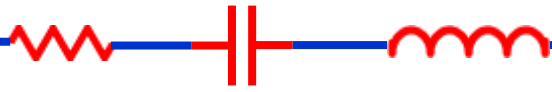

Thevenin's Theorem


- Example 4.10:** Determine the Thevenin equivalent circuit in Fig (a).


Find R_{Th} : Use Fig (b):

But
$$i_x = \frac{0 - v_o}{2} = -\frac{v_o}{2}$$

$$i_o = i_x + \frac{v_o}{4} = -\frac{v_o}{2} + \frac{v_o}{4} = -\frac{v_o}{4} \quad \text{or } v_o = -4i_o$$
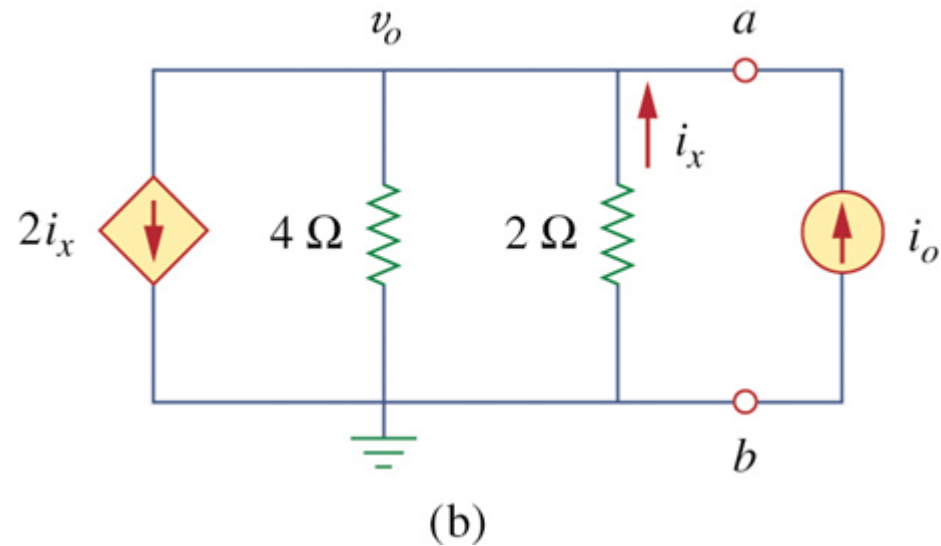
$$\text{Thus } R_{Th} = \frac{v_o}{i_o} = -4\Omega \quad (\text{Supplying power})$$




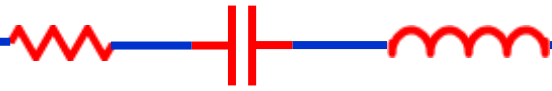


Thevenin's Theorem

- Example 4.10:** Determine the Thevenin equivalent circuit in Fig (a).


Input circuit:

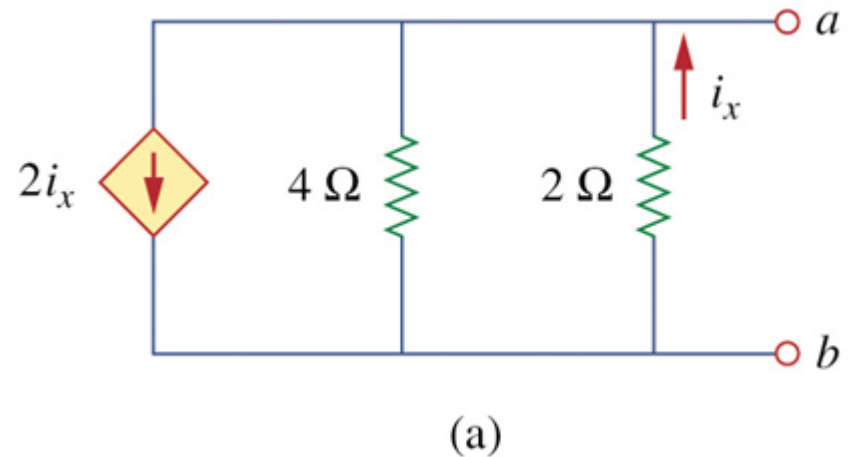

Thevenin Equivalent circuit:

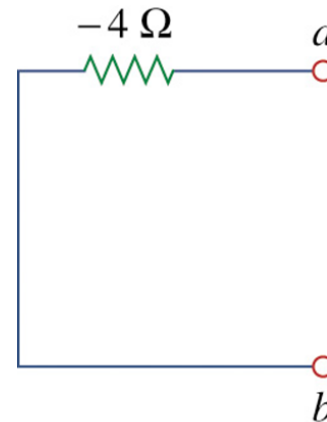


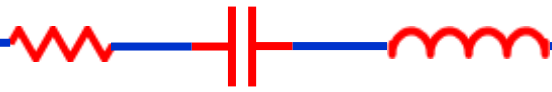- When R_{Th} is negative, you must evaluate (check) if the two circuits are equivalent or not!




Thevenin's Theorem

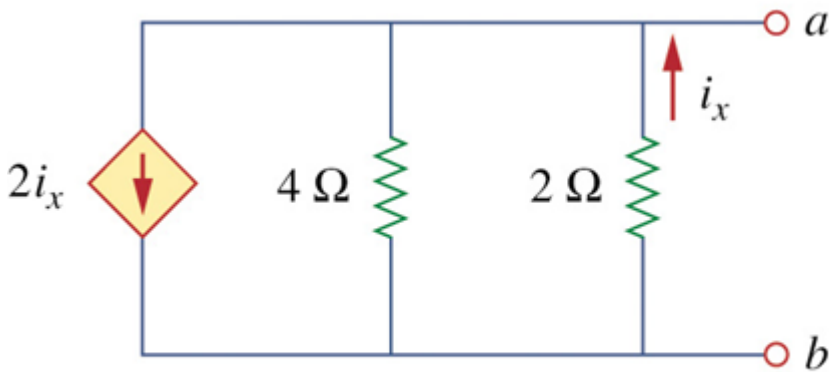
- Example 4.10:** Determine the Thevenin equivalent circuit in Fig (a).




Input circuit: (a)

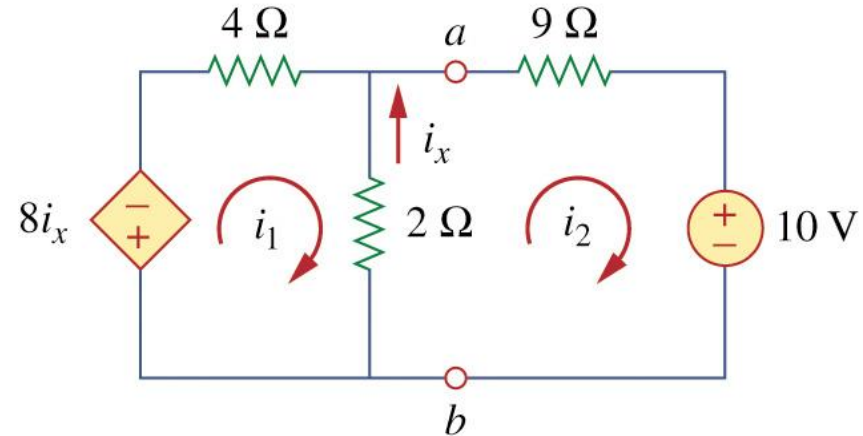

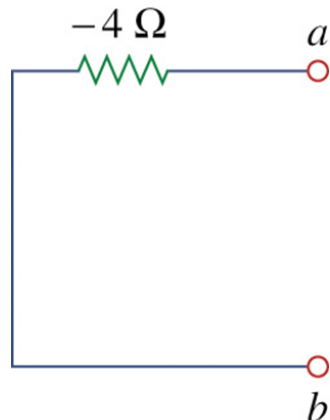
Check with R_L (9Ω) and voltage source ($10V$)



Thevenin Equivalent circuit:

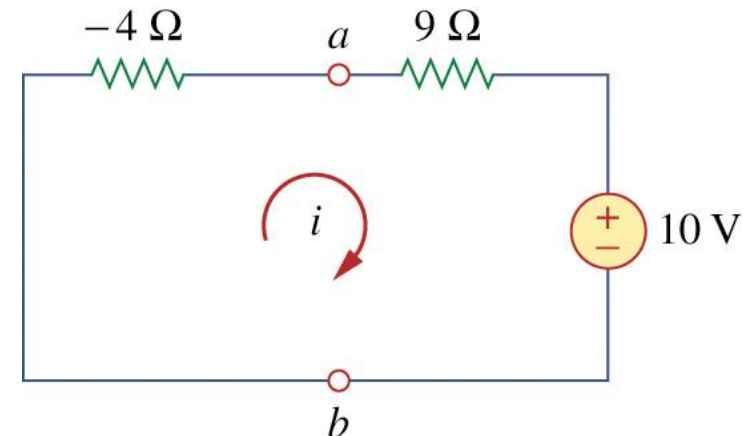

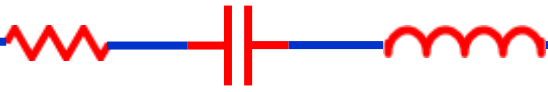Check with R_L (9Ω) and voltage source ($10V$)



Thevenin's Theorem

- Example 4.10:** Determine the Thevenin equivalent circuit in Fig (a).


Input circuit:

$$8i_x + 4i_1 + 2(i_1 - i_2) = 0 \quad , \quad i_x = i_2 - i_1$$

$$-2i_1 + 6i_2 = 0 \quad , \quad i_1 = 3i_2 \quad (1)$$

$$2(i_2 - i_1) + 9i_2 + 10 = 0$$

$$5i_2 = -10 \Rightarrow i_2 = -2A$$

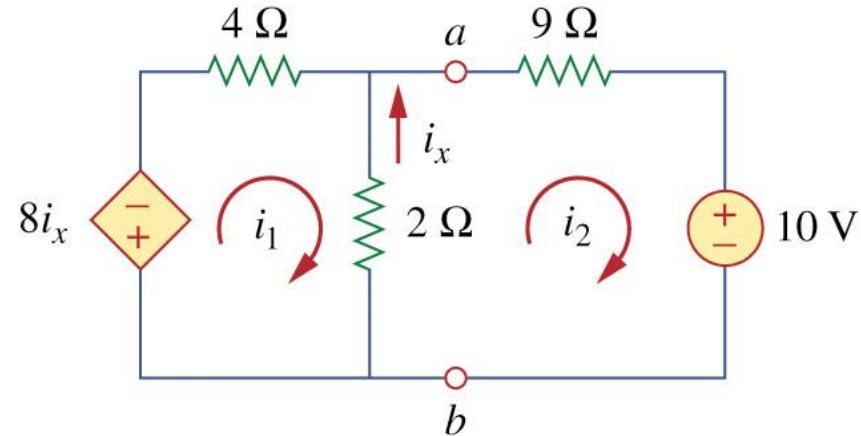


Check with R_L (9Ω) and voltage source ($10V$)

Thevenin Equivalent circuit:


$$-4i + 9i + 10 = 0$$

$$5i = -10 \Rightarrow i = -2A$$

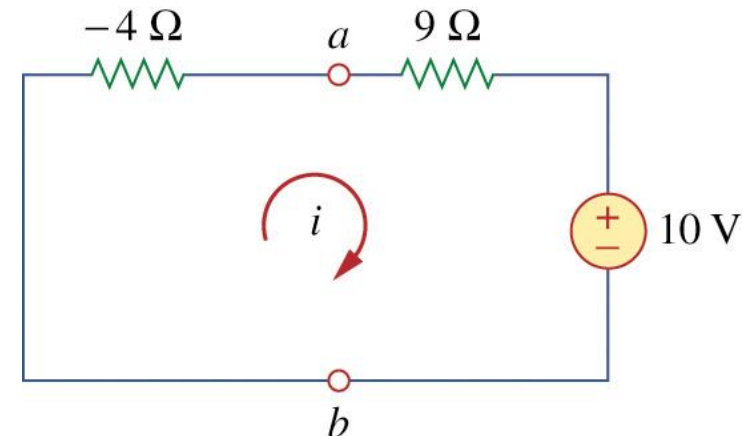Load current in both circuits are equal.
So the Thevenin Equivalent circuit is OK.




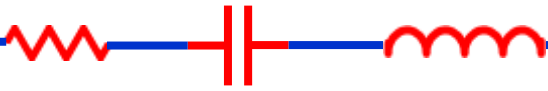Check with R_L (9Ω) and voltage source ($10V$)




Norton's Theorem

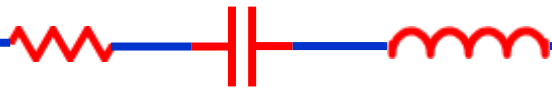- **Norton's theorem** states that a linear two-terminal circuit can be replaced by an equivalent circuit consisting of a **current source I_N in parallel** with a **resistor R_N** .
- **I_N** is the short-circuit current through the terminals and
- **R_N** is the input or equivalent resistance at the terminals when the **independent source are turn off**.




Norton's Theorem


- Property of Linear Circuits

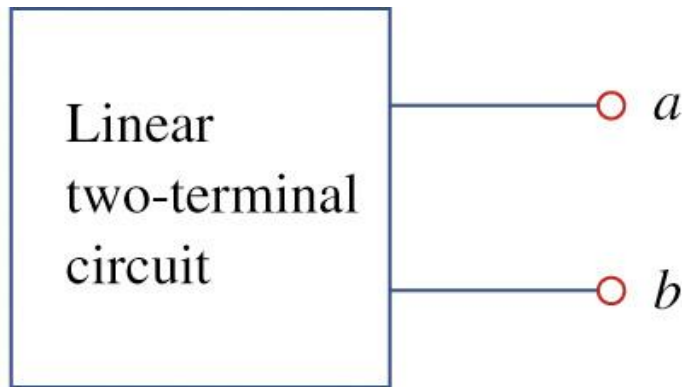


(a)

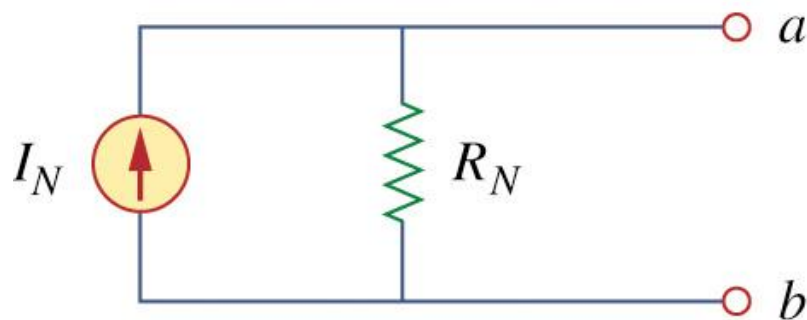

(b)

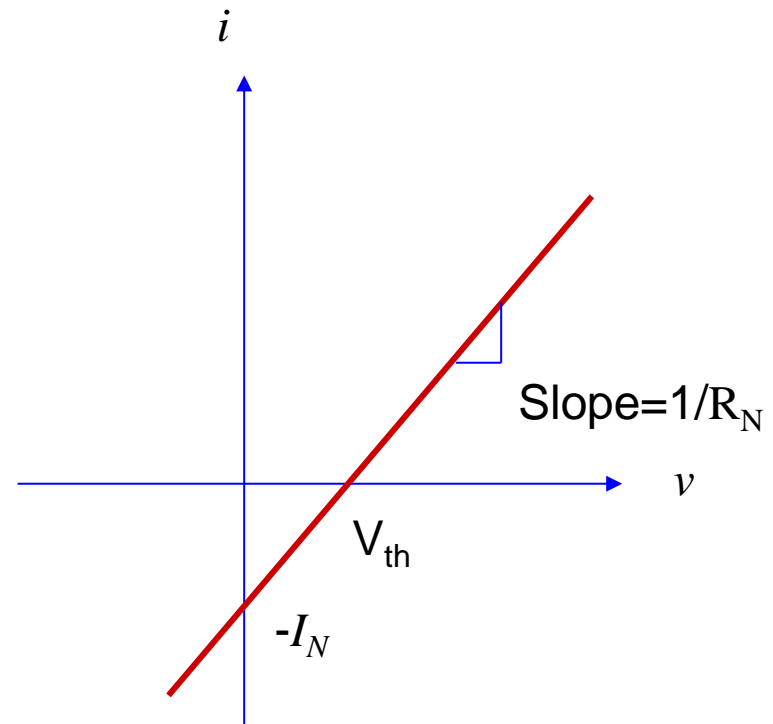

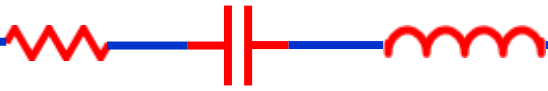

Norton's Theorem


• How to find Norton Current


- Thevenin and Norton resistances are **equal**:

$$R_N = R_{Th}$$

- **Short circuit current** from a to b gives the Norton current:

$$I_N = i_{sc} = \frac{V_{Th}}{R_{Th}}$$

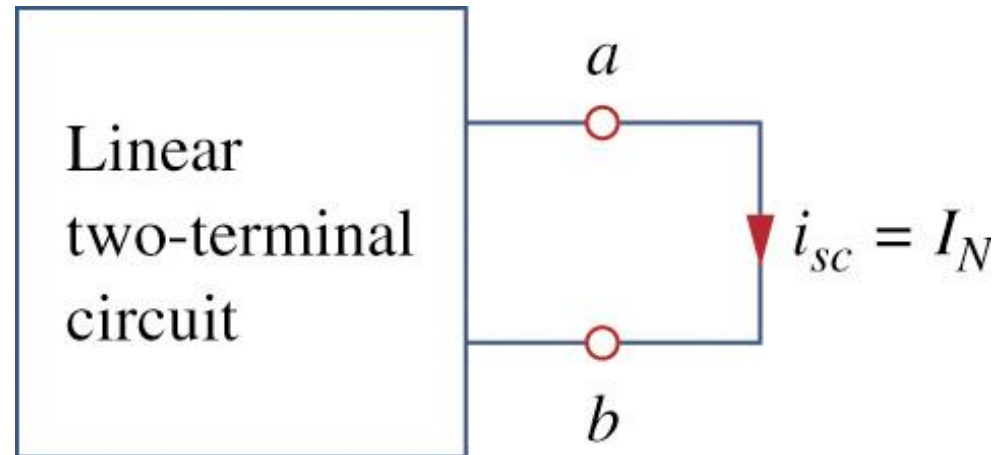

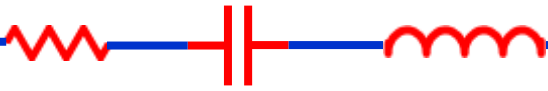


Norton's Theorem

- **Thevenin or Norton equivalent circuit**
 - The **open circuit voltage** v_{oc} across terminals ***a*** and ***b***
 - The **short circuit current** i_{sc} at terminals ***a*** and ***b***
 - The **equivalent or input resistance** R_{in} at terminals ***a*** and ***b*** when all **independent source** are **turn off**.

$$V_{Th} = v_{oc}$$


$$I_N = i_{sc}$$


$$R_{Th} = \frac{V_{Th}}{I_N} = R_N$$

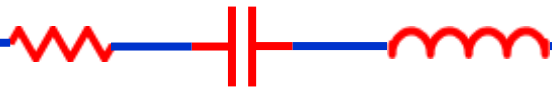

Norton's Theorem

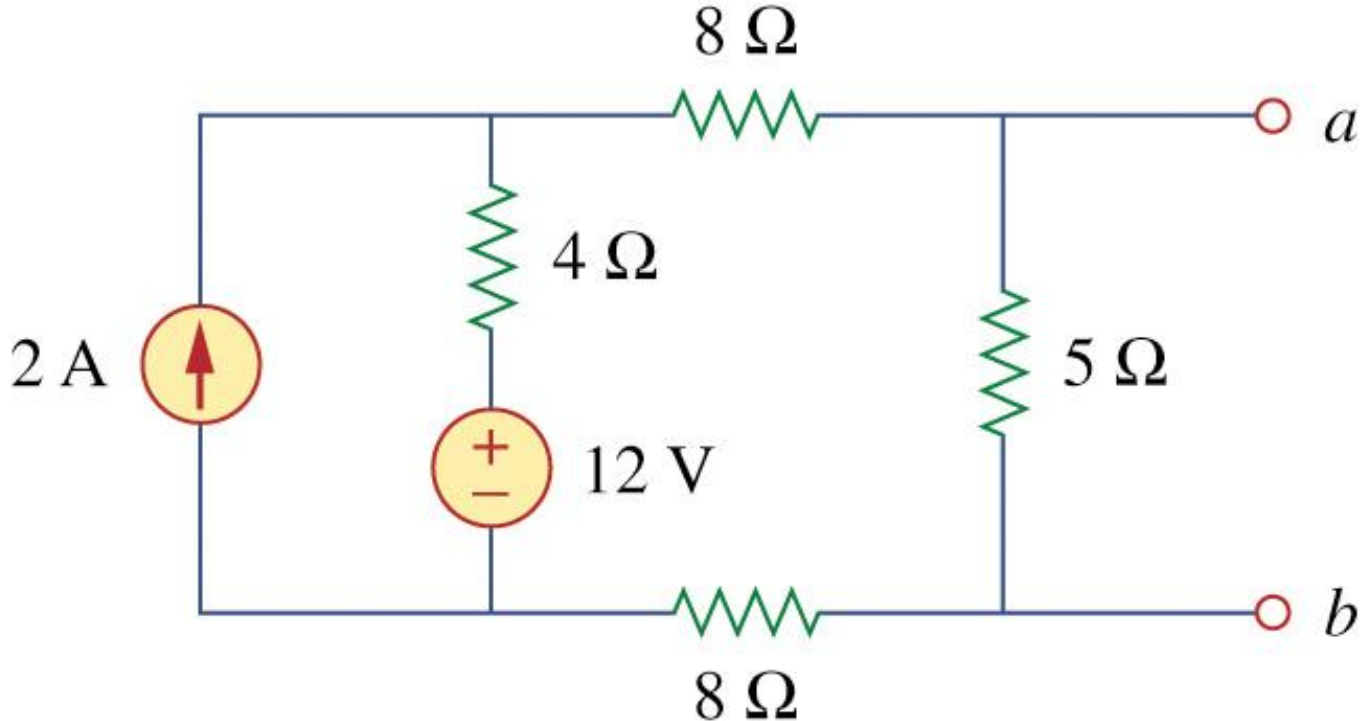- Example 4.11:** Find the Norton equivalent circuit of the circuit in Fig 4.39.



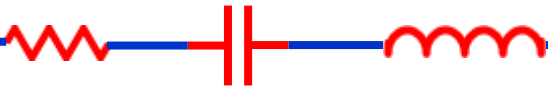


Norton's Theorem


- Example 4.11:** Find the Norton equivalent circuit of the circuit in Fig 4.39.

Find R_N : Use Fig (a):

$$R_N = 5 \parallel (8 + 4 + 8)$$
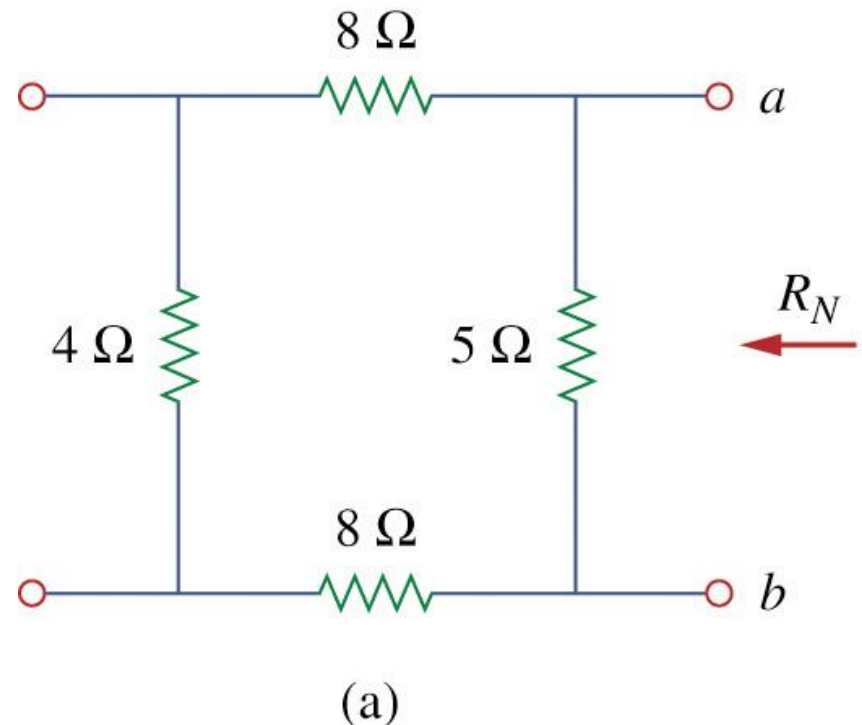
$$= 5 \parallel 20 = \frac{20 \times 5}{25} = 4\Omega$$



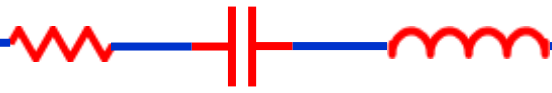

Norton's Theorem


- Example 4.11:** Find the Norton equivalent circuit of the circuit in Fig 4.39.

Find I_N : Use Fig (b):


(**short circuit** terminals **a** and **b**)

$$\text{Mesh : } i_1 = 2A, \quad 20i_2 - 4i_1 - 12 = 0$$

$$i_2 = 1A = i_{sc} = I_N$$

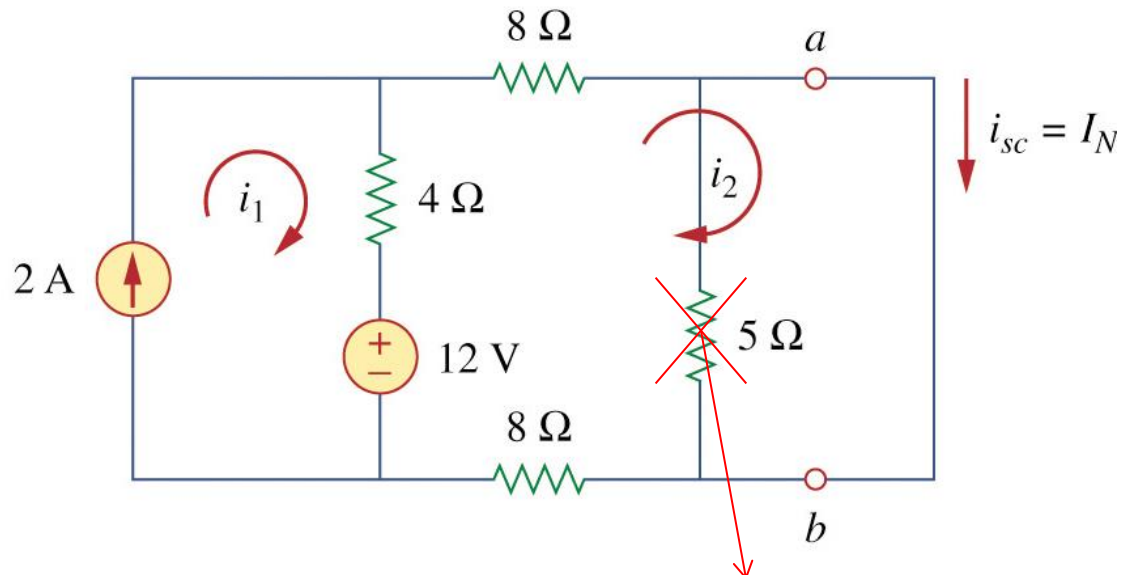

(b) (ignore 5Ω. Because it is shorted)

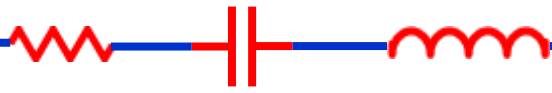

Norton's Theorem

- Example 4.11:** Find the Norton equivalent circuit of the circuit in Fig 4.39.

Find I_N : Use Fig (c): **Alternative Method** $I_N = \frac{V_{Th}}{R_{Th}}$

V_{Th} : (**open circuit voltage** across terminals **a** and **b**)

Mesh analysis:


$$i_3 = 2A, \quad 25i_4 - 4i_3 - 12 = 0$$


$$\therefore i_4 = 0.8A$$

$$\therefore v_{oc} = V_{Th} = 5i_4 = 4V$$

Hence,
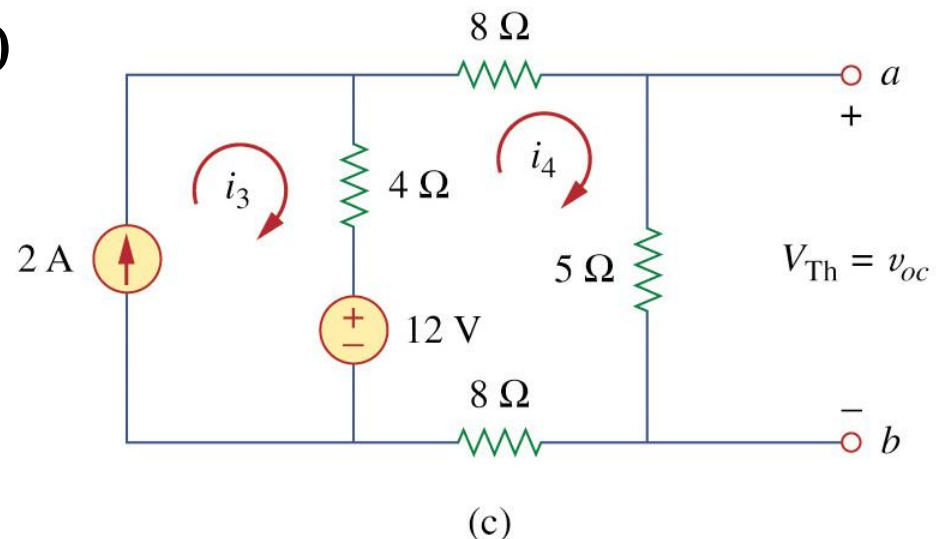
$$I_N = \frac{V_{Th}}{R_{Th}} = 4 / 4 = 1A$$




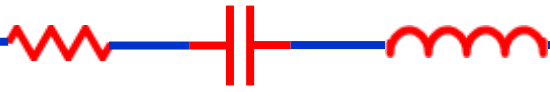


Norton's Theorem


- Example 4.11:** Find the Norton equivalent circuit of the circuit in Fig 4.39.

Input circuit:

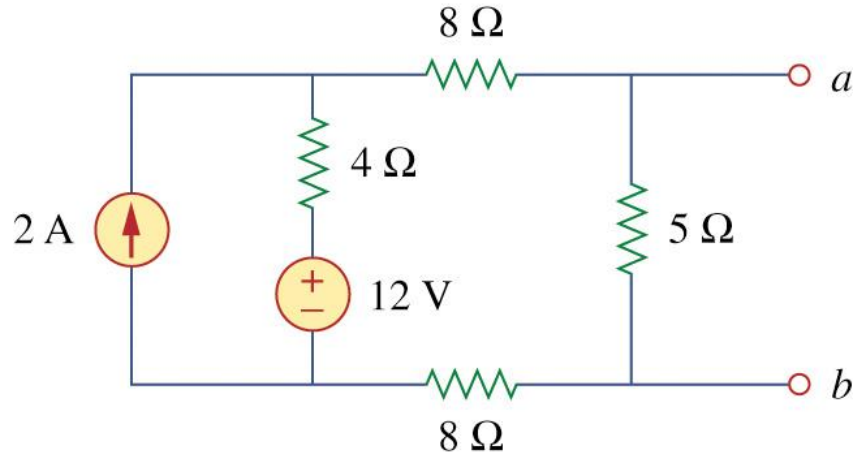


Norton's Equivalent circuit:

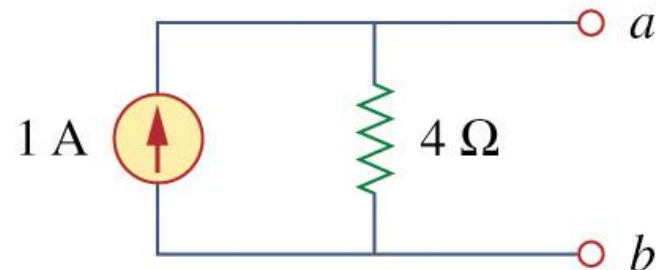


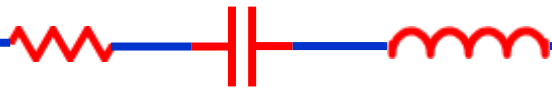

Norton's Theorem

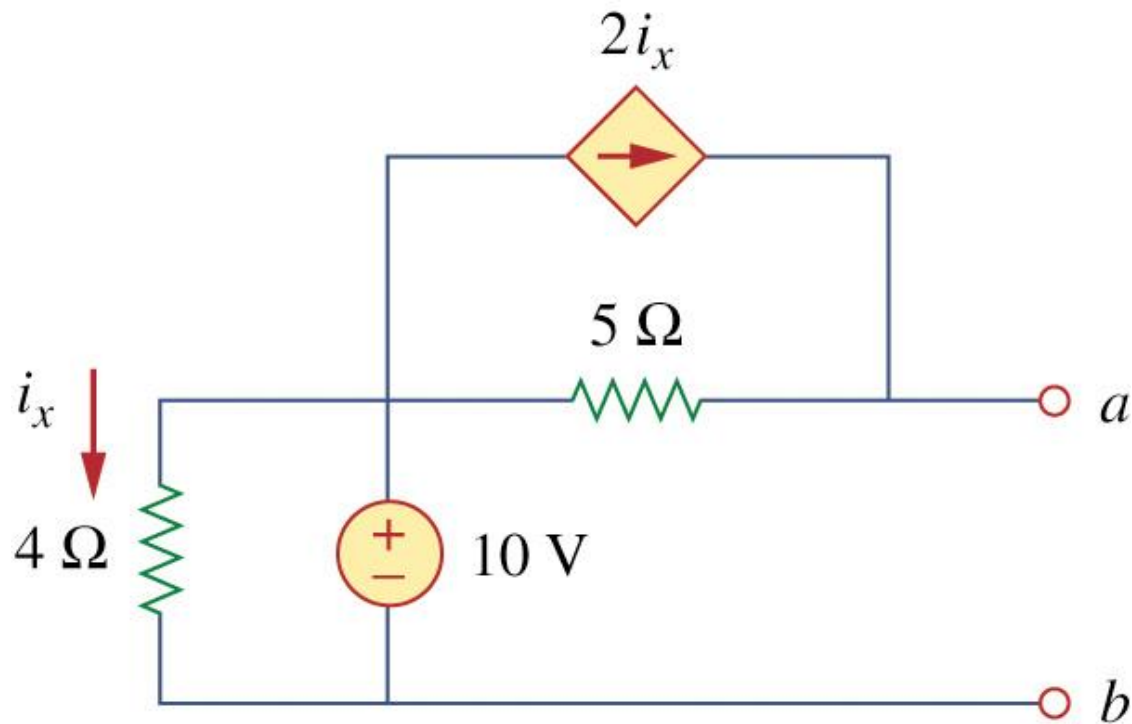- Example 4.12:** Using Norton's theorem, find R_N and I_N of the circuit in Fig 4.43 at terminals a - b .



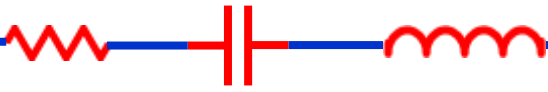

Norton's Theorem

- Example 4.12:** Using Norton's theorem, find R_N and I_N of the circuit in Fig 4.43 at terminals a - b .


Find R_N : Use Fig (a):

- 4Ω resistor shorted
- $5\Omega \parallel v_o \parallel 2i_x$: Parallel


Hence,

$$i_x = 0\text{A}, \quad i_o = \frac{v_o}{5\Omega} = \frac{1\text{V}}{5\Omega} = 0.2\text{A}$$
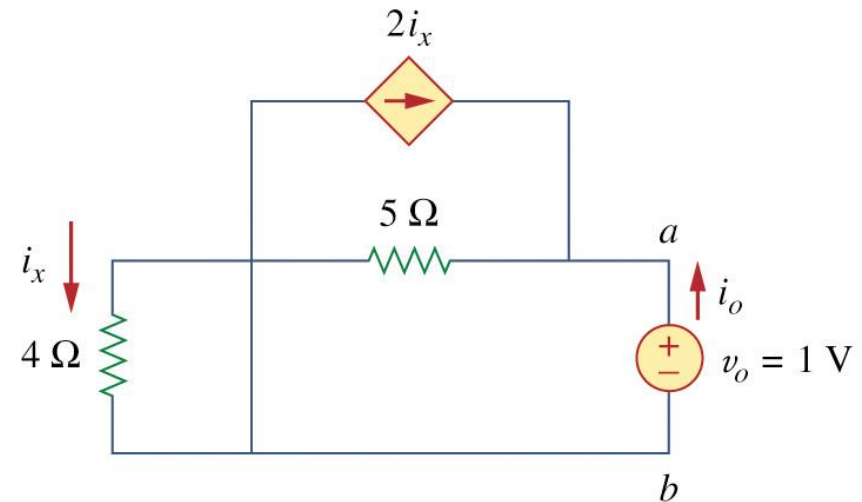
$$\therefore R_N = \frac{v_o}{i_o} = \frac{1}{0.2} = 5\Omega$$



(a)

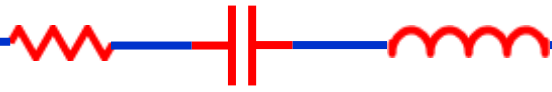

Norton's Theorem

- Example 4.12:** Using Norton's theorem, find R_N and I_N of the circuit in Fig 4.43 at terminals a - b .


Find I_N :

- $4\Omega \parallel 10V \parallel 5\Omega \parallel 2i_x$: Parallel


$$i_x = \frac{10 - 0}{4} = 2.5 \text{ A},$$

$$i_{sc} = i_x + 2i_x = \frac{10}{5} + 2(2.5) = 7 \text{ A}$$

$$\therefore I_N = 7 \text{ A}$$

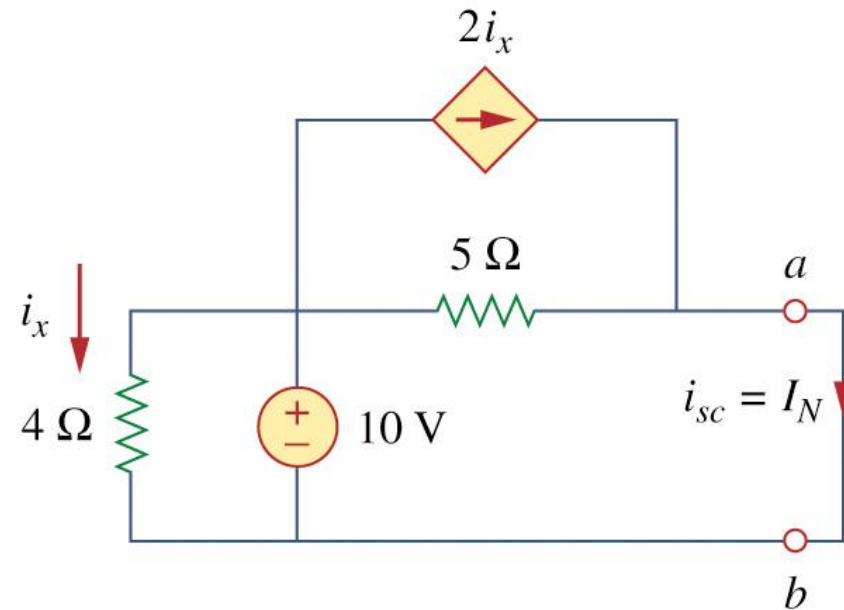


(b)

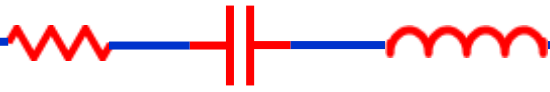


Norton's Theorem


- Example 4.12:** Using Norton's theorem, find R_N and I_N of the circuit in Fig 4.43 at terminals a - b .

Input circuit:

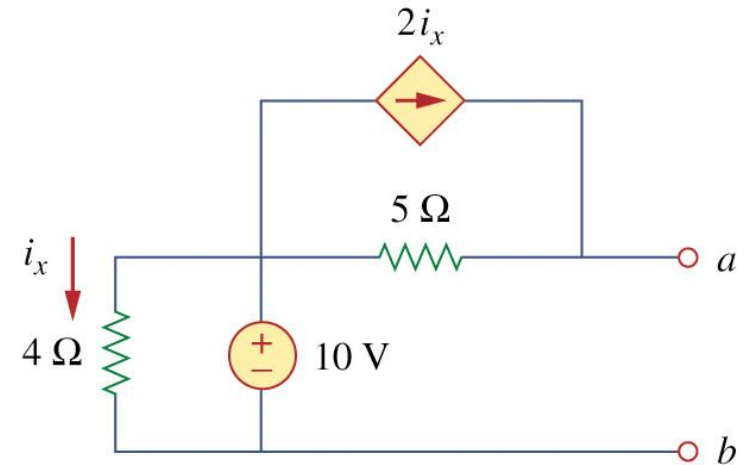


Norton's Equivalent circuit:

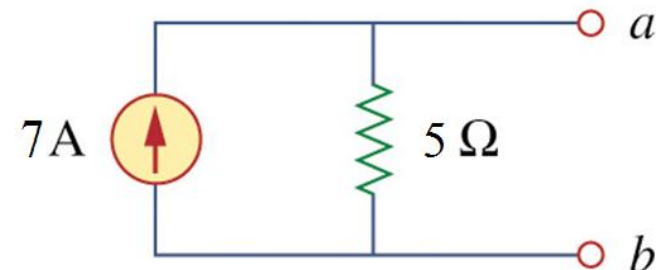

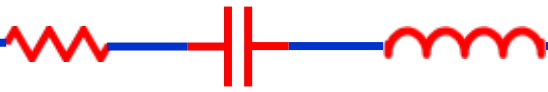


Maximum Power Transfer

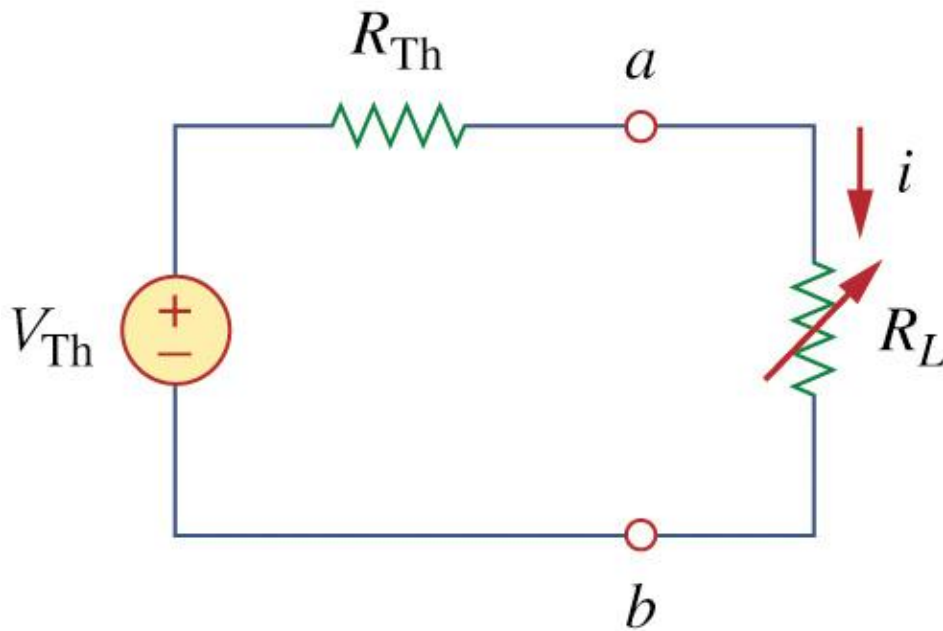- The Thevenin equivalent is useful in finding the **maximum power** a linear circuit can deliver to a load.



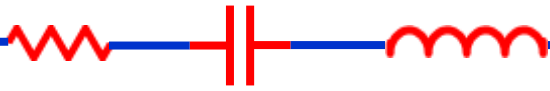
$$p = i^2 R_L = \left(\frac{V_{\text{TH}}}{R_{\text{TH}} + R_L} \right)^2 R_L$$




Maximum Power Transfer

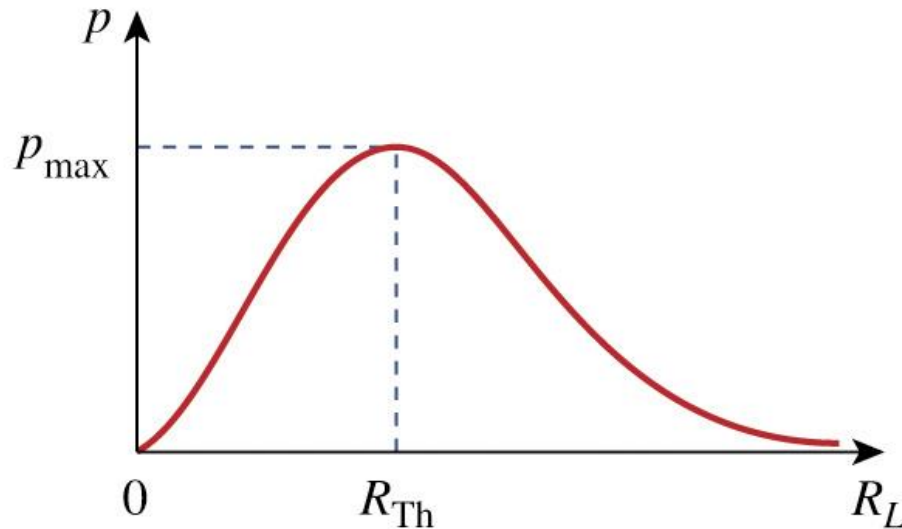- Maximum power** is transferred to the load when the load resistance equals the **Thevenin resistance** as seen from the load ($R_L = R_{TH}$).


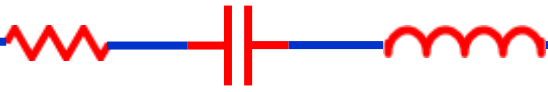
$$p = i^2 R_L = \left(\frac{V_{TH}}{R_{TH} + R_L} \right)^2 R_L$$



Maximum Power Transfer

- P_{\max} can be obtained when:

$$\frac{dp}{dR_L} = 0$$


$$\frac{dp}{dR_L} = V_{TH}^2 \left[\frac{(R_{TH} + R_L)^2 - 2R_L(R_{TH} + R_L)}{((R_{TH} + R_L)^2)^2} \right] = 0$$

$$= V_{TH}^2 \left[\frac{(R_{TH} + R_L)^2 - 2R_L(R_{TH} + R_L)}{(R_{TH} + R_L)^4} \right] = V_{TH}^2 \left[\frac{(R_{TH} + R_L - 2R_L)}{(R_{TH} + R_L)^3} \right] = 0$$

$$\Rightarrow (R_{TH} + R_L - 2R_L) = 0 \quad \Rightarrow (R_{TH} - R_L) = 0$$


$$R_L = R_{TH}$$


$$P_{\max} = \frac{V_{TH}^2}{4R_{TH}}$$

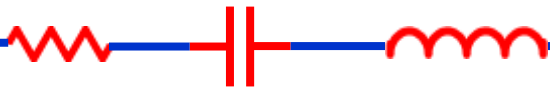

Maximum Power Transfer

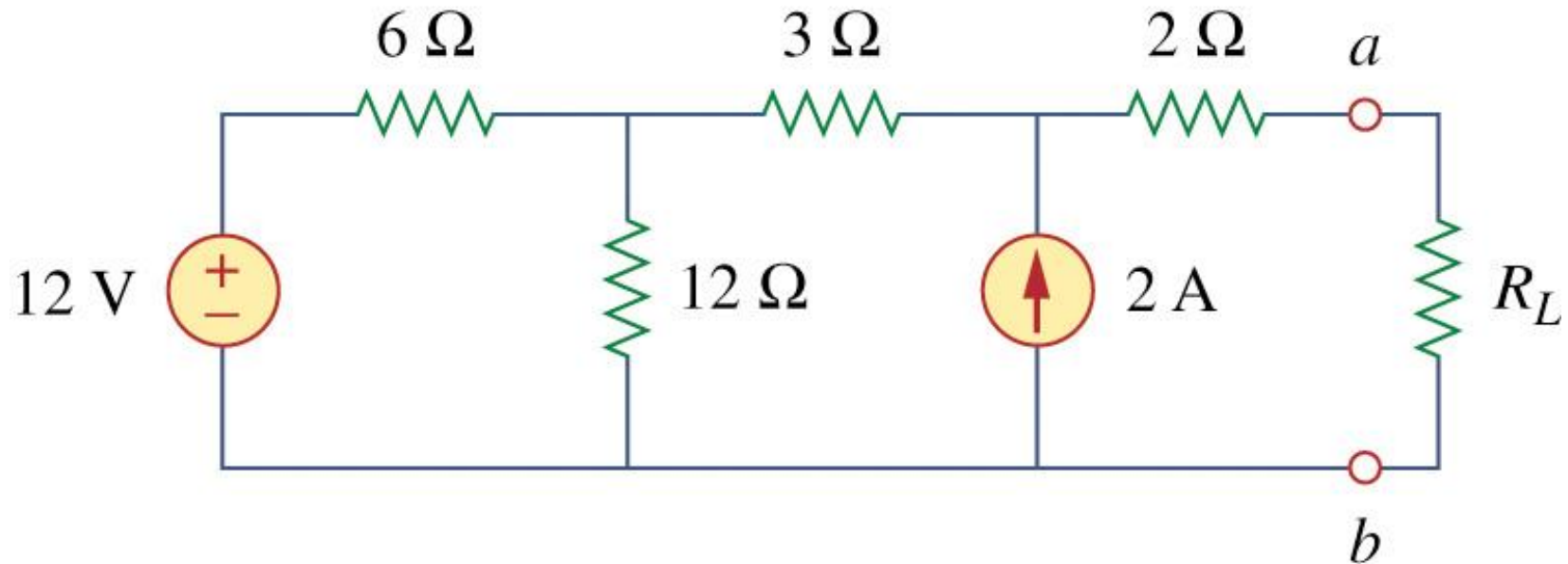- Example 4.13:** Find the value of R_L for maximum power transfer in the circuit of Fig. 4.50. Find the maximum power.



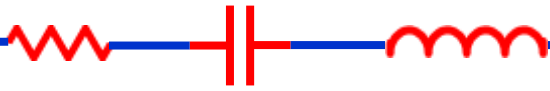


Maximum Power Transfer

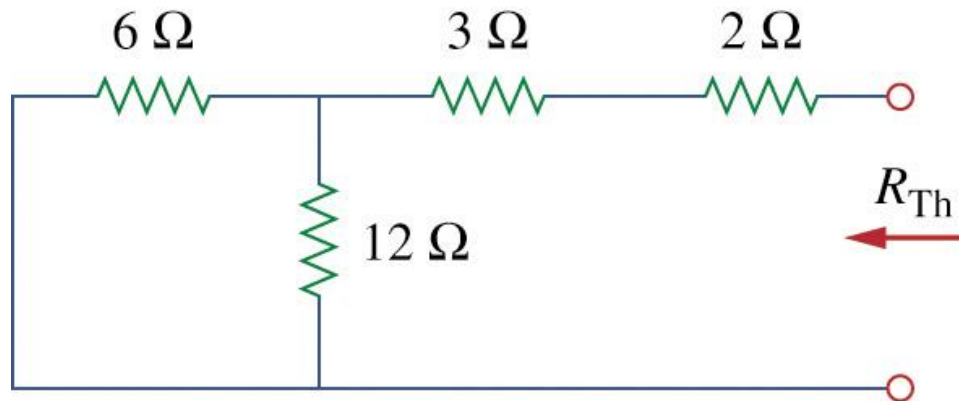
- Example 4.13:** Find the value of R_L for maximum power transfer in the circuit of Fig. 4.50. Find the maximum power.

Find R_{Th} :

$$R_{TH} = 2 + 3 + 6 \parallel 12 = 5 + \frac{6 \times 12}{18} = 9 \Omega$$



(a)

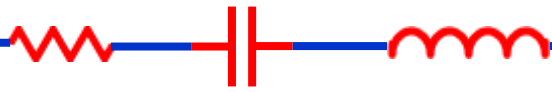

Maximum Power Transfer


- Example 4.13:** Find the value of R_L for maximum power transfer in the circuit of Fig. 4.50. Find the maximum power.

Find V_{Th} :

$$-12 + 18i_1 - 12i_2, \quad i_2 = -2A, \quad i_2 = -\frac{2}{3}A$$

KVL around the outer loop:
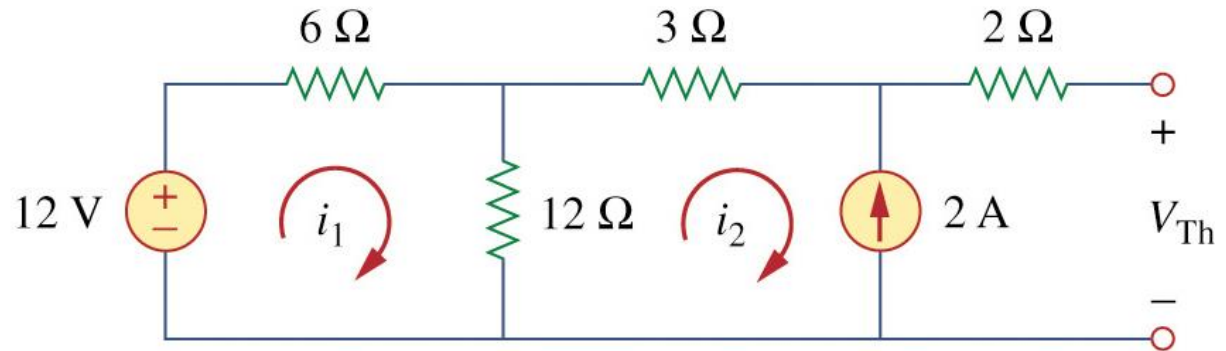
$$-12 + 6i_1 + 3i_2 + 2(0) + V_{TH} = 0 \Rightarrow V_{TH} = 22V$$



(b)

$$R_L = R_{TH} = 9\Omega$$

$$\Rightarrow p_{\max} = \frac{V_{TH}^2}{4R_L} = \frac{22^2}{4 \times 9} = 13.44W$$