



# Decoders and Encoders

## ELCTEC-131

# Basic Decoder

- **Decoder:** A digital circuit designed to detect the presence of a particular digital state.
- Can have one output or multiple outputs.

# Example:

- 2-Input NAND Gate detects the presence of '1 1' on the inputs to generate a '0' output.


# Single-Gate Decoders

- Uses single gates (AND/NAND) and some Inverters.
- Example: 4-Input AND detects '1111' on the inputs to generate a '1' output.


# Inputs

- Inputs are labeled  $D_3$ ,  $D_2$ ,  $D_1$ , and  $D_0$ , with  $D_3$  the MSB (most significant bit) and  $D_0$  the LSB (least significant bit).

# Single-Gate Decoders

 

**a. Active-HIGH indication**

 

**b. Active-LOW indication**

# Single-Gate Examples

- If the inputs to a 4-Input NAND are given as  $\overline{D_1}$ ,  $\overline{D_2}$ ,  $\overline{D_3}$ ,  $D_4$ , then the NAND detects the code 0001. The output is a 0 when the code 0001 is detected.
- This type of decoder is used in Address Decoding for a PC System Board.

# Multiple Output Decoders


- Decoder circuit with  $n$  inputs can activate  $m = 2^n$  load circuits.
- Called a  $n$ -line-to- $m$ -line decoder, such as a 2-to-4 or a 3-to-8 decoder.
- Usually has an active low enable  $\overline{G}$  that enables the decoder outputs.



# Truth Table for a 3-to-8 Decoder

$\overline{G}$	$D_2$	$D_1$	$D_0$	$Y_0$	$Y_1$	$Y_2$	$Y_3$	$Y_4$	$Y_5$	$Y_6$	$Y_7$
1	X	X	X	1	1	1	1	1	1	1	1
0	0	0	0	0	1	1	1	1	1	1	1
0	0	0	1	1	0	1	1	1	1	1	1
0	0	1	0	1	1	0	1	1	1	1	1
●	●	●	●	●	●	●	●	●			


# 3-to-8 Decoder

 

# Simulation

- **Simulation:**The verification of a digital design using a timing diagram before programming the design in a CPLD.
- Used to check the Output Response of a design to an Input Stimulus using a timing diagram.

# Simulation

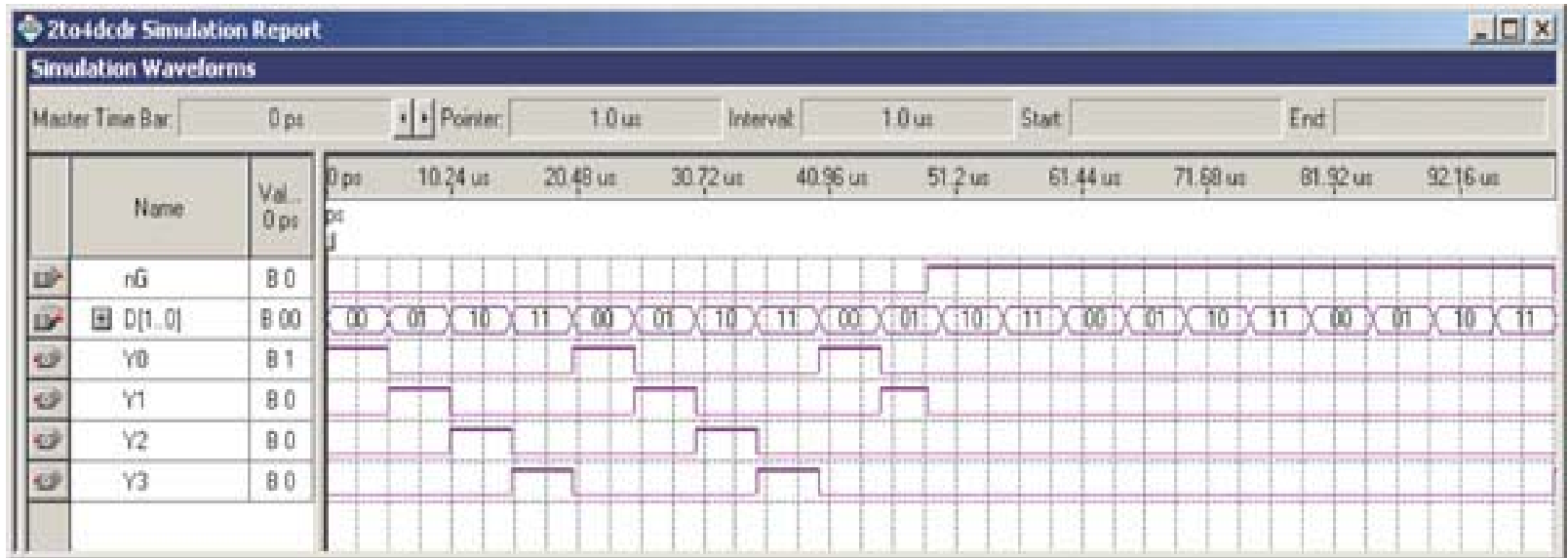

# VHDL Binary Decoder

- Use **select signal assignment statements** constructs or **conditional signal assignment statements** constructs.

# 2-to-4 Decoder VHDL Entity

- Using a select signal assignment statement:

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.ALL;
```

```
ENTITY decode3 IS
```

```
PORT(
```

```
    d : IN STD_LOGIC_VECTOR (1 downto 0);
```

```
    y : OUT STD_LOGIC_VECTOR (3 downto 0));
```

```
END decode3;
```

# Selected Signal Entity

- In the previous slide, the Entity used a STD LOGIC Array for Inputs and Outputs.
- The `Y : OUT STD_LOGIC_VECTOR(3 downto 0)` is equal to  $Y_3, Y_2, Y_1, Y_0$ .

# Data Type

- The `STD_LOGIC` Data Type is similar to `BIT` but has added state values such as `Z`, `X`, `H`, and `L` instead of just `0` and `1`.



# Selected Signal Assignments

- Uses a VHDL Architecture construct called **WITH SELECT**.
- Format is:
  - **WITH (signal input(s)) SELECT.**
  - Signal input states are used to define the output state changes.

# 2-to-4 Decoder VHDL Architecture

```
ARCHITECTURE decoder OF decode3 IS  
BEGIN  
  WITH d SELECT  
    y <= "0001" WHEN "00",  
        "0010" WHEN "01",  
        "0100" WHEN "10",  
        "1000" WHEN "11",  
        "0000" WHEN others;  
END decoder;
```

# Decoder Architecture

- The decoder Architecture used a SELECT to evaluate **d** to determine the Output **y**.
- Both **d** and **y** are defined as an Array (or bus or vector) Data Type.


# Decoder Architecture

- The last state for WHEN OTHERS is added for the other logic states (Z, X, H, L, etc.).


# Seven-Segment Displays

- **Seven-Segment Display:** An array of seven independently controlled LEDs shaped like an 8 that can be used to display decimal digits.

# Seven-Segment Displays

 

# Seven-Segment Displays

 

# Common Anode Display


- Common Anode Display (CA): A seven-segment display where the anodes of all the LEDs are connected together to  $V_{CC}$  and a '0' turns on a segment (a to g).




# Common Cathode Display

- Common Cathode Display (CC): A seven-segment display where all the cathodes are connected and tied to ground, and a '1' turns on a segment.


# Common Cathode Display

 

 a. Circuit requirements for an illuminated LED




b. Common cathode

 

b. Common anode

# Common Cathode Display

 

# Seven-Segment Decoder/Driver – I

- Receives a BCD (Binary Coded Decimal) 4-Bit input, outputs a BCD digit 0000 – 1001 (0 through 9).
- Generates Outputs (a–g) for each of the display LEDs.

# Seven-Segment Decoder/Driver – 2

- Requires a current limit series resistor for each segment.
- Decoders for a CC-SS have active high outputs while decoders for a CA-SS have active low outputs (a to g).

# Seven-Segment Decoder/Driver – 3

- The outputs generated for the binary input combinations of 1010 to 1111 are “don’t cares”.
- The decoder can be designed with VHDL or MSI Logic (7447, 7448).

# SS Decoder/Driver Truth Table


Digit	Seven-Segment Display										
	D3	D2	D1	D0	h0	h1	h2	h3	h4	h5	h6
0	0	0	0	0	0	0	0	0	0	0	1
1	0	0	0	1	1	0	0	1	1	1	1
2	0	0	1	0	0	0	1	0	0	1	0
3	0	0	1	1	0	0	0	0	1	1	0
4	0	1	0	0	1	0	0	1	1	0	0
5	0	1	0	1	0	1	0	0	1	0	0
6	0	1	1	0	1	1	0	0	0	0	0
7	0	1	1	1	0	0	0	1	1	1	1
8	1	0	0	0	0	0	0	0	0	0	0

# SS Decoder/Driver Truth Table

$D_3D_2 \backslash D_1D_0$	00	01	11	10
00	0	1	0	0
01	1	0	0	1
11	X	X	X	X
10	0	0	X	X

Segment a

a. K-map

 

b. Decoder for segment a (common anode)



# Decoder/Driver Entity (CA)

```
ENTITY bcd_7seg IS  
  PORT(  
    d3, d2, d1, d0      : IN BIT;  
    h1,h2,h3,h4,h5,h6  : OUT BIT;  
END bcd_7seg;
```

# Decoder/Driver Architecture – I

**ARCHITECTURE** seven\_segment **OF** bcd\_7seg **IS**

**SIGNAL** input : **BIT\_VECTOR** (3 downto 0);

**SIGNAL** output : **BIT\_VECTOR** (6 downto 0);

**BEGIN**

input <= d3 & d2 & d1 & d0;

-- Uses two intermediate signals called input and output (internal no pins)

-- Creates an array by using the concatenate operator (&)

In this case input(3) <= d3, input(2) <= d2, etc.

# Decoder/Driver Architecture – 2

**WITH input SELECT**

```
output <= “000001” WHEN “0000”,  
         “0011111” WHEN “0001”,  
         “0010011” WHEN “0010”,  
         “0000111” WHEN “0011”,  
         •         •         •  
         •         •         •  
         •         •         •  
         “1111111” WHEN others;
```

# Decoder/Driver Architecture – 3

```
h0    <=    output(6);  
h1    <=    output(5);  
h2    <=    output(4);  
h3    <=    output(3);  
h4    <=    output(2);  
h5    <=    output(1);  
h6    <=    output(0);
```

```
END seven_segment
```

# SS VHDL File Description

- In the preceding example file, a concurrent select signal assignment was used (`WITH (signals) SELECT`).
- The intermediate output signals were mapped to the segments (0 to 6).

# Example:

- when Input ( $D_3 - D_0$ ) is 0001, the decoder sets for CA display
  - $h_0=h_3=h_4=h_5=h_6=1$
  - $h_1=h_2=0$ .

# Sequential Process in VHDL

- A VHDL Process is a construct that encloses sequential statements that are executed when a signal in a sensitivity list changes.

# Sequential Process Basic Format

- Basic Format:

```
PROCESS(Sensitivity List)
```

```
BEGIN
```

```
    Sequential Statements;
```

```
END PROCESS;
```



# Encoders

- **Encoder:** A digital circuit that generates a specific code at its outputs in response to one or more active inputs.
- It is complementary in function to a decoder.

# Encoders

- Output codes are usually Binary or BCD.

# Priority Encoders

- **Priority Encoder:** An encoder that generates a code based on the highest-priority input.
- For example, if input  $D_3 = \text{input } D_5$ , then the output is 101, not 011.  $D_5$  has a higher priority than  $D_3$  and the output will respond accordingly.

# 8-to-3 Encoder Truth Table

Active High Inputs

$D_7$	$D_6$	$D_5$	$D_4$	$D_3$	$D_2$	$D_1$	$D_0$	$Q_2$	$Q_1$	$Q_0$
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
	•					•			•	
1	0	0	0	0	0	0	0	1	1	1

# Priority Encoder Equations

$$Q_2 = D_7 + D_6 + D_5 + D_4$$

$$Q_1 = D_7 + D_6 + \overline{D_5} \overline{D_4} D_3 + \overline{D_5} \overline{D_4} D_2$$

$$Q_0 = D_7 + \overline{D_6} D_5 + \overline{D_6} \overline{D_4} D_3 + \overline{D_6} \overline{D_4} \overline{D_2} D_1$$

# Priority Encoder VHDL Entity

```
-- hi_pri8a.vhd
```

```
ENTITY hi_pri8a IS
```

```
    PORT(
```

```
        d           :IN  BIT_VECTOR (7 downto 0);
```

```
        q           :OUT BIT_VECTOR (2 downto
```

```
        0));
```

```
END hi_pri8a;
```

# Priority Encoder VHDL Architecture

```
ARCHITECTURE a OF hi_pri8a IS  
BEGIN
```

```
-- Concurrent Signal Assignments
```

```
    q(2)    <=    d(7) or d(6) or d(5) or d(4);
```

```
    q(1)    <=    d(7) or d(6)  
                or ((not d(5)) and (not d(4)) and d(3))  
                or ((not d(5)) and (not d(4)) and d(2));
```

```
    q(0)    <=    -- in a similar fashion
```

```
END a;
```

# Another VHDL Encoder – I

```
-- hi_pri8b.vhd
```

```
ENTITY hi_pri8a IS
```

```
    PORT(  
        d
```

```
        :IN  BIT_VECTOR (7 downto 0);
```

```
        q
```

```
        :OUT INTEGER RANGE 0 TO
```

```
        7);
```

```
END hi_pri8b;
```




# Another VHDL Encoder – 2


```
ARCHITECTURE a OF hi_pri8b IS  
BEGIN  
encoder;  
    q <=      7 WHEN d(7) = '1' ELSE  
              6 WHEN d(6) = '1' ELSE  
              5 WHEN d(5) = '1' ELSE  
              4 WHEN d(4) = '1' ELSE  
              3 WHEN d(3) = '1' ELSE  
              2 WHEN d(2) = '1' ELSE  
              1 WHEN d(1) = '1' ELSE  
              0;  
END a;
```

# VHDL Implementation of a Binary Decoder

- Write a VHDL file for a 3-line-to-8-line decoder with active-LOW outputs. Use a selected signal assignment statement. Save the file as


***drive:\qdesigns\labs\lab 11\decode3to8\_vhdl\decode3to8\_vhdl.vhd.*** Use the file to create a new project


- 
- Write a set of simulation criteria for the 3-line-to-8-line decoder you created in step 1 of this procedure

- 
- Use the simulation criteria to create a set of simulation waveforms to test the correctness of your design.
  - Assign pin numbers to the VHDL decoder, as shown in Table 11.3. Compile the design again and download it to the DE1 test board.
 
# Hexadecimal-to-Seven-Segment Decoder

- Create a hexadecimal-to-seven-segment decoder in VHDL, using the segment patterns in Figure 11.3 as a model.
- Save the VHDL file as **`drive:\qdesigns\labs\lab 11\hex7seg\hex7seg.vhd`**. Use the file to create a new project.



- 
- **Assign pin numbers.**
  - **Compile the file and download it to the DEI board.**