
Digital Logic Basics

Chapter 2
S. Dandamudi

Outline


- Basic concepts
 - * Simple gates
 - * Completeness
- Logic functions
 - * Expressing logic functions
 - * Equivalence
- Boolean algebra
 - * Boolean identities
 - * Logical equivalence
- Logic Circuit Design Process
- Deriving logical expressions
 - * Sum-of-products form
 - * Product-of-sums form
- Simplifying logical expressions
 - * Algebraic manipulation
 - * Karnaugh map method
 - * Quine-McCluskey method
- Generalized gates
- Multiple outputs
- Implementation using other gates (NAND and XOR)

Introduction


- Hardware consists of a few simple building blocks
 - * These are called *logic gates*
 - » AND, OR, NOT, ...
 - » NAND, NOR, XOR, ...
- Logic gates are built using transistors
 - » NOT gate can be implemented by a single transistor
 - » AND gate requires 3 transistors
- Transistors are the fundamental devices
 - » Pentium consists of 3 million transistors
 - » Compaq Alpha consists of 9 million transistors
 - » Now we can build chips with more than 100 million transistors

Basic Concepts

 
- Simple gates
 - * AND
 - * OR
 - * NOT
- Functionality can be expressed by a truth table
 - * A truth table lists output for each possible input combination
- Other methods
 - * Logic expressions
 - * Logic diagrams



A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

 

A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

 

A	F
0	1
1	0

Truth table

Basic Concepts (cont'd)

- Additional useful gates
 - * NAND
 - * NOR
 - * XOR
- NAND = AND + NOT
- NOR = OR + NOT
- XOR implements exclusive-OR function
- NAND and NOR gates require only 2 transistors
 - * AND and OR need 3 transistors!



NAND gate

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0



NOR gate

A	B	F
0	0	1
0	1	0
1	0	0
1	1	0



XOR gate

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

Logic symbol

Truth table

Basic Concepts (cont'd)

- Number of functions
 - * With N logical variables, we can define 2^{2^N} functions
 - * Some of them are useful
 - » AND, NAND, NOR, XOR, ...
 - * Some are not useful:
 - » Output is always 1
 - » Output is always 0
 - * "Number of functions" definition is useful in proving completeness property

Basic Concepts (cont'd)

- Complete sets
 - * A set of gates is complete
 - » if we can implement any logical function using only the type of gates in the set
 - You can use as many gates as you want
 - * Some example complete sets
 - » {AND, OR, NOT} ← Not a minimal complete set
 - » {AND, NOT}
 - » {OR, NOT}
 - » {NAND}
 - » {NOR}
 - * Minimal complete set
 - A complete set with no redundant elements.

2003


© S. Dandamudi

Chapter 2: Page 7


To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Basic Concepts (cont'd)


- Proving NAND gate is universal

 

AND gate

 

NOT gate

 

OR gate

2003


© S. Dandamudi

Chapter 2: Page 8

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Basic Concepts (cont'd)


- Proving NOR gate is universal

 

OR gate



NOT gate

 

AND gate

2003


© S. Dandamudi

Chapter 2: Page 9

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Logic Chips

 - Basic building block:
 - » Transistor
- Three connection points
 - * Base
 - * Emitter
 - * Collector
- Transistor can operate
 - * Linear mode
 - » Used in amplifiers
 - * Switching mode
 - » Used to implement digital circuits




2003

© S. Dandamudi

Chapter 2: Page 10

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Logic Chips (cont'd)

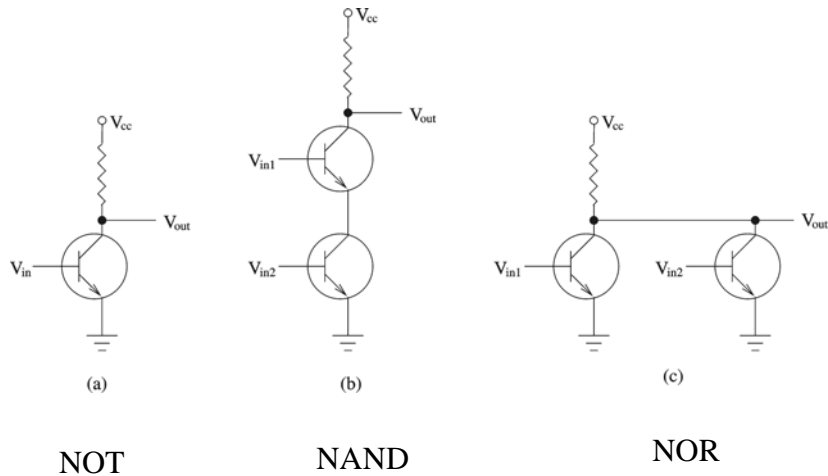

2003


© S. Dandamudi

Chapter 2: Page 11

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Logic Chips (cont'd)

 - Low voltage level: $< 0.4V$
- High voltage level: $> 2.4V$
- Positive logic:
 - * Low voltage represents 0
 - * High voltage represents 1
- Negative logic:
 - * High voltage represents 0
 - * Low voltage represents 1
- Propagation delay
 - * Delay from input to output
 - * Typical value: 5-10 ns




2003

© S. Dandamudi

Chapter 2: Page 12

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Logic Chips (cont'd)

 

2003

© S. Dandamudi

Chapter 2: Page 13

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Logic Chips (cont'd)

- Integration levels
 - * SSI (small scale integration)
 - » Introduced in late 1960s
 - » 1-10 gates (previous examples)
 - * MSI (medium scale integration)
 - » Introduced in late 1960s
 - » 10-100 gates
 - * LSI (large scale integration)
 - » Introduced in early 1970s
 - » 100-10,000 gates
 - * VLSI (very large scale integration)
 - » Introduced in late 1970s
 - » More than 10,000 gates

2003

© S. Dandamudi

Chapter 2: Page 14

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Logic Functions

- Logical functions can be expressed in several ways:
 - * Truth table
 - * Logical expressions
 - * Graphical form
- Example:
 - * Majority function
 - » Output is one whenever majority of inputs is 1
 - » We use 3-input majority function

2003

© S. Dandamudi

Chapter 2: Page 15

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.


Logic Functions (cont'd)

3-input majority function

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

- Logical expression form

$$F = A B + B C + A C$$

 

2003


© S. Dandamudi

Chapter 2: Page 16

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Logical Equivalence

 - All three circuits implement $F = A B$ function



2003

© S. Dandamudi

Chapter 2: Page 17

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Logical Equivalence (cont'd)

- Proving logical equivalence of two circuits
 - * Derive the logical expression for the output of each circuit
 - * Show that these two expressions are equivalent
 - » Two ways:
 - You can use the truth table method
 - For every combination of inputs, if both expressions yield the same output, they are equivalent
 - Good for logical expressions with small number of variables
 - You can also use algebraic manipulation
 - Need Boolean identities

2003


© S. Dandamudi

Chapter 2: Page 18

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Logical Equivalence (cont'd)

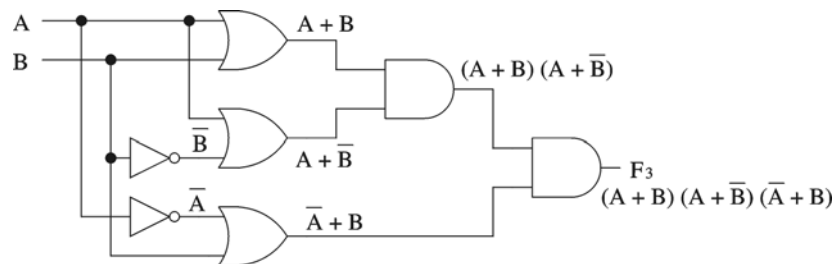- Derivation of logical expression from a circuit
 - * Trace from the input to output
 - » Write down intermediate logical expressions along the path



2003

© S. Dandamudi

Chapter 2: Page 19

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Logical Equivalence (cont'd)

- Proving logical equivalence: Truth table method

A	B	F1 = A B	F3 = (A + B) (A-bar + B) (A + B-bar)
0	0	0	0
0	1	0	0
1	0	0	0
1	1	1	1

2003

© S. Dandamudi

Chapter 2: Page 20

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Boolean Algebra

Boolean identities

Name	AND version	OR version
Identity	$x \cdot 1 = x$	$x + 0 = x$
Complement	$x \cdot \bar{x} = 0$	$x + \bar{x} = 1$
Commutative	$x \cdot y = y \cdot x$	$x + y = y + x$
Distribution	$x \cdot (y+z) = xy+xz$	$x + (y \cdot z) =$ $(x+y) (x+z)$
Idempotent	$x \cdot x = x$	$x + x = x$
Null	$x \cdot 0 = 0$	$x + 1 = 1$

2003

© S. Dandamudi

Chapter 2: Page 21

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Boolean Algebra (cont'd)

- Boolean identities (cont'd)

Name	AND version	OR version
Involution	$\overline{\bar{x}} = x$	---
Absorption	$x \cdot (x+y) = x$	$x + (x \cdot y) = x$
Associative	$x \cdot (y \cdot z) = (x \cdot y) \cdot z$	$x + (y + z) =$ $(x + y) + z$
de Morgan	$\overline{x \cdot y} = \bar{x} + \bar{y}$	$\overline{x + y} = \bar{x} \cdot \bar{y}$

2003

© S. Dandamudi

Chapter 2: Page 22

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Boolean Algebra (cont'd)

- Proving logical equivalence: Boolean algebra method
 - * To prove that two logical functions F1 and F2 are equivalent
 - » Start with one function and apply Boolean laws to derive the other function
 - » Needs intuition as to which laws should be applied and when
 - Practice helps
 - » Sometimes it may be convenient to reduce both functions to the same expression
 - * Example: $F1 = A B$ and $F3$ are equivalent

2003


© S. Dandamudi

Chapter 2: Page 23

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Logic Circuit Design Process

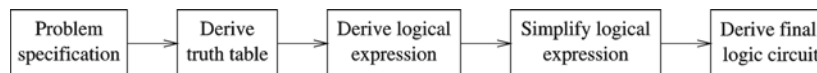- A simple logic design process involves
 - » Problem specification
 - » Truth table derivation
 - » Derivation of logical expression
 - » Simplification of logical expression
 - » Implementation



2003

© S. Dandamudi

Chapter 2: Page 24

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Deriving Logical Expressions

- Derivation of logical expressions from truth tables
 - * sum-of-products (SOP) form
 - * product-of-sums (POS) form
- SOP form
 - * Write an AND term for each input combination that produces a 1 output
 - » Write the variable if its value is 1; complement otherwise
 - * OR the AND terms to get the final expression
- POS form
 - * Dual of the SOP form

2003

© S. Dandamudi

Chapter 2: Page 25

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Deriving Logical Expressions (cont'd)

- | A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |
- 3-input majority function
 - SOP logical expression
 - Four product terms
 - * Because there are 4 rows with a 1 output
- $$F = \bar{A} B C + A \bar{B} C + A B \bar{C} + A B C$$
- Sigma notation
 - $\Sigma(3, 5, 6, 7)$

2003

© S. Dandamudi

Chapter 2: Page 26

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Deriving Logical Expressions (cont'd)

- 3-input majority function

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

- POS logical expression

- Four sum terms

* Because there are 4 rows with a 0 output

$$F = (A + B + C) (A + B + \bar{C}) (A + \bar{B} + C) (\bar{A} + B + C)$$

- Pi notation

$$\Pi (0, 1, 2, 4)$$

2003

© S. Dandamudi

Chapter 2: Page 27


To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Brute Force Method of Implementation

- 3-input even-parity function

- SOP implementation

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 

2003

© S. Dandamudi

Chapter 2: Page 28


To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Brute Force Method of Implementation

3-input even-parity function

• POS implementation

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 

2003

© S. Dandamudi

Chapter 2: Page 29

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Logical Expression Simplification

- Three basic methods
 - * Algebraic manipulation
 - » Use Boolean laws to simplify the expression
 - Difficult to use
 - Don't know if you have the simplified form
 - * Karnaugh map method
 - » Graphical method
 - » Easy to use
 - Can be used to simplify logical expressions with a few variables
 - * Quine-McCluskey method
 - » Tabular method
 - » Can be automated

2003

© S. Dandamudi

Chapter 2: Page 30

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Algebraic Manipulation

- Majority function example

$$\bar{A}BC + A\bar{B}C + AB\bar{C} + ABC =$$

$$\bar{A}BC + A\bar{B}C + AB\bar{C} + ABC + \bar{A}BC + A\bar{B}C$$

Added extra

- We can now simplify this expression as

$$BC + AC + AB$$

- A difficult method to use for complex expressions


2003

© S. Dandamudi

Chapter 2: Page 31

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Karnaugh Map Method

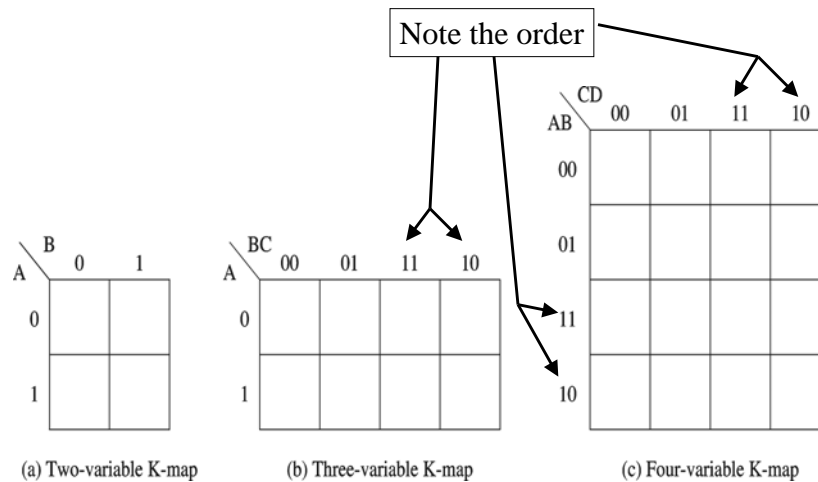

2003


© S. Dandamudi

Chapter 2: Page 32

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Karnaugh Map Method (cont'd)

Simplification examples

 

2003


© S. Dandamudi

Chapter 2: Page 33

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Karnaugh Map Method (cont'd)

First and last columns/rows are adjacent

 

2003


© S. Dandamudi

Chapter 2: Page 34

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Karnaugh Map Method (cont'd)

Minimal expression depends on groupings

 

2003


© S. Dandamudi

Chapter 2: Page 35

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Karnaugh Map Method (cont'd)

No redundant groupings

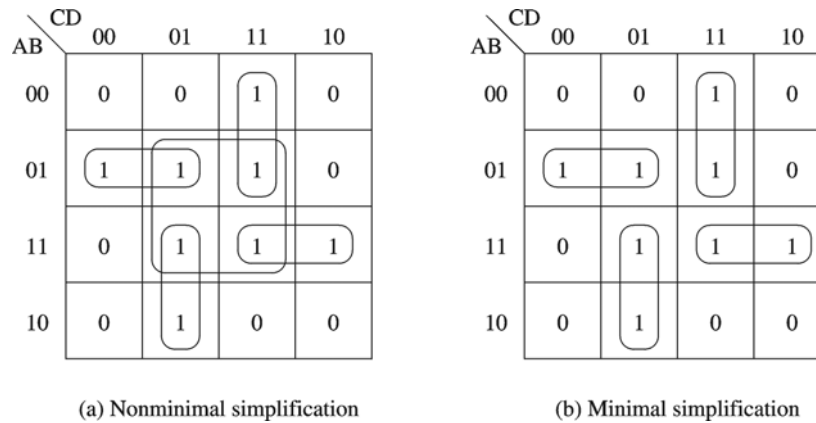

2003

© S. Dandamudi


Chapter 2: Page 36

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Karnaugh Map Method (cont'd)

 - **Example**

- * Seven-segment display
- * Need to select the right LEDs to display a digit



2003

© S. Dandamudi

Chapter 2: Page 37

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Karnaugh Map Method (cont'd)

Truth table for segment d

No	A	B	C	D	Seg.	No	A	B	C	D	Seg.
0	0	0	0	0	1	8	1	0	0	0	1
1	0	0	0	1	0	9	1	0	0	1	1
2	0	0	1	0	1	10	1	0	1	0	?
3	0	0	1	1	1	11	1	0	1	1	?
4	0	1	0	0	0	12	1	1	0	0	?
5	0	1	0	1	1	13	1	1	0	1	?
6	0	1	1	0	1	14	1	1	1	0	?
7	0	1	1	1	0	15	1	1	1	1	?

2003


© S. Dandamudi

Chapter 2: Page 38


To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Karnaugh Map Method (cont'd)

 Don't cares simplify the expression a lot



(a) Simplification with no don't cares

 

(b) Simplification with don't cares

2003


© S. Dandamudi

Chapter 2: Page 39


To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Karnaugh Map Method (cont'd)


Example 7-segment display driver chip

 

(a) Display designations

 

(b) Connection diagram

 

(c) Logic symbol

2003

© S. Dandamudi

Chapter 2: Page 40

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Quine-McCluskey Method

- Simplification involves two steps:
 - * Obtain a simplified expression
 - » Essentially uses the following rule
$$X Y + X \bar{Y} = X$$
 - » This expression need not be minimal
 - Next step eliminates any redundant terms
 - * Eliminate redundant terms from the simplified expression in the last step
 - » This step is needed even in the Karnaugh map method

2003



© S. Dandamudi

Chapter 2: Page 41

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Generalized Gates

  - Multiple input gates can be built using smaller gates
- Some gates like AND are easy to build
- Other gates like NAND are more involved



2003

© S. Dandamudi

Chapter 2: Page 42

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.


Generalized Gates (cont'd)

- Various ways to build higher-input gates


- * Series
- * Series-parallel

- Propagation delay depends on the implementation

 - * Series implementation
 - » 3-gate delay
- * Series-parallel implementation
 - » 2-gate delay



(a) Series implementation

 

(b) Series-parallel implementation

2003

© S. Dandamudi

Chapter 2: Page 43

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Multiple Outputs

Two-output function

A	B	C	F1	F2
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- F1 and F2 are familiar functions

- » F1 = Even-parity function

- » F2 = Majority function

- Another interpretation

- * Full adder

- » F1 = Sum

- » F2 = Carry

2003

© S. Dandamudi

Chapter 2: Page 44

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Implementation Using Other Gates

- Using NAND gates

- * Get an equivalent expression

$$A B + C D = \overline{\overline{A B + C D}}$$

- * Using de Morgan's law

$$A B + C D = \overline{\overline{A B} \cdot \overline{C D}}$$

- * Can be generalized

- » Majority function

$$A B + B C + A C = \overline{\overline{A B} \cdot \overline{B C} \cdot \overline{A C}}$$

2003


© S. Dandamudi

Chapter 2: Page 45

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Implementation Using Other Gates (cont'd)

- Majority function

 

2003


© S. Dandamudi

Chapter 2: Page 46

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Implementation Using Other Gates (cont'd)

Bubble Notation

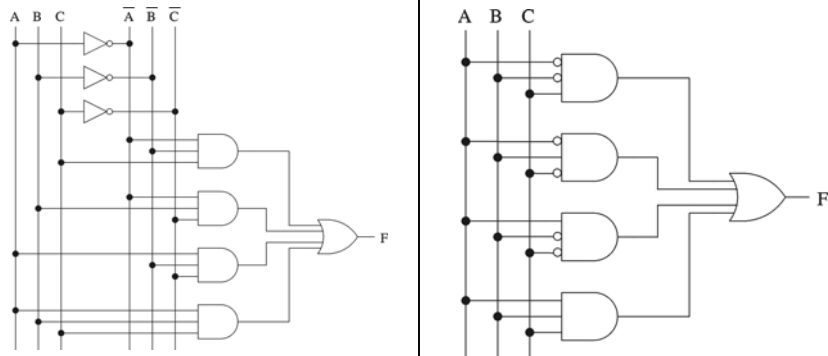

2003


© S. Dandamudi

Chapter 2: Page 47

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Implementation Using Other Gates (cont'd)

- Using XOR gates
 - * More complicated

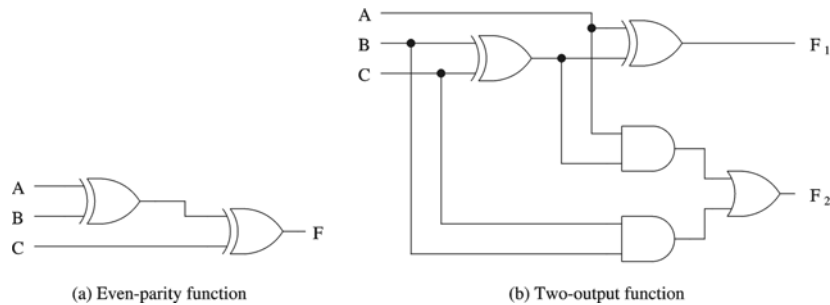

2003

© S. Dandamudi

Chapter 2: Page 48

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Summary

- Logic gates
 - » AND, OR, NOT
 - » NAND, NOR, XOR
- Logical functions can be represented using
 - » Truth table
 - » Logical expressions
 - » Graphical form
- Logical expressions
 - * Sum-of-products
 - * Product-of-sums

2003

© S. Dandamudi

Chapter 2: Page 49

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.

Summary (cont'd)

- Simplifying logical expressions
 - * Boolean algebra
 - * Karnaugh map
 - * Quine-McCluskey
- Implementations
 - * Using AND, OR, NOT
 - » Straightforward
 - * Using NAND
 - * Using XOR

Last slide

2003

© S. Dandamudi

Chapter 2: Page 50

To be used with S. Dandamudi, "Fundamentals of Computer Organization and Design," Springer, 2003.