



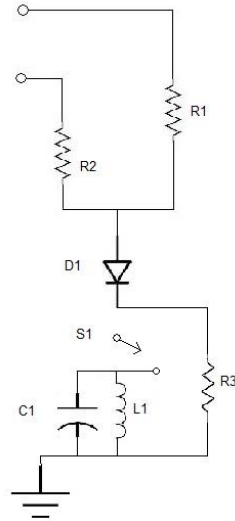
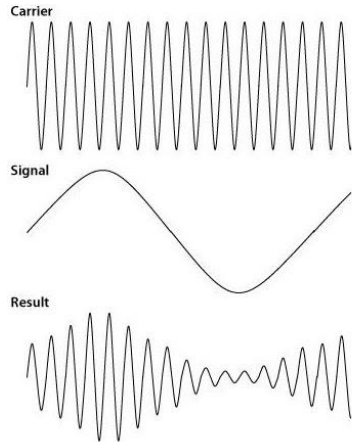


Diode Applications

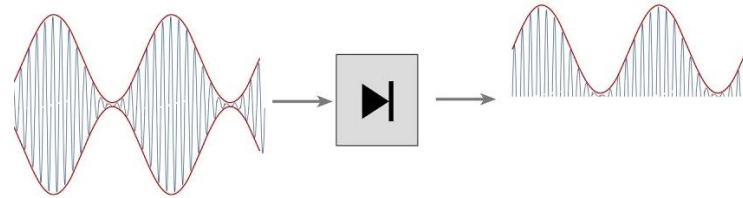


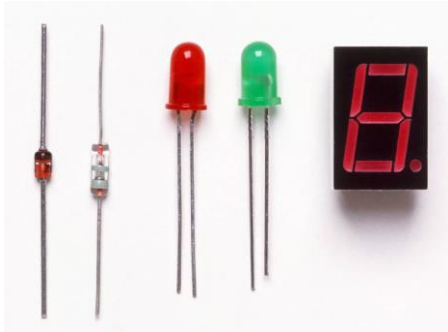

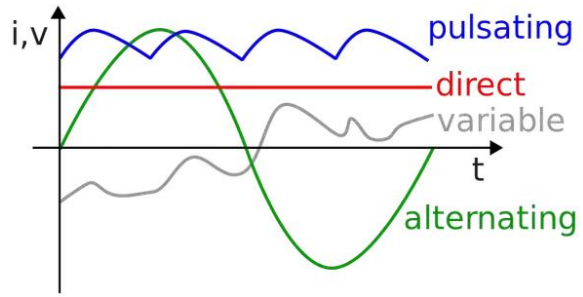


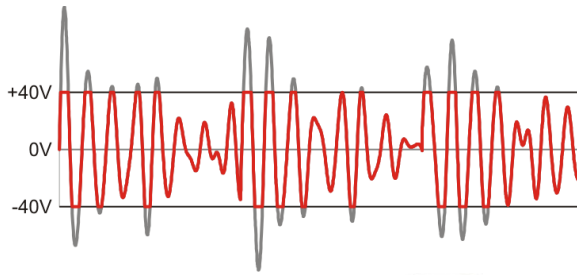


Original Signal

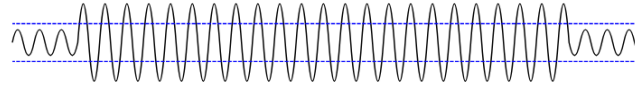

Soft Clipping

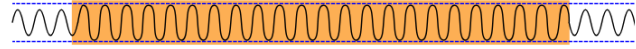

Hard Clipping

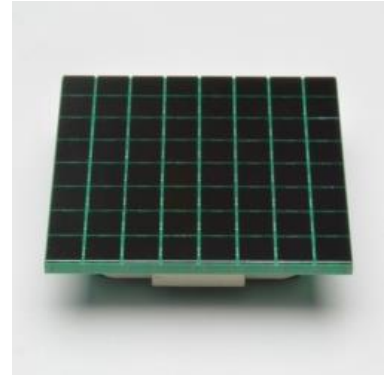

Diode Applications

- Rectifiers
- Signal modulators/demodulators
- Signal mixers
- Voltage regulators
- Light emitting diodes (LED's)
- Circuit Protection
- Wave shaping – limiters / clippers
- Clampers




Rectifiers






Rectifiers

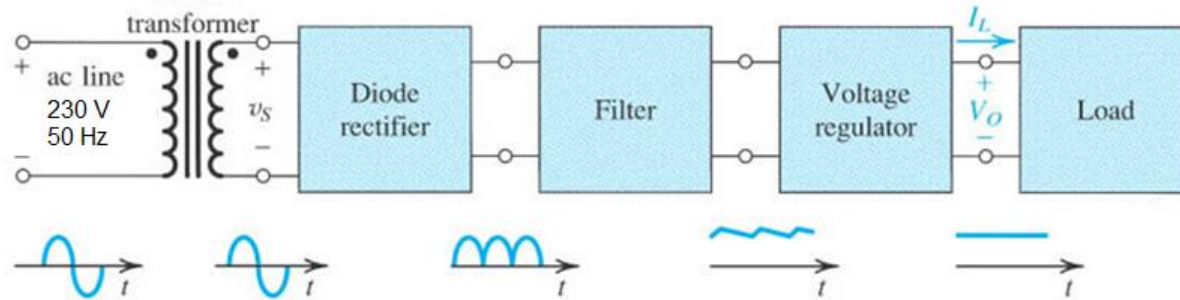
- The basic function of a Rectifier is to convert an AC voltage to a pulsating DC voltage.



Half-wave Rectifier

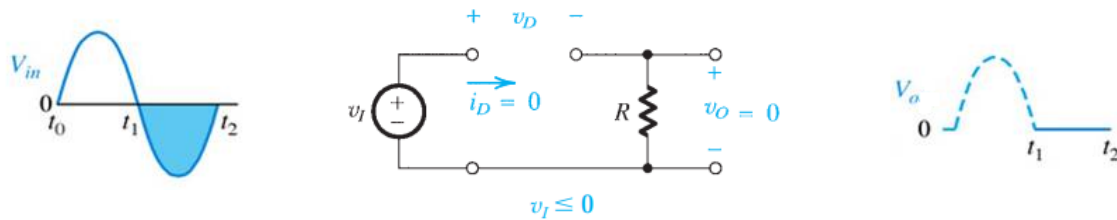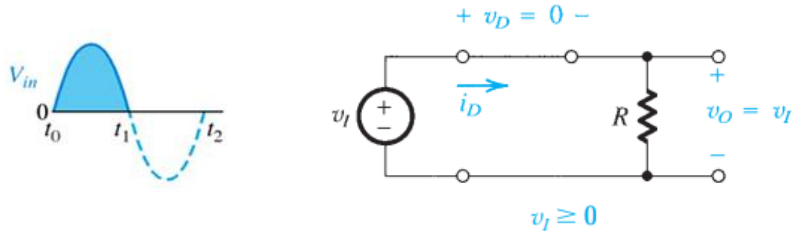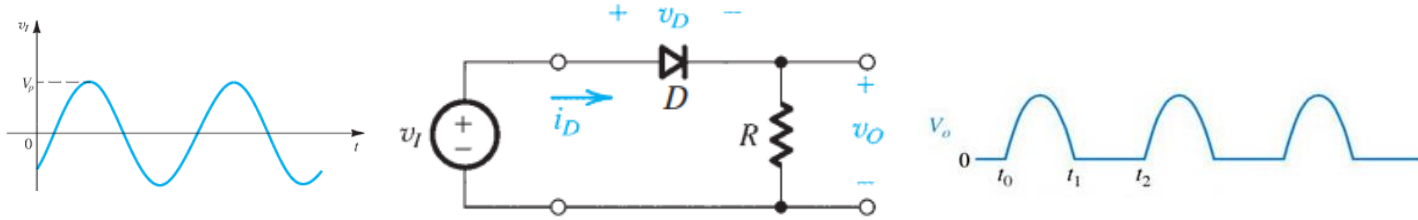


Half-wave Rectifier


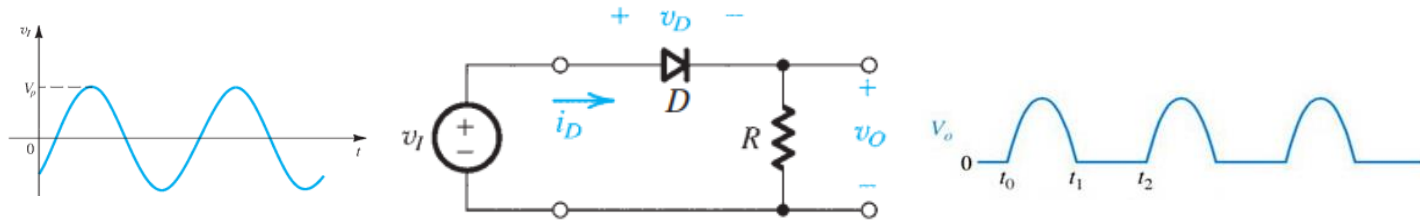


$$v_o = \begin{cases} v_i, & v_i > 0 \\ 0, & v_i < 0 \end{cases}$$

Transfer characteristic

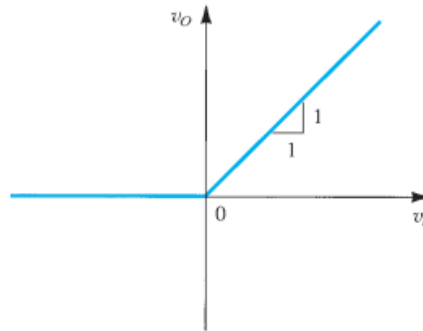


Half-wave Rectifier

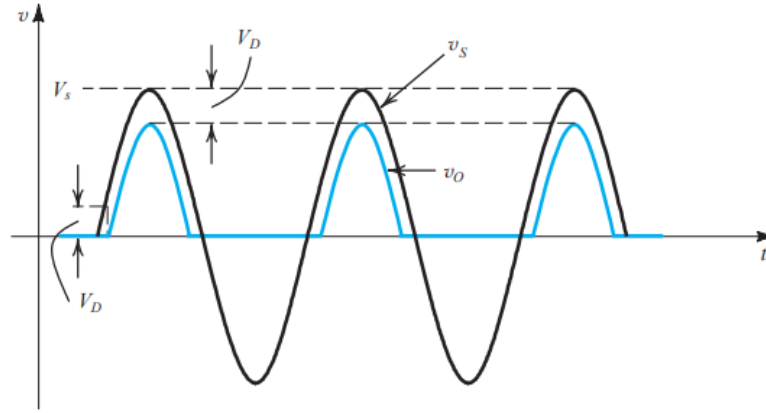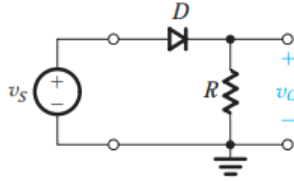


$$V_{\text{out}} = (V_{\text{in}} - 0.7) V$$



Transfer characteristic

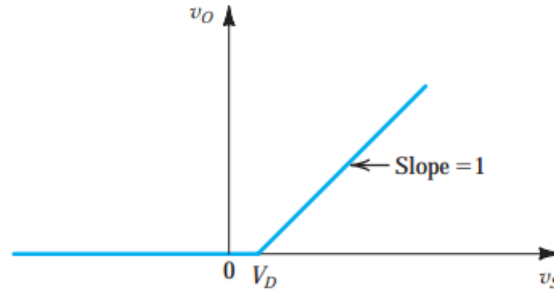

Half-wave Rectifier


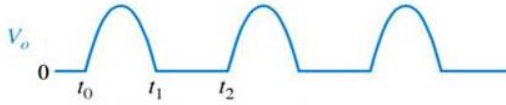


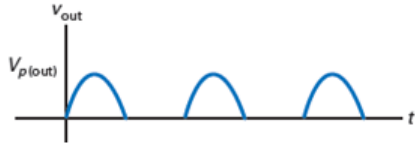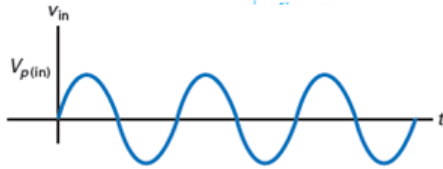- The average V_{DC} or $V_{AVG} = V_p/\pi$



The output frequency is the same as the input frequency.



$$f_{out} = f_{in}$$

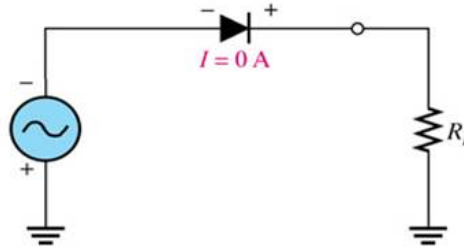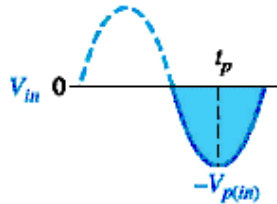

$$PIV = V_{peak}$$



Full-wave Rectifier

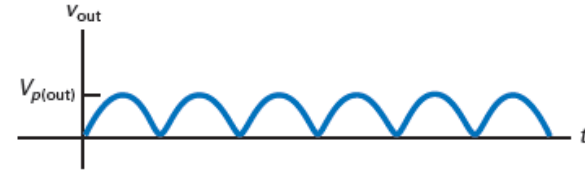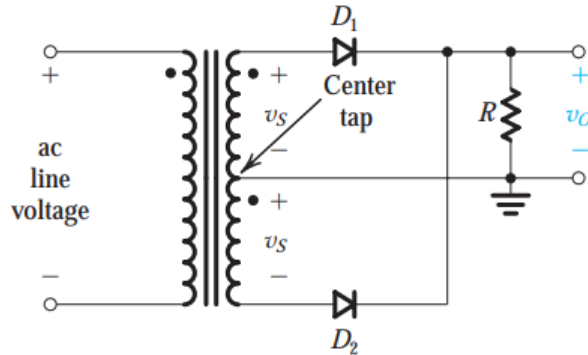- This method of rectification employs two diodes connected to a center-tapped transformer.



- Full-wave signal has twice as many positive cycles as the half-wave signal.


Full-wave Rectifier

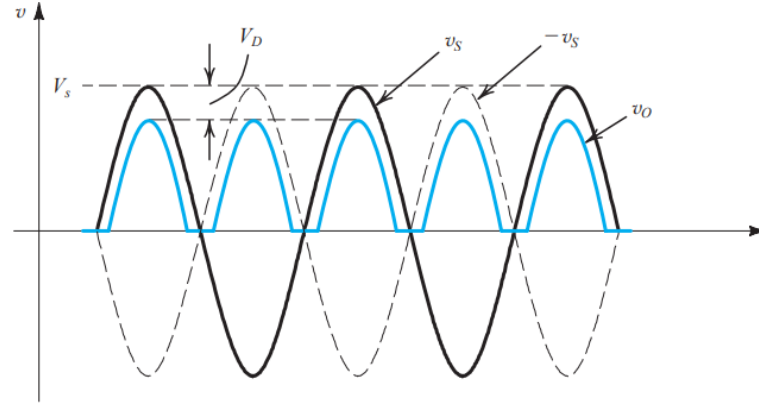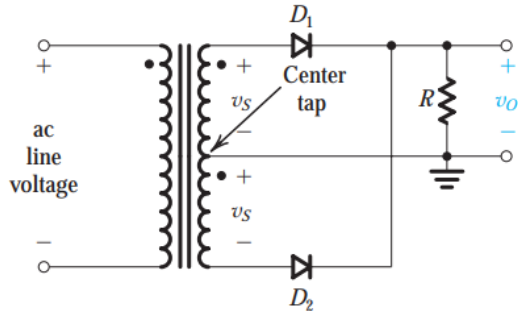


$$V_{\text{out}} = (V_{\text{in}} - 0.7) \text{ V}$$

- The dc or average value V_{DC} or $V_{\text{AVG}} = 2V_p/\pi$

Transfer characteristic


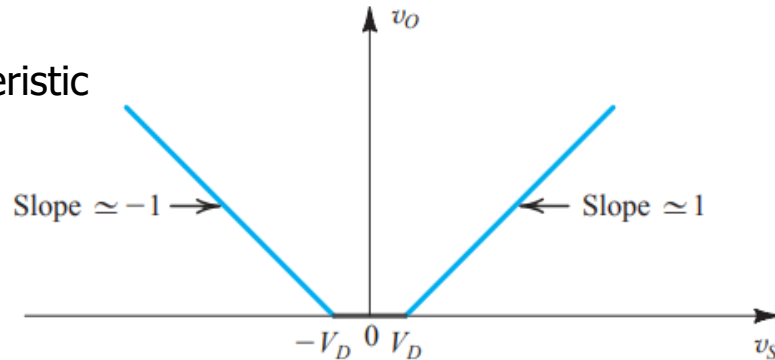


Full-wave Rectifier

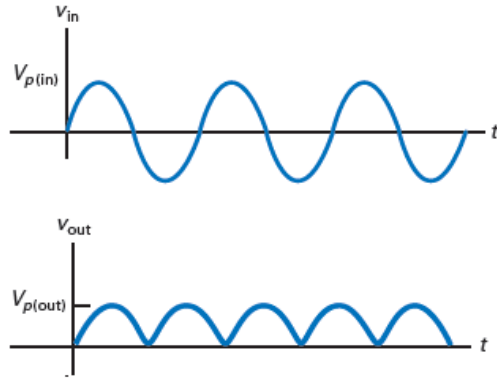

- A full-wave output has twice as many cycles as the sine-wave input.
- Frequency of the full-wave signal is double the input frequency





$$f_{out} = 2f_{in}$$

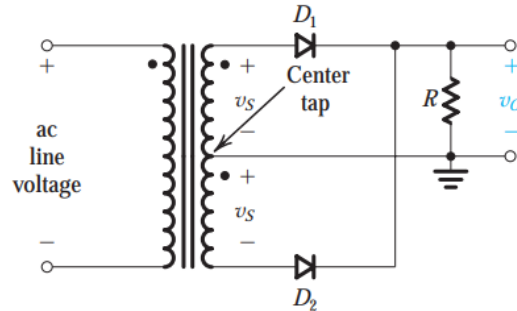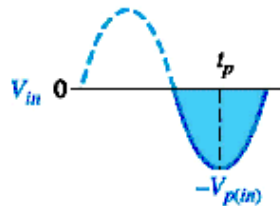


$$PIV = 2V_{peak}$$

Bridge Rectifier

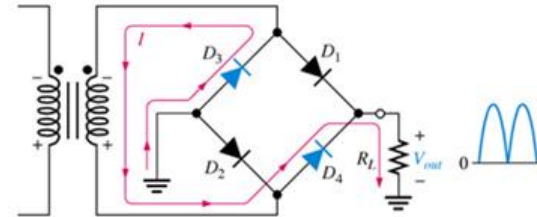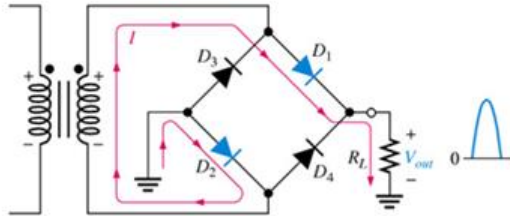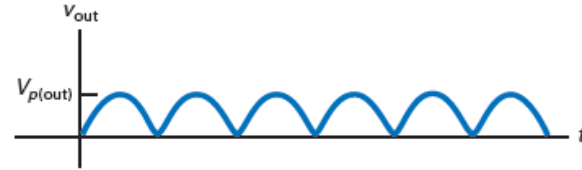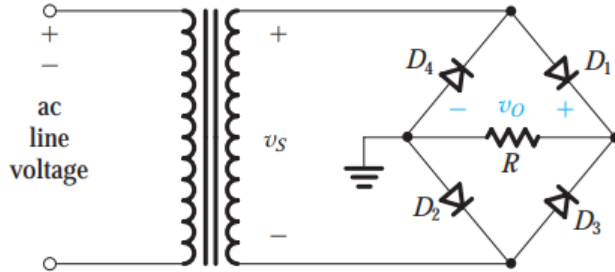
- Similar to full-wave rectifier as it produces a full-wave output voltage
- The entire secondary voltage can be used



Bridge Rectifier

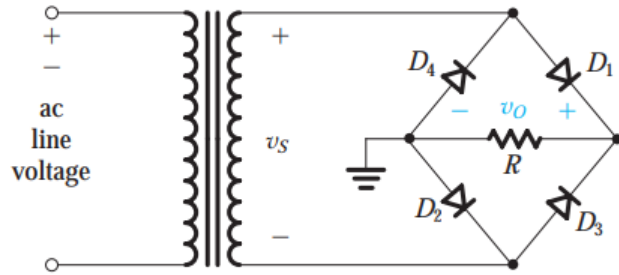

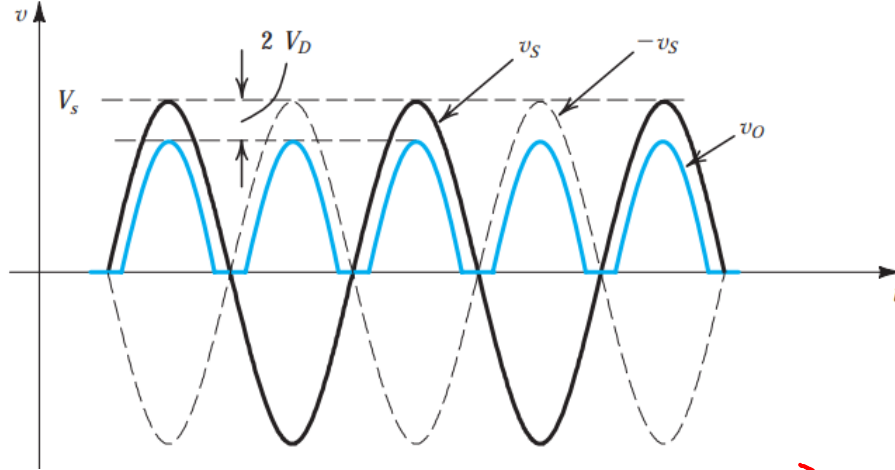
$$V_{\text{out}} = (V_{\text{in}} - 1.4) \text{ V}$$



The dc or average value V_{DC} or $V_{\text{AVG}} = 2V_p/\pi$




Bridge Rectifier

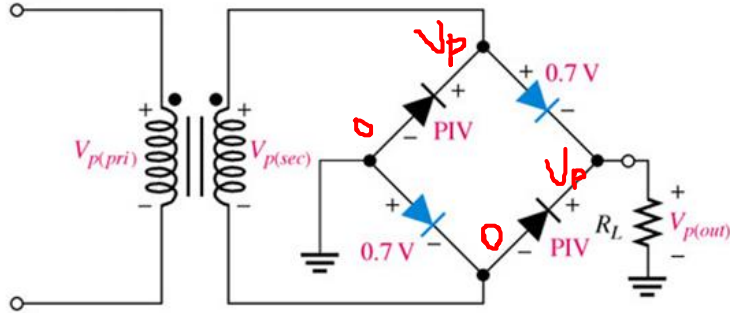

$$PIV = V_{peak}$$

Transfer characteristic


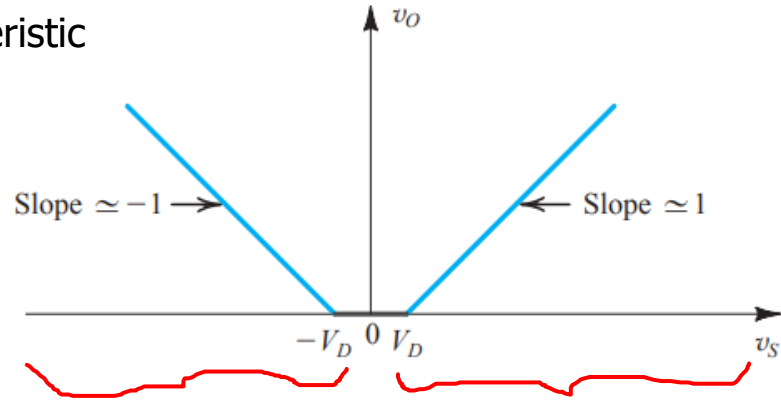


Clippers






Clippers

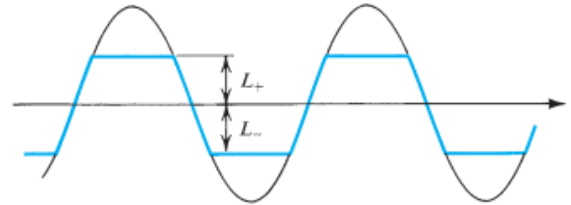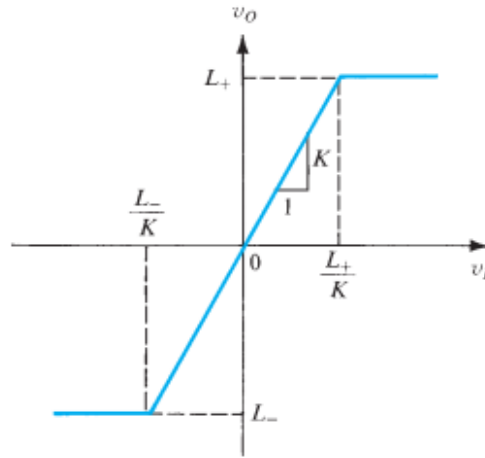- “clip” away a portion of an input signal without distorting the remaining part of the applied waveform




Clippers

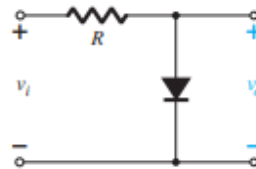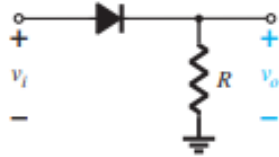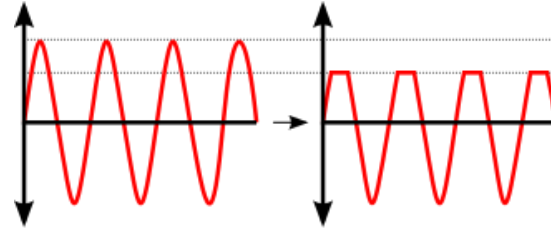- Depending on the orientation of the diode, **the positive or negative region** of the applied signal is “clipped” off
- Two categories:
 - Series clipper
 - Parallel clipper








Clippers




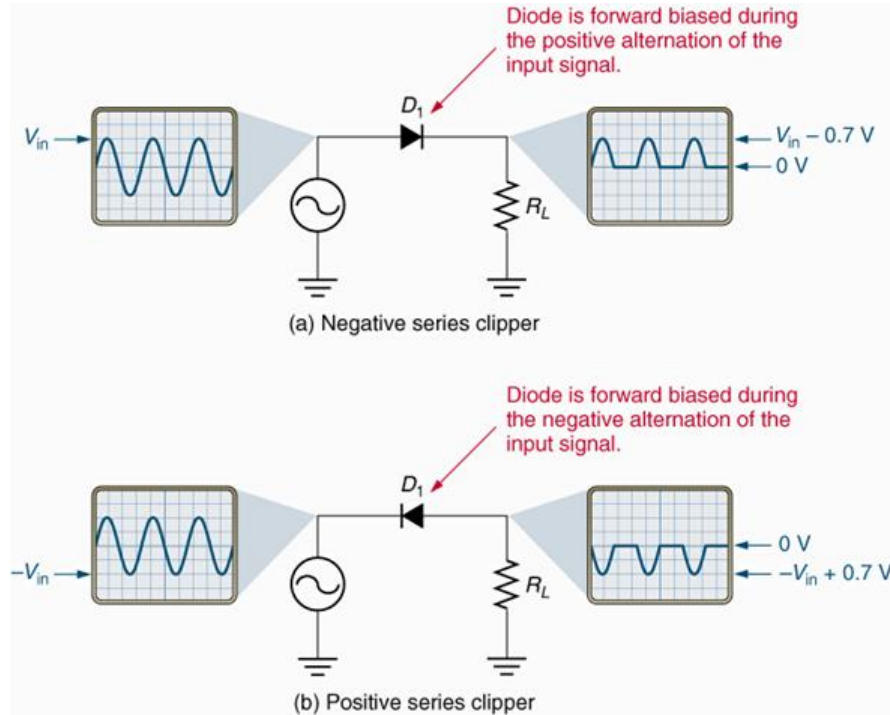
- The half-wave rectifier is an example of the simplest form of diode clipper



Clippers

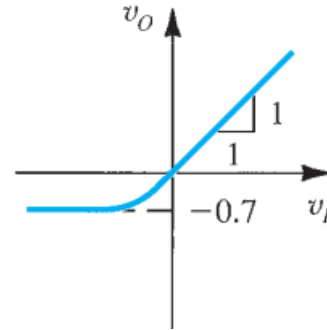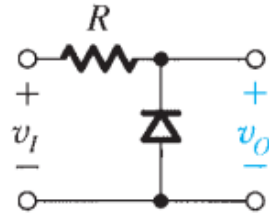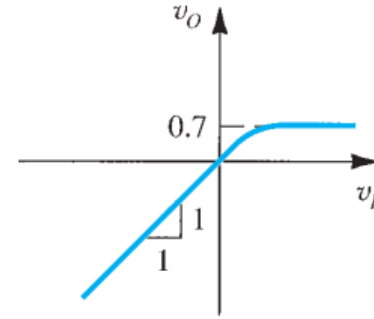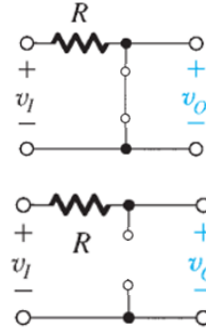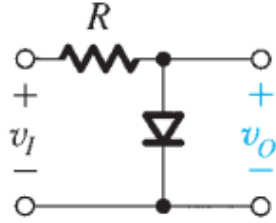


Clippers

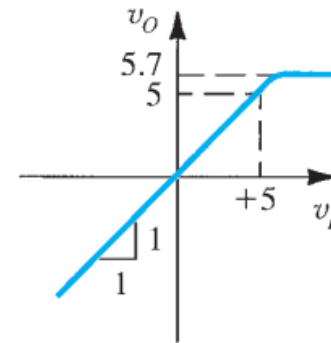
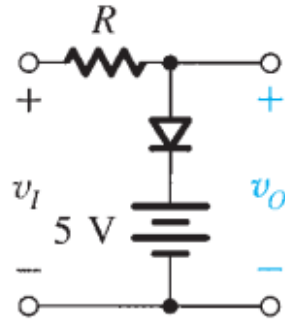
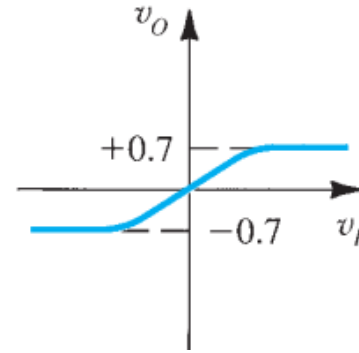
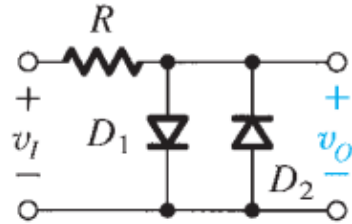


Clampers

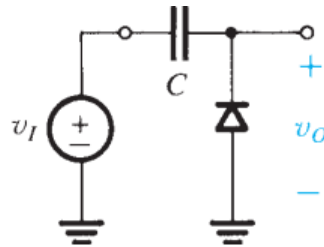- shifts a waveform to a different dc level without changing the shape of the applied signal.
- adds a dc level to an ac voltage - known as dc restorers
- capacitor is connected directly between input and output signals





Clampers

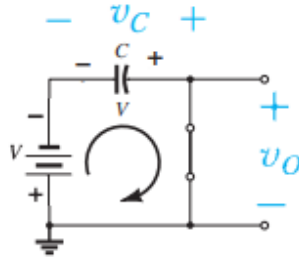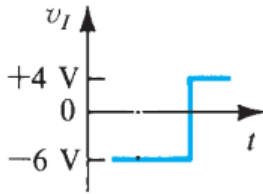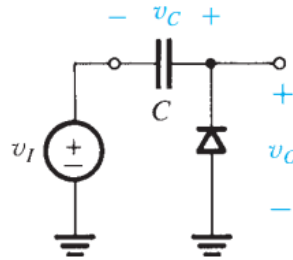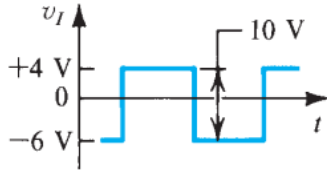

$$v_C = 6V$$



$$v_O = 0.7V$$

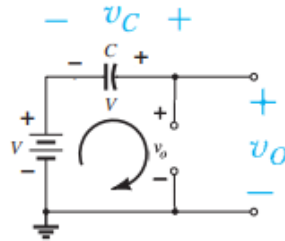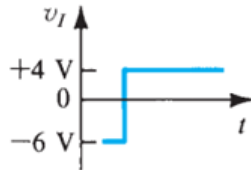

$$v_O = v_I + v_C$$

$$v_O = 4 + 6 = 10V$$



Clampers

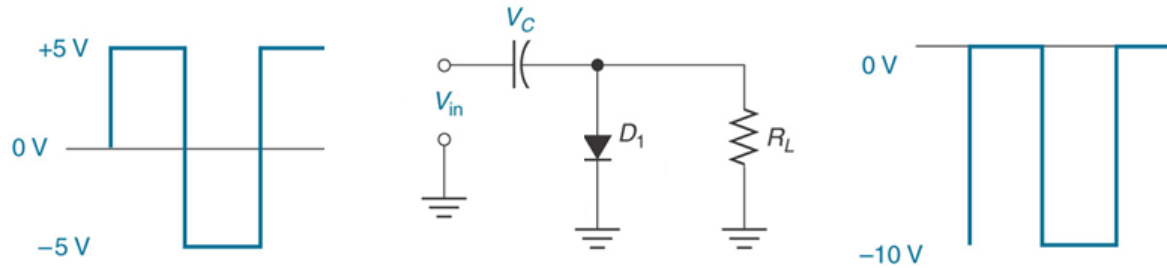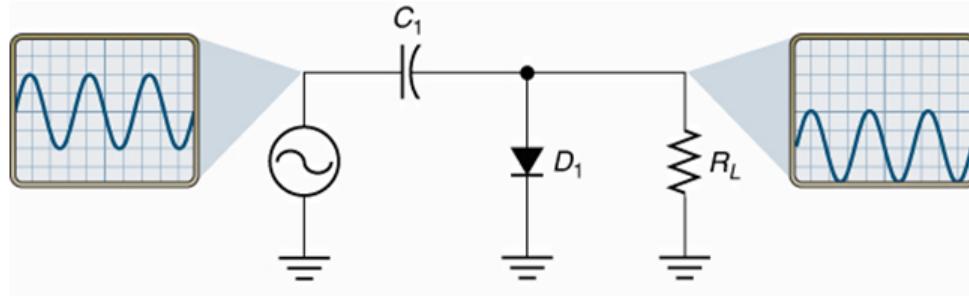

Clampers

Effect of load resistance

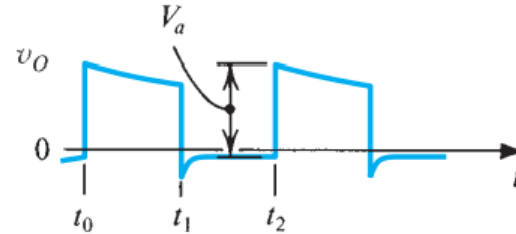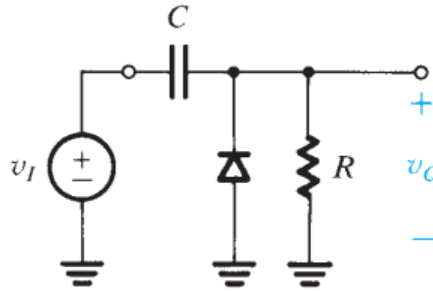- causes the capacitor to discharge and the output voltage to fall when diode is not conducting



- Large value of time constant RC is selected