

# Dynamic Logic Circuits

A. Marzuki


# Introduction

- Introduction
- Pass Transistor Circuits
- Voltage Bootstrapping
- Synchronous Dynamic Circuit Techniques
- High-Performance Dynamic CMOS Circuits

# Introduction

- Dynamic logic is temporary (**transient**) in that output levels will remain valid only for a certain period of time
  - Static logic retains its output level as long as power is applied
- Dynamic logic is normally done with charging and selectively discharging capacitance (i.e. capacitive circuit nodes)
  - **Precharge** clock to charge the capacitance
  - **Evaluate** clock to discharge the capacitance depending on condition of logic inputs
- Advantages over static logic:
  - Avoids duplicating logic twice as both N-tree and P-tree, as in standard CMOS
  - Typically can be used in very high performance applications
  - Very simple sequential memory circuits; amenable to synchronous logic
  - High density achievable
  - Consumes less power (in some cases)
- Disadvantages compared to static logic:
  - Problems with clock synchronization and timing
  - Design is more difficult


# Example

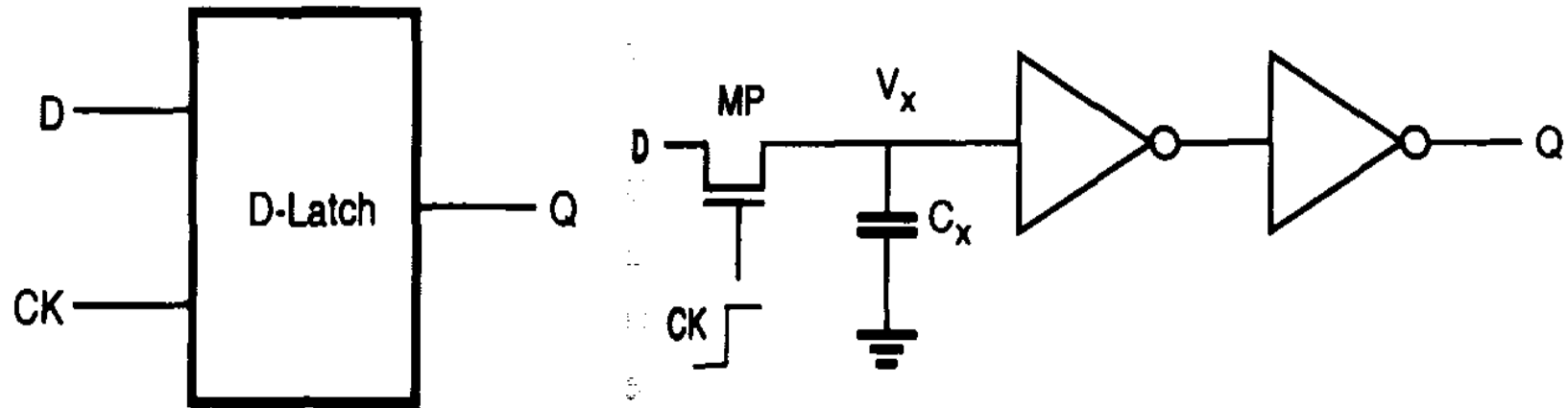

CK = 1  $\rightarrow$  MP on  
capacitor charge up or down  
Q = D

CK = 0  $\rightarrow$  MP off, capacitor isolated from D  
No current path, Q = previous charge

# Example

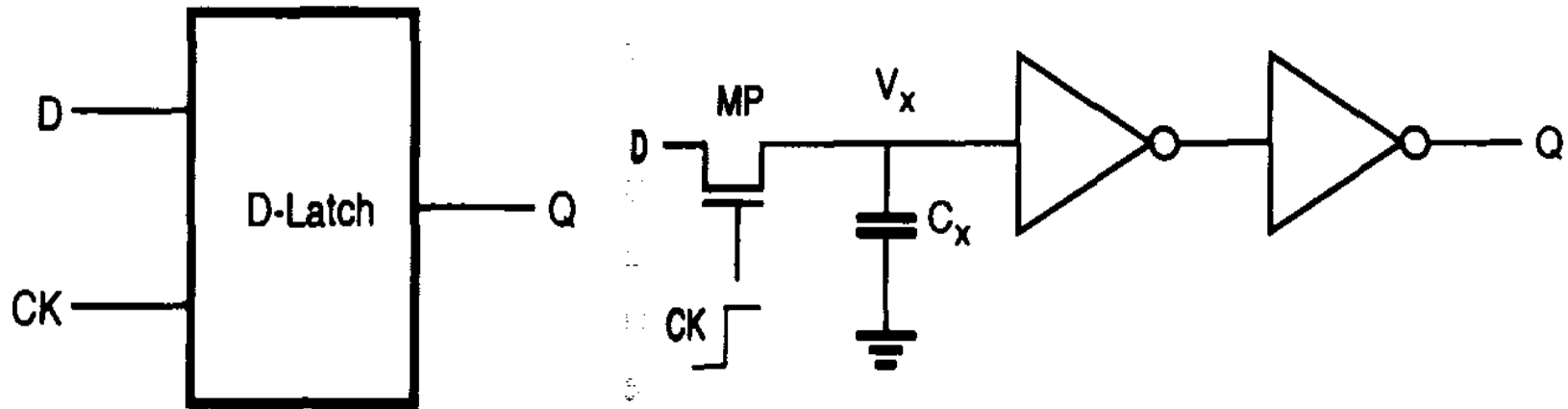

x soft node

Eg:  $V_{DD} = V_{OH} = 5 \text{ V}$ ,  $V_{OL} = 0 \text{ V}$ ,  $V_{IL} = 2.1 \text{ V}$ ,  $V_{IH} = 2.9 \text{ V}$


$CK = 1 \rightarrow V_{in} = 5 \text{ V}$

$C_x$  charge up

$V_x = 4.2 \text{ V}$  (poor conductor)  $\rightarrow V_{out} = 0 \text{ V}$  (1<sup>st</sup> inverter)




$V_{out} = 5 \text{ V}$  (2<sup>nd</sup> inverter)

# Example

 

transistor turns off, logic high is preserved by  $C_x$   
 $V_x$  drops from 4.2 V  $\rightarrow$  to whatever (charge leakage)  
 $V_Q = 5$  V requires  $V_x > 2.9$  V  
 $C_x$  must be restored

   
# Basic Principle of Pass Transistor Circuits (PTC)



- The basic **dynamic logic gate concept** is shown at left (top)
  - the pass transistor MP is an NMOS device, but could also be implemented with a transmission gate TG
  - $C_x$  represents the equivalent capacitance of the input gate of the second NMOS device (part of an inverter or logic gate) as well as the PN junction capacitance of MP's drain (source)
  - When clock CK goes high, MP is turned on and allows the input voltage  $V_{in}$  to be placed on capacitor  $C_x$ 
    - $V_{in}$  could be a high ("1") or a low ("0") voltage
  - When CK goes low, MP is turned off, trapping the charge on  $C_x$
- Operation for a 1 or a 0:
  - If  $V_{in}$  is high (say  $V_{OH}$ ), then MP will allow current to flow into  $C_x$ , charging it up to  $V_{dd} - V_{tn}$  (assume CK up level is  $V_{dd}$ )
  - If  $V_{in}$  is low (say GND), then MP will allow current to flow out of  $C_x$ , discharging it to GND
- Due to leakage from the drain (source) of MP,  $C_x$  can only retain the charge  $Q$  for a given period of time (called soft node)
  - If MP is NMOS,  $C_x$  will discharge to GND
  - If MP is PMOS,  $C_x$  will discharge to VDD
  - If MP is a TG,  $C_x$  could discharge in either direction
 
# Transfer “1” Event

- Charging event with NMOS operating in source-follower mode:



- MP will be saturated during transfer “1” transient
- Max voltage attainable at  $V_x$  will be  $V_{DD} - V_{tn}$ , assuming that the CK pulse height is  $V_{DD}$
- Solve for increasing voltage  $V_x$  versus time:

$$C_x (dV_x/dt) = \frac{1}{2} k_n (V_{DD} - V_x - V_{tn})^2$$

- Solution:

$$t = (2C_x / k_n) \left[ \frac{1}{(V_{DD} - V_x - V_{tn})} - \frac{1}{(V_{DD} - V_{tn})} \right]$$

or, solving for  $V_x(t)$


$$V_x(t) = (V_{DD} - V_{tn}) \left[ 1 - \frac{1}{\left\{ 1 + (V_{DD} - V_{tn}) \left( \frac{k_n}{2C_x} \right) t \right\}} \right]$$

As  $t \rightarrow \text{infinity}$ ,  $V_x(t) \rightarrow V_{DD} - V_{tn}$

Solve for time needed to reach 90%  $(V_{DD} - V_{tn})$ :

- Set  $V_x(t) = 0.9 (V_{DD} - V_{tn}) \rightarrow t_{90\%} = 18 C_x / k_n (V_{DD} - V_{tn})$


- i.e. 18 time constants

 


 
# Transfer “0” Event

- On a transfer “0” event, the NMOS transfer device is in its common source configuration, i.e. the source is at GND and the drain is discharging  $C_x$



- MP is operating in the linear mode for the entire transient since the starting value is  $V_{dd} - V_{tn}$
- Solve for decreasing  $V_x$  with time:

$$C_x (dV_x/dt) = -\beta_n V_x (V_{dd} - V_{tn} - \frac{1}{2} V_x)^2$$


- Solution:

$$t = C_x / (\beta_n (V_{dd} - V_{tn})) \ln\{ (2(V_{dd} - V_{tn}) - V_x) / V_x \}$$


- Solve for time needed for  $V_x$  to fall to 10% ( $V_{dd} - V_{tn}$ ):
  - Set  $V_x(t) = 0.1 (V_{dd} - V_{tn}) \rightarrow t_{10\%} = 2.9 C_x / \beta_n (V_{dd} - V_{tn})$ 
    - i.e. 2.9 time constants
- Therefore, the time to discharge  $C_x$  with an NMOS MP pass transistor is much shorter than the time to charge  $C_x$  due to the source-follower operation during charging.
 
# Leakage and Subthreshold Current in Dynamic Pass Gate



- Charge can leak off the storage capacitor  $C_x$  mainly from two sources:
  - PN junction leakage of the NMOS drain (source) junction
  - Subthreshold current ( $I_{OFF}$ ) through MP when its gate is down at zero volts
- One can solve for the maximum amount of time  $\Delta t$  that charge can be retained on  $C_x$  using the differential equation  $C \, dv/dt = I$ , where
  - $I$  is the total of the reverse PN junction leakage and the  $I_{OFF}$  current
  - $C$  is the total load capacitance due to gate, junction, wire, and poly capacitance
  - the maximum allowable  $\Delta V$  in order to preserve the logic “1” level is known
    - Typically  $\Delta V \sim V_{dd} - V_{tn} - \frac{1}{2} V_{dd} = \frac{1}{2} V_{dd} - V_{tn}$
- The minimum frequency of operation can be found from  $f \sim 1/(2 \Delta t)$



# Dynamic Bootstrapping Technique

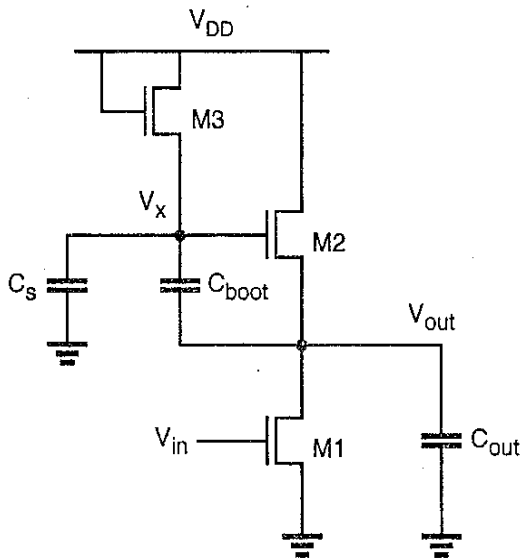

- **Bootstrapping** is a technique that is sometimes used to charge up a transistor gate to a voltage higher than Vdd when that transistor has to drive a line to the full Vdd
- At left is a NMOS bootstrap driver often used in memory circuits to drive a highly capacitive word line
- Operation:
  - When  $V_{in} = \text{high}$ , M1 is on holding  $V_{out}$  low while M3 charges  $V_x$  to  $V_{DD} - V_t$ . Thus,  $C_{boot}$  is charged to  $V_{DD} - V_t - V_{OL}$
  - When  $V_{in}$  goes low, turning M1 off, M2 starts charging  $V_{out}$  high. If  $C_{boot} > C_s$ , most of the increase in  $V_{out}$  is “booted” to  $V_x$ , raising the voltage at  $V_x$  to well above  $V_{DD}$ .

 
 


- It is desired to obtain  $V_x > V_{DD} + V_t$  in order to keep M2 linear, to allow  $V_{out}$  to be charged fully to  $V_{DD}$ .
- Parasitic capacitor  $C_s$  bleeds some of the charge off  $C_{boot}$ , limiting the max voltage on  $V_x$  (charging coupling eq.)
- At left  $C_{boot}$  is implemented with a transistor having source tied to drain.


# Dynamic Latches with a Single Clock

- Dynamic latches eliminate dc feedback leg by storing data on gate capacitance of inverter (or logic gate) and switching charge in or out with a transmission gate
  - Minimum frequency of operation is typically of the order of 50-100 KHz so as not to lose data due to junction or gate leakage from the node
  - Can be clocked at high frequency since very little delay in latch elements
  
# Dynamic Registers with Two Phase Clocks



(a)

 

(b)

- Dynamic register with pass gates and two phase clocking is shown

- Clocks phi1 and phi2 are non-overlapping
- When phi1 is high & phi2 is zero,

- 1<sup>st</sup> pass gate is closed and D data charges gate capacitance C1 of 1<sup>st</sup> inverter
- 2<sup>nd</sup> pass gate is open trapping prior charge on C2

- When phi1 is low and phi2 is high,

- 1<sup>st</sup> pass gate opens trapping D data on C1
- 2<sup>nd</sup> pass gate closes allowing C2 to charge with inverted D data

- If clock skew or sloppy rise/fall time clock buffers cause overlap of phi1 and phi2 clocks,

- Both pass gates can be closed at the same time causing mixing of old and new data and therefore loss of data integrity!



# Dynamic Shift Registers with Enhancement Load

- At left (top) is a dynamic shift register implemented with a technique named **“ratioed dynamic logic”**.



- $\phi_1$  and  $\phi_2$  are non-overlapping clocks
- When  $\phi_1$  is high,  $C_{in1}$  charges to  $V_{DD} - V_t$  if  $V_{in}$  is high or to GND if  $V_{in}$  is low
- When  $\phi_1$  drops and  $\phi_2$  comes up, the input data is trapped on  $C_{in1}$  and yields a logic output on  $C_{out1}$  which is transferred to  $C_{in2}$
- When  $\phi_2$  drops and  $\phi_1$  comes up again, the logic output on  $C_{out1}$  is trapped on  $C_{in2}$ , which yields a logic output on  $C_{out2}$ , which is transferred to  $C_{in3}$ , etc.
- To avoid losing too much voltage on the logic high level,  $C_{out_n} \gg C_{in_{n+1}}$  is desired
- Each inverter must be ratioed to achieve a desired  $V_{OL}$  (e.g. when  $\phi_2$  is high on 1<sup>st</sup> inv)

- The bottom left dynamic shift register is a **“ratioless dynamic logic”** circuit

 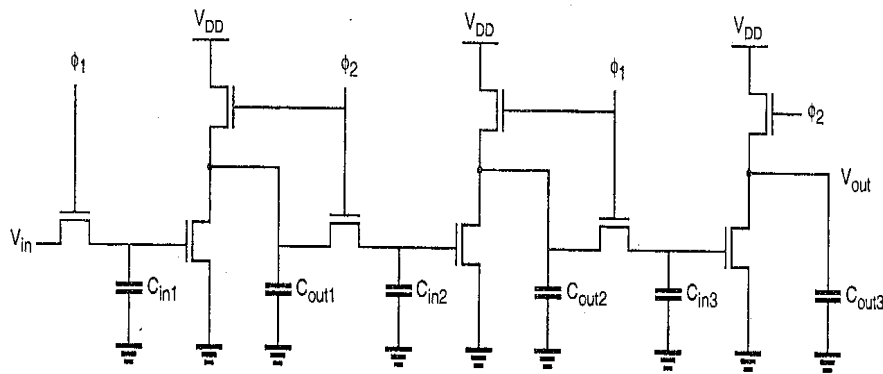- When  $\phi_2$  is high transferring data to  $q_4$  stage 2,  $\phi_1$  has already turned off the stage 1 load transistor, allowing a  $V_{OL} =$





# Dynamic CMOS Logic Gate

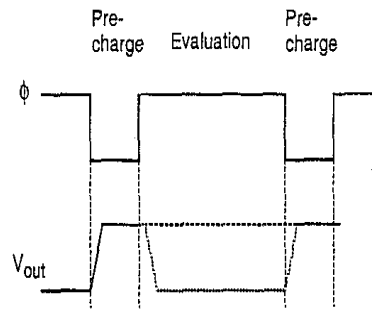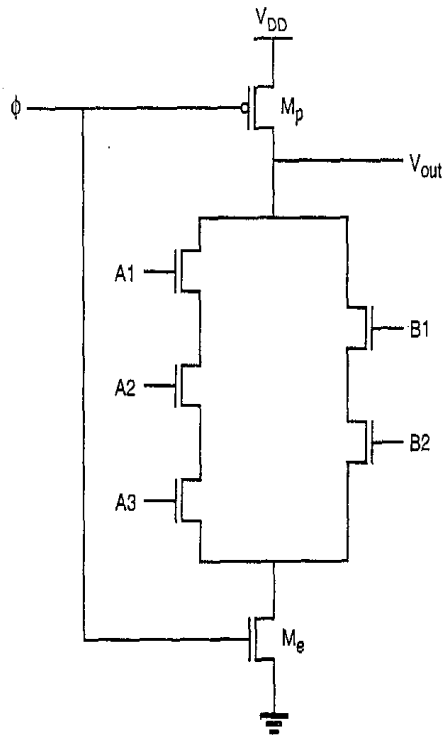

- In dynamic CMOS logic a single clock  $\phi$  can be used to accomplish both the pre-charge and evaluation operations
  - When  $\phi$  is low, PMOS pre-charge transistor  $M_p$  charges  $V_{out}$  to  $V_{DD}$ , since it remains in its linear region during final pre-charge
    - During this time the logic inputs  $A1 \dots B2$  are active; however, since  $M_e$  is off, no charge will be lost from  $V_{out}$
  - When  $\phi$  goes high again,  $M_p$  is turned off and the NMOS evaluate transistor  $M_e$  is turned on, allowing for  $V_{out}$  to be selectively discharged to GND depending on the logic inputs
    - If  $A1 \dots B2$  inputs are such that a conducting path exists between  $V_{out}$  and  $M_e$ , then  $V_{out}$  will discharge to 0
    - Otherwise,  $V_{out}$  remains at  $V_{DD}$

 
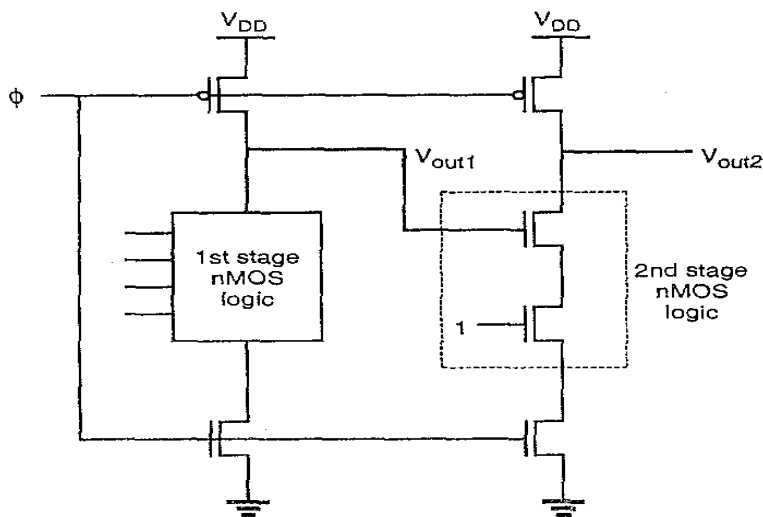
# Cascading Problem in Dynamic CMOS Logic

- If several stages of the previous CMOS dynamic logic circuit are cascaded together using the same clock  $\phi$ , a problem in evaluation involving a built-in “race condition” will exist
- Consider the two stage dynamic logic circuit below:
  - During **pre-charge**, both  $V_{out1}$  and  $V_{out2}$  are pre-charged to  $V_{DD}$
  - When  $\phi$  goes high to begin **evaluate**, all inputs at stage 1 require some finite time to resolve, but during this time charge may erroneously be discharged from  $V_{out2}$ 
    - e.g. assume that eventually the 1<sup>st</sup> stage NMOS logic tree conducts and fully discharges  $V_{out1}$ , but since all the inputs to the N-tree all not immediately resolved, it takes some time for the N-tree to finally discharge  $V_{out1}$  to GND.
    - If, during this time delay, the 2<sup>nd</sup> stage has the input condition shown with bottom NMOS transistor gate at a logic 1, then  $V_{out2}$  will start to fall and discharge its load capacitance until  $V_{out1}$  finally evaluates and turns off the top series NMOS transistor in stage 2
  - The result is an error in the output of the 2<sup>nd</sup> stage  $V_{out2}$





  
# Cascaded Dynamic CMOS Logic Gates: Evaluate Problem



- With simple cascading of dynamic CMOS logic stages, a problem arises in the evaluate cycle:
  - The pre-charged high voltage on Node N2 in stage 2 may be inadvertently (partially) discharged by logic inputs to stage 2 which have not yet reached final correct (low) values from the stage 1 evaluation operation.
  - Can not simply cascade dynamic CMOS logic gates without preventing unwanted bleeding of charge from pre-charged nodes
- Possible Solutions:
  - two phase clocks
  - use of inverters to create Domino Logic
  - NP Domino Logic
  - Zipper/NORA logic


# CMOS Domino Logic

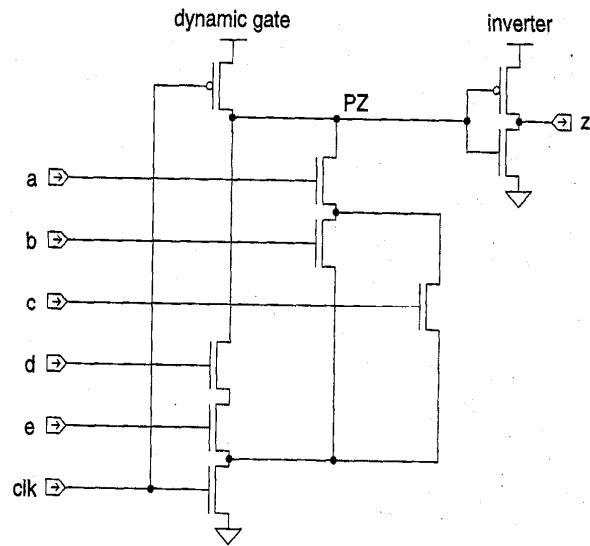

- The problem with faulty discharge of precharged nodes in CMOS dynamic logic circuits can be solved by placing an inverter in series with the output of each gate
  - All inputs to N logic blocks (which are derived from inverted outputs of previous stages) therefore will be at zero volts during precharge and will remain at zero until the evaluation stage has logic inputs to discharge the precharged node PZ.
  - This circuit approach avoids the race problem of “vanilla” cascaded dynamic CMOS
  - However, all circuits only provide non-inverted outputs

 
# Mixing Domino CMOS Logic with Static CMOS Logic

- We can add an **even** number of static CMOS inverting logic gates after a Domino logic stage prior to the next Domino logic stage
  - Even number of inverting stages guarantees that inputs to the second Domino logic stage experience only 0-to-1 transitions
- In the cascaded **Domino** logic structure, the evaluation of each stage ripples through the cascaded stages similar to a chain of Dominos (from which it takes the name)
  - The evaluate cycle must be of sufficient duration to allow all cascaded logic stages (between latches) to complete their evaluation process within the **clock evaluation interval**



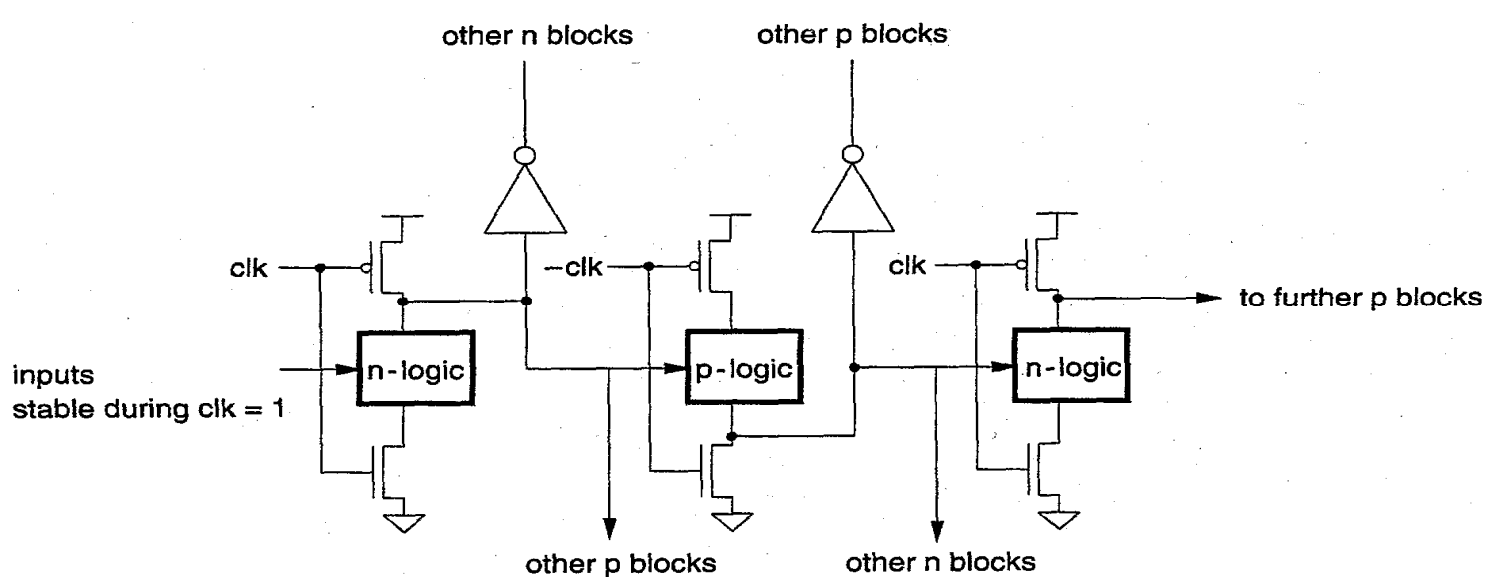
# NP Domino Logic (NORA Logic)

- An elegant solution to the dynamic CMOS logic “erroneous evaluation” problem is to use NP Domino Logic (also called NORA logic) as shown below.
  - Alternate stages of N logic with stages of P logic
    - N logic stages use true clock, normal precharge and evaluation phases, with N logic tree in the pull down leg. P logic stages use a complement clock, with P logic stage tied above the output node.
    - During precharge clk is low (-clk is high) and the P-logic output precharges to ground while N-logic outputs precharge to Vdd.
    - During evaluate clk is high (-clk is low) and both type stages go through evaluation; N-logic tree logically evaluates to ground while P-logic tree logically evaluates to Vdd.
- Inverter outputs can be used to feed other N-blocks from N-blocks, or to feed other P-blocks from P-blocks.





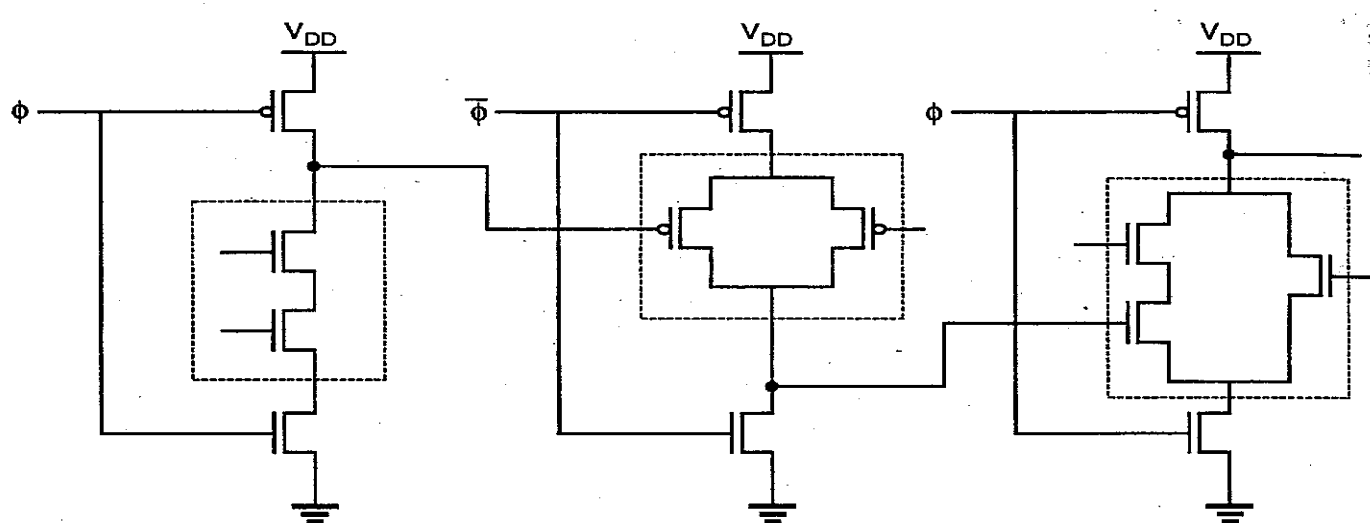
# NORA CMOS Logic Circuit Example

- An example of NP or NORA (No Race) logic is shown below:
- During  $\phi$  low ( $\phi'$  high), each stage pre-charges
  - N logic stages pre-charge to  $V_{DD}$ ; P logic stages pre-charge to GND
- When  $\phi$  goes high ( $\phi'$  low), each stage enters the evaluation phase
  - N logic evaluates to GND; P logic stages evaluate to  $V_{DD}$
  - All NMOS and PMOS stages evaluate one after another in succession, as in Domino logic
- Logic below:
  - Stage 1 is  $X = (A \cdot B)'$
  - Stage 2 is  $G = X' + Y'$
  - Stage 3 is  $Z = (F \cdot G + H)'$




# Pipelined NORA CMOS Circuit Operation

 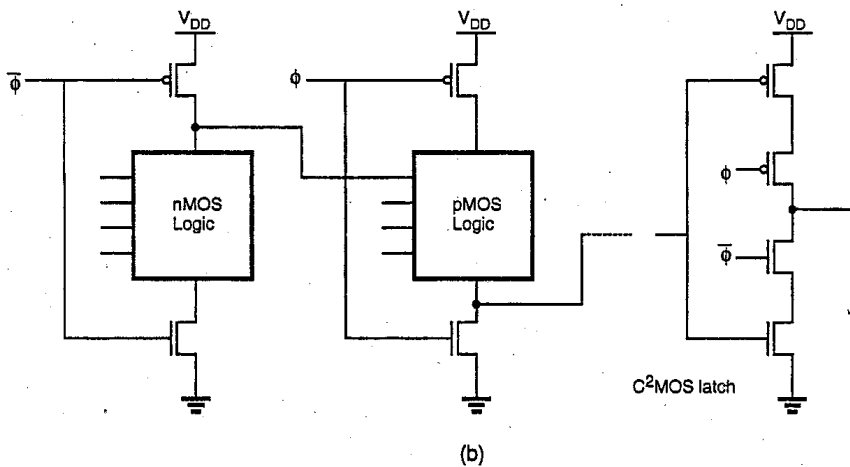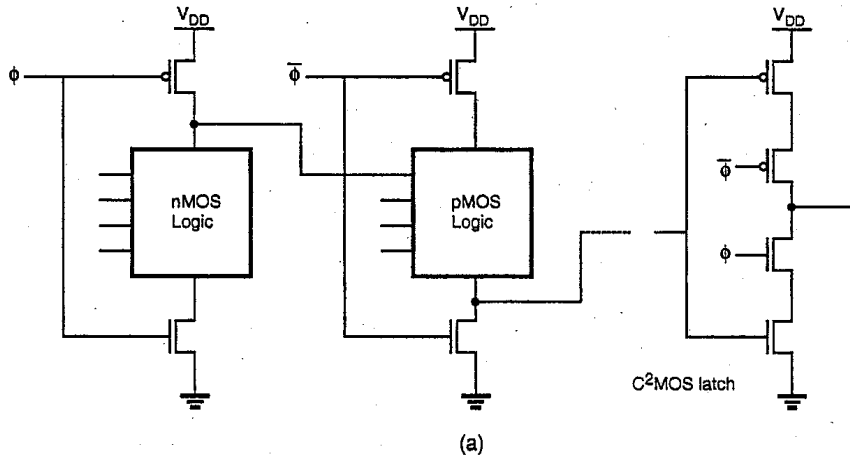


- With pipelined NORA CMOS logic design
  - one can alternate N and P stages between C<sup>2</sup>MOS latches where  $\phi$  high is used for evaluation as shown in (a)
  - Or, one can alternate N and P stages similarly between C<sup>2</sup>MOS latches with  $\phi'$  high used for evaluation as in (b)
  - $\phi$  sections may be alternately cascaded with  $\phi'$  sections as shown in (c)
- During the evaluation phase, the logic ripples through each stage in succession up to the next C<sup>2</sup>MOS latch

# Zipper CMOS Dynamic Logic

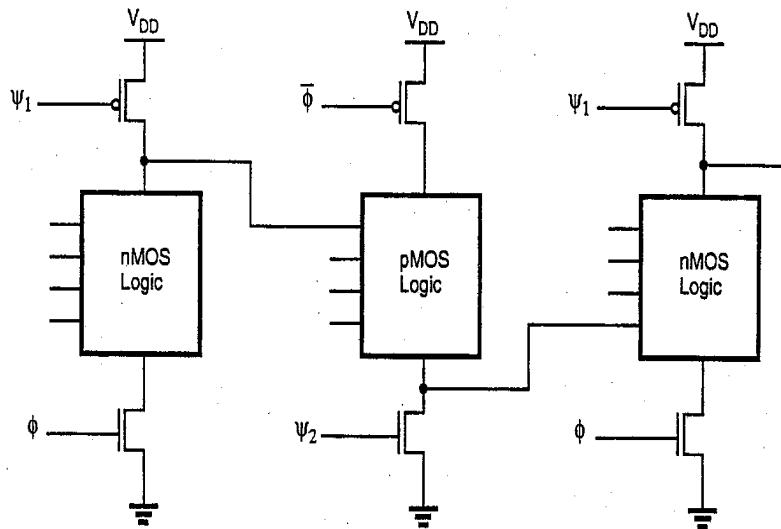


- **Zipper CMOS logic** is a scheme for improving charge leakage and charge sharing problems
- Pre-charge transistors receive a slightly modified clock where the clock pulse (during pre-charge off time) holds the pre-charge transistor at weak conduction in order to provide a trickle pre-charge current during the evaluation phase
  - PMOS pre-charge transistor gates are held at  $V_{DD} - |V_{tp}|$
  - NMOS pre-charge transistor gates are held at  $V_{tn}$  above GND

 
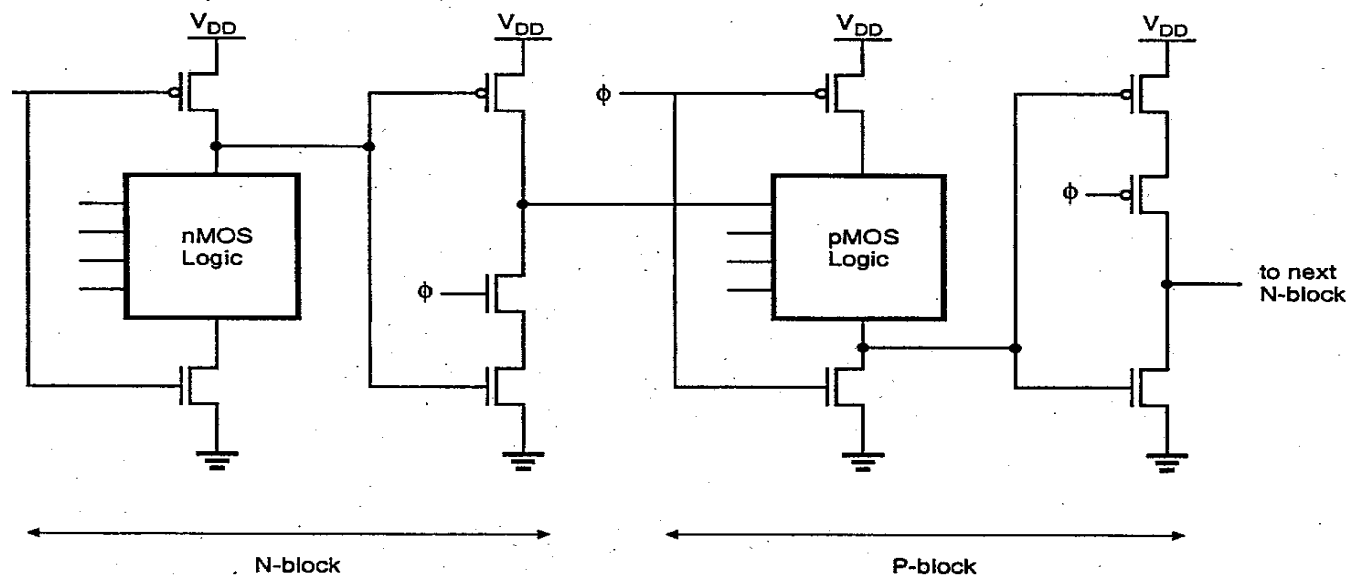
# Pipelined True Single Phase Clock (TSPC) CMOS

- A true single phase clock system (without any inverted clocks required) can be built as shown below
- Each NMOS and PMOS stage is followed by a dynamic latch (inverter) built with only the single phase clock  $\phi$
- The single phase clock  $\phi$  is used for both NMOS and PMOS stages
  - NMOS logic stages pre-charge when  $\phi$  is low and evaluate when  $\phi$  is high
  - PMOS logic stages pre-charge when  $\phi$  is high and evaluate when  $\phi$  is low
- With inverter latches between each stage, an erroneous evaluate condition can not exist
- Attractive circuit for use in pipelined, high performance processor logic





# References

- Lecture material R. W. Knepper SC571
- S-M. Kang and Y. Leblebici , *CMOS Digital Integrated Circuits: Analysis and Design*,, 3rd edition