
 


 
$$\begin{aligned}
 (a+b) \cdot (a+c) &= a + a \cdot b + a \cdot c \\
 &= a \cdot (1+b) + c \\
 &= a \cdot (1+c) + b \\
 &= a + b \cdot c
 \end{aligned}$$



# ECE 410: VLSI Design


## Course Lecture Notes

(Uyemura textbook)

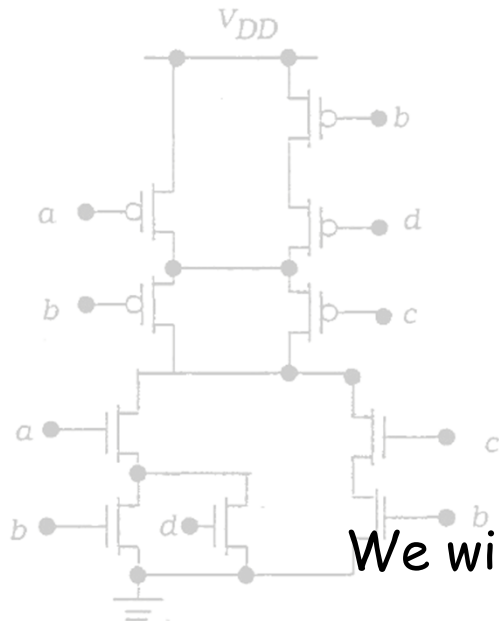

Professor Fathi Salem  
Michigan State University

 We will be updating the notes this Semester.



# Electronics Revolution

---

- Age of electronics
    - microcontrollers, DSPs, and other VLSI chips are everywhere
  - Electronics of today and tomorrow
    - higher performance (speed) circuits
    - low power circuits for portable applications
    - more mixed signal emphasis
      - wireless hardware
      - high performance signal processing
      - Sensors, actuators, and microsystems
- (Digital Camera), Camcorder, PDAs**  
**MP3/CD Player Laptop Cell phone**  
**Games: Nintendo; xbox, etc.**




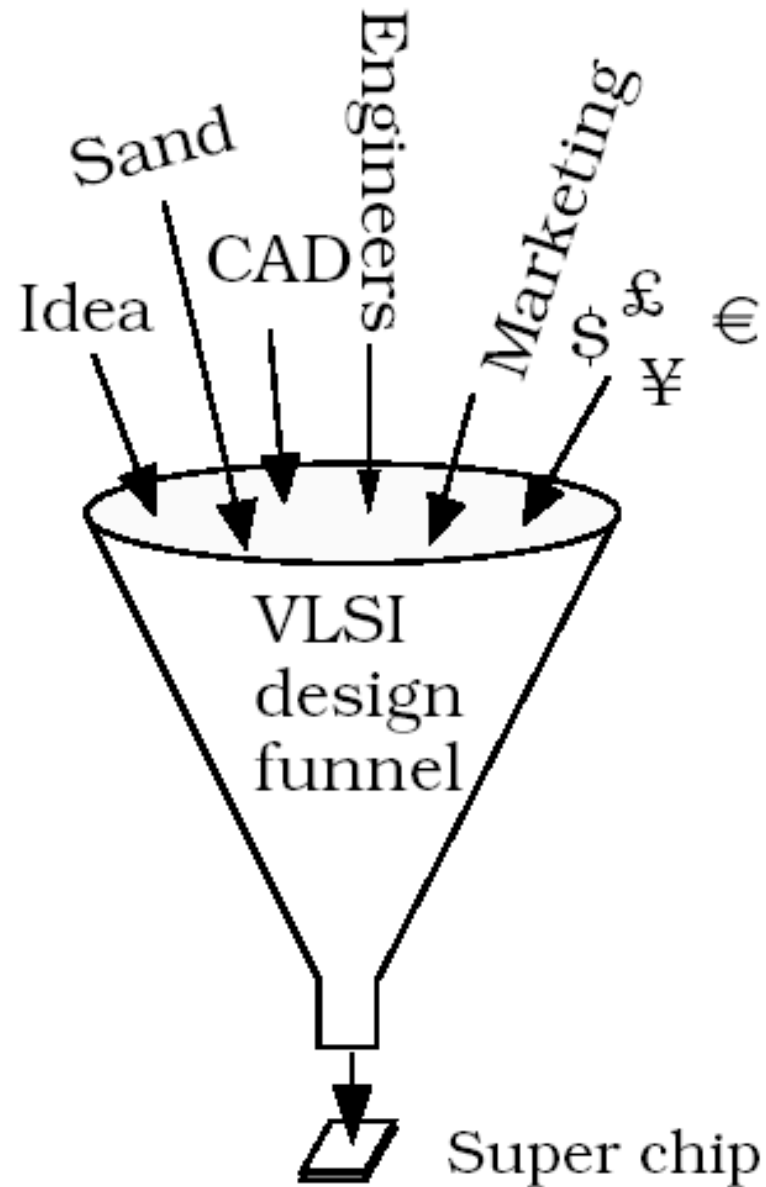


Figure 1.1 (p. 2)  
The VLSI design  
funnel.

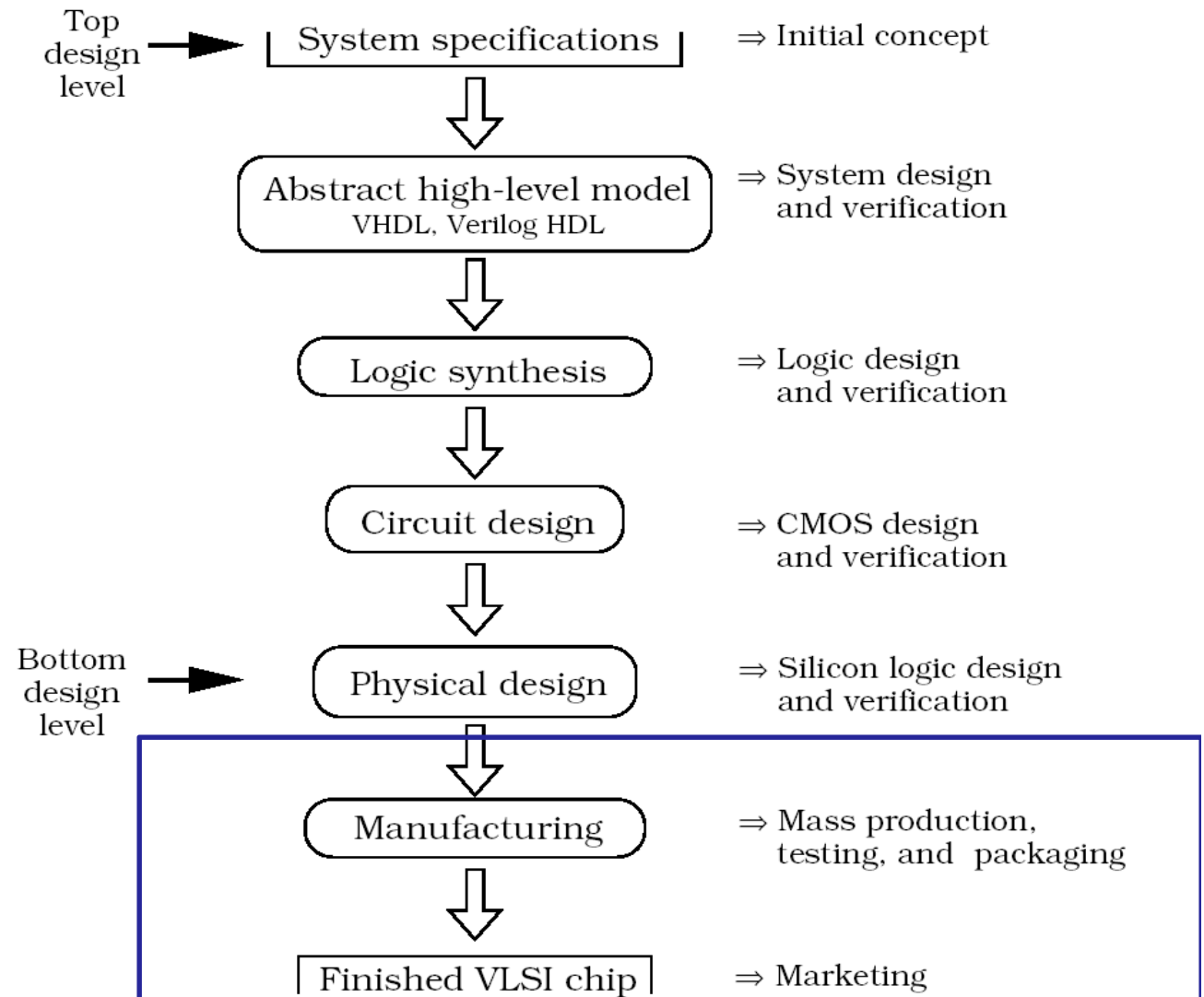

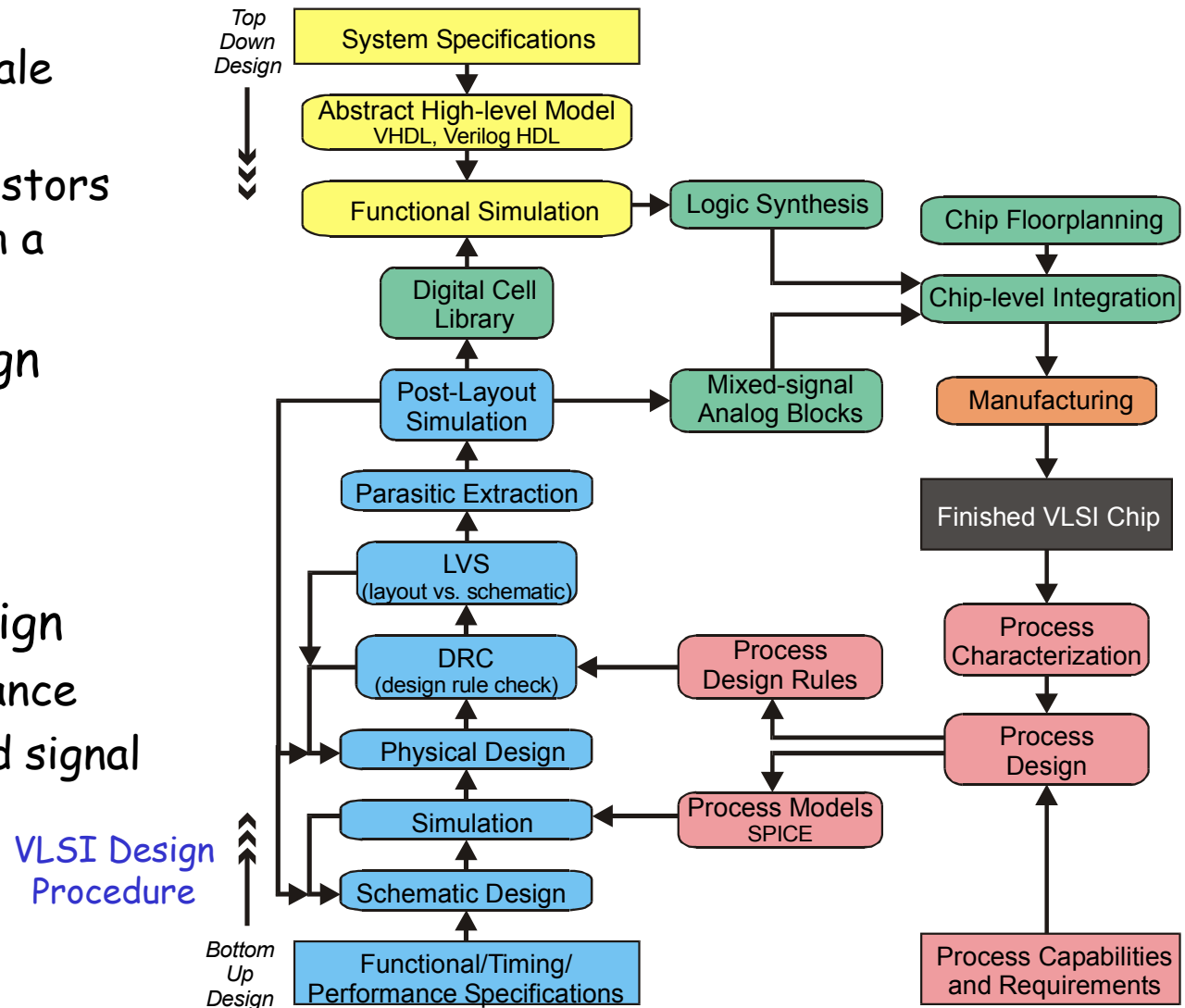


Figure 1.2  
(p.4)  
General  
overview of  
the design  
heirarchy.



# VLSI Design Flow

- VLSI
  - very large scale integration
  - lots of transistors integrated on a single chip
- Top Down Design
  - digital mainly
  - coded design
  - ECE 411
- Bottom Up Design
  - cell performance
  - Analog/mixed signal
  - ECE 410



# Integrated Circuit Technologies

- Why does CMOS dominate--Now?

- other technologies
  - passive circuits
  - III-V devices
  - Silicon BJT

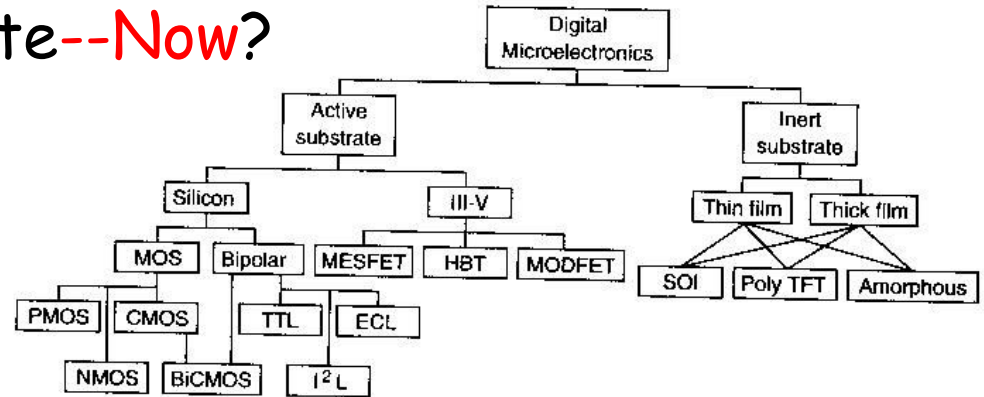


Fig. 1.1 Family of digital IC.

- CMOS dominates because:

- Silicon is cheaper → preferred over other materials
- physics of CMOS is easier to understand???
- CMOS is easier to implement/fabricate
- CMOS provides lower power-delay product
- CMOS is lowest power ★
- can get more CMOS transistors/functions in same chip area


- BUT! CMOS is not the fastest technology!

- BJT and III-V devices are faster





# MOSFET Physical View

- Physical Structure of a MOSFET Device

 

critical dimension = "feature size"

- Schematic Symbol for 4-terminal MOSFET

  


- Simplified Symbols


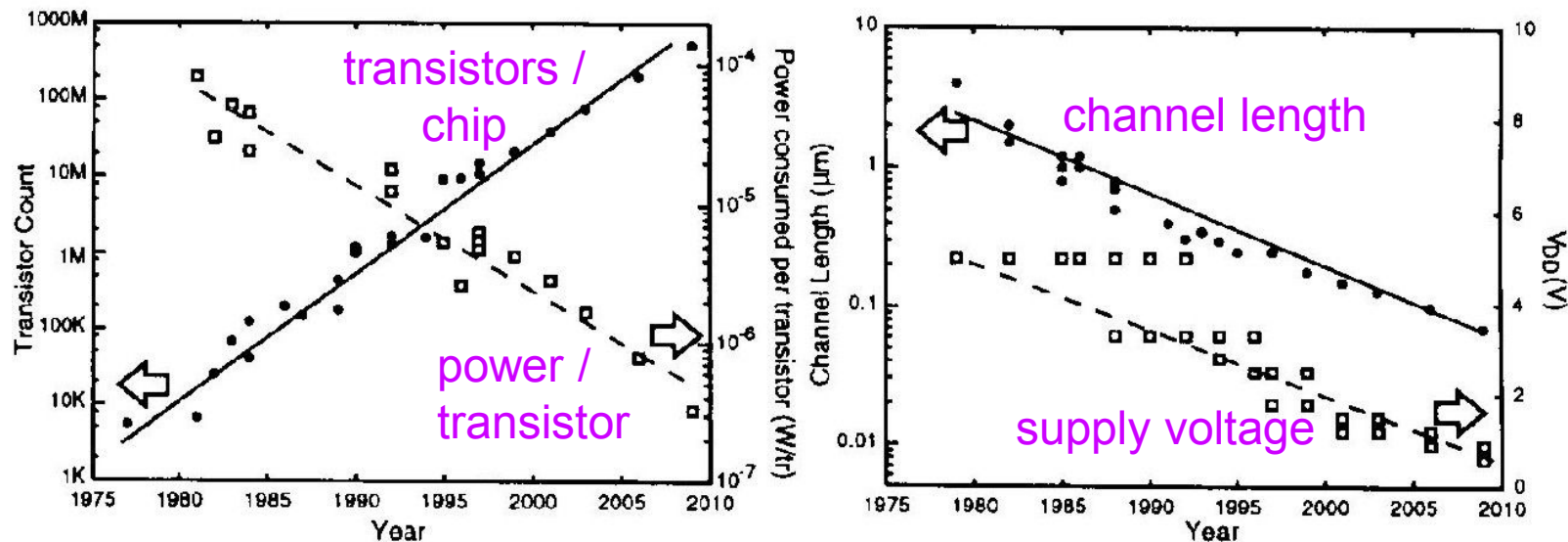
# CMOS Technology Trends

- Variations over time
  - # transistors / chip: increasing with time
  - power / transistor: decreasing with time (constant power density)
  - device channel length: decreasing with time
  - power supply voltage: decreasing with time



ref: Kuo and Lou, Low-Voltage CMOS VLSI Circuits, Fig. 1.3, p. 3


low power/transistor is critical for future ICs




 
# Moore's Law


- In 1965, Gordon Moore realized there was a striking trend; each new generation of memory chip contained roughly *twice as much capacity* as its predecessor, and each chip was released within *18-24 months* of the previous chip. He reasoned, computing power would rise exponentially over relatively brief periods of time.



(ref: <http://www.intel.com/intel/museum/25anniv/hof/moore.htm>)

- Moore's observation, now known as *Moore's Law*, described a trend that has continued and is still **remarkably accurate**. *In 26 years* the number of transistors on a chip has increased more than *3,200 times*, from 2,300 on the 4004 in 1971 to 7.5 million on the Pentium II processor.

## Power Supply Trends

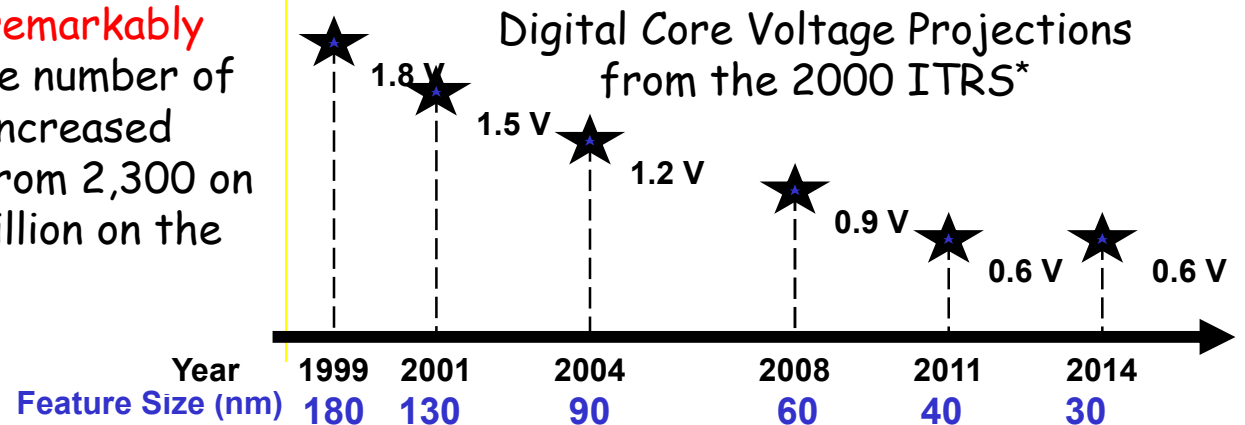

\* <http://public.itrs.net/Files/2000UpdateFinal/ORTC2000final.pdf>



# “Electronics” Building block(s)

---

- MOSFET Device-- 1950+ to 2020
- New elements in nano technologies are emerging. These include:
  - Fin-Transistor
  - Memristor: memory resistor- see IEEE Spectrum
  - Nano-tubes
  - Molecular devices
  - Quantum dots
  - Etc.



# VLSI Design Flow

- VLSI


- very large scale integration
- lots of transistors integrated on a single chip

- Top Down Design

- digital mainly
- coded design
- ECE 411


- Bottom Up Design

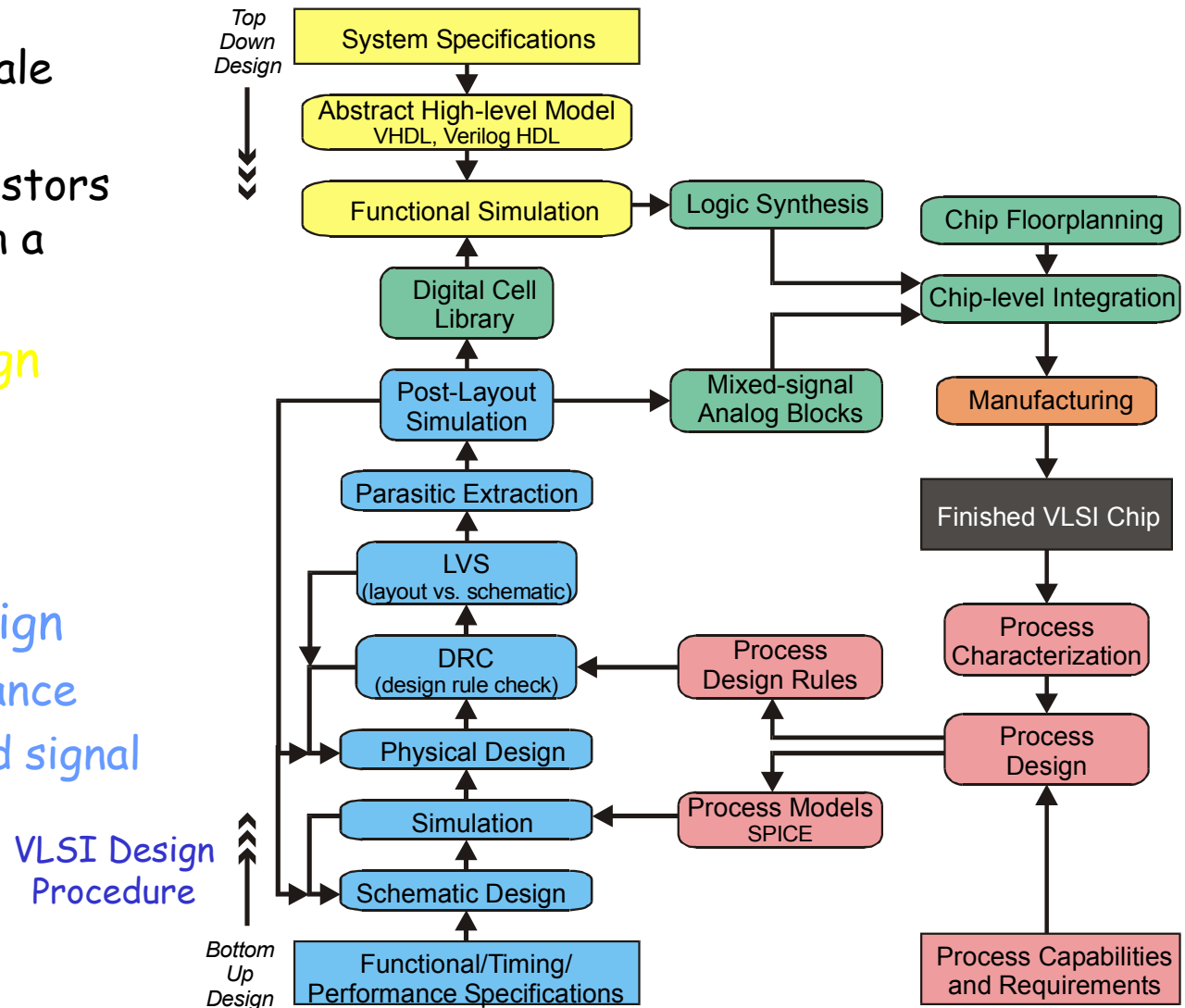- cell performance
- Analog/mixed signal
- ECE 410




# MOSFET Physical View


- Physical Structure of a MOSFET Device

 

- Schematic Symbol for 4-terminal MOSFET

 

- Simplified Symbols

 


# What is a MOSFET?

- Digital integrated circuits rely on transistor switches
  - most common device for digital and mixed signal: MOSFET

- Definitions

 - MOS = Metal Oxide Semiconductor
  - physical layers of the device
- FET = Field Effect Transistor
  - What field? What does the field do?
  - Are other fields important?
- CMOS = Complementary MOS
  - use of both nMOS and pMOS to form a circuit with lowest power consumption.



- Primary Features

- gate; gate oxide (insulator)- very thin ( $\sim 10^{-10}$ )-- exaggerated in Fig.
- source and drain
- channel
- bulk/substrate


NOTE: "Poly" stands for polysilicon in modern MOSFETs


 
# Fundamental Relations in MOSFET


- Electric Fields

- fundamental equation
  - electric field:  $E = V/d$
- vertical field through gate oxide
  - determines charge induced in channel
- horizontal field across channel
  - determines source-to-drain current flow




- Capacitance

 - fundamental equations
  - capacitor charge:  $Q = CV$
  - capacitance:  $C = \epsilon A/d$
- charge balance on capacitor,  $Q+ = Q-$ 
  - charge on gate is balanced by charge in channel
  - what is the source of channel charge? where does it come from?


 
# CMOS Cross Section View

- Cross section of a 2 metal, 1 poly CMOS process



## Typical MOSFET Device (nMOS)


 





Figure 2.11 The final cross section of a CMOS microcircuit with two layers of metal.

 - Layout (top view) of the devices above (partial, simplified)


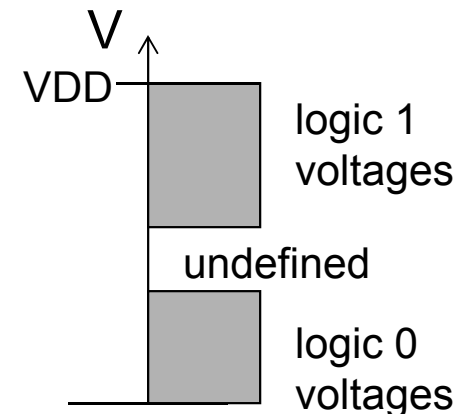  
# CMOS Circuit Basics

- **CMOS** = complementary MOS
  - uses 2 types of MOSFETs to create logic functions
    - nMOS
    - pMOS
- **CMOS Power Supply**
  - typically single power supply
  - **VDD**, with Ground reference
    - typically uses single power supply
    - VDD ranges from (0.6V) 1V to 5V
- **Logic Levels (voltage-based)**
  - all voltages between 0V and VDD
  - Logic '1' = VDD
  - Logic '0' = ground = 0V





# Transistor Switching Characteristics

- nMOS

- switching behavior

- on = closed, when  $V_{in} > V_{tn}$
- off = open, when  $V_{in} < V_{tn}$

- pMOS

- switching behavior

- on = closed, when  $V_{in} < VDD - |V_{tp}|$
- off = open, when  $V_{in} > VDD - |V_{tp}|$




- Digital Behavior

- nMOS

$V_{in}$	$V_{out}$ (drain)	
1	$V_s=0$	device is ON
0	?	device is OFF

- pMOS

$V_{in}$	$V_{out}$ (drain)	
1	?	device is OFF
0	$V_s=VDD=1$	device is ON

 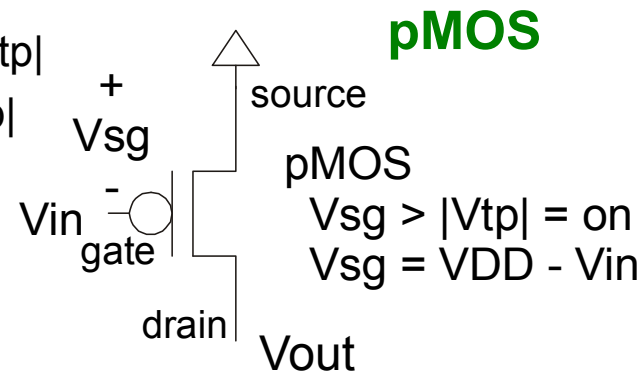 

### Rule to Remember

'source' is at

- lowest potential for nMOS
- highest potential for pMOS



# MOSFET Pass Characteristics

- Each type of transistor is better at passing (to output) one digital voltage than the other



- nMOS passes a good low (0) but not a good high (1)
- pMOS passes a good high (1) but not a good low (0)

TABLE 1.1 The Output Logic Levels of N-SWITCHES and P-SWITCHES

LEVEL	SYMBOL	SWITCH CONDITION
Strong 1	1	P-SWITCH gate = 0, source = $V_{DD}$
Weak 1	1	N-SWITCH gate = 1, source = $V_{DD}$ or P-SWITCH connected to $V_{DD}$
Strong 0	0	N-SWITCH gate = 1, source = $V_{SS}$
Weak 0	0	P-SWITCH gate = 0, source = $V_{SS}$ or N-SWITCH connected to $V_{SS}$
High impedance	Z	N-SWITCH gate = 0 or P-SWITCH gate = 1

## nMOS



on when gate is 'high'

  

Passes a good low  
Max high is  $V_{DD} - V_{tn}$

## pMOS

on when gate is 'low'

  

Passes a good high  
Min low is  $|V_{tp}|$

### Rule to Remember


'source' is at lowest potential (nMOS) and highest potential (pMOS)



# MOSFET Terminal Voltages

- How do you determine one terminal voltage if other 2 are known?

## - nMOS

 

- case 1) if  $V_g > V_i + V_{tn}$ , then  $V_o = V_i$  ( $V_g - V_i > V_{tn}$ )

- here  $V_i$  is the "source" so the nMOS will pass  $V_i$  to  $V_o$


- case 2) if  $V_g < V_i + V_{tn}$ , then  $V_o = V_g - V_{tn}$  ( $V_g - V_i < V_{tn}$ )

- here  $V_o$  is the "source" so the nMOS output is limited

- Example ( $V_{tn}=0.5V$ ):  
 $V_g=5V, V_i=2V \Rightarrow V_o = 2V$   
 $V_g=2V, V_i=2V \Rightarrow V_o = 1.5V$

For nMOS,  
 $\max(V_o) = V_g - V_{tn}$

## - pMOS

 

- case 1) if  $V_g < V_i - |V_{tp}|$ , then  $V_o = V_i$  ( $V_i - V_g > |V_{tp}|$ )

- here  $V_i$  is the "source" so the pMOS will pass  $V_i$  to  $V_o$

- case 2) if  $V_g > V_i - |V_{tp}|$ , then  $V_o = V_g + |V_{tp}|$  ( $V_i - V_g < |V_{tp}|$ )

- here  $V_o$  is the "source" so the pMOS output is limited


- Example ( $V_{tp}=-0.5V$ ):  
 $V_g=2V, V_i=5V \Rightarrow V_o = 5V$   
 $V_g=2V, V_i=2V \Rightarrow V_o = 2.5V$

For pMOS,  
 $\min(V_o) = V_g + |V_{tp}|$


 
# Switch-Level Boolean Logic

- Logic gates are created by using sets of controlled switches
- Characteristics of an **assert-high** switch




**nMOS** acts like an **assert-high** switch

**Figure 2.1** Behavior of an assert-high switch


–  $y = x \cdot A$ , i.e.  $y = x$  iff  $A = 1$  (iff=if and only if)

Series switches  $\Rightarrow$  AND function

 

**Figure 2.2** Series-connected switches

 Parallel switches  $\Rightarrow$  OR function


 


**Figure 2.4** Parallel-connected switches

 

# Switch-Level Boolean Logic

- Characteristics of an **assert-low** switch




**pMOS** acts like an **assert-low** switch

–  $y = x \cdot \bar{A}$ , i.e.  $y = x$  if  $A = 0$


error in figure 2.5

 Series assert-low switches  $\Rightarrow$  ?



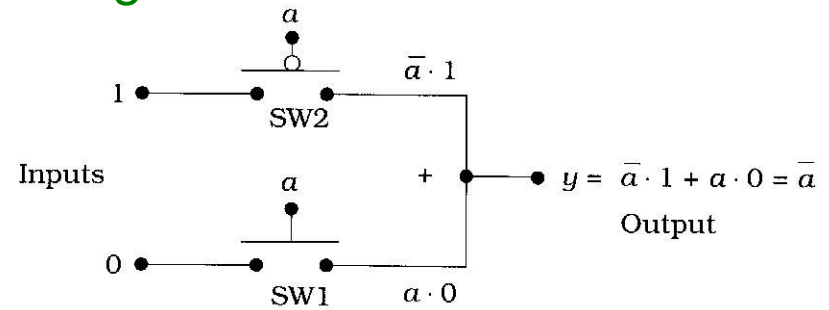**NOR**

**NOT function**, combining assert-high and assert-low switches



$a=1 \Rightarrow$  SW1 closed, SW2 open  $\Rightarrow y=0 = \bar{a}$

$a=0 \Rightarrow$  SW1 open, SW2 closed  $\Rightarrow y=1 = a$

Remember This??

$$\bar{a} \cdot \bar{b} = \overline{a + b}, \quad \bar{a} + \bar{b} = \overline{a \cdot b}$$


DeMorgan relations



# CMOS "Push-Pull" Logic
 
## CMOS Push-Pull Networks

- pMOS
  - "on" when input is low
  - pushes output high
- nMOS
  - "on" when input is high
  - pulls output low



- only one logic network (p or n) is required to produce (1/2-) the logic function???
- but the complementary set allows the "load" to be turned off for zero static power dissipation

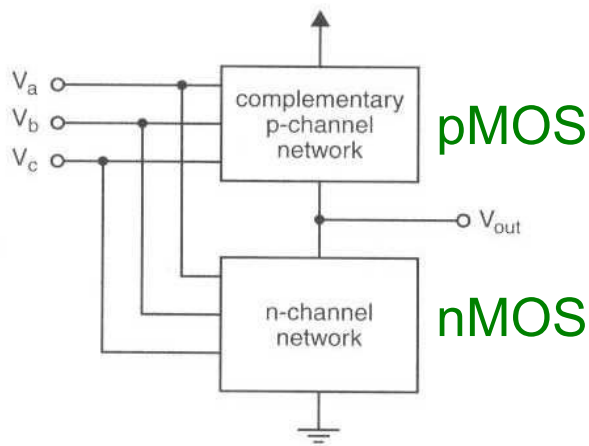


TABLE 1.1 The Output Logic Levels of N-SWITCHES and P-SWITCHES


LEVEL	SYMBOL	SWITCH CONDITION
Strong 1	1	P-SWITCH gate = 0, source = $V_{DD}$
Weak 1	1	N-SWITCH gate = 1, source = $V_{DD}$ or P-SWITCH connected to $V_{DD}$
Strong 0	0	N-SWITCH gate = 1, source = $V_{SS}$
Weak 0	0	P-SWITCH gate = 0, source = $V_{SS}$ or N-SWITCH connected to $V_{SS}$
High impedance	Z	N-SWITCH gate = 0 or P-SWITCH gate = 1

VSS = ground




# Review: Basic Transistor Operation

## CMOS Circuit Basics

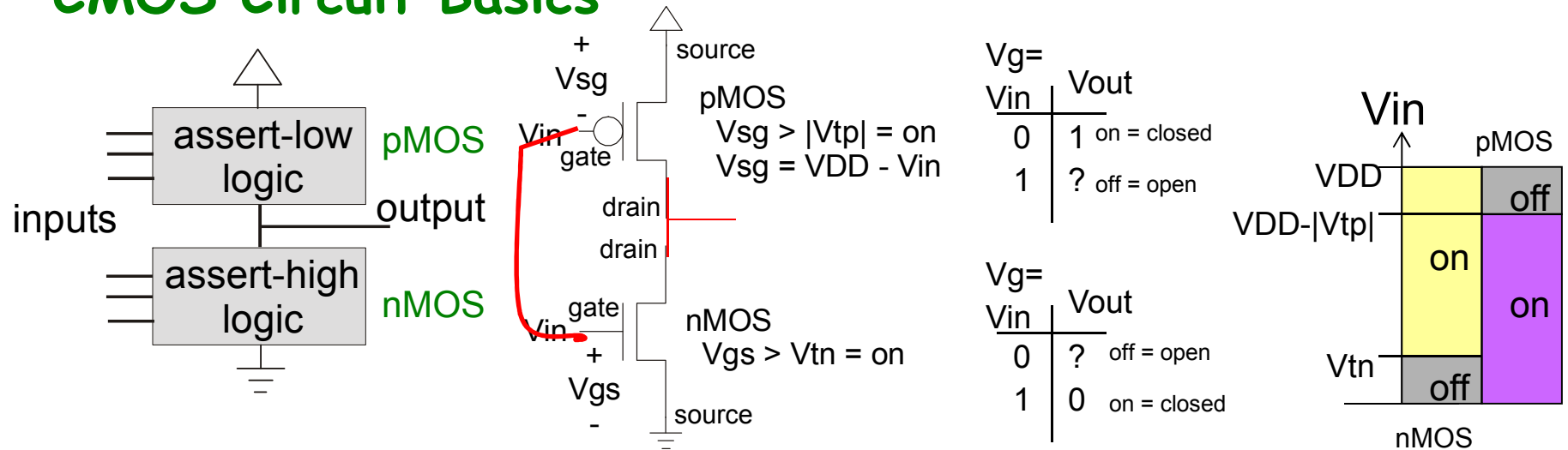
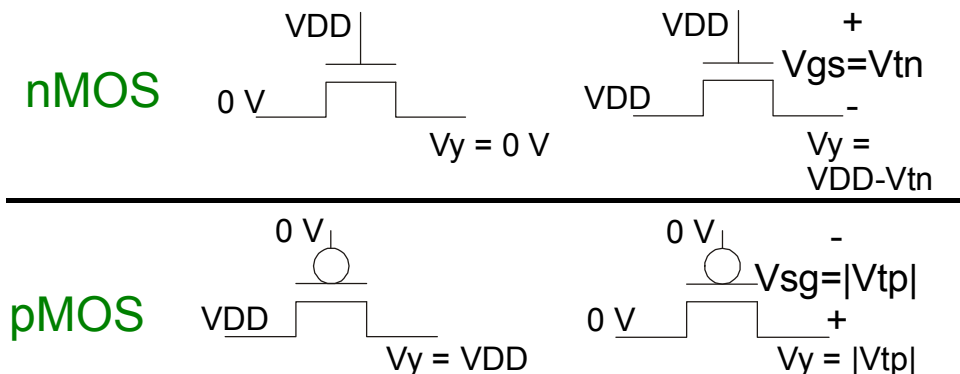
## CMOS Pass Characteristics

'source' is at lowest potential (nMOS) and highest potential (pMOS)




- nMOS
  - 0 in = 0 out
  - VDD in = VDD - V<sub>tn</sub> out
  - strong '0', weak '1'
- pMOS
  - VDD in = VDD out
  - 0 in = |V<sub>tp</sub>| out
  - strong '1', weak '0'



 
# Review: Switch-Level Boolean Logic

- **assert-high switch**

- $y = x \cdot A$ , i.e.  $y = x$  iff  $A = 1$




(a) Open

 


(b) Closed

- series = AND

 


assert-high switch

- parallel = OR

 


- **assert-low switch**

 - $y = x \cdot \bar{A}$ , i.e.  $y = x$  if  $A = 0$




(a) Closed

 

(b) Open

- series = NOR


- parallel = NAND

 


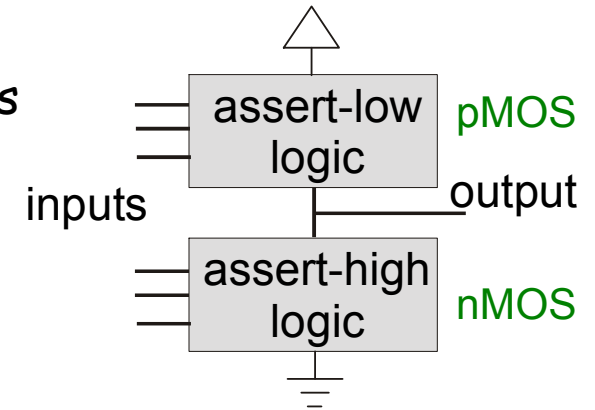
# Creating Logic Gates in CMOS

- All standard Boolean logic functions (INV, NAND, OR, etc.) can be produced in CMOS push-pull circuits.
- Rules for constructing logic gates using CMOS
  - use a complementary nMOS/pMOS pair for each input
  - connect the output to VDD through pMOS txs
  - connect the output to ground through nMOS txs
  - ensure the output is always either high or low
- CMOS produces "inverting" logic
  - CMOS gates are based on the inverter
  - outputs are always inverted logic functions  
e.g., NOR, NAND rather than OR, AND



## Logic Properties

### DeMorgan's Rules

$$(a \cdot b)' = a' + b'$$

$$(a + b)' = a' \cdot b'$$

### Useful Logic Properties

$$1 + x = 1 \quad 0 + x = x$$

$$1 \cdot x = x \quad 0 \cdot x = 0$$

$$x + x' = 1 \quad x \cdot x' = 0$$

$$a \cdot a = a \quad a + a = a$$

$$ab + ac = a(b+c)$$

### Properties which can be proven


$$(a+b)(a+c) = a+bc$$

$$a + a'b = a + b$$



 
# CMOS Inverter

- Inverter Function
  - toggle binary logic of a signal
- Inverter Switch Operation



input low  $\rightarrow$  output high  
 nMOS off/open  
 pMOS on/closed

 
pMOS "on"  
 $\rightarrow$  output high (1)



input high  $\rightarrow$  output low  
 nMOS on/closed  
 pMOS off/open

nMOS "on"  
 $\rightarrow$  output low (0)


- Inverter Symbol

 

- Inverter Truth Table

x	y = $\bar{x}$
0	1
1	0


- CMOS Inverter Schematic

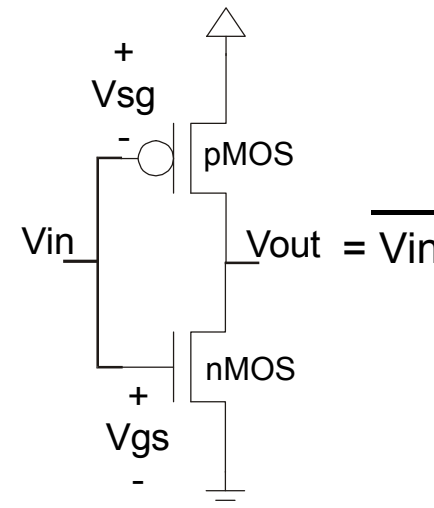

# nMOS Logic Gates

- Study nMOS logic first, more simple than CMOS
- nMOS Logic
  - assume a resistive load to VDD
  - nMOS switches pull output low based on inputs



## nMOS Inverter

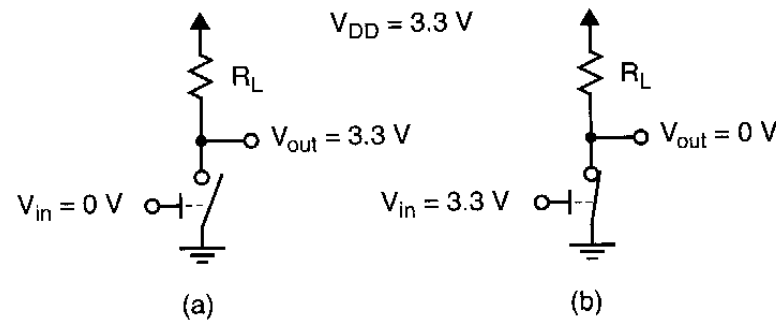

(a) nMOS is **off**  
→ output is high (1)



(b) nMOS is **on**  
→ output is low (0)

## nMOS NOR

  

- parallel switches = OR function
- nMOS pulls low (NOTs the output)

## nMOS NAND

  


- series switches = AND function
- nMOS pulls low (NOTs the output)



# CMOS NOR Gate

- NOR Symbol

 

- Karnaugh map

x \ y	0	1
0	1	0
1	0	0

$$g(x,y) = \bar{x} \cdot \bar{y} \cdot 1 + x \cdot 0 + y \cdot 0$$

- construct Sum of Products equation with all terms
- each term represents a MOSFET path to the output
- '1' terms are connected to VDD via pMOS
- '0' terms are connected to ground via nMOS


- NOR Truth Table

x	y	$\overline{x+y}$
0	0	1
0	1	0
1	0	0
1	1	0



# CMOS NOR Gate

- CMOS NOR Schematic

 

$$g(x,y) = \bar{x} \cdot \bar{y} \cdot 1 + x \cdot 0 + y \cdot 0$$

- output is LOW if x OR y is true
  - parallel nMOS
- output is HIGH when x AND y are false
  - series pMOS


- Important Points

- series-parallel arrangement
  - when nMOS in series, pMOS in parallel, and visa versa
  - true for all CMOS logic gates
  - allows us to construct more complex logic functions




# CMOS NAND Gate

- NAND Symbol

 


- CMOS Schematic

 

- Truth Table

x	y	$\overline{x \cdot y}$
0	0	1
0	1	1
1	0	1
1	1	0

- K-map

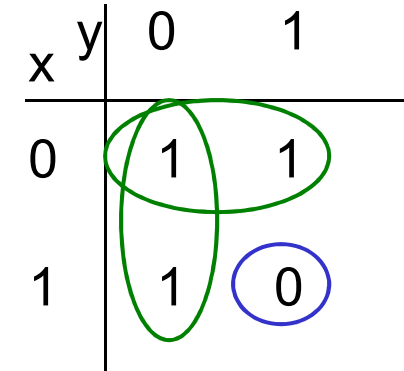

$$g(x,y) = (\overline{x} \cdot \overline{y} \cdot 1) + (\overline{x} \cdot y \cdot 1) + (x \cdot \overline{y} \cdot 1) + (x \cdot y \cdot 0)$$



$$= x \cdot y \cdot 0 + \overline{x} \cdot 1 + \overline{y} \cdot 1$$

- output is LOW if x AND y are true
  - series nMOS
- output is HIGH when x OR y is false
  - parallel pMOS





# 3-Input Gates

- NOR3

  


- NAND3

  

- Alternate Schematic

- what function?

 


- note shared gate inputs
  - is input order important?
  - in series, parallel, both?
- schematic resembles how the circuit will look in *physical layout*




# Review: CMOS NAND/NOR Gates

- NOR Schematic

 

- output is LOW if x OR y is true
  - parallel nMOS
- output is HIGH when x AND y are false
  - series pMOS

- NAND Schematic

 

- output is LOW if x AND y are true
  - series nMOS
- output is HIGH when x OR y is false
  - parallel pMOS





# Complex Combinational Logic

---

- General logic functions

- for example

$$f = \overline{a \cdot (b + c)}, \quad f = \overline{(d \cdot e) + a \cdot (\overline{b} + c)}$$

- How do we construct the CMOS gate?

- use DeMorgan principles to modify expression
  - construct nMOS and pMOS networks

$$\overline{a \cdot b} = \overline{a} + \overline{b}$$

$$\overline{a + b} = \overline{a} \cdot \overline{b}$$

- use Structured Logic
  - AOI (AND OR INV)
  - OAI (OR AND INV)




# Using DeMorgan

- DeMorgan Relations


- NAND-OR rule  $\overline{a \cdot b} = \overline{a} + \overline{b}$

- bubble pushing illustration

 


- bubbles = inversions

 - NOR-AND rule  $\overline{a + b} = \overline{a} \cdot \overline{b}$




to implement pMOS this way, must push all bubbles to the inputs and remove all NAND/NOR output bubbles

 - pMOS and bubble pushing
  - Parallel-connected pMOS



- assert-low OR
- creates NAND function

- Series-connected pMOS

 


- assert-low AND
- creates NOR function



# Rules for Constructing CMOS Gates
 
## The Mathematical Method

- Given a logic function  
$$F = f(a, b, c)$$
- Reduce (using DeMorgan) to eliminate inverted operations
  - inverted variables are OK, but not operations (NAND, NOR)
- Form pMOS network by complementing the **inputs**  
$$F_p = f(\overline{a}, \overline{b}, \overline{c})$$
- Form the nMOS network by complementing the **output**  
$$F_n = \overline{f(a, b, c)} = \overline{F}$$
- Construct  $F_n$  and  $F_p$  using AND/OR series/parallel MOSFET structures
  - series = AND, parallel = OR




## EXAMPLE:

$$F = \overline{ab} \Rightarrow$$

$$F_p = \overline{\overline{a} \overline{b}} = a + b; \quad \text{OR/parallel}$$

 
$$F_n = \overline{\overline{ab}} = ab; \quad \text{AND/series}$$



# CMOS Combinational Logic Example

- Construct a CMOS logic gate to implement the function:

$$F = \overline{a \cdot (b + c)}$$

 

14 transistors (cascaded gates)

- pMOS**

- Apply DeMorgan expansions


$$F = \overline{a} + \overline{(b + c)}$$

$$F = \overline{a} + (\overline{b} \cdot \overline{c})$$

- Invert inputs for pMOS

$$F_p = a + (b \cdot c)$$

- Resulting Schematic

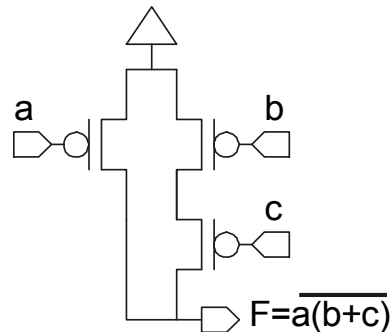


- nMOS**

- Invert output for nMOS


$$F_n = a \cdot (b + c)$$

- Apply DeMorgan none needed

- Resulting Schematic

 

6 transistors (CMOS)

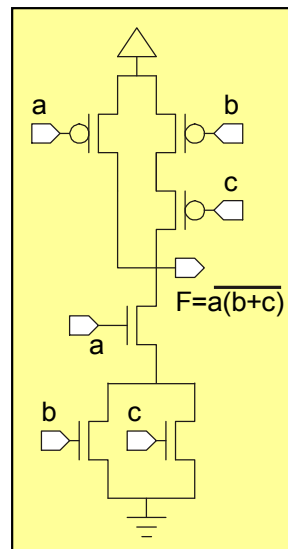

# Structured Logic


---

- Recall CMOS is inherently Inverting logic
- Can use structured circuits to implement general logic functions
- **AOI**: implements logic function in the order AND, OR, NOT (Invert)
  - Example:  $F = a \cdot b + c \cdot d$ 
    - operation order: i) a AND b, c AND d, ii) (ab) OR (cd), iii) NOT
  - Inverted Sum-of-Products (SOP) form
- **OAI**: implements logic function in the order OR, AND, NOT (Invert)
  - Example:  $G = \overline{(x+y) \cdot (z+w)}$ 
    - operation order: i) x OR y, z OR w, ii) (x+y) AND (z+w), iii) NOT
  - Inverted Product-of-Sums (POS) form
- Use a *structured CMOS array* to realize such functions



 
# AOI/OAI nMOS Circuits


- nMOS AOI structure
  - series txs in parallel




$$F = \overline{a \cdot b + c \cdot d}$$

 

 - nMOS OAI structure
  - series of parallel txs



$$F = \overline{(a + e) \cdot (b + f)}$$

 


error in textbook Figure 2.45



 
# AOI/OAI pMOS Circuits


- pMOS AOI structure
  - series of parallel txs
  - opposite of nMOS (series/parallel)



 
- pMOS OAI structure
  - series txs in parallel
  - opposite of nMOS (series/parallel)



Complete CMOS  
AOI/OAI circuits

 

(a) AOI circuit

 

(b) OAI circuit



# Implementing Logic in CMOS

---

- Reducing Logic Functions

- fewest operations  $\Rightarrow$  fewest txs
- minimized function to eliminate txs
- Example:  $x y + x z + x v = x (y + z + v)$

5 operations:  
3 AND, 2 OR

# txs =

3 operations:  
1 AND, 2 OR

# txs =

- Suggested approach to implement a CMOS logic function
  - create nMOS network
    - invert output
    - reduce function, use DeMorgan to eliminate NANDs/NORs
    - implement using **series for AND** and **parallel for OR**
  - create pMOS network
    - complement each operation in nMOS network
      - i.e. make parallel into series and visa versa





# CMOS Logic Example

- Construct the function below in CMOS

$F = a + b \cdot (c + d)$ ; remember AND operations occur before OR


$F_n = a + b \cdot (c + d)$

- nMOS

- Group 2: c & d in parallel
- Group 1: b in series with G2
- Group 3: a parallel to G1/G2

- pMOS

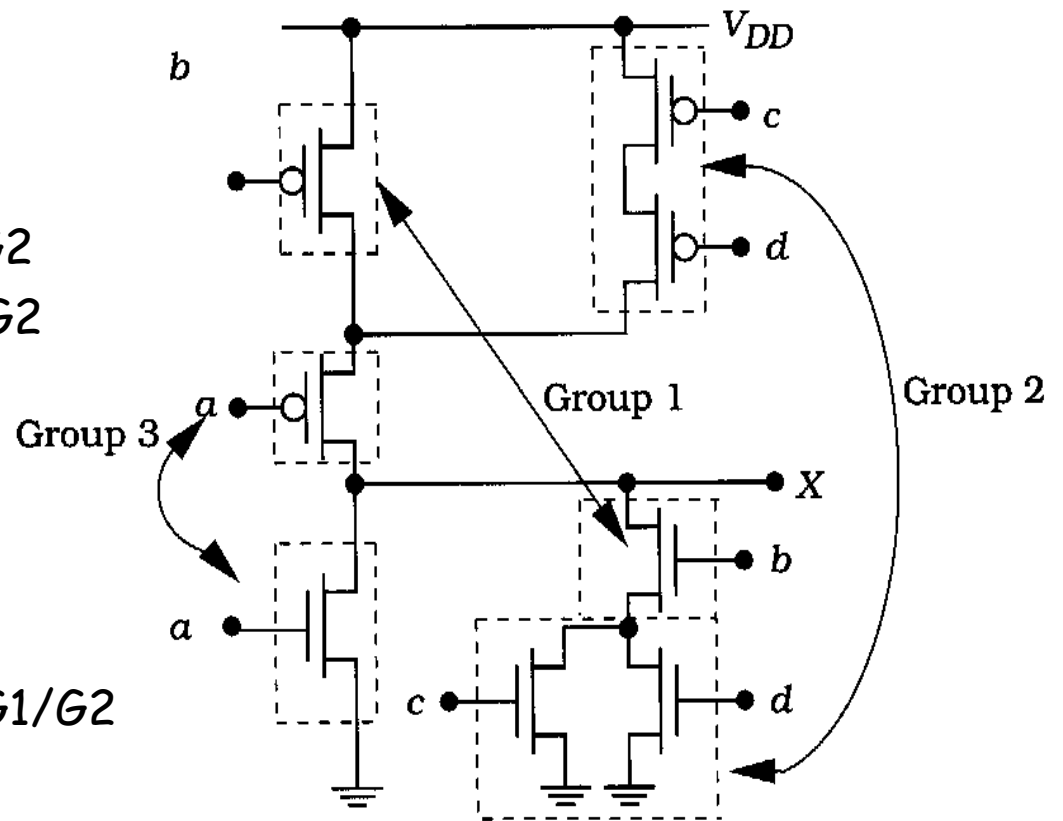- Group 2: c & d in series
- Group 1: b parallel to G2
- Group 3: a in series with G1/G2



- Circuit has an OAOI organization (AOI with extra OR)



# Another Combinational Logic Example

---

- Construct a CMOS logic gate which implements the function:

$$F = \overline{a} \cdot (b + \overline{c})$$

- pMOS

- Apply DeMorgan expansions  
none needed
- Invert inputs for pMOS  
 $F_p = a \cdot (\overline{b} + c)$
- Resulting Schematic ?

- nMOS

- Invert output for nMOS  
 $F_n = \overline{a} \cdot (b + \overline{c})$
- Apply DeMorgan  
 $F_n = a + \overline{(b + \overline{c})}$   
 $F_n = a + (\overline{b} \cdot c)$
- Resulting Schematic ?




# Yet Another Combinational Logic Example

- Implement the function below by constructing the nMOS network and complementing operations for the pMOS:

$$F = \overline{\overline{a}} \cdot b \cdot (a + c)$$

- nMOS
  - Invert Output
    - $F_n = \overline{\overline{a}} \cdot b \cdot (a + c) = \overline{a} \cdot b + \overline{(a + c)}$
  - Eliminate NANDs and NORs
    - $F_n = \overline{a} \cdot b + (\overline{a} \cdot \overline{c})$
  - Reduce Function
    - $F_n = \overline{a} \cdot (b + \overline{c})$
  - Resulting Schematic ?
  - Complement operations for pMOS
    - $F_p = \overline{a} + (b \cdot \overline{c})$

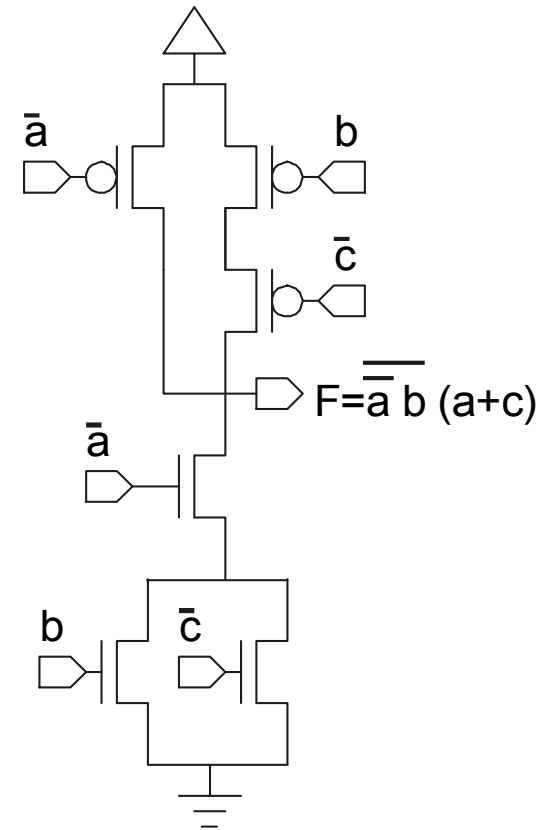


# XOR and XNOR

- Exclusive-OR (XOR)

- $a \oplus b = \bar{a} \cdot b + a \cdot \bar{b}$

- not AOI form

 

a	b	a ⊕ b
0	0	0
0	1	1
1	0	1
1	1	0

- Exclusive-NOR

- $\overline{a \oplus b} = a \cdot b + \bar{a} \cdot \bar{b}$

- inverse of XOR

- XOR/XNOR in AOI form


- XOR:  $\overline{\overline{a \oplus b}} = \overline{a \cdot b + \bar{a} \cdot \bar{b}}$ , formed by complementing XNOR above

- XNOR:  $\overline{a \oplus b} = \overline{\overline{a \cdot b + \bar{a} \cdot \bar{b}}}$ , formed by complementing XOR


thus, interchanging a and  $\bar{a}$  (or b and  $\bar{b}$ ) converts from XOR to XNOR



# XOR and XNOR AOI Schematic

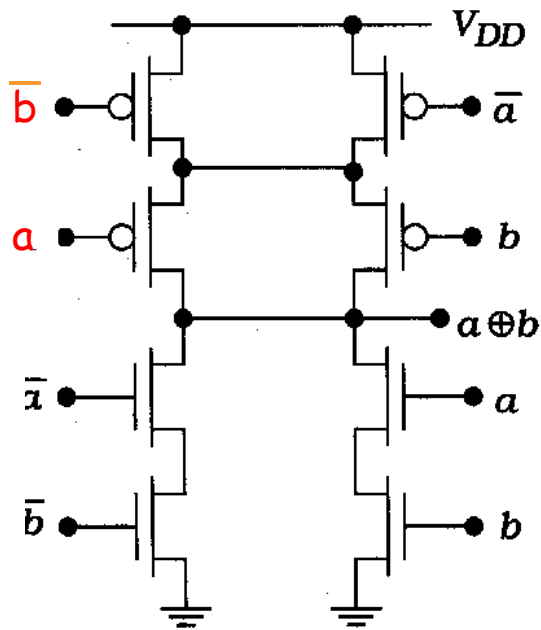

(a) Exclusive-OR

 

(b) Exclusive-NOR

note: see textbook, figure 2.57

$$\text{-XOR: } a \oplus b = \overline{a \cdot b + \overline{a} \cdot \overline{b}}$$

$$\text{-XNOR: } \overline{a \oplus b} = \overline{\overline{a} \cdot b + a \cdot \overline{b}}$$





# CMOS Transmission Gates

- Function

- gated switch, capable of passing both '1' and '0'

- Formed by a parallel nMOS and pMOS tx

 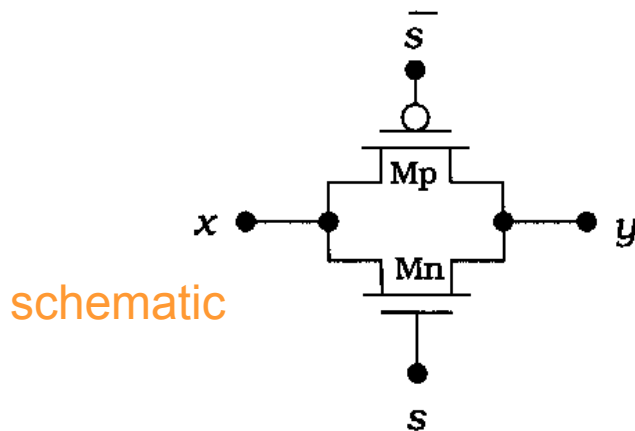recall: pMOS passes a good '1'  
and nMOS passes a good '0'



- Controlled by gate select signals,  $s$  and  $\bar{s}$

- if  $s = 1$ ,  $y = x$ , switch is closed, txs are on

- if  $s = 0$ ,  $y = \text{unknown}$  (high impedance),  
switch open, txs off


$$y = x s, \text{ for } s=1$$



# Transmission Gate Logic Functions

- TG circuits used extensively in CMOS
  - good switch, can pass full range of voltage (VDD-ground)
- 2-to-1 MUX using TGs

$$F = P_0 \cdot \bar{s} + P_1 \cdot s$$

 


$s$	TG0	TG1	$F$
0	Closed	Open	$P_0$
1	Open	Closed	$P_1$




# More TG Functions


- TG XOR and XNOR Gates

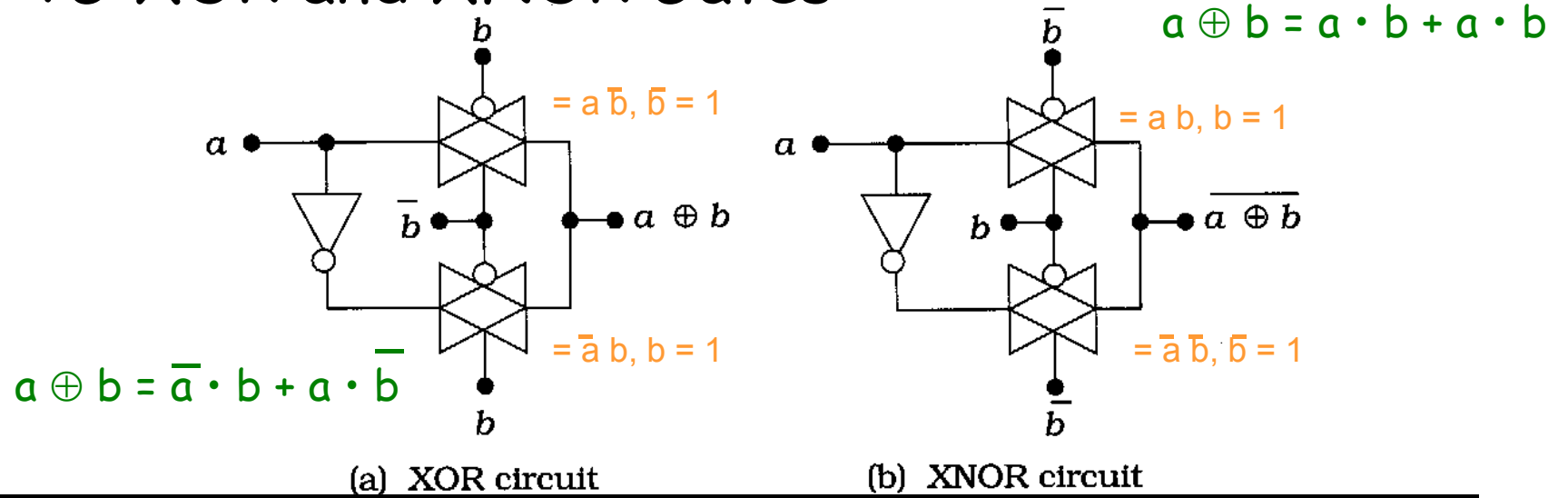

- Using TGs instead of "static CMOS"
  - TG OR gate

  


 


 

**Figure 2.64 (p. 59)**


An XNOR gate that uses both TGs and FETs.

 

 


**Figure 2.65 (p. 60)**  
Complementary clocking signals.






(a) Closed switch



(b) Open switch

 **Figure 2.66 (p. 61)**  
Behavior of a clocked TG.

 




**Figure 2.67 (p. 61)**


Data synchronization using transmission gates.

 

 


**Figure 2.68 (p. 62)**  
Block-level system timing diagram.





(a) Clocked adder



(b) Clocked ALU

**Figure 2.69 (p. 62)**  
**Control of binary words using clocking planes.**

