

ECEN474/704: (Analog) VLSI Circuit Design

Spring 2018

Lecture 5: Layout Techniques



Sam Palermo

Analog & Mixed-Signal Center

Texas A&M University


Announcements

- HW1 is due today
- Exam1 is on 2/13
 - 11:10-12:35PM (10 extra minutes)
 - Closed book w/ one standard note sheet
 - 8.5"x11" front & back
 - Bring your calculator
 - Covers material through lecture 5
 - Previous years' Exam 1s are posted on the website for reference
- Reference Material
 - Razavi Chapter 18 & 19

Agenda

- MOS Fabrication Sequence
- CMOS Design Rules
- Layout Techniques
- Layout Examples

 Fundamentals on Layout Techniques: N-Well CMOS Technologies




Substrate is always connected to the most negative voltage, and is shared by all N-type transistors

MOS Fabrication Sequence


[Razavi]




(a)

 

(b)

 


(c)

 


(d)

MOS Fabrication Sequence


[Razavi]

 


(e)

 

(f)

 


(g)

 

(h)

MOS Fabrication Sequence


[Razavi]

 

"Front-End"


"Back-End"

 - A "silicide" step, where highly conductive metal is deposited on the gate and diffusion regions, reduces transistor terminal resistance
- To prevent potential gate-source/drain shorting an "oxide spacer" is first formed before silicide deposition




Contact and Metal Fabrication

[Razavi]

 

Transistor Geometries

 - λ -based design rules allow a process and feature size-independent way of setting mask dimensions to scale
 - Due to complexity of modern processing, not used often today
- Minimum drawing feature = λ
 - Assume w.c. mask alignment $< 0.75\lambda$
 - Relative misalignment between 2 masks is $< 1.5\lambda$



$$AGate = W * L$$

$$AD, AS = W * X$$


$$PS, PS = W + 2X \text{ (3 sides)}$$

- X depends on contact size
 - 5λ in this example


BASIC SCNA CMOS LAYERS

Physical Layer
N-well
Silicon Nitride
Polysilicon Layer 1
Polysilicon Layer 2
P+ Ion Implant
N+ Ion Implant
Contact cut to n+/p_
Metal 1
Via Oxide Cuts
Metal 2
Pad Contact (Overglass)


P-channel MOSFET

 


N-channel MOSFET

 


Design Rule Basics

 

Minimum width and spacing

 


(a) Mask definition

 


(b) After annealing

Patterning sequence for a doped n+ line.

 


(a) Contact size

 


(b) Side view

Geometry of a contact cut

 


(a) Masking Design

 


(b) Registration tolerance


Contact spacing rule

 

 Depletion regions due to parallel n+ lines




(a) Correct mask sizing

 

 
(b) Incorrect mask sizing

Formation of n+ regions in an n-channel MOSFET



Gate spacing form an n+ edge


Gate overhang in MOSFET layout

 


(a) No overhang

(b) With misalignment


Effect of misalignment without overhang

 

(a) Resist pattern

 

(b) Isotropic etch

 


(c) anisotropic etch


Effect of misalignment without overhang

Mask Number	Mask Layer
1	NWELL
2	ACTIVE
3	POLY
4	SELECT
5	POLY CONTACT
6	ACTIVE CONTACT
7	METAL1
8	VIA
9	METAL2
10	PAD
11	POLY2


Design Rule Layers

 

 
Difference between the drawn and physical values for channel length and the channel width



Structure of a n-channel MOSFET

 


Example of Layout Rules

 


Perspective view of an n-channel MOSFET

- Minimum transistor width is set by minimum diffusion width
 - 2 or 3λ (check with TA)
- Often, we use a slightly larger "minimum" that is equal to the contact height (4λ in this example)

N-channel MOSFET

 


Bulk

 


(a) Cross section



P-channel MOSFET

 

Bulk

 


(b) Circuit symbol

  


(c) Top view


Stick Diagrams

 

(a) Definitions

 


(b) MOSFET

 

Stick diagrams for the CMOS Inverter

The CMOS Inverter


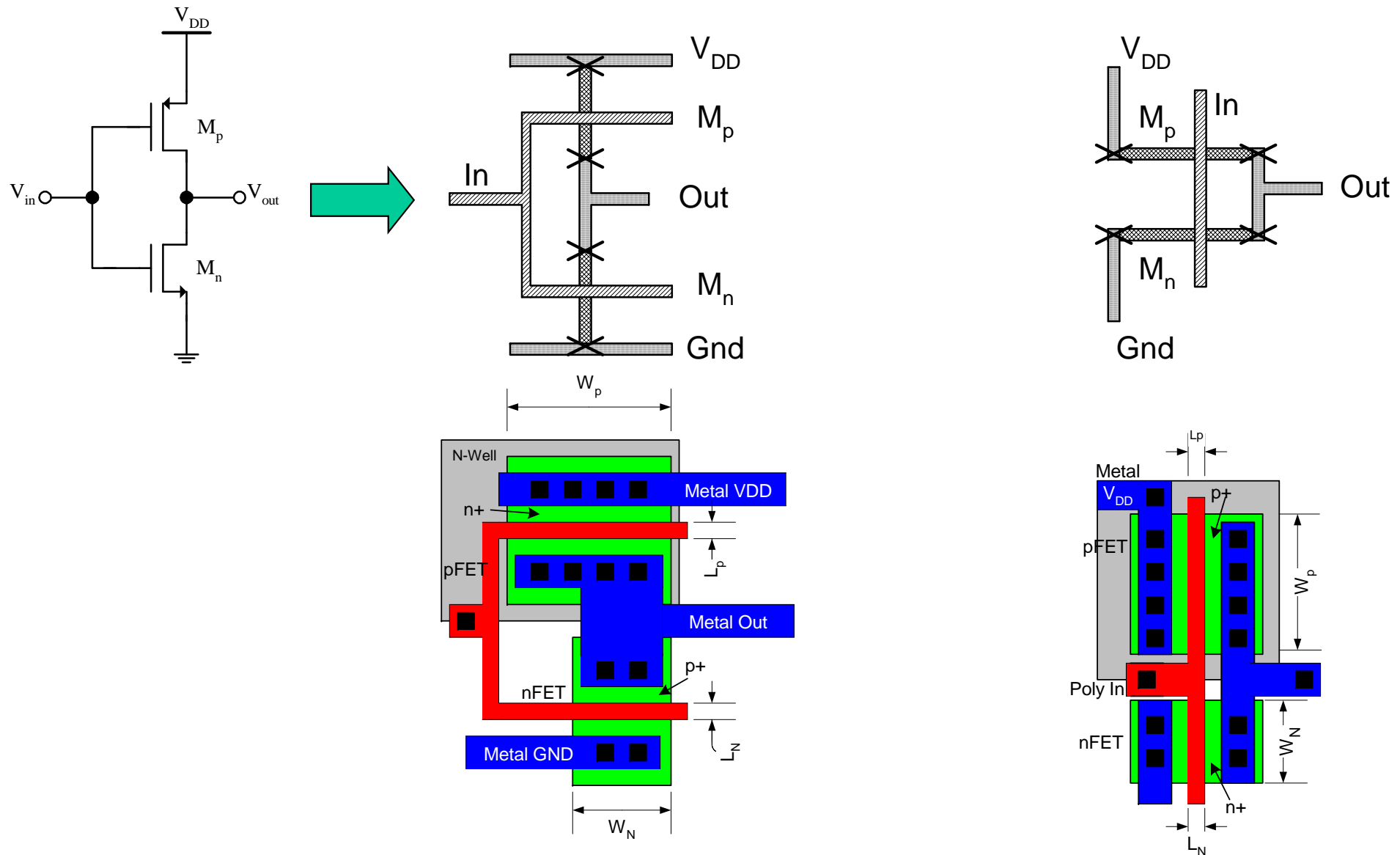


Basic Inverter Layout



Alternate Inverter Layout

Standard Cells: VDD, VSS and output run in Parallel

CMOS NAND2 logic gate

 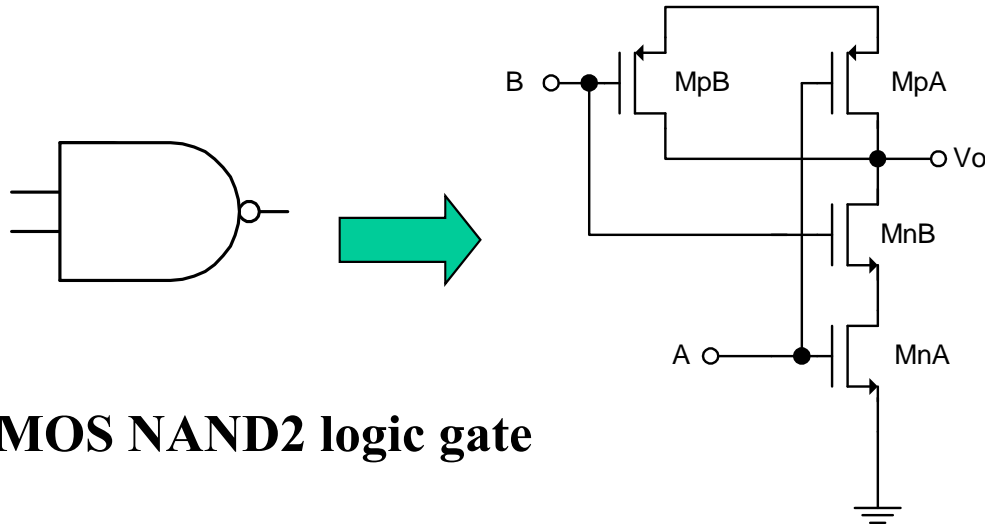



CMOS NOR2 logic gate

 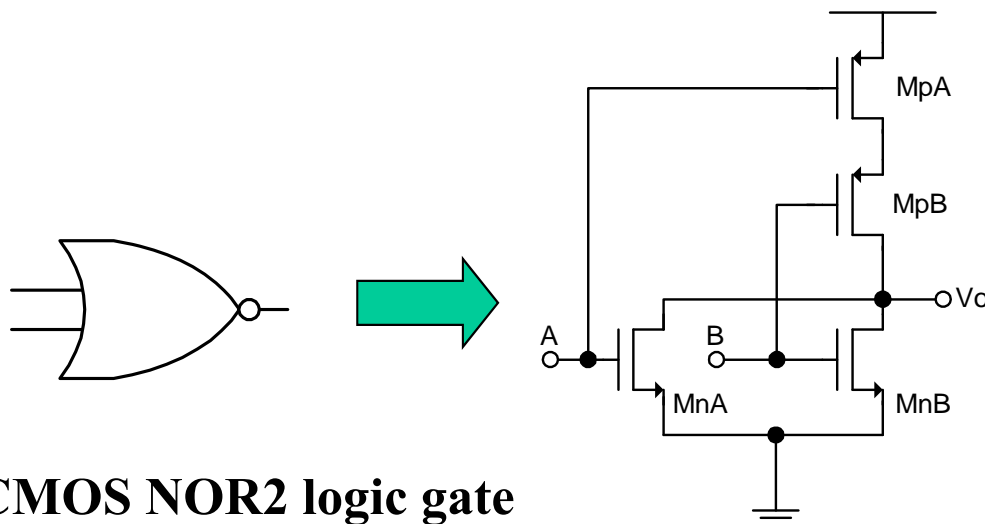


Wide Analog Transistor: Analog techniques

- Unacceptable drain and source resistance
- Stray resistances in transistor structure
- Contacts short the distributed resistance of diffused areas

  Most of the current will be shrunk to this side








Current is spread

 


Transistor orientation

     - Orientation is important in analog circuits for matching purposes



Stacked Transistors


 
- Wide transistors need to be split
- Parallel connection of n elements ($n = 4$ for this example)
- Contact space is shared among transistors
- Parasitic capacitances are reduced (important for high speed)
- Gate resistance is reduced




Note that parasitic capacitors are lesser at the drain

Matched Transistors

  - Simple layouts are prone to process variations, e.g. V_T , K_P , C_{ox}
- Matched transistors require elaborated layout techniques




 Differential pair requiring “matched transistors”




Interdigitized Layout

 - Averages the process variations among transistors
- Common terminal is like a serpentine





Why Interdigitized?

 

- Process variations are averaged among transistors
KPs for M1: $KP1 + KP4 + KP5 + KP8$ (Avg=4.5)
M2: $KP2 + KP3 + KP6 + KP7$ (Avg=4.5)
- Technique maybe good for matching dc conditions
- Uneven total drain area between M1 and M2. This is undesirable for ac conditions: capacitors and other parameters may not be equal
- A more robust approach is needed (Use dummies if needed !!)

A method of achieving better capacitive matching :

  
Using the previous slide values, we would have M2 with $KP=3.5$ and M1 with $KP=5.5$



- Each transistor is split in four equal parts interleaved in two by two's. So that for one pair of pieces of the same transistor we have currents flowing in opposite direction.
- Transistors have the same source and drain area and perimeters, but this topology is more susceptible to gradients (not common centroid)

Common Centroid Layouts

Usually routing is more complex

 

CENTROID
(complex layout)

M1: 8 transistors

(0,3) (0,1)

(1,2) (1,0)

(2,3) (2,1)

(3,2) (3,0)

M2: 8 transistors

(0,2) (0,0)


(1,3) (1,1)

(2,2) (2,0)



(3,3) (3,1)

Common Centroid Layouts

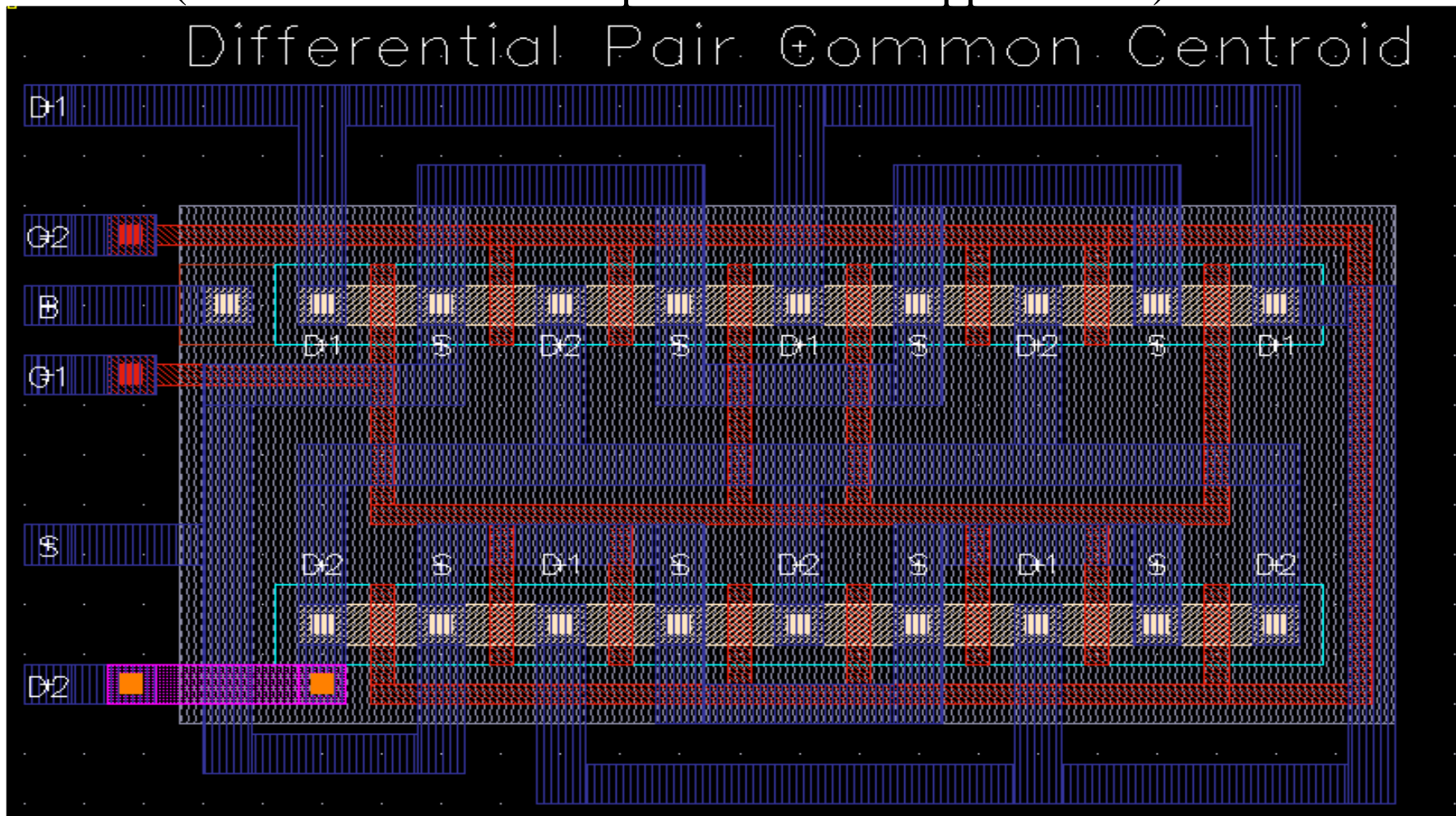- Split into parallel connections of even parts
- Half of them will have the drain at the right side and half at the left
- Be careful how you route the common terminal
- Cross talk (effect of distributed capacitors → RF applications)!



  - Many contacts placed close to one another reduces series resistance and make the surface of metal connection smoother than when we use only one contact; this prevents microcracks in metal;
- Splitting the transistor in a number of equal part connected in parallel reduces the area of each transistor and so reduces further the parasitic capacitances, but accuracy might be degraded!



Integrated Resistors




- Highly resistive layers (p^+ , n^+ , well or polysilicon)
- R defines the resistance of a square of the layer
- Accuracy less than 30%

Resistivity (volumetric measure of material's resistive characteristic)

$$\rho \text{ (}\Omega\text{-cm)}$$


Sheet resistance (measure of the resistance of a uniform film with arbitrary thickness t)

$$R = \rho/t \text{ (}\Omega/\text{)}$$

   


$$R = 2R_{\text{contact}} + (L/W) R$$

Diffusion/Well Resistors

 


Diffused resistance

 


Diffused resistance

well resistance

 


Pinched n-well resistance


Poly Resistors

 


e) **First polysilicon resistance**

 

 f) **First polysilicon resistance with a well shielding**




g) **Second polysilicon resistance**

 

 h) **Second polysilicon resistance with a well shielding**

TYPICAL INTEGRATED RESISTORS

$$R = 2R_{\text{cont}} + \frac{L}{W} R_{\square}$$



Type of layer	Sheet Resistance W/0	Accuracy %	Temperature Coefficient ppm/°C	Voltage Coefficient ppm/V
n + diff	30 - 50	20 - 40	200 - 1K	50 - 300
p + diff	50 - 150	20 - 40	200 - 1K	50 - 300
n - well	2K - 4K	15 - 30	5K	10K
p - well	3K - 6K	15 - 30	5K	10K
pinched n - well	6K - 10K	25 - 40	10K	20K
pinched p - well	9K - 13K	25 - 40	10K	20K
first poly	20 - 40	25 - 40	500 - 1500	20 - 200
second poly	15 - 40	25 - 40	500 - 1500	20 - 200

Special poly sheet resistance for some analog processes might be as high as 1.2 KΩ/

Large Resistors


In order to implement large resistors :

- Use long strips (large L/W)
- Use layers with high sheet resistance (bad performances – see previous table)
 - High temperature coefficient and non-linearity

Layout : rectangular “serpentine”


$$R = \frac{L}{W} R_{\square} = \frac{L}{W} \cdot \frac{\bar{\rho}}{x_j}$$

 - Estimating the resistance in the corners can be difficult



Well-Diffusion Resistor

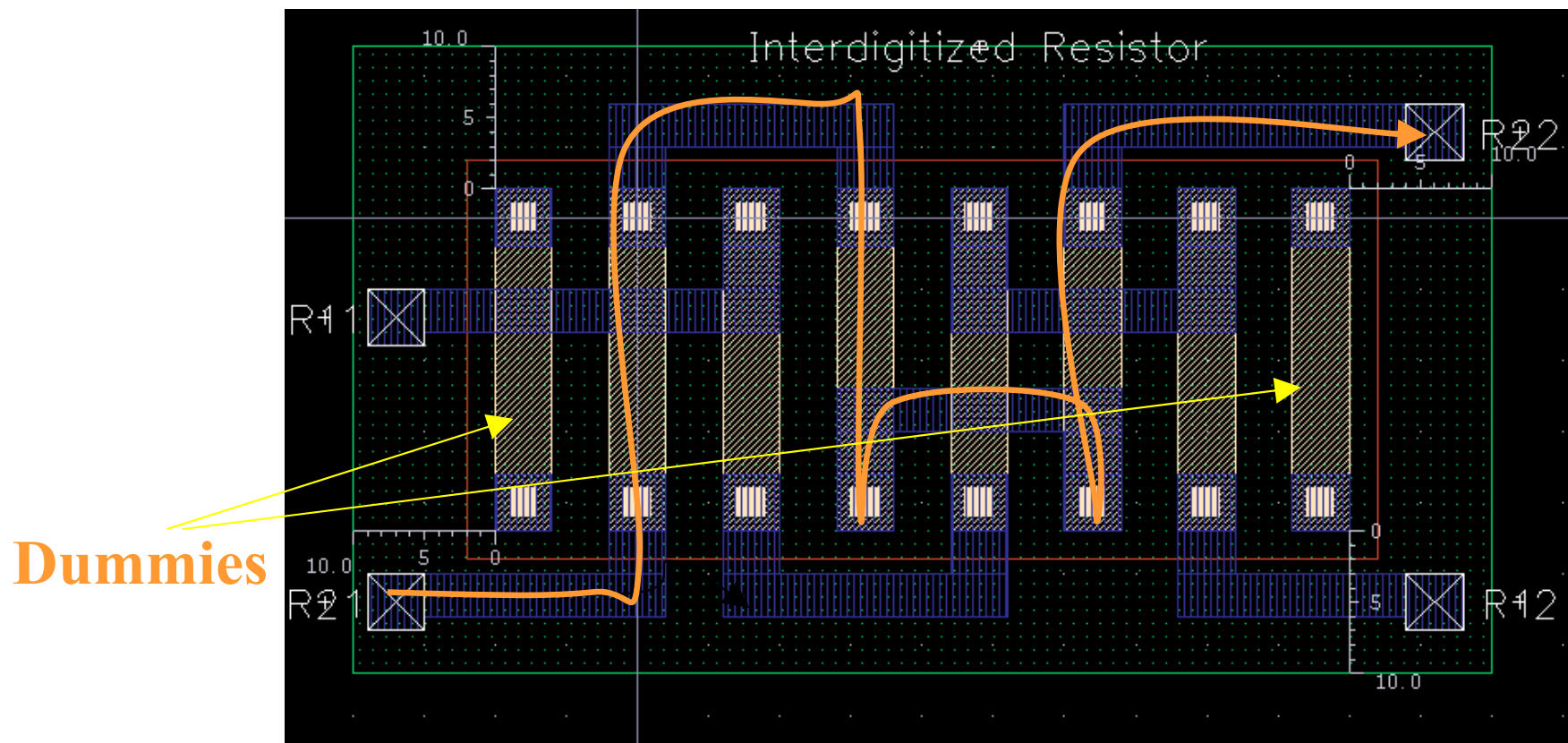- Example shows two long resistors for $K\Omega$ range
- Alternatively, “serpentine” shapes can be used
- Noise problems from the body
 - Substrate bias surrounding the well
 - Substrate bias between the parallel strips




Factors affecting accuracy :

Plastic packages cause a large pressure on the die (= 800 Atm.). It determines a variation of the resistivity.

For <100> material the variation is unisotropic, so the minimum is obtained if the resistance have a 45° orientation.

Temperature :

 Temperature gradient on the chip may produce thermal induced mismatch.



Etching


Wet etching : isotropic (undercut effect)

HF for SiO_2 ; H_3PO_4 for Al

Δx for polysilicon may be $0.2 - 0.4 \mu\text{m}$ with standard deviation $0.04 - 0.08 \mu\text{m}$.


Reactive ion etching (R.I.E.)(plasma etching associated to “bombardment”) : anisotropic.

 Δx for polysilicon is $0.05 \mu\text{m}$ with standard deviation $0.01 \mu\text{m}$




Boundary :

 The etching depends on the boundary conditions




- **Use dummy strips**

 Side diffusion effect : Contribution of endings




 Side Diffusion “widens” R
 R_{\square} is not constant with W




Impact of R_{cont} depends on relative geometry
 Best to always use a resistor W that is at least as large as the contact

Interdigitized structure :

 


MOS Capacitors

 


- One of the most dense capacitors available ($\text{fF}/\mu\text{m}^2$)
- Often used to de-couple DC power supply and bias signals
- Capacitor non-linearity can be important if used in the signal path

Integrated Capacitors


Poly - Diffusion

 

Poly - Poly

 


Metal1 - Poly


 


[Razavi]


Vertical Metal "Sandwich"

 

Lateral Metal-Oxide-Metal (MOM)

  


Poly1 - Poly2 Capacitor

 

Poly 2


Poly 1

 

- Area is determined by poly2
- Problems
 - undercut effects
 - nonuniform dielectric thickness
 - matching among capacitors

Factor affecting **RELATIVE** accuracy/matching

 - Oxide damage
- Impurities
- Bias condition $\left(\frac{\Delta \epsilon_{\text{ox}}}{\epsilon_{\text{ox}}} \right)$
- Bias history (for CVD)
- Stress
- Temperature
- Grow rate $\left(\frac{\Delta t_{\text{ox}}}{t_{\text{ox}}} \right)$
- Poly grain size
- Etching $\left(\frac{\Delta L}{L} \right); \left(\frac{\Delta W}{W} \right)$
- Alignment



$$\frac{\Delta C}{C} \approx 1 - 0.1\%$$

$$\left(\frac{\Delta C}{C} \right)^2 = \left(\frac{\Delta \epsilon_r}{\epsilon_r} \right)^2 + \left(\frac{\Delta t_{\text{ox}}}{t_{\text{ox}}} \right)^2 + \left(\frac{\Delta L}{L} \right)^2 + \left(\frac{\Delta W}{W} \right)^2$$

Note, the absolute C may vary as high as 20% due to process variations

Accuracy of integrated capacitors

Perimeter imperfections effect the total capacitance:

$$C = C_A A$$

$$A = (x - 2\Delta x)(y - 2\Delta y)$$

$$= xy - 2x\Delta y - 2y\Delta x + 4\Delta x \Delta y$$

Assuming that $\Delta x = \Delta y = \Delta e$

$$A = xy - 2\Delta e(x + y) + 4(\Delta e)^2$$

$$A \approx xy - 2\Delta e(x + y)$$

$$\therefore C_e = -2\Delta e(x + y)$$


The relative error is

$$\varepsilon = C_e / C$$

$$= -2\Delta e(x + y) / xy$$

Then maximize the area and minimize the perimeter → use squares!!!

$C_A =$ capacitance per unit area

 


Capacitor Matching

- If we want to match the ratio of two caps C_1 and C_2

$$\frac{C_1}{C_2} = \frac{C_{1,ideal}(1 + e_1)}{C_{2,ideal}(1 + e_2)}$$

 - To minimize the error in the cap ratio, we need to have $e_1 = e_2$. This implies that the **Perimeter/Area** should be equal.
- Generally, we break up both caps C_1 and C_2 into **square** unit caps, C_u



Capacitor Matching

- If both C_1 and C_2 are integer multiples of C_u , then simply use I_1 unit caps for C_1 and I_2 unit caps for C_2

$$\frac{C_1}{C_2} = \frac{I_1 C_u}{I_2 C_u}$$

- If $C_1 = I_1 C_u$ and $C_2 = I_2 C_u + (1 + f) C_u$, where f is a fraction, then we want the non - unit cap, $C_{nu} = (1 + f) C_u$, to have equal

$\frac{\text{Perimeter}}{\text{Area}}$ as a unit cap.

- Why is the non - unit cap $(1 + f) C_u$?

Because we don't want a cap smaller than the unit cap, or bigger than $2C_u$. Overall, we want to use as many unit caps as possible, but none smaller than C_u .

Capacitor Matching

- How to size C_{nu} ?

$$\text{Define } N = 1 + f = \frac{A_{nu}}{A_u} = \frac{x_{nu} y_{nu}}{x_u^2}$$

$$\text{For matching } \frac{P_{nu}}{A_{nu}} = \frac{P_u}{A_u}$$

$$\frac{P_{nu}}{P_u} = \frac{A_{nu}}{A_u} = N = \frac{2(x_{nu} + y_{nu})}{4x_u}$$

$$x_{nu} + y_{nu} = 2Nx_u$$


$$\text{From } N \text{ definition } \Rightarrow x_{nu} = \frac{Nx_u^2}{y_{nu}}$$

Plugging this into the previous expression, we can solve for y_{nu}

$$y_{nu}^2 - 2Nx_u y_{nu} + Nx_u^2 = 0$$

$$y_{nu} = x_u \left(N \pm \sqrt{N^2 - N} \right)$$

 If you want $y_{nu} > x_{nu}$ choose "+", $y_{nu} < x_{nu}$ choose "-"



Capacitor Matching


- If $C_1 = I_1 C_u + (1 + f_1) C_u$ and $C_2 = I_2 C_u + (1 + f_2) C_u$
where $N_1 = 1 + f_1$ and $N_2 = 1 + f_2$

$$x_{nu1} = \frac{N_1 x_u^2}{y_{nu1}} \quad x_{nu2} = \frac{N_2 x_u^2}{y_{nu2}}$$
$$y_{nu1} = x_u \left(N_1 \pm \sqrt{N_1^2 - N_1} \right) \quad y_{nu2} = x_u \left(N_2 \pm \sqrt{N_2^2 - N_2} \right)$$

- Although, generally we have the flexibility to size C_u to set
 $C_1 = I_1 C_u$



Common Centroid Capacitor Layout

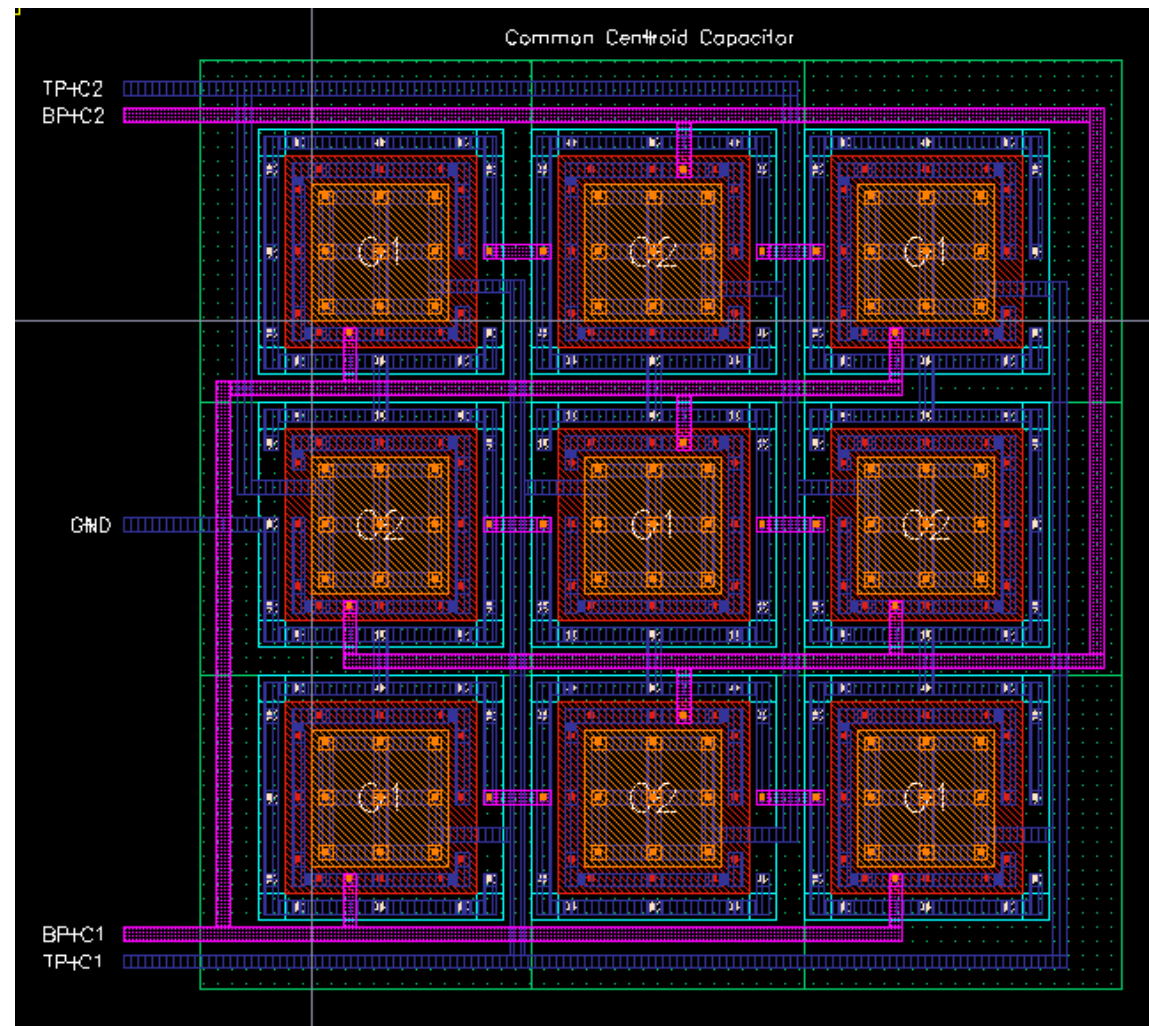- Unit capacitors are connected in parallel to form a larger capacitance
- Typically the ratio among capacitors is what matters
- The error in one capacitor is proportional to perimeter-area ratio
- Use dummies for better matching (See Razavi Book, page 752)



Approximate Common Centroid Structure

Jose Silva-Martinez

  


$$\begin{aligned} C_2 &= C_1 \\ C_3 &= 2C_1 \\ C_4 &= 4C_1 \\ C_5 &= 8C_1 \end{aligned}$$


“Floating” Capacitors

Be aware of **parasitic capacitors**

 
Polysilicon-Polysilicon: Bottom plate capacitance is comparable (10-30 %) with the poly-poly capacitance



 → **Metal1-Metal2:** More clean, but the capacitance per micrometer square is smaller. Good option for very high frequency applications ($C \sim 0.1$ - 0.3 pF).



 C_{P1} , C_{P2}'' are very small (1-5 % of C_1)
 C_{P2}' is around 10-50 % of C_1




C_{P2} is very small (1-5 % of C_1)

Analog Cell Layout Key Points


- Use transistors with the same orientation
- Minimize S/D contact area by stacking transistors (to reduce parasitic capacitance to substrate)
- Respect symmetries
- Use low resistive paths when current needs to be carried (to avoid parasitic voltage drops)
- Shield critical nodes (to avoid undesired noise injection)
- Include guard rings everywhere; e.g. Substrate/well should not have regions larger than 50 μm without guard protections (latchup issues)

Bipolar Transistors – Latchup

[Razavi]

 

Equivalent Circuit

 


- Potential for parasitic BJTs (Vertical PNP and Lateral NPN) to form a positive feedback loop circuit
- If circuit is triggered, due to current injected into substrate, then a large current can be drawn through the circuit and cause damage
- Important to minimize substrate and well resistance with many contacts/guard rings


Stacked Layout for Analog Cells

- ➡ Stack of elements with the same width
- ➡ Transistors with even number of parts have the source (drain) on both sides of the stack
- ➡ Transistors with odd number of parts have the source on one end and the drain on the other. *If matching is critical use dummies*
- ➡ If different transistors share a same node they can be combined in the same stack to share the area of the same node (*less parasitics*)
- ➡ Use superimposed or side by side stacks to integrate the cell

 
- M1 and M2 must match. Layout is interdigitized
- M3 and M4 must match. M6 must be wider by $4 \times M3$
- M7 must be $2 \times M5$
- Layout is an interconnection of 3 stacks; 2 for NMOS and 1 for PMOS
- Capacitor made by poly-poly





Not the best floorplan, but OK

 

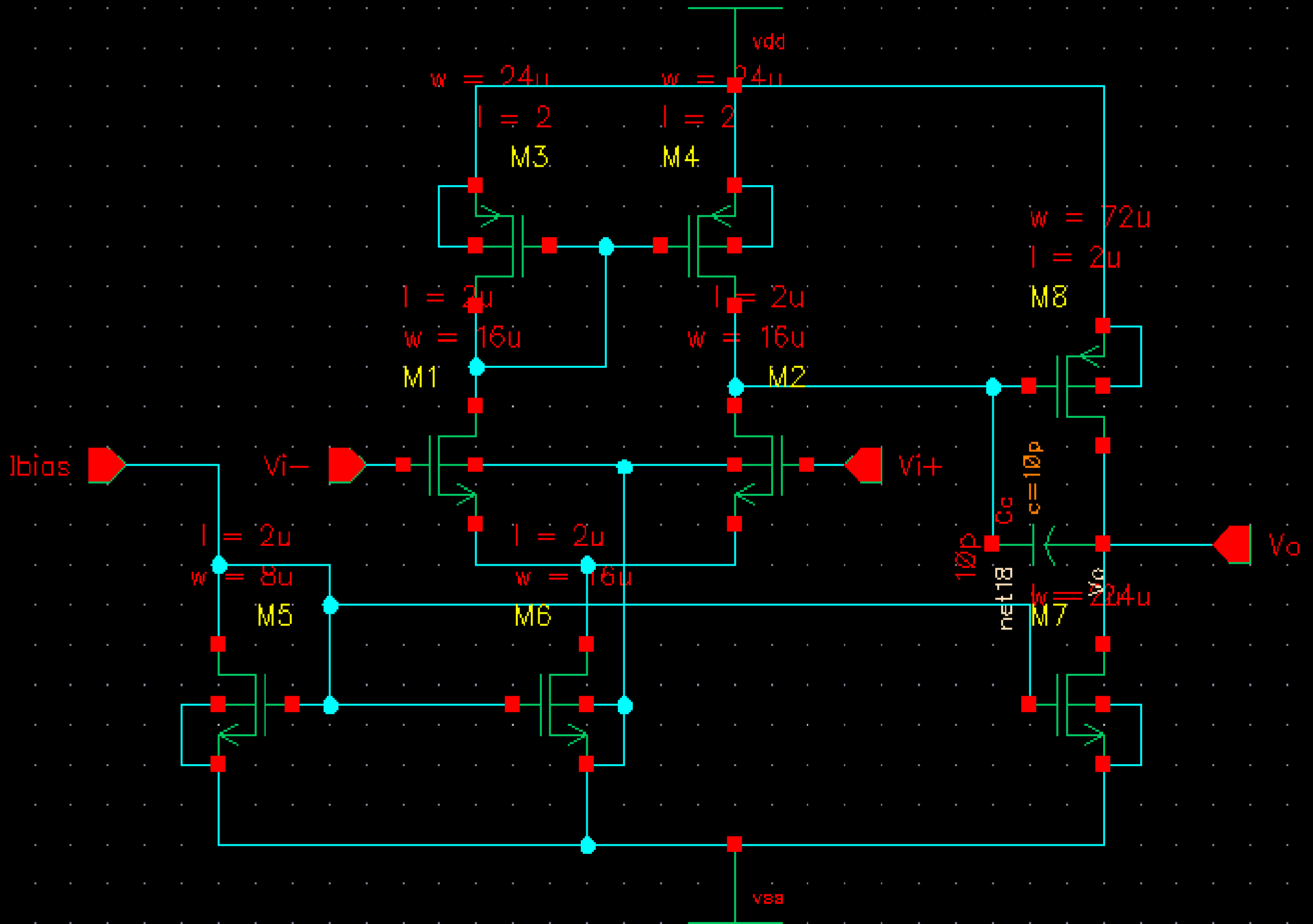Pay attention to your floor plan! It is critical for minimizing iterations: Identify the critical elements



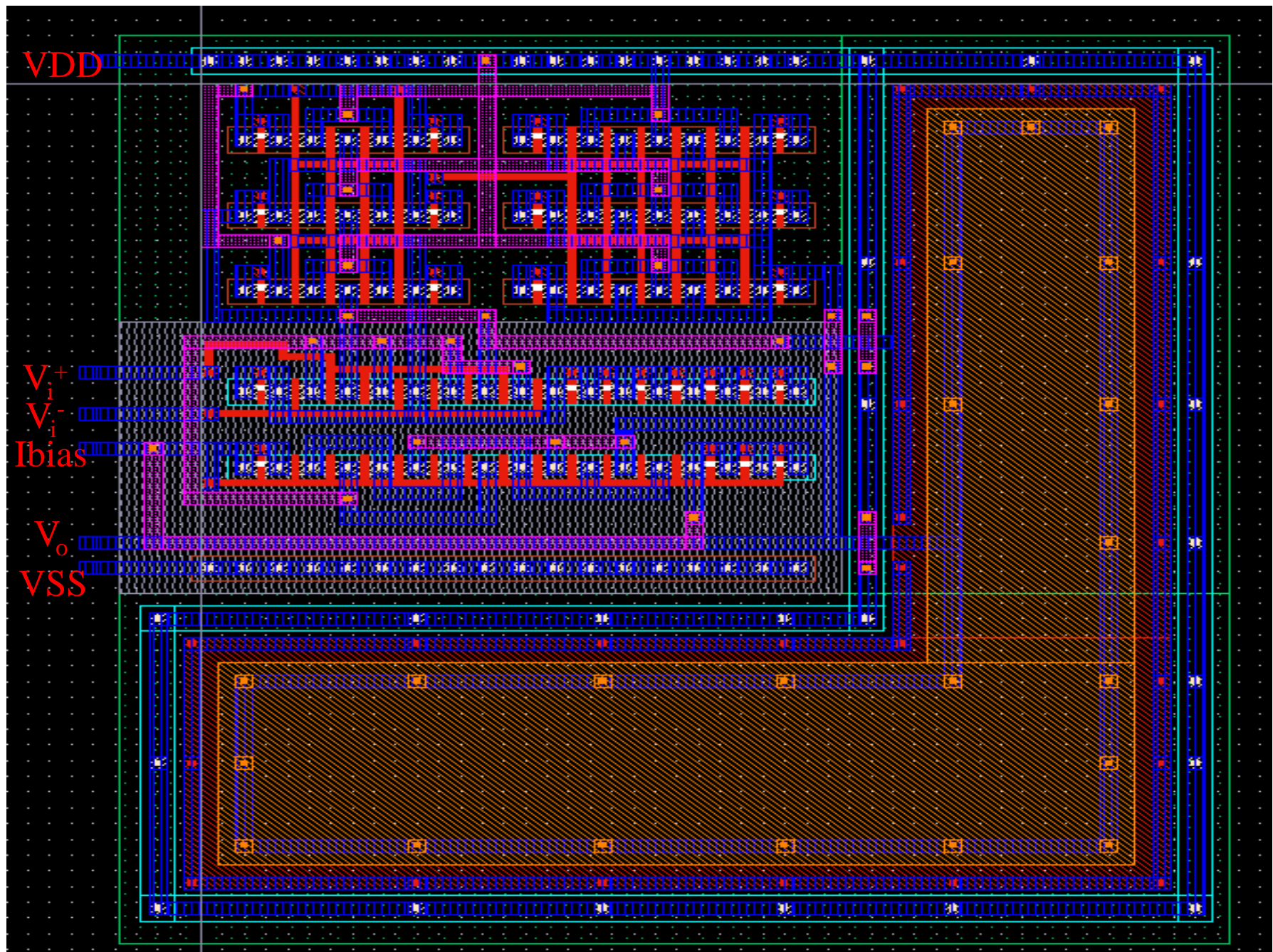

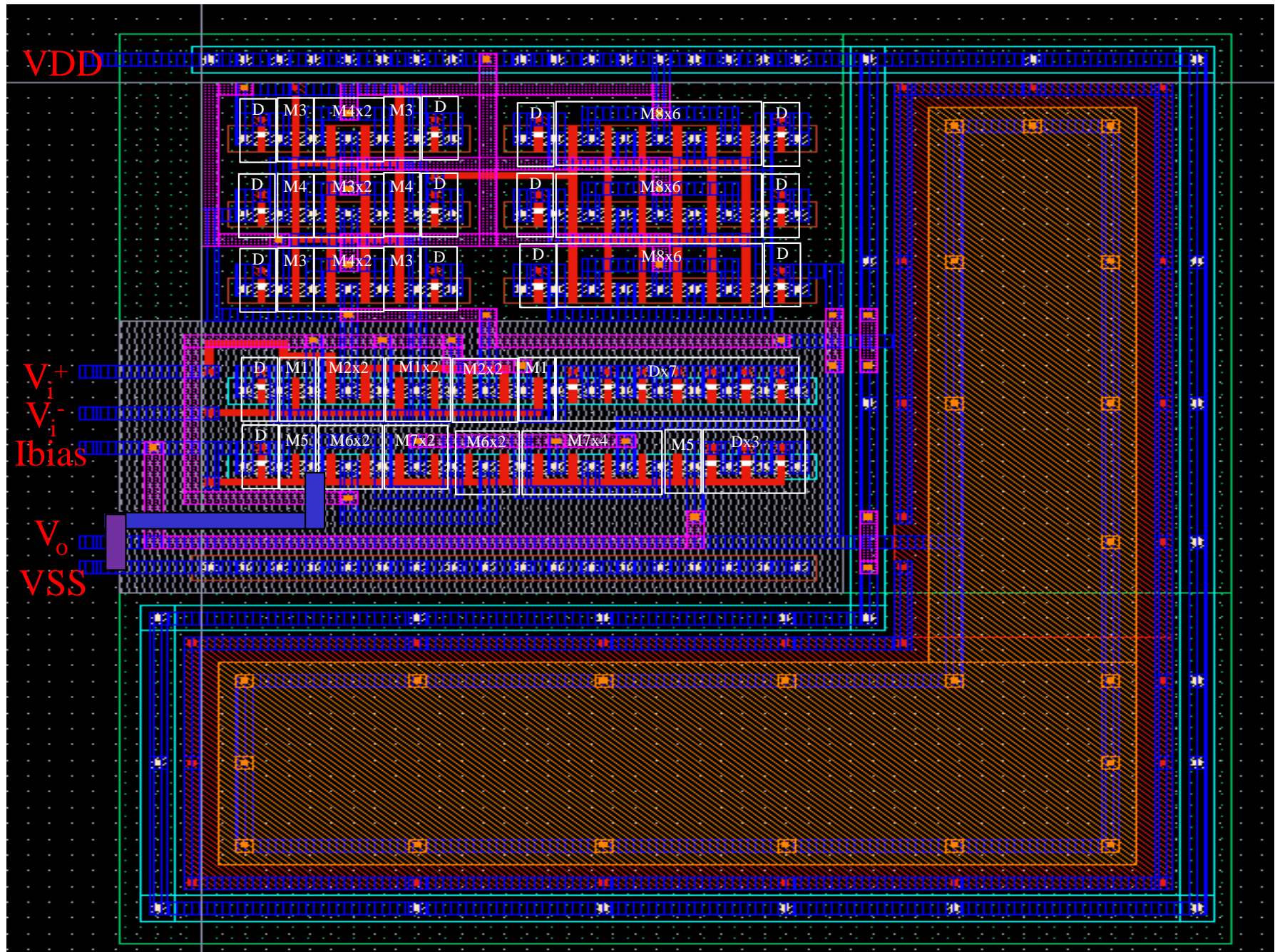

Following slides were provided by some of Dr. Silva's graduate students.

Special thanks to Fabian Silva-Rivas, Venkata Gadde, Marvin Onabajo, Cho-Ying Lu, Raghavendra Kulkarni and Jusung Kim

 


Figure: Layout of a single stage fully differential amplifier and its CMFB circuit.

1. I/p NMOS diff pair
2. PMOS (Interdigitated)
3. Resistors for V_{CM}
4. Capacitors (Common centroid)

Resistive network

Capacitive network
(Common centroid)

Fully differential
amplifier



 



Figure: Layout of a second order Active RC low-pass Filter (Bi-quad)

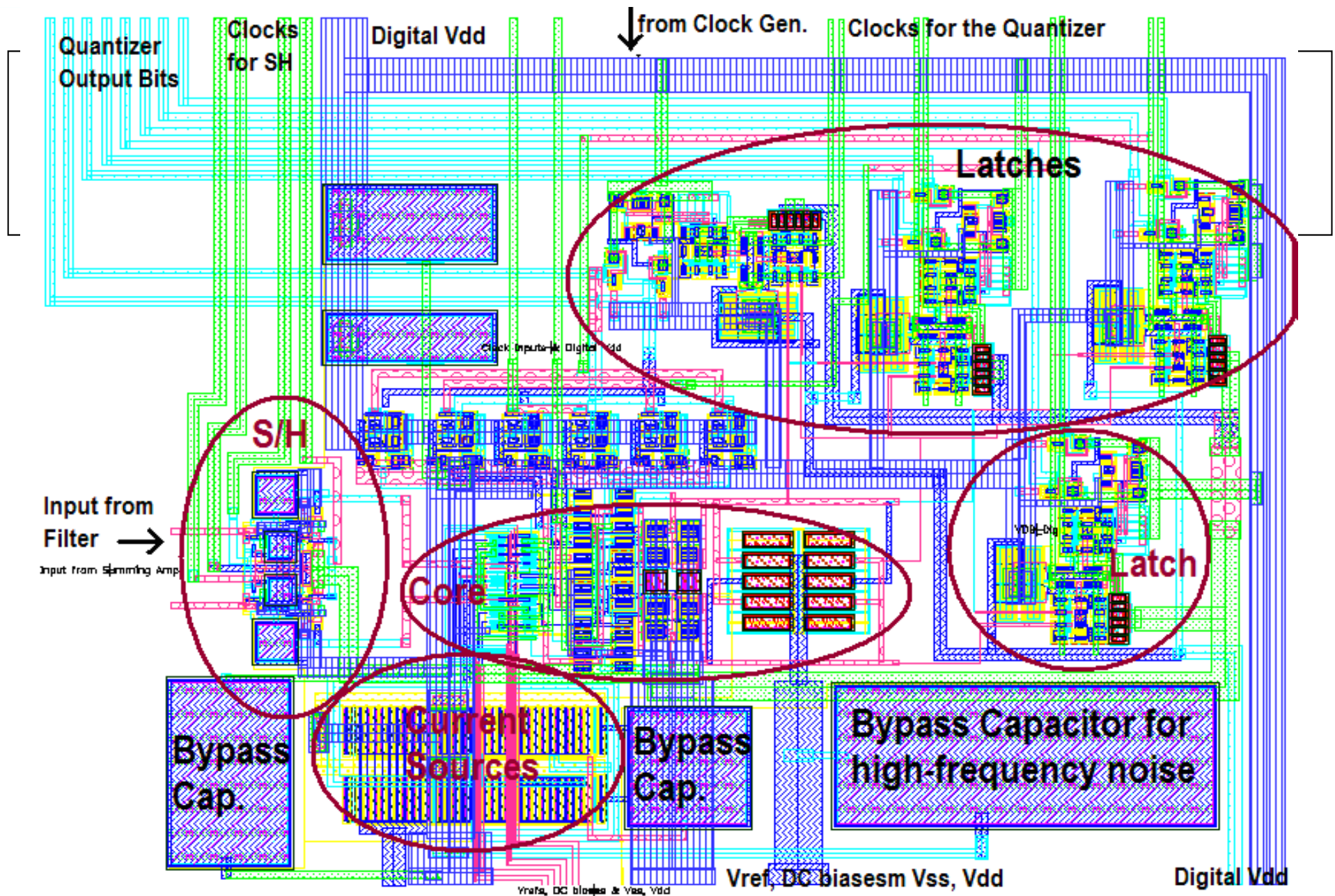


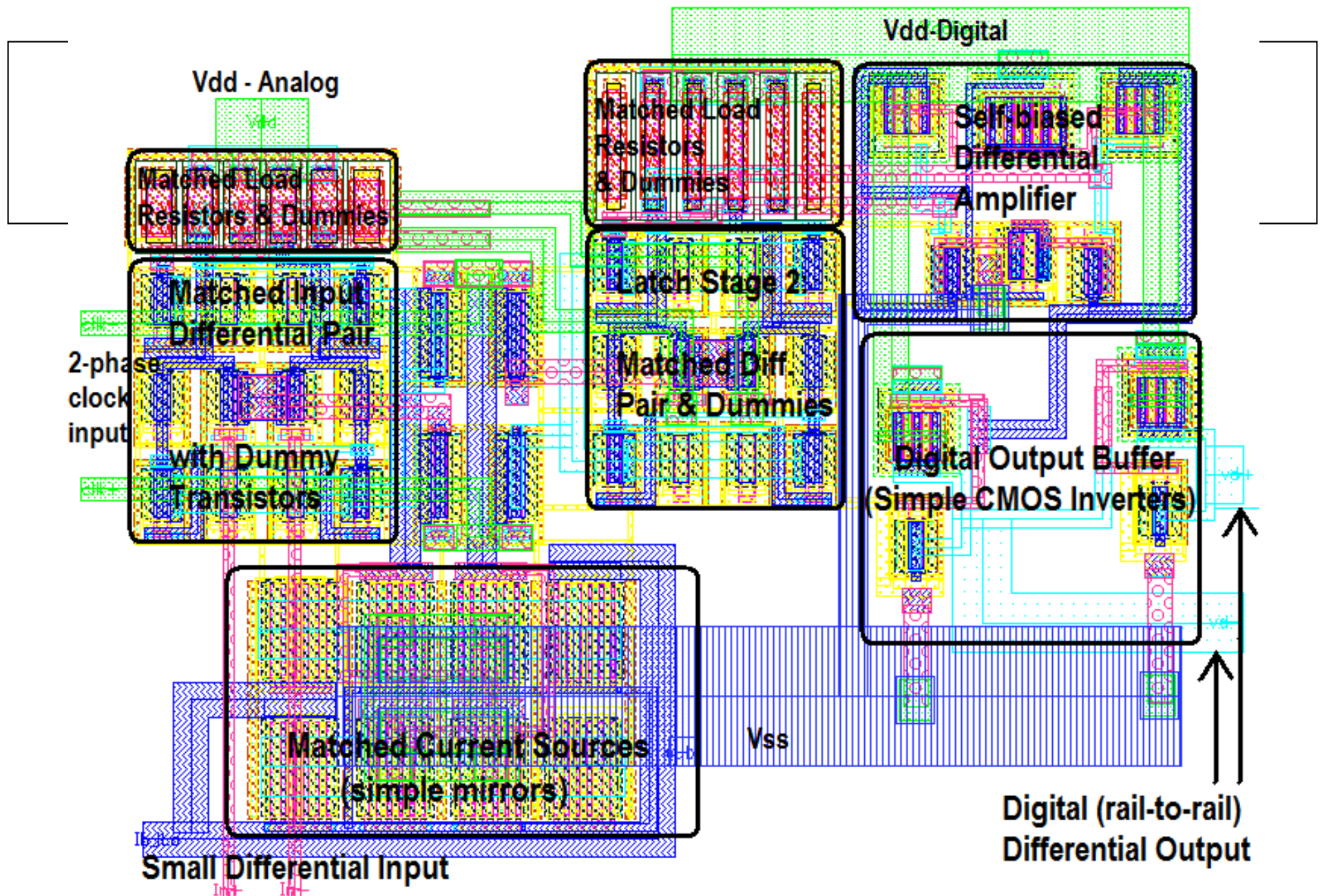
- **3-bit quantizer in Jazz 0.18 μ m CMOS technology**
- S/H: sample-and-hold circuit that is used to sample the continuous-input signal
- Core: contains matched differential pairs and resistors to create accurate reference levels for the analog-to-digital conversion
- Latches: store the output bits; provide interface to digital circuitry with rail-to-rail voltage levels




- **High-speed D-Flip-Flop in Jazz 0.18 μ m CMOS technology**
- Resolves a small differential input with $10\text{mV} < V_{p-p} < 150\text{mV}$ in less than 360ps
- Provides digital output (differential, rail-to-rail) clocked at 400MHz
- The sensitive input stage (1st differential pair) has a separate “analog” supply line to isolate it from the noise on the supply line caused by switching of digital circuitry

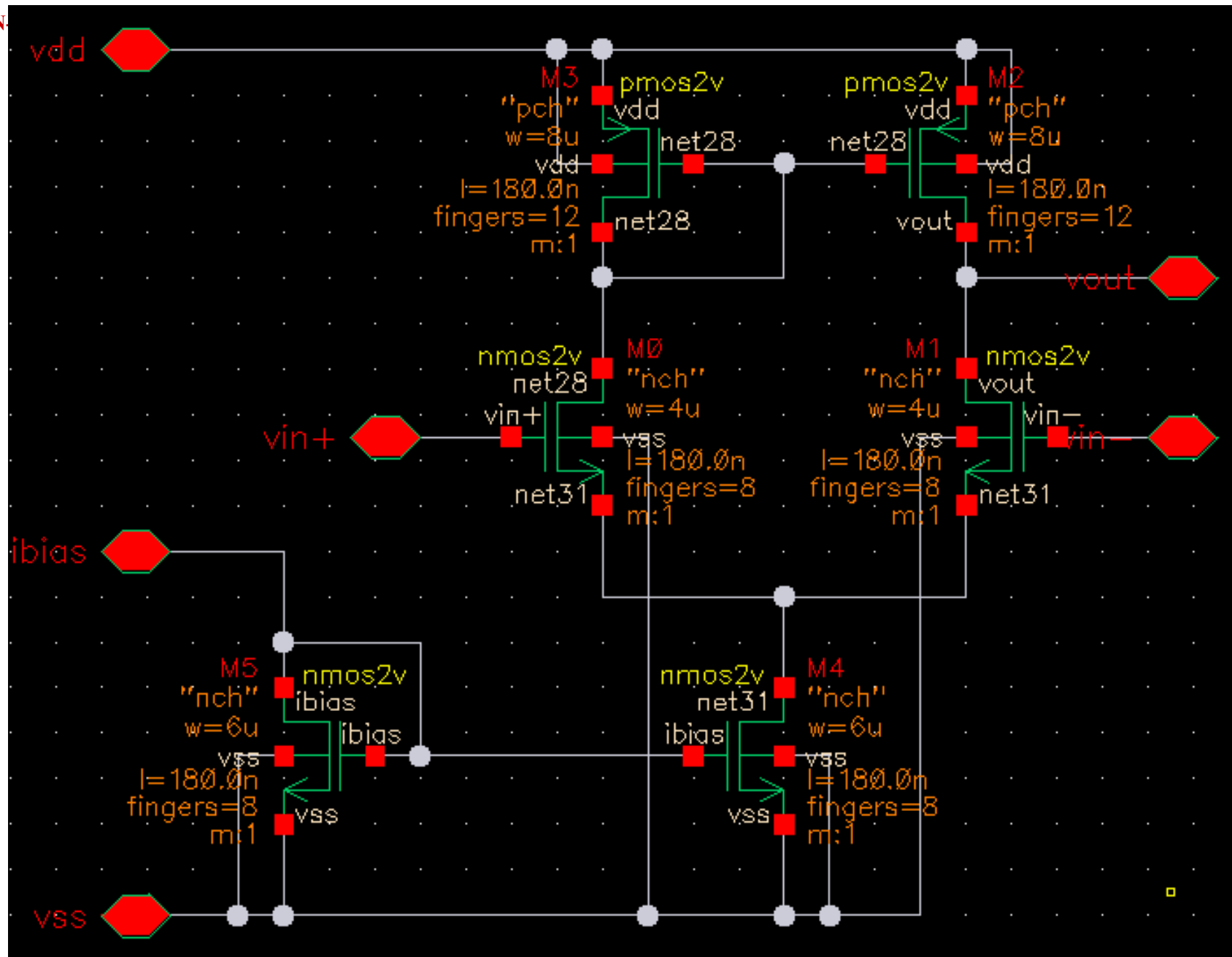

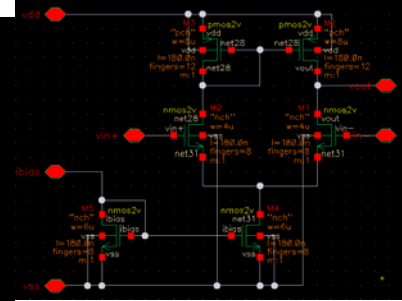
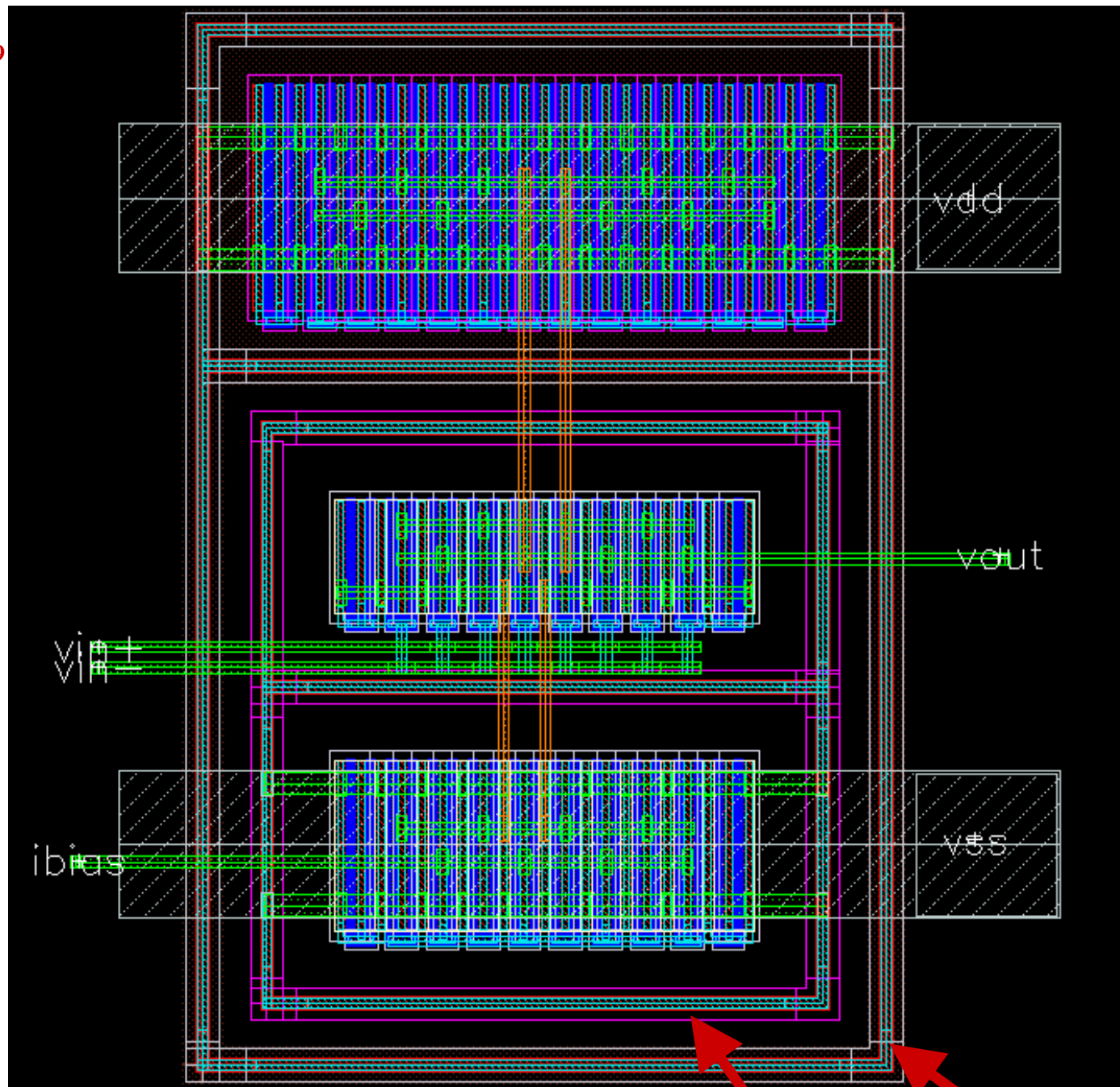
Design example (industrial quality): Simplest OTA



 Overall amplifier: Have a look on the guard rings and additional well!





 
 
BIAS: you may be able to see the dummies, symmetry and S/D connections



From downstairs

Differential pair

 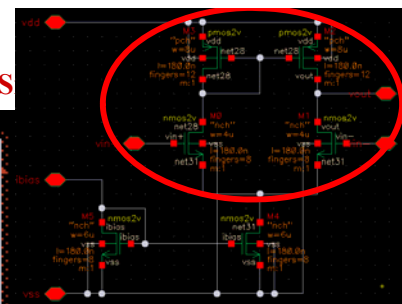

  

Details on the P-type current mirrors

Q-value of Spiral Inductors in CMOS Process

Most of the following slides were taken from


Seminar by: Park, Sang Wook

TAMU, 2003

What is Q?



$$Q \equiv \omega \frac{\text{energy stored}}{\text{average power dissipated}}$$



Simple Inductor Model:

 


$$Q = \frac{\omega L_s}{R_s}$$

Integrated Spiral Inductor "Pi" Model

  


  

Equivalent Circuit & Calculation

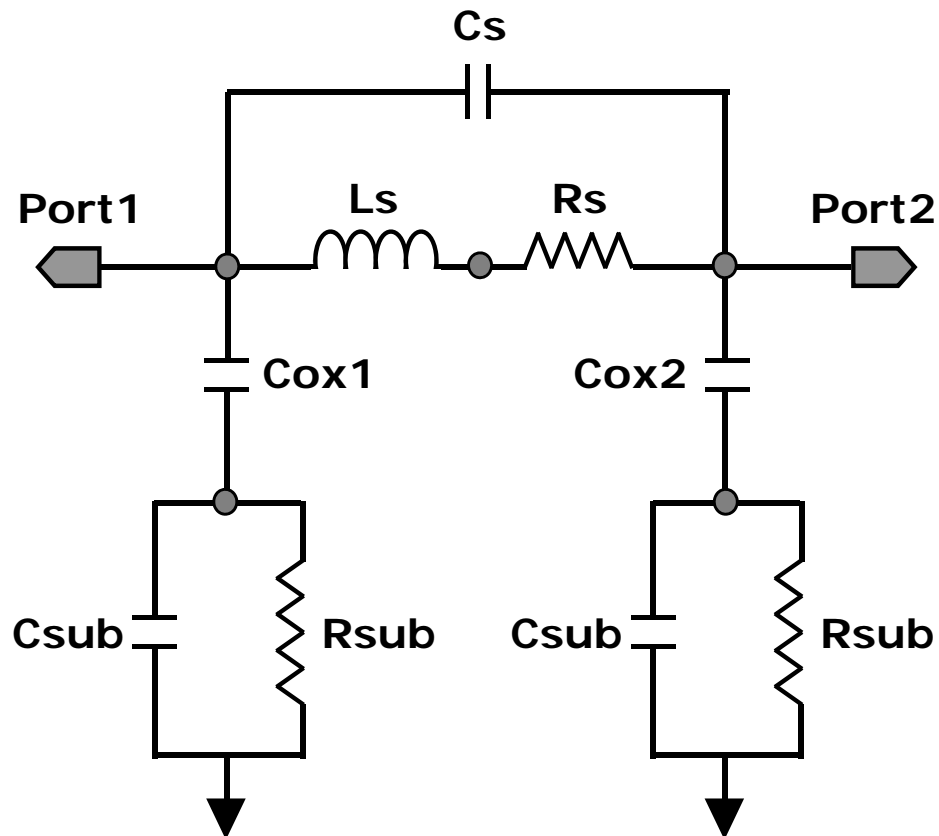


Equivalent Circuit

 


Parameter Calculation

Layout & Structure

 



Layout Split 1

Shape & Radius

 



 
- Shape : Octagon > Square
- Radius : 60 > 30




 
PGS (Patterned Ground Shield) material

PGS : Poly > Nwell > none > Metal1

 

  GS (Ground Shield) type


- **GS : Poly PGS > Poly(nonsal) SGS > Poly(nonsal) PGS > none**
PGS = patterned ground shield
SGS = solid ground shield

  Metal Stack

M 6



M 5/6

 

M 4/5/6




M 3/4/5/6


• **Stack : M6 > M5/6 > M4/5/6 > M3/4/5/6**

TAMU Mixed-Signal Research Chip

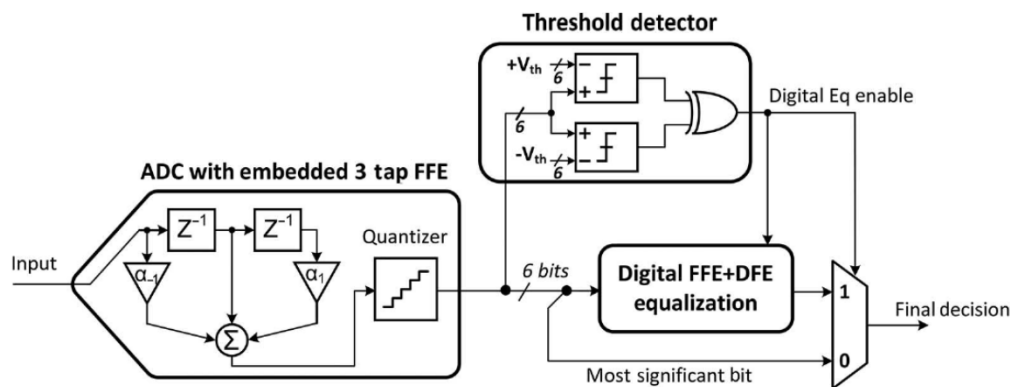
- A 10 Gb/s Hybrid ADC-Based Receiver w/ Embedded Analog and Per-Symbol Dynamically Enabled Digital Equalization



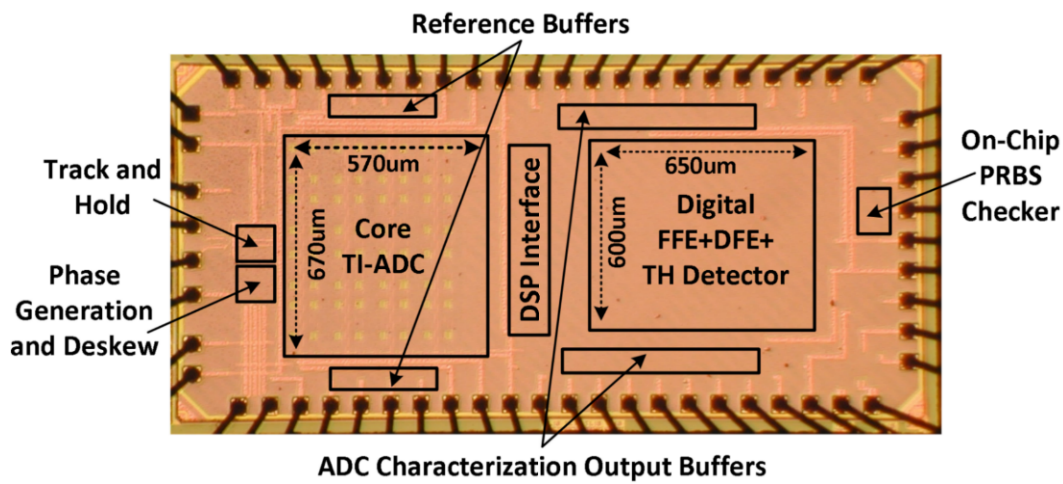- 10GS/s asynchronous SAR ADC with embedded 3-tap FFE
- Digital equalizer with 4-tap FFE and 3-tap DFE
- Fabricated in GP 65nm CMOS



BER w/ 36.4dB Loss Channel

 

A. Shafik et al, "A 10Gb/s Hybrid ADC-Based Receiver with Embedded 3-Tap Analog FFE and Dynamically-Enabled Digital Equalization in 65nm CMOS," ISSCC 2015.

A. Shafik et al, "A 10 Gb/s Hybrid ADC-Based Receiver With Embedded Analog and Per-Symbol Dynamically Enabled Digital Equalization," JSSC 2016. 77

Next Time

- Current Mirrors