

# EE105 – Fall 2014

## Microelectronic Devices and Circuits

Prof. Ming C. Wu


wu@eecs.berkeley.edu

511 Sutardja Dai Hall (SDH)



### Small-Signal Operation

### MOSFET Small-Signal Model - Summary

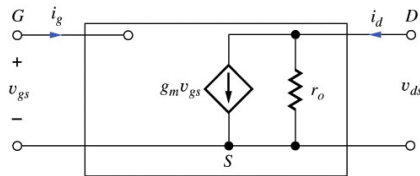

- Since gate is insulated from channel by gate-oxide input resistance of transistor is infinite.
- Small-signal parameters are controlled by the Q-point.
- For the same operating point, MOSFET has lower transconductance and an output resistance that is similar to the BJT.

$$I_G = 0$$

$$I_D = \frac{K_n}{2} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS})$$

**Transconductance:**

$$g_m = \frac{2I_D}{V_{GS} - V_{TN}} = \sqrt{2K_n I_D}$$

**Output resistance:**


$$r_o = \frac{1}{g_o} = \frac{1 + \lambda V_{DS}}{\lambda I_D} \approx \frac{1}{\lambda I_D}$$

**Amplification factor for  $\lambda V_{DS} \ll 1$ :**

$$\mu_f = g_m r_o = \frac{1 + \lambda V_{DS}}{\lambda I_D} \approx \frac{1}{\lambda} \sqrt{\frac{2K_n}{I_D}}$$


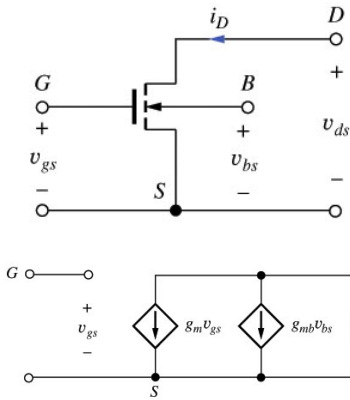
## MOSFET Small-Signal Operation Body Effect in Four-terminal MOSFETs



Drain current depends on threshold voltage which in turn depends on  $v_{SB}$ .  
Back-gate transconductance is:

$$g_{mb} = \left. \frac{\partial i_D}{\partial v_{BS}} \right|_{Q\text{-point}} = - \left. \frac{\partial i_D}{\partial v_{SB}} \right|_{Q\text{-point}}$$


$$g_{mb} = - \left( \frac{\partial i_D}{\partial V_{TN}} \right) \left( \frac{\partial V_{TN}}{\partial v_{SB}} \right) \bigg|_{Q\text{-point}} = -(-g_m \eta) = g_m \eta$$

$0 < \eta < 3$  is called the back-gate transconductance parameter.

bulk terminal is a reverse-biased diode. Hence, no conductance from the bulk terminal to other terminals.


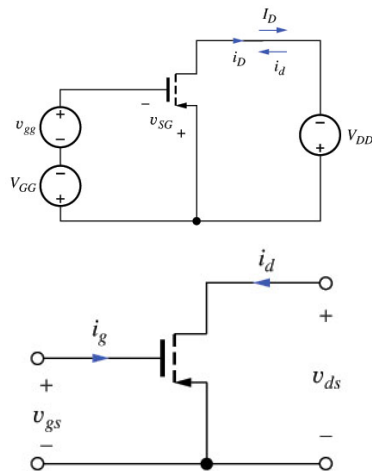
## MOSFET Small-Signal Operation Small-Signal Model for PMOS Transistor




- For a PMOS transistor


$$v_{SG} = V_{GG} - v_{gg}$$

$$i_D = I_D - i_d$$

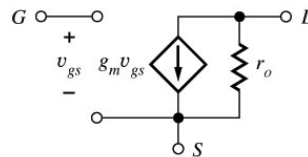- Positive signal voltage  $v_{gg}$  reduces source-gate voltage of the PMOS transistor causing decrease in total current exiting the drain, equivalent to an increase in the signal current entering the drain.
- The NMOS and PMOS small-signal models are the same!



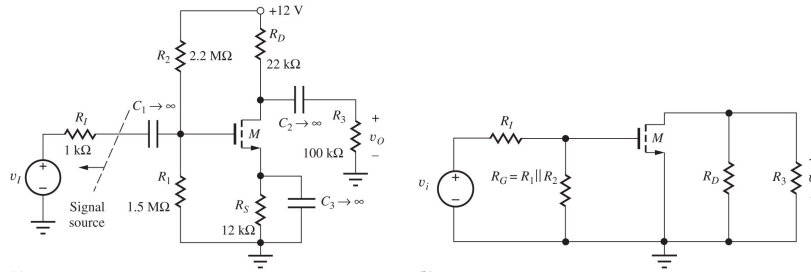
## Common-Source Amplifiers Small-Signal Analysis - ac Equivalent Circuit



- **ac equivalent circuit is constructed by assuming that all capacitances have zero impedance at signal frequency and dc voltage sources are ac ground.**


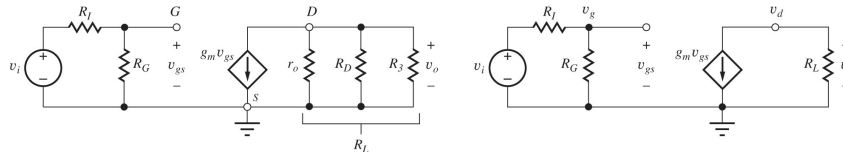
## Common-Source Amplifiers Small-Signal Equivalent Circuit




- **Input voltage is applied to the gate terminal**
- **Output signal appears at the drain terminal**
- **Source is *common* to both input and output signals**  
Thus circuit is termed a **Common-Source (C-S) Amplifier**.
- **The terminal gain of the C-S amplifier is the gain from the gate terminal to the drain terminal**

$$A_{vt}^{CE} = \frac{v_d}{v_g} = -g_m R_L \quad R_L = r_o \parallel R_D \parallel R_3$$


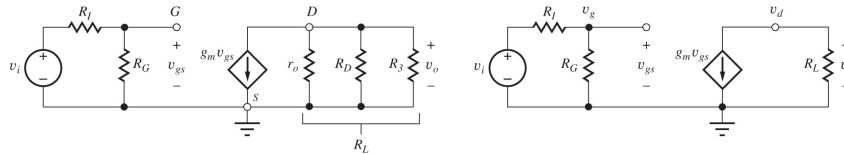
## Common-Source Amplifiers Input Resistance and Signal-Source Gain



Define  $R_{iG}$  as the input resistance looking into the base of the transistor.  
 $R_{in}$  is the resistance presented to  $v_i$

$$R_{iG} = \frac{v_g}{i_i} = R_G$$

$$R_{in} = R_I + R_G$$

The signal source voltage gain is:

$$A_v^{CS} = \frac{v_o}{v_i} = \frac{v_o}{v_g} \frac{v_g}{v_i} = A_{vt}^{CS} \frac{R_G}{R_I + R_G}$$

$$A_v^{CS} = -g_m R_L \left( \frac{R_G}{R_I + R_G} \right)$$



## Common-Source Amplifiers “Rule of Thumb” Design Estimate

$$A_v^{CS} = -g_m R_L \left( \frac{R_G}{R_I + R_G} \right) \cong A_{vt}^{CS} \quad A_{vt}^{CS} = -g_m R_L \quad R_L = r_o \parallel R_D \parallel R_3$$

Typically:  $r_o \gg R_D$  and  $R_3 \gg R_D$

$$A_v^{CS} \cong -g_m R_D = -\frac{I_D R_D}{\left( \frac{V_{GS} - V_{TN}}{2} \right)}$$

$I_D R_D$  represents the voltage dropped across drain resistor  $R_D$

A typical design point is  $I_D R_D = \frac{V_{DD}}{2}$  with  $V_{GS} - V_{TN} = 1 \text{ V}$

$$\therefore A_v^{CS} \cong -V_{DD}$$

Our rule-of-thumb estimate for the C-S amplifier:


the voltage gain equals the power supply voltage.

Note that this is 10 times smaller than that for the BJT!



## Common-Source Amplifiers Voltage Gain Example

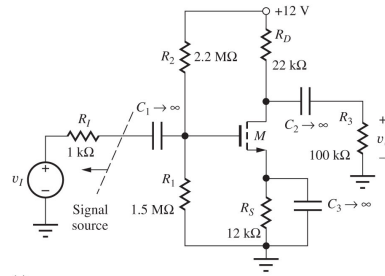- **Problem:** Calculate voltage gain, input resistance and maximum input signal level for a common-source amplifier with a specified Q-point
- **Given data:**  $K_n = 0.50 \text{ mA/V}^2$ ,  $V_{TN} = 1 \text{ V}$ ,
- $\lambda = 0.0133\text{V}^{-1}$ , Q-point is (0.241 mA, 3.81 V)
- **Assumptions:** Transistor is in the active region. Signals are low enough to be considered small signals.
- **Analysis:**




$$g_m = \sqrt{2K_n I_D (1 + \lambda V_{DS})} = 0.503 \text{ mS} \quad r_o = \frac{\lambda^{-1} + V_{DS}}{I_D} = 328 \text{ k}\Omega$$

$$R_G = R_1 \parallel R_2 = 892 \text{ k}\Omega \quad R_L = r_o \parallel R_D \parallel R_3 = 17.1 \text{ k}\Omega$$


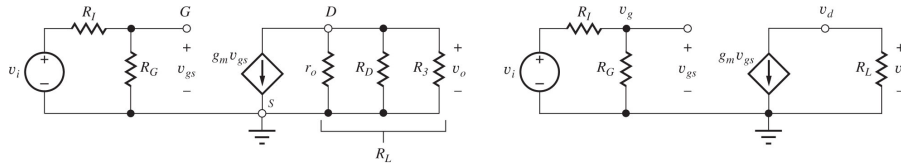
## Common-Source Amplifiers Voltage Gain Example (cont.)



$$g_m = 0.503 \text{ mS} \quad r_o = 328 \text{ k}\Omega \quad R_G = 892 \text{ k}\Omega \quad R_L = 17.1 \text{ k}\Omega$$

$$A_v^{CS} = -g_m R_L \left( \frac{R_G}{R_f + R_G} \right) = -0.503 \text{ mS} (17.1 \text{ k}\Omega) \left( \frac{892 \text{ k}\Omega}{1 \text{ k}\Omega + 892 \text{ k}\Omega} \right) = -8.60 (0.999) = -8.59$$


$$R_{in} = R_f + R_G = 893 \text{ k}\Omega \quad v_{gs} = v_i \left( \frac{R_G}{R_f + R_G} \right) \rightarrow |v_i| \left( \frac{R_G}{R_f + R_G} \right) \leq 0.2 (V_{GS} - V_{TN})$$

$$V_{GS} - V_{TN} \cong \sqrt{\frac{2I_D}{K_n}} = 0.982 \text{ V} \quad \therefore |v_i| \leq 0.2 (0.982 \text{ V}) \left( \frac{893 \text{ k}\Omega}{892 \text{ k}\Omega} \right) = 0.197 \text{ V}$$


Check the rule-of-thumb estimate:  $A_v^{CS} \cong -V_{DD} = -12 \text{ V}$  (ballpark estimate)


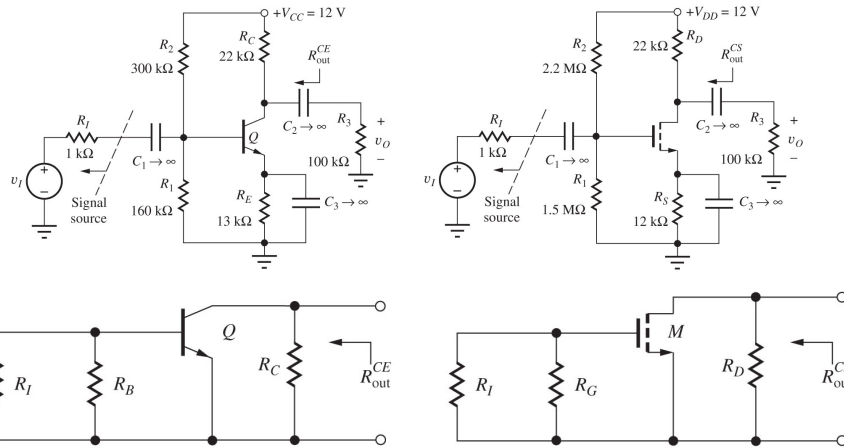
## C-E and C-S Amplifiers Output Resistance


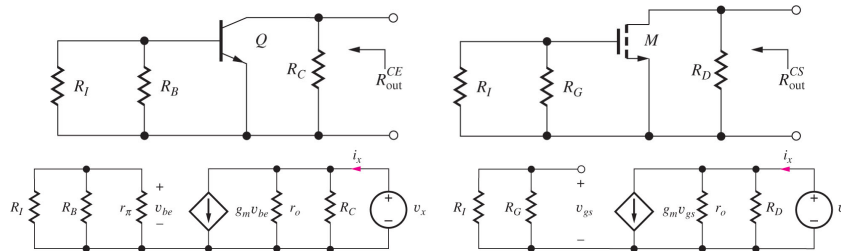
## C-E and C-S Amplifiers Output Resistance (cont.)



Apply test source  $v_x$  and find  $i_x$  (with  $v_i = 0$ )

$$v_{be} = 0 \rightarrow g_m v_{be} = 0$$

$$\therefore R_{out} = \frac{v_x}{i_x} = R_C \parallel r_o$$

$$R_{out} \cong R_C \text{ for } r_o \gg R_C$$

$$v_{gs} = 0 \rightarrow g_m v_{gs} = 0$$

$$\therefore R_{out} = \frac{v_x}{i_x} = R_D \parallel r_o$$

$$R_{out} \cong R_D \text{ for } r_o \gg R_D$$

**For comparable bias points, output resistances of C-S and C-E amplifiers are similar.**



## BJT and FET Small-Signal Model Summary

**TABLE 13.3**  
Small-Signal Parameter Comparison

PARAMETER	BIPOLAR TRANSISTOR	MOSFET
Transconductance $g_m$	$\frac{I_C}{V_T}$	$\frac{2I_D}{V_{GS} - V_{TN}} \cong \sqrt{2K_n I_D}$
Input resistance	$r_\pi = \frac{\beta_o}{g_m} = \frac{\beta_o V_T}{I_C}$	$\infty$
Output resistance $r_o$	$\frac{V_A + V_{CE}}{I_C} \cong \frac{V_A}{I_C}$	$\frac{1}{\lambda} + \frac{V_{DS}}{I_D} \cong \frac{1}{\lambda I_D}$
Intrinsic voltage gain $\mu_f$	$\frac{V_A + V_{CE}}{V_T} \cong \frac{V_A}{V_T}$	$2 \left( \frac{1}{\lambda} + V_{DS} \right) \cong \frac{1}{\lambda} \sqrt{\frac{2K_n}{I_D}}$
Small-signal requirement	$v_{be} \leq 0.005 \text{ V}$	$v_{gs} \leq 0.2(V_{GS} - V_{TN})$

dc i-v active region expressions for use with Table 13.3:

$$\text{BJT: } I_C = I_S \left[ \exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right] \left[ 1 + \frac{V_{CE}}{V_A} \right] \quad V_T = \frac{kT}{q}$$

$$\text{MOSFET: } I_D = \frac{K_n}{2} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS}) \quad K_n = \mu_n C_{ox} \frac{W}{L}$$

$$\text{JFET: } I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2 (1 + \lambda V_{DS})$$




## Common-Emitter / Common-Source Amplifiers Summary

	COMMON-EMITTER AMPLIFIER	COMMON-SOURCE AMPLIFIERS
Terminal gain $A_{vt}$	$-g_m R_L$	$-g_m R_L$
Rule-of-thumb estimate for $g_m R_L$	$-10V_{CC}$	$-V_{DD}$
Voltage gain $A_v$	$A_v = \frac{v_o}{v_i} = -g_m (R_{out} \parallel R_L) \left( \frac{R_{in}}{R_i + R_{in}} \right)$	
Input resistance $R_{in}$	$R_B \parallel r_\pi$	$R_G$
Output resistance $R_{out}$	$R_C \parallel r_o \cong R_C$	$R_D \parallel r_o \cong R_D$
Input signal phase	0.005 V	$0.2(V_{GS} - V_{TN})$ or $0.2(V_{GS} - V_P)$


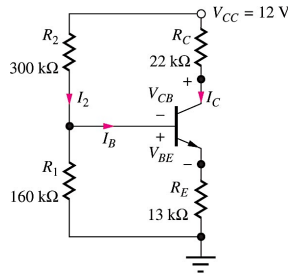
## Amplifier Power Dissipation

Static power dissipation in amplifiers is found from their dc equivalent circuits.




(a)

(a) Total power dissipated in BJT:

$$P_D = V_{CE} I_C + V_{BE} I_B$$

Total power supplied is:

$$P_S = V_{CC} (I_C + I_2)$$

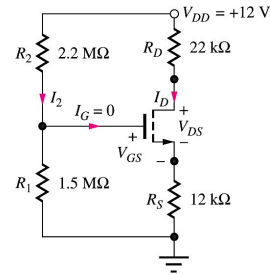

(b)

(b) Total power dissipated in MOSFET:



$$P_D = V_{DS} I_D$$

Total power supplied is:

$$P_S = V_{DD} (I_D + I_2)$$



## Amplifier Signal Range

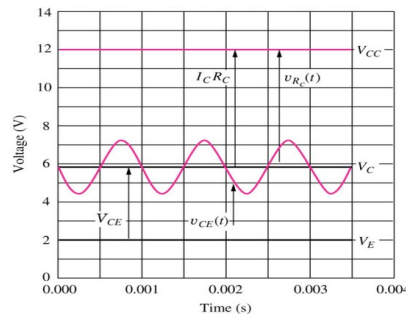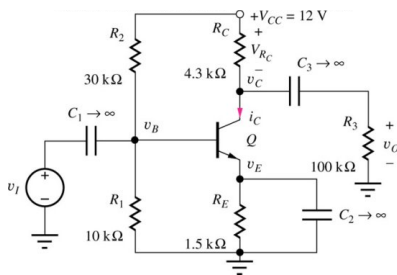

$v_{CE} = V_{CE} - V_m \sin \omega t$  where  $V_m$  is the output signal. Active region operation requires  $v_{CE} \geq v_{BE}$  So:  $V_m \leq V_{CE} - V_{BE}$

Also:  $v_{RC}(t) = I_C R_C - V_m \sin \omega t \geq 0$

$$\therefore V_m \leq \min [I_C R_C, (V_{CE} - V_{BE})]$$

Similarly for MOSFETs:

$$V_m \leq \min [I_D R_D, (V_{DS} - (V_{GS} - V_{TN}))]$$

