Learning Objectives

- a. Review the induced AC voltage output for a three phase AC generator as a function of time and as phasors.
- b. Define a three-wire Y-Y three phase circuit and a four-wire Y-Y three phase circuit
- c. Define the symbols for line to neutral voltages, line to line voltages, line currents, and phase impedances that will be used in three phase circuits
- d. Analyze Ohm's law in a three-wire Y-Y three phase circuit and in a four-wire Y-Y three phase circuit using a basic three phase generator that produces three balanced voltages which are connected to balanced loads
- e. Analyze Kirchhoff's current law in a three-wire Y-Y three phase circuit and in a four-wire Y-Y three phase circuit using a basic three phase generator that produces three balanced voltages with a Y connected balanced purely resistive loads

A three-phase source generates three separate ac voltage signals, all of the same peak value, but differing from each other by a phase separation of 120°. All commercial power in the U.S. is distributed and delivered as a three phase voltage. (Which raises the obvious question: *Why would we do such a thing?* -- We will defer that question until after we learn to analyze three-phase systems.)

Consider a three phase source that produces the three separate sinusoidal voltages shown below:



The voltages have the same peak value, the same frequency, and are offset by 120°. For example, if the RMS value of each waveform is $E_{AN} = E_{BN} = E_{CN}$, then the three waveforms shown above are

$$e_{AN} = \sqrt{2}E_{AN}\sin(\omega t)$$

$$e_{BN} = \sqrt{2}E_{BN}\sin(\omega t - 120^{\circ})$$

$$e_{CN} = \sqrt{2}E_{CN}\sin(\omega t - 240^{\circ}) = \sqrt{2}E_{CN}\sin(\omega t + 120^{\circ})$$

Our three voltages can be represented as phasors:

$$\overline{\mathbf{E}}_{\mathrm{AN}} = E_{AN} \angle 0^{\circ}$$

$$\overline{\mathbf{E}}_{\rm BN} = E_{\rm BN} \angle -120^{\circ}$$
$$\overline{\mathbf{E}}_{\rm CN} = E_{\rm CN} \angle 120^{\circ}$$

What is the sum of our three sinusoids $e_{AN} + e_{BN} + e_{CN}$ at any moment of time?

$$e_{AN} + e_{BN} + e_{CN} = \sqrt{2}E_{AN}\sin\left(\omega t\right) + \sqrt{2}E_{BN}\sin\left(\omega t - 120^\circ\right) + \sqrt{2}E_{CN}\sin\left(\omega t + 120^\circ\right)$$

If $E_{AN} = E_{BN} = E_{CN} = E$ this becomes

$$e_{AN} + e_{BN} + e_{CN} = \sqrt{2}E\left(\sin\left(\omega t\right) + \sin\left(\omega t - 120^\circ\right) + \sin\left(\omega t + 120^\circ\right)\right)$$

Using trig identities, it is not hard to show that the sum on the right is always equal to zero. Thus,

$$e_{AN} + e_{BN} + e_{CN} = 0$$

<u>The Y-Connected Generator</u> In the Y-connected generator, our three voltage sources above are connected as shown below.



Note that the negative terminals of the three sources are connected together at the point labeled *N*, called *the neutral*. Each of our three voltages in the arrangement above is termed a *phase voltage*. Our three phase Y-connected generator is connected to a load via three *lines*. We have labeled the phasor currents on each of these three lines as \bar{I}_A , \bar{I}_B and \bar{I}_C .

Note the labeling of points A, B and C in the picture above. You might have the physical three-phase Y-connected generator shown below, where you have access only to the lines labeled A, B and C. Specifically, it might be the case that you do not have access to the neutral point.



Since we only have access to the lines *A*, *B* and *C*, we are interested in the line voltages – the voltages between the lines – which we denote \overline{E}_{AB} , \overline{E}_{BC} and \overline{E}_{CA} . So, in the picture below, let's calculate the line voltage \overline{E}_{AB} .



By KVL we have

$$\overline{\mathbf{E}}_{AB} = E_{AN} \angle 0^{\circ} - E_{BN} \angle -120^{\circ}.$$

Since the RMS phase voltages are equal, let $E_{AN} = E_{BN} = E$, and our equation above becomes

$$\overline{\mathbf{E}}_{AB} = E \angle 0^{\circ} - E \angle -120^{\circ}$$

Shifting the right-hand side of the equation to rectangular coordinates, we have

$$\overline{E}_{AB} = E - \left\{ E \cos\left(-120^\circ\right) + jE \sin\left(-120^\circ\right) \right\}$$

Simplifying, we have

$$\overline{\mathbf{E}}_{AB} = E - \left\{ -E\left(\frac{1}{2}\right) + jE\left(\frac{\sqrt{3}}{2}\right) \right\}$$

and simplifying further,

$$\overline{\mathbf{E}}_{AB} = \left(\frac{3}{2}\right)E + j\left(\frac{\sqrt{3}}{2}\right)E$$

Converting this back to polar form yields the important result:

$$\overline{\mathrm{E}}_{AB} = \sqrt{3}E \ \angle 30^{\circ}$$

Using the same technique, we can solve for the other two line voltages:

$$\overline{\mathbf{E}}_{BC} = \sqrt{3}E \angle -90^{\circ}$$
$$\overline{\mathbf{E}}_{CA} = \sqrt{3}E \angle 150^{\circ}$$

So, for a Y-connected generator, if we know the phase voltages we can immediately get the line voltages, and vice versa:

Phase Voltages	Line Voltages
$\overline{\mathbf{E}}_{AN} = E \angle 0^{\circ} \blacksquare$	$\overline{E}_{AB} = \sqrt{3}E \angle 30^{\circ}$
$\overline{E}_{BN} = E \angle -120^{\circ}$	$\overline{E}_{BC} = \sqrt{3}E \angle -90^{\circ}$
$\overline{E}_{CV} = E \angle 120^\circ$	$\overline{E}_{CA} = \sqrt{3}E \angle 150^\circ$

Furthermore, there is no reason that the phase for \overline{E}_{AN} be fixed at zero. If the phase of \overline{E}_{AN} is θ , the relationships between phase and line voltages are:

Phase Voltages	Line Voltages
$\overline{E}_{AN} = E \angle \theta$	$\overrightarrow{E}_{AB} = \sqrt{3}E \angle \theta + 30^{\circ}$
$\overline{E}_{EN} = E \angle -120^\circ + \theta$	$\overrightarrow{\mathbf{E}}_{BC} = \sqrt{3}E \angle -90^\circ + \theta$
$\overline{E}_{CV} = E \angle 120^\circ + \theta$	$\Rightarrow \overline{E}_{CA} = \sqrt{3}E \angle 150^\circ + \theta$

1 <u>Example</u>: Consider the three phase system shown on the left. You are given one of the phase voltages:

$$\mathbf{E}_{AN} = 7620 \angle -18^{\circ} \mathrm{V}$$

Determine:

- a. **E**_{BN}
- b. **E***CN*
- c. The three line-to-line voltages

Solution:



The Y-Connected Generator With a Y-Connected Load

Suppose we connect a load to our Y-connected generator as shown below. A load in this configuration is, for obvious reasons, called a Y-connected load. We would like to analyze this circuit; i.e., we would like to determine the line currents and the various voltages.



In EE301 the load will always be balanced. That means, in the picture above, $Z_{an} = Z_{bn} = Z_{cn}$. Hmm... as far as analysis goes, this doesn't look too pretty, does it?

Suppose we could connect a wire between the points labeled *N* and *n* above, resulting in this circuit:



Would this circuit be easier to analyze? Yes! Much easier! For example, $I_A = \frac{V_{an}}{Z_{an}}$. But we can't just

put wires into our circuit to make analysis easier. Or can we?

Let's consider a concrete example. Suppose, in the figure above, with a wire connected between the points labeled *N* and *n*, we have $Z_{an} = Z_{bn} = Z_{cn} = 12 \Omega$ and $\mathbf{E}_{AN} = 120 \angle 0^\circ$. Then we can calculate $\bar{\mathbf{I}}_A$, $\bar{\mathbf{I}}_B$ and $\bar{\mathbf{I}}_C$ as:

$$I_A = 10 \angle 0^\circ$$
$$\overline{I}_B = 10 \angle -120^\circ$$
$$\overline{I}_C = 10 \angle 120^\circ$$

Then what is \overline{I}_N ?

$$\bar{I}_N = \bar{I}_A + \bar{I}_B + \bar{I}_C = 10\angle 0^\circ + 10\angle 120^\circ + 10\angle -120^\circ$$

But this is the same calculation we did at the top of page 2! Thus, $\overline{I}_N = 0$!!!

So, what's the point?

We can connect the wire from *N* to *n* without changing the circuit since no current flows in this wire. But the addition of this wire makes circuit analysis easier!

- 2 <u>Example</u>: In the circuit on the right, $\mathbf{E}_{AN} = 277 \angle -30^{\circ} \text{ V}$
 - a. Determine all of the phase voltages and line voltages
 - b. Determine the line currents

Solution:



Y-Y system definitions

Line voltages are the voltages between the lines A, B and C (ECA, EAB, EBC, Vca, Vab, Vbc). **Phase voltages** are the voltages across phases (EAN, EBN, ECN, VAN, VBN, VCN).

For the generator, EAN, EBN, ECN are the phase voltages.

For Δ loads, **phase voltage** and **line voltage** are the same thing.



3 <u>Example</u>: Consider the balanced circuit shown below.



- a. Determine θ_2 and θ_3
- b. Determine the line voltages
- c. Determine the line currents
- d. Repeat the problem if we remove the wire connecting N to n

It is worth reiterating again:

For Y loads, line current and phase current are the same.

$$\mathbf{I}_{a} = \mathbf{V}_{an} / \mathbf{Z}_{an}$$



You should have gathered from the symmetry that for a Y-Y balanced circuit, if we know one current, say \bar{I}_a , then we can immediately write down \bar{I}_b and \bar{I}_c . Specifically, if $\bar{I}_a = I \angle \theta$ then

$$\bar{\mathbf{I}}_b = I \angle \theta - 120^\circ$$
$$\bar{\mathbf{I}}_c = I \angle \theta + 120^\circ$$

<u>The Δ -connected Load</u> For fun and excitement, we sometimes connect out balanced load in a delta configuration:



Line currents are the currents in the line conductors.
 Phase currents are the currents through phases .

For EE301, the impedances on each branch of the delta are the same; i.e., the load is balanced..

Notice that in this configuration, the line currents (shown in green above) that appear at the load are <u>not</u> equal to the phase currents within the load.

Note that the line voltages that appear at the load <u>are equal</u> to the phase voltages within the load.

Again, note the distinction between Y-Y and Y- Δ configurations:

For Y-Y: the line currents equal the phase currents; the line voltages do not equal the phase voltages.

For Y- Δ : the line voltages equal the phase voltages; the line currents do not equal the phase currents.

Line/Phase Currents for a Delta Circuit

Line/Phase Currents for a Delta Circuit Relationship between line and phase currents

$\mathbf{I}_{ab} = \mathbf{V}_{ab} \ / \ \mathbf{Z}_{ab}$
$\mathbf{I}_{a}=\mathbf{I}_{ab}-\mathbf{I}_{ca}$
$\mathbf{I}_a = \sqrt{3}\mathbf{I}_{ab} \angle -30^\circ$



For a balanced Δ system, the magnitude of line current is 1.732 times the magnitude of the phase current and line current lags phase current by 30°. Therefore, given any current at a point in a balanced, 3-phase Δ system, you can determine the remaining 5 currents by inspection.

