

# **Electric Circuit Analysis using Simulink**


Bikramjit Goswami

Department of EEE

Assam Don Bosco University


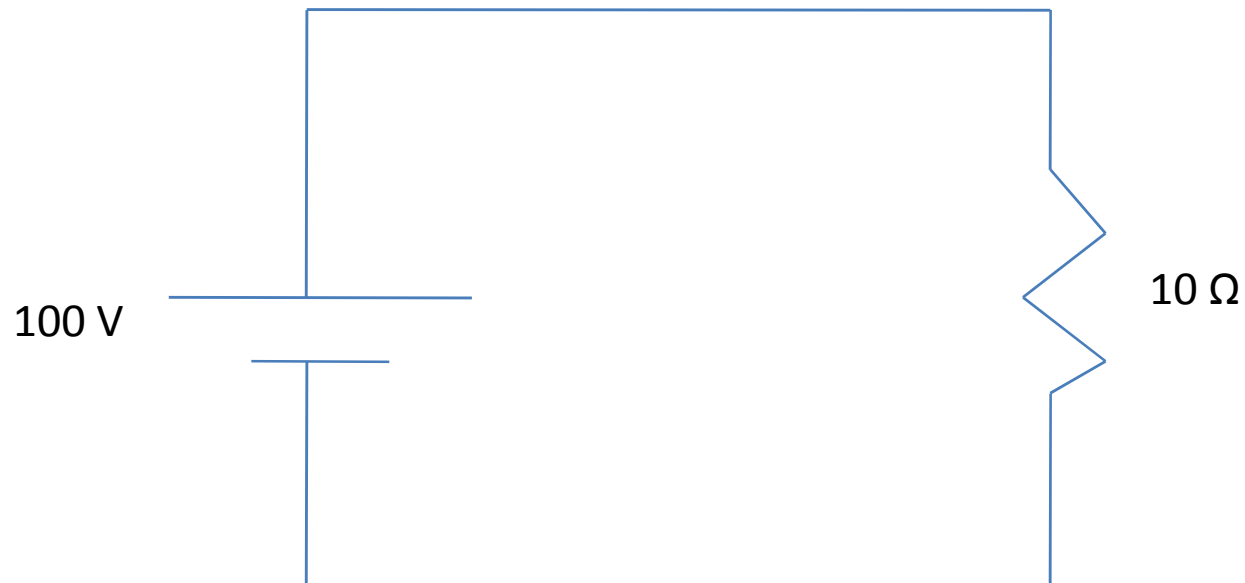
# To start with


Simulate the simple DC circuit shown below in Simulink and calculate the voltage, current & power in it.




# Steps

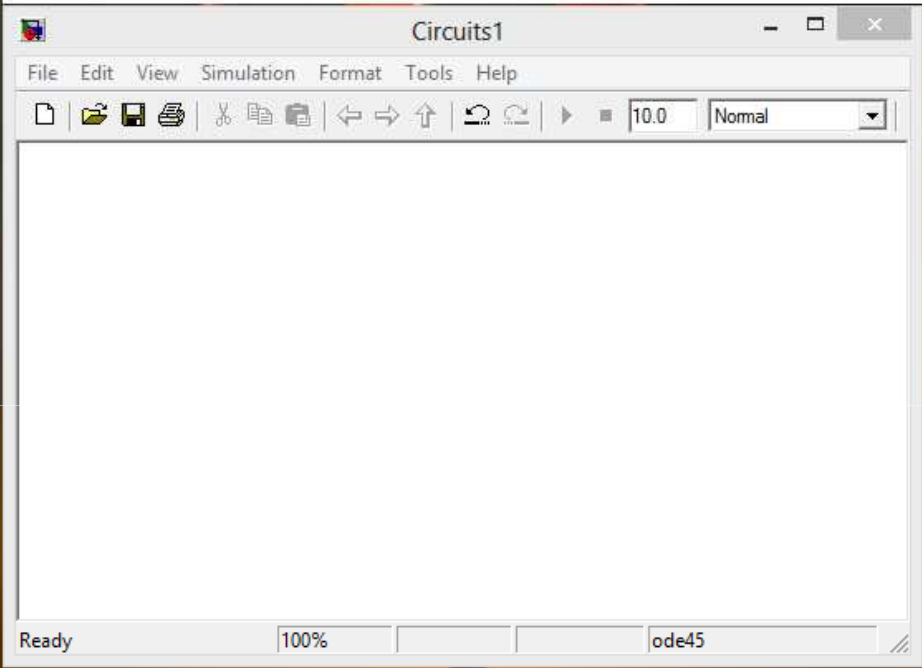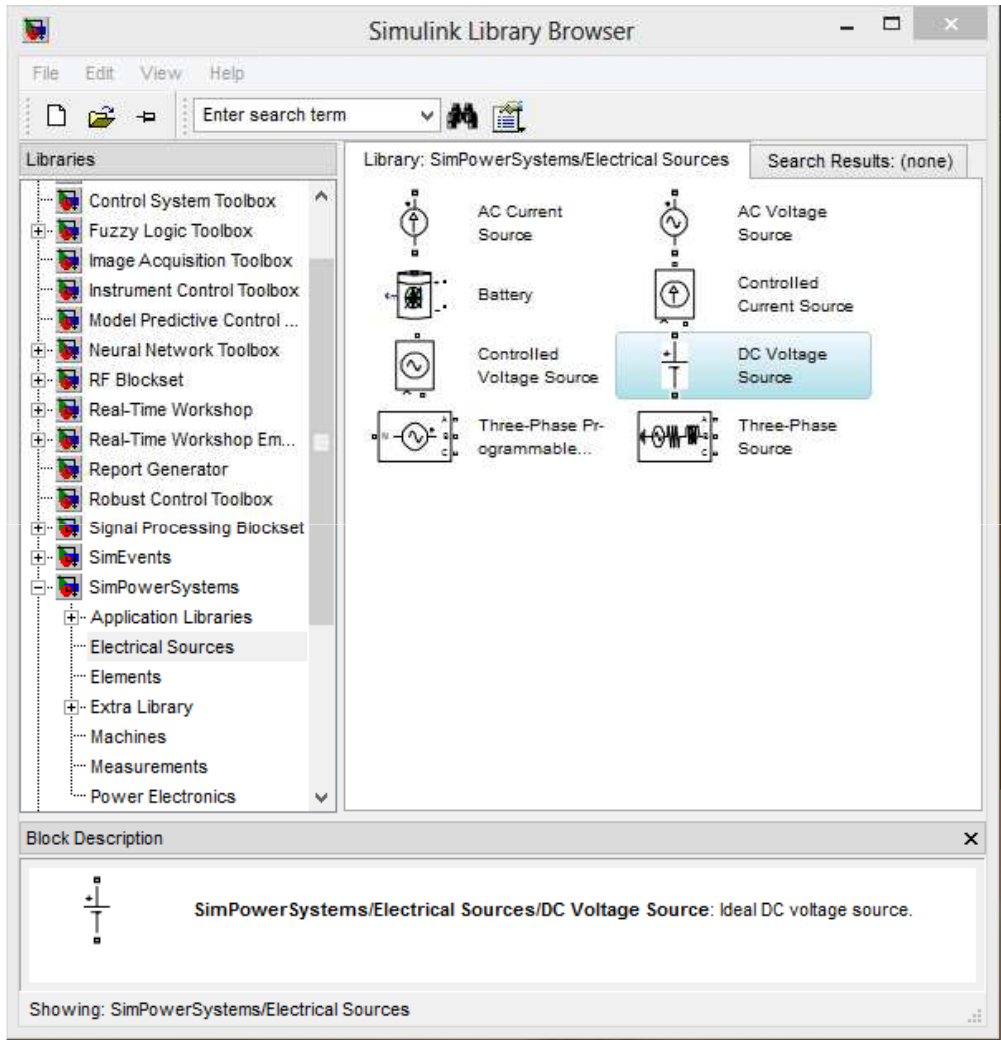- 1) Find the required components- (i) DC Voltage Source and (ii) Resistance.
- 2) Go to Simulink Library.
- 3) Choose SimPowerSystems in Simulink library.
- 4) Choose Electrical Sources in SimPowerSystems.
- 5) Choose DC Voltage Source and bring it to the Simulink Workspace.
- 6) Change the voltage to 100 V if required.




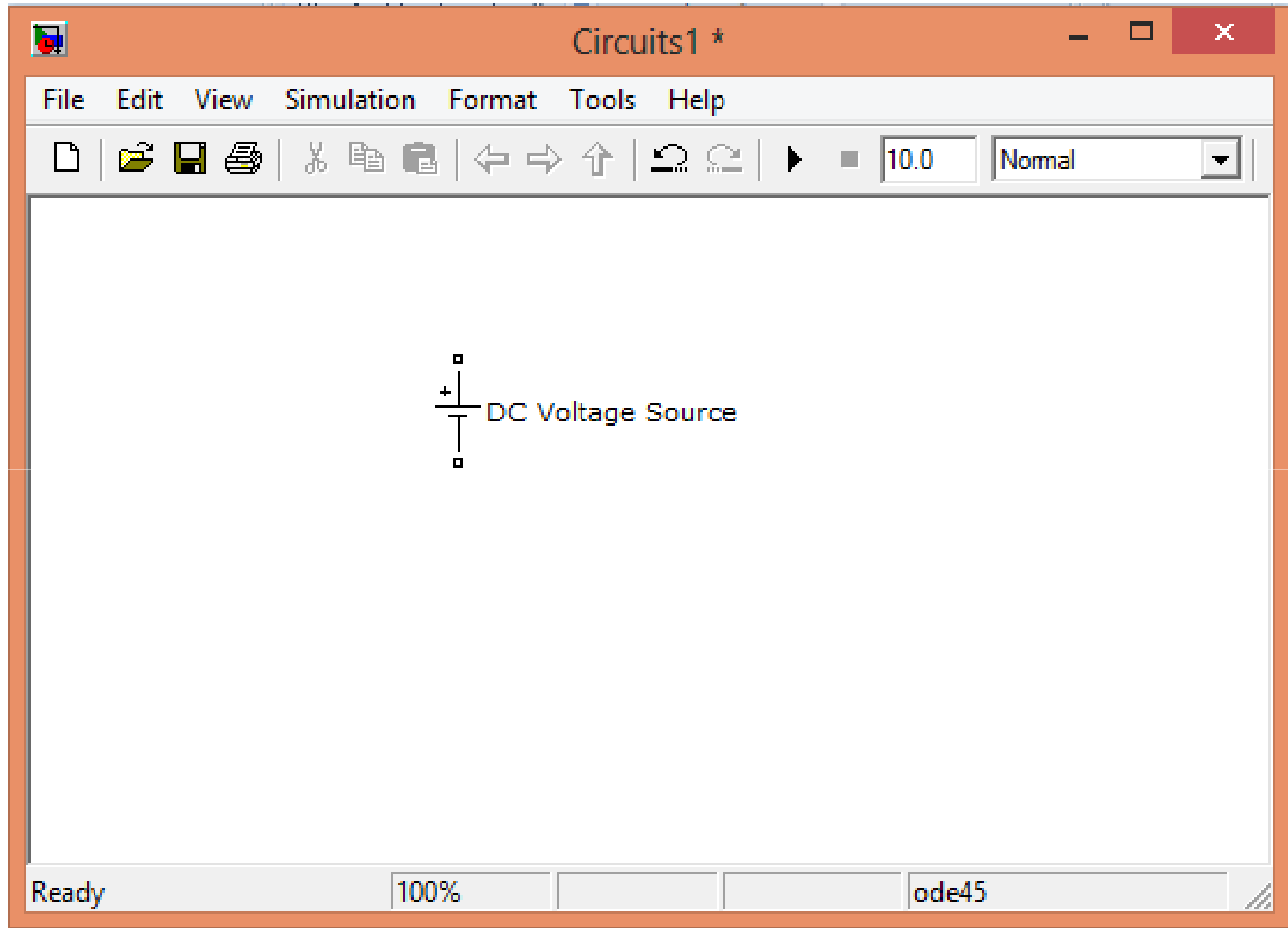

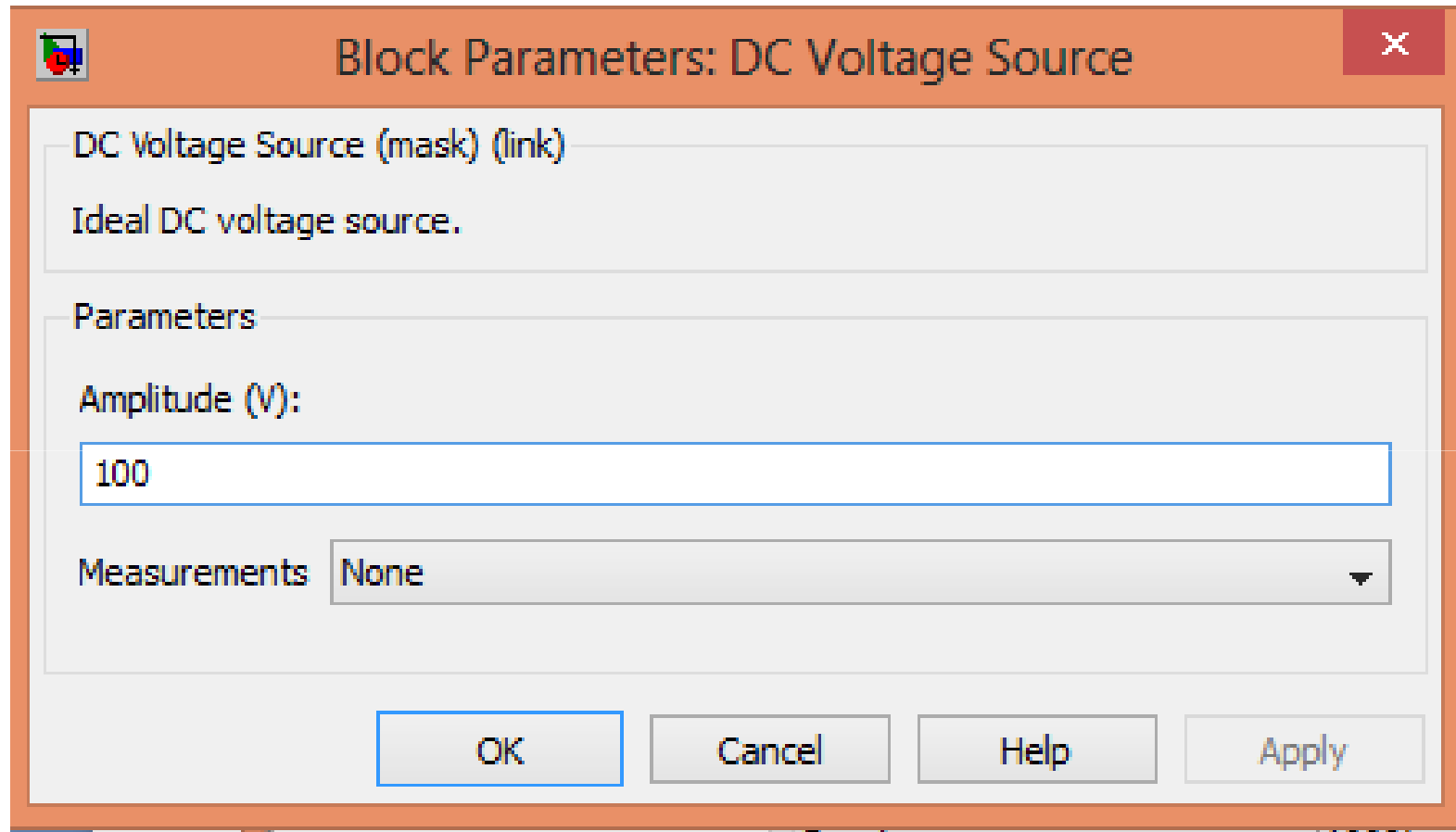



# Steps

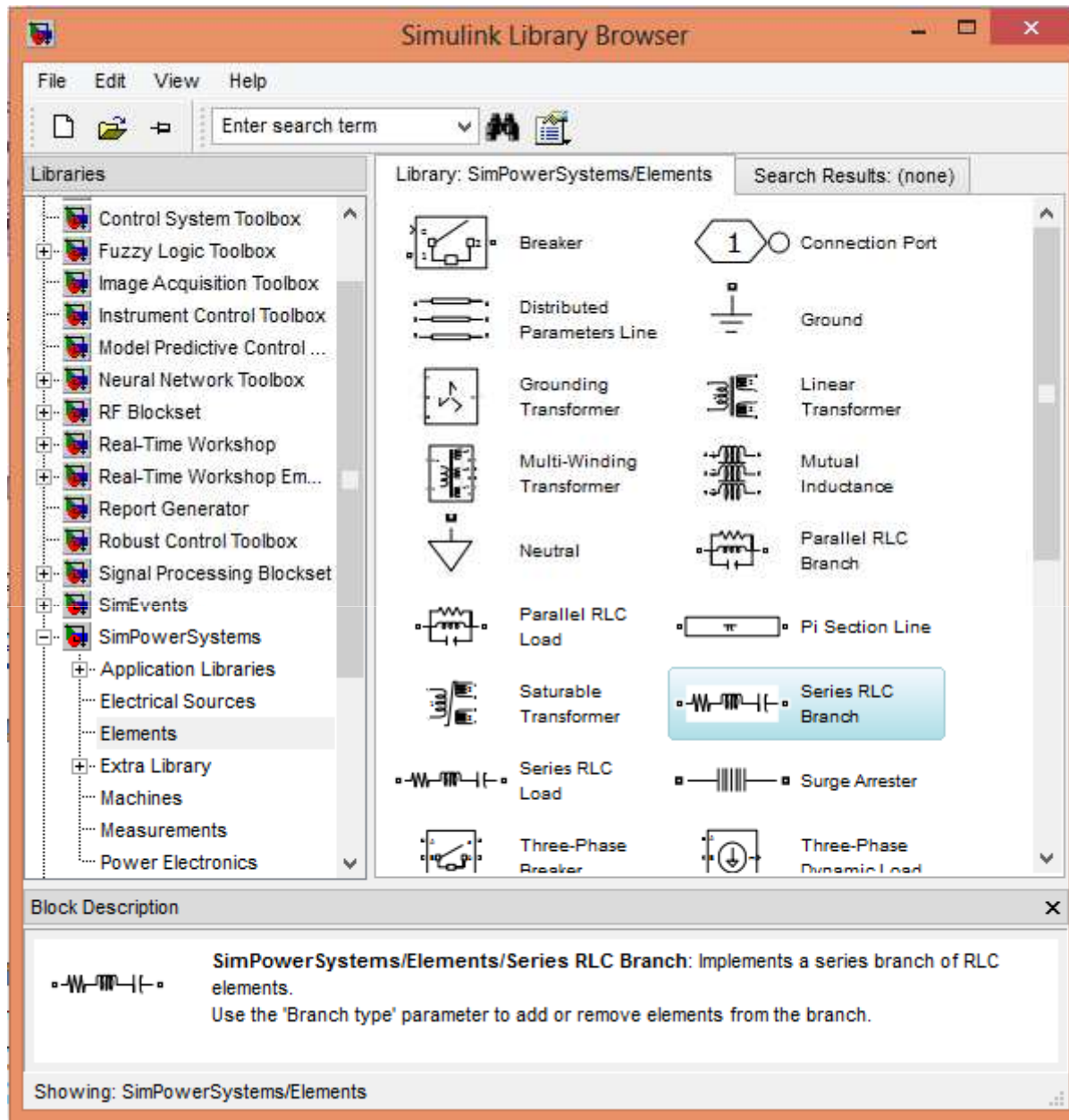- 7) Choose Elements in SimPowerSystems.
- 8) Choose Series RLC branch from Elements.
- 9) Double click on the RLC branch and change the block parameter to R.
- 10) Give it a value of 10 ohms.






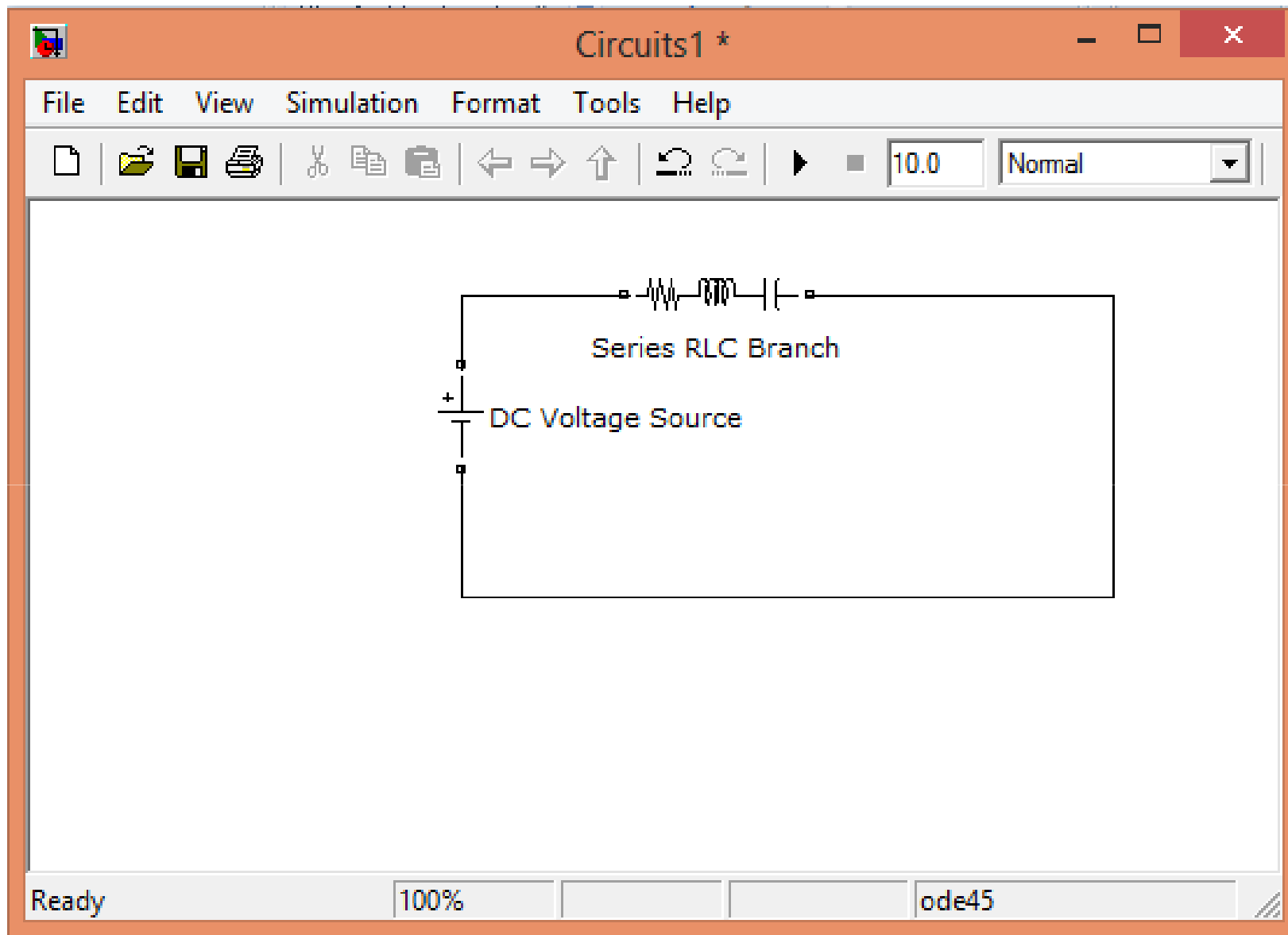

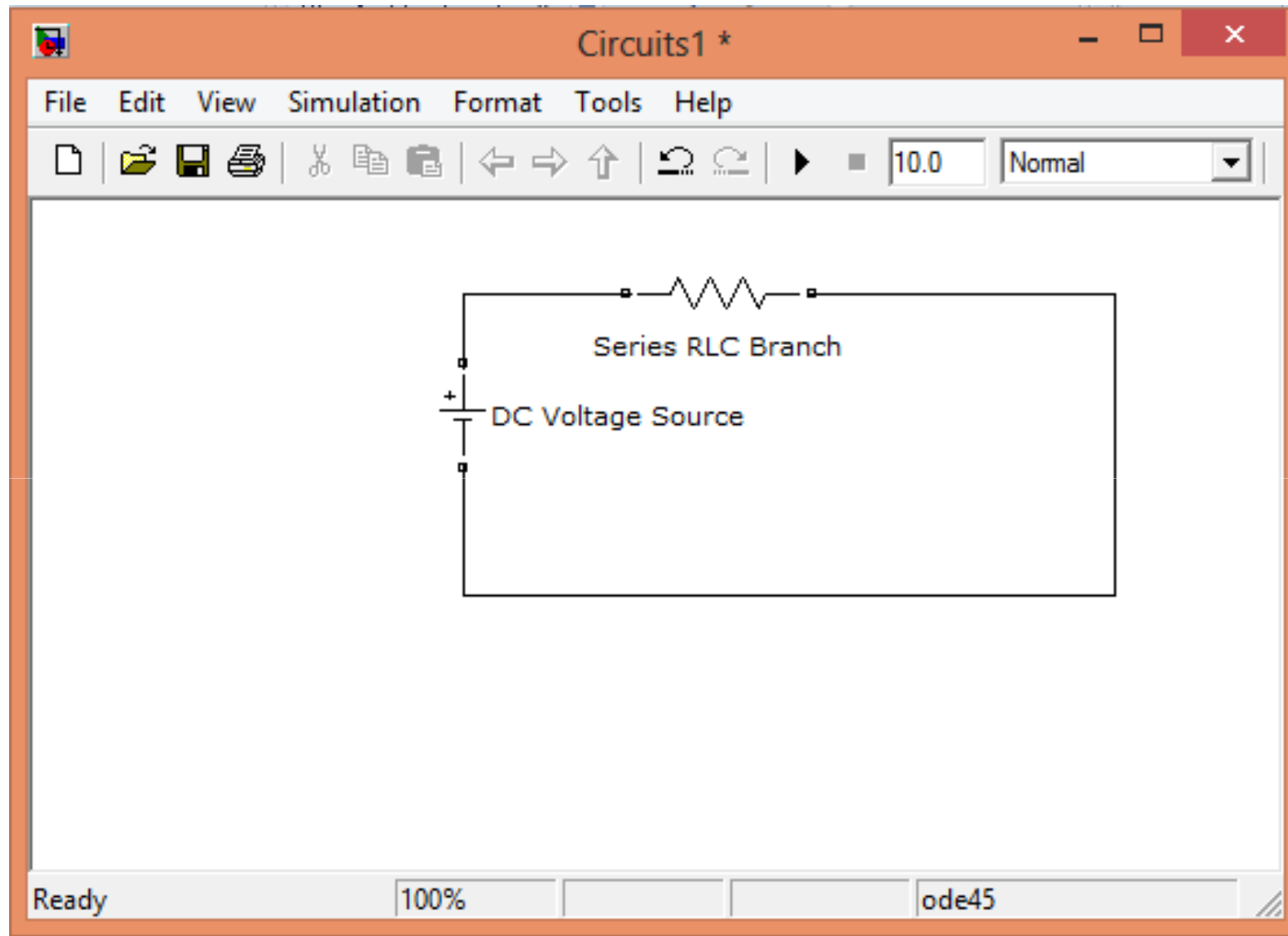



# Measure the current and voltage

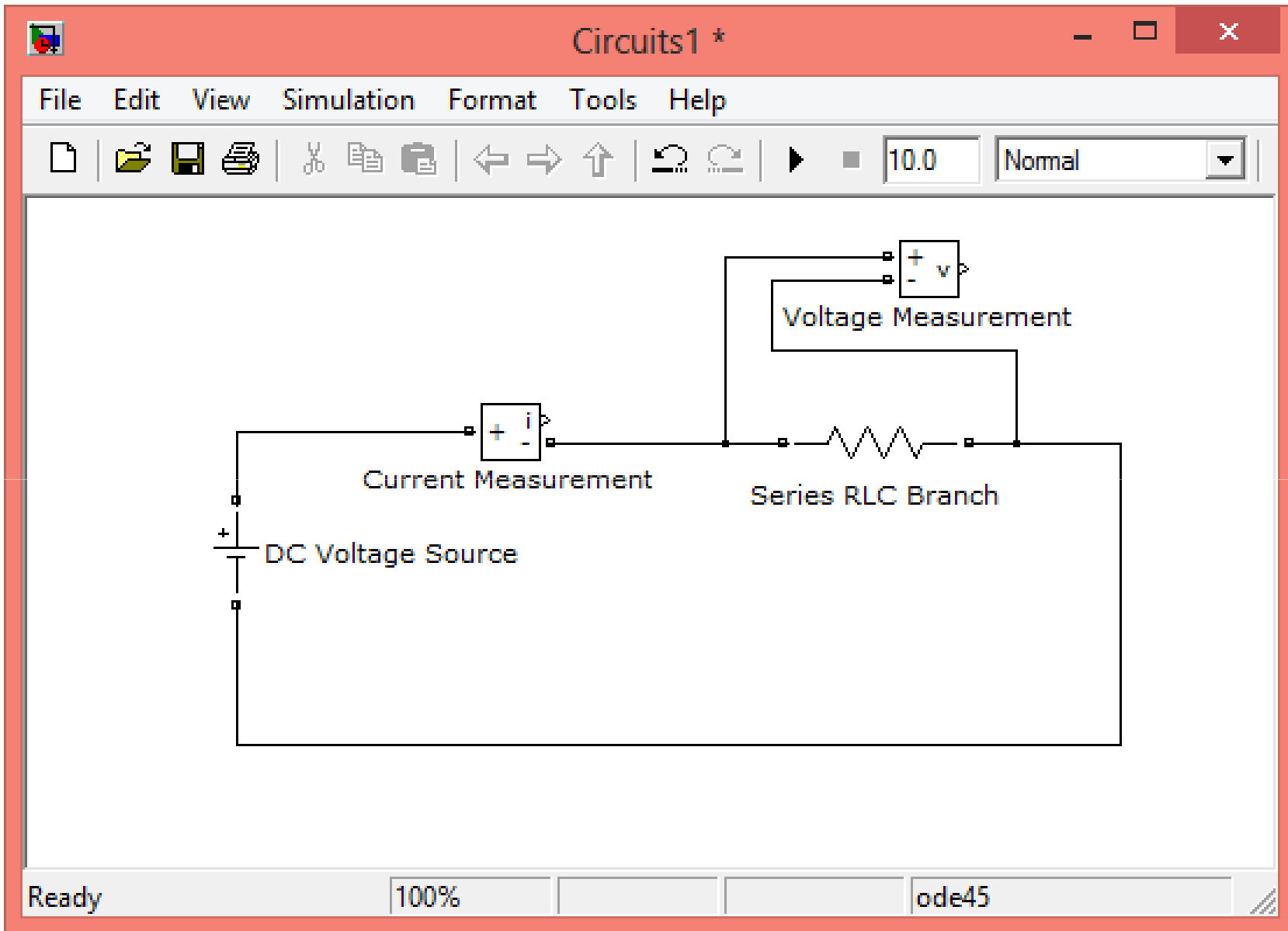
- 1) Simulink library browser →  
SimPowerSystems → Measurements →  
Current Measurement block.
- 2) Connect it in series in the circuit.
- 3) Simulink library browser →  
SimPowerSystems → Measurements →  
Voltage Measurement block.
- 4) Connect it in parallel to the resistance in the circuit.




# Viewing the results

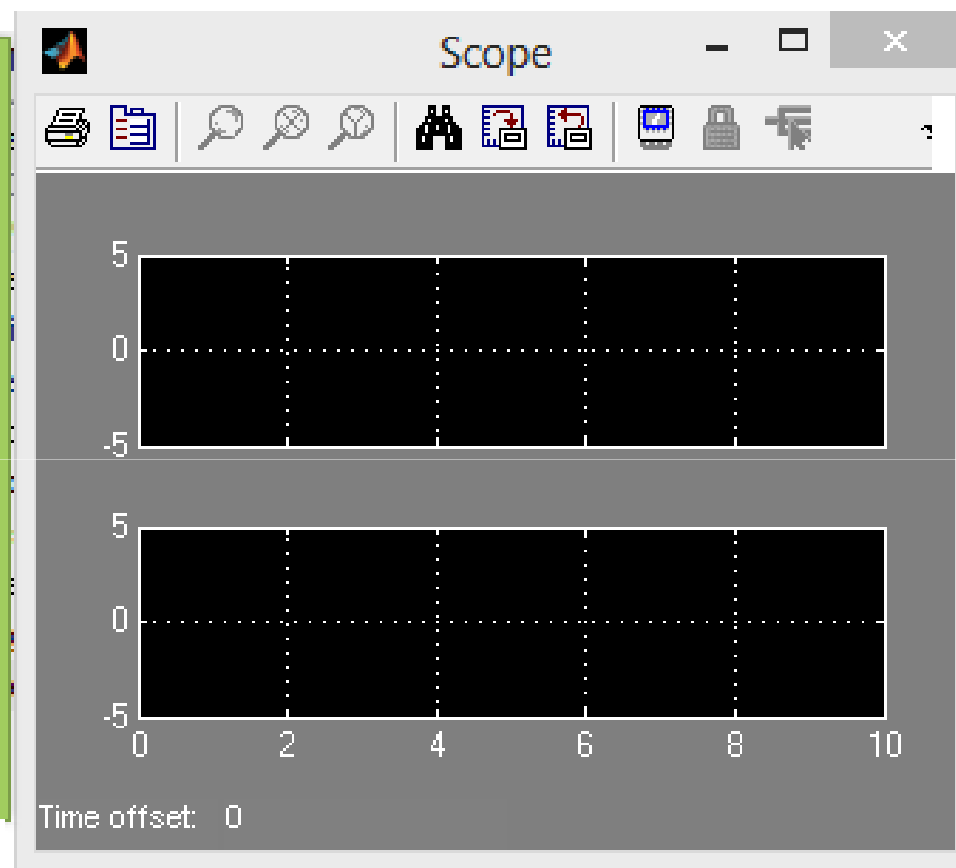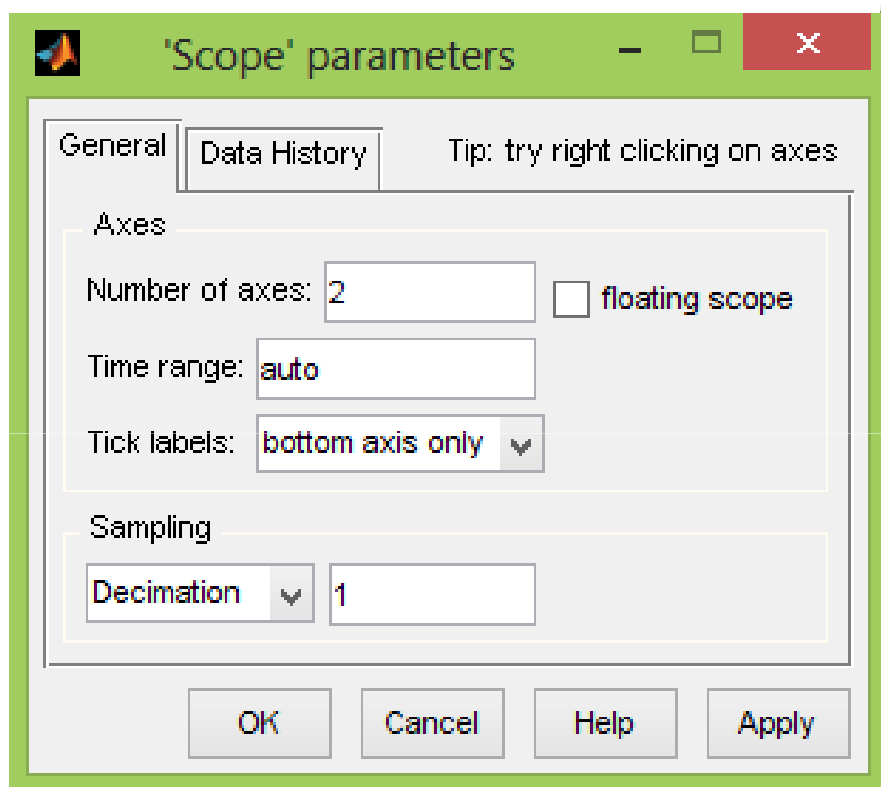- 1) Simulink → Commonly used blocks → Scope
- 2) Scope → Parameters → No. of axes → 2
- 3) Connect the inputs to Current & Voltage measurement block outputs



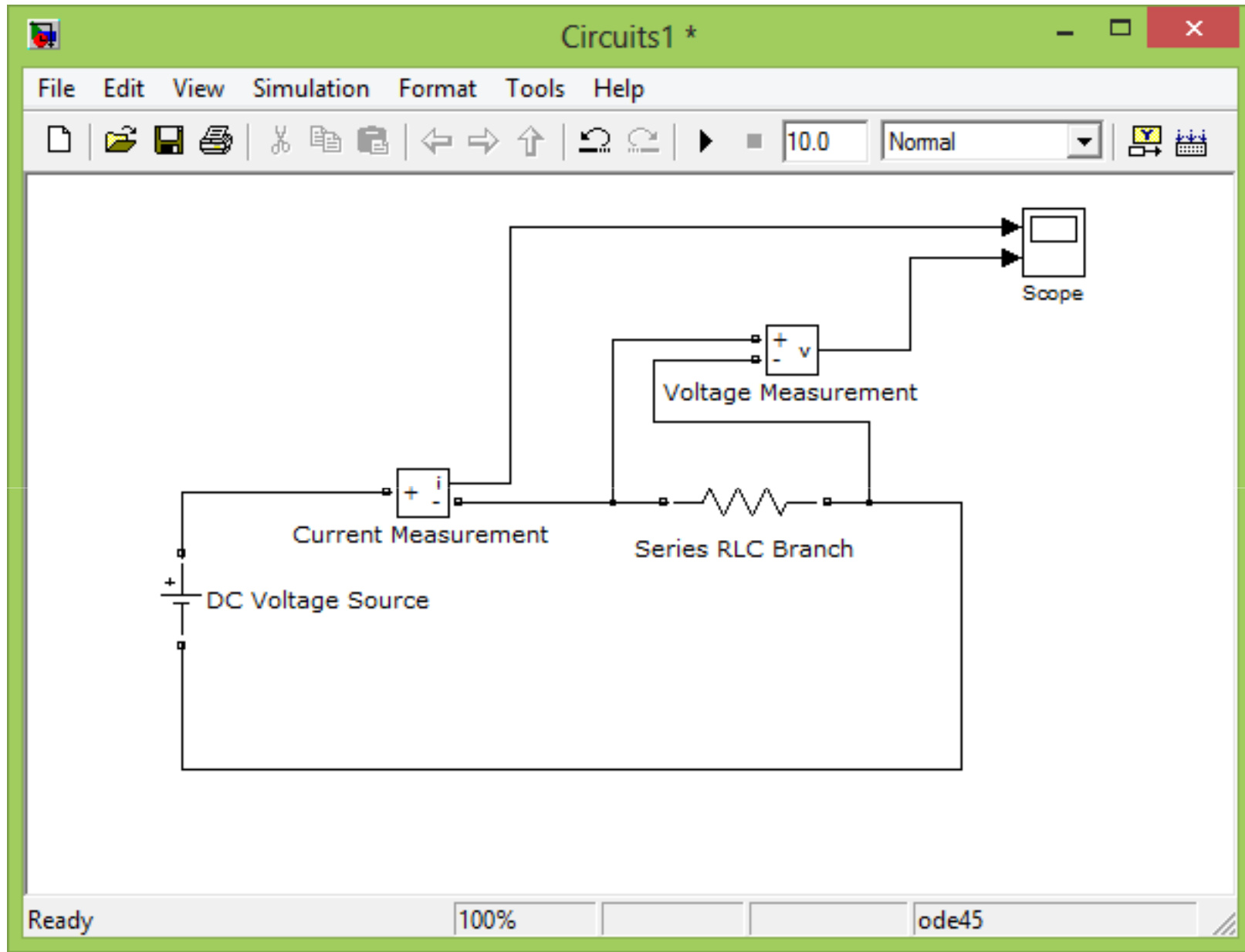

# Bring powergui block to the workspace

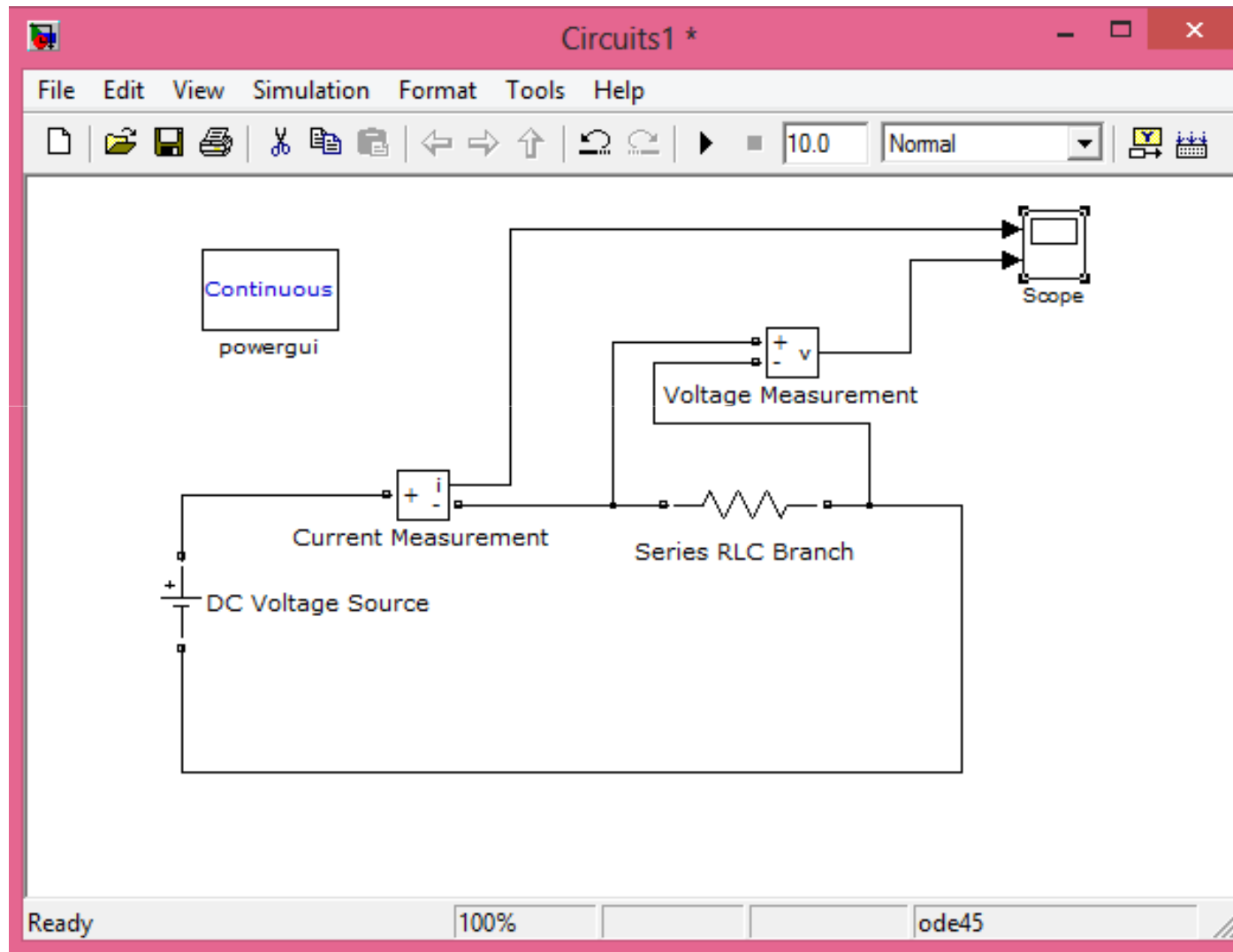




# Steps for observing the output

Run the simulink model

Double click on the Scope


Observe the graphs


Use Autoscale option if required

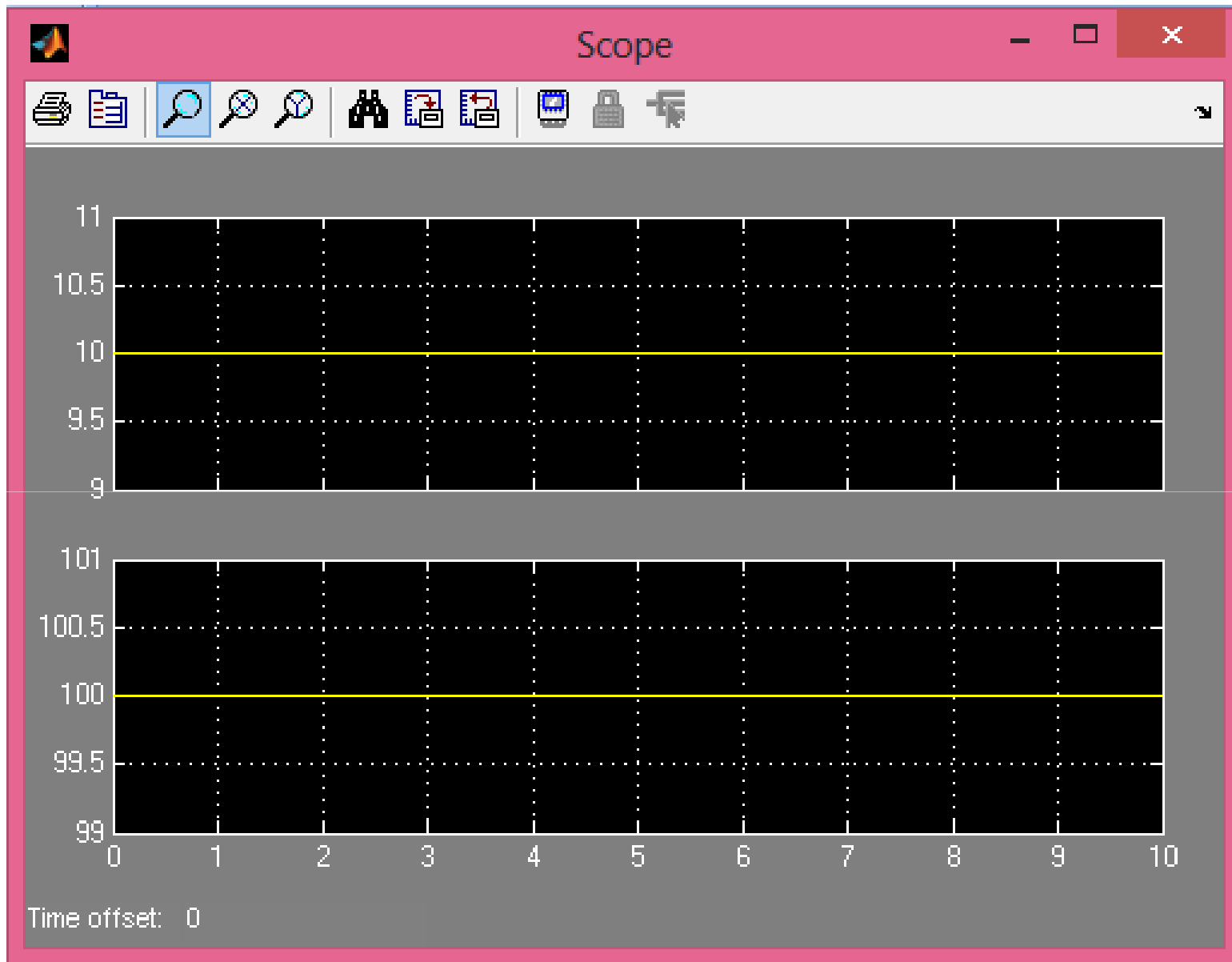

# Measure the Power

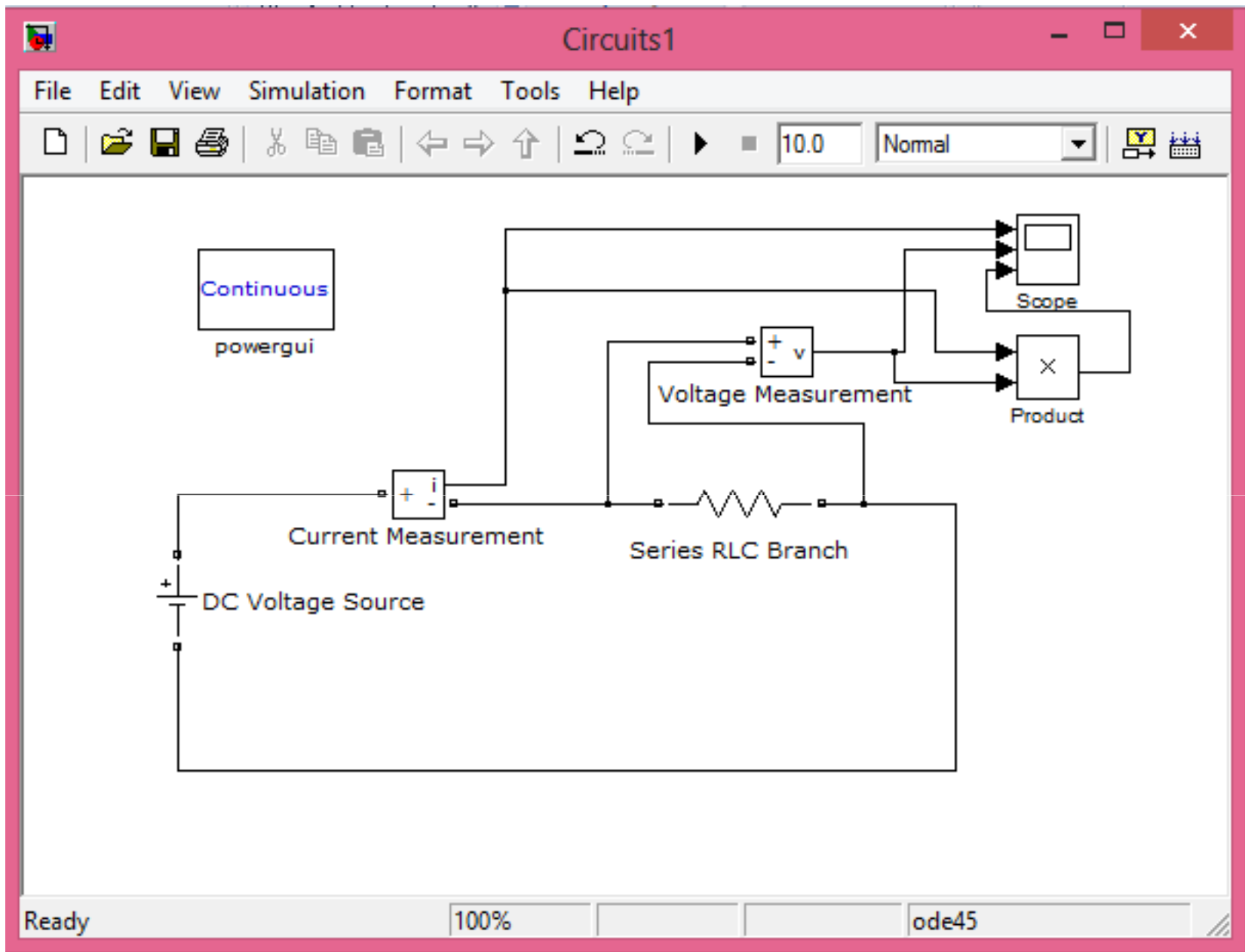
- 1)  $P=VI$
- 2) Simulink → Math Operations → Product
- 3) Connect the inputs to Current & Voltage measurement block outputs



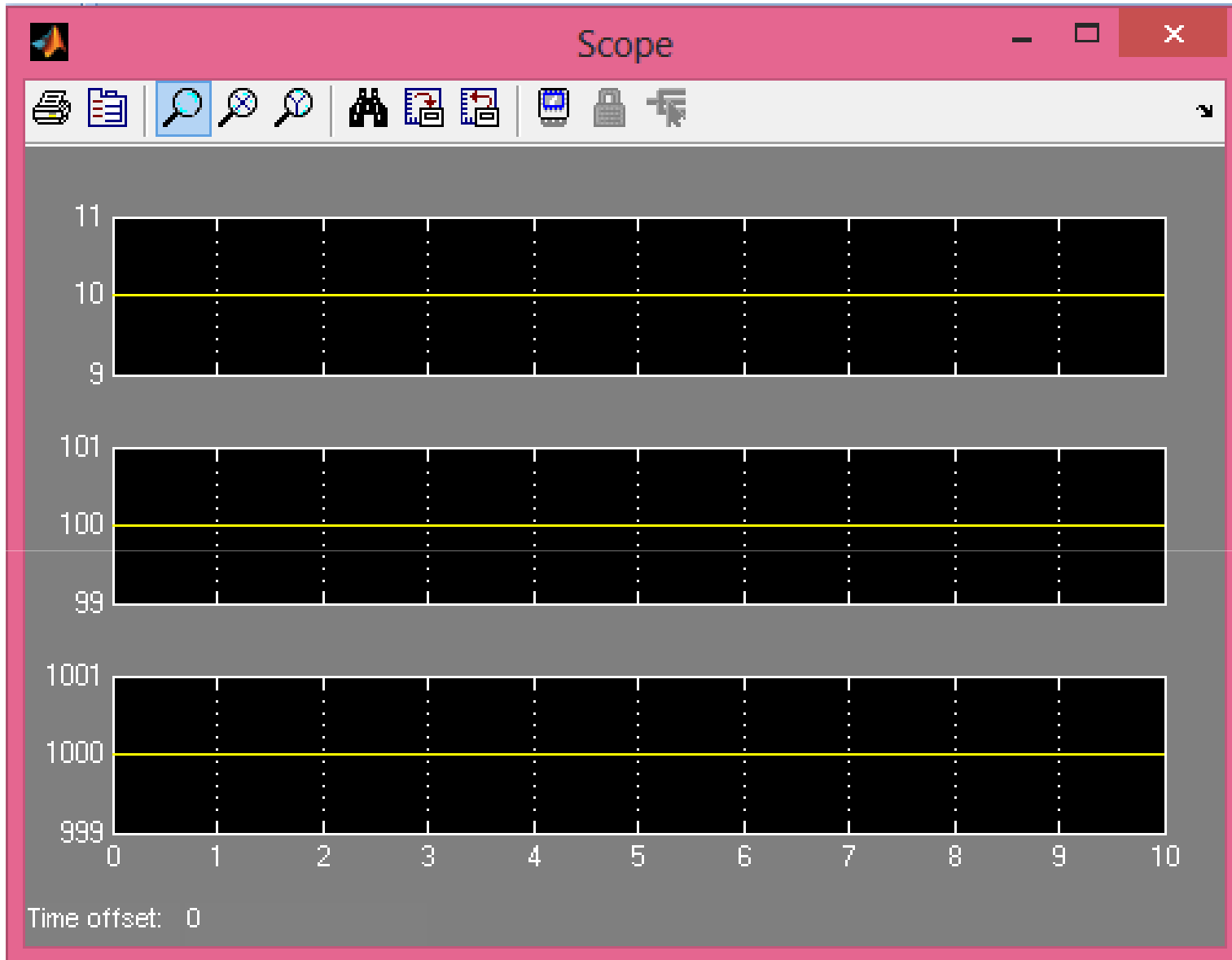


## Voltage, Current and Power Outputs
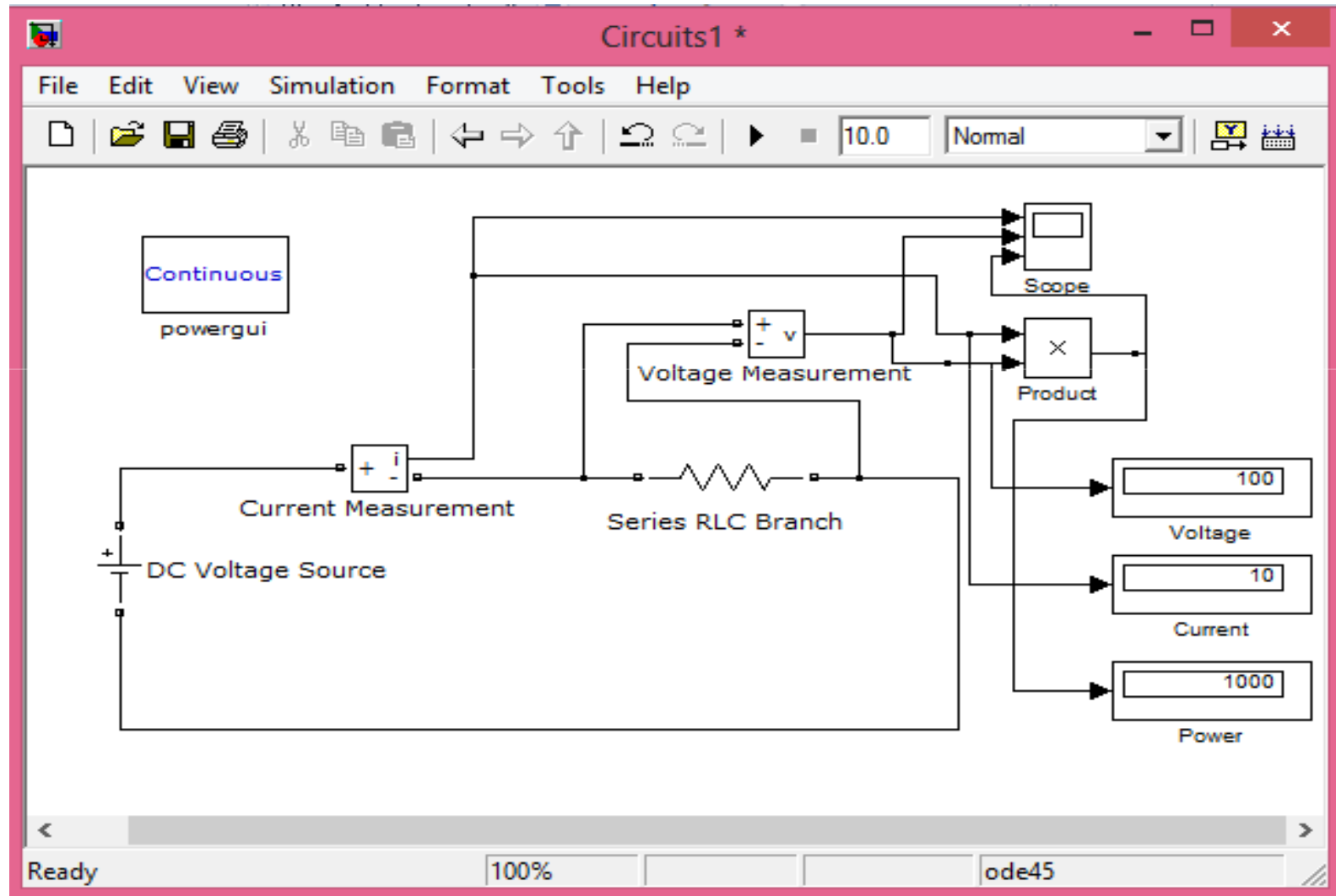
# Use Display block to observe the values of V, I and P


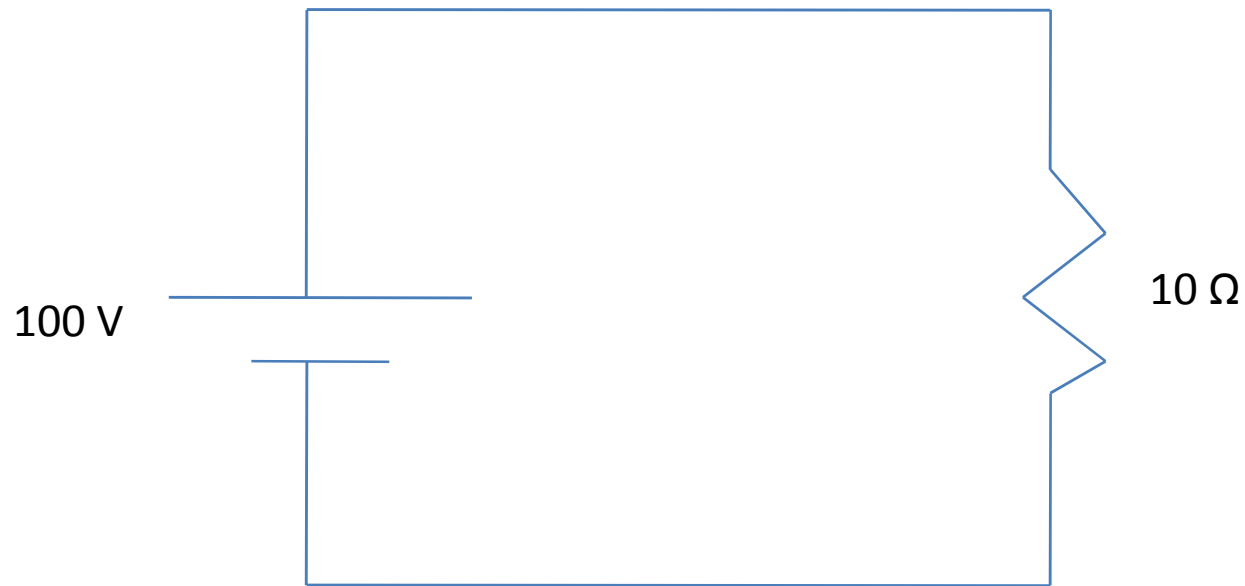
# Simulation of the same circuit using another method in Simulink



# Corresponding equations of the circuit

$$V = IR$$

$$I = \frac{V}{R}$$


$$P = \frac{V^2}{R} = I^2 R$$




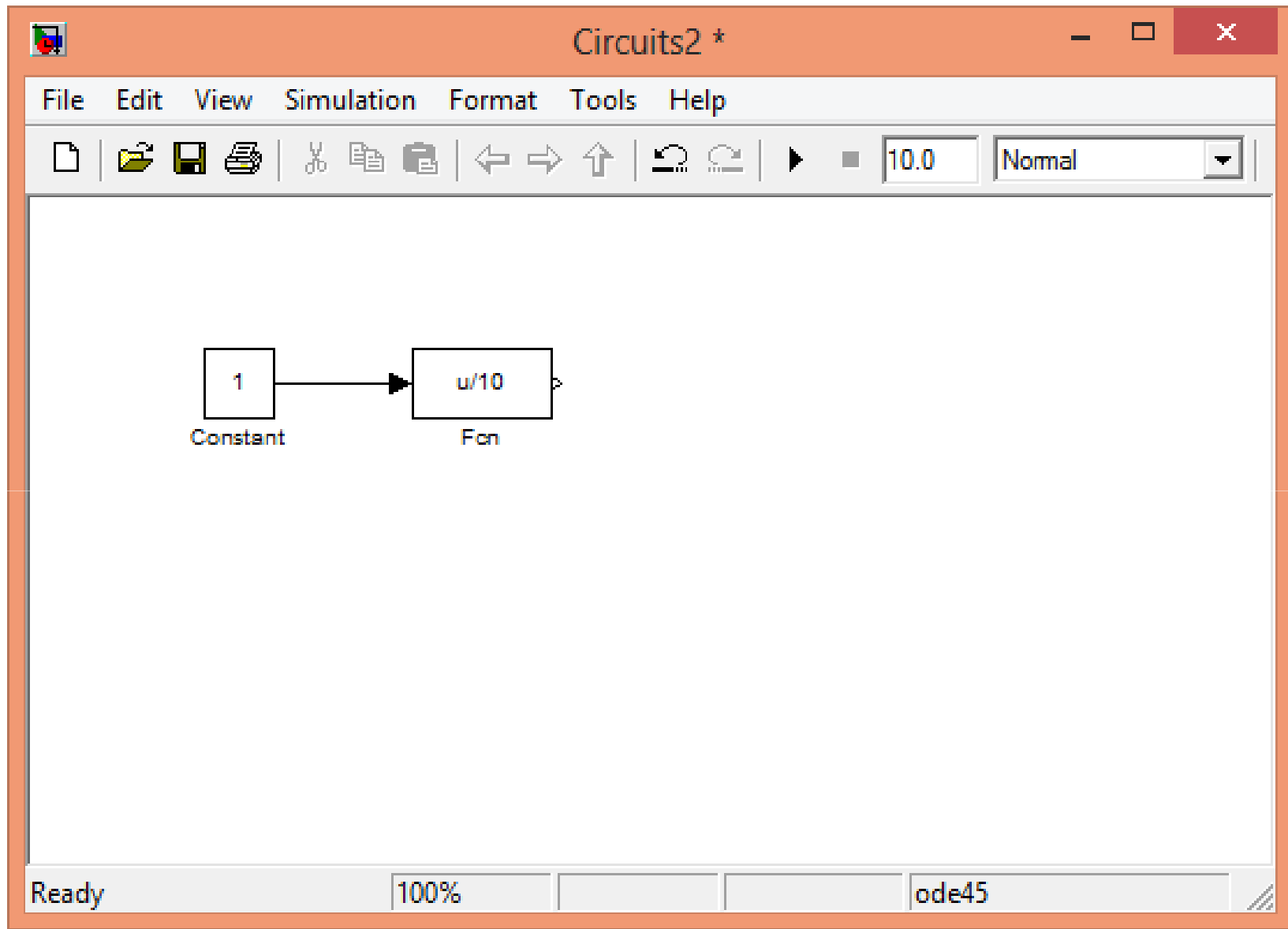
# Steps

Simulink → Commonly used blocks →  
Constant → Change the value of the block to  
100 by double clicking (Corresponding to 100  
V of the source)

Bring Fcn block from Simulink library →  
Double click → Change the function to  $u/10$   
(Corresponding to  $V/R$ , as  $R=10\ \Omega$ )



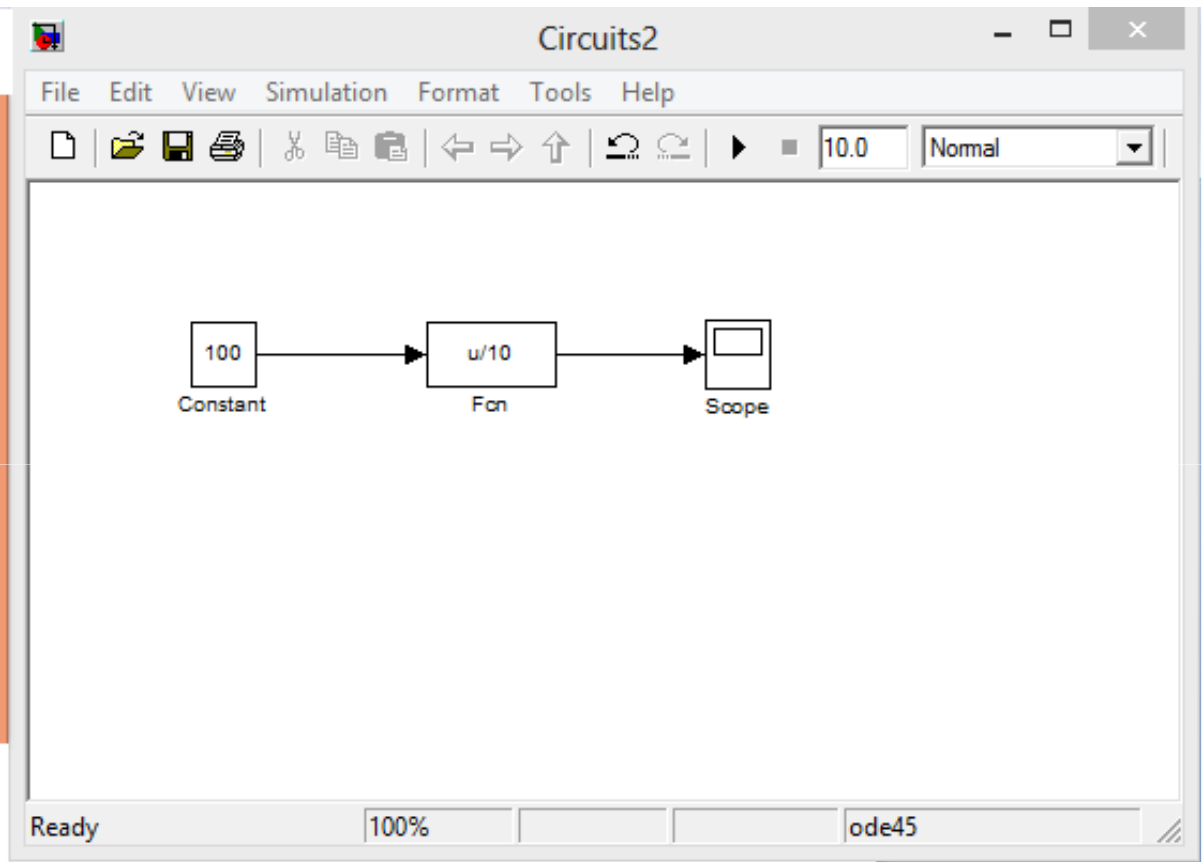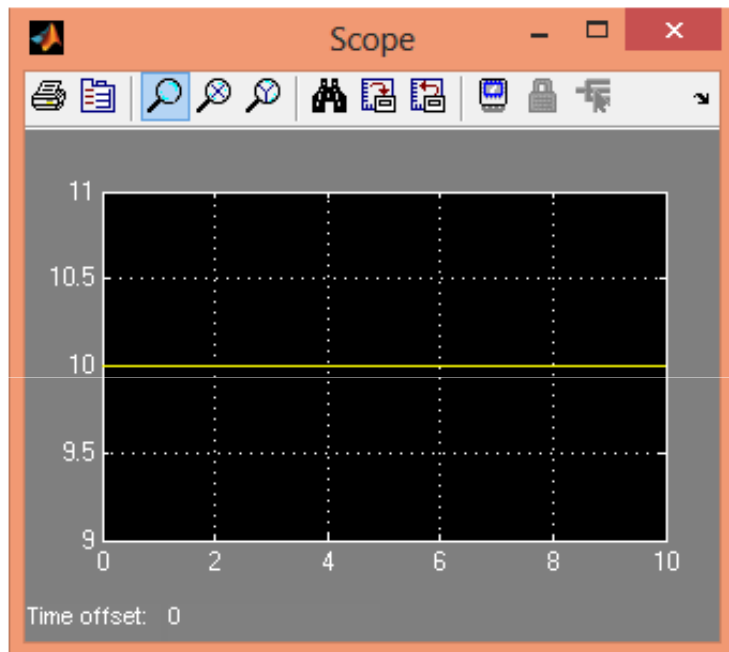**Scope connected to the output of the  
Fcn block will show the current**





# For measurement of Power

Use another Fcn block.

Change its expression to  $(u*u/10)$ , corresponding to  $V^2/R$ ).

Connect its input to Constant voltage block output.


Connect its output to a display.

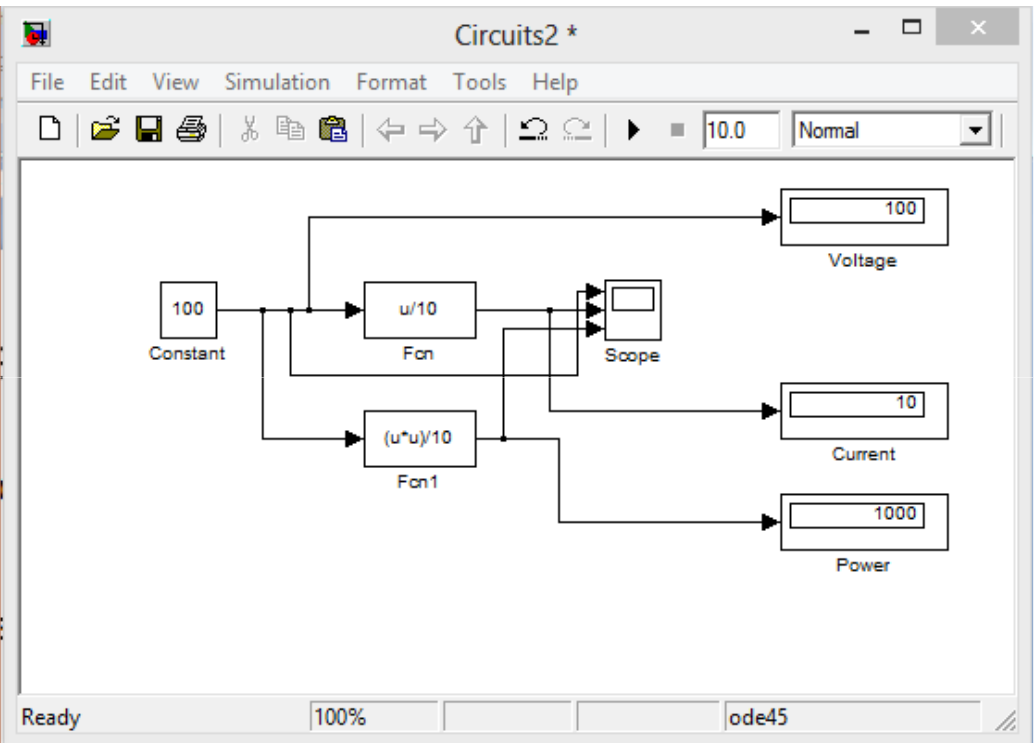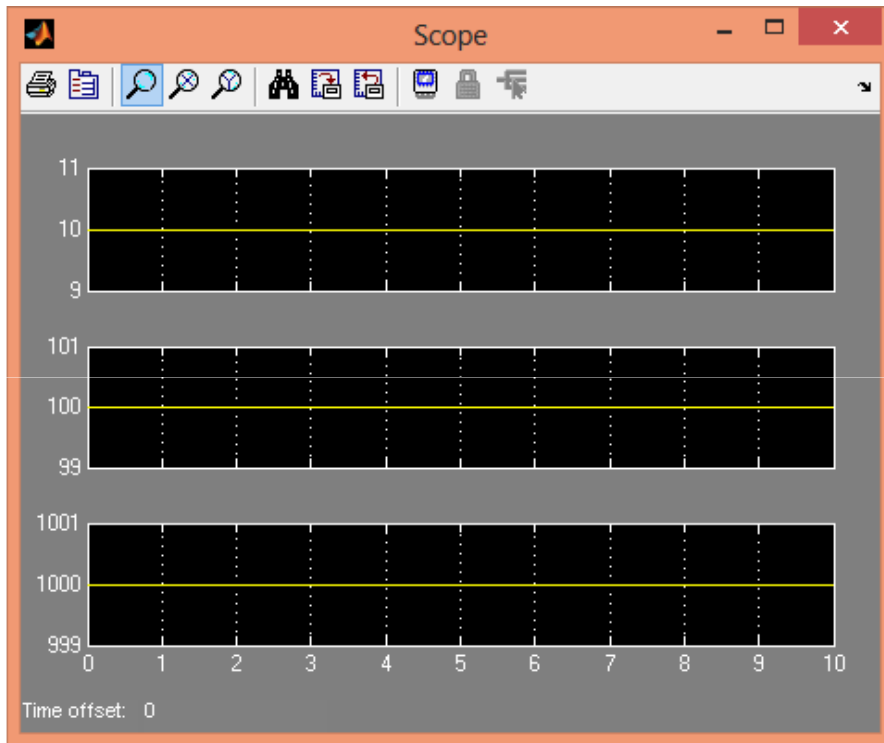

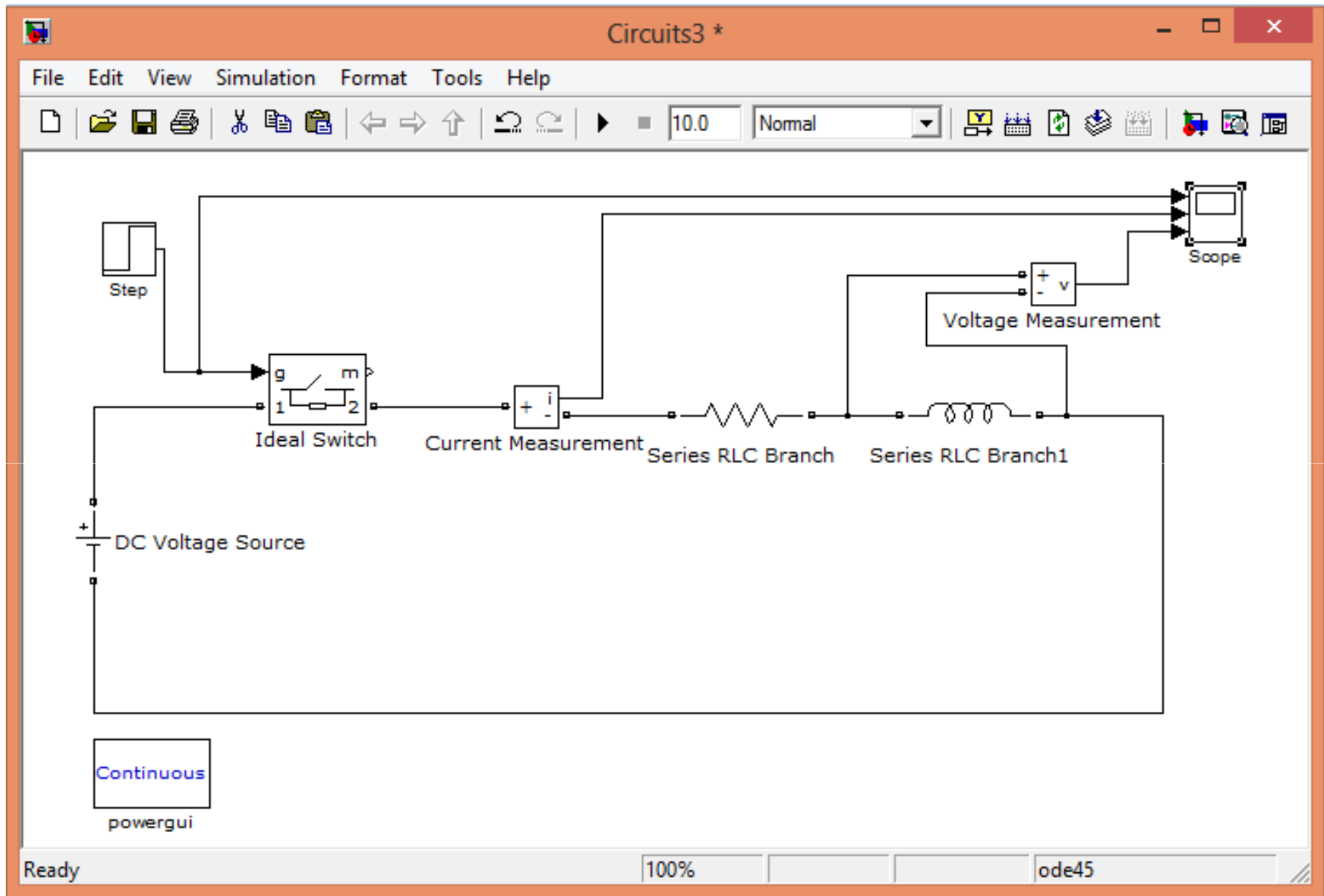
# Simulation of R-L Series Circuit

Hands-on:

Please follow the steps as shown on the screen.





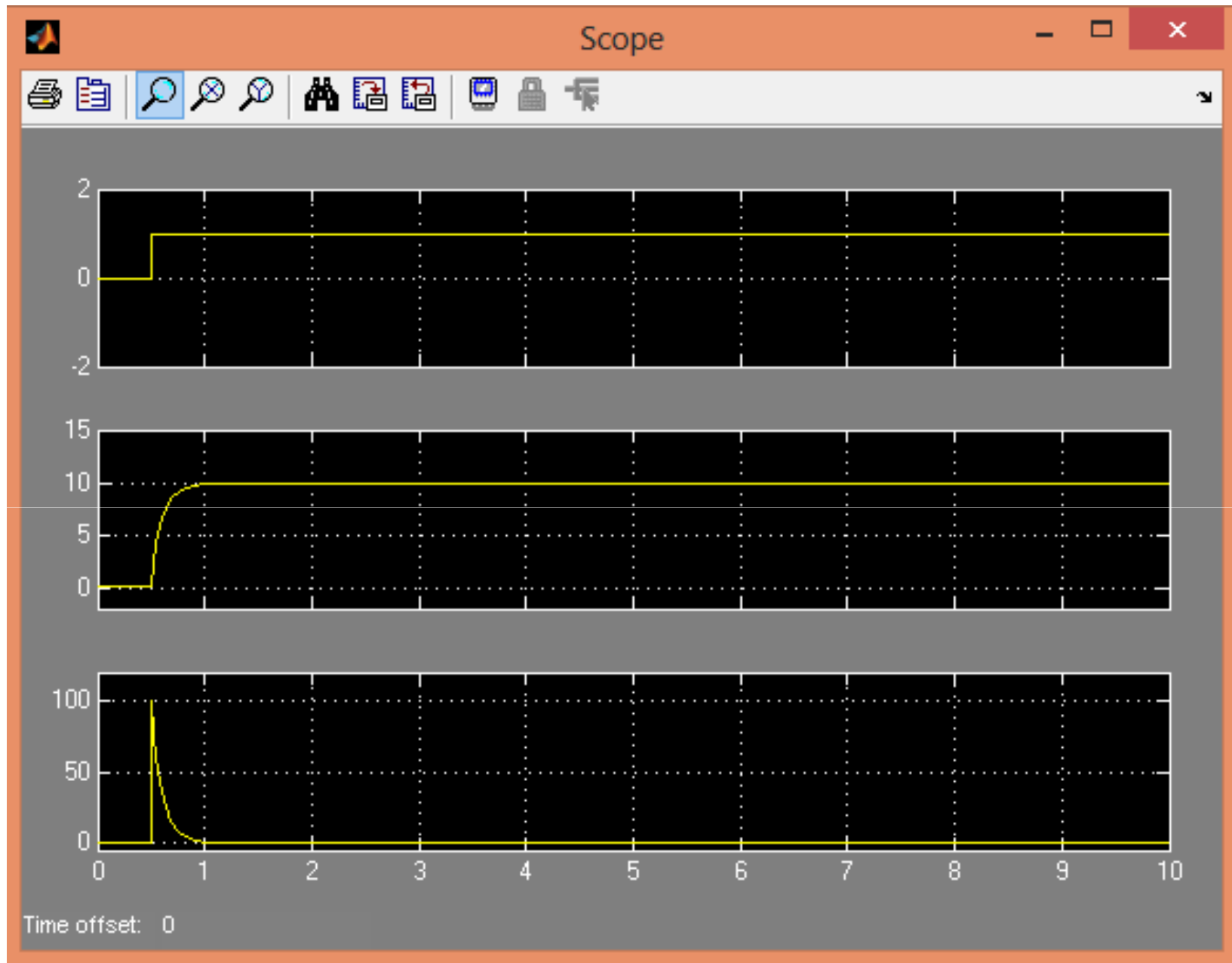

**Questions please ?????**

**End of Day-2 Session-2**

**Thank You**