 


Electronic Devices

Ninth Edition

Floyd

Chapter 8




Summary

The FET

The idea for a field-effect transistor (FET) was first proposed by Julius Lilienthal, a physicist and inventor. In 1930 he was granted a U.S. patent for the device.

 His ideas were later refined and developed into the FET. Materials were not available at the time to build his device. A practical FET was not constructed until the 1950's. Today FETs are the most widely used components in integrated circuits.





Summary

The JFET


The JFET (or Junction Field Effect Transistor) is a normally ON device. For the n -channel device illustrated, when the drain is positive with respect to the source and there is no gate-source voltage, there is current in the channel.

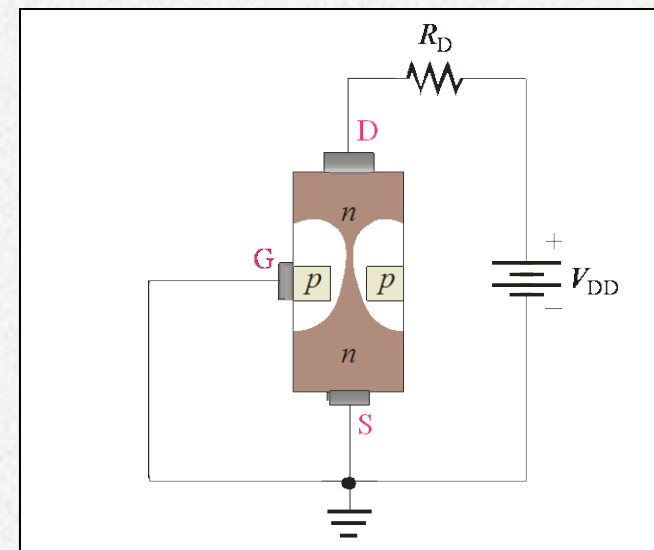When a negative gate voltage is applied to the FET, the electric field causes the channel to narrow, which in turn causes current to decrease.




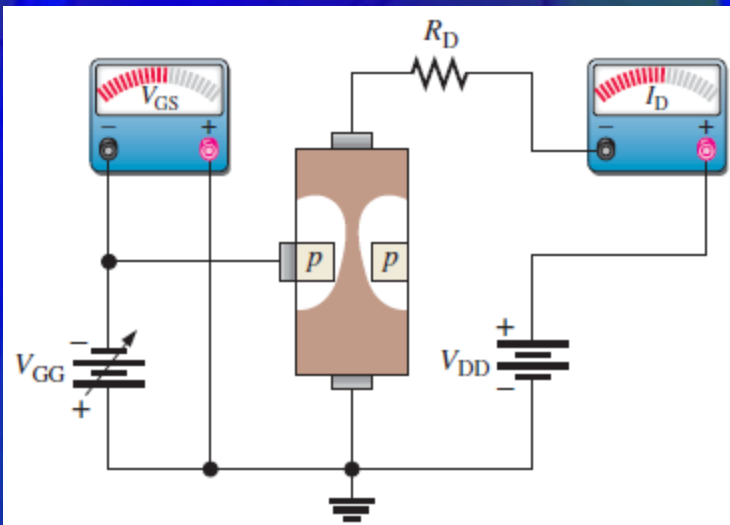

(a) JFET biased for conduction

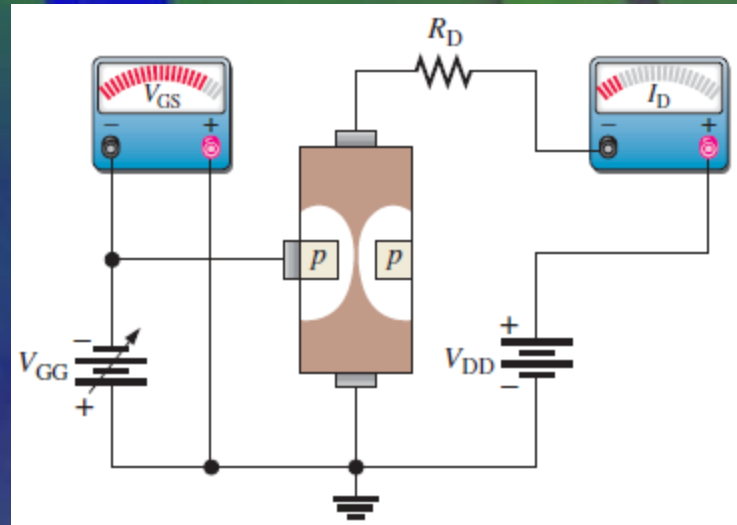

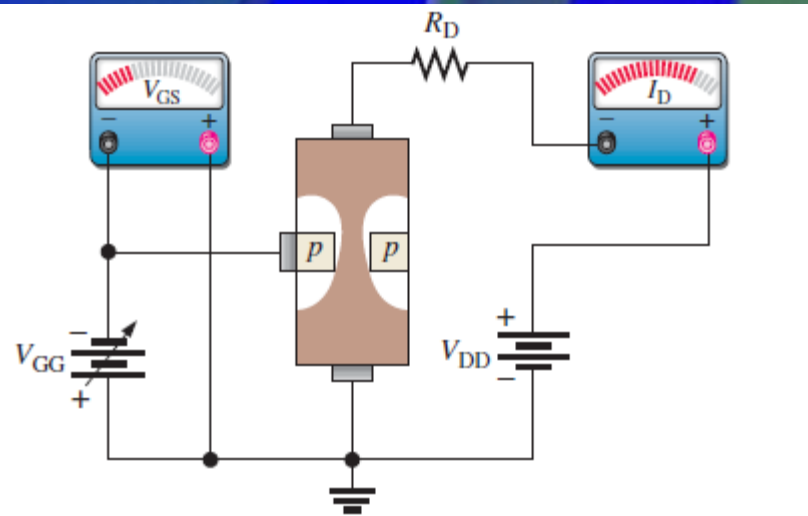(b) Greater V_{GG} narrows the channel (between the white areas) which increases the resistance of the channel and decreases I_D .




(c) Less V_{GG} widens the channel (between the white areas) which decreases the resistance of the channel and increases I_D .

Summary

The JFET

As in the base of bipolar transistors, there are two types of JFETs: n -channel and p -channel. The dc voltages are opposite polarities for each type.

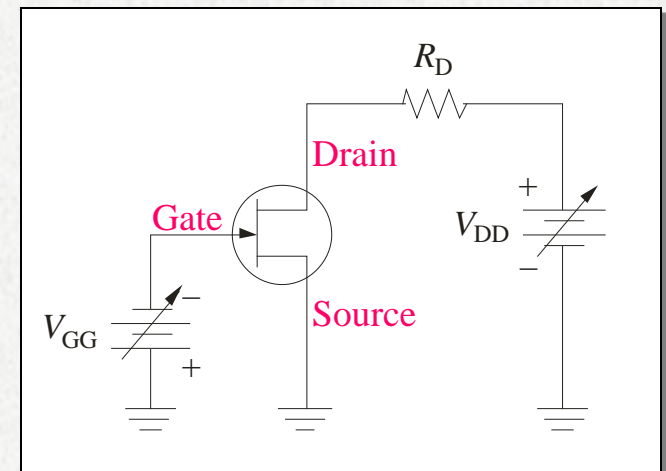The symbol for an n -channel JFET is shown, along with the proper polarities of the applied dc voltages. For an n -channel device, the gate is always operated with a negative (or zero) voltage with respect to the source.



Summary


The JFET

There are three regions in the characteristic curve for a JFET as illustrated for the case when $V_{GS} = 0$ V.

Between A and B is the **Ohmic region**, where current and voltage are related by Ohm's law.

From B to C is the **active** (or *constant-current*) **region** where current is essentially independent of V_{DS} .

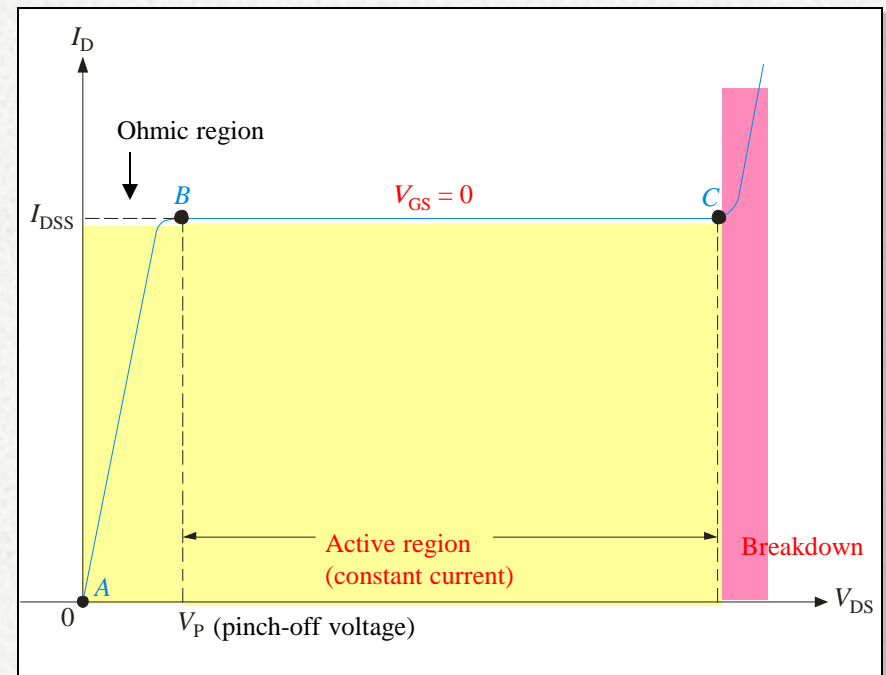Beyond C is the **breakdown region**. Operation here can damage the FET.




Summary

The JFET

When V_{GS} is set to different values, the relationship between V_{DS} and I_D develops a family of characteristic curves for the device.

 An n -channel characteristic is illustrated here. Notice that V_p is positive and has the same magnitude as $V_{GS(off)}$.



Summary


The JFET

A plot of V_{GS} to I_D is called the transfer or transconductance curve. The transfer curve is a plot of the output current (I_D) to the input voltage (V_{GS}).

The transfer curve is based on the equation

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2$$

 By substitution, you can find other points on the curve for plotting the universal curve.



Summary

The JFET

Example:

A certain 2N5458 JFET has $I_{DSS} = 6.0 \text{ mA}$ and $V_{GS(off)} = -3.5 \text{ V}$.

(a) Show the values of the these end points on the transfer curve.


(b) Show the point for the case when $I_D = 3.0 \text{ mA}$.

Solution:

(b) When $I_D = \frac{1}{2} I_{DSS}$,

$$V_{GS} = 0.3 V_{GS(off)}$$

Therefore, $V_{GS} = -1.05 \text{ V}$

 

Summary

The JFET

The transconductance is the ratio of a change in output current (ΔI_D) to a change in the input voltage (ΔV_{GS}).


This definition is $g_m = \frac{\Delta I_D}{\Delta V_{GS}}$

The following approximate formula is useful for calculating g_m if you know g_{m0} .

$$g_m = g_{m0} \left(1 - \frac{V_{GS}}{V_{GS(off)}} \right)$$

The value of g_{m0} can be found from

$$g_{m0} = \frac{2I_{DSS}}{|V_{GS(off)}|}$$

 

Summary

The JFET


Because the slope changes at every point along the curve, the transconductance is not constant, but depends on where it is measured.

Example:

What is the transconductance for the JFET at the point shown?

Solution:
 
$$\begin{aligned}g_m &= \frac{\Delta I_D}{\Delta V_{GS}} = \frac{5.7 \text{ mA} - 3.7 \text{ mA}}{-0.7 \text{ V} - (-1.3 \text{ V})} \\ &= \frac{2.0 \text{ mA}}{0.6 \text{ V}} = 3.33 \text{ mS}\end{aligned}$$



Electrical Characteristics TA = 25°C unless otherwise noted

Symbol	Parameter	Test Conditions	Min	Typ	Max	Units
--------	-----------	-----------------	-----	-----	-----	-------

OFF CHARACTERISTICS

$V_{(BR)GSS}$	Gate-Source Breakdown Voltage	$I_G = 10 \mu A, V_{DS} = 0$	- 25			V
I_{GSS}	Gate Reverse Current	$V_{GS} = -15 V, V_{DS} = 0$ $V_{GS} = -15 V, V_{DS} = 0, T_A = 100^\circ C$			- 1.0 - 200	nA nA
$V_{GS(off)}$	Gate-Source Cutoff Voltage	$V_{DS} = 15 V, I_D = 10 nA$	5457 5458 5459	- 0.5 - 1.0 - 2.0	- 6.0 - 7.0 - 8.0	V V V
V_{GS}	Gate-Source Voltage	$V_{DS} = 15 V, I_D = 100 \mu A$ $V_{DS} = 15 V, I_D = 200 \mu A$ $V_{DS} = 15 V, I_D = 400 \mu A$	5457 5458 5459	- 2.5 - 3.5 - 4.5		V V V

ON CHARACTERISTICS

I_{DSS}	Zero-Gate Voltage Drain Current*	$V_{DS} = 15 V, V_{GS} = 0$	5457 5458 5459	1.0 2.0 4.0	3.0 6.0 9.0	5.0 9.0 16	mA mA mA
-----------	----------------------------------	-----------------------------	----------------------	-------------------	-------------------	------------------	----------------

SMALL SIGNAL CHARACTERISTICS

g_{fs}	Forward Transfer Conductance*	$V_{DS} = 15 V, V_{GS} = 0, f = 1.0 kHz$	5457 5458 5459	1000 1500 2000		5000 5500 6000	$\mu mhos$ $\mu mhos$ $\mu mhos$
g_{os}	Output Conductance*	$V_{DS} = 15 V, V_{GS} = 0, f = 1.0 kHz$			10	50	$\mu mhos$
C_{iss}	Input Capacitance	$V_{DS} = 15 V, V_{GS} = 0, f = 1.0 MHz$			4.5	7.0	pF
C_{rss}	Reverse Transfer Capacitance	$V_{DS} = 15 V, V_{GS} = 0, f = 1.0 MHz$			1.5	3.0	pF
NF	Noise Figure	$V_{DS} = 15 V, V_{GS} = 0, f = 1.0 kHz,$ $R_G = 1.0 megohm, BW = 1.0 Hz$				3.0	dB

* Pulse Test: Pulse Width $\leq 300 ms$, Duty Cycle $\leq 2\%$

Summary

JFET Input Resistance

The input resistance of a JFET is given by: $R_{IN} = \left| \frac{V_{GS}}{I_{GSS}} \right|$

where I_{GSS} is the current into the reverse biased gate.

JFETs have very high input resistance, but it drops when the temperature increases.

Example:

Compare the input resistance of a 2N5485 at 25 °C and at 100 °C. The specification sheet shows that for $V_{GS} = -20$ V, $I_{GSS} = 1$ nA at 25 °C and 0.2 μA at 100 °C.

Solution: At 25 °C, $R_{IN} = \left| \frac{V_{GS}}{I_{GSS}} \right| = \left| \frac{20 \text{ V}}{1 \text{ nA}} \right| = 20 \text{ G}\Omega!$

At 100 °C, $R_{IN} = \left| \frac{V_{GS}}{I_{GSS}} \right| = \left| \frac{20 \text{ V}}{0.2 \text{ }\mu\text{A}} \right| = 100 \text{ M}\Omega$

Summary

JFET Biasing

Self-bias is simple and effective, so it is the most common biasing method for JFETs. With self bias, the gate is essentially at 0 V.

An n -channel JFET is illustrated. The current in R_S develops the necessary reverse bias that forces the gate to be less than the source.


Example:

Assume the resistors are as shown and the drain current is 3.0 mA. What is V_{GS} ?

Solution:

$$V_G = 0 \text{ V}; V_S = (3.0 \text{ mA})(330 \Omega) = 0.99 \text{ V}$$
 
$$V_{GS} = 0 - 0.99 \text{ V} = -0.99 \text{ V}$$



Summary

JFET Biasing

You can use the transfer curve to obtain a reasonable value for the source resistor in a self-biased circuit.


Example:

What value of R_S should you use to set the Q point as shown?

Solution:


The Q point is approximately at $I_D = 4.0$ mA and $V_{GS} = -1.25$ V.

$$R_S = \left| \frac{V_{GS}}{I_D} \right| = \frac{1.25 \text{ V}}{3.0 \text{ mA}} = 375 \Omega$$

 

Summary

Graphical Analysis of a Self-Biased JFET

 


First, calculate V_{GS} when I_D is zero.

$$V_{GS} = -I_D R_S = (0)(470 \Omega) = 0 \text{ V}$$

Next, calculate V_{GS} when $I_D = I_{DSS}$.

$$V_{GS} = -I_D R_S = -(10 \text{ mA})(470 \Omega) = -4.7 \text{ V}$$

 Q-point of the circuit as shown, where $I_D = 5.07 \text{ mA}$ and $V_{GS} = -2.3 \text{ V}$.




Summary

JFET Biasing

Voltage-divider biasing is a combination of a voltage-divider and a source resistor to keep the source more positive than the gate.

V_G is set by the voltage-divider and is independent of V_S . V_S must be larger than V_G in order to maintain the gate at a negative voltage with respect to the source.

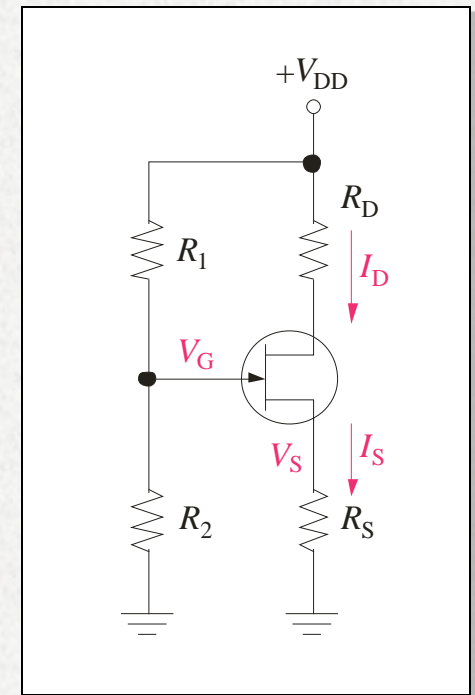Voltage-divider bias helps stabilize the bias for variations between transistors.



Summary

JFET Biasing



A graphical analysis of voltage-divider biasing is illustrated. A typical transconductance curve for the 2N5485 is shown with $I_{DSS} = 6.5 \text{ mA}$ and $V_{GS(off)} = -2.2 \text{ V}$.

Start with V_G :

$$V_G = 2.79 \text{ V}$$



$$V_G/R_S = 2.79 \text{ mA}$$

 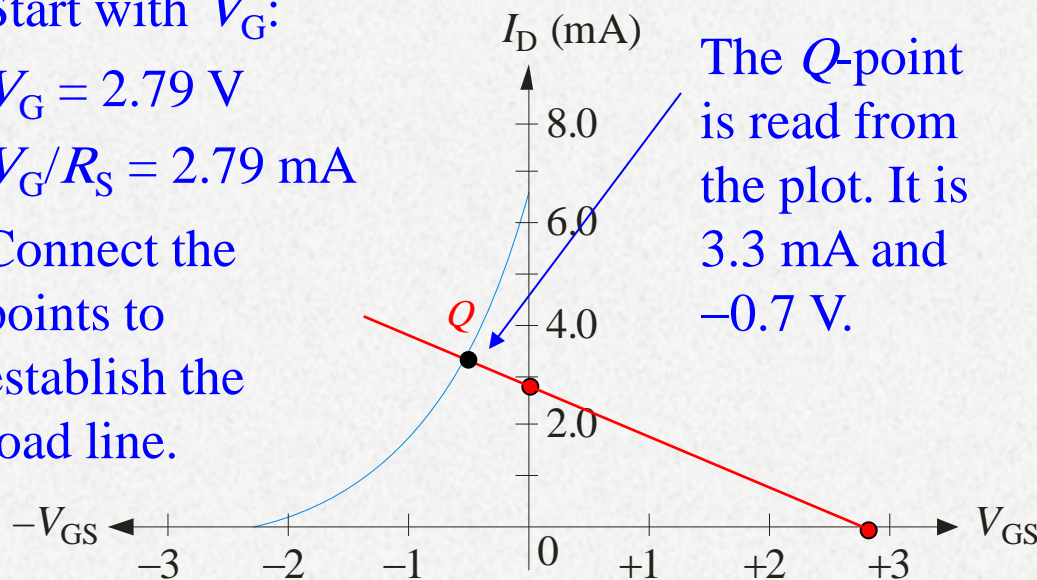Connect the points to establish the load line.



Summary

Q-Point Stability

 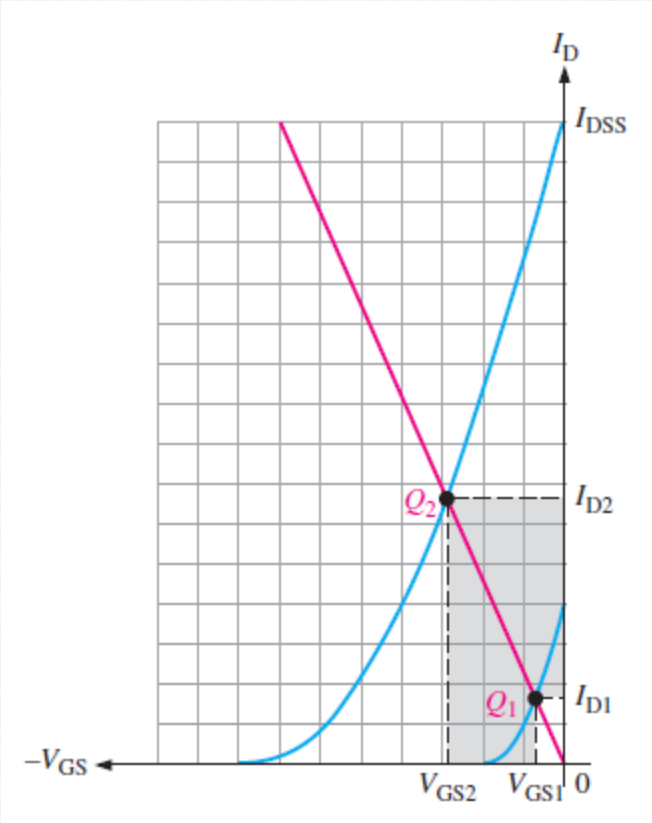

Summary



Current-Source Bias

if $V_{EE} \gg V_{BE}$

$$I_E = \frac{V_{EE} - V_{BE}}{R_E} \cong \frac{V_{EE}}{R_E}$$

Since $I_E \cong I_D$

$$I_D \cong \frac{V_{EE}}{R_E}$$

  


Summary

JFET Biasing

An even more stable form of bias is current-source bias. The current-source can be either a BJT or another FET. With current-source biasing, the drain current is essentially independent of V_{GS} .

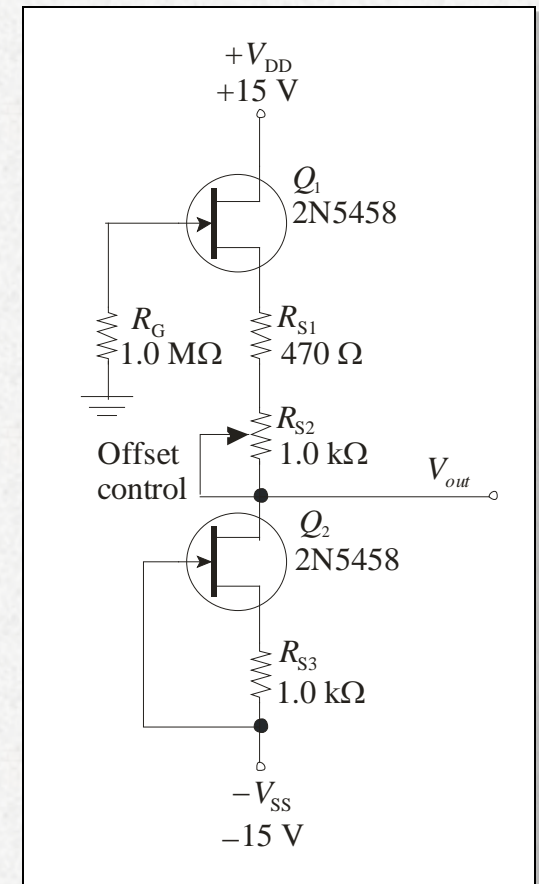In this circuit Q_2 serves as a current source for Q_1 . An advantage to this particular circuit is that the output can be adjusted (using R_{S2}) for 0 V DC.




Summary

JFET Ohmic Region




As described before, the ohmic region is between the origin and the active region. A JFET operated in this region can act as a variable resistor.

 Data from an actual FET is shown. The slopes (which represent conductance) of successive V_{GS} lines are different in the ohmic region. This difference is exploited for use as a voltage controlled resistance.



Summary


JFET Ohmic Region

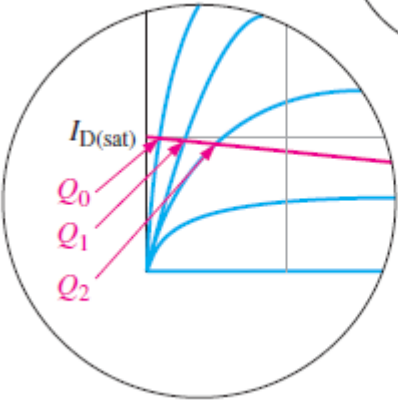  

$$I_{D(sat)} = \frac{V_{DD}}{R_D}$$

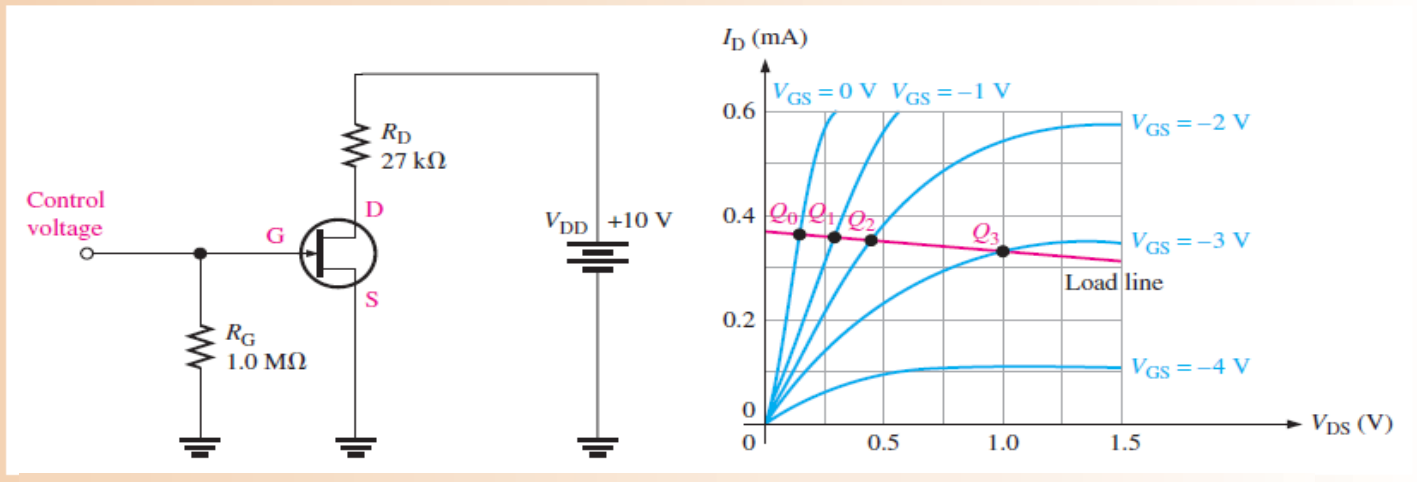EXAMPLE 8–14

An n -channel JFET is biased in the ohmic region as shown in Figure 8–32. The graph shows an expanded section of the load line in the ohmic region. As V_{GS} is



varied from 0 V to -3 V as indicated, assume that the graph shows the following Q-point values:

$$Q_0: I_D = 0.360 \text{ mA}, V_{DS} = 0.13 \text{ V}$$

$$Q_1: I_D = 0.355 \text{ mA}, V_{DS} = 0.27 \text{ V}$$

$$Q_2: I_D = 0.350 \text{ mA}, V_{DS} = 0.42 \text{ V}$$

$$Q_3: I_D = 0.33 \text{ mA}, V_{DS} = 0.97 \text{ V}$$

Determine the range of R_{DS} as V_{GS} is varied from 0 V to -3 V.

Solution

$$Q_0: R_{DS} = \frac{V_{DS}}{I_D} = \frac{0.13 \text{ V}}{0.360 \text{ mA}} = 361 \Omega$$

$$Q_1: R_{DS} = \frac{V_{DS}}{I_D} = \frac{0.27 \text{ V}}{0.355 \text{ mA}} = 760 \Omega$$

$$Q_2: R_{DS} = \frac{V_{DS}}{I_D} = \frac{0.42 \text{ V}}{0.350 \text{ mA}} = 1.2 \text{ k}\Omega$$

$$Q_3: R_{DS} = \frac{V_{DS}}{I_D} = \frac{0.97 \text{ V}}{0.26 \text{ mA}} = 2.9 \text{ k}\Omega$$


When V_{GS} is varied from 0 V to -3 V, R_{DS} changes from 361Ω to $2.9 \text{ k}\Omega$.

Summary

JFET Ohmic Region

Here is a circuit in which the JFET is used as a variable resistor. Notice that the drain is connected through a capacitor, which means the JFET's Q -point is at the origin.

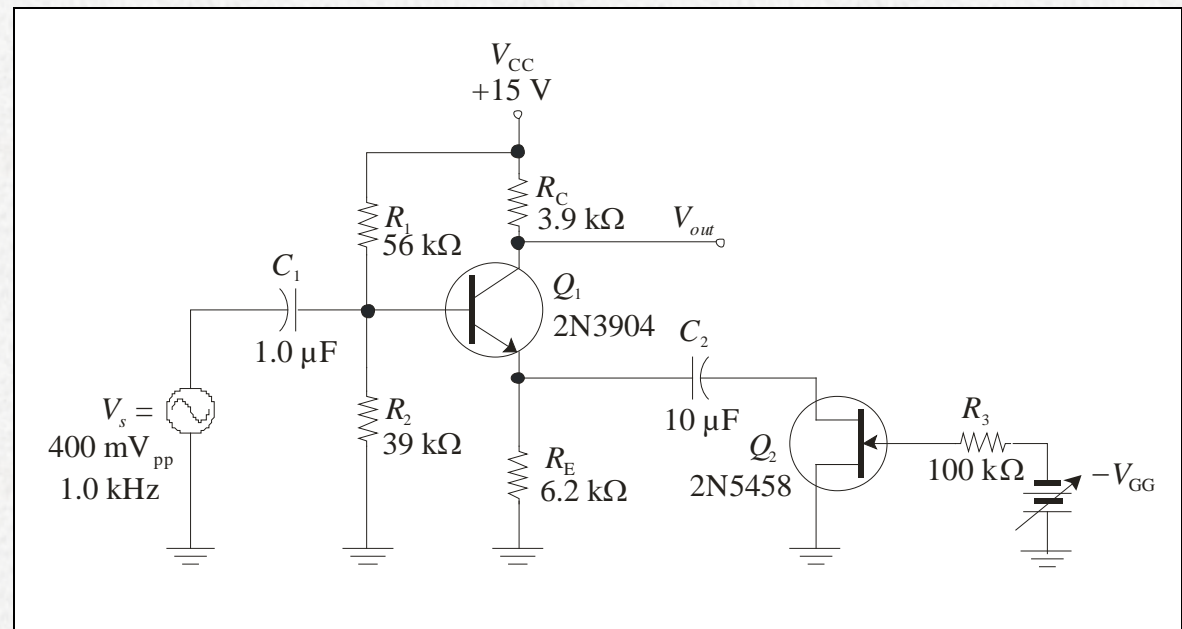The gain of the BJT depends on the dc voltage setting of V_{GG} .




Summary

The MOSFET

The metal oxide semiconductor FET uses an insulated gate to isolate the gate from the channel. Two types are the enhancement mode (E-MOSFET) and the depletion mode (D-MOSFET).

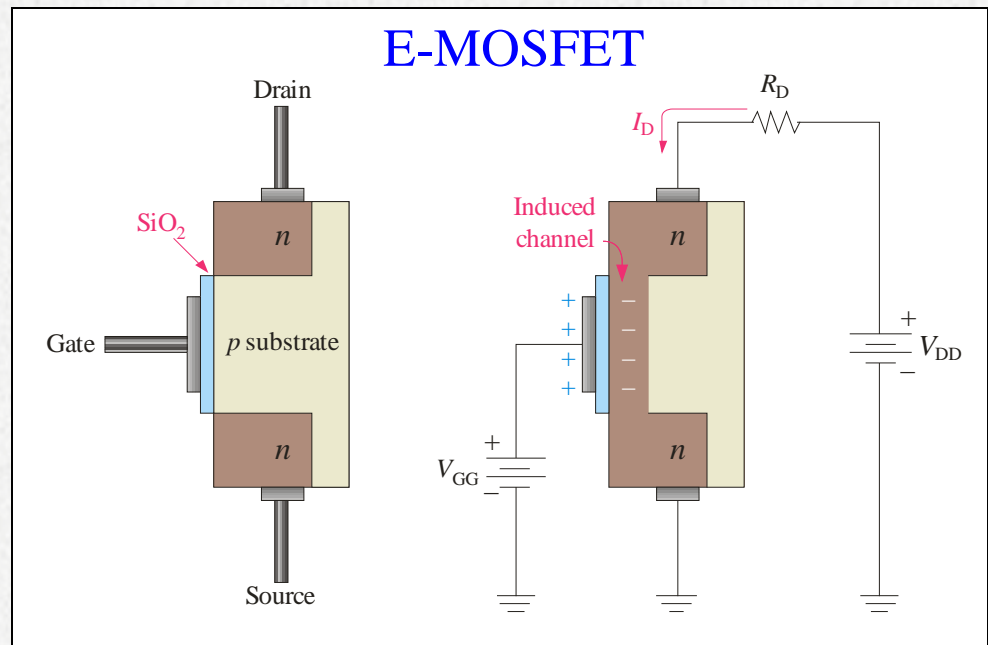An E-MOSFET has no channel until it is induced by a voltage applied to the gate, so it operates only in enhancement mode. An n -channel type is illustrated here; a positive gate voltage induces the channel.




Summary

The MOSFET

The D-MOSFET has a channel that can be controlled by the gate voltage. For an n -channel type, a negative voltage depletes the channel; and a positive voltage enhances the channel.

 
A D-MOSFET can operate in either mode, depending on the gate voltage.



Summary

The MOSFET

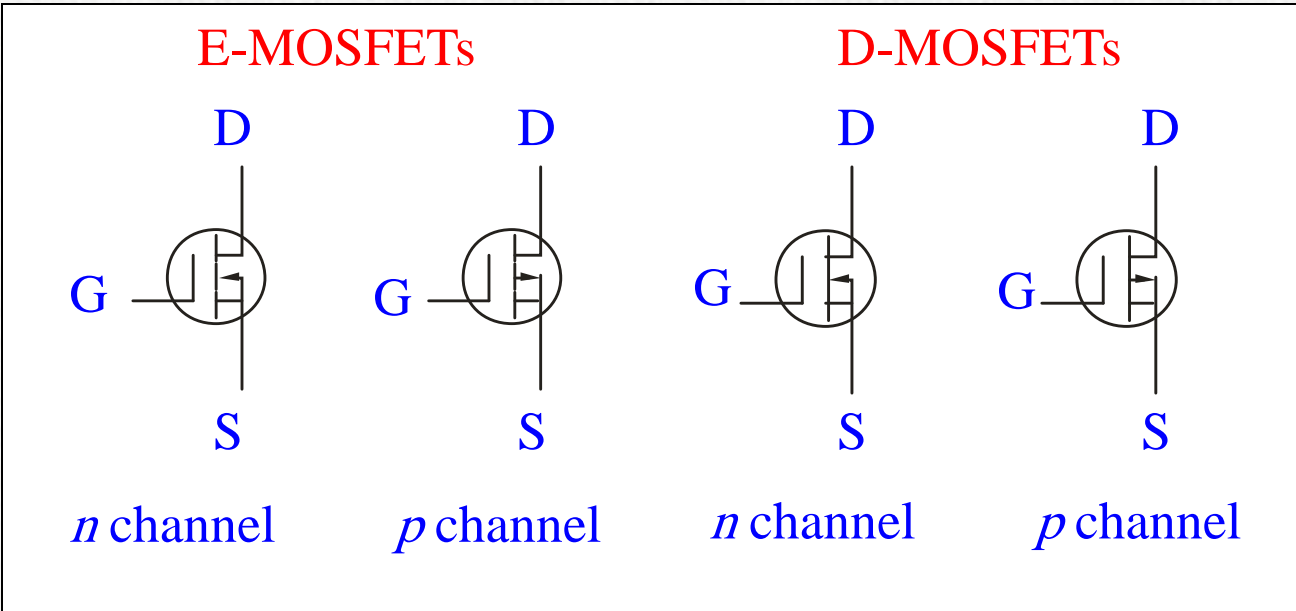MOSFET symbols are shown. Notice the broken line representing the E-MOSFET that has an induced channel. The *n* channel has an inward pointing arrow.




Summary

The MOSFET

The transfer curve for a MOSFET is has the same parabolic shape as the JFET but the position is shifted along the x -axis. The transfer curve for an n -channel E-MOSFET is entirely in the first quadrant as shown.

The curve starts at $V_{GS(th)}$, which is a nonzero voltage that is required to have channel conduction. The equation for the drain current is

$$I_D = K (V_{GS} - V_{GS(th)})^2$$

 

EXAMPLE 8–16

The datasheet (see www.fairchild.com) for a 2N7002 E-MOSFET gives $I_{D(\text{on})} = 500 \text{ mA}$ (minimum) at $V_{GS} = 10 \text{ V}$ and $V_{GS(\text{th})} = 1 \text{ V}$. Determine the drain current for $V_{GS} = 5 \text{ V}$.

Solution First, solve for K using Equation 8–4.

$$K = \frac{I_{D(\text{on})}}{(V_{GS} - V_{GS(\text{th})})^2} = \frac{500 \text{ mA}}{(10 \text{ V} - 1 \text{ V})^2} = \frac{500 \text{ mA}}{81 \text{ V}^2} = 6.17 \text{ mA/V}^2$$

Next, using the value of K , calculate I_D for $V_{GS} = 5 \text{ V}$.

$$I_D = K(V_{GS} - V_{GS(\text{th})})^2 = (6.17 \text{ mA/V}^2)(5 \text{ V} - 1 \text{ V})^2 = \mathbf{98.7 \text{ mA}}$$


Summary

The MOSFET

Recall that the D-MOSFET can be operated in either mode. For the n -channel device illustrated, operation to the left of the y -axis means it is in depletion mode; operation to the right means it is in enhancement mode.

As with the JFET, I_D is zero at $V_{GS(off)}$. When V_{GS} is 0, the drain current is I_{DSS} , which for this device is *not* the maximum current. The equation for drain current is

 
$$I_D \cong I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2$$



Summary

MOSFET Biasing

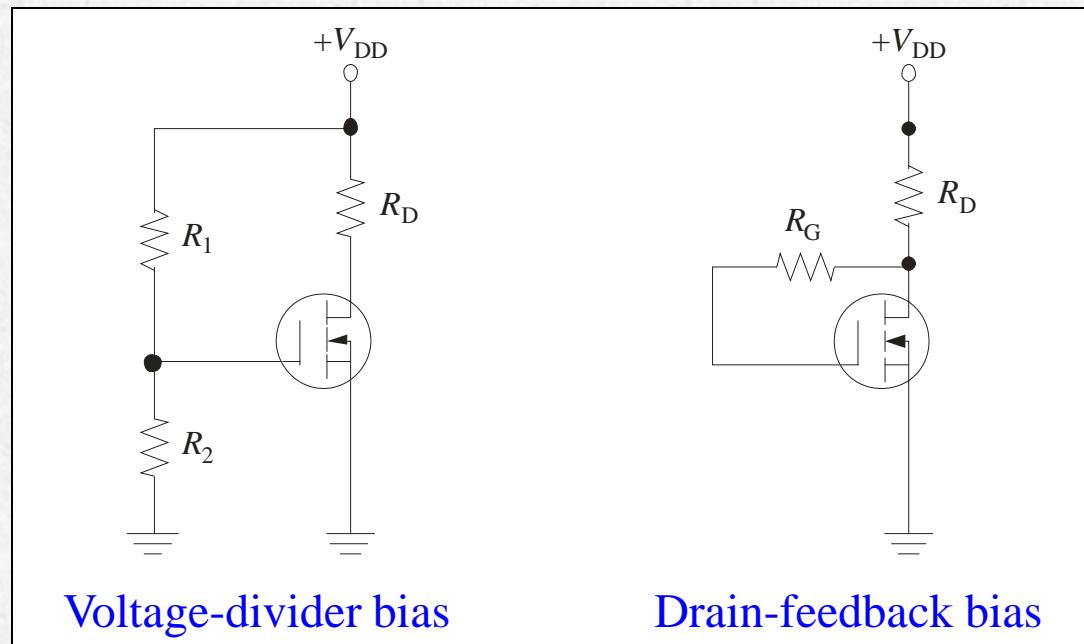E-MOSFETs can be biased using bias methods like the BJT methods studied earlier. Voltage-divider bias and drain-feedback bias are illustrated for n -channel devices.




Voltage-divider bias

Drain-feedback bias

Summary

MOSFET Biasing


The simplest way to bias a D-MOSFET is with zero bias. This works because the device can operate in either depletion or enhancement mode, so the gate can go above or below 0 V.

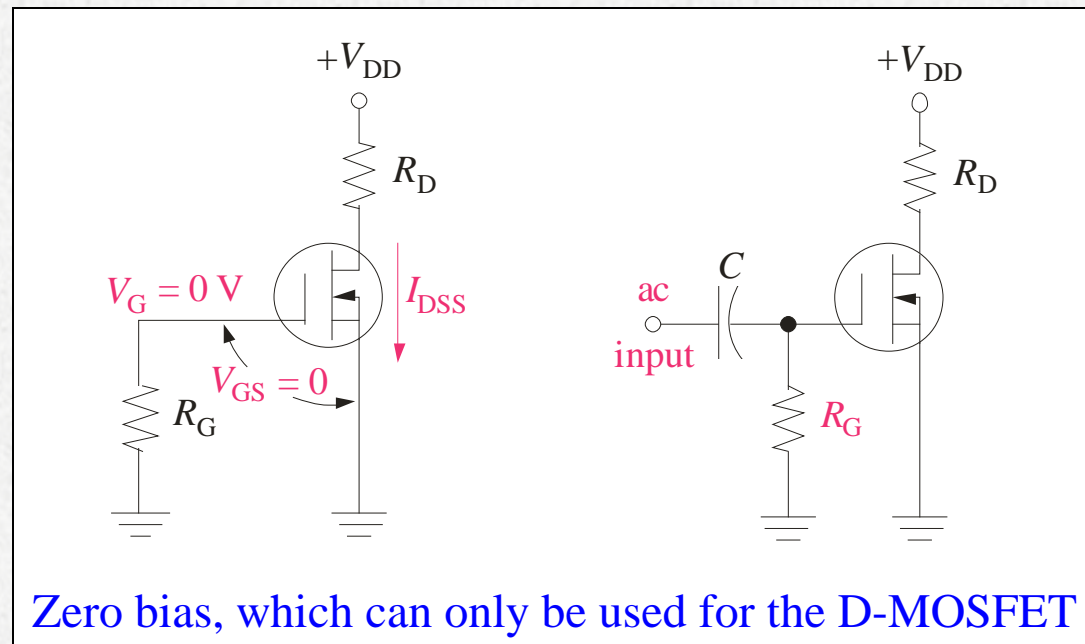

EXAMPLE 8-18

Determine V_{GS} and V_{DS} for the E-MOSFET circuit in Figure 8-47. Assume this particular MOSFET has minimum values of $I_{D(on)} = 200 \text{ mA}$ at $V_{GS} = 4 \text{ V}$ and $V_{GS(th)} = 2 \text{ V}$.

► **FIGURE 8-47**

 

Solution For the E-MOSFET in Figure 8-47, the gate-to-source voltage is

$$V_{GS} = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD} = \left(\frac{15 \text{ k}\Omega}{115 \text{ k}\Omega} \right) 24 \text{ V} = 3.13 \text{ V}$$

To determine V_{DS} , first find K using the minimum value of $I_{D(on)}$ and the specified voltage values.

$$K = \frac{I_{D(on)}}{(V_{GS} - V_{GS(th)})^2} = \frac{200 \text{ mA}}{(4 \text{ V} - 2 \text{ V})^2} = \frac{200 \text{ mA}}{4 \text{ V}^2} = 50 \text{ mA/V}^2$$

Now calculate I_D for $V_{GS} = 3.13 \text{ V}$.

$$\begin{aligned} I_D &= K(V_{GS} - V_{GS(th)})^2 = (50 \text{ mA/V}^2)(3.13 \text{ V} - 2 \text{ V})^2 \\ &= (50 \text{ mA/V}^2)(1.13 \text{ V})^2 = 63.8 \text{ mA} \end{aligned}$$

Finally, calculate V_{DS} .

$$V_{DS} = V_{DD} - I_D R_D = 24 \text{ V} - (63.8 \text{ mA})(200 \Omega) = 11.2 \text{ V}$$

Selected Key Terms

JFET Junction field-effect transistor; one of two major types of field-effect transistors.

Drain One of three terminals of a FET analogous to the collector of a BJT.

Source One of three terminals of a FET analogous to the emitter of a BJT.

Gate One of three terminals of a FET analogous to the base of a BJT.


Selected Key Terms

Transconductance (g_m) The ratio of a change in drain current to a change in gate-to-source voltage in a FET.

MOSFET Metal oxide semiconductor field effect transistor; one of two major types of FETs; sometimes called IGFET.

Depeletion In a MOSFET, the process of removing or depleting the channel of charge carriers and thus decreasing the channel conductivity.


Enhancement In a MOSFET, the process of creating a channel or increasing the conductivity of the channel by the addition of charge carriers.

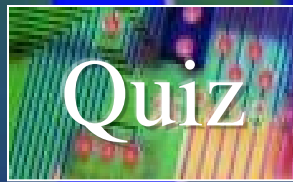The word "Quiz" is written in a white, serif font, centered within a square frame. The background of the frame is a colorful, abstract pattern of vertical and diagonal lines in shades of green, blue, and red.

Quiz

1. If an n -channel JFET has a positive drain voltage and the gate-source voltage is zero, the drain current will be

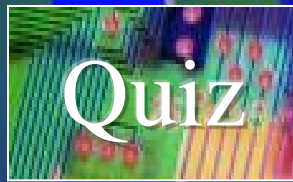- a. zero
- b. I_{DSS}
- c. I_{GSS}
- d. none of the above



Quiz


2. For a JFET, two voltages with the same magnitude but opposite signs are

- a. V_D and V_p
- b. V_D and V_S
- c. $V_{GS(th)}$ and V_{cutoff}
- d. V_p and $V_{GS(off)}$

Quiz

3. A set of characteristic curves for a JFET are shown. The blue lines represent different values of

 - a. V_{DS}
- b. V_{GS}
- c. V_S
- d. V_{th}



Quiz


4. *Transconductance* can be expressed as

a. $g_m = \frac{\Delta I_D}{\Delta V_{GS}}$

b. $g_m = \frac{\Delta I_G}{\Delta V_{DS}}$

c. $g_m = \frac{\Delta I_D}{\Delta V_{DS}}$

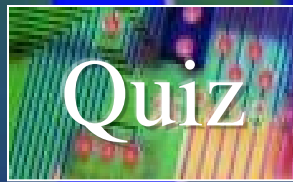d. $g_m = \frac{\Delta I_G}{\Delta V_{GS}}$



Quiz

5. JFETs *cannot* be biased using

- a. self bias
- b. voltage-divider bias
- c. zero bias
- d. current-source bias

Quiz


6. The JFET operating point in the circuit shown is

a. at the origin

b. at I_{sat}

c. at V_{CC}


d. undefined

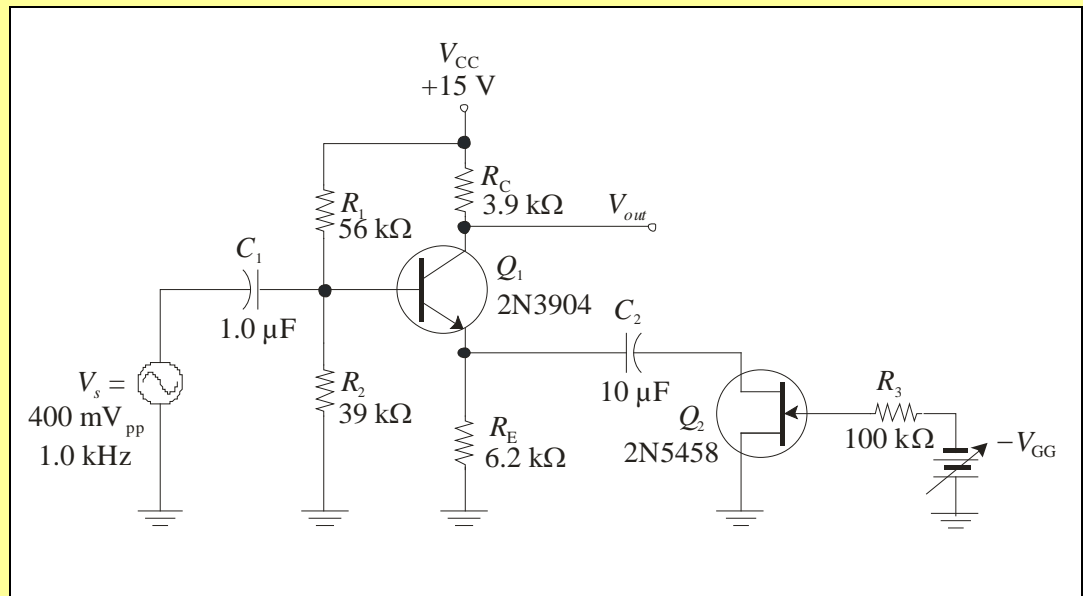

Quiz


7. The JFET in this circuit acts like a(n)

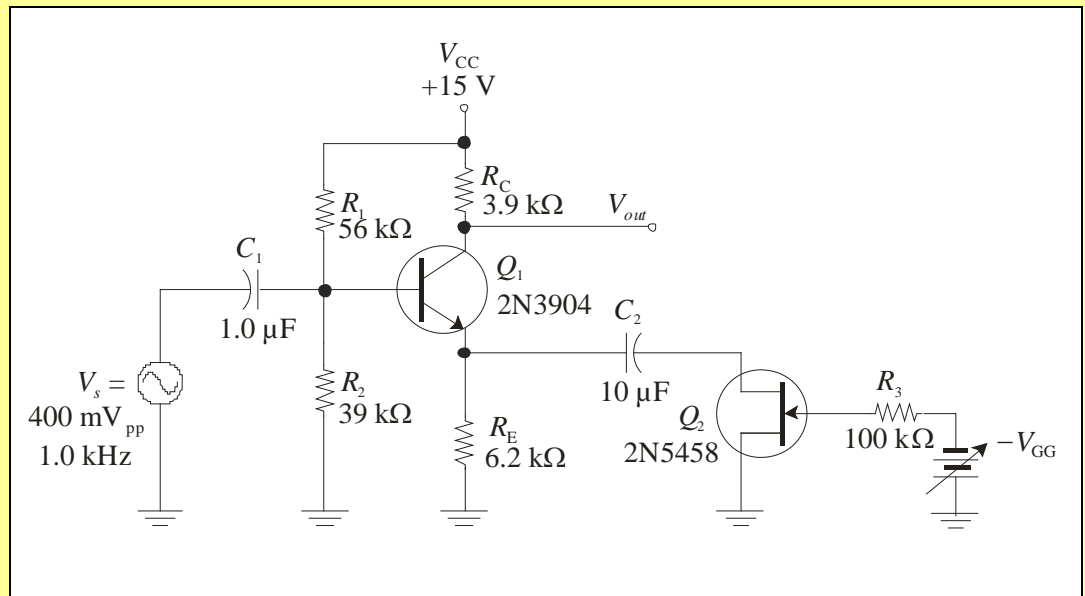- a. voltage source
- b. amplifier
- c. capacitor
- d. resistor



Quiz

 
8. The symbol for a p -channel E-MOSFET is




Quiz

9. The transfer curve shown is for an n -channel

 - a. E-MOSFET
- b. D-MOSFET
- c. JFET
- d. all of the above




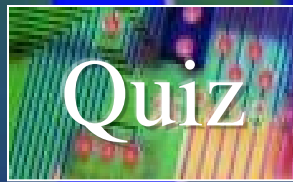The word "Quiz" is written in a white, serif font and is centered within a square frame. The background of the frame is a colorful, abstract pattern of vertical and diagonal lines in shades of green, blue, and red.

Quiz

10. A type of FET that can use the same bias method as a BJT is a(n)

- a. E-MOSFET
- b. D-MOSFET
- c. JFET
- d. all of the above

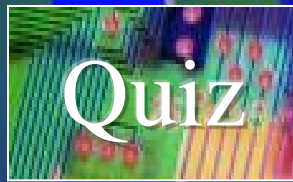The word "Quiz" is written in a white, serif font, centered within a square frame. The background of the frame is a colorful, abstract pattern of vertical lines in shades of green, blue, and red.

Quiz

Answers:

- | | |
|------|-------|
| 1. b | 6. a |
| 2. d | 7. d |
| 3. b | 8. b |
| 4. a | 9. a |
| 5. c | 10. a |