 


Lecture 42: Review of active MOSFET circuits

Prof. J. S. Smith



Observed Behavior: I_D - V_{DS}




- For low values of drain voltage, the device is like a resistor
- As the voltage is increases, the resistance behaves non-linearly and the rate of increase of current slows
- Eventually the current stops growing and remains essentially constant (current source)

Final Exam

- Covers the course from the beginning
- Date/Time: SATURDAY, MAY 15, 2004 8-11A
- Location: BECHTEL auditorium
- One page (Two sides) of notes


Observed Behavior: I_D - V_{DS}

 

As the drain voltage increases, the E field across the oxide at the drain end is reduced, and so the charge is less, and the current no longer increases proportionally. As the gate-source voltage is increased, this happens at higher and higher drain voltages.
The start of the saturation region is shaped like a parabola

Finding $I_D = f(V_{GS}, V_{DS})$

 - Approximate inversion charge $Q_N(y)$: drain is higher than the source \rightarrow less charge at drain end of channel



Average Inversion Charge

$$Q_N(y) \approx -\frac{C_{ox}(V_{GS} - V_T) + C_{ox}(V_{GD} - V_T)}{2}$$

$$Q_N(y) \approx -\frac{C_{ox}(V_{GS} - V_T) + C_{ox}(V_{GS} - V_{SD} - V_T)}{2}$$

$$Q_N(y) \approx -\frac{C_{ox}(2V_{GS} - 2V_T) - C_{ox}V_{SD}}{2} = -C_{ox}(V_{GS} - V_T - \frac{V_{DS}}{2})$$

- Charge at drain end is lower since field is lower
- Notice that this only works if the gate is inverted along its entire length
- If there is an inversion along the entire gate, it works well because Q is proportional to V everywhere the gate is inverted

Inversion Charge at Source/Drain

The charge under the gate along the gate, but we are going to make a simple approximation, that the average charge is the average of the charge near the source and drain

$$Q_N(y) \approx \frac{Q_N(y=0) + Q_N(y=L)}{2}$$

$$Q_N(y=0) = -C_{ox}(V_{GS} - V_{Tn})$$

$$Q_N(y=L) = -C_{ox}(V_{GD} - V_{Tn})$$

$$V_{GD} = V_{GS} - V_{DS}$$

Drift Velocity and Drain Current

“Long-channel” assumption: use mobility to find v

$$v(y) = -\mu_n E(y) \approx -\mu_n (-\Delta V / \Delta y) = \frac{\mu_n V_{DS}}{L}$$


And now the current is just charge per area, times velocity, times the width:

$$I_D = -WvQ_N \approx W\mu \frac{V_{DS}}{L} C_{ox}(V_{GS} - V_T - \frac{V_{DS}}{2})$$

$$I_D \approx \frac{W}{L} \mu C_{ox} (V_{GS} - V_T - \frac{V_{DS}}{2}) V_{DS}$$

Inverted Parabolas

Square-Law Characteristics

 

Square-Law Current in Saturation

Current stays at maximum (where $V_{DS} = V_{GS} - V_{TN}$)

$$I_D = \frac{W}{L} \mu C_{ox} (V_{GS} - V_T - \frac{V_{DS}}{2}) V_{DS}$$

$$I_{D,sat} = \frac{W}{L} \mu C_{ox} (V_{GS} - V_T - \frac{V_{GS} - V_T}{2}) (V_{GS} - V_T)$$


$$I_{D,sat} = \frac{W}{L} \frac{\mu C_{ox}}{2} (V_{GS} - V_T)^2$$

Measurement: I_D increases slightly with increasing V_{DS} model with linear "fudge factor"


$$I_{D,sat} = \frac{W}{L} \frac{\mu C_{ox}}{2} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

The Saturation Region

 When $V_{DS} > V_{GS} - V_{TN}$, there isn't any inversion charge at the drain ... according to our simplistic model



A Simple Circuit: An MOS Amplifier

 


Small Signal Analysis


- Step 1: Find DC operating point. Calculate (estimate) the DC voltages and currents (ignore small signals sources)
- Substitute the small-signal model of the MOSFET/BJT/Diode and the small-signal models of the other circuit elements.
- Solve for desired parameters (gain, input impedance, ...)

Small-Signal Analysis

 
Step 1. Find DC Bias – ignore small-signal source



A Simple Circuit: An MOS Amplifier

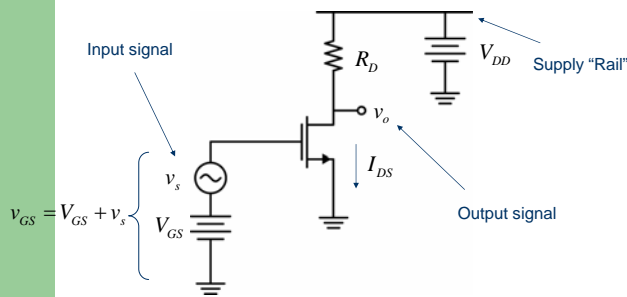


Small-Signal Modeling

 

What are the small-signal models of the DC supplies?

Shorts!

Small-Signal Models of Ideal Supplies

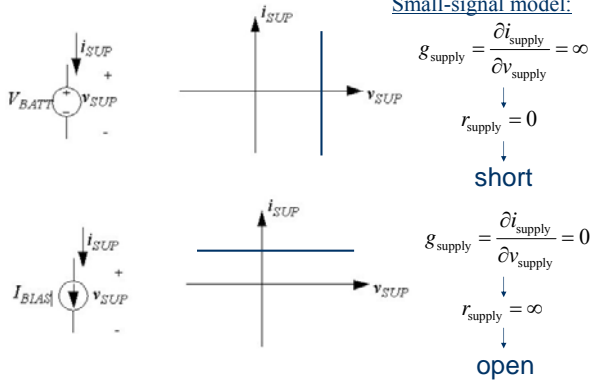

Low-Frequency Voltage Gain

Consider first $\omega \rightarrow 0$ case ... capacitors are open-circuits

$$v_{out} = -g_m v_s (R_D \parallel r_o)$$

$$A_v = -g_m (R_D \parallel r_o)$$


Transconductance

Design Variable

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T) = \frac{2I_{D,SAT}}{V_{GS} - V_T}$$

Design Variables

Small-Signal Circuit for Amplifier

 

Voltage Gain (Cont.)

Substitute transconductance:

$$A_v = \left(-\frac{2I_{D,SAT}}{V_{GS} - V_T} \right) (R_D \parallel r_o) \longrightarrow g_m R_D$$


Output resistance: typical value $\lambda_n = 0.05 \text{ V}^{-1}$

$$r_o = \left(\frac{1}{\lambda_n I_{D,SAT}} \right) = \left(\frac{1}{0.05 \cdot 0.1} \right) \text{ k}\Omega = 200 \text{ k}\Omega$$

Voltage gain:

$$A_v = -\left(\frac{2 \cdot 0.1}{0.32} \right) (25 \parallel 200) = -14.3$$

Input and Output Waveforms

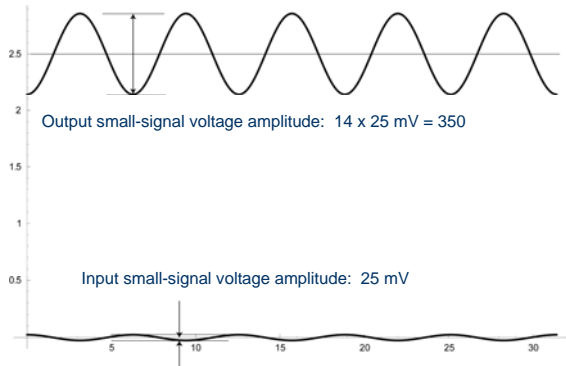

Maximum Output Amplitude

$$v_{out}(t) = -2.18 \text{ V} \cos(\omega t) \rightarrow v_s(t) = 152 \text{ mV} \cos(\omega t)$$

How accurate is the small-signal (linear) model?

$$\frac{v_s}{V_{GS} - V_{Tn}} = \frac{0.152}{0.32} \approx 0.5$$

Significant error in neglecting third term in expansion of $i_D = i_D(v_{GS})$

What Limits the Output Amplitude?

- $v_{OUT}(t)$ reaches V_{SUP} or $0 \dots$ or
- MOSFET leaves constant-current region and enters triode region


$$V_{DS} \leq V_{DS,SAT} = V_{GS} - V_{Tn} = 0.31 \text{ V}$$

$$v_{o,MIN} = V_{DS,SAT} = 0.32 \text{ V}$$


$$amp = 2.5 - 0.32 \text{ V} = 2.18 \text{ V}$$

One-Port Models (EECS 40)

 - A terminal pair across which a voltage and associated current are defined




Small-Signal Two-Port Models

 


- We assume that input port is linear and that the amplifier is *unilateral*:
 - Output depends on input but input is independent of output.
- Output port : depends linearly on the current and voltage at the input and output ports
- Unilateral assumption is good as long as “overlap” capacitance is small (MOS)

Two-Port Small-Signal Amplifiers

 


Transconductance Amplifier

 


Transresistance Amplifier

Two-Port Small-Signal Amplifiers

 


Voltage Amplifier

 


Current Amplifier


Common-Source Amplifier (again)

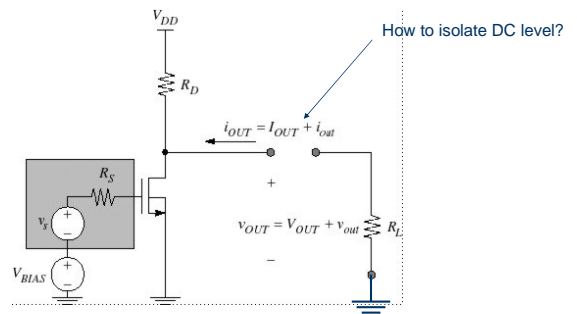


DC Bias

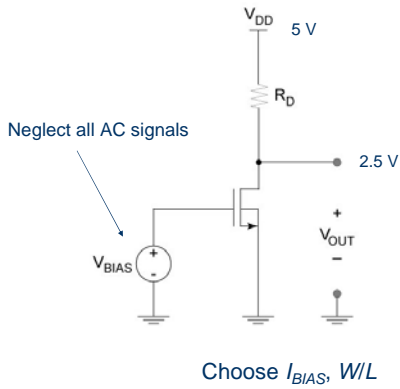

Small-Signal Analysis

 


Load-Line Analysis to find Q

 


Two-Port Parameters:

 Find R_{in} , R_{out} , G_m Generic Transconductance Amp





Two-Port CS Model

Reattach source and load one-ports:

 

Current Source Supply

  

- Solution: Use a current source!
- Current independent of voltage for ideal source

Maximize Gain of CS Amp


$$A_v = -g_m R_D \parallel r_o$$

- Increase the g_m (more current)
- Increase R_D (free? Don't need to dissipate extra power)
- Limit: Must keep the device in saturation


$$V_{DS} = V_{DD} - I_D R_D > V_{DS,sat}$$

- For a fixed current, the load resistor can only be chosen so large
- To have good swing we'd also like to avoid getting too close to saturation

CS Amp with Current Source Supply

 


Load Line for DC Biasing

 


Both the I-source and the transistor are idealized for DC bias analysis

P-Channel CS Amplifier

 

DC bias: $V_{SG} = V_{DD} - V_{BIAS}$ sets drain current $-I_{Dp} = I_{SUP}$


Two-Port Parameters

 


$$R_{in} = \infty$$

$$G_m = g_m$$


$$R_{out} = r_o \parallel r_{oc}$$

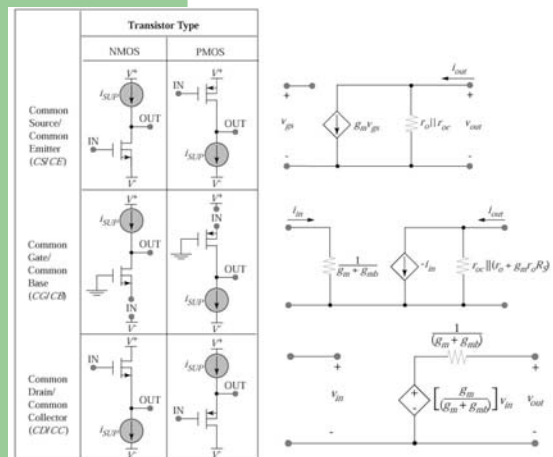


Common Gate Amplifier

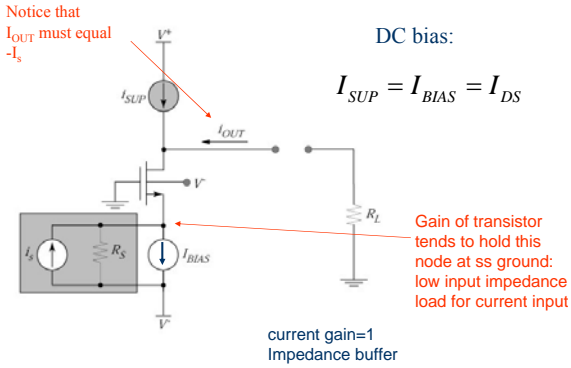

CG Input Resistance

 

CG as a Current Amplifier: Find A_i

 

$$i_{out} = i_d = -i_t$$

$$A_i = -1$$

Approximations...

- We have this messy result


$$\frac{1}{R_{in}} = \frac{i_t}{v_t} = \frac{g_m + g_{mb} + \frac{1}{r_o}}{1 + \frac{r_{oc} \parallel R_L}{r_o}}$$

- But we don't need that much precision. Let's start approximating:

$$g_m + g_{mb} \gg \frac{1}{r_o} \quad r_{oc} \parallel R_L \approx R_L \quad \frac{R_L}{r_o} \approx 0$$

$$R_{in} = \frac{1}{g_m + g_{mb}}$$

CG Output Resistance

 

$$\frac{v_s}{R_S} - g_m v_{gs} - (-g_{mb} v_s) + \frac{v_s - v_t}{r_o} = 0$$

$$v_s \left(\frac{1}{R_S} + g_m + g_{mb} + \frac{1}{r_o} \right) = \frac{v_t}{r_o}$$

Approximating the CG R_{out}

$$R_{out} = r_{oc} \parallel [r_o + g_m r_o R_S + g_{mb} r_o R_S + R_S]$$

The exact result is complicated, so let's try to make it simpler:

$$g_m \approx 500 \mu S \quad g_{mb} \approx 50 \mu S \quad r_o \approx 200 k\Omega$$

$$R_{out} \cong r_{oc} \parallel [r_o + g_m r_o R_S + R_S]$$

Assuming the source resistance is less than r_o ,

$$R_{out} \approx r_{oc} \parallel [r_o + g_m r_o R_S] = r_{oc} \parallel [r_o (1 + g_m R_S)]$$

CG Output Resistance


Substituting $v_s = i_t R_S$

$$i_t R_S \left(\frac{1}{R_S} + g_m + g_{mb} + \frac{1}{r_o} \right) = \frac{v_t}{r_o}$$

The output resistance is $(v_t / i_t) \parallel r_{oc}$

$$R_{out} = r_{oc} \parallel \left(R_S \left(\frac{r_o}{R_S} + g_m r_o + g_{mb} r_o + 1 \right) \right)$$

CG Two-Port Model

 


Function: a current buffer

- Low Input Impedance
- High Output Impedance

Common-Drain Amplifier

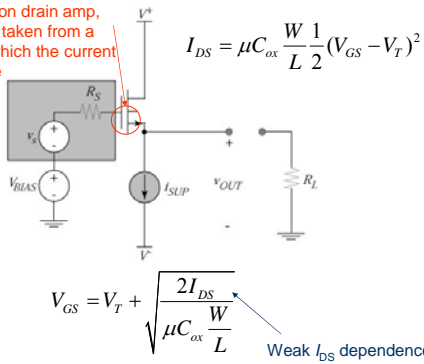In the common drain amp, the output is taken from a terminal of which the current is a sensitive function



CD Voltage Gain (Cont.)

KCL at source node: $\frac{v_{out}}{r_{oc} \parallel r_o} = g_m(v_t - v_{out}) - g_{mb}v_{out}$


$$\left(\frac{1}{r_{oc} \parallel r_o} + g_{mb} + g_m \right) v_{out} = g_m v_t$$

Voltage gain (for v_{SB} not zero):

$$\frac{v_{out}}{v_{in}} = \frac{g_m}{\frac{1}{r_{oc} \parallel r_o} + g_{mb} + g_m}$$

$$\frac{v_{out}}{v_{in}} \approx \frac{g_m}{g_{mb} + g_m} \approx 1$$

CD Voltage Gain

 


Note $v_{gs} = v_t - v_{out}$

$$\frac{v_{out}}{r_{oc} \parallel r_o} = g_m v_{gs} - g_{mb} v_{out}$$

$$\frac{v_{out}}{r_{oc} \parallel r_o} = g_m (v_t - v_{out}) - g_{mb} v_{out}$$

CD Output Resistance

 

Sum currents at output (source) node:


$$R_{out} = r_o \parallel r_{oc} \parallel \frac{v_t}{i_t} \quad i_t = g_m v_t + g_{mb} v_t$$

$$R_{out} \approx \frac{1}{g_m + g_{mb}}$$

CD Output Resistance (Cont.)

$r_o \parallel r_{oc}$ is much larger than the inverses of the transconductances \rightarrow ignore
 
$$R_{out} \approx \frac{1}{g_m + g_{mb}}$$




Function: a voltage buffer

- High Input Impedance
- Low Output Impedance

Bias sensitivity

- When a transistor biasing circuit is designed, it is important to realize that the characteristics of the transistor can vary widely, and that passive components vary significantly also.
- Biasing circuits must therefore be designed to produce a usable bias without counting on specific values for these components.
- One example is a BJT base bias in a CE amp. A slight change in the base-emitter voltage makes a very large difference in the quiescent point. The insertion of a resistor at the emitter will improve sensitivity.

	Transistor Type	
	NMOS	PMOS
Common Source/ Common Emitter (CS/CE)		
Common Gate/ Common Base (CG/CB)		
Common Drain/ Common Collector (CD/CC)		

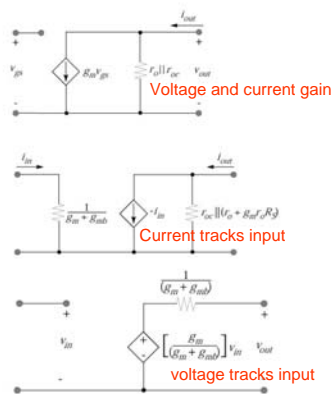


Insensitivity to transistor parameters

- Most of the circuit parameters are independent of variation of the transistor parameters, and depend only on resistance ratios. That is often a design goal, but in integrated circuits we will not want to use so many resistors.

NMOS pullup

 - Rather than using a big (and expensive) resistor, let's look at a NMOS transistor as an active pullup device




Note that when the transistor is connected this way, it is not an amplifier, it is a two terminal device. When the gate is connected to the drain of this NMOS device, it will be in saturation, so we get the equation for the drain current:

$$I_D = \left(\frac{W}{2L}\right) \mu_n C_{ox} (V_{SG} - V_{Tn})^2 (1 + \lambda_n V_{SD})$$

IV for NMOS pull-up

 - The I-V characteristic of this pull-up device:



Small signal model

- So we have:

$$I_D = \left(\frac{W}{2L}\right) \mu_n C_{ox} (V_{SG} - V_{Tn})^2 (1 + \lambda_n V_{SD})$$

$$= \left(\frac{W}{2L}\right) \mu_n C_{ox} (\Delta V - V_{Tn})^2 (1 + \lambda_n \Delta V) \approx \left(\frac{W}{2L}\right) \mu_n C_{ox} (\Delta V - V_{Tn})^2$$

- The N channel MOSFET's transconductance is:


$$g_m = \frac{\partial}{\partial V_{SG}} (i_D) \Big|_Q = \left(\frac{W}{L}\right) \mu_n C_{ox} (V_{SG} - V_{Tn}) \cong \sqrt{2 \left(\frac{W}{L}\right) \mu_n C_{ox} (I_D)}$$

- And so the small signal model for this device will be a resistor with a resistance:

$$r = \left(\frac{1}{g_m}\right)$$

Active Load

 - We can use this as the pullup device for an NMOS common source amplifier:




$$I_{D1} = \left(\frac{W_1}{2L_1}\right) \mu_n C_{ox} (V_{gs1} - V_{Tn1})^2$$

$$I_{D2} = \left(\frac{W_2}{2L_2}\right) \mu_n C_{ox} (V_{gs2} - V_{Tn2})^2$$

$$V_0 = V_{DD} - V_{gs2}$$

$$V_0 = V_{DD} - V_{t2} - \sqrt{\frac{2I_2}{\mu_n C_{ox} (W_2 / L_2)}}$$

Active Load

 


Since $I_2=I_1$ we have:

$$V_0 = V_{DD} - V_{i2} - \sqrt{\frac{2I_1}{\mu_n C_{ox} (W_2/L_2)}}$$

And since: $V_{gs1} = V_i$

$$V_0 = V_{DD} - V_{m1} - \sqrt{\frac{(W_1/L_1)}{(W_2/L_2)}} (V_i - V_{t1})$$

CMOS Diode Connected Transistor

 

- Short gate/drain of a transistor and pass current through it
- Since $V_{GS} = V_{DS}$, the device is in saturation since $V_{DS} > V_{GS} - V_T$
- Since FET is a square-law (or weaker) device, the I-V curve is very soft compared to PN junction diode


Behavior

- If the output voltage goes higher than one threshold below VDD, transistor 2 goes into cutoff and the amplifier will clip.
- If the output goes too low, then transistor 1 will fall out of the saturation mode.
- Within these limitations, this stage gives a good linear amplification.


Diode Equivalent Circuit

$$R_D = \left(\frac{di_{OUT}}{dv_{OUT}} \Big|_{i_{OUT}=0} \right)^{-1} = \frac{v_t}{i_t}$$


$$R_D \approx \frac{1}{g_m}$$

 

Equivalent Circuit:

 


The Integrated "Current Mirror"

 


- M_1 and M_2 have the same V_{GS}
- If we neglect CLM ($\lambda=0$), then the drain currents are equal
- Since λ is small, the currents will nearly mirror one another even if V_{out} is not equal to V_{GS1}
- We say that the current I_{REF} is mirrored into i_{OUT}
- Notice that the mirror works for small and large signals!

Small-Signal Resistance of I -Source

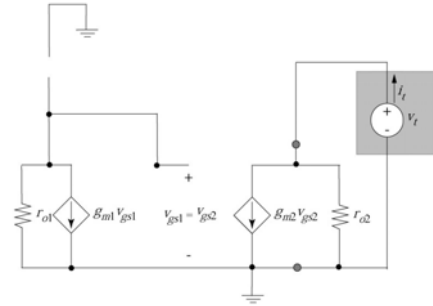


Current Mirror as Current Sink

 


- The output current of M_2 is only weakly dependent on v_{OUT} due to high output resistance of FET
- M_2 acts like a current source to the rest of the circuit

Improved Current Sources

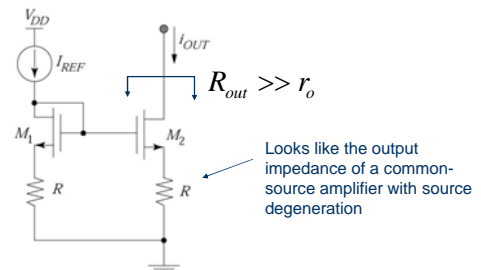Goal: increase r_{oc}
 Approach: look at *amplifier* output resistance results ... to see topologies that boost resistance



Effect of Source Degeneration

 

- Equivalent resistance loading gate is dominated by the diode resistance ... assume this is a small impedance
- Output impedance is boosted by factor $(1 + g_m R_s)$



Drawback of Cascode I-Source

Minimum output voltage to keep both transistors in saturation:


$$V_{OUT,MIN} = V_{DS4,MIN} + V_{DS2,MIN}$$

$$V_{DS2,MIN} > V_{GS2} - V_{T0} = V_{DSAT2}$$
  
$$V_{D4} > V_{DSAT2} + V_{GS4} = V_{GS2} + V_{GS4} - V_{T0}$$



Cascode (or Stacked) Current Source

 

Insight: $V_{GS2} = \text{constant}$ AND $V_{DS2} = \text{constant}$

Small-Signal Resistance r_{oc} :



$$R_o \approx (1 + g_m R_s) r_o$$

$$R_o \approx (1 + g_m r_o) r_o$$

$$R_o \approx g_m r_o^2 \gg r_o$$


Current Sinks and Sources

  Sink: output current goes to ground *Source*: output current comes from voltage supply




Current Mirrors

 We only need one reference current to set up all the current sources and sinks needed for a multistage amplifier.



Start: Two-Stage Voltage Amplifier

 • Use two-port models to explore whether the combination “works”



Results of new 2-port: $R_{in} = R_{in1}$, $R_{out} = R_{out2}$

$$A_v = -G_{m1} (R_{in2} \parallel R_{out1}) \times (-G_{m2} R_{out2})$$

$$A_v = G_{m1} G_{m2} (R_{in2} \parallel R_{out1}) (R_{out2})$$

Summary of Cascaded Amplifiers

General goals:

1. Boost the gain (except for buffers)
2. Improve frequency response
3. Optimize the input and output resistances:

	R_{in}	R_{out}
Voltage:	∞	0
Current:	0	∞
Transconductance:	∞	∞
Transresistance:	0	0

Cascading stages



Input resistance: ∞

Voltage gain (2-port parameter):

$$A_v = -g_{m1} (r_{o1} \parallel r_{oc1}) \times g_{m2} (-r_{o2} \parallel r_{oc2})$$

Output resistance:

$$R_{out} = \frac{1}{g_m + g_{mb}}$$