 



# Fast Addition: Carry Lookahead
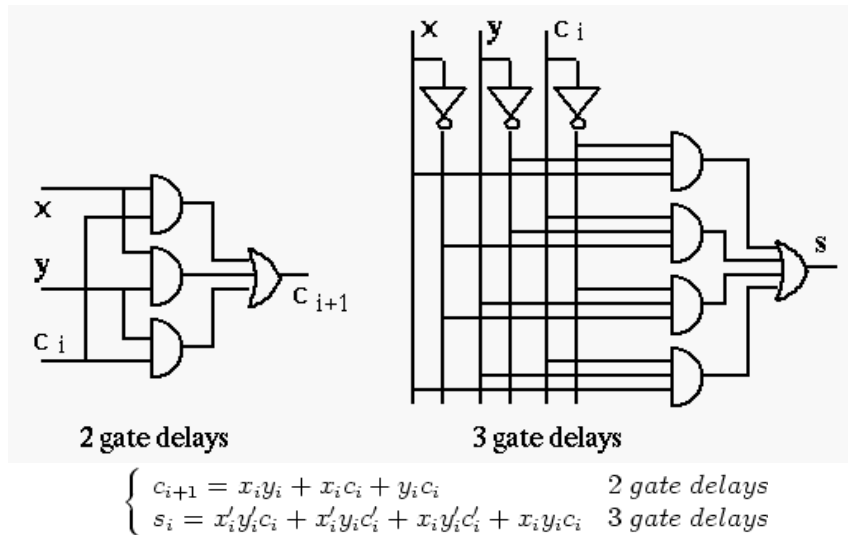
## Ripple-carry Adder

The  $n$ -bit adder below is called a ripple-carry adder, as the carry  $c_i$  needs to be passed on through all lower bits to compute the sums for the higher bits.



Recall the logic operations in the  $i^{\text{th}}$  full adder:



The total time for computing the final  $n$ -bit sum from  $X$ ,  $Y$  and  $c_0$  is  $2(n - 1) + 3$  gate delays. When  $n = 64$ , there will be 129 gate delays. How can we speed up this process?

## Carry-lookahead Adder

The bottle neck for ripple carry addition is the calculation of  $c_i$ , which takes linear time proportional to  $n$ , the number of bits in the adder. To improve this, we define

- **Generate function:**  $g_i = x_i \cdot y_i$

If  $g_i = 1$ , the  $i^{\text{th}}$  bit generates a carry,  $c_i = 1$ .

- **Propagate function:**  $p_i = x_i + y_i$

If  $p_i = 1$ , the  $i^{\text{th}}$  bit propagates a carry  $c_i$  from the  $(i - 1)^{\text{th}}$  bit to the  $(i + 1)^{\text{th}}$  bit.

Both  $g_i$  and  $p_i$  can be generated for all  $n$  bits in constant time (1 gate delay).


$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i = x_i y_i + c_i (x_i + y_i) = g_i + p_i c_i$$

*Interpretation:*  $c_{i+1}$  is either generated in the  $i^{\text{th}}$  bit ( $g_i = 1$ ), or propagated from the  $(i-1)^{\text{th}}$  bit ( $c_i = 1$  and  $p_i = 1$ ), or maybe both.


$$\begin{aligned}
 c_{i+1} &= g_i + p_i c_i \\
 &= g_i + p_i (g_{i-1} + p_{i-1} c_{i-1}) \\
 &= g_i + p_i g_{i-1} + p_i p_{i-1} (g_{i-2} + p_{i-2} c_{i-2}) \\
 &= \dots \\
 &= g_i + p_i g_{i-1} + p_i p_{i-1} g_{i-2} + p_i p_{i-1} p_{i-2} g_{i-3} + \dots + p_i p_{i-1} \dots p_1 p_0 c_0
 \end{aligned}$$

Now all  $c_i$ ,  $i = 0, \dots, n-1$  can be generated in a constant time (independent of  $n$ ) of two more gate delays after  $g_i$  and  $p_i$  are available.

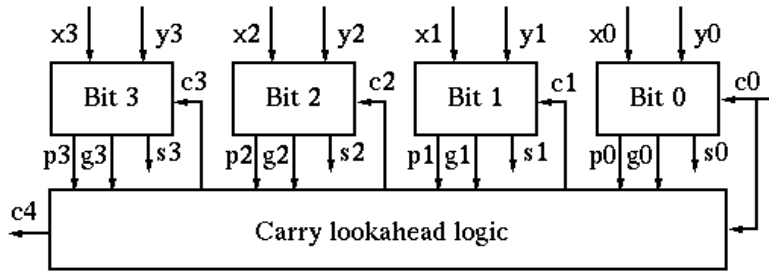*Interpretation:*  $c_{i+1} = 1$  if (a) at least one of the previous bits can generate a carry ( $g_j = 1$ ,  $j = 1, \dots, i$  or  $g_0 = c_0 = 1$ ), and (b) this carry can be propagated through all the bits to reach the  $(i+1)^{\text{th}}$  bit ( $p_i p_{i-1} \dots g_i = 1$ ).



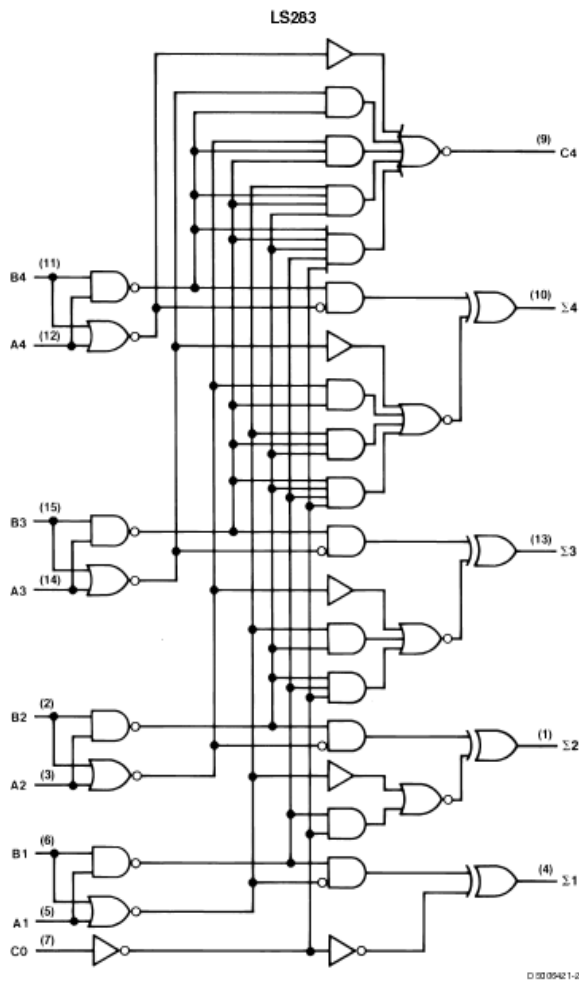This is the logic diagram of the MSI chip 74x283 for a 4-bit adder:




Operations	Number of Gate Delays
Generate $g_i$ and $p_i$	1
Generate $c_i$	2
Generate $s_i$	3
Total	6

All carries  $c_n, \dots, c_0$  can be generated by the carry-lookahead logic in two gate delays after  $g_i$  and  $p_i$  are available, and all sum bits  $s_{n-1}, \dots, s_0$  can be made available in constant time of six gate delays, independent of the number of bits in the adder.
 
### Two-level Carry Lookahead

The carry lookahead adder requires AND and OR gates with as many inputs as  $n + 1$  (for  $c_n$ ), which is impractical to realize in hardware. To compromise, we pack  $n = 4$  bits as a block with carry lookahead, and still use ripple carry between the blocks ( $c_4, c_8, c_{12}$  and  $c_{16}$ ).



There are  $n/4$  blocks in an  $n$ -bit adder, and the total gate delays can be found as:

Operations	Number of Gate Delays
Generate $g_i$ and $p_i$	1
Generate $c_i$ ( $i=1,2,3,4$ ) in block 1	2
Generate $c_i$ ( $i=5,6,7,8$ ) in block 2	2
.....	.....
Generate $s_i$	3
Total	$1 + 2(n/4) + 3$

When  $n = 64$ , the number of gate delays is 36.

To improve the speed further using the same idea, define second-level generate and propagate functions:

■  $P_i = p_{4i+3}p_{4i+2}p_{4i+1}p_{4i}$

If all four bits in a block propagate, the block propagates a carry.

■  $G_i = g_{4i+3} + p_{4i+3}g_{4i+2} + p_{4i+3}p_{4i+2}g_{4i+1} + p_{4i+3}p_{4i+2}p_{4i+1}g_{4i}$


If at least one of the four bits generates carry and it can be propagated to the MSB, the block generates a carry.

Now  $c_4$  can be generated in constant time (independent of  $n$ ):

$$c_4 = (g_3 + p_3g_2 + p_3p_2g_1 + p_3p_2p_1g_0) + (p_3p_2p_1p_0)c_0 = G_0 + P_0c_0$$

Similarly,  $c_8 = G_1 + P_1c_4$ ,  $c_{12} = G_2 + P_2c_8$  and  $c_{16} = G_3 + P_3c_{12}$  can be generated in constant time.

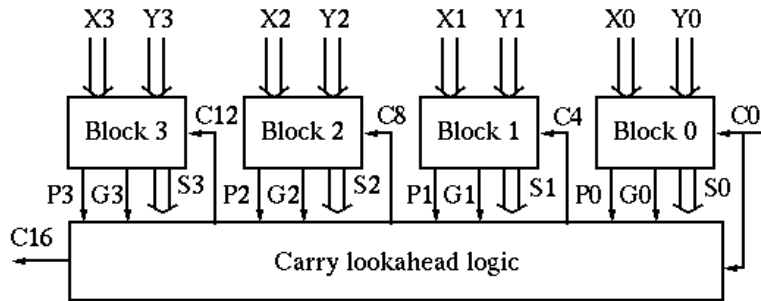Combining four blocks of 4-bit carry-lookahead adder as a super block, we get a 16-bit adder with two levels of carry-lookahead logic.



There are  $n/16$  super blocks in an  $n$ -bit adder, and the total gate delays can be found as:

Operations	Number of Gate Delays
Generate all $g_i$ and $p_i$	1
Generate all $G_i$ and $P_i$ ( $i = 0, 1, 2, \dots$ )	2
Generate $c_i$ ( $i = 4, 8, 12, 16$ ) in Block 0	2
Generate $c_i$ ( $i = 20, 24, 28, 32$ ) in Block 1	2
.....	.....
Generate $s_i$	3
Total	$1 + 2 + 2(n/16) + 3$

When  $n = 64$ , the number of gate delays is 14.

The very same idea can be carried out to a third level, with the carries  $c_{16}$ ,  $c_{32}$ ,  $c_{48}$  and  $c_{64}$  generated simultaneously by the third-level carry-look ahead logic:

$$c_{16} = G_0 + P_0 c_0$$

$$P_0 = P_3 P_2 P_1 P_0$$

$$G_0 = G_4 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0$$

Operations	Number of Gate Delays
Generate all $g_i$ and $p_i$	1
Generate all $G_i$ and $P_i$ ( $i = 0, 1, 2, \dots$ )	2
Generate all $\mathbf{G}_i$ and $\mathbf{P}_i$ ( $i = 0, 1, 2, \dots$ )	2
Generate $c_i$ ( $i = 16, 32, 48, 64$ ) in super block 0	2
.....	.....
Generate $s_i$	3
Total	$1 + 2 + 2 + 2(n/64) + 3$

When  $n = 64$ , the number of gate delays is 10.


## Multiplication

Example for multiplication:  $13 \times 11 = 143$ . The paper-and-pencil method:

$$\begin{array}{r}
 \phantom{000} 1 \ 1 \ 0 \ 1 \\
 \times \phantom{00} 1 \ 0 \ 1 \ 1 \\
 \hline
 \phantom{000} 1 \ 1 \ 0 \ 1 \\
 \phantom{00} 1 \ 1 \ 0 \ 1 \\
 \phantom{000} 0 \ 0 \ 0 \ 0 \\
 + \phantom{000} 1 \ 1 \ 0 \ 1 \\
 \hline
 1 \ 0 \ 0 \ 0 \ 1 \ 1 \ 1 \ 1
 \end{array}$$

Improve the method so that only two numbers are added each time:
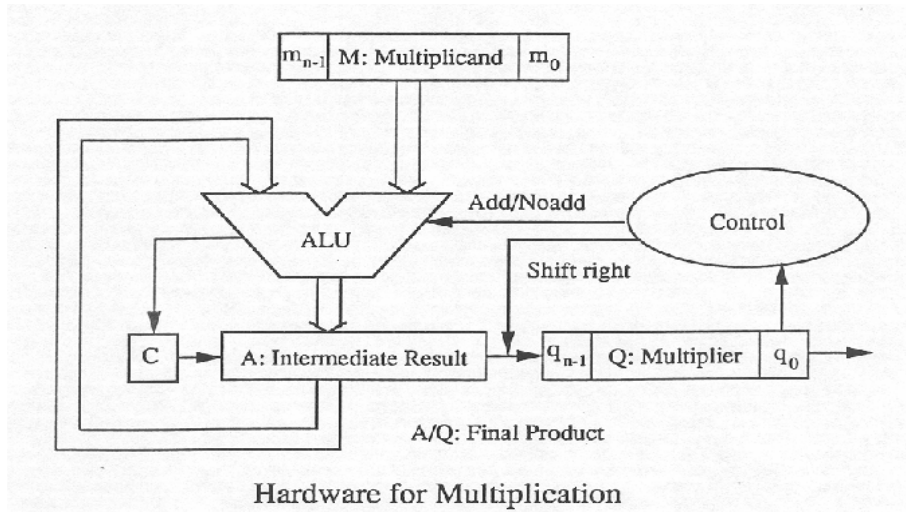
$$\begin{array}{r}
 \phantom{000} 1 \ 1 \ 0 \ 1 \\
 \times \phantom{00} 1 \ 0 \ 1 \ 1 \\
 \hline
 \phantom{000} 1 \ 1 \ 0 \ 1 \\
 + \phantom{000} 1 \ 1 \ 0 \ 1 \\
 \hline
 \phantom{000} 1 \ 0 \ 0 \ 1 \ 1 \ 1 \\
 \phantom{000} 0 \ 0 \ 0 \ 0 \\
 \hline
 \phantom{000} 1 \ 0 \ 0 \ 1 \ 1 \ 1 \\
 + \phantom{000} 1 \ 1 \ 0 \ 1 \\
 \hline
 1 \ 0 \ 0 \ 0 \ 1 \ 1 \ 1 \ 1
 \end{array}$$



### Algorithm for hardware multiplication

```

Do n times:
{
    if ( $q_0=0$ ) then  $A \leftarrow A+M$ ;
    right shift  $A$  and  $Q$  by 1 bit
}

```

Note: When  $A$  and  $Q$  are right shifted, the MSB of  $A$  is filled with 0 and the LSB of  $A$  becomes the MSB of  $Q$ , and the LSB of  $Q$  is lost.

Continuing the example  $13 \times 11 = 143$ : Always use three registers  $M$ ,  $A$ , and  $Q$ . Initially, the multiplicand is  $13 = 1101_2$  in  $M$ , the multiplier is  $11 = 1011_2$  in  $Q$  and  $A$  is zero.


	[M]	1101		
	[A]	0000	[Q]	1011
$q_0=1$ , add $A=[A]+[M]$	+	1101		
	0	1101		1011
right shift $A/Q$	0	0110		1101
$q_0=1$ , add $A=[A]+[M]$	+	1101		
	1	0011		1101
right shift $A/Q$	0	1001		1110
$q_0=0$ , right shift $A/Q$	0	0100		1111
$q_0=1$ , add $A=[A]+[M]$	+	1101		
	1	0001		1111
right shift $A/Q$	0	1000		1111

The upper half of the product  $010001111_2$  is in register  $A$ , while the lower half is in register  $Q$ .

## Division

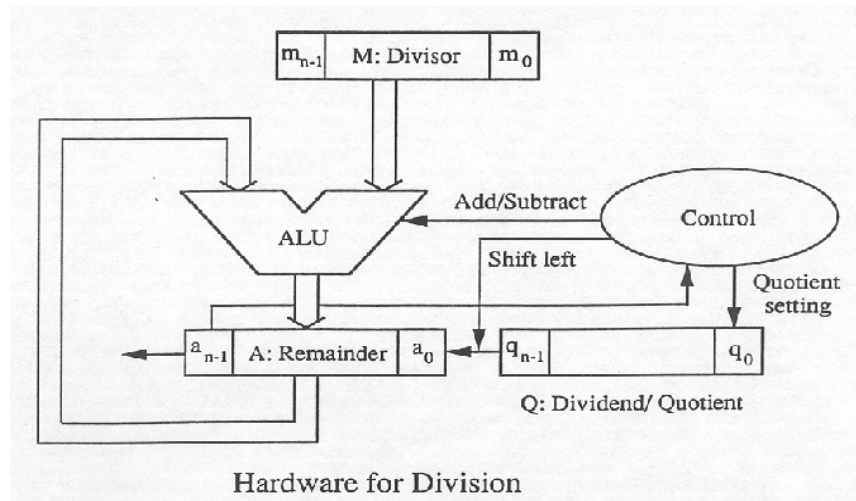Example for division:  $27 \div 13 = 21\frac{1}{13}$

$$\begin{array}{r}
 \text{Quotient} \\
 \text{Divisor } 1101 \overline{)100010010} \\
 \underline{-1101} \\
 10000 \\
 \underline{-1101} \\
 1110 \\
 \underline{-1101} \\
 1 \\
 \text{Remainder}
 \end{array}$$



Algorithm for hardware division (restoring):

```

Do n times:
{
    left shift A and Q by 1 bit;
    A ← A - M;
    if A < 0 (a_{n-1} = 1) then q_0 ← 0, A ← A + M (restore)
    else q_0 ← 1;
}
    
```

Note: When  $A$  and  $Q$  are left shifted, the MSB of  $Q$  becomes the LSB of  $A$  and the MSB of  $A$  is lost. The LSB of  $Q$  is made available for the next quotient bit.

Example:  $8 \div 3 = 2\frac{2}{3}$

Initially, the divisor  $3 = 0011_2$  is in register  $M$ , the dividend  $8 = 1000_2$  is in register  $Q$  and register  $A$  is zero.

	[M]	0011		
	[A]	0000	[Q]	1000
left shift A/Q		0001		000 <sub>2</sub>
$A = [A] - [M]$	+	1101		
$A < 0$		1110		0000
$A = [A] + [M]$	+	0011		
		0001		0000
left shift A/Q		0010		000 <sub>2</sub>
$A = [A] - [M]$	+	1101		
$A < 0$		1111		0000
$A = [A] + [M]$	+	0011		
		0010		0000
left shift A/Q		0100		000 <sub>2</sub>
$A = [A] - [M]$	+	1101		
$A > 0$		0001		0001
left shift A/Q		0010		001 <sub>2</sub>
$A = [A] - [M]$	+	1101		
$A < 0$		1111		0010
$A = [A] + [M]$	+	0011		
		0010		0010

Note that subtraction by 3 is implemented by adding its 2s-complement  $-3 = 1101_2$ . The quotient  $2 = 0010_2$  is in register  $Q$  and the remainder  $2 = 0010_2$  is in register  $A$ .

### Non-restoring Division

In the algorithm above, if the subtraction produces a non-negative result ( $A \geq 0$ ), registers  $A$  and  $Q$  are left shifted and the next subtraction is carried out. But if the subtraction produces a negative result ( $A < 0$ ), the dividend need be first restored by adding the divisor back before left shift  $A$  and  $Q$  and the next subtraction:

- If  $A \geq 0$ , then  $2A - M$  (left shift and subtract);
- If  $A < 0$ , then  $2(A + M)$  (restore, left shift and subtract).

When  $A < 0$ , the restoration is avoided by combining the two steps. This leads to a faster non-restoring division algorithm:

Algorithm for hardware division (non-restoring):

```

Do n times:
{
    left shift A and Q by 1 bit;
    if (previous A >= 0) then A ← A - M
    else A ← A + M;
    if (current A >= 0) then q0 ← 1
    else q0 ← 0;
}
if (A < 0) then A ← A + M (remainder must be positive);

```



	[M]	0011		
	[A]	0000	[Q]	1000
left shift A/Q		0001		000.
A=[A]-[M]	+	1101		
A < 0		1110		0000
left shift A/Q		1100		000.
A = [A] + [M]	+	0011		
A < 0		1111		0000
left shift A/Q		1110		000.
A = [A] + [M]	+	0011		
A > 0		0001		0001
left shift A/Q		0010		001.
A = [A] - [M]	+	1101		
A < 0		1111		0010
A = [A] + [M]	+	0011		
		0010		0010

The quotient  $2 = 0010_2$  is in register  $Q$  and the remainder  $2 = 0010_2$  is in register  $A$ . The restoring division requires two operations (subtraction followed by an addition to restore) for each zero in the quotient. But non-restoring division only requires one operation (either addition or subtraction) for each bit in the quotient.

## Signed Multiplication

The following example shows that signed 2s-complement representation can be used to represent negative operands as well as positive ones in multiplication.

Example:  $(-5) \times (-4) = 20$

4: 000100; -4: 111110; 5: 000101; -5: 111011

Use  $n = 6$  bits to represent the product.

We first represent both operands in signed 2s-complement, and then carry out the normal multiplication:

$$\begin{array}{r}
 \phantom{11111} \phantom{00} \phantom{11} \phantom{00} \phantom{11} \\
 \phantom{11111} \phantom{00} \phantom{11} \phantom{00} \phantom{11} \phantom{00} \\
 \phantom{11111} \phantom{00} \phantom{11} \phantom{00} \phantom{11} \phantom{00} \phantom{11} \\
 \phantom{11111} \phantom{00} \phantom{11} \phantom{00} \phantom{11} \phantom{00} \phantom{11} \phantom{00} \\
 \phantom{11111} \phantom{00} \phantom{11} \phantom{00} \phantom{11} \phantom{00} \phantom{11} \phantom{00} \phantom{11} \\
 \hline
 1111100011 \\
 111100011 \\
 11100011 \\
 1100011 \\
 \hline
 . . . . . 010100
 \end{array}$$

The last six bits of the result are  $010100_2$ , representing a positive product ( $20_{10}$ ). Note:

- Both positive and negative operands should be properly sign extended whenever needed.
- When the multiplier is negative represented in signed 2s-complement, each 1 added in front due to the sign extension requires an addition of the multiplicand to the partial product. However, you only need to consider enough bits to guarantee  $n$  bits required in the result.

As shown in a homework problem, this method works in all cases of both positive and negative multiplicands and multipliers.

## Fast Multiplication: Booth's Algorithm

Booth's algorithm serves two purposes:

- Fast multiplication (when there are consecutive 0s or 1s in the multiplier)
- Signed multiplication

First, consider two decimal multiplications:  $98765 \times 10001$  and  $98765 \times 9999$ . It is obvious that if straight forward multiplication is used, the first one is easier than the second, as only two single-digit multiplications are needed for the first, while four are needed for the second. However, as we also realize that:

$$98765 \times 10001 = 98765 \times (10000 + 1) = 98765 \times 10000 + 98765$$

and

$$98765 \times 9999 = 98765 \times (10000 - 1) = 98765 \times 10000 - 98765$$

the two multiplications should be equally easy.

### Example 1

If there is a sequence of 0s in the multiplier, the multiplication is easy, as all 0s can be skipped.

$$\begin{array}{r} 22 \\ \times 17 \\ \hline 154 \\ + 22 \\ \hline 374 \end{array} \quad \begin{array}{r} 010110 \\ \times 010001 \\ \hline 010110 \\ + 010110 \\ \hline 010110110 \end{array}$$

### Example 2

However, it does not help if there is a sequence of 1s in the multiplier. We have to go through each one of them:

$$\begin{array}{r} 22 \\ \times 14 \\ \hline 88 \\ + 22 \\ \hline 308 \end{array} \quad \begin{array}{r} 010110 \\ \times 001110 \\ \hline 010110 \\ 010110 \\ + 001110 \\ \hline 01001101100 \end{array}$$

How can we enjoy a sequence of 1s as well as a sequence of 0s? We first realize that

$$001110 = 010000 - 000010$$

or, in general, a string of 1s in the multiplier  $A$  can be written as:

$$\begin{array}{r} d d \underline{0} \underline{1} \underline{1} \dots \underline{1} \underline{1} \underline{0} d d \\ = d d \underline{1} \underline{0} \dots 0 0 0 d d \\ - 0 0 0 0 \dots 0 \underline{1} \underline{0} 0 0 \end{array}$$

where  $d$  is "don't care" (either 0 or 1). If we define the first part above as  $A_{\text{leftend}} = dd10\dots00dd$  and the second part as  $A_{\text{rightend}} = 0000\dots1000$ , then the multiplication becomes:

$$B \times A = B \times (A_{\text{leftend}} - A_{\text{rightend}}) = B \times A_{\text{leftend}} - B \times A_{\text{rightend}}$$

In other words, only the two ends of a string of 1s in the multiplier need to be taken care of. At the left end, the multiplicand is added to the partial product, while at the right end, the multiplicand is subtracted from the partial product. The above multiplication can therefore be written as:

0 1 0 1 1 0		0 1 0 1 1 0
x 0 <u>0</u> <u>1</u> <u>1</u> <u>0</u>		x 0 <u>0</u> <u>1</u> <u>1</u> <u>0</u>
0 1 0 1 1 0		0 1 0 1 1 0
- 0 1 0 1 1 0		+ 1 1 1 1 0 1 0 1 0
0 1 0 0 1 1 0 1 0 0		0 1 0 0 1 1 0 1 0 0

On the right side above, the subtraction is carried out by adding 2s-complement. We observe that if there is a sequence of 1s in the multiplier, only the two ends need to be taken care of, while all 1s in between do not require any operation.

Booth's algorithm for multiplication is based on this observation. To do a multiplication  $B \times A$ , where  $B = b_{n-1}b_{n-2} \dots b_1b_0$  is the multiplicand and  $A = a_{n-1}a_{n-2} \dots a_1a_0$  is the multiplier, we check every two consecutive bits in  $A$  at a time:

$a_i$	$a_{i-1}$	$a_{i-1} - a_i$	Operations
0	0	0	in middle of string of 0. No operation.
1	0	-1	beginning of string of 1. Subtract B from partial product
1	1	0	in middle of string of 1. No operation.
0	1	1	end of string of 1. Add B to partial product

where  $i = 0, 1, \dots, n - 1$ , and when  $i = 0$ ,  $a_{i-1} = a_{-1} = 0$ .

Why does it work? What we did can be summarized as the following:

$$\begin{aligned}
 \text{Product} &= (a_{-1} - a_0) \times B \times 2^0 + (a_0 - a_1) \times B \times 2^1 + \dots + (a_{n-2} - a_{n-1}) \times 2^{n-1} \\
 &= B \times \left( -a_{n-1} \times 2^{n-1} + \sum_{i=0}^{n-2} a^i \times 2^i \right) \\
 &= B \times \text{Val}(A)
 \end{aligned}$$

Recall that the value of a signed 2s-complement number (either positive or negative) can be found by

$$\text{Val}(A = a_{n-1} \dots a_0) = -a_{n-1} \times 2^{n-1} + \sum_{i=0}^{n-2} a^i \times 2^i$$

## Another Example

Assume  $n = 7$  bits available. Multiply  $B = 22 = 0010110_2$  by  $A = -34 = 1011110_2$ . First represent both operands and their negation in signed 2s-complement, then carry out the multiplication in the hardware:

$q_i q_{i-1}$	Action	[M]	[A]	[Q]	
		0010110	0000000	1011110	0
00	right shift		0000000	0101111	0
10	-B	+	1101010		
			1101010	0101111	0
	right shift		1110101	0010111	1
11	right shift		1111010	1001011	1
11	right shift		1111101	0100101	1
11	right shift		1111110	1010010	1
01	+B	+	0010110		
			0010100	1010010	1
	right shift		0001010	0101001	0
10	-B	+	1101010		
			1110100	0101001	0
	right shift		1111010	0010100	1

The upper half of the final result 1111010 0010100 is in register [A] while the lower half is in register [Q]. The product is given in signed 2s-complement and its actual value is negative of the 2s-complement:

$$B \times A = \overline{1111010\ 0010100} = -00001011101100 = -748_{10}$$

Also note that:

- As the operands are in signed 2s-complement form, the arithmetic shift is used for the right shifts above, i.e., the MSB bit (sign bit) is always repeated, while all other bits are shifted to the right. This guarantees proper sign extension for both positive and negative values represented in signed 2s-complement.
- When the multiplicand is negative, represented by signed 2s-complement, it needs to be complemented again for subtraction (when the LSB of the multiplier is 1 and the extra bit is 0, i.e., the beginning of a string of 1s).