

POLYTECHNIC UNIVERSITY OF BARI

DEI - Department of Electrical and Information Engineering

Introduction to Simulink



MATLAB SIMULINK[®]

Eng. Domenico Buongiorno Prof. Vitoantonio Bevilacqua



Simulink

- Simulink is a <u>graphical programming environment</u> for modeling, simulating and analyzing multidomain dynamical systems.
- Its primary interface is a graphical block diagramming tool and a customizable set of block libraries.
- It offers tight <u>integration</u> with the rest of the <u>MATLAB</u> environment and can either drive MATLAB or be scripted from it.
- Simulink is widely used in <u>automatic control</u> and <u>digital signal processing</u> for multidomain simulation and Model-Based Design.







Why Simulink?

- Simulink, <u>makes simulations easier to achieve</u>, by using blocks that correspond to codes you do not see.
- With Simulink, the model of the system you want to simulate is more readable, because it is represented by graphics.
- You can use Matlab to simulate a system, but you have to program your own routines added to the ones that are provided by Matlab.
- Simulink easily allows to simulate <u>hybrid systems</u> that include both continuous and discrete blocks.





Why Simulink?

- Simulink easily allows to design and simulate <u>complex state machines and flow</u> <u>charts.</u>
- Coupled with another of MathWorks's products, Simulink can automatically <u>generate C source code for real-time</u> implementation of systems.



 <u>Simulink Real-Time</u> (formerly known as xPC Target), together with x86-based real-time systems, is an environment for <u>simulating and testing Simulink and</u> <u>Stateflow models in real-time on the physical system</u>.







Why Simulink?

Simulink also supports specific embedded targets (e.g. Arduino, Raspberry).







RLC Series Circuit: Step Response

$$V_{in}(t) = Ri(t) + L \frac{di(t)}{dt} + V_C(t)$$
$$V_{out}(t) = V_C(t) = \frac{1}{C} \int_0^t i(\tau) d\tau$$



State Variables:

- $X_A(t) = V_c(t)$
- $X_B(t) = i(t)$

Initial state conditions

- $\bullet \quad X_A(0) = 0 V$
- $\bullet \quad X_B(0) = 0 A$

Electrical parameters:

- $V_{in}(t) = 5 V$
- $R = 2 \Omega$
- *L* = 2 *H*
- C = 0.5 F





RLC Series Circuit: Step Response

$$V_{in}(t) = Ri(t) + L \frac{di(t)}{dt} + V_C(t)$$
$$V_{out}(t) = V_C(t) = \frac{1}{c} \int_0^t i(\tau) d\tau$$

State Variables:

•
$$X_A(t) = V_c(t)$$

• $X_B(t) = i(t)$

$$\dot{X}_A = \frac{1}{c} X_B(t)$$
 $\dot{X}_B(t) = \frac{1}{L} (V_{in}(t) - RX_B(t) - X_A(t))$









RLC Series Circuit: Step Response







RLC Series Circuit: Bode plot with Matlab



Engineering

DUSTRIAL FORMATICS

RLC Series Circuit: Resonance



Engineering

RLC Series Circuit: Resonance







RLC Series Circuit: Resonance







PID Tuning











thank you!

Email: domenico.buongiorno@poliba.it vitoantonio.bevilacqua@poliba.it