 


# INTRODUCTION TO VHDL

**K. Siozios**

Section of Electronics and Electronic Computers  
Department of Physics  
Aristotle University of Thessaloniki (AUTH), Greece



**“It is not the strongest of the species that survive,  
nor the most intelligent,  
but the one most responsive to change”**

**Charles Darwin**

It is not the strongest (**ASIC**) of the species that survive,  
nor the most intelligent (**CPU**),  
but the one most responsive to change (**FPGA**)

Charles Darwin

# Reconfigurable Architectures Today

**Google... statistics**

Google **asic**  
 About 21,600,000 results

Google **fpga**  
 About 24,800,000 results

**Reconfigurable Architectures**

Hardware building blocks + software

1980 1990 2000 2010

TL c/p/DSP ASIC Reco

2009 2011 2014 2017 2020

0.42	1.00	2.56	3.27	14.06
0.60	1.00	3.52	3.73	25.10
0.87	1.00	3.87	8.73	23.10

Total wire-length (Km) vs Year (2003-2015)

Constant die size = 140mm

Relative Delay vs Process Technology Node (nm)


2:1, 9:1

5 Km !!!

Popularity

Progress

End of Device Scaling?

 

# Moore's Law

---

 



Fig. 2 Number of components per integrated function for minimum cost per component extrapolated vs time.

*"The number of transistors incorporated in a chip will approximately double every 24 months."*

—Gordon Moore, Intel Co-Founder

# Moore's Law in Microprocessors

## 35 YEARS OF MICROPROCESSOR TREND DATA

 

Original data collected and plotted by M. Horowitz, F. Labonte, O. Shacham, K. Olukotun, L. Hammond and C. Batten  
Dotted line extrapolations by C. Moore

K. Siozios, Department of Physics, Aristotle University of Thessaloniki

# Moore's Law: CPUs and FPGAs


---

CPU	Transistor count	Process
Pentium 4	42,000,000	180 nm
Atom	47,000,000	45 nm
AMD K8	105,900,000	130 nm
Itanium 2	220,000,000	130 nm
Cell	241,000,000	90 nm
Core 2 Duo	291,000,000	65 nm
Core i7 (Quad)	731,000,000	45 nm
Six-Core Xeon 7400	1,900,000,000	45 nm
POWER6	789,000,000	65 nm
16-Core SPARC T3	1,000,000,000	40 nm
8-core POWER7	1,200,000,000	45 nm
Quad-core z196	1,400,000,000	45 nm
Dual-Core Itanium 2	1,700,000,000	90 nm

FPGA	Transistor count	Process
Virtex	~70,000,000	
Virtex-E	~200,000,000	
Virtex-II	~350,000,000	130 nm
Virtex-II PRO	~430,000,000	
Virtex-4	1,000,000,000	90 nm
Virtex-5	1,100,000,000	65 nm
Stratix IV	2,500,000,000	40 nm
Stratix V	3,800,000,000	28 nm
Virtex-7	6,800,000,000	28 nm



# Productivity Trends

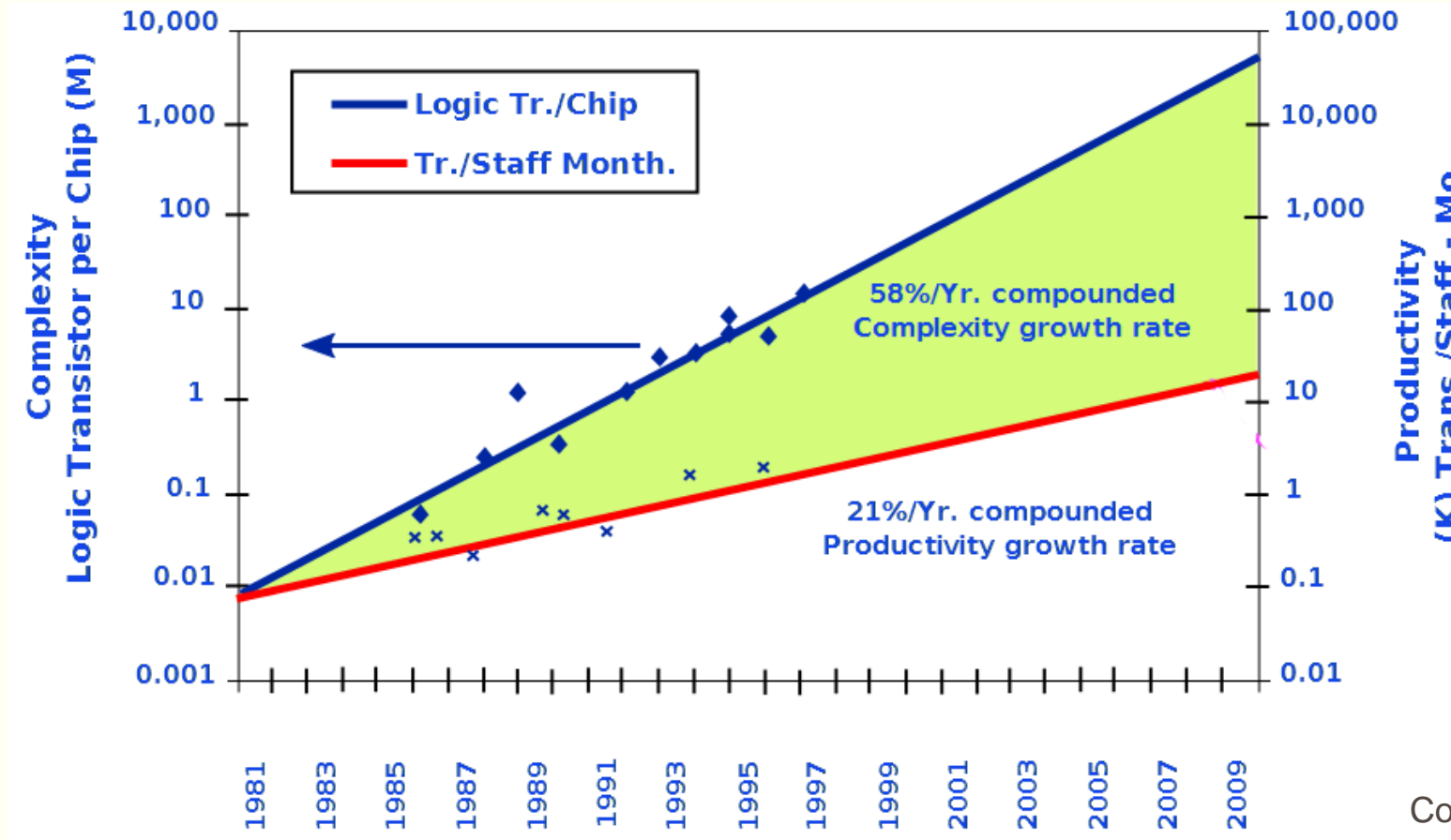


Courtesy, ITRS Roadmap

Source: Sematech


## Complexity outpaces design productivity

K. Siozios, Department of Physics, Aristotle University of Thessaloniki


# Abstraction Drives Design Productivity

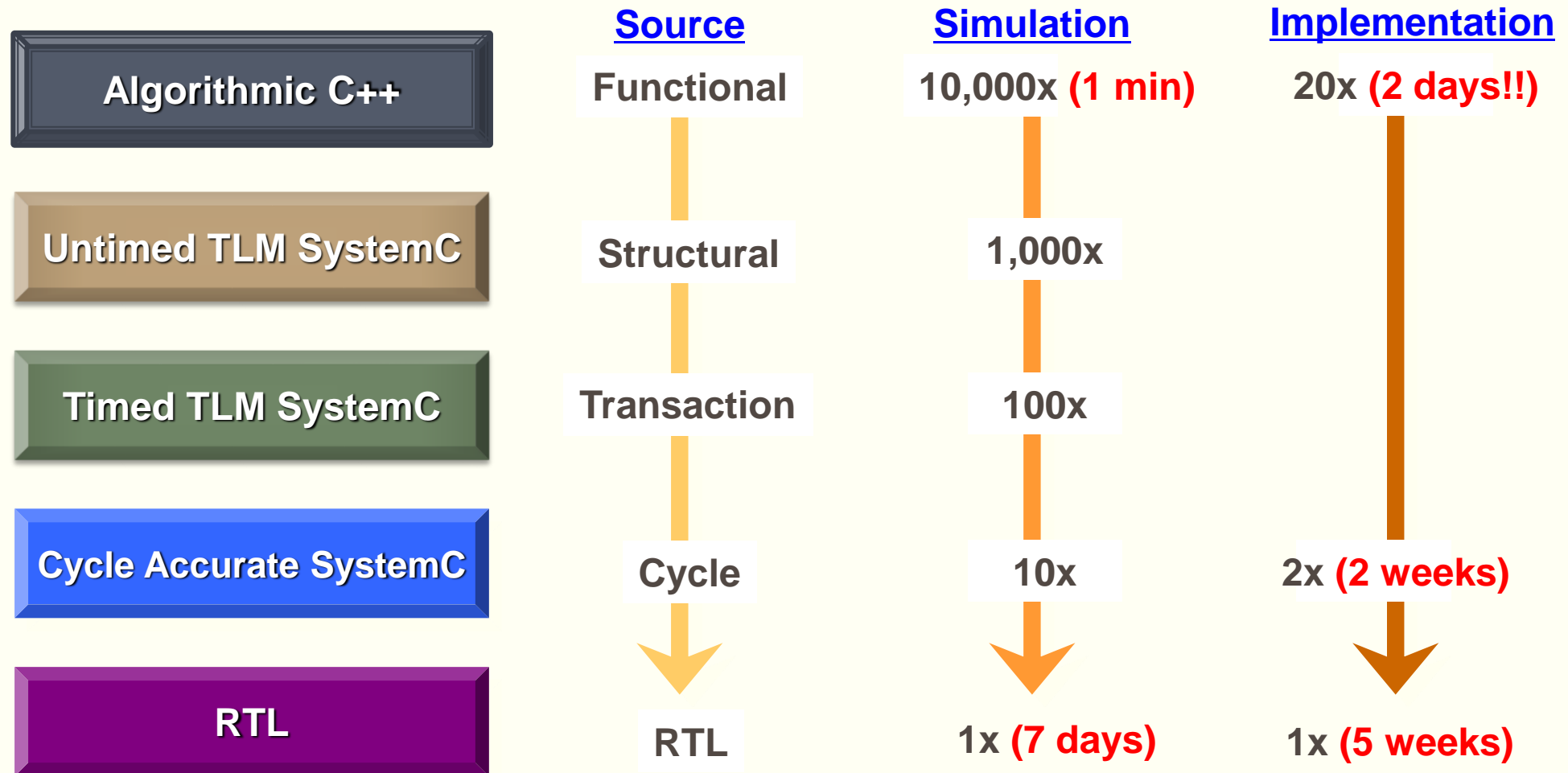


# Design Languages & Tasks

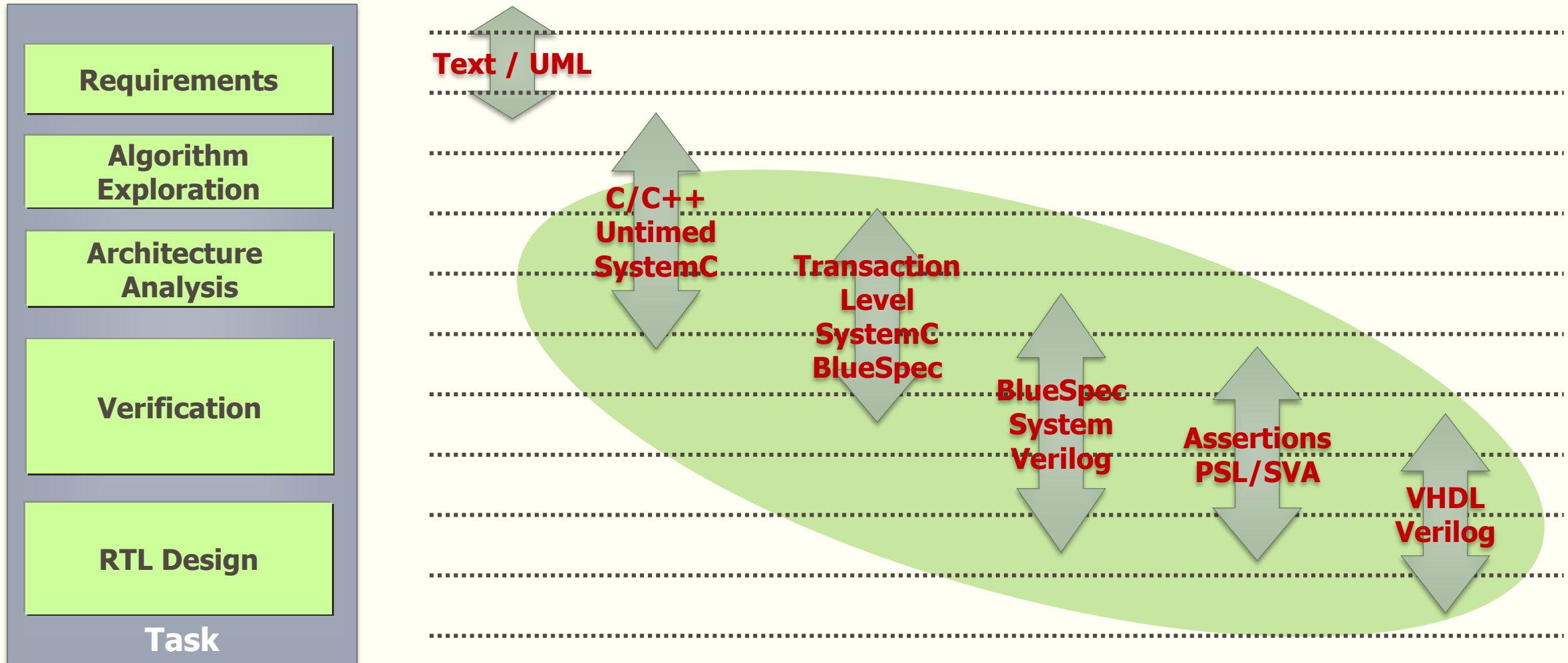


# Gajski's & Khun's Y-chart

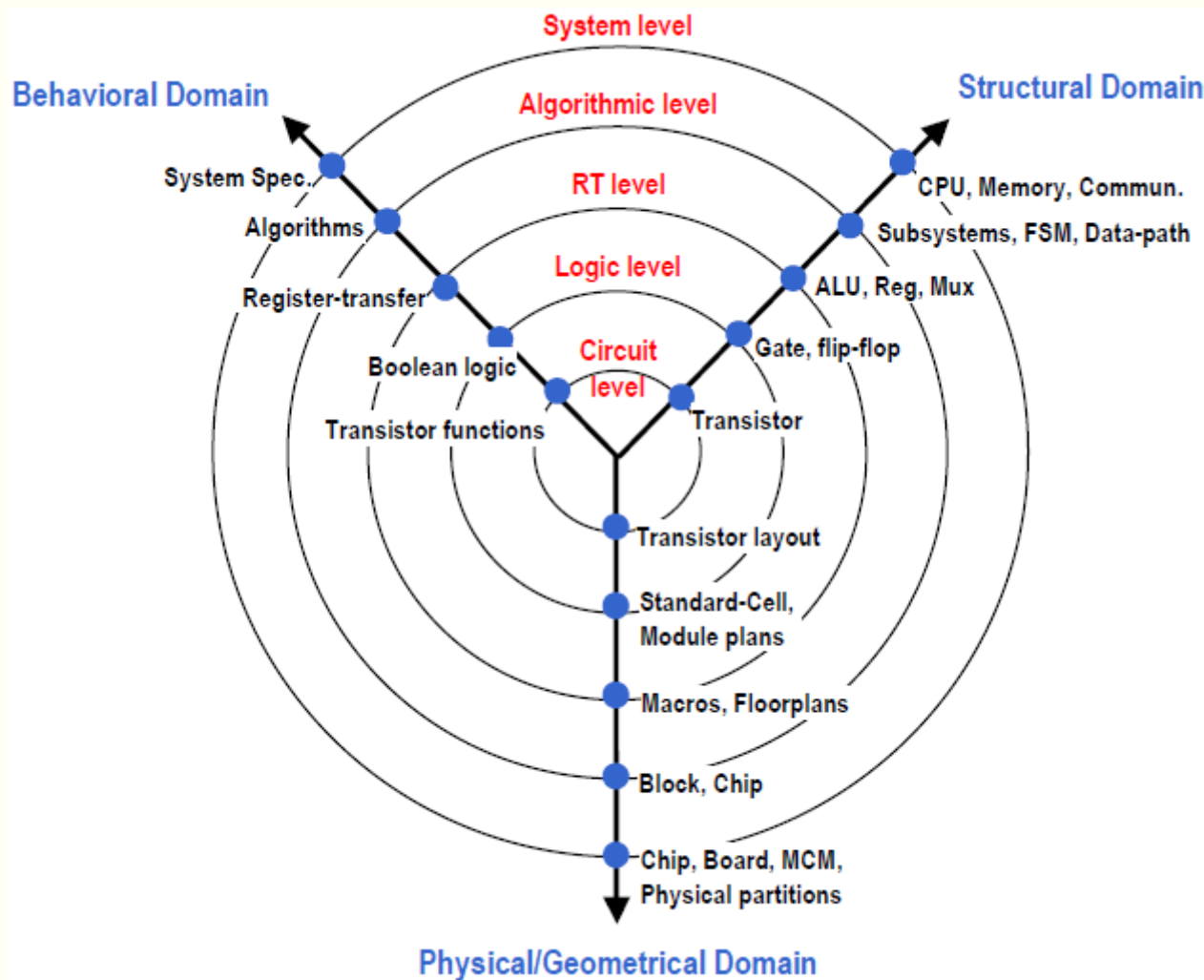

# 1-bit ALU (schematic)

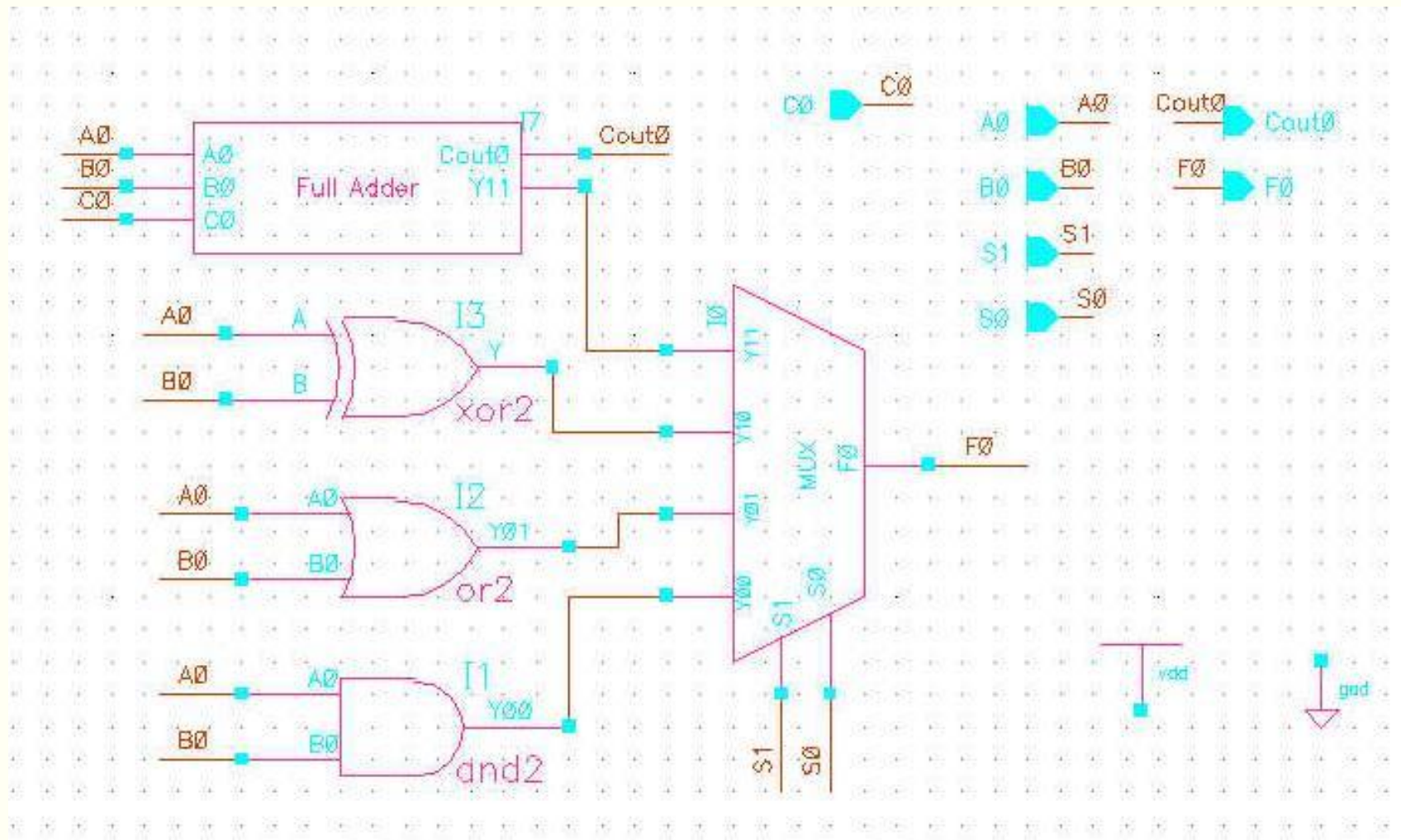


# 1-bit ALU (layout)

 
 
# 4004 $\mu$ P (1971)


---

- 4-bit CPU
- First complete CPU on chip
- First commercially available CPU
- 2,300 transistors
- MIPS: 0.092
- Clock speed: 1MHz



# 8008 $\mu$ P (1972)


---

 



# 8080 $\mu$ P (1974)


---

 

K. Siozios, Department of Physics, Aristotle University of Thessaloniki

# 8088 $\mu$ P (1978)


---

 

K. Siozios, Department of Physics, Aristotle University of Thessaloniki


# 8286 $\mu$ P (1982)

---

 

# 8386 $\mu$ P (1985)


---

 

K. Siozios, Department of Physics, Aristotle University of Thessaloniki


# 8486 $\mu$ P (1989)

---

 

# Pentium $\mu$ P (1993)


---

 

K. Siozios, Department of Physics, Aristotle University of Thessaloniki

# Pentium II $\mu$ P (1997)


---

 

K. Siozios, Department of Physics, Aristotle University of Thessaloniki

# Pentium II XEON $\mu$ P (1998)

---

 


K. Siozios, Department of Physics, Aristotle University of Thessaloniki



# Pentium III $\mu$ P (1999)


---

 


K. Siozios, Department of Physics, Aristotle University of Thessaloniki


# Pentium 4 $\mu$ P (2000)

---

 

 


Wafer of Intel® Xeon™ processors

 

Wafer of Itanium® processors

# VHDL: Very Hard Difficult Language

**VHDL: Very Hard Difficult Language**

 

**Very High-Speed Integrated Circuit Hardware Description Language**



*VHDL is a language for describing digital hardware used by industry worldwide*

# VHDL

---

---

How to write HDL code:

 
 


# VHDL

---

How **NOT** to write HDL code:

  
if a=b then  
x=a^b  
else if a>b then  
...


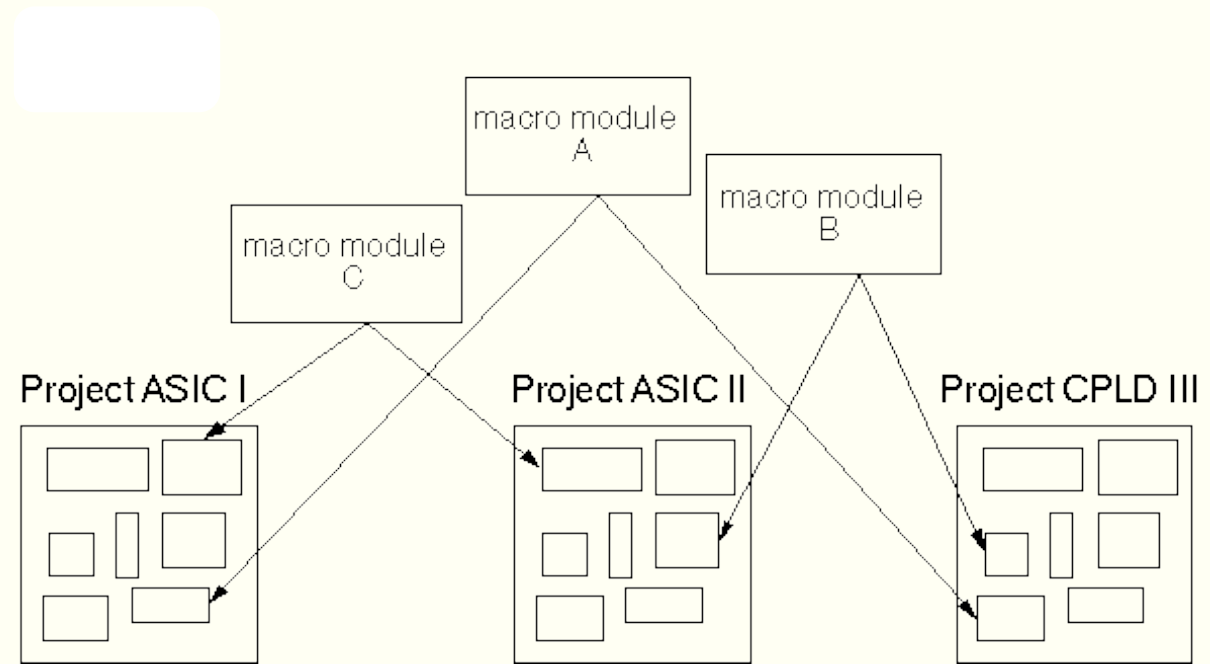
# Advantages of VHDL

---

- Technology/vendor independent
- Portable
- Reusable





# Genesis of VHDL

---

---

## ▪ State of art circa 1980

- Multiple design entry methods and hardware description languages in use
- No or limited portability of designs between CAD tools from different vendors
- Objective: shortening the time from a design concept to implementation from 18 months to 6 months

# History of VHDL

---

- June 1981: Woods Hole Workshop
- July 1983: contract awarded to develop VHDL
  - Intermetrics
  - IBM
  - Texas Instruments
- August 1985: VHDL Version 7.2 released
- December 1987: VHDL became IEEE Standard 1076-1987 and in 1988 an ANSI standard

# VHDL Standards

---

- **P1076** Standard VHDL Language Reference Manual ([VASG](#)) VHDL-87, VHDL-93, VHDL-01, VHDL-08
- **P1076.1** Standard VHDL Analog and Mixed-Signal Extensions ([VHDL-AMS](#))
- **P1076.1.1** Standard VHDL Analog and Mixed-Signal Extensions - Packages for Multiple Energy Domain Support ([StdPkgs](#)) - this group is now part of 1076.1
- **P1076.2** IEEE Standard VHDL Mathematical Packages ([math](#))
- **P1076.3** Standard VHDL Synthesis Packages ([vhdlsynth](#))
- **P1076.4** Standard VITAL ASIC (Application Specific Integrated Circuit) Modeling Specification ([VITAL](#)) - This group is now part of 1076.
- **P1164** Standard Multivalued Logic System for VHDL Model Interoperability (Std\_logic\_1164) ([vhdl-std-logic](#))

# VHDL vs Verilog

---


---

VHDL	Verilog
Government Developed	Commercially Developed
Ada based	C based
Strongly Type Cast	Mildly Type Cast
Difficult to learn	Easier to Learn
More Powerful	Less Powerful

# VHDL Subsets


---

---

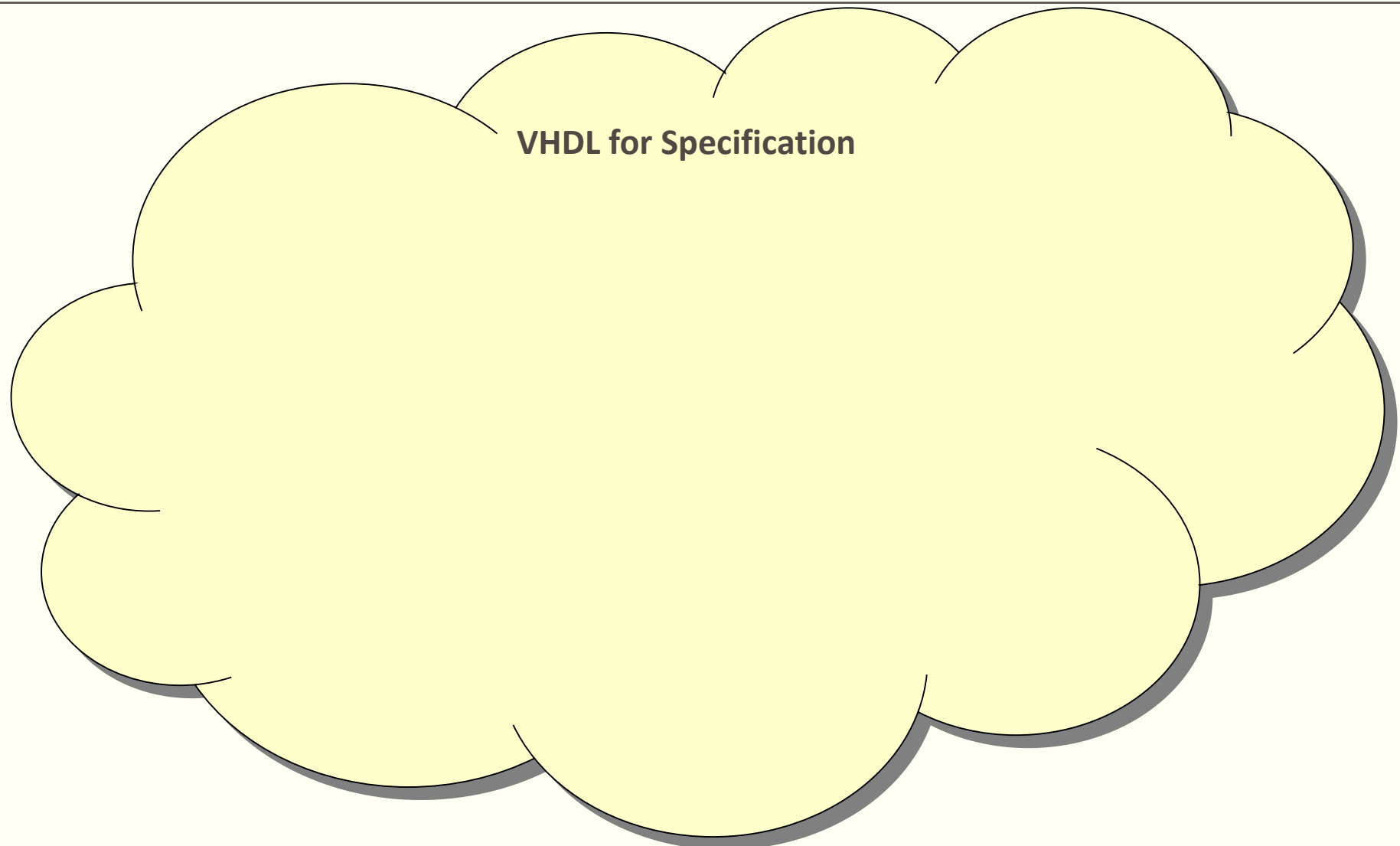


# VHDL Subsets

---

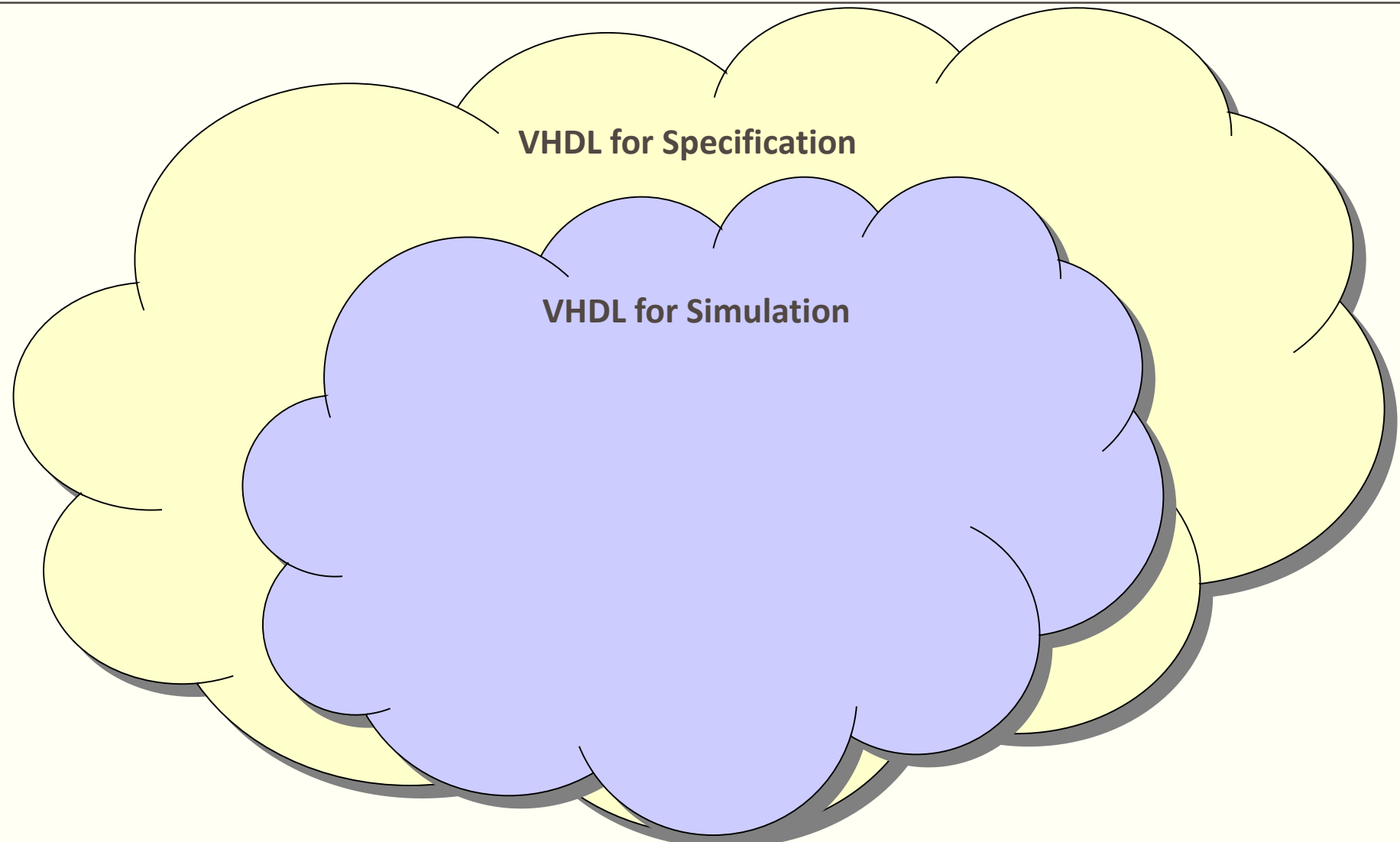

# VHDL Subsets

---

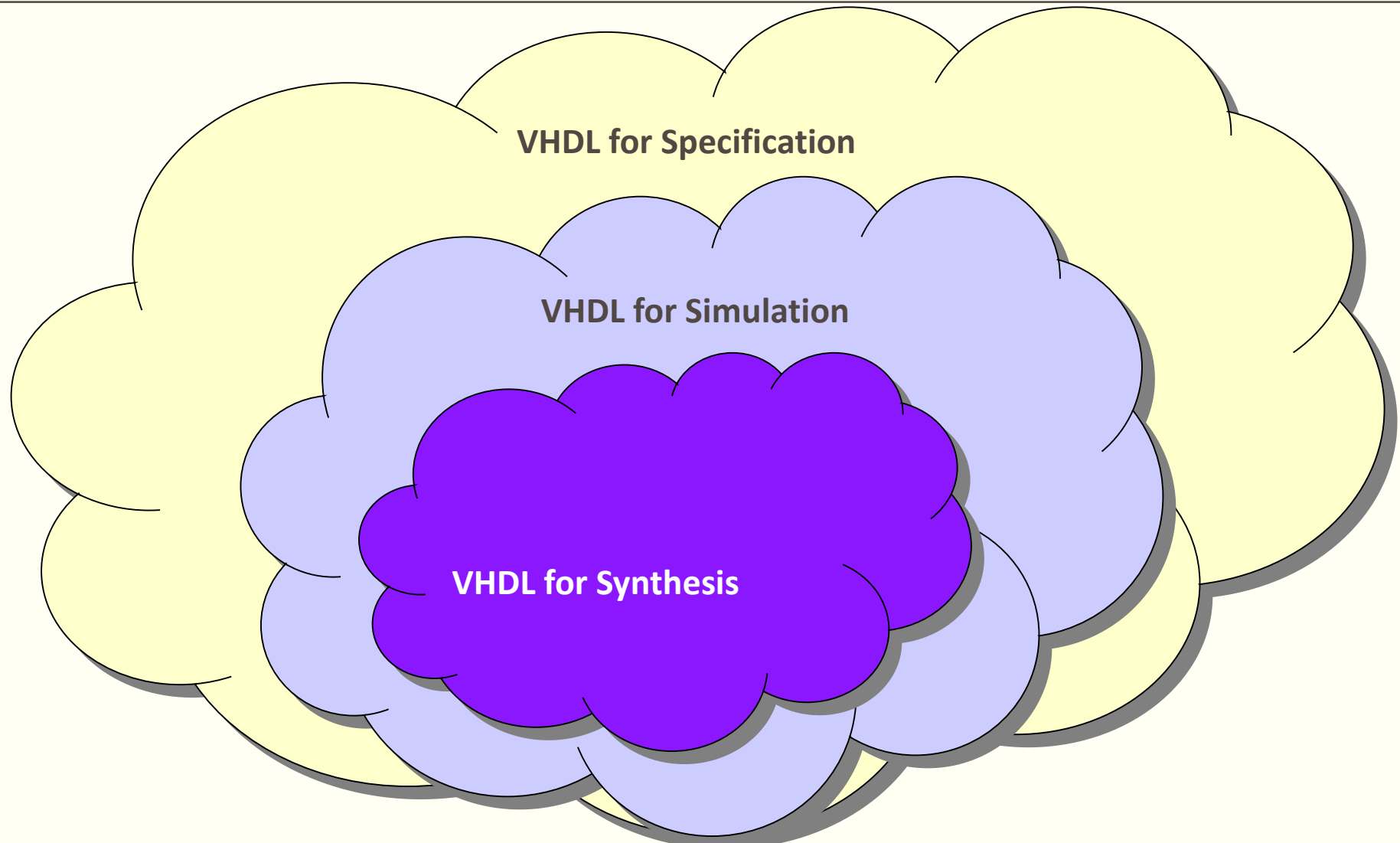

# Design Flow

---

Design and implement a simple unit permitting to speed up encryption with RC5-similar cipher with fixed key set on 8031 microcontroller. Unlike in the experiment 5, this time your unit has to be able to perform an encryption algorithm by itself, executing 32 rounds.....

## Specification



# Design Flow

---

Design and implement a simple unit permitting to speed up encryption with RC5-similar cipher with fixed key set on 8031 microcontroller. Unlike in the experiment 5, this time your unit has to be able to perform an encryption algorithm by itself, executing 32 rounds.....

Specification

 VHDL description

```
Library IEEE;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity RC5_core is
  port(
    clock, reset, encr_decr: in std_logic;
    data_input: in std_logic_vector(31 downto 0);
    data_output: out std_logic_vector(31 downto 0);
    out_full: in std_logic;
    key_input: in std_logic_vector(31 downto 0);
    key_read: out std_logic;
  );
end AES_core;
```

# Design Flow

---


Design and implement a simple unit permitting to speed up encryption with RC5-similar cipher with fixed key set on 8031 microcontroller. Unlike in the experiment 5, this time your unit has to be able to perform an encryption algorithm by itself, executing 32 rounds.....

Specification

VHDL description

```
Library IEEE;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_unsigned.all;  
  
entity RC5_core is  
  port(  
    clock, reset, encr_decr: in std_logic;  
    data_input: in std_logic_vector(31 downto 0);  
    data_output: out std_logic_vector(31 downto 0);  
    out_full: in std_logic;  
    key_input: in std_logic_vector(31 downto 0);  
    key_read: out std_logic;  
  );  
end AES_core;
```

Functional simulation

 

# Design Flow


Design and implement a simple unit permitting to speed up encryption with RC5-similar cipher with fixed key set on 8031 microcontroller. Unlike in the experiment 5, this time your unit has to be able to perform an encryption algorithm by itself, executing 32 rounds.....

Specification


VHDL description

```
Library IEEE;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_unsigned.all;  
  
entity RC5_core is  
  port(  
    clock, reset, encr_decr: in std_logic;  
    data_input: in std_logic_vector(31 downto 0);  
    data_output: out std_logic_vector(31 downto 0);  
    out_full: in std_logic;  
    key_input: in std_logic_vector(31 downto 0);  
    key_read: out std_logic;  
  );  
end AES_core;
```

Functional simulation

 

Synthesis

 

# Design Flow


Design and implement a simple unit permitting to speed up encryption with RC5-similar cipher with fixed key set on 8031 microcontroller. Unlike in the experiment 5, this time your unit has to be able to perform an encryption algorithm by itself, executing 32 rounds.....

Specification


VHDL description

```
Library IEEE;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_unsigned.all;  
  
entity RC5_core is  
  port(  
    clock, reset, encr_decr: in std_logic;  
    data_input: in std_logic_vector(31 downto 0);  
    data_output: out std_logic_vector(31 downto 0);  
    out_full: in std_logic;  
    key_input: in std_logic_vector(31 downto 0);  
    key_read: out std_logic;  
  );  
end AES_core;
```


Synthesis

 

Functional simulation

 

Post-synthesis simulation

 

 
# Physical Implementation Flow

---




Implementation (Mapping, Placing & Routing)




# Physical Implementation Flow

---

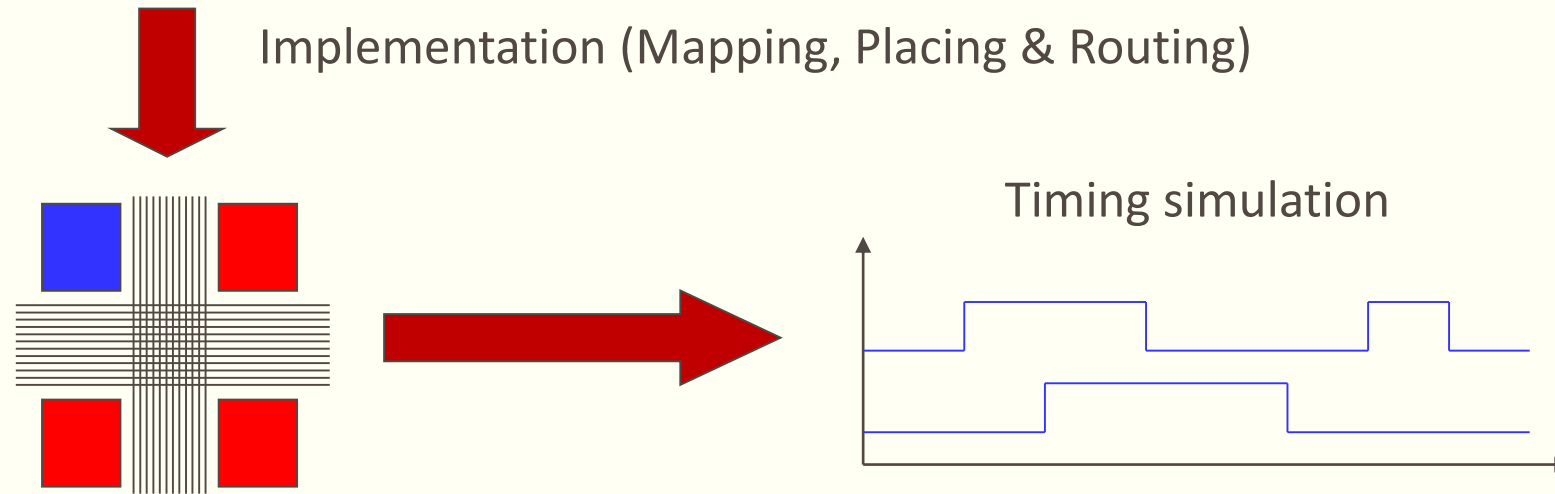


# Physical Implementation Flow

---

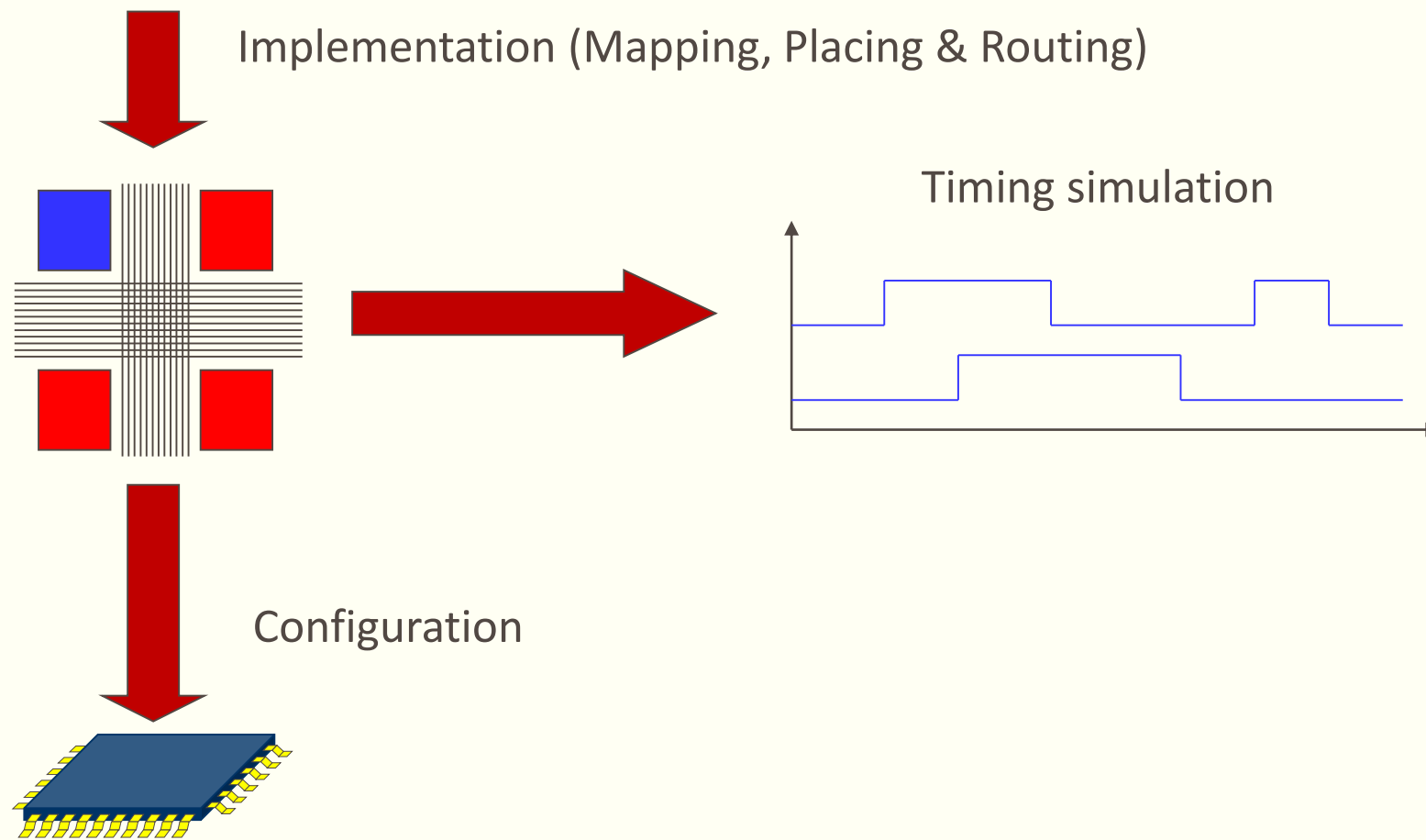

# Physical Implementation Flow

---

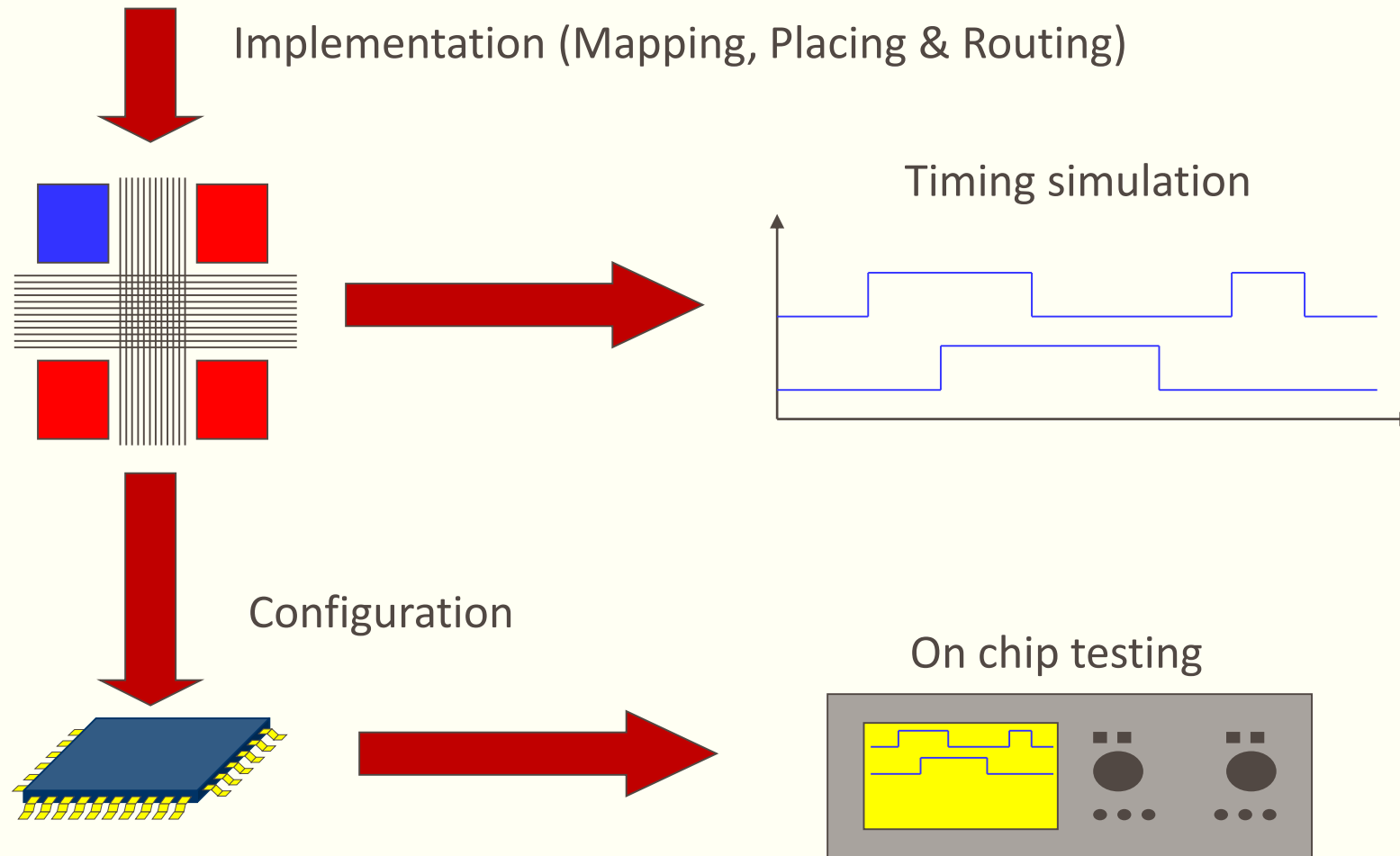



# EDA Tools

---

- ModelSim – [www.model.com](http://www.model.com), [www.mentor.com](http://www.mentor.com)
- ModelSim Xilinx Edition – [www.xilinx.com](http://www.xilinx.com)
- Leonardo Spectrum – [www.mentor.com](http://www.mentor.com)
- Xilinx ISE – [www.xilinx.com](http://www.xilinx.com)

# Translating Code into Circuits



```
architecture MLU_DATAFLOW of MLU is
signal A1:STD_LOGIC;
signal B1:STD_LOGIC;
signal Y1:STD_LOGIC;
signal MUX_0, MUX_1, MUX_2, MUX_3: STD_LOGIC;

begin
  A1<=A when (NEG_A='0') else not A;
  B1<=B when (NEG_B='0') else not B;
  Y<=Y1 when (NEG_Y='0') else not Y1;

  MUX_0<=A1 and B1;
  MUX_1<=A1 or B1;
  MUX_2<=A1 xor B1;
  MUX_3<=A1 xnor B1;

  with (L1 & L0) select
    Y1 <= MUX_0 when "00",
          MUX_1 when "01",
          MUX_2 when "10",
          MUX_3 when others;
end MLU_DATAFLOW;
```


VHDL description

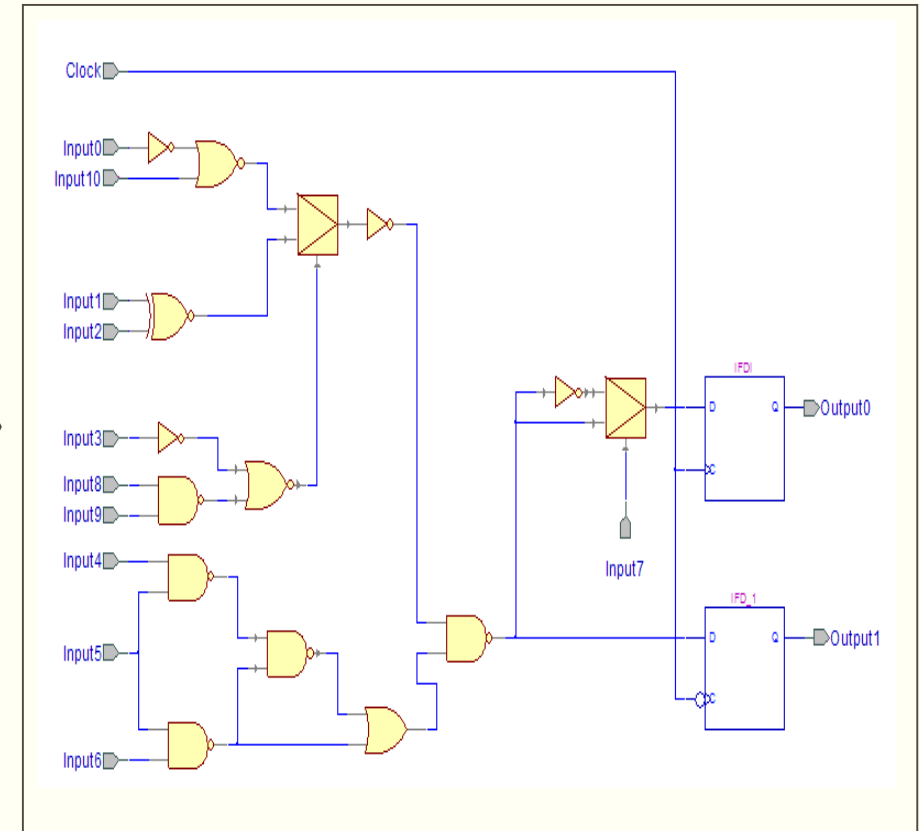 

Circuit netlist

# VHDL Design Styles


---

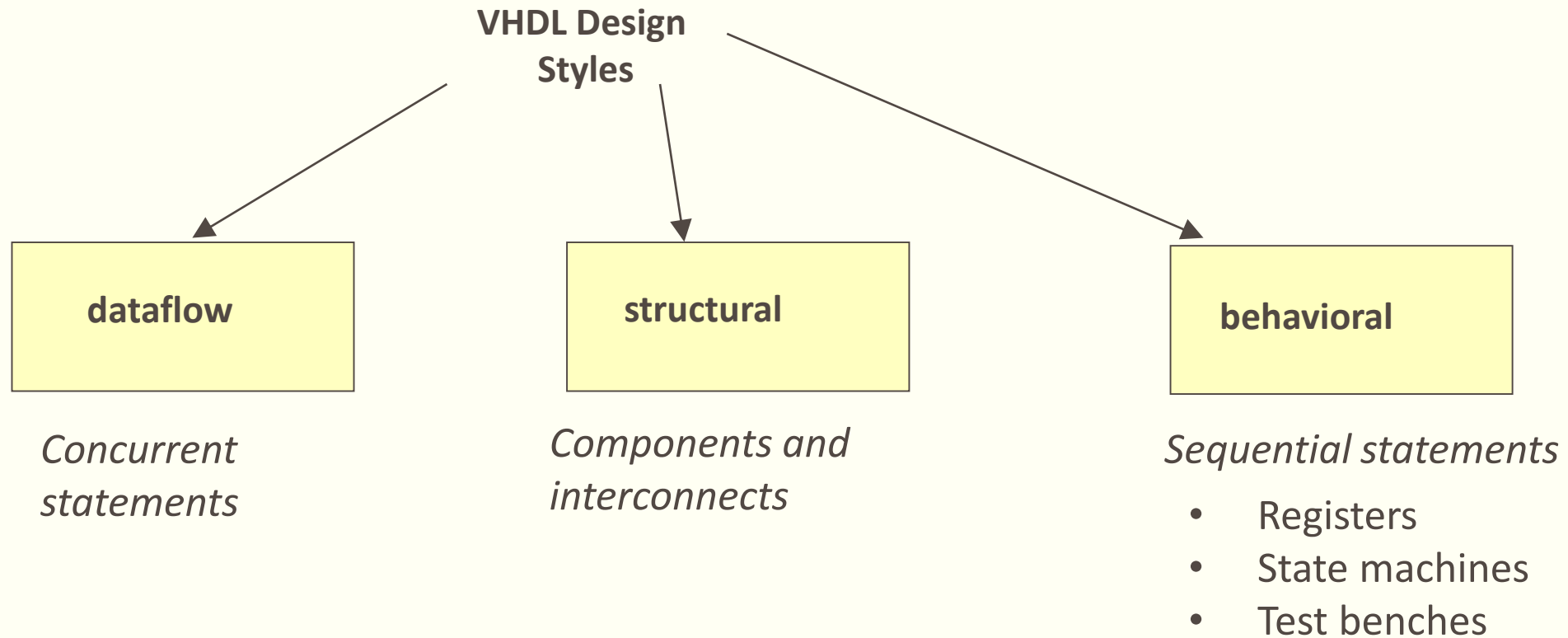

# VHDL Design Styles

---

---

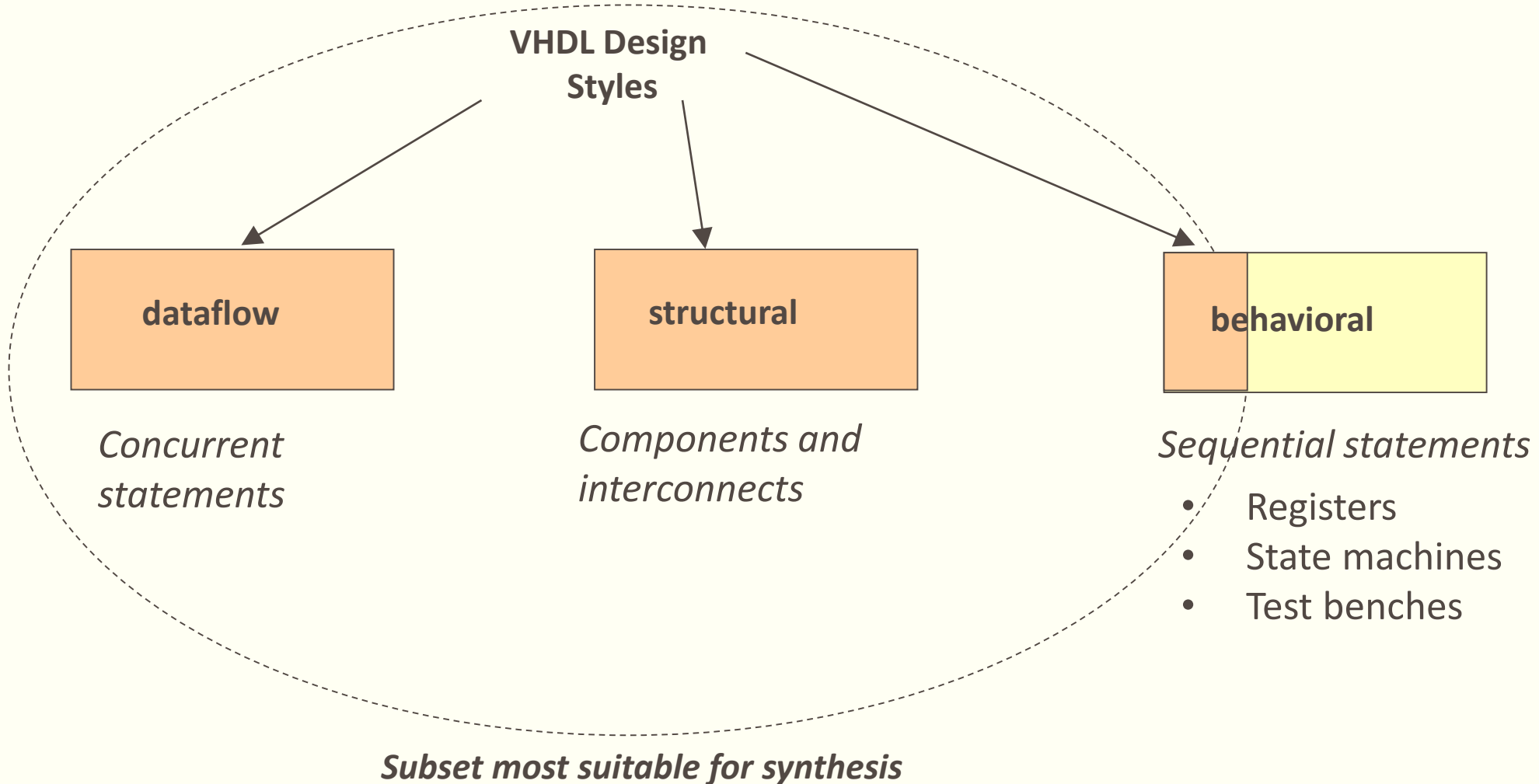

# Dataflow Description

---

- Describes how data moves through the system and the various processing steps.
- Data Flow uses series of concurrent statements to realize logic.
  - Concurrent statements are evaluated at the same time; thus, order of these statements doesn't matter.
- Data Flow is most useful style when series of Boolean equations can represent a logic.
- Data Flow describes best combinational logic.

# Structural Description

---

---

- Structural design is the simplest to understand.
  - This style is the closest to schematic capture and utilizes simple building blocks to compose logic functions.
- Components are interconnected in a hierarchical manner.
- Structural descriptions may connect simple gates or complex, abstract components.
- Structural style is useful when expressing a design that is naturally composed of sub-blocks.

## Behavioral Description

---

---

- It accurately models what happens on the inputs and outputs of the black box (no matter what is inside and how it works).
- This style uses PROCESS and sequential statements to realize logic, which are executed one after the other, like in most programming languages.
- Behavioral descriptions describe best sequential logic.

# Naming and Labeling

---

- VHDL is not case sensitive

Example:

Names or labels

**databus**

**Databus**

**DataBus**

**DATABUS**

are all equivalent



# Naming and Labeling

---

---

## General rules of thumb (according to VHDL-87)

1. All names should start with an alphabet character (a-z or A-Z)
2. Use only alphabet characters (a-z or A-Z) digits (0-9) and underscore (\_)
3. Do not use any punctuation or reserved characters within a name (!, ?, ., &, +, -, etc.)
4. Do not use two or more consecutive underscore characters (\_\_) within a name (e.g., Sel\_\_A is invalid)
5. All names and labels in a given entity and architecture must be unique

# Free Format

---

- VHDL is a “free format” language
- No formatting conventions, such as spacing or indentation imposed by VHDL compilers. Space and carriage return treated the same way.

Example:

**if (a=b) then**

*or*

**if           (a=b)           then**

*or*

**if (a =**

**b) then**

**are all equivalent**

# Comments

---

- Comments in VHDL are indicated with a “double dash”, i.e., “--”
  - Comment indicator can be placed anywhere in the line
  - Any text that follows in the same line is treated as a comment
  - Carriage return terminates a comment
  - No method for commenting a block extending over a couple of lines


Examples:

```
-- main subcircuit
```

```
Data_in <= Data_bus;    -- reading data from the input  
FIFO
```

# Design Entity

---


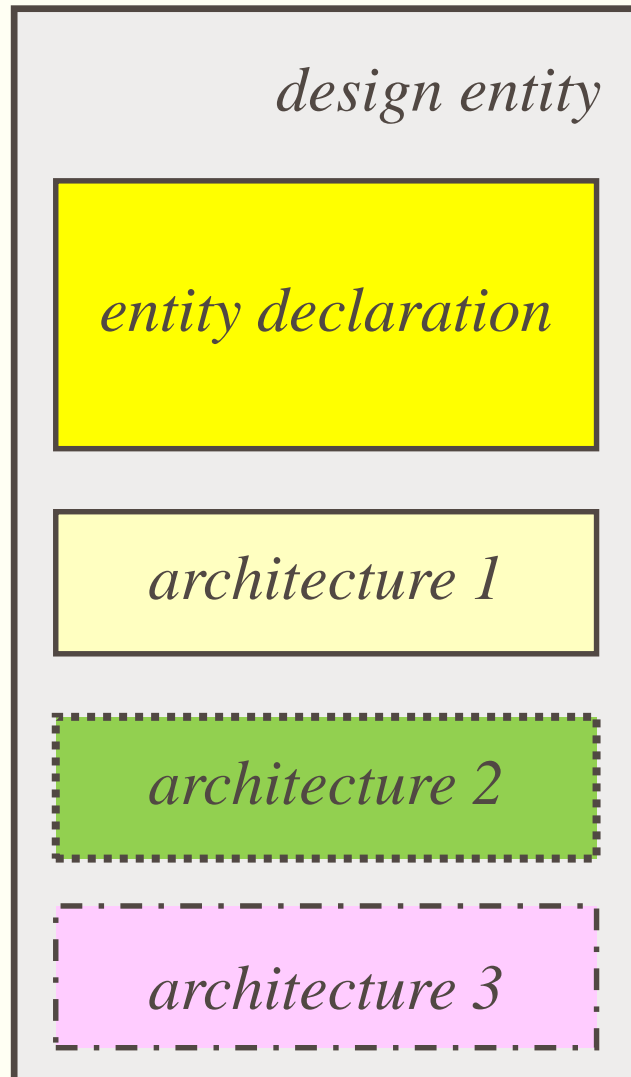


*Design Entity* - most basic building block of a design

One *entity* can have many different *architectures*
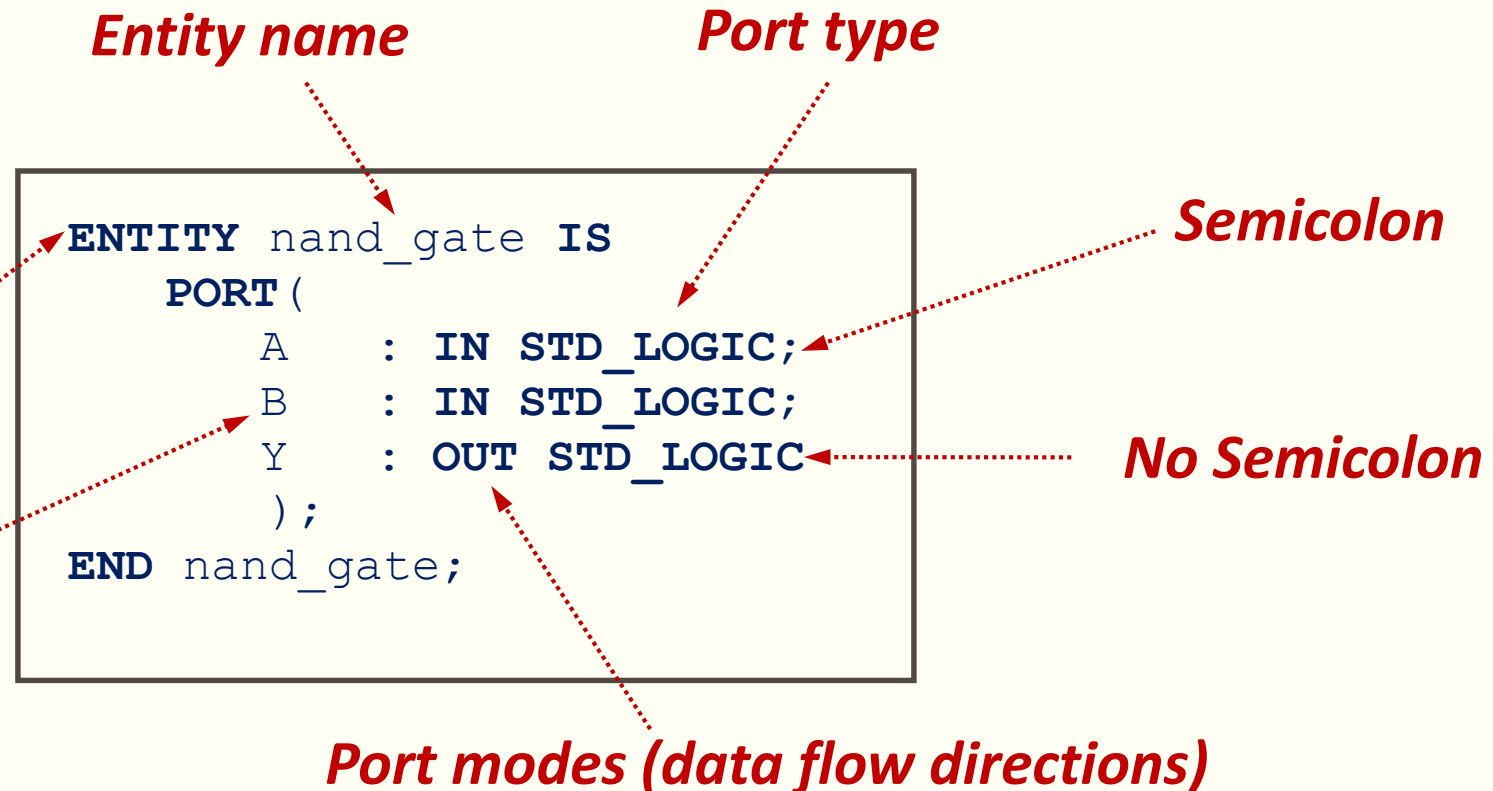 
# Entity Declaration

Entity Declaration describes the interface of the component, i.e. input and output ports.





# Entity Declaration - Syntax

---

```
ENTITY entity_name IS
    PORT (
        port_name : signal_mode signal_type;
        port_name : signal_mode signal_type;
        .....
        port_name : signal_mode signal_type);
END entity_name;
```
 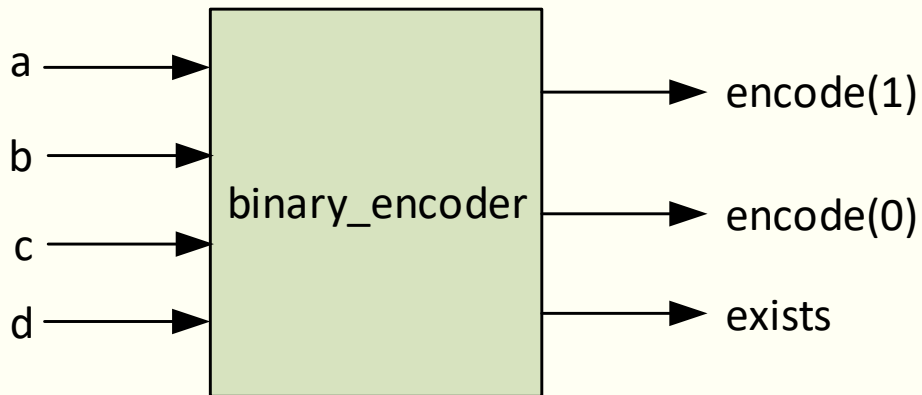
# Entity Declaration - Example

Write the entity declaration for the 4-2 binary encoder




```
ENTITY nand_gate IS
  PORT (
    A      : IN STD_LOGIC;
    B      : IN STD_LOGIC;
    Y      : OUT STD_LOGIC
  );
END nand_gate;
```
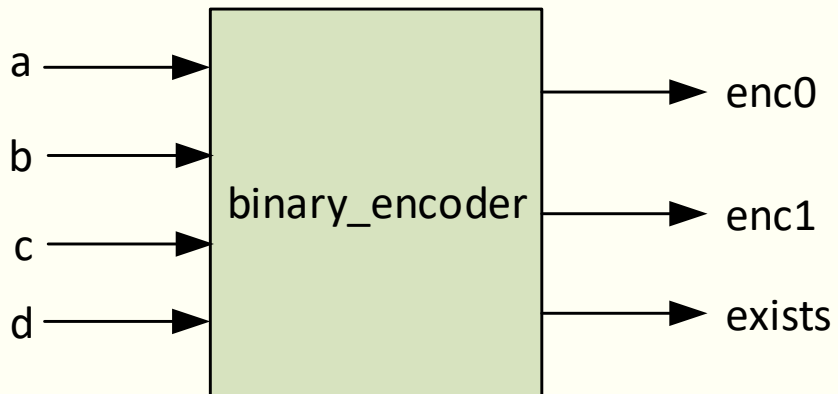
# Entity Declaration - Example

---

Write the entity declaration for the 4-2 binary encoder (with priority)




```
entity binary_encoder is
  port (
    a: in std_logic;
    b: in std_logic;
    c: in std_logic;
    d: in std_logic;
    enc0: out std_logic;
    enc1: out std_logic;
    exists: inout std_logic
  );
end binary_encoder;
```


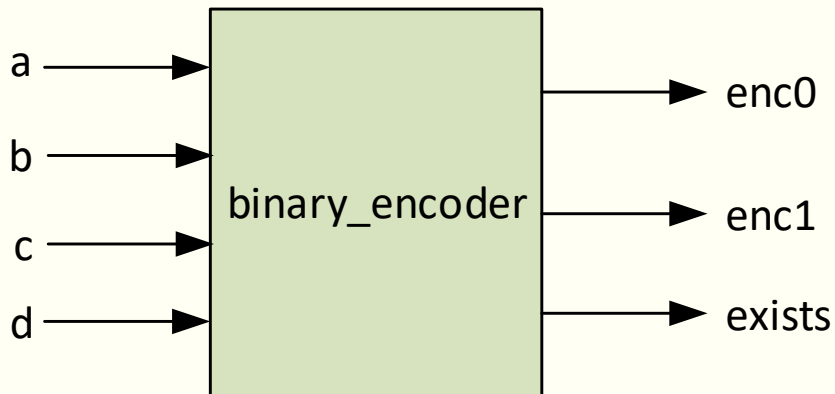
# Entity Declaration - Example

Refinement

Write the entity declaration for the 4-2 binary encoder (with priority)



```
entity binary_encoder is
  port (
    a: in std_logic;
    b: in std_logic;
    c: in std_logic;
    d: in std_logic;
    enc: out std_logic_vector(1 downto 0);
    exists: inout std_logic
  );
end binary_encoder;
```

# Architecture

---

- Describes an implementation of a design entity.
- Architecture example:

```
ARCHITECTURE model OF nand_gate IS  
BEGIN  
    z <= a NAND b;  
END model;
```

# Architecture - Syntax


---

```
ARCHITECTURE architecture_name OF entity_name IS  
    [ declarations ]  
BEGIN  
    code  
END architecture_name ;
```

# Entity Declaration & Architecture

---

nand\_gate.vhd

 


```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
  
ENTITY nand_gate IS  
    PORT (A : IN STD_LOGIC;  
          B : IN STD_LOGIC;  
          Y : OUT STD_LOGIC);  
END nand_gate;  
  
ARCHITECTURE model OF nand_gate IS  
BEGIN  
    Y <= A NAND B;  
END model;
```


# Port Mode In

---


---

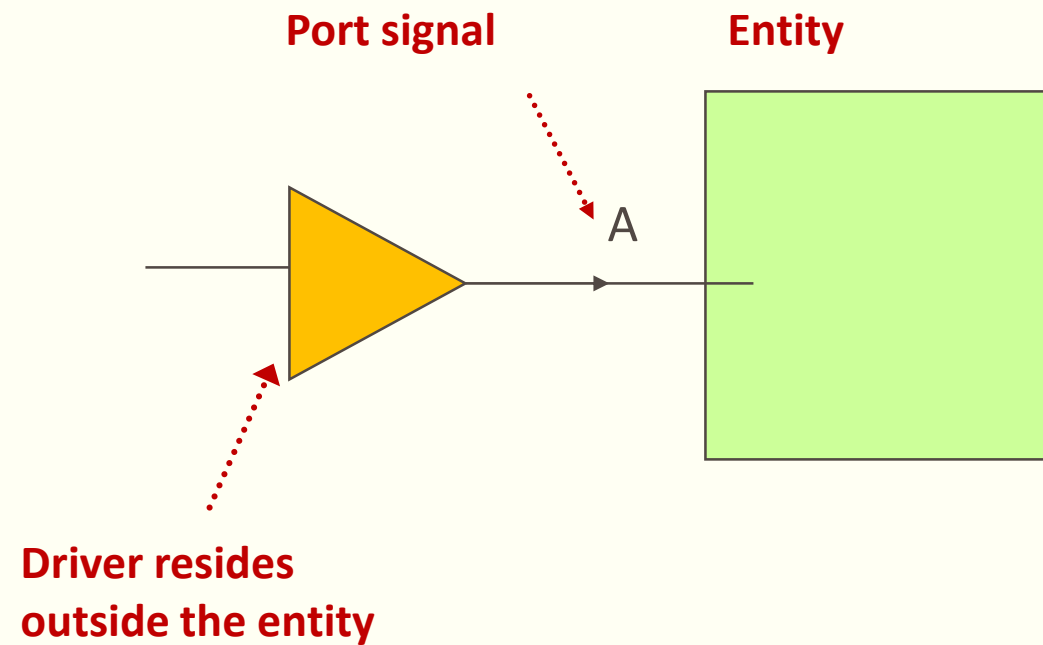

# Port Mode Out

 


# Port Mode Out with Signal

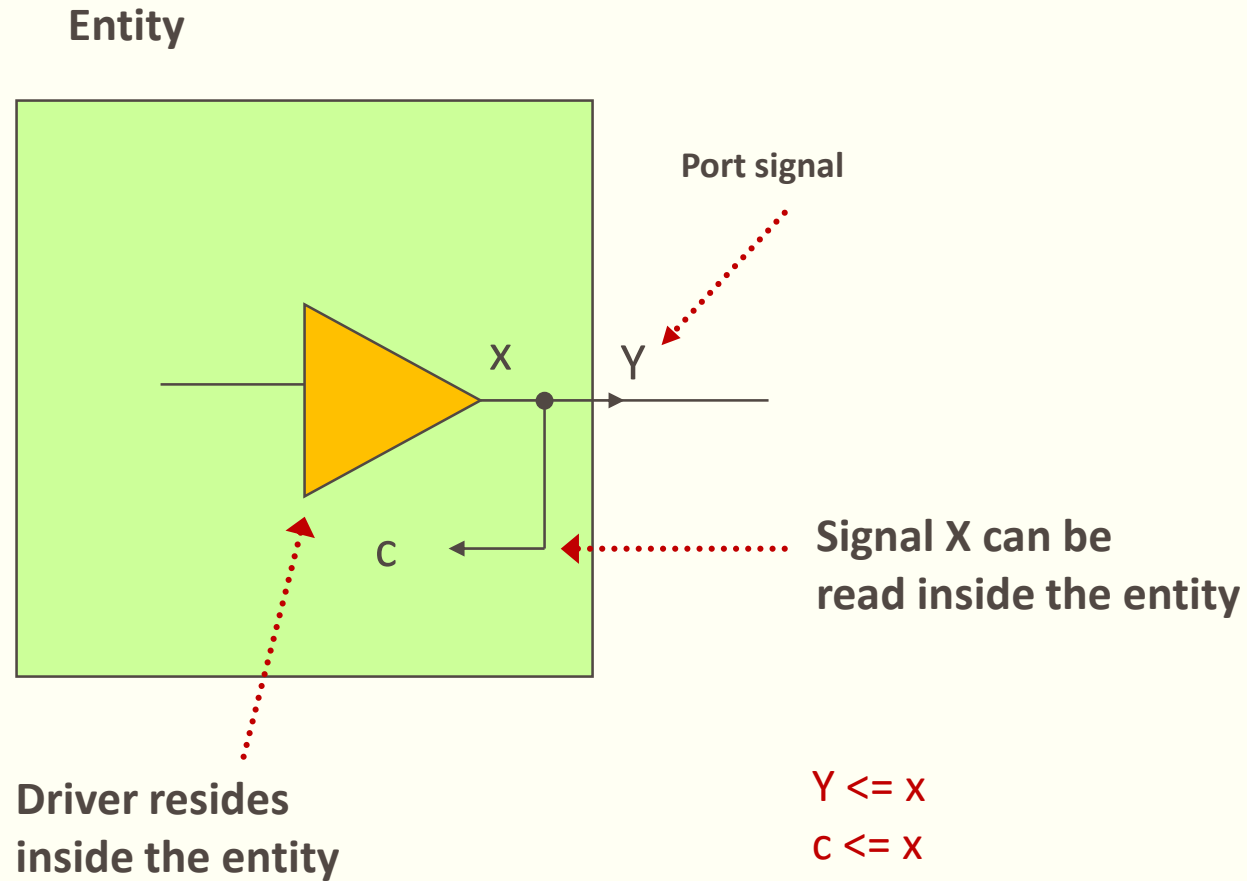

# Port Mode Inout

---

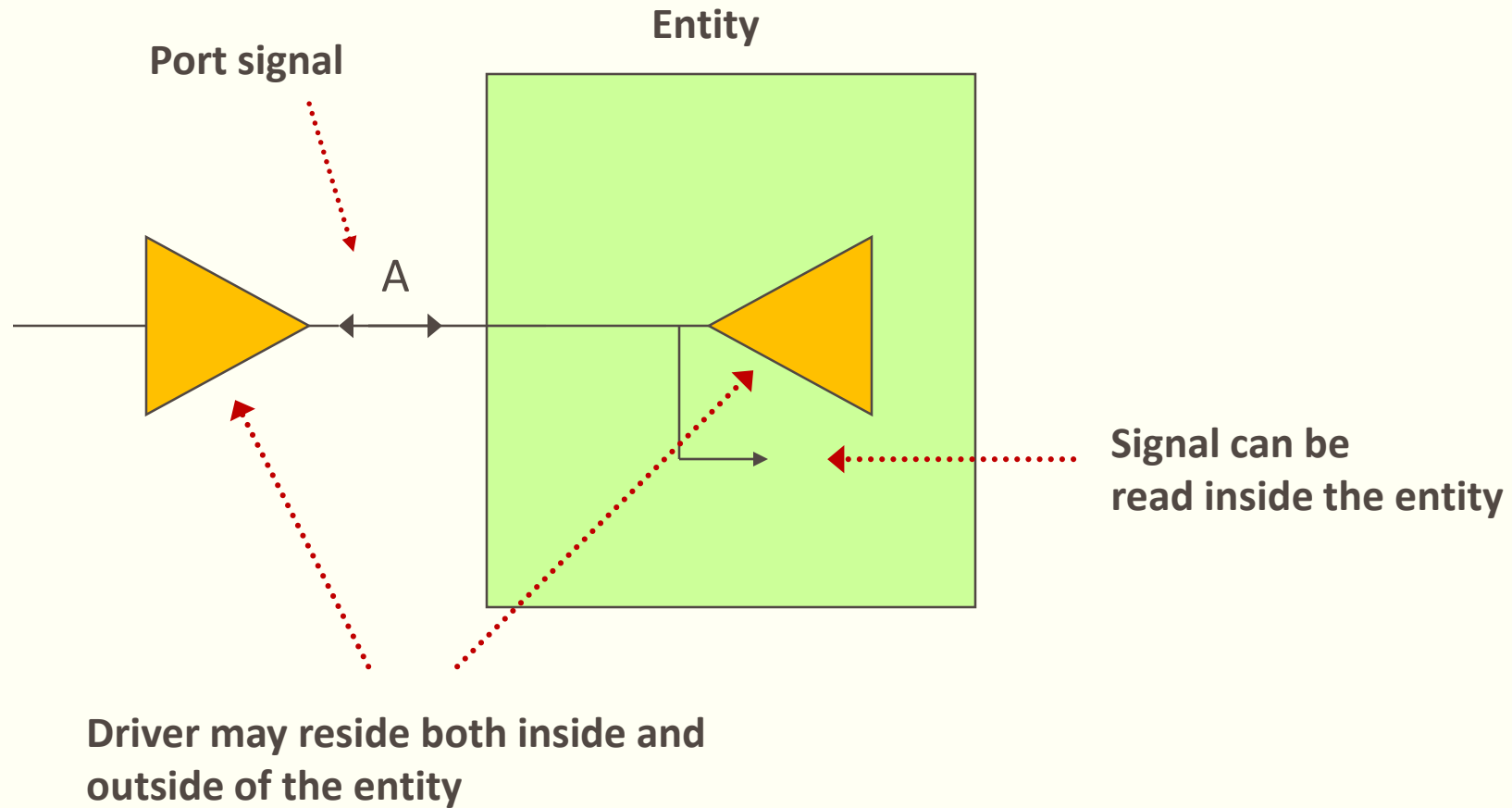




# Port Mode Buffer

---

---

 

# Port Modes

---

The Port Mode of the interface describes the direction in which data travels with respect to the component

- **In:** Data comes in this port and can only be read within the entity. It can appear **only on the right side** of a signal or variable assignment.
- **Out:** The value of an output port can only be updated within the entity. **It cannot be read.** It can only appear **on the left side** of a signal assignment.
- **Inout:** The value of a bi-directional port can be read and updated within the entity model. It can appear on **both sides** of a signal assignment.
- **Buffer:** Used for a signal that is an output from an entity. The value of the signal can be used inside the entity, which means that in an assignment statement the signal can appear on the left and right sides of the  $\leq$  operator

# Library Declaration

---

Library declaration

Use all definitions from the  
package std\_logic\_1164

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY nand_gate IS
    PORT (
        A    : IN STD_LOGIC;
        B    : IN STD_LOGIC;
        Y    : OUT STD_LOGIC);
END nand_gate;

ARCHITECTURE model OF nand_gate IS
BEGIN
    Y <= A NAND B;
END model;
```


# Library Declaration - Syntax

---

```
LIBRARY library_name;  
USE library_name.package_name.package_parts;
```

# Parts of a Library

---

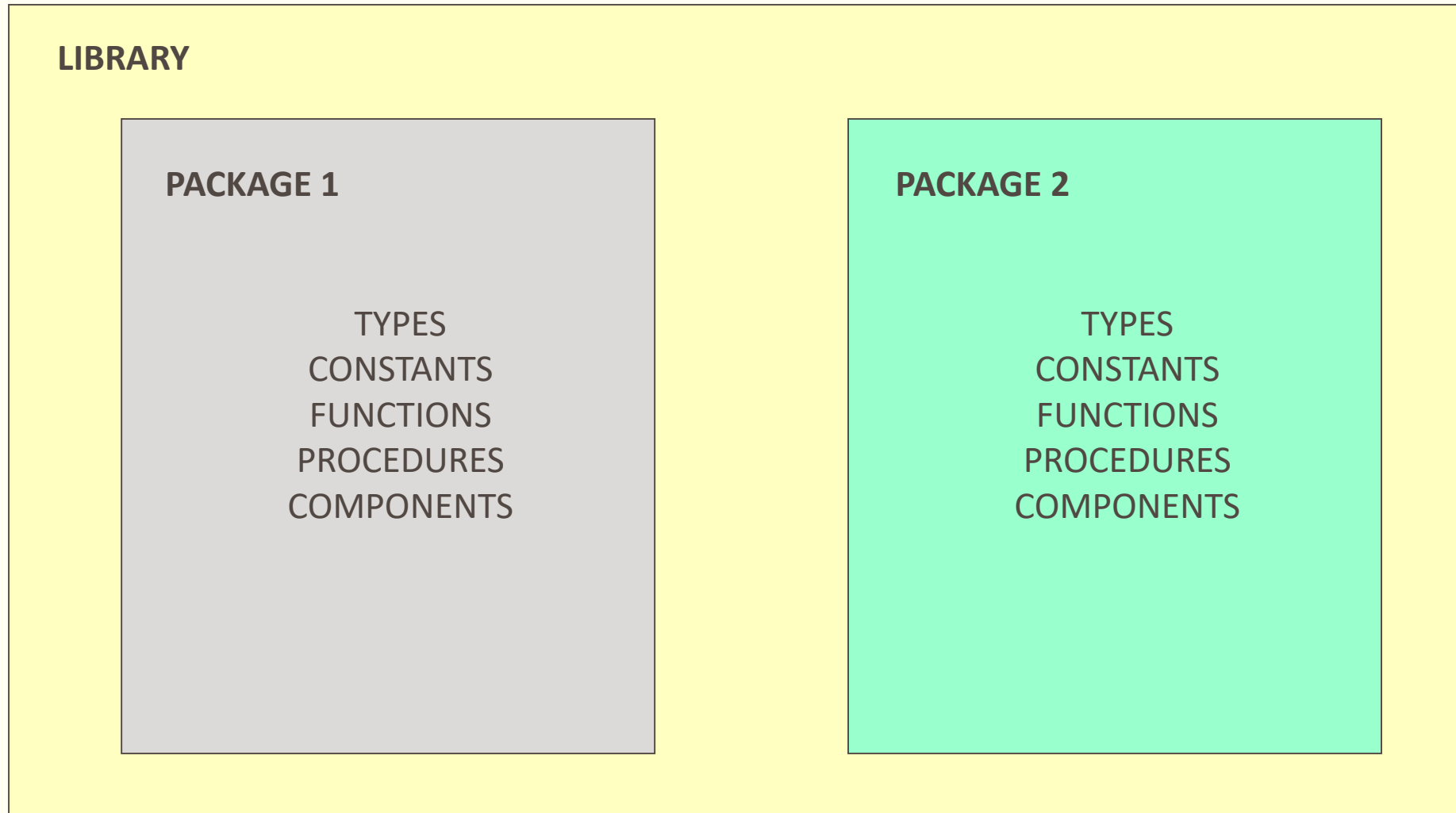

# Common Libraries

---

**ieee**

Specifies multi-level logic system, including STD\_LOGIC, and STD\_LOGIC\_VECTOR data types.

Need to be explicitly declared

---

**std**

Specifies pre-defined data types (BIT, BOOLEAN, INTEGER, REAL, SIGNED, UNSIGNED, etc.), arithmetic operations, basic type conversion functions, basic text i/o functions, etc.

Visible by default

**work**

Current designs after compilation.

# STD\_LOGIC


---

---

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY nand_gate IS
    PORT (
        A    : IN STD_LOGIC;
        B    : IN STD_LOGIC;
        Y    : OUT STD_LOGIC);
END nand_gate;

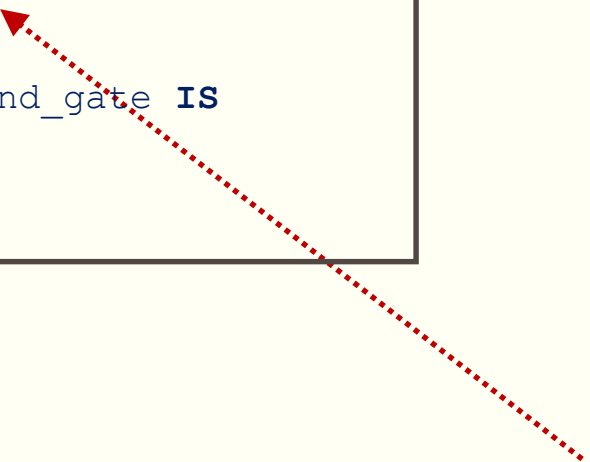ARCHITECTURE model OF nand_gate IS
BEGIN
    Y <= A NAND B;
END model;
```



What is **STD\_LOGIC** you ask?

# STD\_LOGIC Type

---

---


Value	Meaning
'X'	Forcing (Strong driven) Unknown
'0'	Forcing (Strong driven) 0
'1'	Forcing (Strong driven) 1
'Z'	High Impedance
'W'	Weak (Weakly driven) Unknown
'L'	Weak (Weakly driven) 0. Models a pull down.
'H'	Weak (Weakly driven) 1. Models a pull up.
'-'	Don't Care



# STD\_LOGIC Meaning

---

X

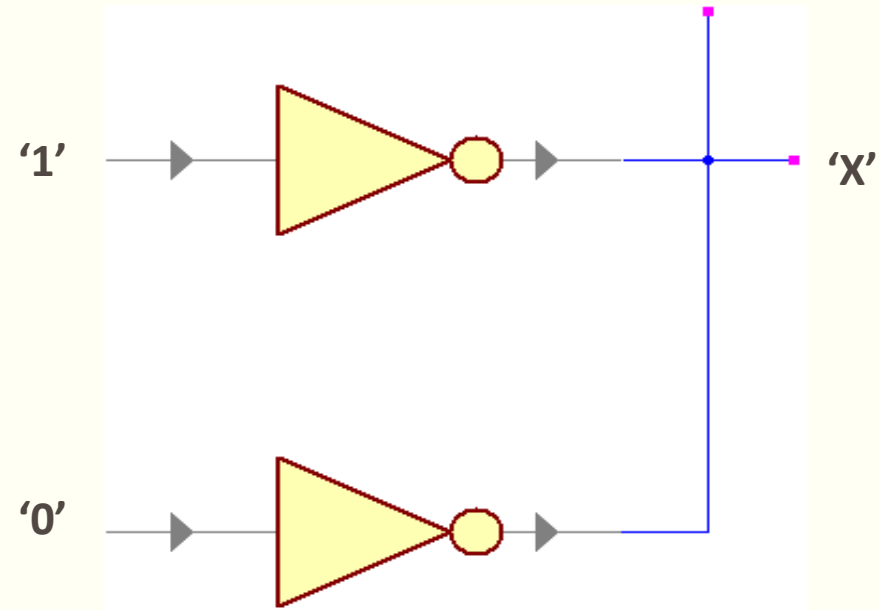


Contention on the bus

# STD\_LOGIC Meaning

---



---

 

# STD\_LOGIC Meaning

---

---

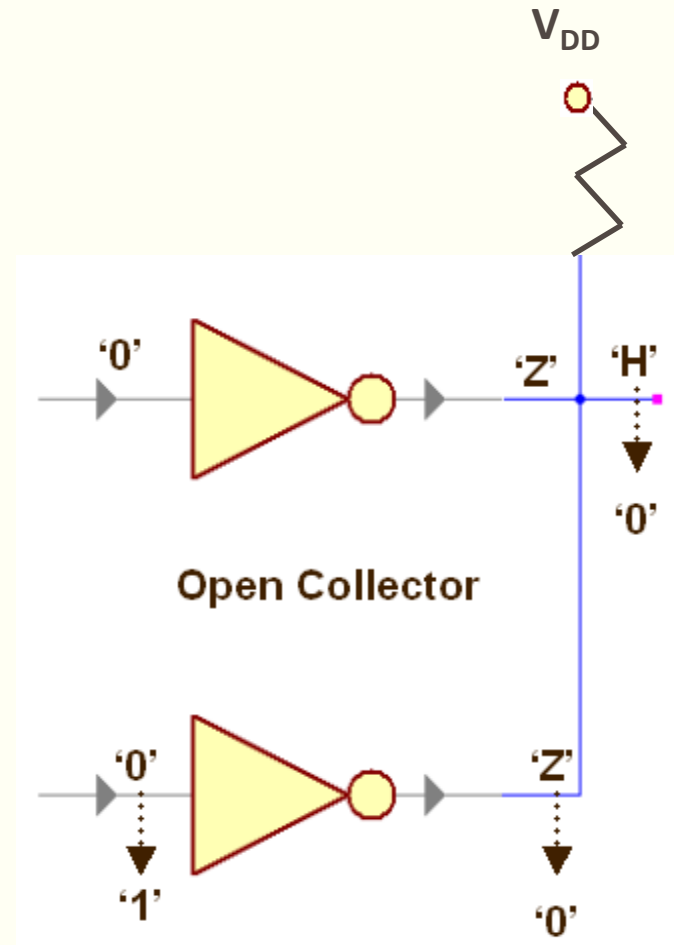 

# STD\_LOGIC Meaning

---

- Do not care
- Can be assigned to outputs for the case of invalid inputs(may produce significant improvement in resource utilization after synthesis).
- Use with caution '1' = '-' give FALSE



# Resolving Logic Levels

---


---

	X	0	1	Z	W	L	H	-
X	X	X	X	X	X	X	X	X
0	X	0	X	0	0	0	0	X
1	X	X	1	1	1	1	1	X
Z	X	0	1	Z	W	L	H	X
W	X	0	1	W	W	W	W	X
L	X	0	1	L	W	L	W	X
H	X	0	1	H	W	W	H	X
-	X	X	X	X	X	X	X	X


# Wires and Buses

---

SIGNAL a : STD\_LOGIC;

 

 SIGNAL b : STD\_LOGIC\_VECTOR(7 DOWNTO 0);



# Standard Logic Vectors

---

```
SIGNAL a: STD_LOGIC;  
SIGNAL b: STD_LOGIC_VECTOR(3 DOWNTO 0);  
SIGNAL c: STD_LOGIC_VECTOR(3 DOWNTO 0);  
SIGNAL d: STD_LOGIC_VECTOR(7 DOWNTO 0);  
SIGNAL e: STD_LOGIC_VECTOR(15 DOWNTO 0);  
SIGNAL f: STD_LOGIC_VECTOR(8 DOWNTO 0);  
  
a <= '1';  
b <= "0000";           -- Binary base assumed by default  
c <= B"0000";         -- Binary base explicitly specified  
d <= "0110_0111";     -- You can use '_' to increase readability  
e <= X"AF67";         -- Hexadecimal base  
f <= O"723";          -- Octal base
```

# Concatenation

---

```
SIGNAL a: STD_LOGIC_VECTOR(3 DOWNTO 0);
SIGNAL b: STD_LOGIC_VECTOR(3 DOWNTO 0);
SIGNAL c, d, e: STD_LOGIC_VECTOR(7 DOWNTO 0);

a <= "0000";
b <= "1111";
c <= a & b;           -- c = "0000_1111"


d <= '0' & "0001111"; -- d <= "0_0001111"

e <= '0' & '0' & '0' & '0' & '1' & '1' & '1' & '1';
-- e <= "00001111"
```



# XOR3 Example


---

 

**Give the entity declaration for the XOR3 gate**

# Entity xor3


---

 

```
ENTITY xor3 IS  
  PORT (  
    A : IN STD_LOGIC;  
    B : IN STD_LOGIC;  
    C : IN STD_LOGIC;  
    Result : OUT STD_LOGIC  
  );  
end xor3;
```

# Entity xor3

---

 


```
ENTITY xor3 IS  
  PORT (  
    A : IN STD_LOGIC;  
    B : IN STD_LOGIC;  
    C : IN STD_LOGIC;  
    Result : OUT STD_LOGIC  
  );  
end xor3;
```

**Give the architecture (dataflow) for the XOR3 gate**

# Dataflow Architecture

---

 

```
ARCHITECTURE dataflow OF xor3 IS
```

```
SIGNAL U1_out: STD_LOGIC;
```

```
BEGIN
```

```
    U1_out <=A XOR B;
```

```
    Result <=U1_out XOR C;
```




```
END dataflow;
```

# Structural Architecture

```
ARCHITECTURE structural OF xor3 IS
SIGNAL U1_OUT: STD_LOGIC;
COMPONENT xor2
  PORT (
    I1 : IN STD_LOGIC;
    I2 : IN STD_LOGIC;
    Y  : OUT STD_LOGIC
  );
END COMPONENT;

BEGIN
  U1: xor2 PORT MAP (I1 => A,
                    I2 => B,
                    Y  => U1_OUT);

     U2: xor2 PORT MAP (I1 => U1_OUT,
                    I2 => C,
                    Y  => Result);
END structural;
```



# Component Instantiation

---

- Named association connectivity (**recommended**)

```
COMPONENT xor2 IS
  PORT (
    I1 : IN STD_LOGIC;
    I2 : IN STD_LOGIC;
    Y  : OUT STD_LOGIC
  );
END COMPONENT;

U1: xor2 PORT MAP (I1 => A,
                  I2 => B,
                  Y  => U1_OUT);
```


# Component Instantiation

---

- Positional association connectivity (**not recommended**)

```
COMPONENT xor2 IS
  PORT (
    I1 : IN STD_LOGIC;
    I2 : IN STD_LOGIC;
    Y  : OUT STD_LOGIC
  );
END COMPONENT;


U1: xor2 PORT MAP (A, B, U1_OUT);
```

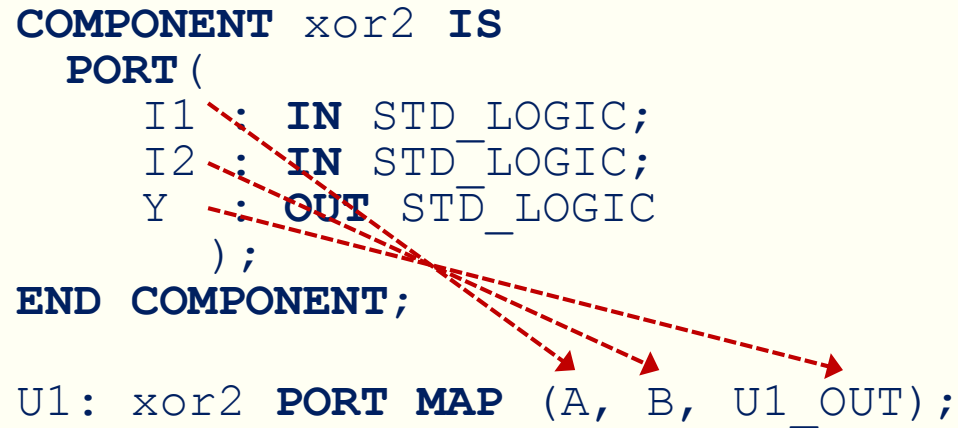
 
# Behavioral Architecture

---

```
ARCHITECTURE behavioral OF xor3 IS
BEGIN
xor3_behave: PROCESS (A,B,C)
BEGIN
  IF ((A XOR B XOR C) = '1') THEN
    Result <= '1';
  ELSE
    Result <= '0';
  END IF;
END PROCESS xor3_behave;
END behavioral;
```





# Dataflow VHDL


---

## *Major instructions*

### Concurrent statements


- concurrent signal assignment ( $\Leftarrow$ )
- conditional concurrent signal assignment (*when-else*)
- selected concurrent signal assignment (*with-select-when*)
- generate scheme for equations (*for-generate*)

# MLU Block Diagram

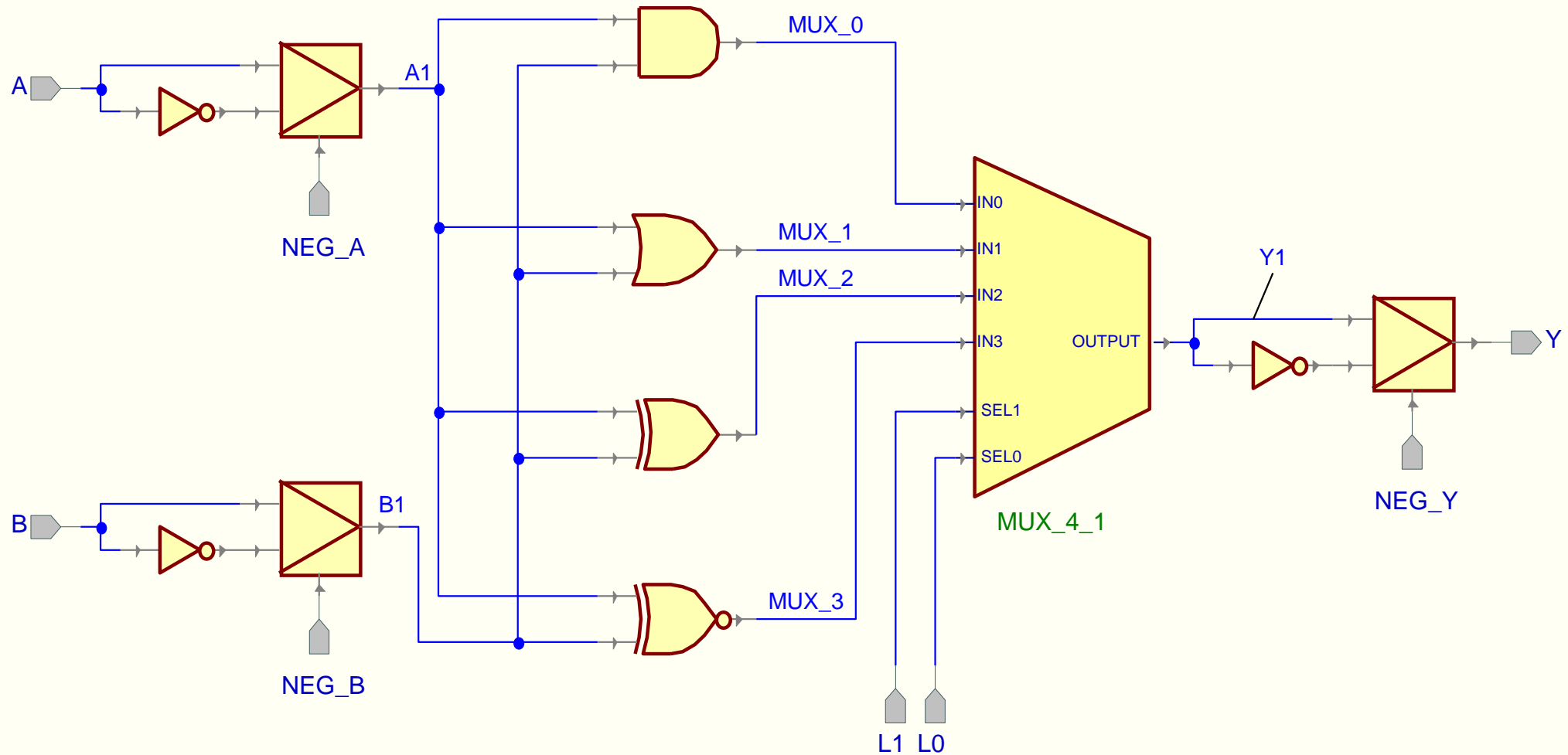
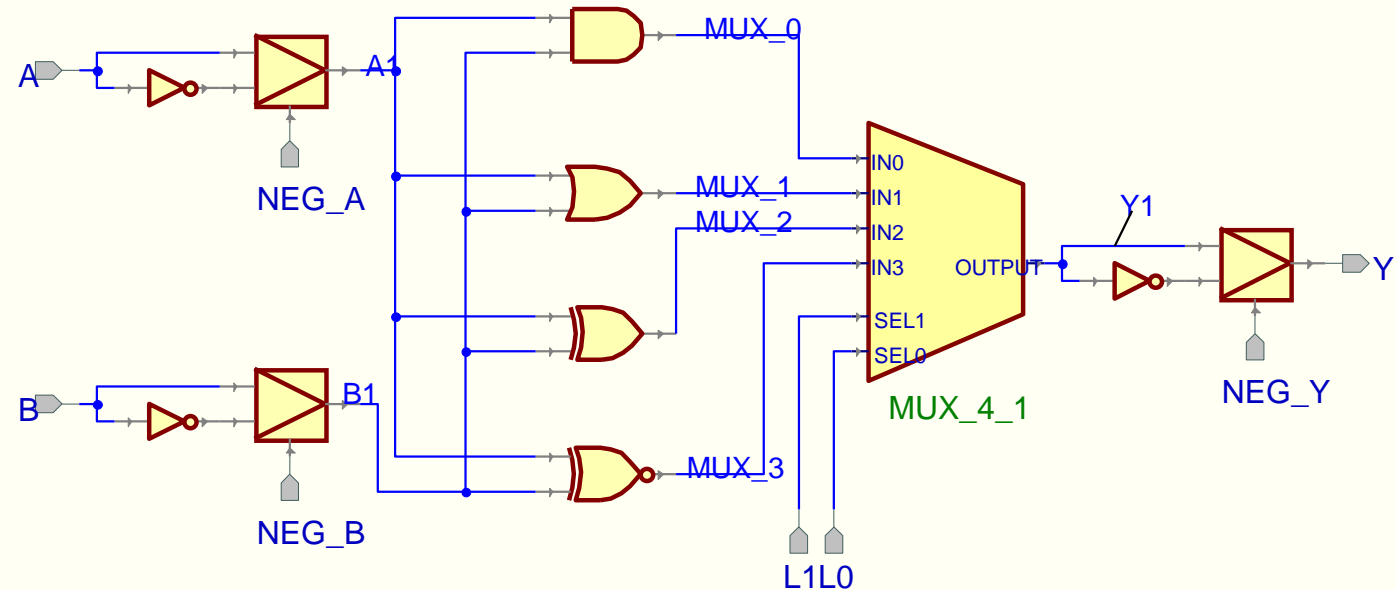
# MLU Entity Declaration


```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
  
ENTITY mlu IS  
  PORT (  
    NEG_A : IN STD_LOGIC;  
    NEG_B : IN STD_LOGIC;  
    NEG_Y : IN STD_LOGIC;  
    A      : IN STD_LOGIC;  
    B      : IN STD_LOGIC;  
    L1     : IN STD_LOGIC;  
    L0     : IN STD_LOGIC;  
    Y      : OUT STD_LOGIC  
  );  
END mlu;
```


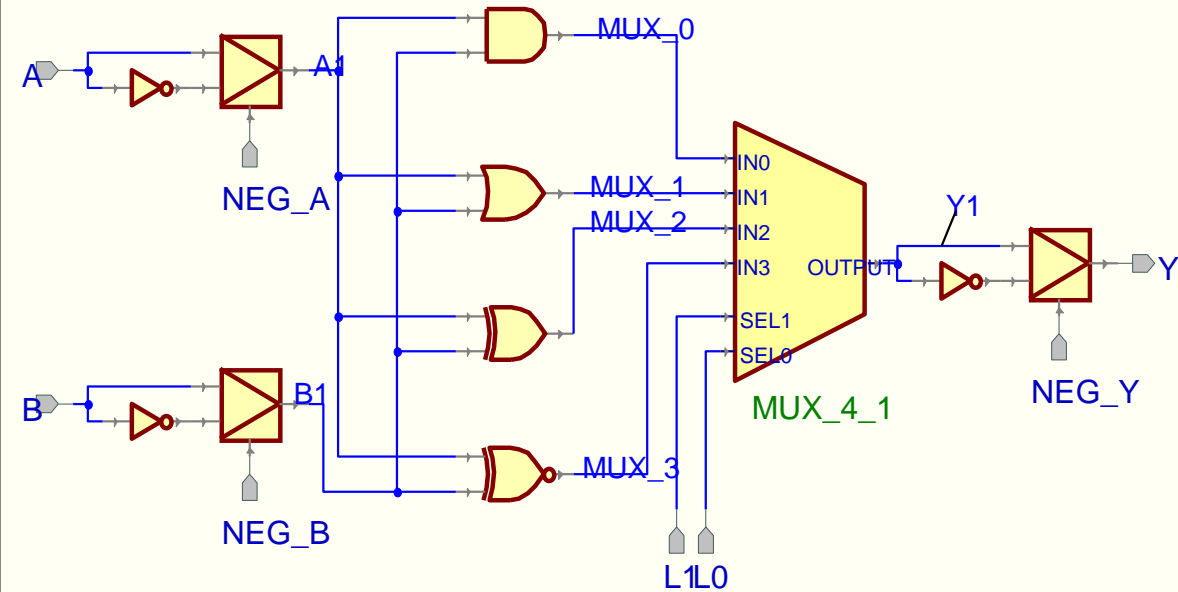
# MLU Architecture: Declarations

```
ARCHITECTURE mlu_dataflow OF mlu IS
```

```
SIGNAL A1 : STD_LOGIC;  
SIGNAL B1 : STD_LOGIC;  
SIGNAL Y1 : STD_LOGIC;  
SIGNAL MUX_0 : STD_LOGIC;  
SIGNAL MUX_1 : STD_LOGIC;  
SIGNAL MUX_2 : STD_LOGIC;  
SIGNAL MUX_3 : STD_LOGIC;  
SIGNAL L: STD_LOGIC_VECTOR(1 DOWNTO 0);
```



# MLU Architecture: Body


```
BEGIN
  A1<= NOT A  WHEN (NEG_A='1') ELSE A;
  B1<= NOT B  WHEN (NEG_B='1') ELSE B;
  Y  <= NOT Y1 WHEN (NEG_Y='1') ELSE Y1;

  MUX_0 <= A1  AND  B1;
  MUX_1 <= A1  OR   B1;
  MUX_2 <= A1  XOR  B1;
  MUX_3 <= A1  XNOR B1;

  L <= L1 & L0;

  with (L) select
    Y1  <=  MUX_0 WHEN "00",
           MUX_1 WHEN "01",
           MUX_2 WHEN "10",
           MUX_3 WHEN OTHERS;

END mlu_dataflow;
```

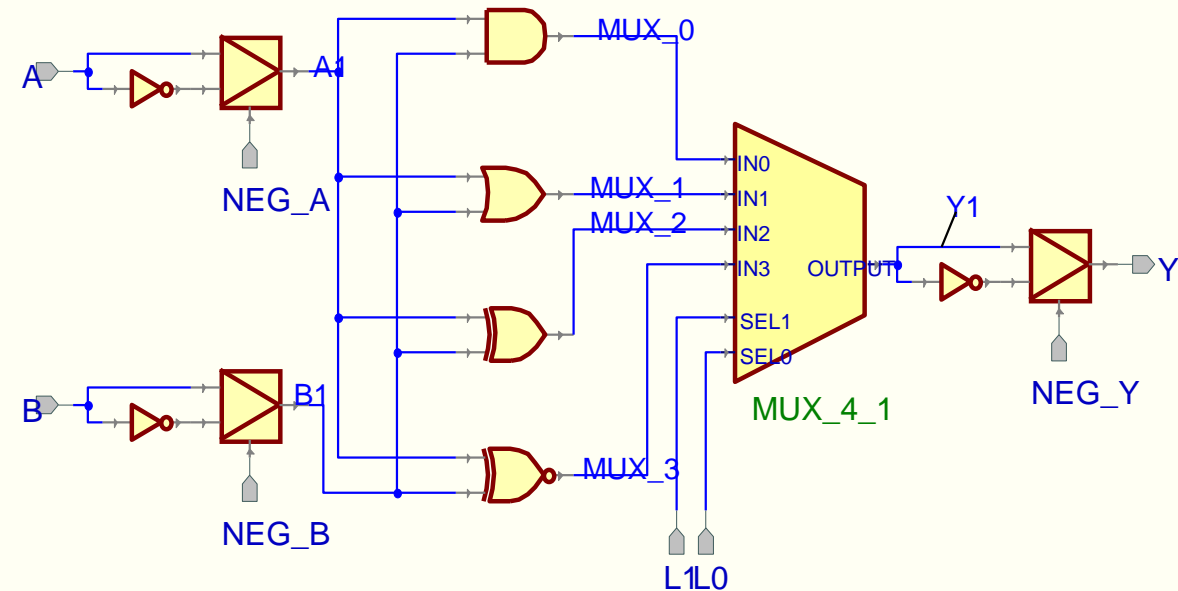


# FOR ... GENERATE

---

```
label: FOR identifier IN range GENERATE
        BEGIN
            {Concurrent Statements}
        END GENERATE;
```

# PARITY Example


---

 
 
# PARITY: Entity Declaration

---


```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
  
ENTITY parity IS  
  PORT (  
    parity_in  : IN STD_LOGIC_VECTOR(7 DOWNTO 0);  
    parity_out : OUT STD_LOGIC  
  );  
END parity;
```






# PARITY: Block Diagram

---

 

# PARITY: Block Diagram

---

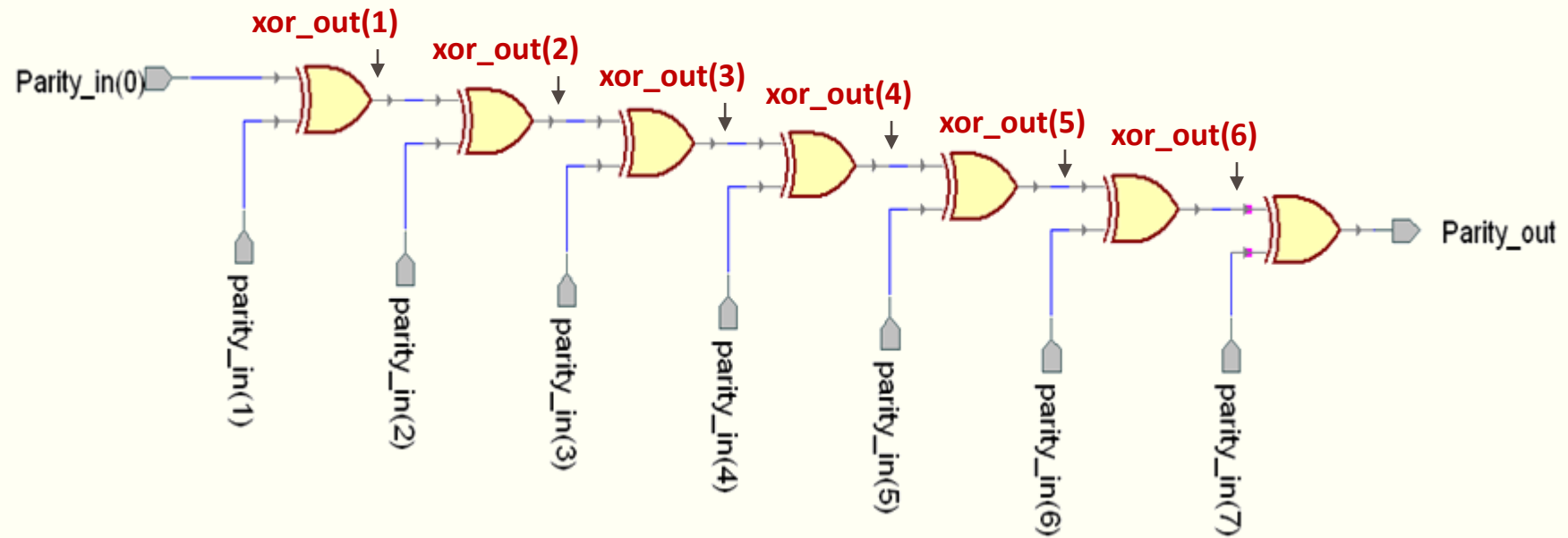

## PARITY: Architecture

---


```
ARCHITECTURE parity_dataflow OF parity IS
SIGNAL xor_out: std_logic_vector (6 downto 1);

BEGIN
    xor_out(1) <= parity_in(0) XOR parity_in(1);
    xor_out(2) <= xor_out(1) XOR parity_in(2);
    xor_out(3) <= xor_out(2) XOR parity_in(3);
    xor_out(4) <= xor_out(3) XOR parity_in(4);
    xor_out(5) <= xor_out(4) XOR parity_in(5);
    xor_out(6) <= xor_out(5) XOR parity_in(6);
    parity_out <= xor_out(6) XOR parity_in(7);

END parity_dataflow;
```

## PARITY: Block Diagram 2

---

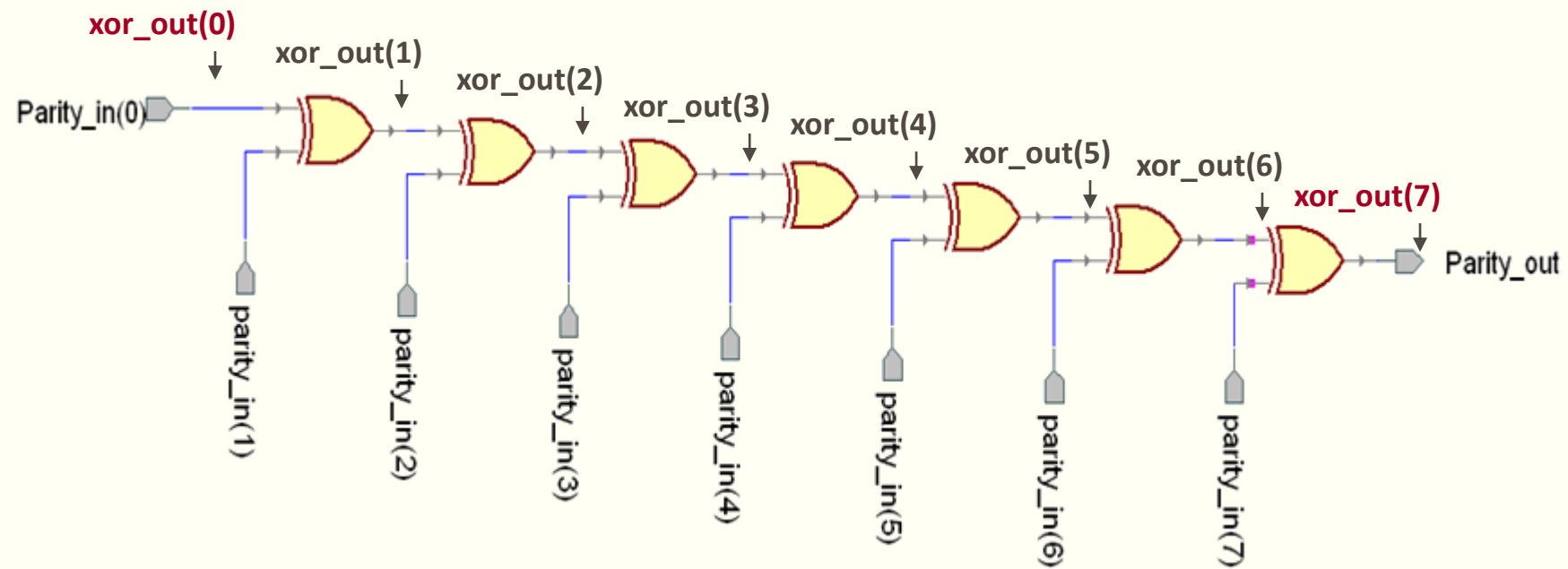

## PARITY: Architecture 2

---

```
ARCHITECTURE parity_dataflow OF parity IS

SIGNAL xor_out: STD_LOGIC_VECTOR (7 downto 0);

BEGIN

    xor_out(0) <= parity_in(0);
    xor_out(1) <= xor_out(0) XOR parity_in(1);
    xor_out(2) <= xor_out(1) XOR parity_in(2);
    xor_out(3) <= xor_out(2) XOR parity_in(3);
    xor_out(4) <= xor_out(3) XOR parity_in(4);
    xor_out(5) <= xor_out(4) XOR parity_in(5);
    xor_out(6) <= xor_out(5) XOR parity_in(6);
    xor_out(7) <= xor_out(6) XOR parity_in(7);
    parity_out <= xor_out(7);

END parity_dataflow;
```

## PARITY: Architecture 3

---

```
ARCHITECTURE parity_dataflow OF parity IS

SIGNAL xor_out: STD_LOGIC_VECTOR (7 DOWNT0 0);

BEGIN
    xor_out(0) <= parity_in(0);

    G2: FOR i IN 1 TO 7 GENERATE
        xor_out(i) <= xor_out(i-1) XOR parity_in(i);
    end generate G2;

    parity_out <= xor_out(7);

END parity_dataflow;
```

# Simple Rules

---

- For combinational logic, use **only concurrent** statements:
  - concurrent signal assignment ( $\Leftarrow$ )
  - conditional concurrent signal assignment (when-else)
  - selected concurrent signal assignment (with-select-when)
  - generate scheme for equations (for-generate)

# Simple Rules

---

- For circuits composed of
  - simple logic operations (logic gates)
  - simple arithmetic operations (addition, subtraction, multiplication)
  - shifts/rotations by a constant

use **concurrent signal assignment** ( $\Leftarrow$ )



# Simple Rules

---

- For circuits composed of
  - Multiplexers
  - decoders, encoders
  - tri-state buffers

use:

- conditional concurrent signal assignment (when-else)
- selected concurrent signal assignment (with-select-when)

# Arithmetic Operators

---

- Synthesizable arithmetic operations:
  - Addition, +
  - Subtraction, -
  - Comparisons, >, >=, <, <=
  - Multiplication, \*
  - Division by a power of 2,  $/2^{**}6$  (equivalent to right shift)
  - Shifts by a constant, SHL, SHR

# Arithmetic Operators

---

---


- The result of synthesis of an arithmetic operation is a
  - combinational circuit
  - without pipelining

The exact internal **architecture** used (and thus delay and area of the circuit) **may depend** on the **timing constraints** specified during synthesis (e.g., the requested maximum clock frequency).

# Anatomy of a Process

---

OPTIONAL

 

```
[label:] process [(sensitivity list)]  
    [declaration part]  
begin  
    statement part  
end process [label];
```

## Statement Part

---

- Contains **Sequential** Statements to be Executed Each Time the Process Is Activated
- Analogous to Conventional Programming Languages

# What is a Process

---

- A process is a sequence of instructions referred to as sequential statements.
- A process can be given a unique name using an optional LABEL
- This is followed by the keyword PROCESS
- The keyword BEGIN is used to indicate the start of the process
- All statements within the process are executed **SEQUENTIALLY**. Hence, order of statements is important.
- A process must end with the keywords END PROCESS.

The Keyword PROCESS

TESTING: process  
begin


```
TEST_VECTOR<="00";  
wait for 10 ns;  
TEST_VECTOR<="01";  
wait for 10 ns;  
TEST_VECTOR<="10";  
wait for 10 ns;  
TEST_VECTOR<="11";  
wait for 10 ns;
```

end process;
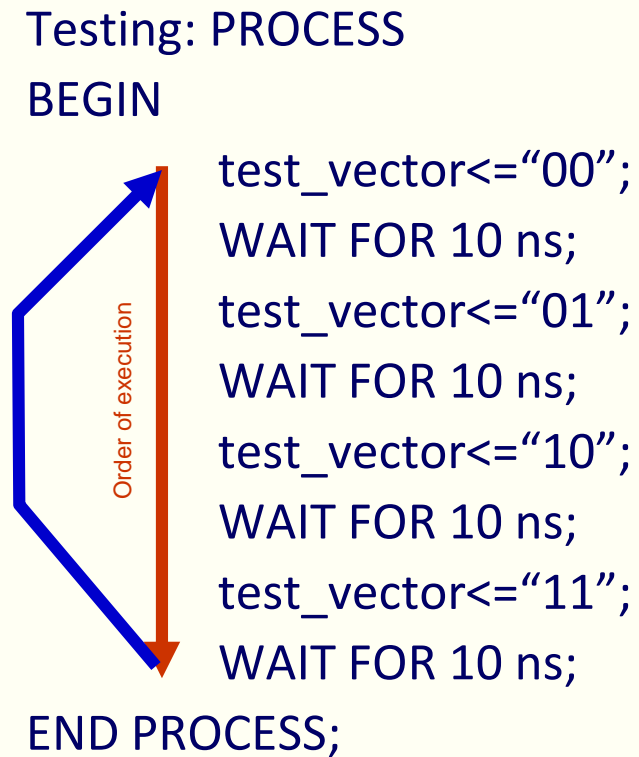
# Execution of Statements

---

- The execution of statements continues sequentially till the last statement in the process.
- After execution of the last statement, the control is again passed to the beginning of the process.



Program control is passed to the first statement after BEGIN

# WAIT Statement

---

- The last statement in the PROCESS is a **WAIT** instead of WAIT FOR 10 ns.
- This will cause the PROCESS to **suspend indefinitely** when the WAIT statement is executed.
- This form of WAIT can be used in a process included in a testbench when all possible combinations of inputs have been tested or a non-periodical signal has to be generated.

Testing: PROCESS

BEGIN

test\_vector<="00";  
WAIT FOR 10 ns;  
test\_vector<="01";  
WAIT FOR 10 ns;  
test\_vector<="10";  
WAIT FOR 10 ns;  
test\_vector<="11";

Order of execution

**WAIT;**

END PROCESS;

Program execution stops here




## WAIT FOR vs WAIT

---

---

 **WAIT FOR:** waveform will keep repeating itself forever




**WAIT :** waveform will keep its state after the last wait instruction.


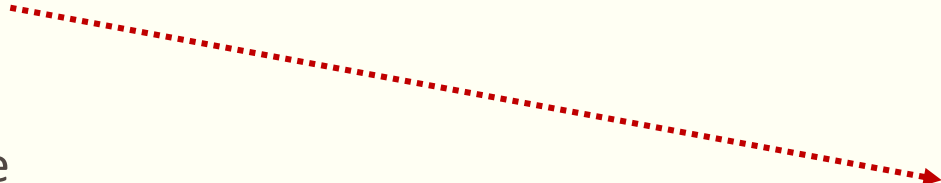
# Sensitivity List

---

- List of signals to which the process is sensitive.
- Whenever there is an event on any of the signals in the sensitivity list, the process fires.
- Every time the process fires, it will run in its entirety.
- **WAIT statements are NOT ALLOWED in a process with SENSITIVITY LIST.**



```
label: process (sensitivity list)  
           declaration part  
begin  
           statement part  
end process;
```


# Process Suitability

---

- Processes Describe Sequential Behavior
- Processes in VHDL Are Very Powerful Statements
  - Allow to define an arbitrary behavior that may be difficult to represent by a real circuit
  - Not every process can be synthesized
- Use Processes with Caution in the Code to Be Synthesized
- Use Processes Freely in Testbenches
 
# Component Equivalent of a Process

```
priority: PROCESS (clk)
BEGIN
  IF w(3) = '1' THEN
    y <= "11" ;
  ELSIF w(2) = '1' THEN
    y <= "10" ;
  ELSIF w(1) = c THEN
    y <= a and b ;
  ELSE
    z <= "00" ;
  END IF ;
END PROCESS ;
```



- All signals which appear on the left of signal assignment statement (<=) are outputs e.g. *y*, *z*
- All signals which appear on the right of signal assignment statement (<=) or in logic expressions are inputs e.g. *w*, *a*, *b*, *c*
- All signals which appear in the sensitivity list are inputs e.g. *clk*
- Note that not all inputs need to be included in the sensitivity list

# IF Statement - Syntax

---

If Statement

```
if boolean expression then
    statements
elsif boolean expression then
    statements
else boolean expression then
    statements
end if;
```

else and elsif are optional

## IF Statement: Example

---


```
SELECTOR: process
begin
    WAIT UNTIL Clock'EVENT AND Clock = '1' ;
    IF Sel = "00" THEN
        f <= x1;
    ELSIF Sel = "10" THEN
        f <= x2;
    ELSE
        f <= x3;
    END IF;
end process;
```

## 2-to-4 Decoder

---

$En$	$w_1$	$w_0$	$y_0$	$y_1$	$y_2$	$y_3$
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

(a) Truth table

 


(b) Graphical symbol

# Dataflow Description (1/2)

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY dec2to4 IS
    PORT ( w      : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
          En     : IN      STD_LOGIC ;
          y      : OUT     STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
END dec2to4 ;

 ARCHITECTURE dataflow OF dec2to4 IS
    SIGNAL Enw : STD_LOGIC_VECTOR(2 DOWNTO 0) ;
BEGIN
    Enw <= En & w ;
    WITH Enw SELECT
        y <= "0001" WHEN "100",
            "0010" WHEN "101",
            "0100" WHEN "110",
            "1000" WHEN "111",
            "0000" WHEN OTHERS ;
END dataflow ;
```



(b) Graphical symbol



## Dataflow Description (2/2)

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY dec2to4 IS
    PORT ( w      : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
          En     : IN      STD_LOGIC ;
          y      : OUT     STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
END dec2to4 ;


ARCHITECTURE dataflow OF dec2to4 IS
    SIGNAL Enw : STD_LOGIC_VECTOR(2 DOWNTO 0) ;
BEGIN
    Enw <= En & w ;
    WITH Enw SELECT
        y <= "0001" WHEN "100",
            "0010" WHEN "101",
            "0100" WHEN "110",
            "1000" WHEN "111",
            "0000" WHEN OTHERS ;
END dataflow ;
```

$En$	$w_1$	$w_0$	$y_0$	$y_1$	$y_2$	$y_3$
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

(a) Truth table
 
## Behavioral Description (1/2)

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY dec2to4 IS
    PORT ( w      : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
          En     : IN      STD_LOGIC ;
          y      : OUT     STD_LOGIC_VECTOR(0 TO 3) ) ;
END dec2to4 ;
ARCHITECTURE Behavior OF dec2to4 IS
BEGIN
    PROCESS ( w, En )
    BEGIN
        IF En = '1' THEN
            CASE w IS
                WHEN "00" =>      y <= "1000" ;
                WHEN "01" =>      y <= "0100" ;
                WHEN "10" =>      y <= "0010" ;
                WHEN OTHERS =>    y <= "0001" ;
            END CASE ;
        ELSE
            y <= "0000" ;
        END IF ;
    END PROCESS ;
END Behavior ;
```



(b) Graphical symbol

## Behavioral Description (2/2)

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY dec2to4 IS
    PORT ( w      : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
          En      : IN      STD_LOGIC ;
          y       : OUT     STD_LOGIC_VECTOR(0 TO 3) ) ;
END dec2to4 ;
ARCHITECTURE Behavior OF dec2to4 IS
BEGIN
    PROCESS ( w, En )
    BEGIN
        IF En = '1' THEN
            CASE w IS
                WHEN "00" =>      y <= "1000" ;
                WHEN "01" =>      y <= "0100" ;
                WHEN "10" =>      y <= "0010" ;
                WHEN OTHERS =>    y <= "0001" ;
            END CASE ;
        ELSE
            y <= "0000" ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

$En$	$w_1$	$w_0$	$y_0$	$y_1$	$y_2$	$y_3$
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

(a) Truth table

# 7 Segment Display

```
LIBRARY ieee ; USE ieee.std_logic_1164.all ;
ENTITY seg7 IS
    PORT (bcd : IN  STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          leds : OUT STD_LOGIC_VECTOR(1 TO 7) ) ;
END seg7 ;
ARCHITECTURE Behavior OF seg7 IS
BEGIN
    PROCESS ( bcd )
    BEGIN
        CASE bcd IS
            --      abcdefg
            WHEN "0000" => leds <= "1111110" ;
            WHEN "0001" => leds <= "0110000" ;
            WHEN "0010" => leds <= "1101101" ;
            WHEN "0011" => leds <= "1111001" ;
            WHEN "0100" => leds <= "0110011" ;
            WHEN "0101" => leds <= "1011011" ;
            WHEN "0110" => leds <= "1011111" ;
            WHEN "0111" => leds <= "1110000" ;
            WHEN "1000" => leds <= "1111111" ;
            WHEN "1001" => leds <= "1110011" ;
            WHEN OTHERS => leds <= "-----" ;
        END CASE ;
    END PROCESS ;
END Behavior ;
```

# Comparator

---

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY compare1 IS
    PORT ( A, B : IN    STD_LOGIC ;
          AeqB : OUT   STD_LOGIC ) ;
END compare1 ;

ARCHITECTURE Behavior OF compare1 IS
BEGIN
    PROCESS ( A, B )
    BEGIN
        AeqB <= '0' ;
        IF A = B THEN
            AeqB <= '1' ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

# Latch Inference

---


```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY implied IS
    PORT ( A, B : IN    STD_LOGIC ;
          AeqB : OUT   STD_LOGIC ) ;
END implied ;

ARCHITECTURE Behavior OF implied IS
BEGIN
    PROCESS ( A, B )
    BEGIN
        IF A = B THEN
            AeqB <= '1' ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

# Latch Inference

---

 

# Combinational Circuits with Processes

---

- Rules that need to be followed:
  - All inputs to the combinational circuit should be included in the sensitivity list
  - No other signals should be included in the sensitivity list
  - None of the statements within the process should be sensitive to rising or falling edges
  - All possible cases need to be covered in the internal **IF** and **CASE** statements in order to avoid implied latches



# Covering all Combinations with IF

---

## Using ELSE

```
IF A = B THEN
    AeqB <= '1' ;
ELSE
    AeqB <= '0' ;
```

## Using default values

```
AeqB <= '0' ;
IF A = B THEN
    AeqB <= '1' ;
```

# Covering all Combinations with CASE

---

Using WHEN OTHERS

```
CASE y IS
  WHEN S1 => z <= "10";
  WHEN S2 => z <= "01";
  WHEN OTHERS => z <= "00";
END CASE;
```


```
CASE y IS
  WHEN S1 => z <= "10";
  WHEN S2 => z <= "01";
  WHEN S3 => z <= "00";
  WHEN OTHERS => z <= "--";
END CASE;
```

Using default values

```
z <= "00";
CASE y IS
  WHEN S1 => z <= "10";
  WHEN S2 => z <= "10";
END CASE;
```

# Sequential Logic: D Latch


Graphical symbol

 

Truth table


Clock	D	$Q(t+1)$
0	–	$Q(t)$
1	0	0
1	1	1

Timing diagram

 

# Sequential Logic: D Flip-flop


Graphical symbol

 

Truth table

Clk	D	$Q(t+1)$
↑	0	0
↑	1	1
0	—	$Q(t)$
1	—	$Q(t)$

Timing diagram

 


# VHDL Code: D Latch

---

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY latch IS
    PORT ( D, Clock : IN  STD_LOGIC ;
          Q          : OUT STD_LOGIC) ;
END latch ;

 ARCHITECTURE Behavior OF latch IS
BEGIN
    PROCESS ( D, Clock )
    BEGIN
        IF Clock = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior;
```




# VHDL Code: D Flip-flop

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY flipflop IS
    PORT ( D, Clock : IN  STD_LOGIC ;
          Q          : OUT STD_LOGIC) ;
END flipflop ;

 ARCHITECTURE Behavior_1 OF flipflop IS
BEGIN
    PROCESS ( Clock )
    BEGIN
        IF Clock'EVENT AND Clock = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior_1 ;
```




# VHDL Code: D Flip-flop

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY flipflop IS
    PORT ( D, Clock : IN  STD_LOGIC ;
          Q          : OUT STD_LOGIC) ;
END flipflop ;

 ARCHITECTURE Behavior_1 OF flipflop IS
BEGIN
    PROCESS ( Clock )
    BEGIN
        IF rising_edge(Clock) THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior_1 ;
```




# VHDL Code: D Flip-flop

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY flipflop IS
    PORT ( D, Clock : IN  STD_LOGIC ;
          Q         : OUT STD_LOGIC) ;
END flipflop ;

 ARCHITECTURE Behavior_2 OF flipflop IS
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL Clock'EVENT AND Clock = '1' ;
        Q <= D ;
    END PROCESS ;
END Behavior_2 ;
```






# VHDL Code: D Flip-flop

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY flipflop IS
    PORT ( D, Clock : IN  STD_LOGIC ;
          Q         : OUT STD_LOGIC) ;
END flipflop ;

 ARCHITECTURE Behavior_2 OF flipflop IS
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL rising_edge(Clock) ;
        Q <= D ;
    END PROCESS ;
END Behavior_2 ;
```




# VHDL Code: D Flip-flop Async Reset

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY flipflop IS
    PORT ( D, Resetn, Clock : IN  STD_LOGIC ;
          Q                : OUT STD_LOGIC) ;
END flipflop ;

 
ARCHITECTURE Behavior OF flipflop IS
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            Q <= '0' ;
        ELSIF Clock'EVENT AND Clock = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```


 
# VHDL Code: D Flip-flop Sync Reset

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY flipflop IS
    PORT ( D, Resetn, Clock : IN  STD_LOGIC ;
          Q                : OUT STD_LOGIC) ;
END flipflop ;

ARCHITECTURE Behavior OF flipflop IS
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL Clock'EVENT AND Clock = '1' ;
        IF Resetn = '0' THEN
            Q <= '0' ;
        ELSE
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```



## Variables: Example

---

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
  
ENTITY Numbits IS  
    PORT ( X      : IN      STD_LOGIC_VECTOR(1 TO 3) ;  
          Count  : OUT     INTEGER RANGE 0 TO 3) ;  
END Numbits ;
```

# Variables: Example

---

```
ARCHITECTURE Behavior OF Numbits IS

BEGIN

  PROCESS (X) - count the number of bits in X equal to 1
    VARIABLE Tmp: INTEGER;
    BEGIN
      Tmp := 0;
      FOR i IN 1 TO 3 LOOP
        IF X(i) = '1' THEN
          Tmp := Tmp + 1;
        END IF;
      END LOOP;
      Count <= Tmp;
    END PROCESS;

END Behavior ;
```

# Variables: Features

---

- Can only be declared **within processes** and subprograms (functions & procedures)
- **Initial value** can be explicitly specified in the declaration
- When assigned take an assigned value **immediately**
- Variable assignments represent the desired **behavior**, not the structure of the circuit
- Should be avoided, or at least used with **caution** in a synthesizable code

# Variable vs Signal – Variable Example

---

```
ARCHITECTURE Behavior OF Numbits IS

BEGIN

    PROCESS (X) - count the number of bits in X equal to 1
    VARIABLE Tmp: INTEGER;
    BEGIN
        Tmp := 0;
        FOR i IN 1 TO 3 LOOP
            IF X(i) = '1' THEN
                Tmp := Tmp + 1;
            END IF;
        END LOOP;
        Count <= Tmp;
    END PROCESS;

END Behavior ;
```

# Variable vs Signal: NAND Gate

---

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY NANDn IS
    GENERIC (n: INTEGER := 8)
    PORT (    X: IN STD_LOGIC_VECTOR(1 TO n);
           Y: OUT STD_LOGIC);
END NANDn;
```



# Variable vs Signal: NAND Gate - Var

---

```
ARCHITECTURE behaviorall OF NANDn IS
BEGIN

    PROCESS (X)
        VARIABLE Tmp: STD_LOGIC;
        BEGIN
            Tmp := X(1);

            AND_bits: FOR i IN 2 TO n LOOP
                Tmp := Tmp AND X( i ) ;
            END LOOP AND_bits ;

            Y <= NOT Tmp ;

        END PROCESS;

    END behaviorall ;
```

# Variable vs Signal: NAND Gate - Signal

---

```
ARCHITECTURE dataflow1 OF NANDn IS

    SIGNAL Tmp: STD_LOGIC_VECTOR(1 TO n);

BEGIN
    Tmp(1) <= X(1);

    AND_bits: FOR i IN 2 TO n GENERATE
        Tmp(i) <= Tmp(i-1) AND X(i) ;
    END LOOP AND_bits ;

    Y <= NOT Tmp(n) ;


END dataflow1 ;
```

# Structural VHDL

---


- Major instructions:
  - component instantiation (port map)
  - generate scheme for component instantiations (for-generate)
  - component instantiation with generic (generic map, port map)

# Structural VHDL: Example

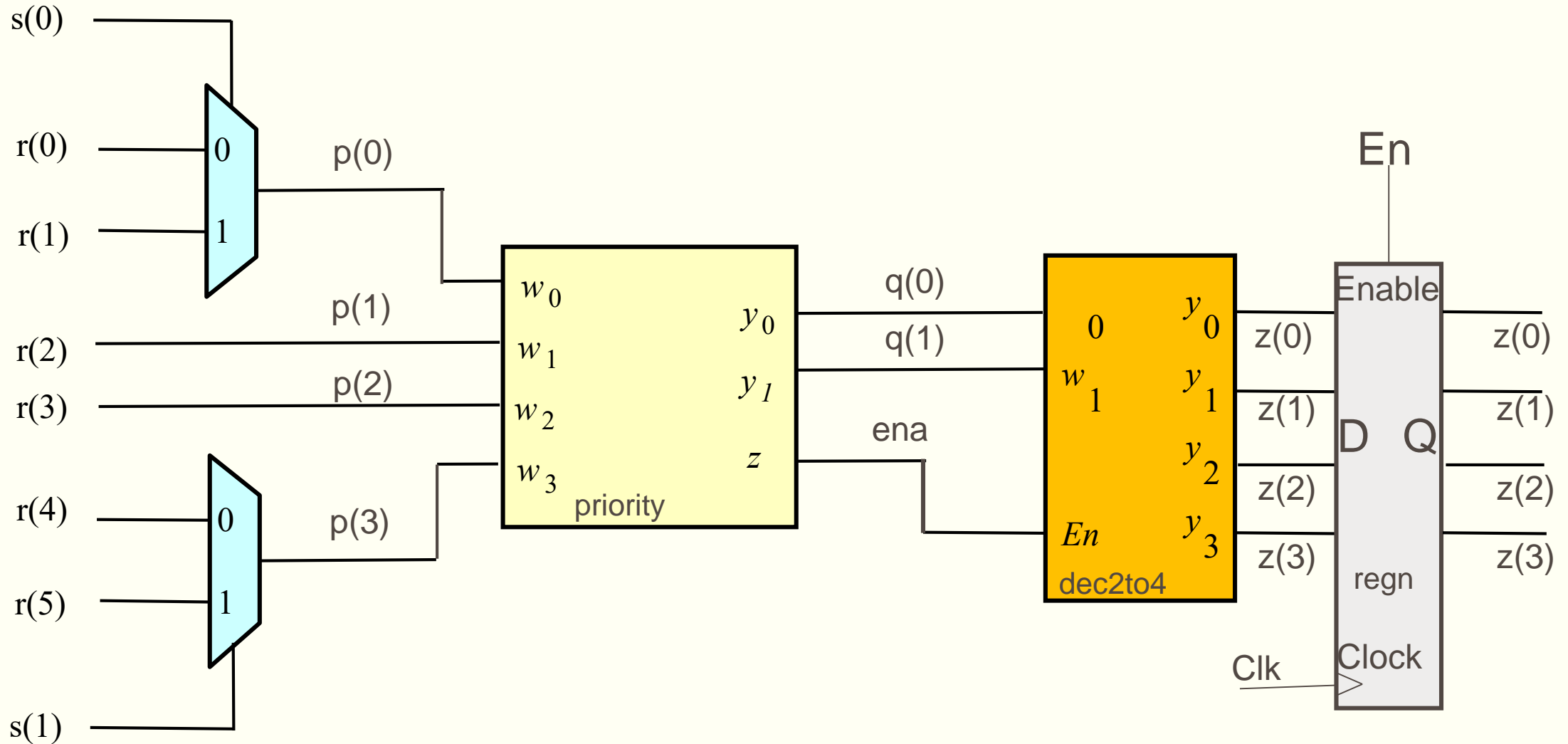

# 2-to-1 Multiplexer

---

 

(a) Graphical symbol

$s$	$f$
0	$w_0$
1	$w_1$

(b) Truth table

# VHDL Code for 2-to-1 Multiplexer

---

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;


ENTITY mux2to1 IS
PORT ( w0, w1, s : IN  STD_LOGIC ;
      f : OUT STD_LOGIC ) ;
END mux2to1 ;

ARCHITECTURE dataflow OF mux2to1 IS
BEGIN
    f <= w0 WHEN s = '0' ELSE w1 ;
END dataflow ;
```

# Priority Encoder

---

---

 

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$	$z$
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

# VHDL Code for Priority Encoder

---

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY priority IS
    PORT (w      : IN    STD_LOGIC_VECTOR(3 DOWNT0 0) ;
          y      : OUT  STD_LOGIC_VECTOR(1 DOWNT0 0) ;
          z      : OUT  STD_LOGIC ) ;
END priority ;

ARCHITECTURE dataflow OF priority IS
BEGIN
    y <= "11" WHEN w(3) = '1' ELSE
        "10" WHEN w(2) = '1' ELSE
        "01" WHEN w(1) = '1' ELSE
        "00" ;
    z <= '0' WHEN w = "0000" ELSE '1' ;
END dataflow ;
```




## 2-to-4 Decoder

---

$En$	$w_1$	$w_0$	$y_0$	$y_1$	$y_2$	$y_3$
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

(a) Truth table

 

(b) Graphical symbol

# VHDL Code for 2-to-4 Decoder

---

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;


ENTITY dec2to4 IS
    PORT (w : IN          STD_LOGIC_VECTOR(1 DOWNTO 0) ;
          En : IN         STD_LOGIC ;
          y : OUT STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
END dec2to4 ;

ARCHITECTURE dataflow OF dec2to4 IS
    SIGNAL Enw : STD_LOGIC_VECTOR(2 DOWNTO 0) ;
BEGIN
    Enw <= En & w ;
    WITH Enw SELECT
        y <= "0001" WHEN "100",
            "0010" WHEN "101",
            "0100" WHEN "110",
            "1000" WHEN "111",
            "0000" WHEN OTHERS ;
END dataflow ;
```

 
# N-bit Register with Enable

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY regn IS
    GENERIC ( N : INTEGER := 8 ) ;
    PORT ( D: IN  STD_LOGIC_VECTOR(N-1 DOWNTO 0) ;
Enable, Clock : IN  STD_LOGIC ;
          Q : OUT STD_LOGIC_VECTOR(N-1 DOWNTO 0) ) ;
END regn ;

ARCHITECTURE Behavior OF regn IS
BEGIN
    PROCESS (Clock)
    BEGIN
        IF (Clock'EVENT AND Clock = '1' ) THEN
            IF Enable = '1' THEN
                Q <= D ;
            END IF ;
        END IF ;
    END PROCESS ;
END Behavior ;
```



# Circuit Built with Components

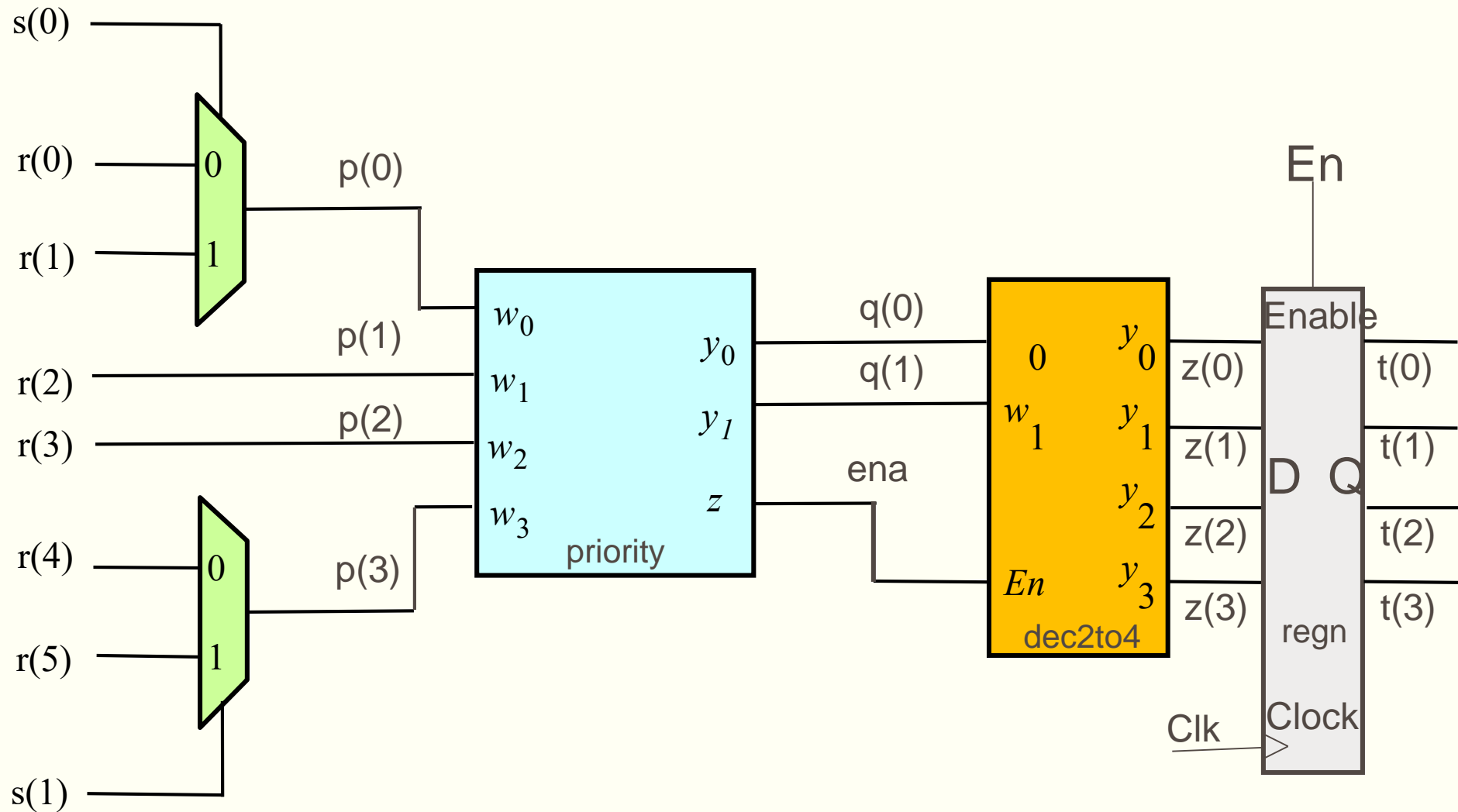

# Structural Description

---

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY priority_resolver IS
    PORT (r : IN STD_LOGIC_VECTOR(5 DOWNTO 0) ;
          s : IN STD_LOGIC_VECTOR(1 DOWNTO 0) ;
          clk : IN STD_LOGIC;
          en : IN STD_LOGIC;
          t : OUT STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
END priority_resolver;

ARCHITECTURE structural OF priority_resolver IS

    SIGNAL p: STD_LOGIC_VECTOR (3 DOWNTO 0) ;
    SIGNAL q: STD_LOGIC_VECTOR (1 DOWNTO 0) ;
    SIGNAL z: STD_LOGIC_VECTOR (3 DOWNTO 0) ;
    SIGNAL ena: STD_LOGIC ;
```

# Structural Description

---

```
COMPONENT mux2to1
  PORT (w0, w1, s : IN  STD_LOGIC ;
        f: OUT  STD_LOGIC ) ;
END COMPONENT ;

COMPONENT priority
  PORT (w   : IN   STD_LOGIC_VECTOR(3 DOWNTO 0) ;
        y   : OUT  STD_LOGIC_VECTOR(1 DOWNTO 0) ;
        z   : OUT  STD_LOGIC ) ;
END COMPONENT ;

COMPONENT dec2to4
  PORT (w   : IN   STD_LOGIC_VECTOR(1 DOWNTO 0) ;
        En  : IN   STD_LOGIC ;
        y   : OUT  STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
END COMPONENT ;
```

# Structural Description

---

```
COMPONENT regn
  GENERIC ( N : INTEGER := 8 ) ;
  PORT    ( D : IN      STD_LOGIC_VECTOR(N-1 DOWNT0 0) ;
           Enable, Clock : IN STD_LOGIC ;
           Q : OUT     STD_LOGIC_VECTOR(N-1 DOWNT0 0) ) ;
END COMPONENT ;
```

# Structural Description

---

```
BEGIN
```

```
u1: mux2to1 PORT MAP (w0 => r(0) ,  
                      w1 => r(1) ,  
                      s => s(0) ,  
                      f => p(0)) ;
```

```
p(1) <= r(2) ;  
p(1) <= r(3) ;
```

```
u2: mux2to1 PORT MAP (w0 => r(4) ,  
                      w1 => r(5) ,  
                      s => s(1) ,  
                      f => p(3)) ;
```

```
u3: priority PORT MAP (w => p ,  
                      y => q ,  
                      z => ena) ;
```

```
u4: dec2to4 PORT MAP (w => q ,  
                     En => ena ,  
                     y => z) ;
```



# Structural Description

---

```
u5: regn GENERIC MAP (N => 4)
      PORT MAP (D => z ,
                Enable => En ,
                Clock => Clk,
                Q => t );
END structural;
```

## Structural Description – Pos. Assoc.

---

```
BEGIN
```

```
u1: mux2to1 PORT MAP (r(0), r(1), s(0), p(0));
```

```
p(1) <= r(2);
```

```
p(1) <= r(3);
```

```
u2: mux2to1 PORT MAP (r(4), r(5), s(1), p(3));
```

```
u3: priority PORT MAP (p, q, ena);
```

```
u4: dec2to4 PORT MAP (q, ena, z);
```

```
u5: regn GENERIC MAP(4) PORT MAP (z, En, Clk, t);
```

```
END structural;
```

# Configuration Declaration

---

```
CONFIGURATION SimpleCfg OF priority_resolver IS

  FOR structural

    FOR ALL: mux2to1
      USE ENTITY work.mux2to1 (dataflow) ;
    END FOR;

    FOR u3: priority
      USE ENTITY work.priority (dataflow) ;
    END FOR;

    FOR u4: dec2to4
      USE ENTITY work.dec2to4 (dataflow) ;
    END FOR;

  END FOR;

END SimpleCfg;
```

# Configuration Specification

---

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE work.GatesPkg.all;

ENTITY priority_resolver IS
    PORT (r : IN  STD_LOGIC_VECTOR(5 DOWNTO 0) ;
          s : IN  STD_LOGIC_VECTOR(1 DOWNTO 0) ;
          z : OUT STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
END priority_resolver;

ARCHITECTURE structural OF priority_resolver IS

    SIGNAL    p : STD_LOGIC_VECTOR (3 DOWNTO 0) ;
    SIGNAL    q : STD_LOGIC_VECTOR (1  DOWNTO 0) ;
    SIGNAL    ena: STD_LOGIC ;

    FOR ALL: mux2to1      USE ENTITY work.mux2to1 (dataflow) ;
    FOR u3:  priority     USE ENTITY work.priority (dataflow) ;
    FOR u4:  dec2to4      USE ENTITY work.dec2to4 (dataflow) ;
```


# Structural VHDL

---

- Major instructions:
  - component instantiation (port map)
  - component instantiation with generic (generic map, port map)
  - generate scheme for component instantiations (for-generate)

# 16-to-1 Multiplexer

---

 

# VHDL Code for 4-to-1 Multiplexer

---

---

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux4to1 IS
    PORT (w0, w1, w2, w3 : IN    STD_LOGIC ;
          s                : IN    STD_LOGIC_VECTOR(1 DOWNTO 0) ;
          f                : OUT STD_LOGIC ) ;
END mux4to1 ;

ARCHITECTURE Dataflow OF mux4to1 IS
BEGIN
    WITH s SELECT
        f <= w0 WHEN "00",
            w1 WHEN "01",
            w2 WHEN "10",
            w3 WHEN OTHERS ;
END Dataflow ;
```

# Straightforward Code for 16-to-1 MUX

---

---

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY Example1 IS
    PORT ( w      : IN    STD_LOGIC_VECTOR(0 TO 15) ;
          s      : IN    STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          f      : OUT   STD_LOGIC ) ;
END Example1 ;
```



# Straightforward Code for 16-to-1 MUX

```
ARCHITECTURE Structure OF Example1 IS
```

```
    COMPONENT mux4to1
```

```
        PORT (w0, w1, w2, w3      : IN    STD_LOGIC  ;
              s                    : IN    STD_LOGIC_VECTOR(1 DOWNTO 0) ;
              f                    : OUT    STD_LOGIC  ) ;
```

```
    END COMPONENT ;
```

```
    SIGNAL m : STD_LOGIC_VECTOR(0 TO 3) ;
```

```
BEGIN
```

```
    Mux1: mux4to1 PORT MAP ( w(0), w(1), w(2), w(3),      s(1 DOWNTO 0), m(0) ) ;
```

```
    Mux2: mux4to1 PORT MAP ( w(4), w(5), w(6), w(7),      s(1 DOWNTO 0), m(1) ) ;
```

```
    Mux3: mux4to1 PORT MAP ( w(8), w(9), w(10), w(11),    s(1 DOWNTO 0), m(2) ) ;
```

```
    Mux4: mux4to1 PORT MAP ( w(12),w(13),w(14), w(15),    s(1 DOWNTO 0), m(3) ) ;
```

```
    Mux5: mux4to1 PORT MAP ( m(0), m(1), m(2),  m(3),      s(3 DOWNTO 2),  f  ) ;
```

```
END Structure ;
```

# Modified Code for 16-to-1 MUX

---

---

```
ARCHITECTURE Structure OF Example1 IS
```

```
COMPONENT mux4to1
```

```
PORT (w0, w1, w2, w3 : IN STD_LOGIC ;
```

```
      s : IN STD_LOGIC_VECTOR(1 DOWNTO 0) ;
```

```
      f : OUT STD_LOGIC ) ;
```

```
END COMPONENT ;
```

```
SIGNAL m : STD_LOGIC_VECTOR(0 TO 3) ;
```

```
BEGIN
```

```
    G1: FOR i IN 0 TO 3 GENERATE
```

```
        Muxes: mux4to1 PORT MAP (
```

```
            w(4*i), w(4*i+1), w(4*i+2), w(4*i+3), s(1 DOWNTO 0), m(i) ) ;
```

```
    END GENERATE ;
```

```
    Mux5: mux4to1 PORT MAP ( m(0), m(1), m(2), m(3), s(3 DOWNTO 2), f ) ;
```

```
END Structure ;
```

# Array Attributes

---

---

Attribute	Description
A'left(N)	left bound of index range of dimension N of A
A'right(N)	right bound of index range of dimension N of A
A'low(N)	lower bound of index range of dimension N of A
A'high(N)	upper bound of index range of dimension N of A
A'range(N)	index range of dimension N of A
A'reverse_range(N)	reversed index range of dimension N of A
A'length(N)	length of index range of dimension N of A
A'ascending(N)	true if index range of dimension N of A is an ascending range, false otherwise

## Array Attributes: Example

---

```
type A is array (1 to 4, 31 downto 0);
```

```
A' left (1)      = 1
```

```
A' right (2)     = 0
```

```
A' low (1)       = 1
```

```
A' high (2)      = 31
```

```
A' range (1)     = 1 to 4
```

```
A' length (2)    = 32
```

```
A' ascending (2) = false
```

# Attributes of Scalar Types

---

---

Attributes	Description
T'left	first (leftmost) value in T
T'right	last (rightmost) value in T
T'low	least value in T
T'high	greatest value in T

## Not available in VHDL-87:

Attributes	Description
T'ascending	<b>true</b> if T is an ascending range, <b>false</b> otherwise
T'image(x)	a string representing the value of x
T'value(s)	the value in T that is represented by s

## Attributes of Scalar Types: Examples

---

```
type index_range is range 21 downto 11;
```

```
index_range'left           = 21
```

```
index_range'right         = 11
```

```
index_range'low           = 11
```

```
index_range'high          = 21
```

```
index_range'ascending     = false
```

```
index_range'image(14)     = "14"
```

```
index_range'value("20")   = 20
```

# Attributes of Discrete Types

---

---

Attributes	Description
$T'pos(x)$	position number of $x$ in $T$
$T'val(n)$	value in $T$ at position $n$
$T'succ(x)$	value in $T$ at position one greater than position of $x$
$T'pred(x)$	value in $T$ at position one less than position of $x$
$T'leftof(x)$	value in $T$ at position one to the left of $x$
$T'rightof(x)$	value in $T$ at position one to the right of $x$

## Attributes of Discrete Types: Examples

---

```
type logic_level is (unknown, low, undriven, high);  
  
logic_level'pos(unknown)           = 0  
logic_level'val(3)                  = high  
logic_level'succ(unknown)           = low  
logic_level'pred(undriven)          = low  
logic_level'leftof(unknown)         error  
logic_level'rightof(undriven)       = high
```




## Attributes of Signals

---

- `signal_name'event` returns true if there is a *change* in a value of the signal.
- `signal_name'active` returns true if a value was assigned to the signal (even if the new value is the same as the current signal value).
- `signal_name'transaction` bit that returns true if a value was assigned to the signal (even if the new value is the same as the current signal value).
- `signal_name'last_event` returns the elapsed time since the last event that happened to the signal.
- `signal_name'last_active` returns the elapsed time since the last time that the signal was active.
- `signal_name'last_value` returns the last value that was assigned to the signal.

# Testbenches

---

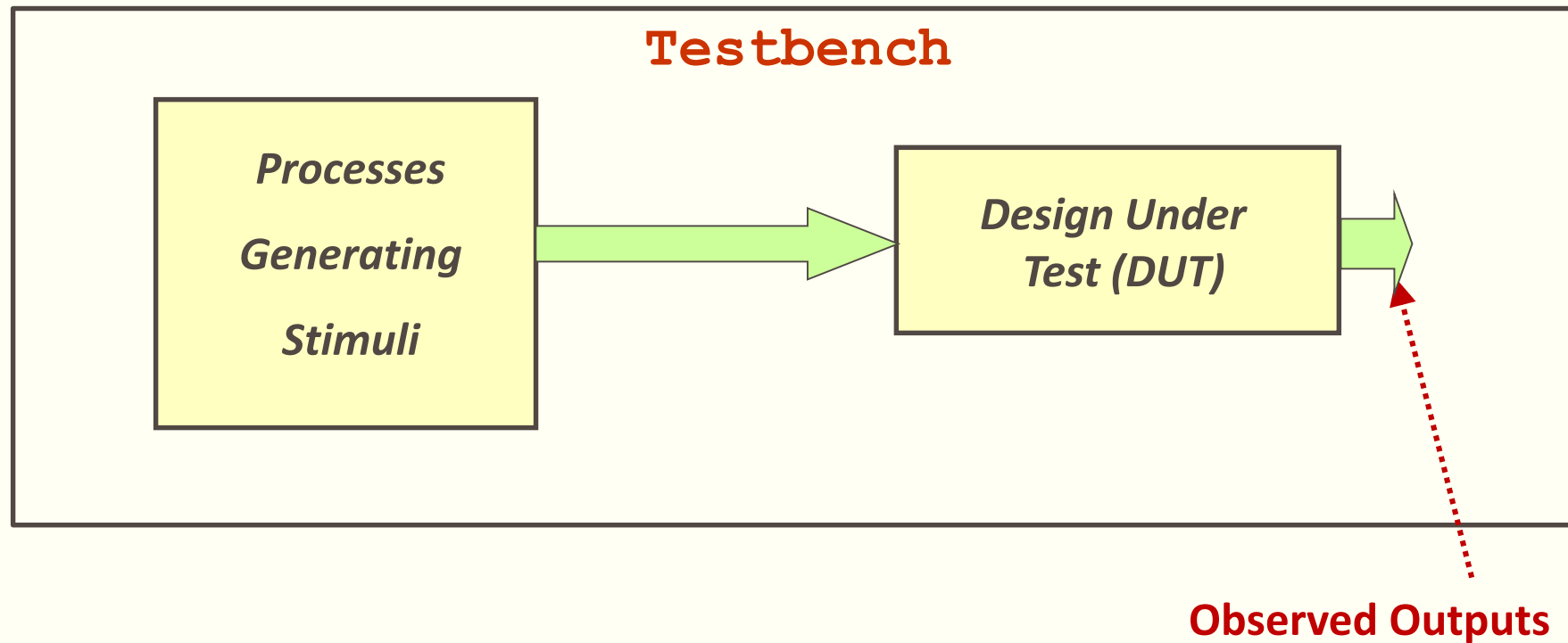

## Testbench Definition

---

- Testbench applies stimuli (drives the inputs) to the Design Under Test (DUT) and (optionally) verifies expected outputs.
- The results can be viewed in a waveform window or written to a file.
- Since Testbench is written in VHDL, it is not restricted to a single simulation tool (portability).
- The same Testbench can be easily adapted to test different implementations (i.e. different architectures) of the same design.

# Testbench Template

---

```
ENTITY tb IS
    --TB entity has no ports
END tb;

ARCHITECTURE arch_tb OF tb IS

    --Local signals and constants

    COMPONENT TestComp --All Design Under Test component declarations
        PORT ( );
    END COMPONENT;

    -----
BEGIN
    testSequence: PROCESS
        -- Input stimuli
    END PROCESS;

    DUT:TestComp PORT MAP(
        -- Instantiations of DUTs
    );
END arch_tb;
```

# Generating Selected Values

```
SIGNAL test_vector : STD_LOGIC_VECTOR(2 downto 0);

BEGIN

    .....

    testing: PROCESS
    BEGIN
        test_vector <= "000";
        WAIT FOR 10 ns;
        test_vector <= "001";
        WAIT FOR 10 ns;
        test_vector <= "010";
        WAIT FOR 10 ns;
        test_vector <= "011";
        WAIT FOR 10 ns;
        test_vector <= "100";
        WAIT FOR 10 ns;
    END PROCESS;

    .....

END behavioral;
```

## Generating all Values

---

```
SIGNAL test_vector : STD_LOGIC_VECTOR(3 downto 0) := "0000";

BEGIN
    .....

    testing: PROCESS
    BEGIN
        WAIT FOR 10 ns;
        test_vector <= test_vector + 1;
    end process TESTING;

    .....
END behavioral;
```

# Generating all Values

---

```
SIGNAL test_ab : STD_LOGIC_VECTOR(1 downto 0);
SIGNAL test_sel : STD_LOGIC_VECTOR(1 downto 0);

BEGIN
    .....
    double_loop: PROCESS
    BEGIN
        test_ab <="00";
        test_sel <="00";
        for I in 0 to 3 loop
            for J in 0 to 3 loop
                wait for 10 ns;
                test_ab <= test_ab + 1;
            end loop;
            test_sel <= test_sel + 1;
        end loop;
    END PROCESS;
    .....
END behavioral;
```

# Generating Periodic Signals

---

```
CONSTANT clk1_period : TIME := 20 ns;
CONSTANT clk2_period : TIME := 200 ns;
SIGNAL clk1 : STD_LOGIC;
SIGNAL clk2 : STD_LOGIC := '0';

BEGIN
.....
  clk1_generator: PROCESS
    clk1 <= '0';
    WAIT FOR clk1_period/2;
    clk1 <= '1';
    WAIT FOR clk1_period/2;
  END PROCESS;

  clk2 <= not clk2 after clk2_period/2;

.....
END behavioral;
```



# Generating 1 Time Signals

---

```
CONSTANT reset1_width : TIME := 100 ns;
CONSTANT reset2_width : TIME := 150 ns;
SIGNAL reset1 : STD_LOGIC;
SIGNAL reset2 : STD_LOGIC := '1';


BEGIN

    .....
    reset1_generator: PROCESS
        reset1 <= '1';
        WAIT FOR reset_width;
        reset1 <= '0';
        WAIT;
    END PROCESS;
    reset2_generator: PROCESS
        WAIT FOR reset_width;
        reset2 <= '0';
        WAIT;
    END PROCESS;

    .....
END behavioral;
```

# Structure of a Digital System

---

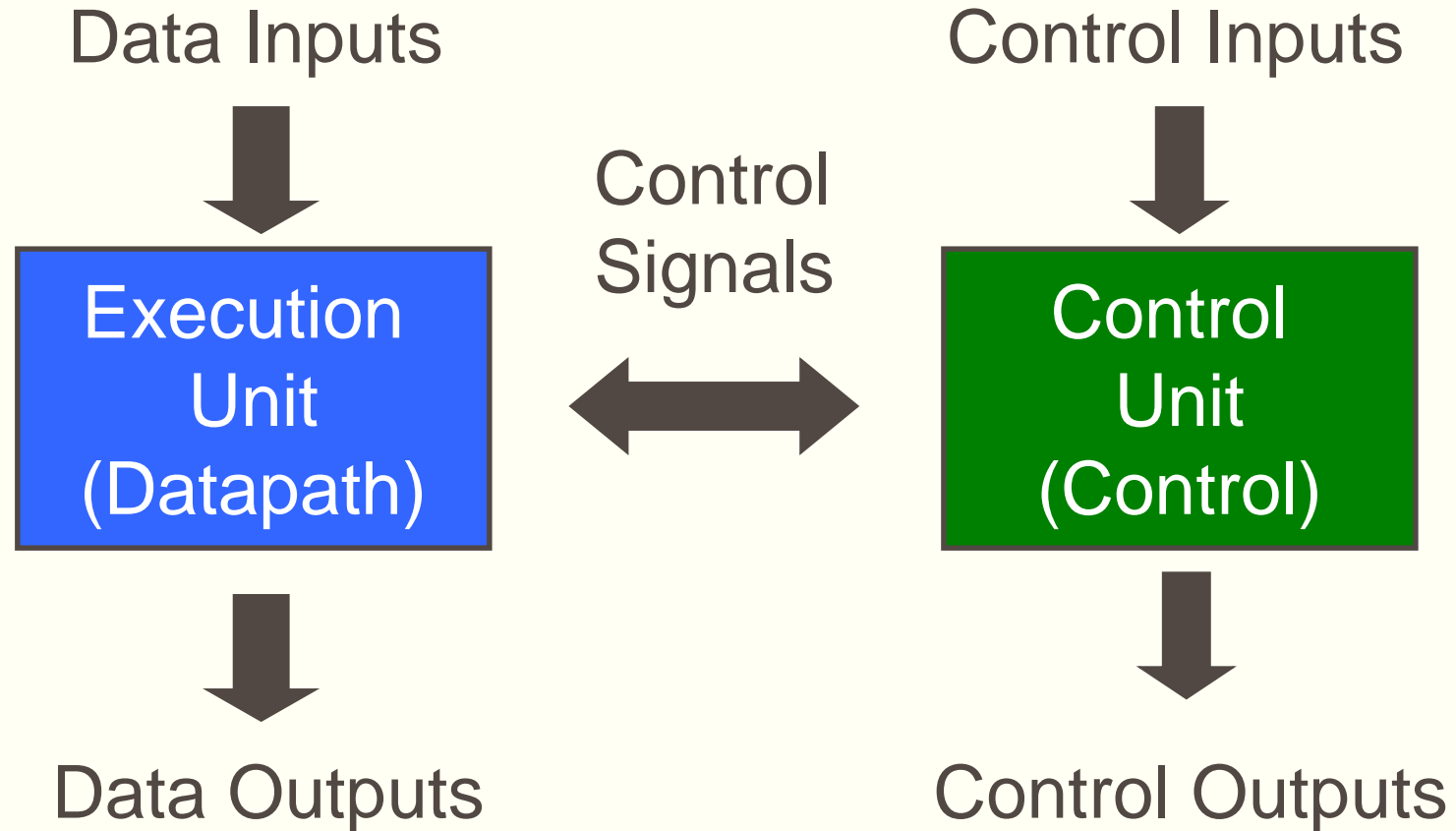

# Datapath

---

- Provides all necessary resources and interconnects among them to perform specified task
- Examples of resources
  - Adders, Multipliers, Registers, Memories, etc.

# Control


---

- Controls data movements in an operational circuit by switching multiplexers and enabling or disabling resources
- Follows some 'program' or schedule
- Often implemented as Finite State Machine (FSM) or collection of Finite State Machines
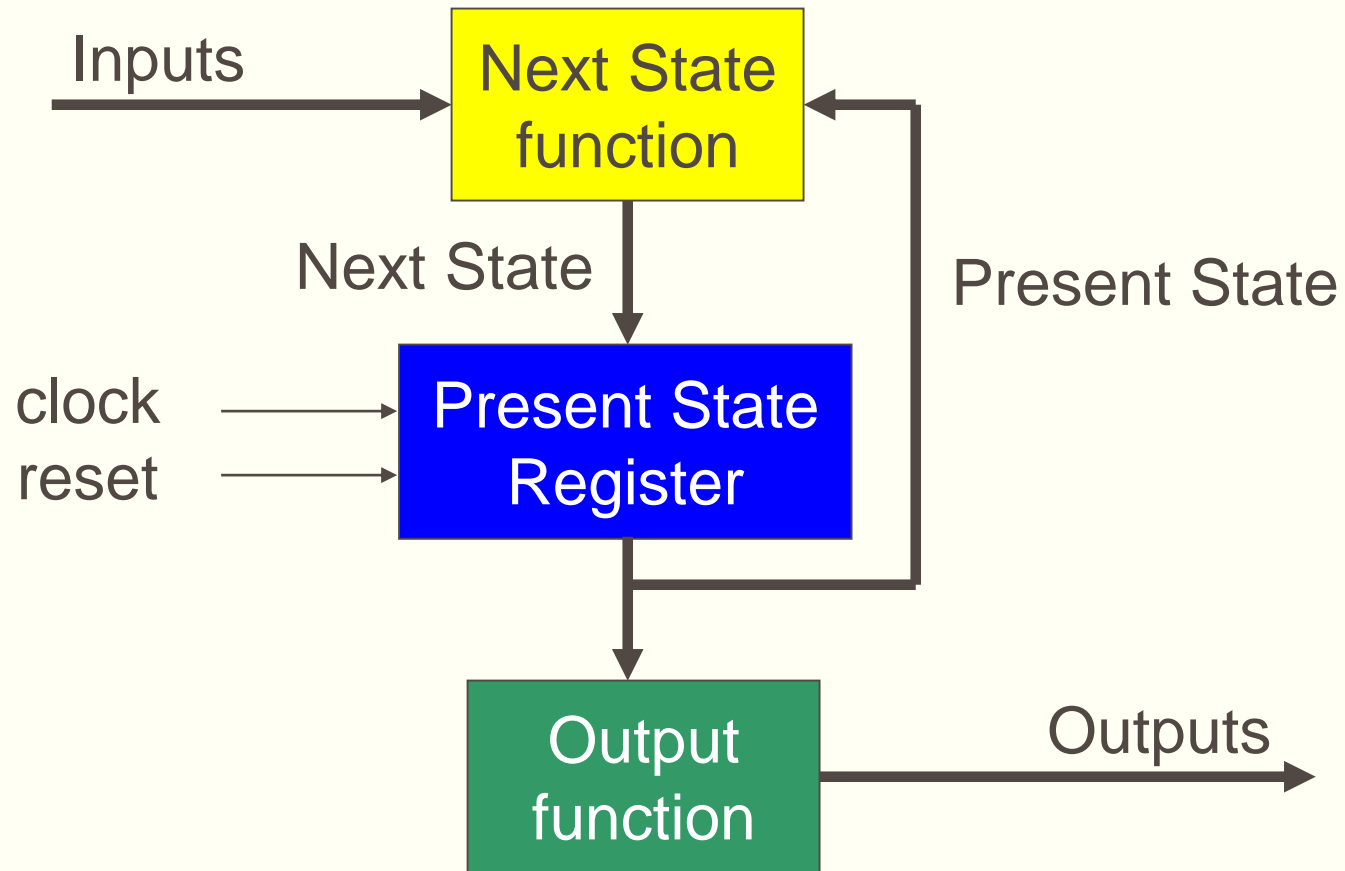
# Moore FSM

---


Output is a function of a present state only


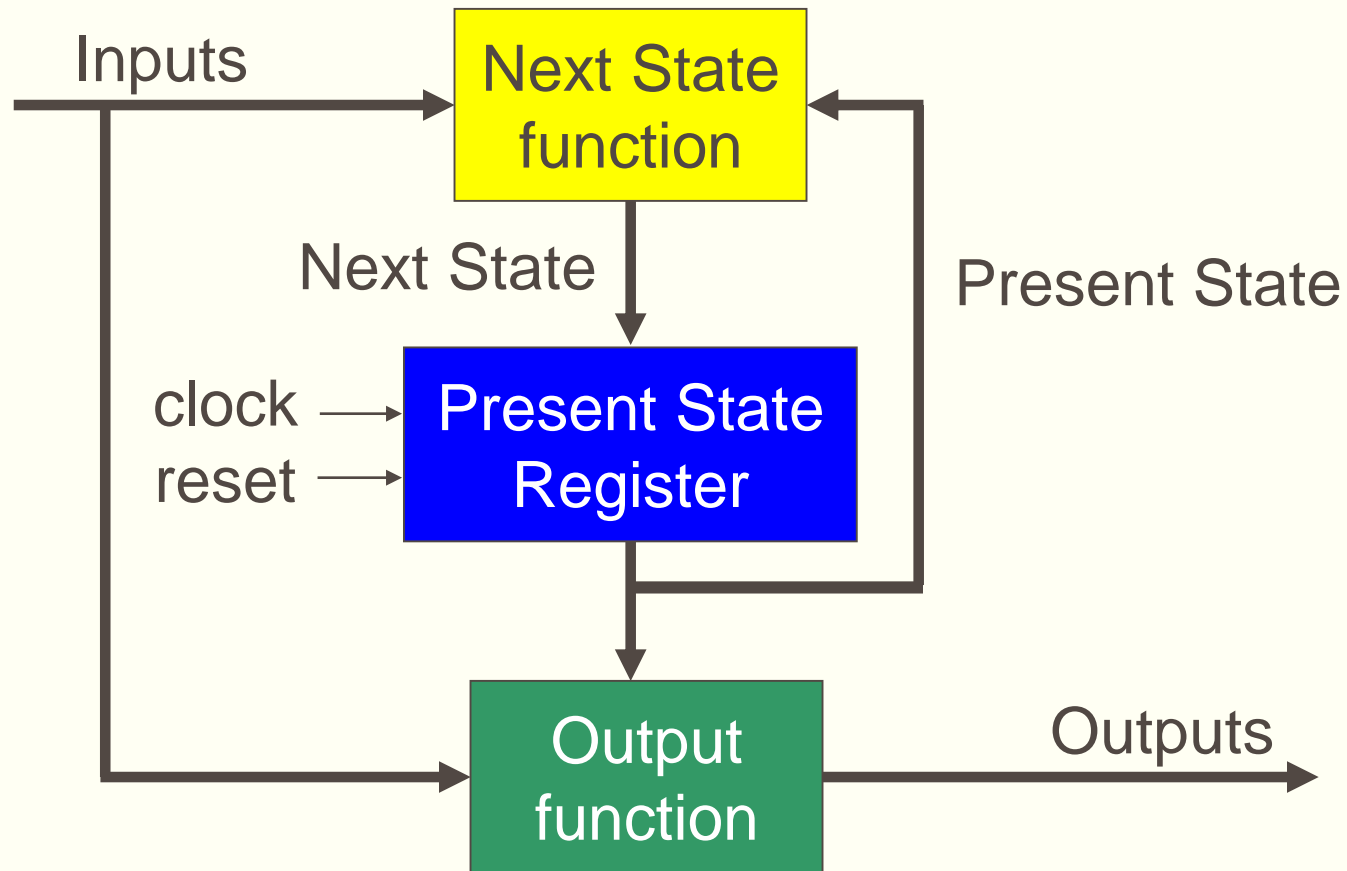
# Mealy FSM

---


Output is a function of a present state and inputs



# Moore FSM

---


---

 

# Mealy FSM

---

---

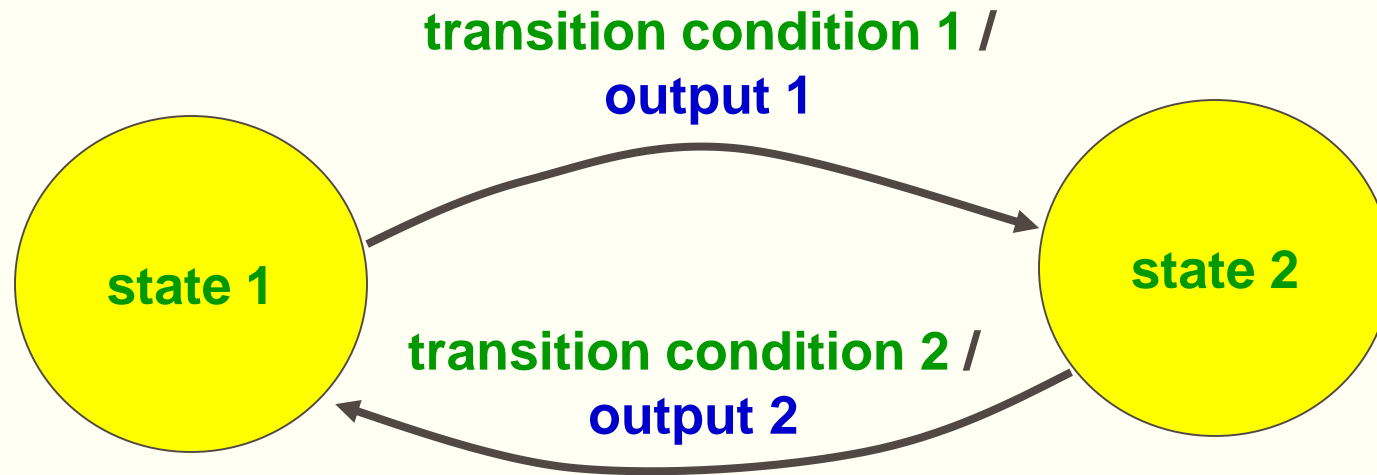



# FSMs in VHDL

---

- Finite State Machines (FSM) can be easily described with processes
- Synthesis tools understand FSM description if certain rules are followed
  - **State transitions** should be described **in a process** sensitive to *clock* and *asynchronous reset* signals **only**
  - **Outputs** described **as concurrent statements** outside the process

# Moore FSM in VHDL

---

---

```
TYPE state IS (S0, S1, S2);
SIGNAL Moore_state: state;

U_Moore: PROCESS (clock, reset)
BEGIN
    IF(reset = '1') THEN
        Moore_state <= S0;
    ELSIF (clock = '1' AND clock'event) THEN
        CASE Moore_state IS
            WHEN S0 =>
                IF input = '1' THEN
                    Moore_state <= S1;
                ELSE
                    Moore_state <= S0;
                END IF;
        END CASE;
    END IF;
```

continue...


```
        WHEN S1 =>
            IF input = '0' THEN
                Moore_state <= S2;
            ELSE
                Moore_state <= S1;
            END IF;
        WHEN S2 =>
            IF input = '0' THEN
                Moore_state <= S0;
            ELSE
                Moore_state <= S1;
            END IF;
        END CASE;
    END IF;
END PROCESS;

Output <= '1' WHEN Moore_state = S2
ELSE '0' ;
```

# State Diagram

---

Moore FSM that recognizes sequence "10"

 

# Mealy FSM in VHDL

---

```
TYPE state IS (S0, S1);
SIGNAL Mealy_state: state;

U_Mealy: PROCESS(clock, reset)
BEGIN
    IF(reset = '1') THEN
        Mealy_state <= S0;
    ELSIF (clock = '1' AND clock'event) THEN
        CASE Mealy_state IS
            WHEN S0 =>
                IF input = '1' THEN
                    Mealy_state <= S1;
                ELSE
                    Mealy_state <= S0;
                END IF;
        END CASE;
    END IF;
END PROCESS;
```


```
        WHEN S1 =>
            IF input = '0' THEN
                Mealy_state <= S0;
            ELSE
                Mealy_state <= S1;
            END IF;
        END CASE;
    END IF;
END PROCESS;

Output <= '1' WHEN (Mealy_state = S1 AND
    input = '0') ELSE '0';
```

# State Diagram

---

Mealy FSM that Recognizes Sequence "10"

 

# Basic Logic Gates

---

```
-----  
-- OR gate  
--  
-- two descriptions provided  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
-----  
entity OR_ent is  
port(  x: in std_logic;  
      y: in std_logic;  
      F: out std_logic  
);  
end OR_ent;  
-----
```

# Basic Logic Gates

---

```
architecture OR_arch of OR_ent is
begin

    process(x, y)
    begin
        -- compare to truth table
        if ((x='0') and (y='0')) then
            F <= '0';
        else
            F <= '1';
        end if;
    end process;
end OR_arch;

architecture OR_beh of OR_ent is
begin
    F <= x or y;
end OR_beh;
```

# Basic Logic Gates

---

```
-----  
-- XNOR gate  
--  
-- two descriptions provided  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
-----  
entity XNOR_ent is  
port(  x: in std_logic;  
      y: in std_logic;  
      F: out std_logic  
);  
end XNOR_ent;  
-----
```



# Basic Logic Gates

---

```
architecture behv1 of XNOR_ent is
begin
    process (x, y)
    begin
        -- compare to truth table
        if (x/=y) then
            F <= '0';
        else
            F <= '1';
        end if;
    end process;
end behv1;

architecture behv2 of XNOR_ent is
begin
    F <= x xnor y;
end behv2;
```

# Combinational Circuits

```
-----  
-- Combinational Logic Design  
-- by Weijun Zhang, 04/2001  
-- A simple example of VHDL Structure Modeling we might define  
-- two components in two separate files, in main file, we use  
-- port map statement to instantiate the mapping relationship  
-- between each components and the entire circuit.  
-----
```

```
library ieee;          -- component #1  
use ieee.std_logic_1164.all;
```

```
entity OR_GATE is  
port(X:   in std_logic;  
      Y:   in std_logic;  
      F2:  out std_logic  
);  
end OR_GATE;
```

# Combinational Circuits

---

```
architecture behv of OR_GATE is
begin
process (X,Y)
begin
    F2 <= X or Y;      -- behavior des.
end process;
end behv;
```

```
-----

library ieee;          -- component #2
use ieee.std_logic_1164.all;
```

```
entity AND_GATE is
port(
    A:      in std_logic;
    B: in std_logic;
    F1: out std_logic
);
end AND_GATE;
```

# Combinational Circuits

---

```
architecture behv of AND_GATE is
begin
  process (A,B)
  begin
    F1 <= A and B;      -- behavior des.
  end process;
end behv;

-----

library ieee;          -- top level circuit
use ieee.std_logic_1164.all;
use work.all;

entity comb_ckt is
port(input1: in std_logic;
      input2: in std_logic;
      input3: in std_logic;
      output: out std_logic
);
end comb_ckt;
```

# Combinational Circuits

---

```
architecture struct of comb_ckt is component AND_GATE is
port( A:  in std_logic;
      B:  in std_logic;
      F1: out std_logic
);
end component;

component OR_GATE is                                -- as entity of OR_GATE
port( X: in std_logic;
      Y: in std_logic;
      F2: out std_logic
);
end component;

signal wire: std_logic;                            -- signal just like wire
```

# Combinational Circuits

---

---

```
begin
```

```
    -- use sign "=>" to clarify the pin mapping
```

```
    Gate1: AND_GATE port map (A=>input1, B=>input2, F1=>wire);
```

```
    Gate2: OR_GATE port map (X=>wire, Y=>input3, F2=>output);
```

```
end struct;
```

---

# Tri-state Driver

---

```
-----  
-- VHDL model for tri state driver by Weijun Zhang, 05/2001  
-- this friver often used to control system outputs  
-----
```

```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity tristate_dr is  
port( d_in: in std_logic_vector(7 downto 0);  
      en: in std_logic;  
      d_out: out std_logic_vector(7 downto 0)  
);  
end tristate_dr;
```

## Tri-state Driver

---

```
architecture behavior of tristate_dr is
begin

    process (d_in, en)
    begin
        if en='1' then
            d_out <= d_in;
        else
            -- array can be created simply by using vector
            d_out <= "ZZZZZZZZ";
        end if;
    end process;

end behavior;
```



# Multiplexor

---

---

```
-----  
-- VHDL code for 4:1 multiplexor -- by Weijun Zhang, 04/2001  
-- Multiplexor is a device to select different inputs to  
  outputs. We use 3 bits vector to describe its I/O ports  
-----
```

```
library ieee;  
use ieee.std_logic_1164.all;  
-----
```

```
entity Mux is  
port( I3: in std_logic_vector(2 downto 0);  
      I2: in std_logic_vector(2 downto 0);  
      I1: in std_logic_vector(2 downto 0);  
      I0: in std_logic_vector(2 downto 0);  
      S: in std_logic_vector(1 downto 0);  
      O: out std_logic_vector(2 downto 0)  
);  
end Mux;
```

# Multiplexor

---

```
architecture behv1 of Mux is
begin
    process (I3, I2, I1, I0, S)
    begin
        -- use case statement
        case S is
            when "00" =>    O <= I0;
            when "01" =>    O <= I1;
            when "10" =>    O <= I2;
            when "11" =>    O <= I3;
            when others => O <= "ZZZ";
        end case;
    end process;
end behv1;
```

# Multiplexor

---

```
architecture behv2 of Mux is
begin
    -- use when.. else statement
    O <= I0 when S="00" else
        I1 when S="01" else
        I2 when S="10" else
        I3 when S="11" else
        "ZZZ";
end behv2;
```

# Decoder

---

```
-----  
-- 2:4 Decoder  
-- by Weijun Zhang, 04/2001  
-- decoder is a kind of inverse process of multiplexor  
-----
```

```
library ieee;  
use ieee.std_logic_1164.all;  
-----  
entity DECODER is  
port( I: in std_logic_vector(1 downto 0);  
      O: out std_logic_vector(3 downto 0)  
);  
end DECODER;  
-----
```

# Decoder

---

```
architecture behv of DECODER is
begin
  -- process statement
  process (I)
  begin
    -- use case statement
    case I is
      when "00" => O <= "0001";
      when "01" => O <= "0010";
      when "10" => O <= "0100";
      when "11" => O <= "1000";
      when others => O <= "XXXX";
    end case;
  end process;
end behv;
```

# Decoder

---

```
architecture when_else of DECODER is
begin
    -- use when..else statement
    O <= "0001" when I = "00" else
    "0010" when I = "01" else
    "0100" when I = "10" else
    "1000" when I = "11" else
    "XXXX";
end when_else;
```

# Adder

---

---

```
-----  
-- VHDL code for n-bit adder by Weujun Zhang, 04/2001  
-- function of adder: A plus B to get n-bit sum and 1 bit carry  
-- we may use generic statement to set the parameter n of the adder.  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_arith.all;  
use ieee.std_logic_unsigned.all;  
-----  
entity ADDER is  
generic(n: natural :=2);  
port(A: in std_logic_vector(n-1 downto 0);  
      B: in std_logic_vector(n-1 downto 0);  
      carry: out std_logic;  
      sum: out std_logic_vector(n-1 downto 0)  
);  
end ADDER;
```

# Adder

---

```
architecture behv of ADDER is
    -- define a temporary signal to store the result

    signal result: std_logic_vector(n downto 0);

begin
    -- the 3rd bit should be carry

    result <= ('0' & A) + ('0' & B);
    sum <= result(n-1 downto 0);
    carry <= result(n);

end behv;
```



# Comparator

---

```
-----  
-- n-bit Comparator by Weijun Zhang, 04/2001  
-- this simple comparator has two n-bit inputs &  
-- three 1-bit outputs  
-----
```

```
library ieee;  
use ieee.std_logic_1164.all;  
-----
```

```
entity Comparator is  
generic(n: natural :=2);  
port(A: in std_logic_vector(n-1 downto 0);  
      B: in std_logic_vector(n-1 downto 0);  
      less: out std_logic;  
      equal: out std_logic;  
      greater: out std_logic  
);  
end Comparator;
```

# Comparator

---

```
architecture behv of Comparator is
begin
  process (A,B)
  begin
    if (A<B) then
      less <= '1';
      equal <= '0';
      greater <= '0';
    elsif (A=B) then
      less <= '0';
      equal <= '1';
      greater <= '0';
    else
      less <= '0';
      equal <= '0';
      greater <= '1';
    end if;
  end process;
end behv;
```

# ALU

---

---

```
-----  
-- Simple ALU Module  
-- by Weijun Zhang, 04/2001  
--  
-- ALU stands for arithmetic logic unit.  
-- It perform multiple operations according to  
-- the control bits.  
-- we use 2's complement subtraction in this example  
-- two 2-bit inputs & carry-bit ignored  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_unsigned.all;  
use ieee.std_logic_arith.all;  
-----
```

# ALU

---

---

```
entity ALU is
```

```
port( A: in std_logic_vector(1 downto 0);  
      B: in std_logic_vector(1 downto 0);  
      Sel: in std_logic_vector(1 downto 0);  
      Res: out std_logic_vector(1 downto 0)  
);
```

```
end ALU;
```

---

# ALU

```
architecture behv of ALU is
begin
    process (A,B,Sel)
    begin
        -- use case statement to achieve different operations of ALU
        case Sel is
            when "00" =>
                Res <= A + B;
            when "01" =>
                Res <= A + (not B) + 1;
            when "10" =>
                Res <= A and B;
            when "11" =>
                Res <= A or B;
            when others =>
                Res <= "XX";
        end case;
    end process;
end behv;
```

---

# Multiplier

---

```
-----  
-- Example of doing multiplication showing  
-- (1) how to use variable with in process  
-- (2) how to use for loop statement  
-- (3) algorithm of multiplication  
--  
-- by Weijun Zhang, 05/2001  
-----
```

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_arith.all;  
use ieee.std_logic_unsigned.all;  
  
-- two 4-bit inputs and one 8-bit outputs  
entity multiplier is  
port(num1, num2: in std_logic_vector(1 downto 0);  
      product: out std_logic_vector(3 downto 0)  
);  
end multiplier;
```

# Multiplier

---

---

```
architecture behv of multiplier is
begin
process(num1, num2)
    variable num1_reg: std_logic_vector(2 downto 0);
    variable product_reg: std_logic_vector(5 downto 0);
begin
    num1_reg := '0' & num1;
    product_reg := "0000" & num2;
    -- use variables doing computation
    -- algorithm is to repeat shifting/adding
    for i in 1 to 3 loop
        if product_reg(0)='1' then
            product_reg(5 downto 3) := product_reg(5 downto 3) + num1_reg(2 downto 0);
        end if;
        product_reg(5 downto 0) := '0' & product_reg(5 downto 1);
    end loop;
    -- assign the result of computation back to output signal
    product <= product_reg(3 downto 0);
end process;
end behv;
```

# Simple Latch

---

```
-----  
-- Simple D Latch  
-- by Weijun Zhang, 04/2001  
-- latch is simply controlled by enable bit  
-- but has nothing to do with clock signal  
-- notice this difference from flip-flops  
-----  
library ieee ;  
use ieee.std_logic_1164.all;  
-----  
entity D_latch is  
port(data_in: in std_logic;  
      enable:      in std_logic;  
      data_out:  out std_logic  
);  
end D_latch;  
-----
```



# Simple Latch

---

```
architecture behv of D_latch is
begin

    -- compare this to D flipflop

    process(data_in, enable)
    begin
        if (enable='1') then
            -- no clock signal here
            data_out <= data_in;
        end if;
    end process;

end behv;
```

---

# D Flip-flop

---

```
-----  
-- D Flip-Flop  
-- by Weijun Zhang, 04/2001  
--  
-- Flip-flop is the basic component in  
-- sequential logic design  
-- we assign input signal to the output  
-- at the clock rising edge  
-----  
  
library ieee ;  
use ieee.std_logic_1164.all;  
use work.all;  
-----  
  
entity dff is  
port( data_in: in std_logic;  
      clock: in std_logic;  
      data_out: out std_logic  
);  
end dff;
```

# D Flip-flop

---

---

```
-----  
architecture behv of dff is  
begin  
  
    process(data_in, clock)  
    begin  
  
        -- clock rising edge  
  
        if (clock='1' and clock'event) then  
            data_out <= data_in;  
        end if;  
  
    end process;  
  
end behv;  
-----
```

# JK Flip-flop

---

```
-----  
-- JK Flip-Flop with reset  
-- by Weijun Zhang, 04/2001  
--  
-- the description of JK Flip-Flop is based  
-- on functional truth table  
-- concurrent statement and signal assignment  
-- are using in this example  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
-----  
  
entity JK_FF is  
port ( clock: in std_logic;  
       J, K: in std_logic;  
       reset: in std_logic;  
       Q, Qbar: out std_logic  
);  
end JK_FF;
```

# JK Flip-flop

---

---

-----

```
architecture behv of JK_FF is
```

```
-- define the useful signals here
```

```
signal state: std_logic;
```

```
signal input: std_logic_vector(1 downto 0);
```

# JK Flip-flop

---

```
begin
  -- combine inputs into vector
  input <= J & K;
  p: process(clock, reset) is
  begin
    if (reset='1') then
      state <= '0';
    elsif (rising_edge(clock)) then
      -- compare to the truth table
      case (input) is
        when "11" => state <= not state;
        when "10" => state <= '1';
        when "01" => state <= '0';
        when others => null;
      end case;
    end if;
  end process;
```

# JK Flip-flop

---

---

```
-- concurrent statements  
Q <= state;  
Qbar <= not state;  
  
end behv;
```

---

# Register

---

```
-----  
-- n-bit Register  
-- by Weijun Zhang, 04/2001  
-----  
library ieee ;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_unsigned.all;  
-----  
  
entity reg is  
  
generic(n: natural :=2);  
port( I: in std_logic_vector(n-1 downto 0);  
      clock: in std_logic;  
      load: in std_logic;  
      clear: in std_logic;  
      Q: out std_logic_vector(n-1 downto 0)  
);  
end reg;
```



# Register

---

```
-----  
architecture behv of reg is  
    signal Q_tmp: std_logic_vector(n-1 downto 0);  
begin  
    process(I, clock, load, clear)  
    begin  
        if clear = '0' then          -- use 'range in signal assignment  
            Q_tmp <= (Q_tmp'range => '0');  
        elsif (clock='1' and clock'event) then  
            if load = '1' then  
                Q_tmp <= I;  
            end if;  
        end if;  
    end process;  
    -- concurrent statement  
    Q <= Q_tmp;  
end behv;  
-----
```

# Shift Register

---

```
-----  
-- 3-bit Shift-Register/Shifter  
-- by Weijun Zhang, 04/2001  
-- reset is ignored  
-----
```

```
library ieee ;  
use ieee.std_logic_1164.all;  
-----
```

```
entity shift_reg is  
port(  I: in std_logic;  
       clock: in std_logic;  
       shift: in std_logic;  
       Q: out std_logic  
);  
end shift_reg;  
-----
```

# Shift Register

---

```
architecture behv of shift_reg is
    -- initialize the declared signal
    signal S: std_logic_vector(2 downto 0) := "111";

begin
    process(I, clock, shift, S)
    begin        -- everything happens upon the clock changing
        if clock'event and clock='1' then
            if shift = '1' then
                S <= I & S(2 downto 1);
            end if;
        end if;
    end process;

    -- concurrent assignment
    Q <= S(0);

end behv;
```

---

# Counter

---

```
-----  
-- VHDL code for n-bit counter by Weijun Zhang, 04/2001  
-- this is the behavior description of n-bit counter  
-- another way can be used is FSM model.  
-----
```

```
library ieee ;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_unsigned.all;  
-----  
entity counter is  
  
generic(n: natural :=2);  
port(clock: in std_logic;  
      clear: in std_logic;  
      count: in std_logic;  
      Q: out std_logic_vector(n-1 downto 0)  
);  
end counter;  
-----
```

# Counter

---

```
architecture behv of counter is
    signal Pre_Q: std_logic_vector(n-1 downto 0);

begin
    -- behavior describe the counter
    process(clock, count, clear)
    begin
        if clear = '1' then
            Pre_Q <= Pre_Q - Pre_Q;
        elsif (clock='1' and clock'event) then
            if count = '1' then
                Pre_Q <= Pre_Q + 1;
            end if;
        end if;
    end process;
    -- concurrent assignment statement
    Q <= Pre_Q;

end behv;
```

---

# FSM

---

```
-----  
-- VHDL FSM (Finite State Machine) modeling  
-- by Weijun Zhang, 04/2001  
--  
-- FSM model consists of two concurrent processes state_reg  
-- and comb_logic we use case statement to describe the  
-- state transistion. All the inputs and signals are  
-- put into the process sensitive list.  
-----  
library ieee ;  
use ieee.std_logic_1164.all;  
-----  
entity seq_design is  
port(a:          in std_logic;  
     clock:      in std_logic;  
     reset:      in std_logic;  
     x:  out std_logic  
);  
end seq_design;  
-----
```

# FSM

---

```
architecture FSM of seq_design is
-- define the states of FSM model

type state_type is (S0, S1, S2, S3);
signal next_state, current_state: state_type;

begin
  -- cocurrent process#1: state registers
  state_reg: process(clock, reset)
  begin

    if (reset='1') then
      current_state <= S0;
    elsif (clock'event and clock='1') then
      current_state <= next_state;
    end if;

  end process;
end process;
```

# FSM

---

```
-- cocurrent process#2: combinational logic
comb_logic: process(current_state, a)
begin
  -- use case statement to show the state transition
  case current_state is
    when S0 => x <= '0';
      if a='0' then next_state <= S0;
      elsif a='1' then next_state <= S1;
      end if;

    when S1 => x <= '0';
      if a='0' then next_state <= S1;
      elsif a='1' then next_state <= S2;
      end if;
```



# FSM

---

---

```
when S2 => x <= '0';
    if a='0' then next_state <= S2;
    elsif a='1' then next_state <= S3;
    end if;

when S3 => x <= '1';
    if a='0' then next_state <= S3;
    elsif a='1' then next_state <= S0;
    end if;

when others => x <= '0';
    next_state <= S0;
end case;
end process;
end FSM;
```

---

# RAM

---

```
-----  
-- a simple 4*4 RAM module by Weijun Zhang  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_arith.all;  
use ieee.std_logic_unsigned.all;  
-----  
entity SRAM is  
generic( width: integer:=4; depth: integer:=4; addr: integer:=2);  
port(   Clock: in std_logic;  
        Enable: in std_logic;  
        Read: in std_logic;  
        Write: in std_logic;  
        Read_Addr: in std_logic_vector(addr-1 downto 0);  
        Write_Addr: in std_logic_vector(addr-1 downto 0);  
        Data_in: in std_logic_vector(width-1 downto 0);  
        Data_out: out std_logic_vector(width-1 downto 0)  
);  
end SRAM;
```

# RAM

---

```
architecture behav of SRAM is
-- use array to define the bunch of internal temporary signals
type ram_type is array (0 to depth-1) of std_logic_vector(width-1 downto 0);
signal tmp_ram: ram_type;
begin
    -- Read Functional Section
    process(Clock, Read)
    begin
        if (Clock'event and Clock='1') then
            if Enable='1' then
                if Read='1' then
                    -- builtin function conv_integer change the type
                    -- from std_logic_vector to integer
                    Data_out <= tmp_ram(conv_integer(Read_Addr));
                else
                    Data_out <= (Data_out'range => 'Z');
                end if;
            end if;
        end if;
    end process;
end architecture;
```

# RAM

---

---

```
-- Write Functional Section
process(Clock, Write)
begin
    if (Clock'event and Clock='1') then
        if Enable='1' then
            if Write='1' then
                tmp_ram(conv_integer(Write_Addr)) <= Data_in;
            end if;
        end if;
    end if;
end process;
```

```
end behav;
```

---

# ROM

---

```
-----  
-- 32*8 ROM module by Weijun Zhang, 04/2001  
-- ROM model has predefined content for read only purpose  
-----
```

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_arith.all;  
use ieee.std_logic_unsigned.all;  
  
entity ROM is  
port(Clock: in std_logic;  
      Reset: in std_logic;  
      Enable: in std_logic;  
      Read: in std_logic;  
      Address: in std_logic_vector(4 downto 0);  
      Data_out: out std_logic_vector(7 downto 0)  
);  
end ROM;
```

```
-----
```

# ROM

```
architecture Behav of ROM is type ROM_Array is array (0 to 31)
  of std_logic_vector(7 downto 0);

  constant Content: ROM_Array := (
    0 => "00000001",      -- Suppose ROM has
    1 => "00000010",      -- prestored value
    2 => "00000011",      -- like this table
    3 => "00000100",      --
    4 => "00000101",      --
    5 => "00000110",      --
    6 => "00000111",      --
    7 => "00001000",      --
    8 => "00001001",      --
    9 => "00001010",      --
    10 => "00001011",     --
    11 => "00001100",     --
    12 => "00001101",     --
    13 => "00001110",     --
    14 => "00001111",     --
    OTHERS => "11111111"  --
  );
```

# ROM

---

---

```
begin
  process(Clock, Reset, Read, Address)
  begin
    if( Reset = '1' ) then
      Data_out <= "ZZZZZZZZ";
    elsif( Clock'event and Clock = '1' ) then
      if Enable = '1' then
        if( Read = '1' ) then
          Data_out <= Content(conv_integer(Address));
        else
          Data_out <= "ZZZZZZZZ";
        end if;
      end if;
    end if;
  end process;
end Behav;
```

---

## GCD Calculator - Behavioral

---

```
-----  
-- Behavior Design of GCD calculator  
-- by Weijun Zhang, 05/2001  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_arith.all;  
use work.all;  
-----  
entity gcd1 is  
port(   Data_X:      in unsigned(3 downto 0);  
       Data_Y:      in unsigned(3 downto 0);  
       Data_out:    out unsigned(3 downto 0)  
);  
end gcd1;
```



# GCD Calculator - Behavioral

---

```
architecture behv of gcd1 is
begin
  process(Data_X, Data_Y)
  variable tmp_X, tmp_Y: unsigned(3 downto 0);
  begin
    tmp_X := Data_X;
    tmp_Y := Data_Y;
    for i in 0 to 15 loop
      if (tmp_X/=tmp_Y) then
        if (tmp_X < tmp_Y) then
          tmp_Y := tmp_Y - tmp_X;
        else
          tmp_X := tmp_X - tmp_Y;
        end if;
      else
        Data_out <= tmp_X;
      end if;
    end loop;
  end process;
end behv;
```

---

# GCD Calculator - FSM D

---

---

```
-----  
-- GCD design using FSM D by Weijun Zhang, 04/2001  
-- GCD algorithm behavior modeling (GCD.vhd)  
-- the calculator has two 4-bit inputs and one output  
-- NOTE: idle state required to obtain the correct synthesis results  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_arith.all;  
use work.all;  
-----  
entity gcd is  
port (clk: in std_logic;  
      rst: in std_logic;  
      go_i: in std_logic;  
      x_i: in unsigned(3 downto 0);  
      y_i: in unsigned(3 downto 0);  
      d_o: out unsigned(3 downto 0)  
);  
end gcd;
```

# GCD Calculator - FSM D

```
architecture FSM D of gcd is
begin
  process(rst, clk)
    -- define states using variable
    type S_Type is (ST0, ST1, ST2);
    variable State: S_Type := ST0 ;
    variable Data_X, Data_Y: unsigned(3 downto 0);
  begin
    if (rst='1') then      -- initialization
      d_o <= "0000";
      State := ST0;
    elsif (clk'event and clk='1') then
      case State is
        when ST0 =>      -- starting
          if (go_i='1') then
            Data_X := x_i;
            Data_Y := y_i;
            State := ST1;
          else
            State := ST0;
          end if;
        -- other states
      end case;
    end if;
  end process;
end architecture;
```

## GCD Calculator - FSMD

```
when ST1 => State := ST2;           -- idle state
when ST2 =>                           -- computation
    if (Data_X/=Data_Y) then
        if (Data_X<Data_Y) then
            Data_Y := Data_Y - Data_X;
        else
            Data_X := Data_X - Data_Y;
        end if;
        State := ST1;
    else
        d_o <=Data_X;                -- done
        State := ST0;
    end if;
when others =>                         -- go back
    d_o <= "ZZZZ";
    State := ST0;
end case;
end if;
end process;
end FSMD;
```

## GCD Calculator – FSM+D

---

---

```
-----  
-- GCD CALCULATOR by Weijun Zhang, 04/2001  
-- we can put all the components in one document (gcd2.vhd)  
-- or put them in separate files  
-- this is the example of RT level modeling (FSM + DataPath)  
-- the code is synthesized by Synopsys design compiler  
-----  
-- Component: MULTIPLEXOR -----  
library IEEE;  
use IEEE.std_logic_1164.all;  
use IEEE.std_logic_arith.all;  
use IEEE.std_logic_unsigned.all;  
  
entity mux is  
    port(rst, sLine: in std_logic;  
         load, result: in std_logic_vector( 3 downto 0 );  
         output: out std_logic_vector( 3 downto 0 )  
    );  
end mux;
```

## GCD Calculator – FSM+D

---

```
architecture mux_arc of mux is
begin
  process( rst, sLine, load, result )
  begin
    if( rst = '1' ) then
      output <= "0000";           -- do nothing
    elsif sLine = '0' then
      output <= load;            -- load inputs
    else
      output <= result;         -- load results
    end if;
  end process;
end mux_arc;
```

## GCD Calculator – FSM+D

---

```
-- Component: COMPARATOR -----  
  
library IEEE;  
use IEEE.std_logic_1164.all;  
use IEEE.std_logic_arith.all;  
use IEEE.std_logic_unsigned.all;  
  
entity comparator is  
    port( rst: in std_logic;  
          x, y: in std_logic_vector( 3 downto 0 );  
          output: out std_logic_vector( 1 downto 0 )  
        );  
end comparator;
```

## GCD Calculator – FSM+D

---

```
architecture comparator_arc of comparator is
begin
    process( x, y, rst )
    begin
        if( rst = '1' ) then
            output <= "00";           -- do nothing
        elsif( x > y ) then
            output <= "10";           -- if x greater
        elsif( x < y ) then
            output <= "01";           -- if y greater
        else
            output <= "11";           -- if equivalence
        end if;
    end process;
end comparator_arc;
```



## GCD Calculator – FSM+D

---

---

```
-- Component: SUBTRACTOR -----  
  
library IEEE;  
use IEEE.std_logic_1164.all;  
use IEEE.std_logic_arith.all;  
use IEEE.std_logic_unsigned.all;  
  
entity subtractor is  
    port( rst: in std_logic;  
          cmd: in std_logic_vector( 1 downto 0 );  
          x, y: in std_logic_vector( 3 downto 0 );  
          xout, yout: out std_logic_vector( 3 downto 0 )  
        );  
end subtractor;
```

## GCD Calculator – FSM+D

```
architecture subtractor_arc of subtractor is
begin
  process( rst, cmd, x, y )
  begin
    if( rst = '1' or cmd = "00" ) then          -- not active
      xout <= "0000";
      yout <= "0000";
    elsif( cmd = "10" ) then                    -- x is greater
      xout <= ( x - y );
      yout <= y;
    elsif( cmd = "01" ) then                    -- y is greater
      xout <= x;
      yout <= ( y - x );
    else                                         -- x and y are equal
      xout <= x;
      yout <= y;
    end if;
  end process;
end subtractor_arc;
```

## GCD Calculator – FSM+D

---

---

```
-- Component: REGISTER -----  
  
library IEEE;  
use IEEE.std_logic_1164.all;  
use IEEE.std_logic_arith.all;  
use IEEE.std_logic_unsigned.all;  
  
entity regis is  
    port( rst, clk, load: in std_logic;  
          input: in std_logic_vector( 3 downto 0 );  
          output: out std_logic_vector( 3 downto 0 )  
    );  
end regis;
```

## GCD Calculator – FSM+D

---

```
architecture regis_arc of regis is
begin
    process( rst, clk, load, input )
    begin
        if( rst = '1' ) then
            output <= "0000";
        elsif( clk'event and clk = '1') then
            if( load = '1' ) then
                output <= input;
            end if;
        end if;
    end process;
end regis_arc;
```

## GCD Calculator – FSM+D

---

```
-- component: FSM controller -----  
  
library IEEE;  
use IEEE.std_logic_1164.all;  
use IEEE.std_logic_arith.all;  
use IEEE.std_logic_unsigned.all;  
  
entity fsm is  
    port( rst, clk, proceed: in std_logic;  
          comparison: in std_logic_vector( 1 downto 0 );  
          enable, xsel, ysel, xld, yld: out std_logic  
        );  
end fsm;
```

## GCD Calculator – FSM+D

---

```
architecture fsm_arc of fsm is
    type states is ( init, s0, s1, s2, s3, s4, s5 );
    signal nState, cState: states;

begin
    process( rst, clk )
    begin
        if( rst = '1' ) then
            cState <= init;
        elsif( clk'event and clk = '1' ) then
            cState <= nState;
        end if;
    end process;
end
```

## GCD Calculator – FSM+D

---

```
process( proceed, comparison, cState )
begin
  case cState is
    when init =>
      if( proceed = '0' ) then nState <= init;
      else nState <= s0;
      end if;

    when s0 => enable <= '0';
      xsel <= '0';
      ysel <= '0';
      xld <= '0';
      yld <= '0';
      nState <= s1;

    when s1 => enable <= '0';
      xsel <= '0';
      ysel <= '0';
      xld <= '1';
      yld <= '1';
      nState <= s2;
```

## GCD Calculator – FSM+D

---

```
when s2 => xld <= '0';
  yld <= '0';
  if( comparison = "10" ) then nState <= s3;
  elsif( comparison = "01" ) then nState <= s4;
  elsif( comparison = "11" ) then nState <= s5;
end if;
when s3 => enable <= '0';
  xsel <= '1';
  ysel <= '0';
  xld <= '1';
  yld <= '0';
  nState <= s2;
when s4 => enable <= '0';
  xsel <= '0';
  ysel <= '1';
  xld <= '0';
  yld <= '1';
  nState <= s2;
```



## GCD Calculator – FSM+D

---

```
    when s5 => enable <= '1';
        xsel <= '1';
        ysel <= '1';
        xld <= '1';
        yld <= '1';
        nState <= s0;

    when others => nState <= s0;
end case;
end process;
end fsm_arc;
```

# GCD Calculator – FSM+D

---

---

```
-----  
-- GCD Calculator: top level design using structural modeling  
-- FSM + Datapath (mux, registers, subtractor and comparator)  
-----
```

```
library IEEE;  
use IEEE.std_logic_1164.all;  
use IEEE.std_logic_arith.all;  
use IEEE.std_logic_unsigned.all;  
use work.all;  
  
entity gcd is  
    port( rst, clk, go_i: in std_logic;  
          x_i, y_i: in std_logic_vector( 3 downto 0 );  
          d_o: out std_logic_vector( 3 downto 0 )  
    );  
end gcd;
```

## GCD Calculator – FSM+D

---

```
architecture gcd_arc of gcd is
  component fsm is
  port( rst, clk, proceed: in std_logic;
        comparison: in std_logic_vector( 1 downto 0 );
  enable, xsel, ysel, xld, yld: out std_logic
    );
  end component;

  component mux is
  port( rst, sLine: in std_logic;
        load, result: in std_logic_vector( 3 downto 0 );
        output: out std_logic_vector( 3 downto 0 )
    );
  end component;

  component comparator is
  port( rst: in std_logic;
        x, y: in std_logic_vector( 3 downto 0 );
        output: out std_logic_vector( 1 downto 0 )
    );
  end component;
```

## GCD Calculator – FSM+D

---

```
component subtractor is
  port( rst: in std_logic;
        cmd: in std_logic_vector( 1 downto 0 );
        x, y: in std_logic_vector( 3 downto 0 );
        xout, yout: out std_logic_vector( 3 downto 0 )
        );
end component;

component regis is
  port( rst, clk, load: in std_logic;
        input: in std_logic_vector( 3 downto 0 );
        output: out std_logic_vector( 3 downto 0 )
        );
end component;

signal xld, yld, xsel, ysel, enable: std_logic;
signal comparison: std_logic_vector( 1 downto 0 );
signal result: std_logic_vector( 3 downto 0 );

signal xsub, ysub, xmux, ymux, xreg, yreg: std_logic_vector( 3 downto 0 );
```

## GCD Calculator – FSM+D

---

---

```
begin
  -- doing structure modeling here
  -- FSM controller
  TOFSM: fsm port map(      rst, clk, go_i, comparison,
                        enable, xsel, ysel, xld, yld );
  -- Datapath
  X_MUX:  mux port map( rst, xsel, x_i, xsub, xmux );
  Y_MUX:  mux port map( rst, ysel, y_i, ysub, ymux );
  X_REG:  regis port map( rst, clk, xld, xmux, xreg );
  Y_REG:  regis port map( rst, clk, yld, ymux, yreg );
  U_COMP: comparator port map( rst, xreg, yreg, comparison );
  X_SUB:  subtractor port map( rst, comparison, xreg, yreg, xsub, ysub );
  OUT_REG: regis port map( rst, clk, enable, xsub, result );

  d_o <= result;
end gcd_arc;
```

# FIR Filter

---

```
-----  
-- FIR Digital Filter Design (DSP example)  
-- VHDL Data-Flow modeling  
-- KEYWORD: generate, array, range, constant and subtype  
-----  
library IEEE;                                -- declare the library  
use IEEE.std_logic_1164.all;  
use IEEE.std_logic_arith.all;  
-----  
entity FIR_filter is  
port( rst:   in   std_logic;  
      clk:   in   std_logic;  
      coef_ld: in   std_logic;  
      start: in   std_logic;  
      o_enable: in std_logic;  
      bypass: in   std_logic;  
      Xn_in:  in   std_logic_vector(3 downto 0);  
      Yn_in:  in   std_logic_vector(15 downto 0);  
      Xn_out: out  std_logic_vector(3 downto 0);  
      Yn_out: out  std_logic_vector(15 downto 0)  
); end FIR_filter;
```

# FIR Filter

---

```
architecture BEH of FIR_filter is
    constant K:          integer := 4;          -- circuit has four stages

    -- use type and subtype to define the complex signals
    subtype bit4 is      std_logic_vector(3 downto 0);
    subtype bit8 is      std_logic_vector(7 downto 0);
    subtype bit16 is     std_logic_vector(15 downto 0);

    type klx4  is        array (K downto 0) of bit4;
    type kx8   is        array (K-1 downto 0) of bit8;
    type klx8  is        array (K downto 0) of bit8;
    type kx16  is        array (K-1 downto 0) of bit16;
    type klx16 is        array (K downto 0) of bit16;

    -- define signal in type of arrays
    signal     REG1, REG2, COEF      : klx4;
    signal     MULT8                  : kx8;
    signal     MULT16                 : kx16;
    signal     SUM                     : klx16;
    signal     Xn_tmp                  : bit4;
    signal     Yn_tmp                  : bit16;
```

# FIR Filter

---

```
begin

    -- initialize the first stage of FIR circuit

    REG2(K) <= Xn_in when (start='1')
        else (REG2(K)'range => '0');
    REG1(K) <= (REG1(K)'range => '0');
    SUM(K) <= Yn_in;
    COEF(K) <= Xn_in;
```



# FIR Filter

---

```
-- start the computation, use generate to obtain the multiple stages
gen8: for j in K-1 downto 0 generate
  stages: process (rst, clk)
  begin
    if (rst='0') then
      REG1(j) <= (REG1(j)'range => '0');
      REG2(j) <= (REG2(j)'range => '0');
      COEF(j) <= (COEF(j)'range => '0');
      MULT16(j) <= (MULT16(j)'range => '0');
      SUM(j) <= (SUM(j)'range => '0');
    elsif (clk'event and clk='1') then
      REG1(j) <= REG2(j+1); REG2(j) <= REG1(j);
      if (coef_ld = '1') then COEF(j) <= COEF(j+1); end if;
      MULT8(j) <= signed(REG1(j))*signed(COEF(j));
      MULT16(j)(7 downto 0) <= MULT8(j);
      if (MULT8(j)(7)='0') then MULT16(j)(15 downto 8) <= "00000000";
      else MULT16(j)(15 downto 8) <= "11111111";
      end if;
      SUM(j) <= signed(MULT16(j))+signed(SUM(j+1));
    end if;
  end process;
end generate;
```

# FIR Filter

---

---

```
-- control the outputs by concurrent statements
```

```
Xn_tmp <= Xn_in when bypass = '1' else  
          REG2(0) when coef_ld = '0' else  
          COEF(0);
```


```
Yn_tmp <= Yn_in when bypass = '1' else  
          SUM(0);
```

```
Xn_out <= Xn_tmp when o_enable = '0' else  
          (Xn_out'range => 'Z');
```

```
Yn_out <= Yn_tmp when o_enable = '0' else  
          (Yn_out'range => 'Z');
```

```
end BEH;
```

---

 

---

THANK YOU

---