

## Lecture 18

### Bipolar Junction Transistors (BJTs)

In this lecture you will learn:

- The operation of bipolar junction transistors
- Forward and reverse active operations, saturation, cutoff
- Ebers-Moll model
- Small signal models

### Bipolar Transistors



First Bipolar Transistor (AT&T Bell Labs)




First Bipolar Transistor (AT&T Bell Labs)




William Shockley, John Bardeen, Walter Brattain  
(Nobel Prize for the Transistor, AT&T Bell Labs)


### NPN Bipolar Junction Transistor

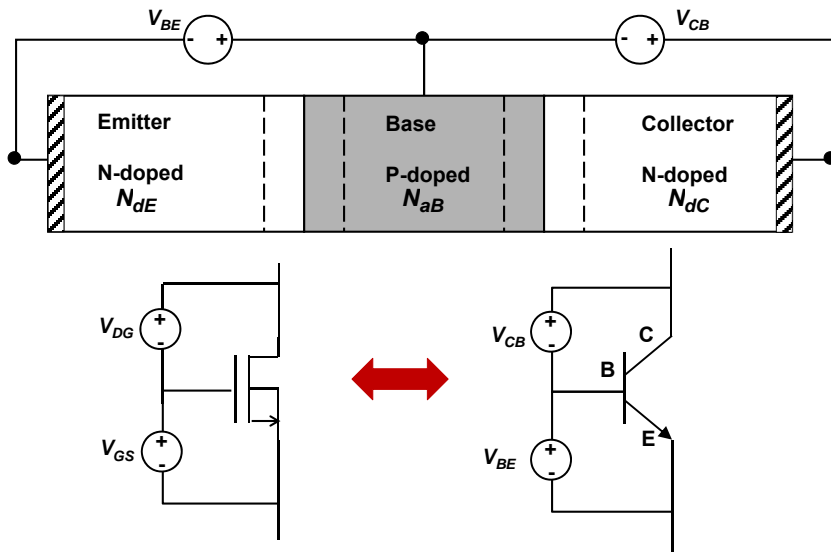


### PNP Bipolar Junction Transistor

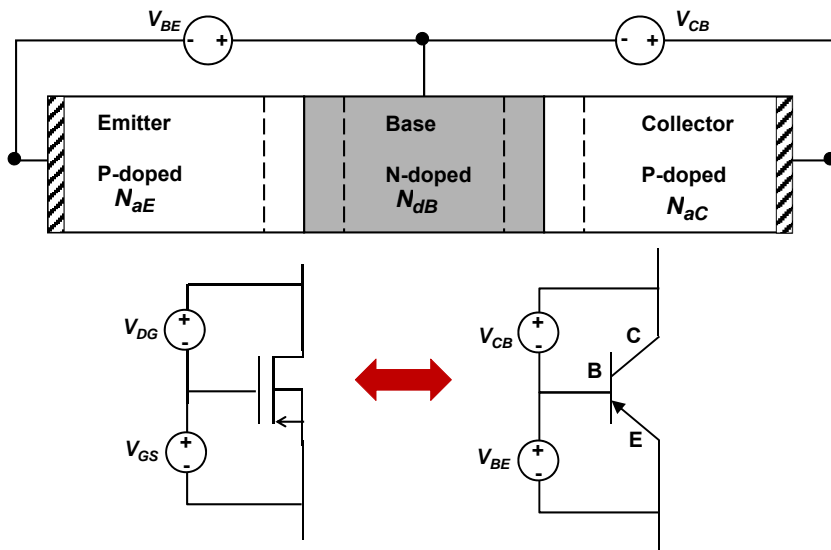

### A Silicon NPN BJT

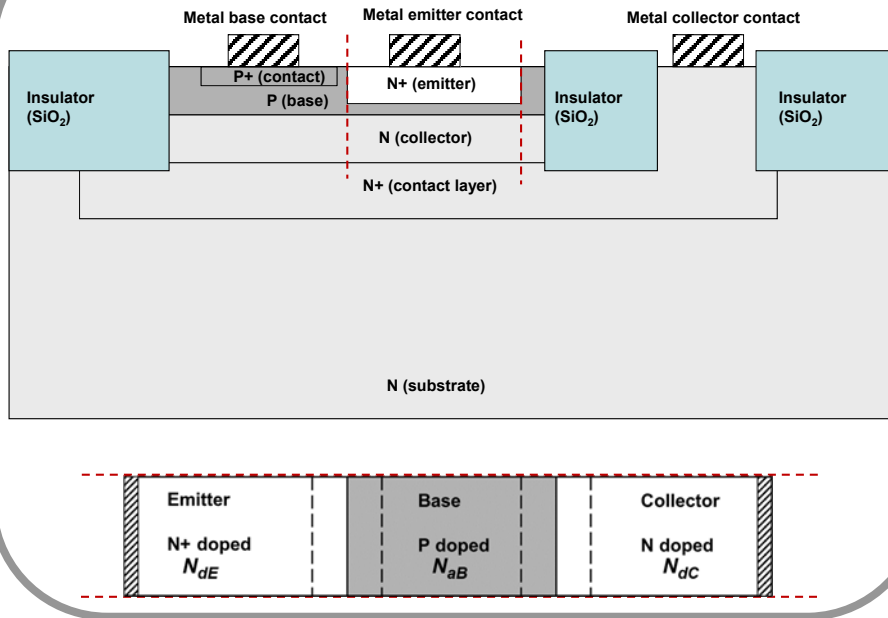

### NPN BJT: Basic Operation

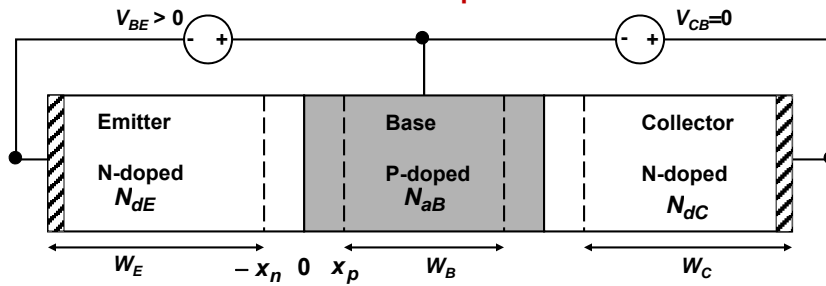

Suppose:

The base-emitter junction is **forward biased**


$$V_{BE} > 0$$

The base-collector junction is **zero biased**

$$V_{CB} = 0$$

This biasing scheme will put the device in the “**forward active**” operation (to be discussed fully later)


### NPN BJT: Basic Operation

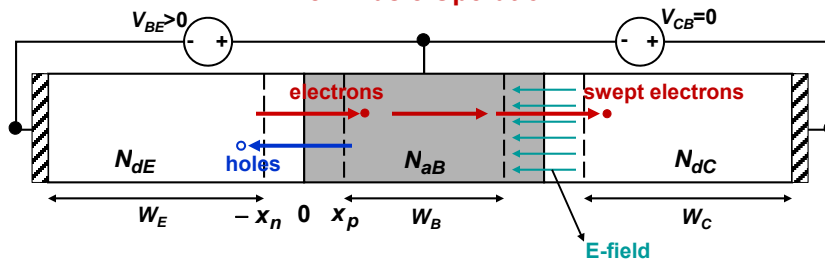

Consider the action in the base first ( $V_{BE} > 0$  and  $V_{CB} = 0$ )

- The electrons diffuse from the emitter, cross the depletion region, and enter the base
- In the base, the electrons are the minority carriers
- In the base, the electrons diffuse towards the collector
- As soon as the electrons reach the base-collector depletion region they are immediately swept away into the collector by the strong electric fields in the depletion region

### NPN BJT: Electron-Hole Populations

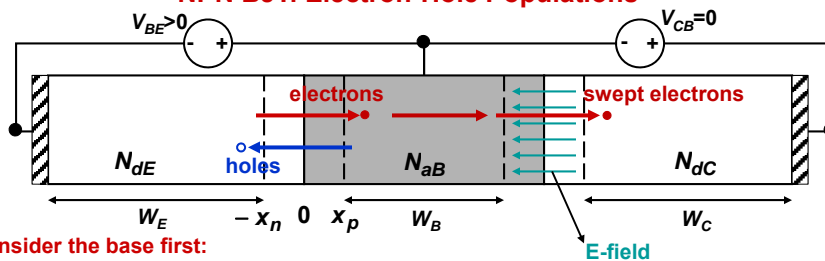

Consider the base first:

In the base, the electron population can be written as:

$$n(x) = n_{po} + n'(x)$$

Equilibrium electron density
Excess electron density

$$\left. \begin{array}{l} n_{po} = \frac{n_i^2}{N_{aB}} \end{array} \right\}$$


In the base, the excess electron population satisfies the differential equation:

$$\frac{\partial^2 n'(x)}{\partial x^2} - \frac{n'(x)}{L_n^2} = 0$$

Boundary conditions

$$\left. \begin{array}{l} n'(x_p) = \frac{n_i^2}{N_{aB}} \left( e^{\frac{qV_{BE}}{KT}} - 1 \right) \\ n'(x_p + W_B) = \frac{n_i^2}{N_{aB}} \left( e^{\frac{qV_{BC}}{KT}} - 1 \right) = 0 \end{array} \right\}$$

### NPN BJT: Electron-Hole Populations

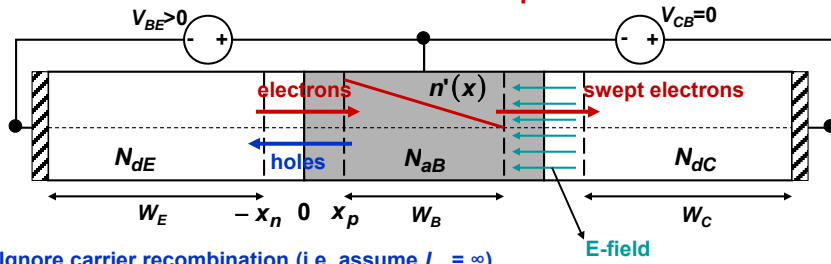


- Ignore carrier recombination (i.e. assume  $L_n = \infty$ )

$$\frac{\partial^2 n'(x)}{\partial x^2} = 0 \quad \left. \begin{array}{l} \text{Boundary} \\ \text{conditions} \end{array} \right\} \begin{array}{l} n'(x_p) = \frac{n_i^2}{N_{aB}} \left( e^{\frac{qV_{BE}}{KT}} - 1 \right) \\ n'(x_p + W_B) = \frac{n_i^2}{N_{aB}} \left( e^{\frac{qV_{BC}}{KT}} - 1 \right) = 0 \end{array}$$

Solution is:

$$n'(x) = n'(x_n) \left( 1 - \frac{x - x_p}{W_B} \right) = \frac{n_i^2}{N_{aB}} \left( e^{\frac{qV_{BE}}{KT}} - 1 \right) \left( 1 - \frac{x - x_p}{W_B} \right)$$

### NPN BJT: Electron-Hole Populations

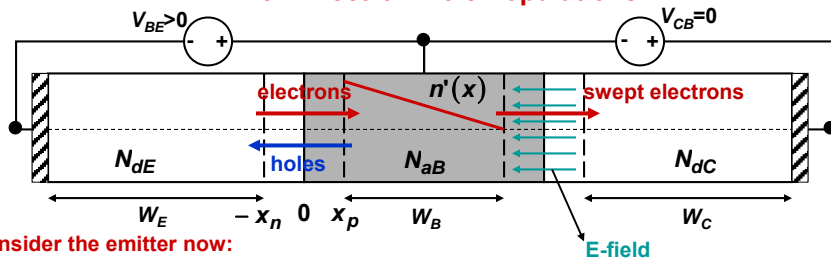

Consider the emitter now:


In the emitter, the hole population can be written as:

$$p(x) = p_{no} + p'(x) \quad \left. \begin{array}{l} \text{Equilibrium hole density} \\ \text{Excess hole density} \end{array} \right\} p_{no} = \frac{n_i^2}{N_{dE}}$$

In the emitter, the excess hole population satisfies the differential equation:

$$\frac{\partial^2 p'(x)}{\partial x^2} - \frac{p'(x)}{L_p^2} = 0 \quad \left. \begin{array}{l} \text{Boundary} \\ \text{conditions} \end{array} \right\} \begin{array}{l} p'(-x_n) = \frac{n_i^2}{N_{dE}} \left( e^{\frac{qV_{BE}}{KT}} - 1 \right) \\ p'(-x_n - W_E) = 0 \end{array}$$

### NPN BJT: Electron-Hole Populations

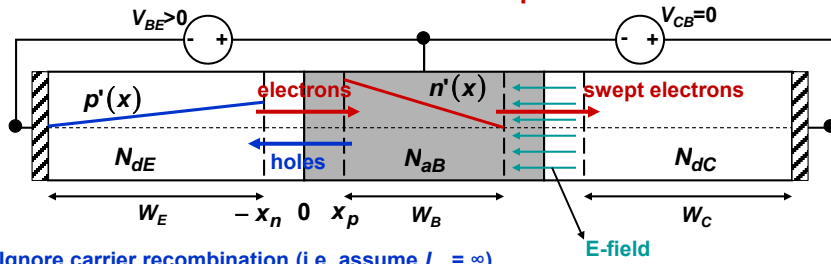


- Ignore carrier recombination (i.e. assume  $L_p = \infty$ )

$$\frac{\partial^2 p'(x)}{\partial x^2} = 0 \quad \left. \vphantom{\frac{\partial^2 p'(x)}{\partial x^2} = 0} \right\} \begin{array}{l} \text{Boundary} \\ \text{conditions} \end{array} \rightarrow \begin{array}{l} p'(-x_n) = \frac{n_i^2}{N_{dE}} \left( e^{\frac{qV_{BE}}{KT}} - 1 \right) \\ p'(-x_n - W_E) = 0 \end{array}$$

Solution is:

$$p'(x) = p'(-x_n) \left( 1 + \frac{x+x_n}{W_E} \right) = \frac{n_i^2}{N_{dE}} \left( e^{\frac{qV_{BE}}{KT}} - 1 \right) \left( 1 + \frac{x+x_n}{W_E} \right)$$
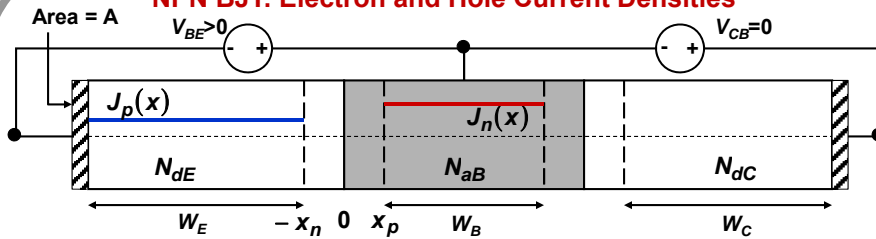
### NPN BJT: Electron and Hole Current Densities



In the base:

- The electron current is:


$$J_n(x) \approx q D_n \frac{\partial n(x)}{\partial x} = q n_i^2 \frac{D_n}{N_{aB} W_B} \left( e^{\frac{qV_{BE}}{KT}} - 1 \right)$$

In the emitter:

- The hole current is:

$$J_p(x) \approx -q D_p \frac{\partial p(x)}{\partial x} = q n_i^2 \frac{D_p}{N_{dE} W_E} \left( e^{\frac{qV_{BE}}{KT}} - 1 \right)$$

### NPN BJT: Terminal Currents

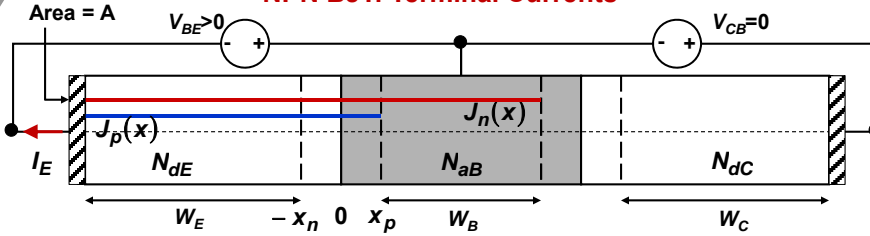


#### Emitter current:

- The current flowing out of the emitter is the sum of the total electron and total hole currents in the emitter:

$$I_E = qn_i^2 A \left( \frac{D_p}{N_{dE}W_E} + \frac{D_n}{N_{aB}W_B} \right) \left( e^{\frac{qV_{BE}}{KT}} - 1 \right)$$

### NPN BJT: Terminal Currents

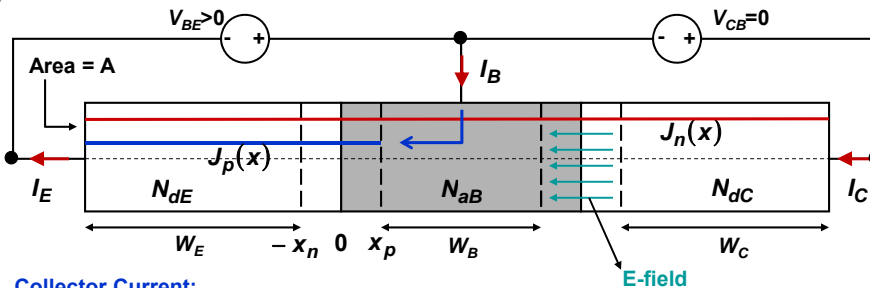

#### Collector Current:



- The current going into the collector is due to the electrons that got swept from the Base through the Base-Collector depletion region by the electric-fields:

$$I_C = qn_i^2 A \left( \frac{D_n}{N_{aB}W_B} \right) \left( e^{\frac{qV_{BE}}{KT}} - 1 \right)$$
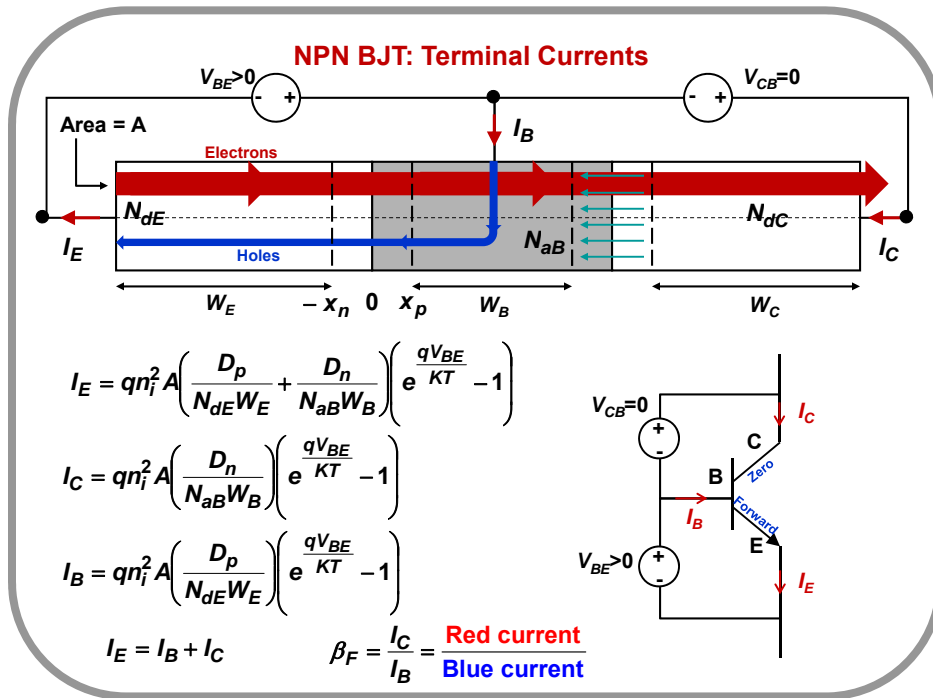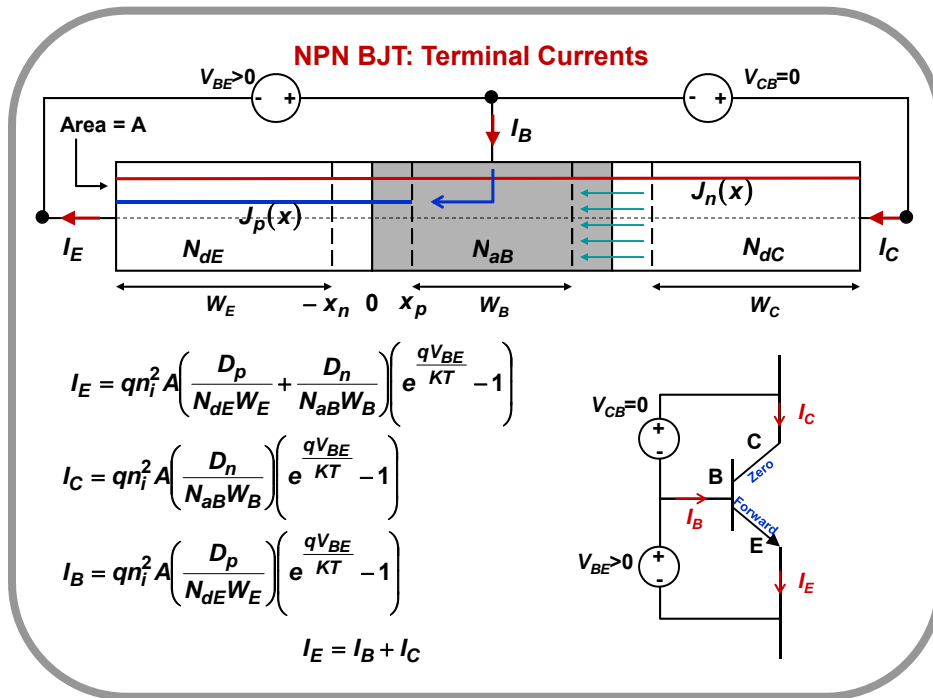
#### Base Current:

- The current going into the Base is due to the holes that got injected from the base into the emitter:

$$I_B = qn_i^2 A \left( \frac{D_p}{N_{dE}W_E} \right) \left( e^{\frac{qV_{BE}}{KT}} - 1 \right)$$





### NPN BJT: Circuit Level Parameters

**Current gain  $\beta_F$ :**

Current gain of the BJT in the forward active operation is defined as the ratio of the collector and base currents:

$$\beta_F = \frac{I_C}{I_B} = \frac{D_n}{N_{aB}W_B} \frac{N_{dE}W_E}{D_p} \Rightarrow I_C = \beta_F I_B$$

Typical values of  $\beta_F$  are between 20-200 and:

$$N_{dE} \gg N_{aB} > N_{dC}$$

**$\alpha_F$ :**


In the forward active operation  $\alpha_F$  is defined as the ratio of the collector and emitter currents:

$$\alpha_F = \frac{I_C}{I_E} = \frac{\frac{D_n}{N_{aB}W_B}}{\frac{D_p}{N_{dE}W_E} + \frac{D_n}{N_{aB}W_B}} \Rightarrow I_C = \alpha_F I_E$$

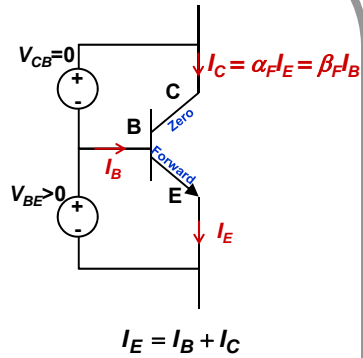**Transistor relation:**


$\alpha_F$  and  $\beta_F$  are related:

$$\beta_F = \frac{\alpha_F}{1 - \alpha_F}$$


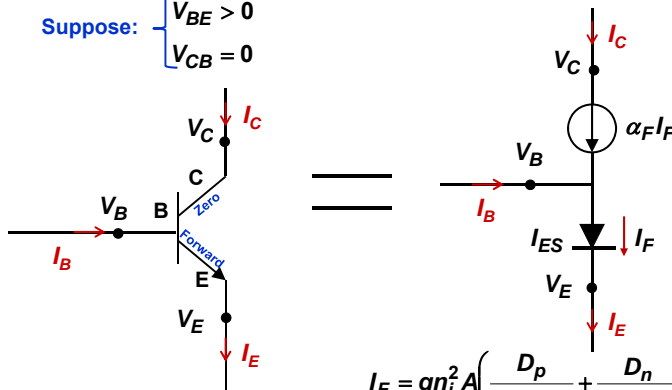
### NPN BJT: Ebers-Moll Model for Forward Active Operation

Suppose:  $\begin{cases} V_{BE} > 0 \\ V_{CB} = 0 \end{cases}$




$$I_F = qn_i^2 A \left( \frac{D_p}{N_{dE}W_E} + \frac{D_n}{N_{aB}W_B} \right) \left( e^{\frac{qV_{BE}}{KT}} - 1 \right)$$

$$= I_{ES} \left( e^{\frac{qV_{BE}}{KT}} - 1 \right)$$

$$\begin{aligned} I_B &= (1 - \alpha_F) I_F \\ I_C &= \alpha_F I_F \\ I_E &= I_F \end{aligned}$$

The circuit level simplified model with an **ideal diode** and a **current-controlled current source** models the NPN transistor in the forward active operation

### NPN BJT: Forward Active Operation

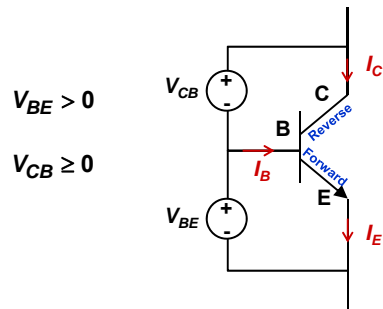


Forward active operation

$$\beta_F = \frac{I_C}{I_B}$$

$$\alpha_F = \frac{I_C}{I_E}$$

$$\beta_F = \frac{\alpha_F}{1 - \alpha_F}$$
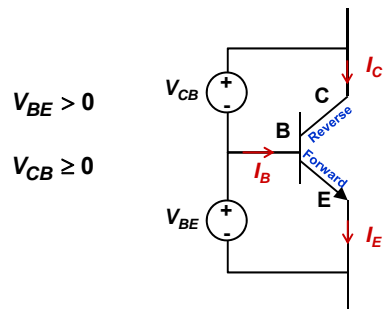
### NPN BJT: Forward and Reverse Active Operations




Forward active operation

$$\beta_F = \frac{I_C}{I_B}$$

$$\alpha_F = \frac{I_C}{I_E}$$
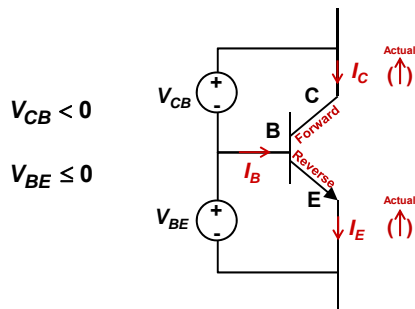
$$\beta_F = \frac{\alpha_F}{1 - \alpha_F}$$



Reverse active operation

$$\beta_R = -\frac{I_E}{I_B} = \frac{D_n}{N_{aB}W_B} \frac{N_{dC}W_C}{D_p}$$



$$\alpha_R = \frac{I_E}{I_C}$$

$$\beta_R = \frac{\alpha_R}{1 - \alpha_R}$$

In a well designed transistor:  $\beta_F \gg \beta_R$
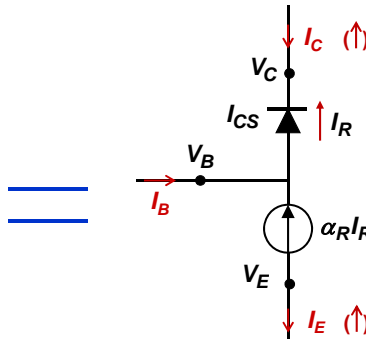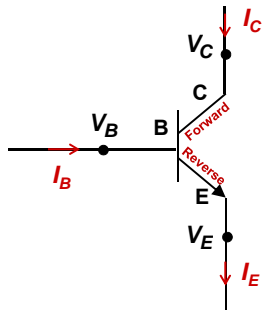
### NPN BJT: Ebers-Moll Model for Reverse Active Operation

Suppose:  $\begin{cases} V_{BC} > 0 \\ V_{BE} = 0 \end{cases}$



$$I_R = qn_i^2 A \left( \frac{D_p}{N_{dC}W_C} + \frac{D_n}{N_{aB}W_B} \right) \left( e^{\frac{qV_{BC}}{KT}} - 1 \right)$$



$$= I_{CS} \left( e^{\frac{qV_{BC}}{KT}} - 1 \right)$$

$$\begin{aligned} I_B &= (1 - \alpha_R) I_R \\ I_C &= -I_R \\ I_E &= -\alpha_R I_R \end{aligned}$$

The circuit level simplified model with an ideal diode and a current-controlled current source models the NPN transistor in the reverse active operation

### NPN BJT: Ebers-Moll Model and Terminal Currents

Terminal currents:

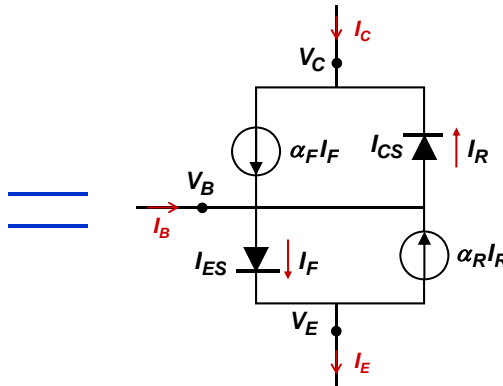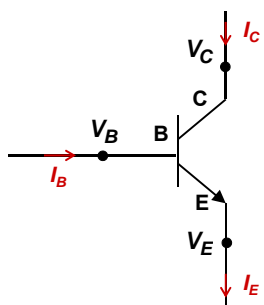


$$I_R = I_{CS} \left( e^{\frac{qV_{BC}}{KT}} - 1 \right)$$

$$I_F = I_{ES} \left( e^{\frac{qV_{BE}}{KT}} - 1 \right)$$

And

$$\begin{aligned} I_B &= (1 - \alpha_F) I_F + (1 - \alpha_R) I_R \\ I_C &= \alpha_F I_F - I_R \\ I_E &= I_F - \alpha_R I_R \end{aligned}$$

### NPN BJT: Regimes of Operation - I

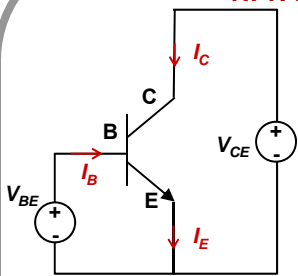

In forward active operation:



$$I_B > 0 \quad V_{BE} > 0 \quad V_{CB} \geq 0$$

Since:  $V_{CE} = V_{CB} + V_{BE}$

$\Rightarrow$  In forward active operation:  $V_{CE} \geq V_{BE}$

$$I_C = qn_i^2 A \left( \frac{D_n}{N_{aB}W_B} \right) \left( e^{\frac{qV_{BE}}{KT}} - 1 \right) = \beta_F I_B$$

$\Rightarrow$  Independent of  $V_{CE}$

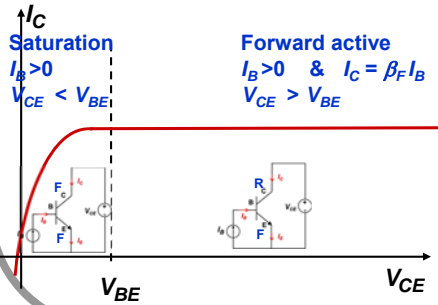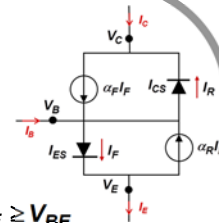

**Forward active:**

Base-emitter junction forward biased  
Base-collector junction reverse biased

$$I_B > 0 \quad V_{BE} > 0 \quad V_{CB} \geq 0$$


**Saturation:**

Base-emitter junction forward biased  
Base-collector junction forward biased

$$I_B > 0 \quad V_{BE} > 0 \quad V_{CB} < 0$$


### Carrier Densities in Different Regimes of Operation

Forward active:

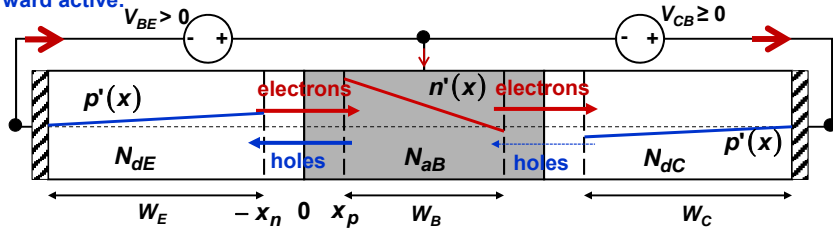


$$N_{dE} \gg N_{aB} > N_{dC}$$

Saturation:

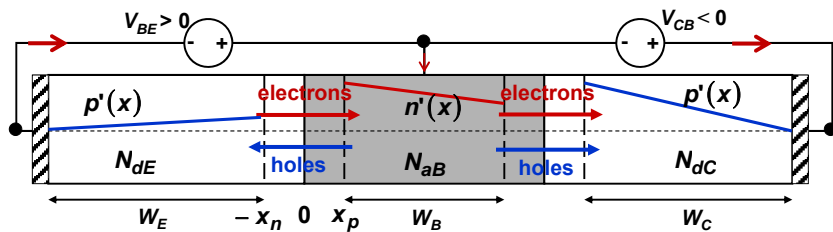

The forward biased base-collector junction reduces the collector current!

## NPN-BJT: Regimes of Operation - II

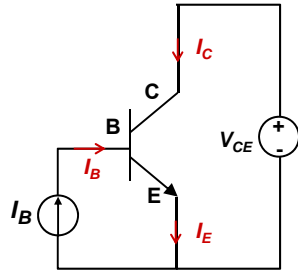


**Forward active:**  
 Base-emitter junction forward biased  
 Base-collector junction reversed biased  
 $I_B > 0$   $V_{BE} > 0$   $V_{CB} \geq 0$   
 $I_C = \beta_F I_B$


**Saturation:**  
 Base-emitter junction forward biased  
 Base-collector junction forward biased  
 $I_B > 0$   $V_{BE} > 0$   $V_{CB} < 0$

**Cutoff:**  
 Base current zero  
 $I_B = 0$

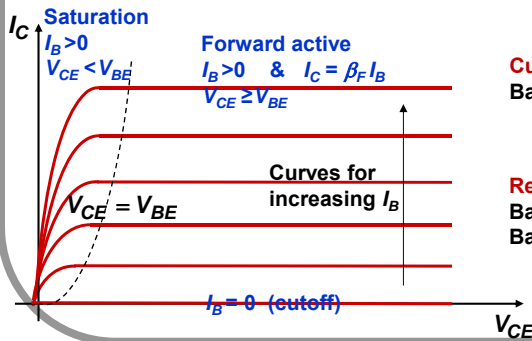
**Reverse active:**  
 Base-emitter junction reverse biased  
 Base-collector junction forward biased  
 $I_B > 0$   $V_{BE} \leq 0$   $V_{CB} < 0$   
 $I_E = -\beta_R I_B$


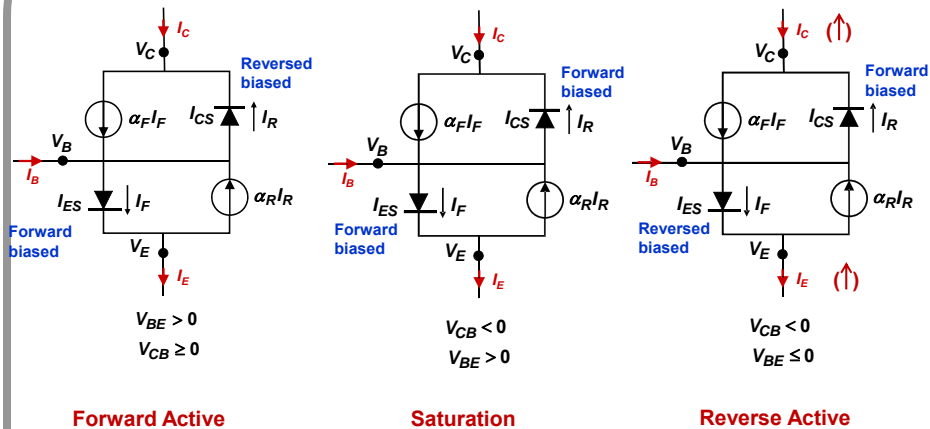
## NPN BJT: Different Regimes of Operation



### NPN BJT: A Simple Amplifier Circuit

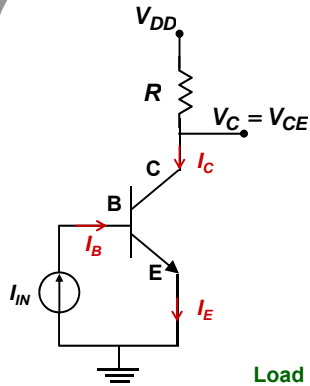

Current gain (in forward active regime):


$$\frac{I_{OUT}}{I_{IN}} = \frac{I_C}{I_B} = \beta_F$$

Load line equation:


$$V_{CE} = V_{DD} - I_C R$$

$$\Rightarrow I_C = \frac{V_{DD} - V_{CE}}{R}$$

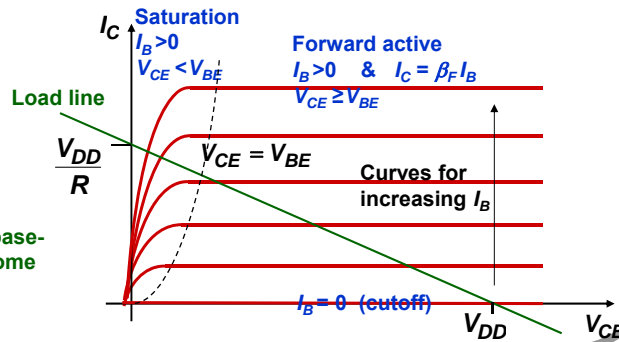**Lesson:** Don't let the base-collector junction become forward biased



### NPN BJT

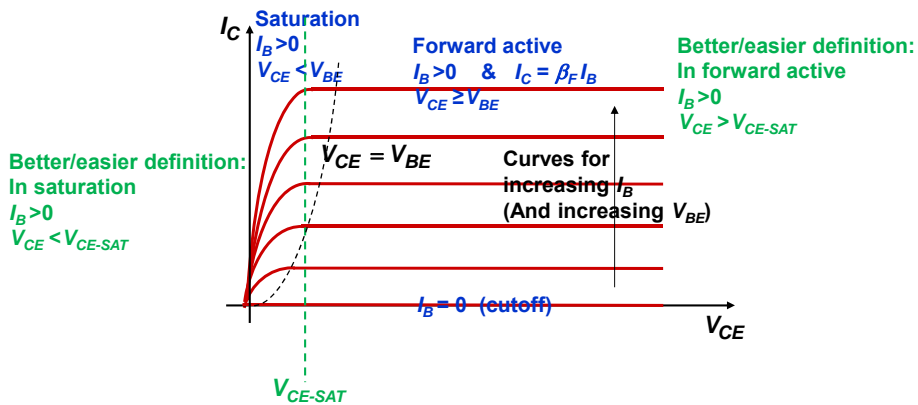


### NPN BJT: Voltage Biasing of a Simple Amplifier Circuit

$$V_{BE-ON} \sim 0.6 \text{ V}$$

$$V_{CE-SAT} \sim 0.2 \text{ V}$$

Acting as a current source

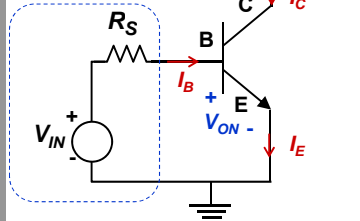

Approximate analysis of transistor DC biasing:

If:  $V_{IN} < V_{BE-ON} \Rightarrow I_B \approx 0 \Rightarrow$  Transistor in cut-off

If:  $V_{IN} \geq V_{BE-ON} \Rightarrow$

$$V_{IN} = I_B R_S + V_{BE-ON}$$

$$I_B = \frac{V_{IN} - V_{BE-ON}}{R_S}$$

Assume forward active operation ( $V_{CE} > V_{CE-SAT}$ ):

$$I_C = \beta_F I_B$$

$$V_{OUT} = V_{DD} - I_C R = V_{DD} - \beta_F \left( \frac{V_{IN} - V_{BE-ON}}{R_S} \right) R$$

Final Step - confirm if the assumption of forward active operation was valid:

$$V_{CE} \geq V_{CE-SAT}$$



$$\Rightarrow V_{CE} = V_{OUT} = V_{DD} - I_C R = V_{DD} - \beta_F \left( \frac{V_{IN} - V_{BE-ON}}{R_S} \right) R \geq V_{CE-SAT}$$

### NPN BJT Amplifier Circuit: Transfer Curve

$$V_{BE-ON} \sim 0.6 \text{ V}$$

$$V_{CE-SAT} \sim 0.2 \text{ V}$$

Acting as a current source

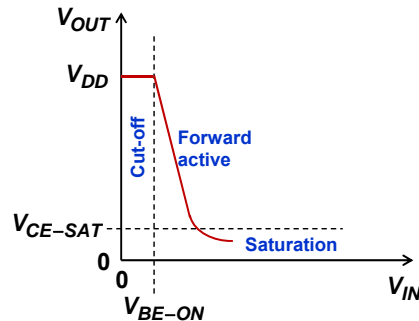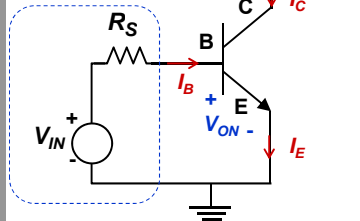



If:  $V_{IN} < V_{BE-ON} \Rightarrow I_B \approx 0 \Rightarrow V_{OUT} = V_{DD}$  [Transistor in cut-off]

If:  $V_{IN} \geq V_{BE-ON} \Rightarrow I_B = \frac{V_{IN} - V_{BE-ON}}{R_S}$

$$V_{OUT} = V_{DD} - I_C R = V_{DD} - \beta_F \frac{R}{R_S} (V_{IN} - V_{BE-ON})$$

If:  $I_B > 0$  &  $V_{CE} = V_{OUT} \leq V_{CE-SAT} \Rightarrow$  [Transistor in saturation]

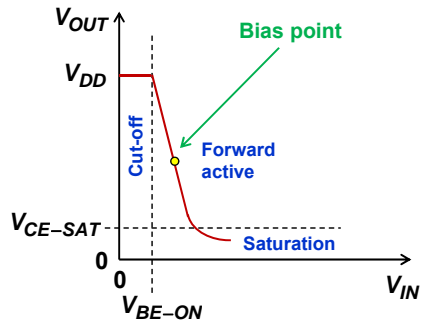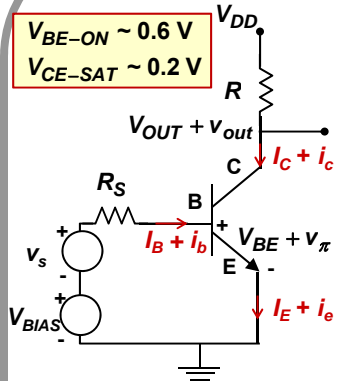
### NPN BJT Common Emitter (CE) Voltage Amplifier



We need better techniques to calculate the voltage gain of such amplifier circuits

We need small signal models of the BJTs!

### NPN BJT: Small Signal Circuit Model

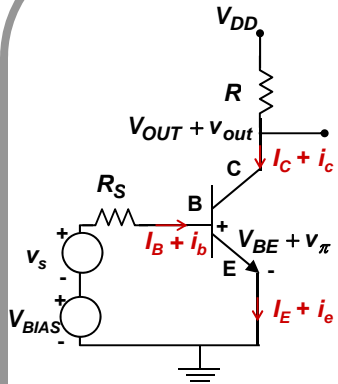

Base current:

$$I_B = qn_i^2 A \left( \frac{D_p}{N_d E W_E} \right) \left( e^{\frac{qV_{BE}}{KT}} - 1 \right)$$

$$= I_{BS} \left( e^{\frac{qV_{BE}}{KT}} - 1 \right)$$

$$\Rightarrow I_B + i_b = I_{BS} \left( e^{\frac{q(V_{BE} + v_\pi)}{KT}} - 1 \right)$$

$$\Rightarrow i_b = \frac{\partial I_B}{\partial V_{BE}} v_\pi = \frac{q(I_B + I_{BS})}{KT} v_\pi \approx \frac{qI_B}{KT} v_\pi = g_\pi v_\pi$$

$$\Rightarrow g_\pi = \frac{qI_B}{KT}$$

Collector current:


$$I_C + i_c = \beta_F (I_B + i_b)$$

$$\Rightarrow i_c = \beta_F i_b = \beta_F g_\pi v_\pi = g_m v_\pi$$


$$g_m = \beta_F g_\pi = \beta_F \frac{qI_B}{KT} = \frac{qI_C}{KT} \leftarrow \text{Increases linearly with the collector current}$$




### NPN BJT: Small Signal Circuit Model

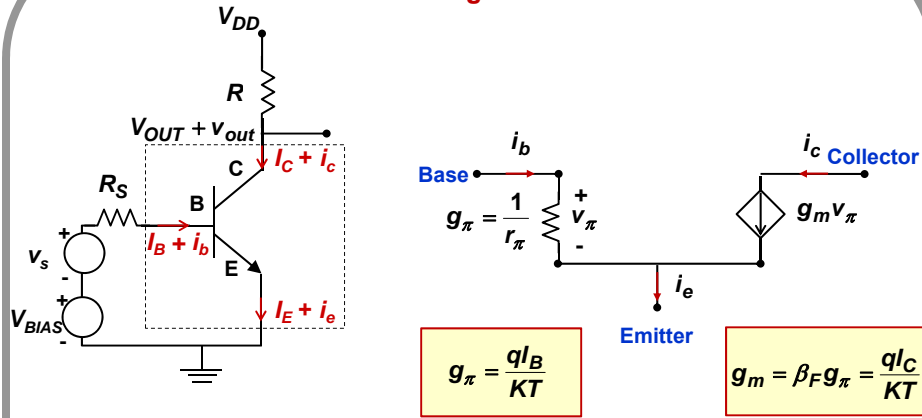
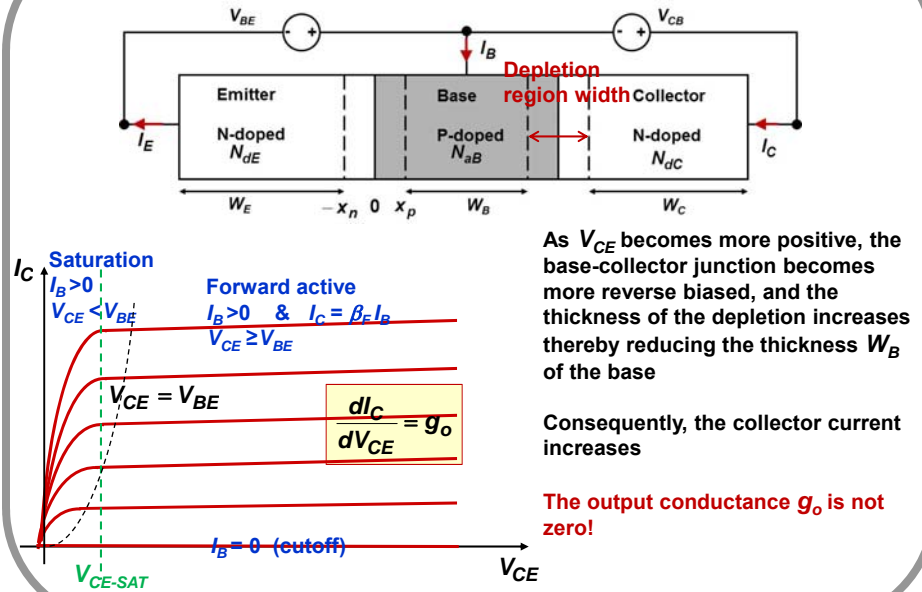
### NPN BJT: Forward Active Current vs $V_{CE}$


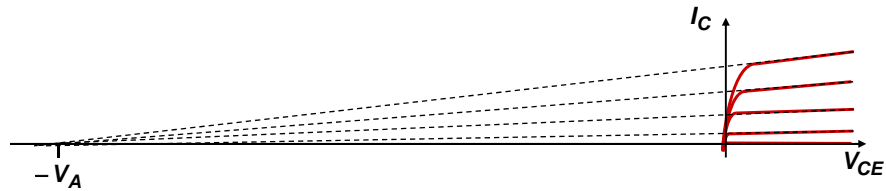
### NPN BJT: Output Conductance and the Early Voltage




The slope of the  $I_C$  vs  $V_{CE}$  curves are modeled using the early voltage  $V_A$ :

$$\frac{dI_C}{dV_{CE}} = g_o = \frac{I_C}{V_A} = \lambda_n I_C$$


The early voltage is usually in the 50-200 V range

### NPN BJT: Output Conductance

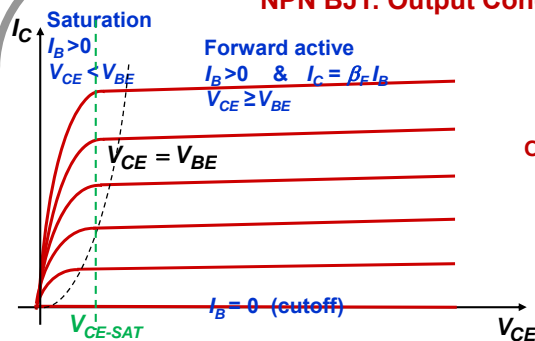


Output conductance:

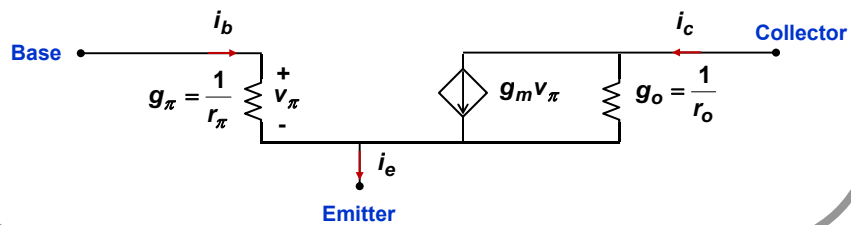
$$g_o = \frac{1}{r_o} = \frac{\partial I_C}{\partial V_{CE}}$$


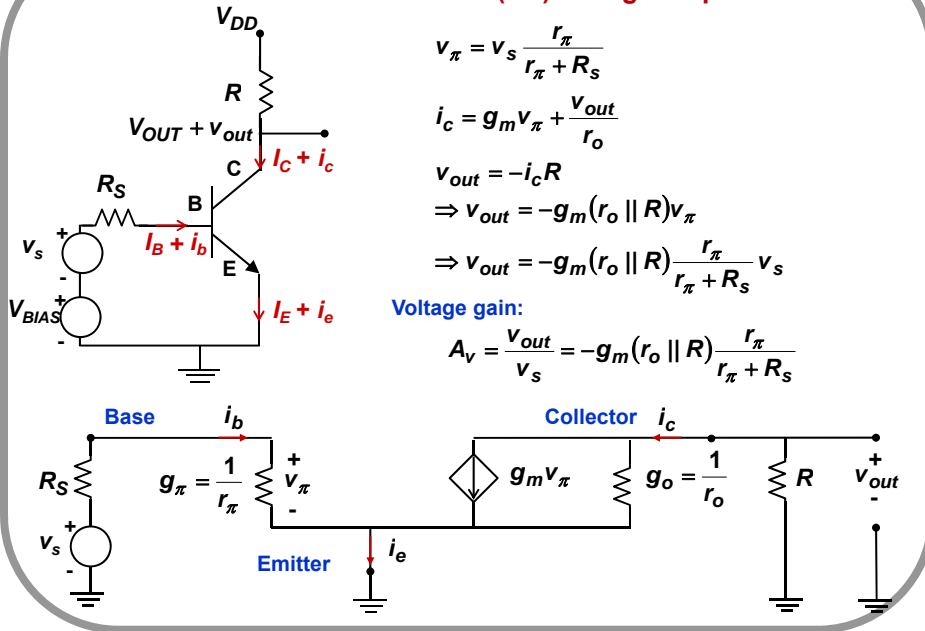
### NPN BJT Common Emitter (CE) Voltage Amplifier


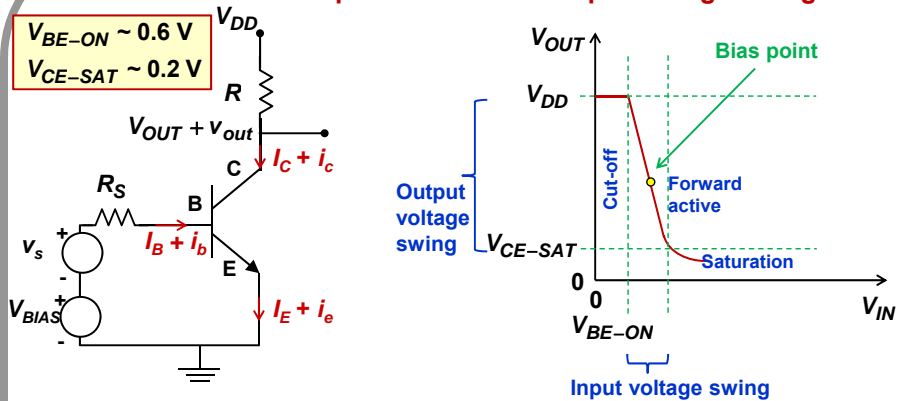
### NPN BJT CE Amplifier: Limits of Output Voltage Swing



#### Minimum output voltage and maximum input voltage:

If the output voltage becomes too small (happens when the input voltage becomes too large), the BJT will go into the **saturation region** (in the saturation region the gain is small)

#### Maximum output voltage and minimum input voltage:

If the input voltage becomes too small the BJT will go into **cut-off**

