

Lecture 2: Non-Ideal Amps and Op-Amps

Prof. Ali M. Niknejad

Practical Op-Amps


- Linear Imperfections:
 - Finite open-loop gain ($A_0 < \infty$)
 - Finite input resistance ($R_i < \infty$)
 - Non-zero output resistance ($R_o > 0$)
 - Finite bandwidth / Gain-BW Trade-Off
- Other (non-linear) imperfections:
 - Slew rate limitations
 - Finite swing
 - Offset voltage
 - Input bias and offset currents
 - Noise and distortion

Simple Model of Amplifier





- Input capacitance and output capacitance are added
- Any amplifier has input capacitance due to transistors and packaging / board parasitics
- Output capacitance is usually dominated by the load
 - Driving cables or a board trace
 - Intrinsic capacitance of actuator

Transfer Function

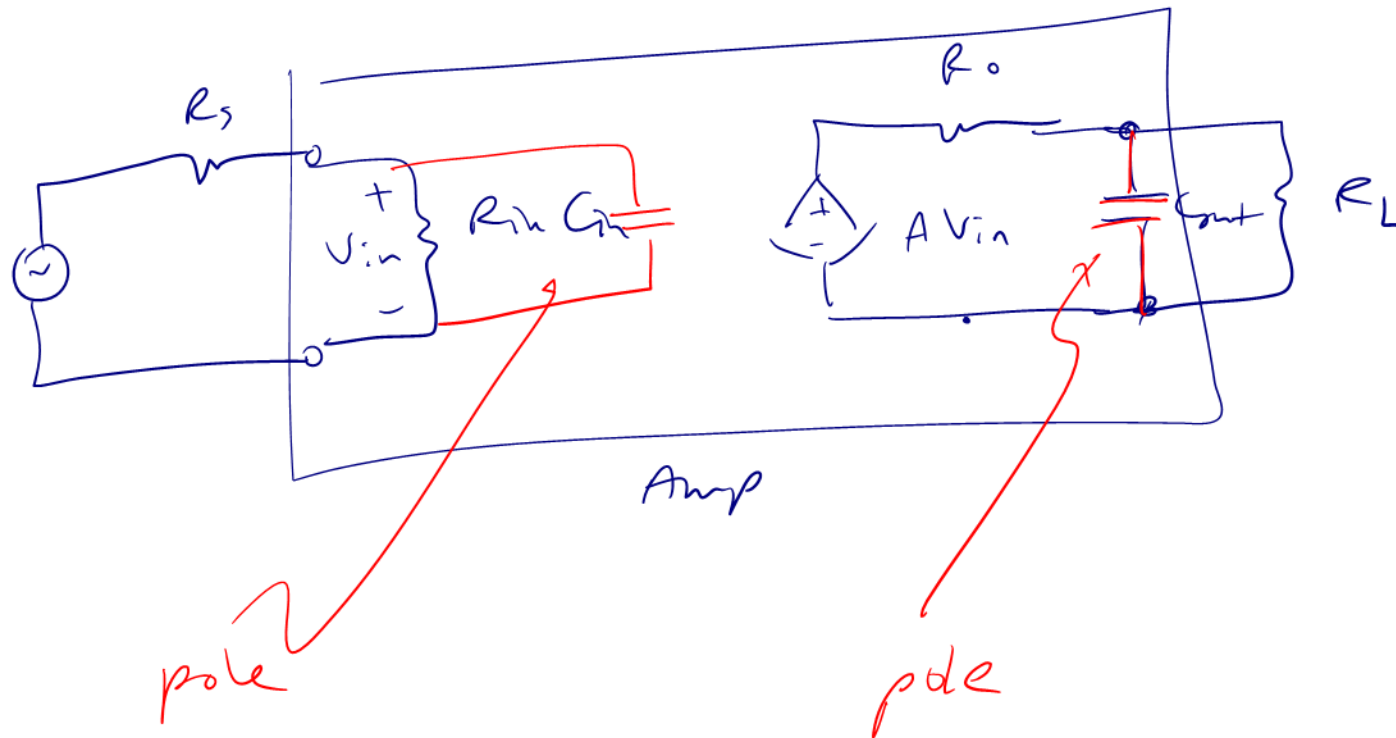


- Using the concept of impedance, it's easy to derive the transfer function

Operational Transconductance Amp

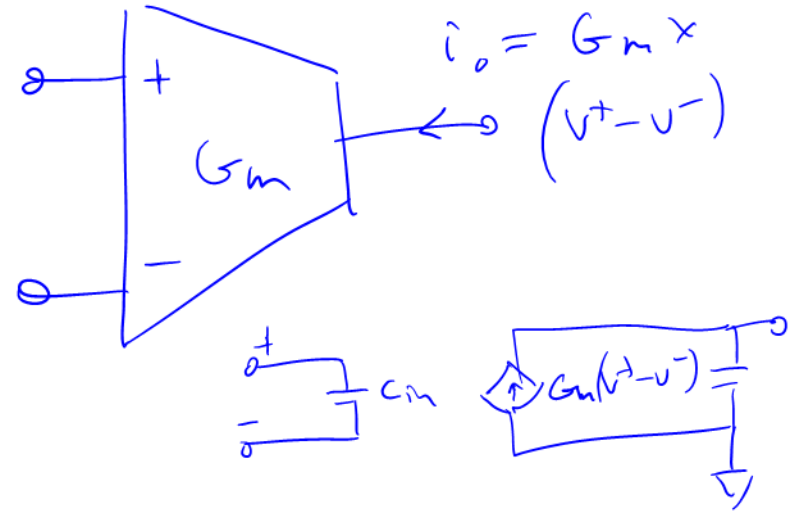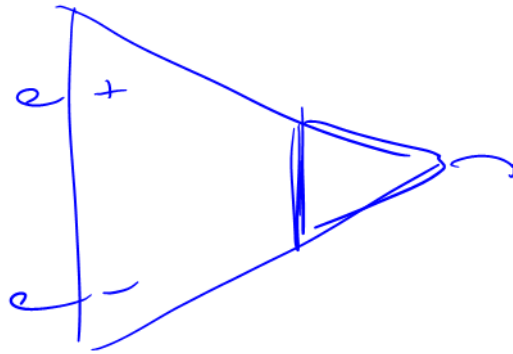

- Also known as an “OTA”
 - If we “chop off” the output stage of an op-amp, we get an OTA
- An OTA is essentially a G_m amplifier. It has a current output, so if we want to drive a load resistor, we need an output stage (buffer)
- Many op-amps are internally constructed from an OTA + buffer


Op-Amp Model

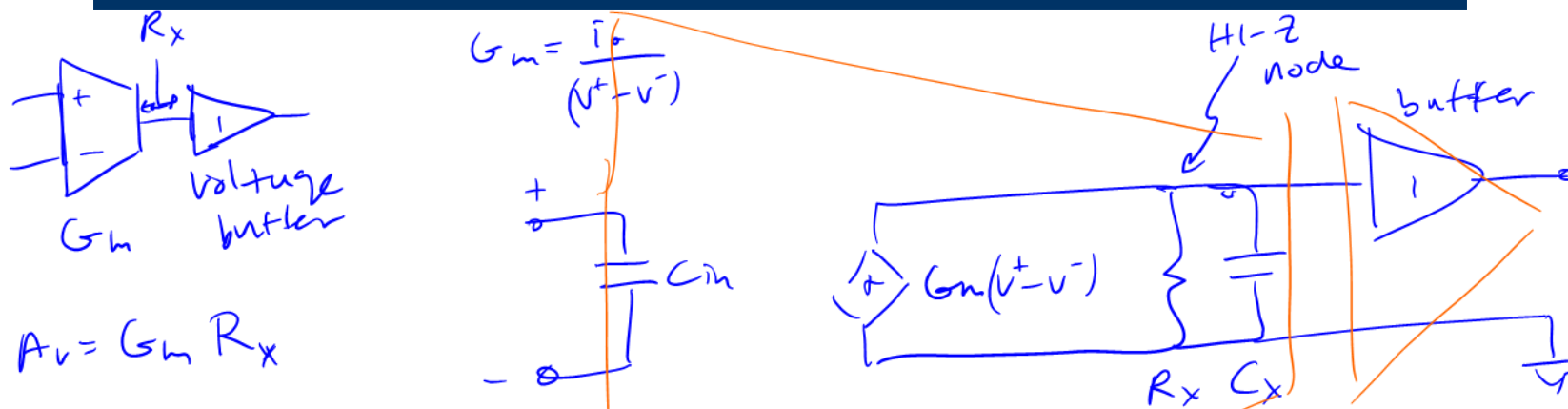

- The following model closely resembles the insides of an op-amp.
- The input OTA stage drives a high Z node to generate a very large voltage gain.
- The output buffer then can drive a low impedance load and preserve the high voltage gain

Op-Amp Gain / Bandwidth

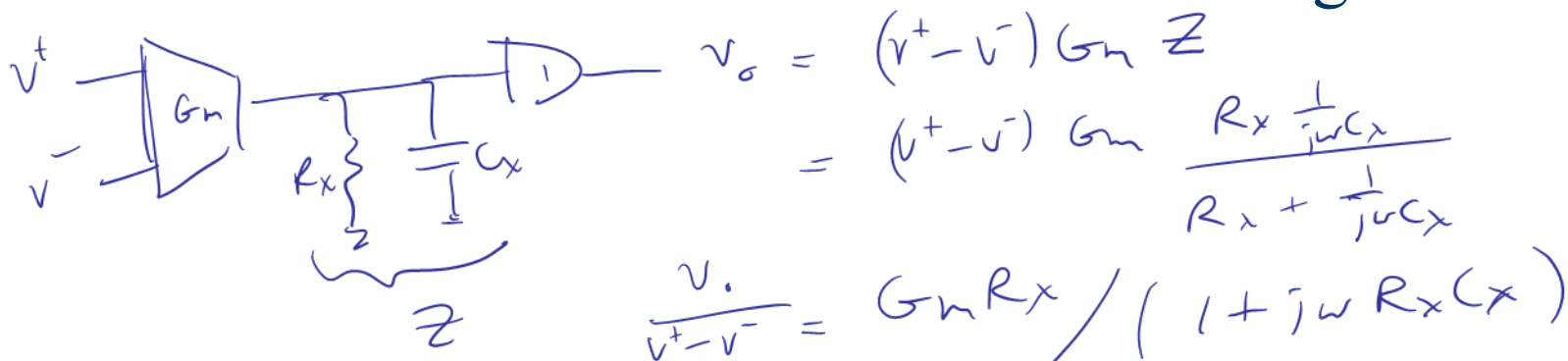- The dominant frequency response of the op-amp is due to the time constant formed at the high-Z node



- An interesting observation is that the gain-bandwidth product depends on G_m and C_x only

$$BW = \frac{1}{R_x C_x}$$


$$G_o \times BW =$$

$$G_o = G_m R_x$$

$$GBW = \frac{G_m}{C_x}$$

Preview: Driving Capacitive Loads

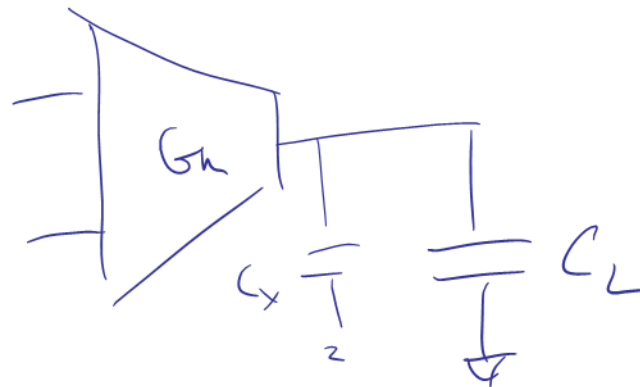- In many situations, the load is capacitor rather than a resistor
- For such cases, we can directly use an OTA (rather than a full op-amp) and the gain / bandwidth product are now determined by the load capacitance



$$GBW = \frac{G_m}{(C_L + C_x)}$$

$$= \frac{G_m}{C_L}$$


$$C_L \gg C_x$$

OTA Power Consumption

- For a fixed load, the current consumption of the OTA is fixed by the gain/bandwidth requirement, assuming load dominates


$$C_L \gg C_x$$

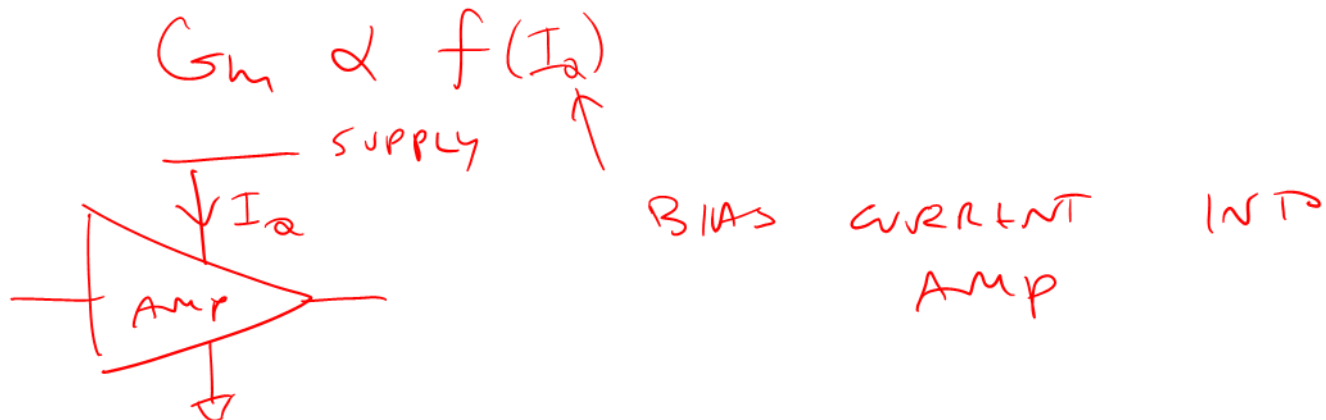- G_m scales with current, so driving a larger capacitance requires more power



Gain/Bandwidth Trade-off

Open-Loop Frequency Response

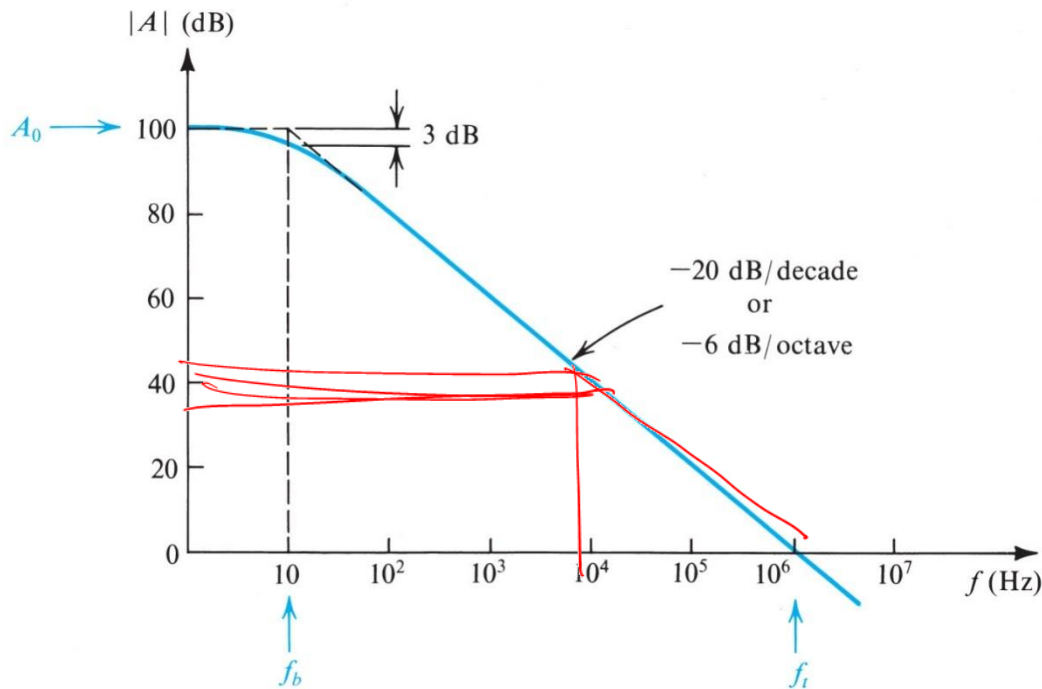

$$A(j\omega) = \frac{A_0}{1 + j\omega/\omega_b}$$

A_0 : dc gain

ω_b : 3dB frequency

$\omega_t = A_0\omega_b$: unity-gain bandwidth
(or "gain-bandwidth product")

For high frequency, $\omega \gg \omega_b$

$$A(j\omega) = \frac{\omega_t}{j\omega}$$

$$\omega \gg \omega_b \quad \left| \frac{j\omega}{\omega_b} \right| \gg 1 \quad \text{GBW}$$

$$A(j\omega) \approx \frac{A_0}{j\frac{\omega}{\omega_b}} = \frac{A_0 \omega_b}{j\omega} = \text{GBW} / j\omega$$

UNITY GAIN FREQUENCY $\rightarrow \omega_t = \text{GBW}$

Single pole response with a dominant pole at ω_b

$$|A(j\omega)| = 1 \approx \frac{\text{GBW}}{\omega_t}$$

UNITY GAIN

FREQUENCY $\rightarrow \omega_t = \text{GBW}$

Bandwidth Extension

- Suppose the core amplifier is single pole with bandwidth:

$$G(\omega) = \frac{G_0 \leftarrow \text{DC GAW}}{1 + j \frac{\omega}{\omega_b} \leftarrow \text{BW}}$$

- When used feedback, the overall transfer function is given by

$$G_{CL} = \frac{G}{1 + Gf} = \frac{\frac{G_0}{1 + j\omega/\omega_b}}{1 + \frac{G_0}{1 + j\omega/\omega_b} f}$$

$$G_{CL} = \frac{G_0}{(1 + j\frac{\omega}{\omega_b}) + G_0 f}$$

$$= \frac{G_0 / (1 + G_0 f)}{1 + j \frac{\omega}{\omega_b (1 + G_0 f)}} = \frac{G_{L_0}(\text{DC})}{1 + j \frac{\omega}{\omega_b'}}$$

BW EXPANSION

Gain / Bandwidth Product in Feedback

- Even though the bandwidth expanded by $(1+T)$, the gain drops by the same factor. So overall the gain-bandwidth (GBW) product is constant
- The GBW product depends only on the G_m of the op-amp and the C_x internal capacitance (or load in the case of an OTA)

$$\omega_b = (1+T) \omega_b$$

$$G_{CL} = \frac{G}{1+T}$$

$$\omega_b G_{CL} = \cancel{(1+T)} \omega_b \frac{G}{\cancel{(1+T)}} = G \omega_b = \underline{\underline{GBW}}$$

Unity Gain Frequency

- The GBW product is also known as the unity gain frequency.
- To see this, consider the frequency at which the gain drops to unity

$$|G(\omega_t)| = \left| \frac{G_0}{1 + j \frac{\omega_t}{\omega_b}} \right| = 1$$

$$G_0 = \sqrt{1 + \left(\frac{\omega_t}{\omega_b}\right)^2}$$

$$G_0^2 - 1 = \left(\frac{\omega}{\omega_b}\right)^2$$

$$\omega = \omega_b \sqrt{G_0^2 - 1} \approx \underbrace{\omega_b G_0}_{\text{GBW}}$$


Unity Gain Feedback Amplifier

- An amplifier that has a feedback factor $f=1$, such as a unity gain buffer, has the full GBW product frequency range


$$\omega_b' = \omega_b (1 + T)$$

$$T = G f = G \quad f = 1$$
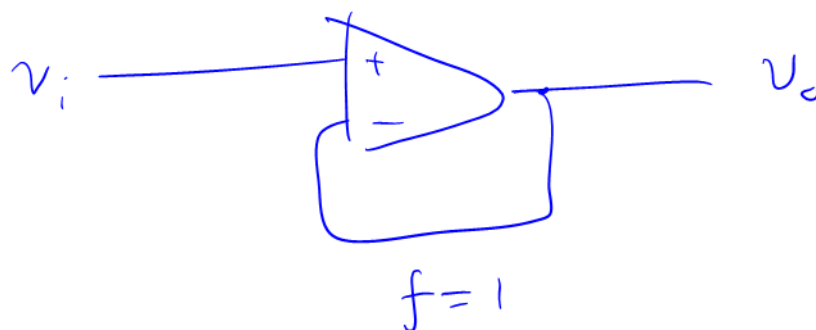
$$\omega_b' = \omega_b \cdot (1 + G) = \text{GBW!} \quad \text{Full BANDWIDTH!}$$



Closed-Loop Op Amp

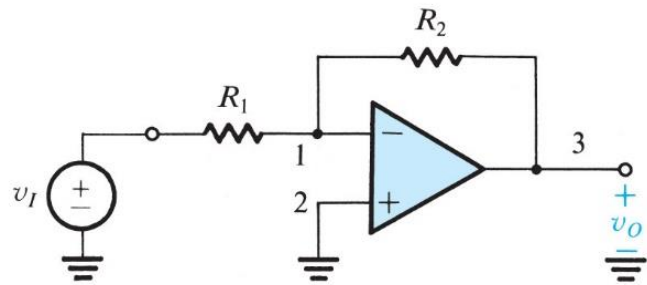

$$v_o = G(v^+ - v^-)$$

$$= G(0 - v^-) = -Gv^-$$

Say $i^- = i^+ = 0A$

$$\frac{v_i - v^-}{R_1} = \frac{v^- - v_o}{R_2}$$

$$v_i \frac{1}{R_1} = v^- \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{v_o}{R_2}$$

$$v_i = v^- \left(1 + \frac{R_1}{R_2} \right) - \frac{R_1}{R_2} v_o$$

$$= -\frac{v_o}{G} \left(1 + \frac{R_1}{R_2} \right) - \frac{R_1}{R_2} v_o = -v_o \left(\frac{R_1}{R_2} + \frac{1}{G} + \frac{R_1}{R_2} \frac{1}{G} \right)$$

$$\frac{v_o}{v_i} = \frac{-R_2/R_1}{\frac{1}{G} \frac{R_2}{R_1} + \left(\frac{1}{G} + 1 \right)} = \frac{-R_2/R_1}{\left(\frac{1 + j\omega/\omega_b}{G_0} + 1 \right) + \frac{R_2}{R_1} \frac{(1 + j\omega/\omega_b)}{G_0}}$$

$$\frac{V_o}{V_i} = \frac{-R_2/R_1}{\frac{1}{G} \frac{R_2}{R_1} + \left(\frac{1}{G} + 1\right)} = \frac{-R_2/R_1}{\left(\frac{1 + j\omega/\omega_b}{G_0} + 1\right) + \frac{R_2}{R_1} \frac{(1 + j\frac{\omega}{\omega_b})}{G_0}}$$

$$= \frac{-R_2/R_1 \cdot G_0}{1 + j\frac{\omega}{\omega_b} + G_0 + \frac{R_2}{R_1} (1 + j\frac{\omega}{\omega_b})} = \frac{-\frac{R_2}{R_1} G_0 / (1 + G_0 + \frac{R_2}{R_1})}{1 + j\frac{\omega}{\omega_b} \frac{(1 + \frac{R_2}{R_1})}{1 + G_0 + \frac{R_2}{R_1}}}$$

DC GAIN: $-\frac{R_2}{R_1} \frac{G_0}{1 + G_0 + \frac{R_2}{R_1}} \approx -\frac{R_2}{R_1}$

NEW BW: $\omega_b' = \omega_b \frac{(1 + G_0 + \frac{R_2}{R_1})}{1 + \frac{R_2}{R_1}}$

$\approx \frac{\omega_b G_0}{1 + \frac{R_2}{R_1}}$ EXPANSION FACTOR

Frequency Response of Closed-Loop Inverting Amplifier Example

$$f_b' = (1 + T) f_b$$


$$G_{CL} = \frac{G_o}{(1 + T)}$$

$$GBW = f_b' G_{CL} = (1 + T) f_b \times \frac{G_o}{(1 + T)} = f_b G_o$$

Same unity-gain frequency: f_t

GBW DROPS
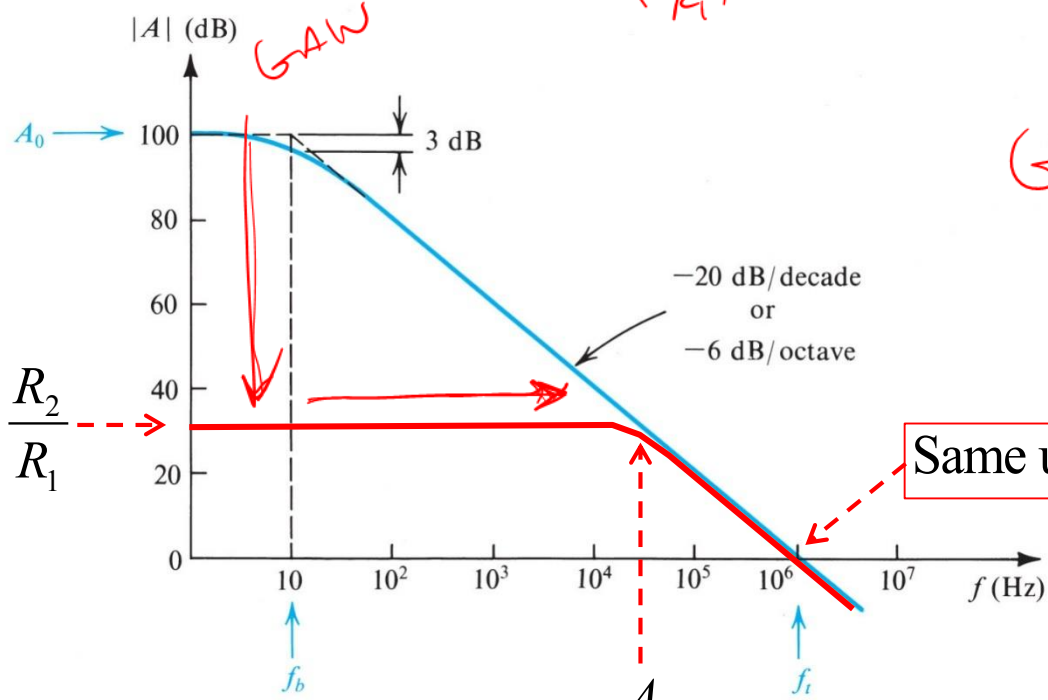
$$\frac{A_o}{\left(\frac{R_2}{R_1}\right)}$$



$$f_{3dB} \gg \frac{A_o}{R_2 / R_1} f_b$$

Non-Dominant Poles

- As we have seen, poles in the system tend to make an amplifier less stable. A single pole cannot do harm since it has a maximum phase shift of 90°
- A second pole in the system is not affected by feedback (prove this) and it will add phase shift as the frequency approaches this second pole
- For this reason, non-dominant poles should be at a much higher frequency than the unity-gain frequency

Positive Feedback


- Positive Feedback is also useful
- We can create a comparator circuit with *hysteresis*
- Also, as long as $T < 1$, we can get stable gain ... instead of reducing the gain (negative feedback), positive feedback enhances the gain.
- In theory we can boost the gain to any desired level simply by making T close to unity:

$$T = 1 - \epsilon$$

- ϵ is a very small number
 - In practice if the gain varies over process / temperature / voltage, then the circuit can go stable and oscillate
 - Positive feedback also has a narrow-banding effect

Back to Circuit Model

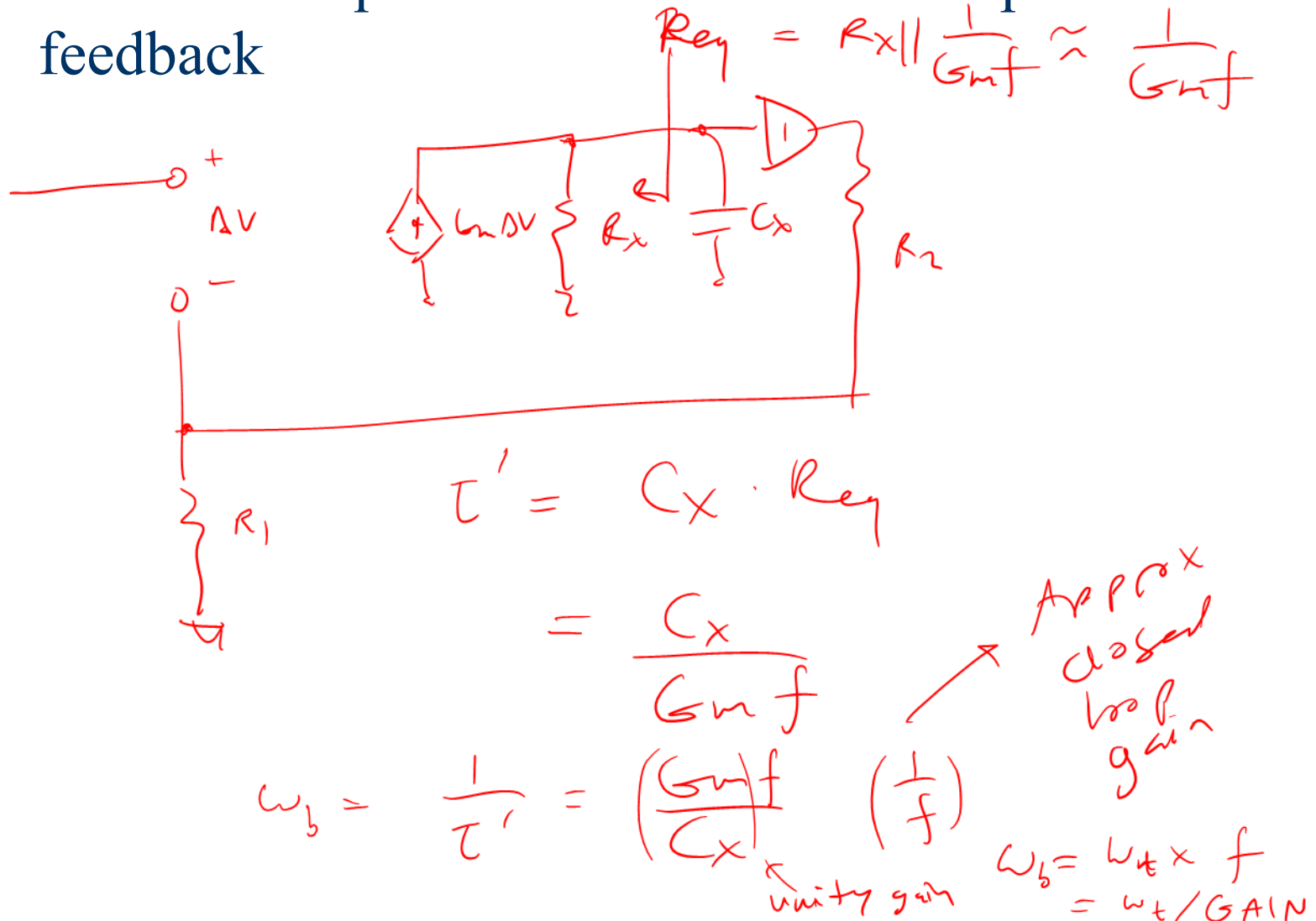- Here's the equivalent circuit for an amplifier with feedback



Circuit Interpretation

- Here we see the action of the feedback is to lower the impedance seen by the G_m by the loop gain, which expands the bandwidth by the same factor

Comment: This is advanced stuff
So don't worry if the
circuit interpretation is not
100% clear!