

Lecture 26

- Energy and Power
- Resistors in Series
- Real batteries
- Resistors in Parallel
- Example of Resistor Circuits
- Grounding

Energy and Power

- In battery: chemical energy \rightarrow potential...of charges: $\Delta U = q\Delta V_{bat} = q\mathcal{E}$
- power (rate at which energy supplied to charges): $P_{bat} = \frac{dU}{dt} = \frac{dq}{dt}\mathcal{E}$

$$P_{bat} = I\mathcal{E} \quad (\text{power delivered by an emf})$$

- In resistor: work done on charges $qEd \rightarrow$ kinetic (accelerate) between collisions \rightarrow thermal energy of lattice after collisions

After many collisions over length L of resistor:

$$\Delta E_{th} = qEL = q\Delta V_R$$

rate at which energy is transferred from current to resistor:


$$P_R = \frac{dE_{th}}{dt} = \frac{dq}{dt}\Delta V_R = I\Delta V_R$$

For basic circuit: $P_R = P_{bat}$ (energy conservation)

Using Ohm's law: $P_R = I\Delta V_R = I^2R = \frac{(\Delta V_R)^2}{R}$ (power dissipated by a resistor)

$$E_{chem} \rightarrow U \rightarrow K \rightarrow E_{th} \rightarrow \text{light}...$$

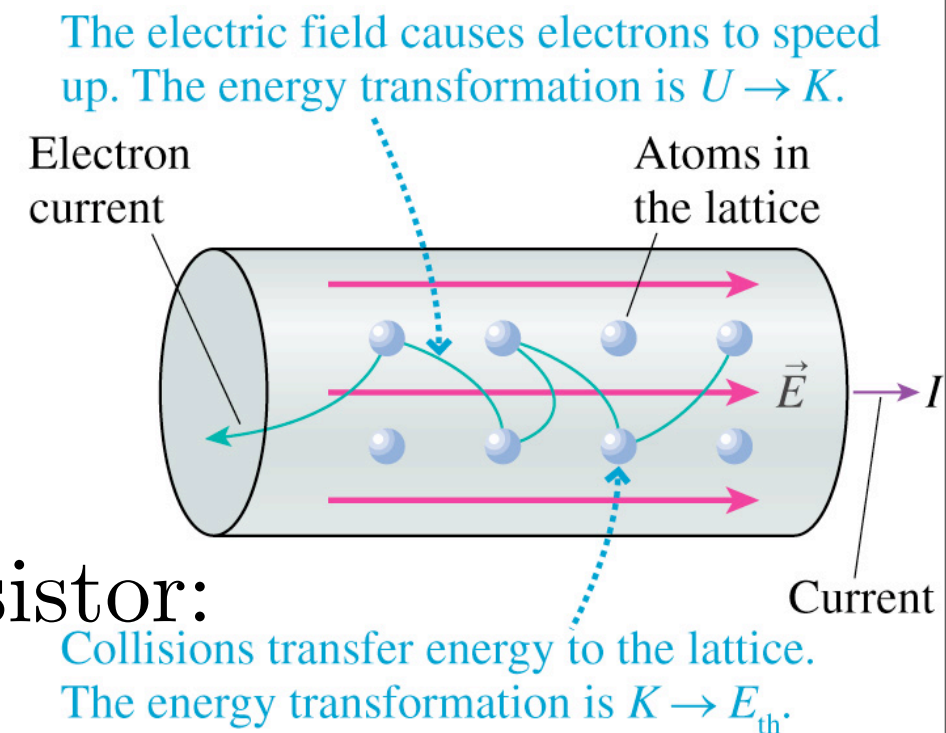- Common units: P_R kW in Δt hours $\rightarrow P_R\Delta t$ kilowatt hours




Copyright © 2004 Pearson Education, Inc., publishing as Addison Wesley

Example on electric power


- A standard 100 W (120 V) lightbulb contains a 9.00 cm-long tungsten filament. The high-temperature resistivity of tungsten is 9.0×10^{-7} ohm-meter. What is the diameter of the filament?

Resistors in Series

(a) Two resistors in series

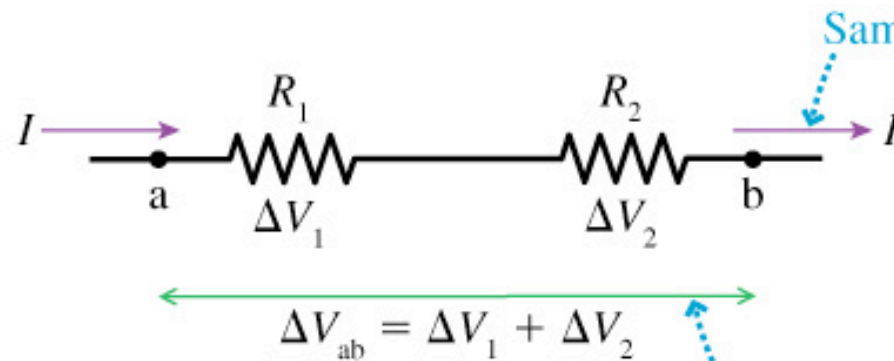

(b) An equivalent resistor

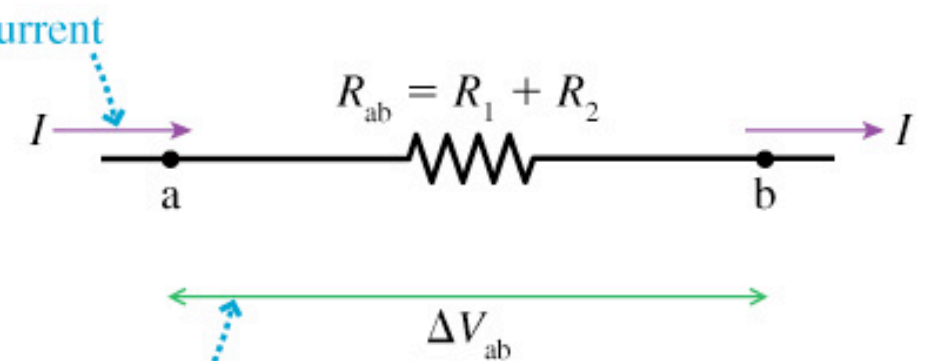

Same current

Same potential difference

- current same in each resistor: $\Delta V_1 = IR_1$; $\Delta V_2 = IR_2 \Rightarrow \Delta V_{ab} = I(R_1 + R_2)$
- equivalent resistor: $R_{ab} = \frac{\Delta V_{ab}}{I} = \frac{I(R_1 + R_2)}{I} = R_1 + R_2$

$$R_{eq} = R_1 + R_2 + \cdots + R_N \quad (\text{series resistors})$$

Ammeters

- measures current in circuit element (placed in series):


$$R_{eq} = R_{load} + R_{ammeter}$$

ideal, $R_{ammeter} = 0 \Rightarrow$ current not changed

(a)



(b)

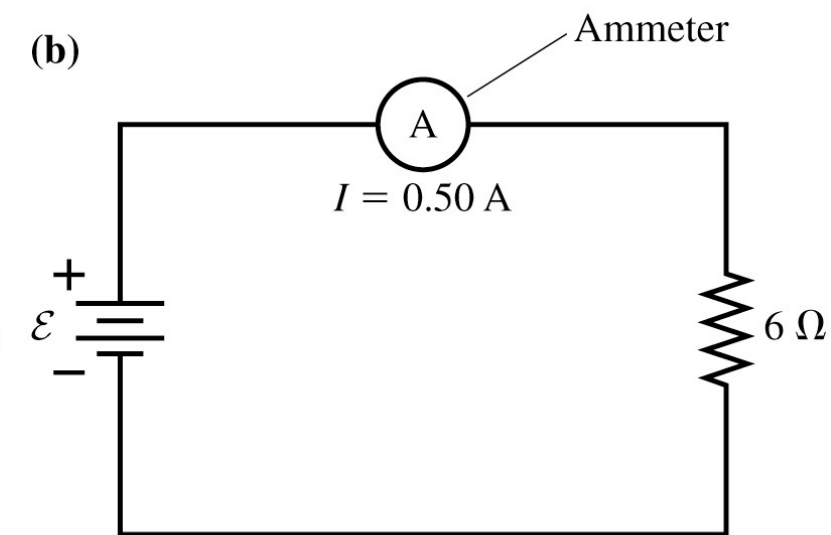

Real Batteries

- terminal (user) voltage

$$\Delta V_{bat} = \mathcal{E} - I r$$

- for resistor connected:

$$I = \frac{\mathcal{E}}{R_{eq}} = \frac{\mathcal{E}}{R + r}$$

$$\Delta V_R = I R = \frac{R}{R + r} \mathcal{E}$$


$$\Delta V_{bat} = \mathcal{E} - I r;$$

$$\Delta V_R = \Delta V_{bat} \neq \mathcal{E}$$

- replace high by zero resistance $\rightarrow I_{short} = \frac{\mathcal{E}}{r}$
(∞ for ideal, $r = 0$)

- maximum possible current battery can produce


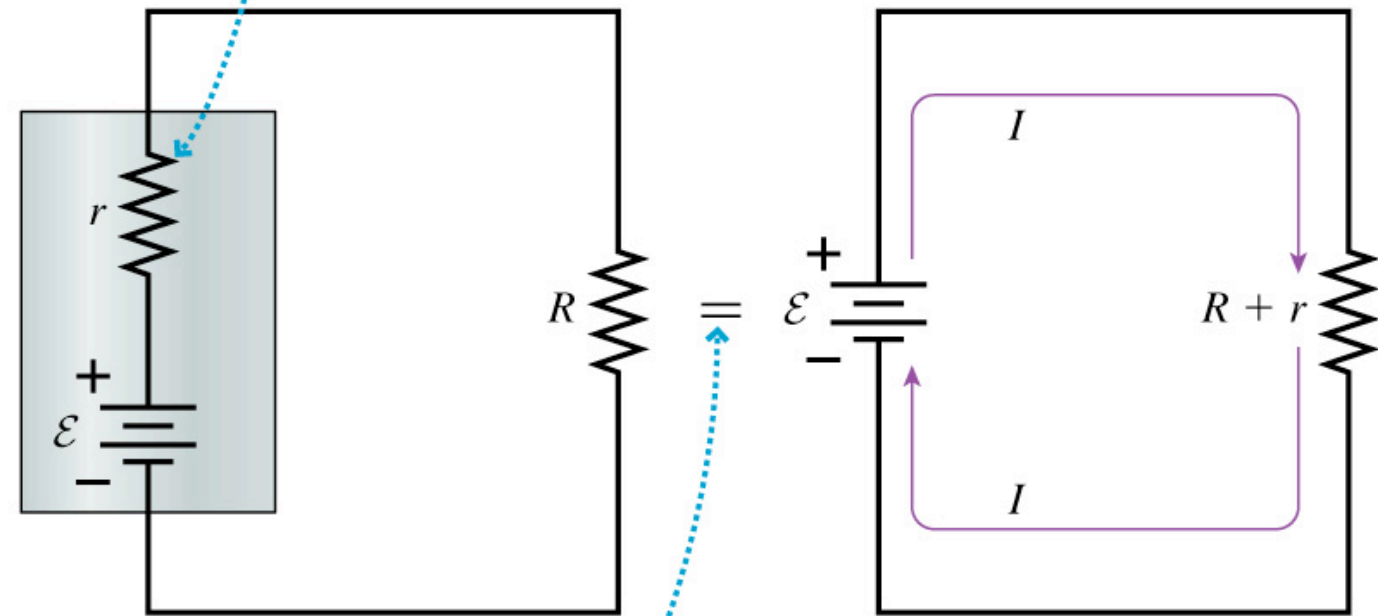
Although physically separated, the internal resistance r is electrically in series with R .




This means the two circuits are equivalent.

Short Circuit

This wire is shorting out the battery.

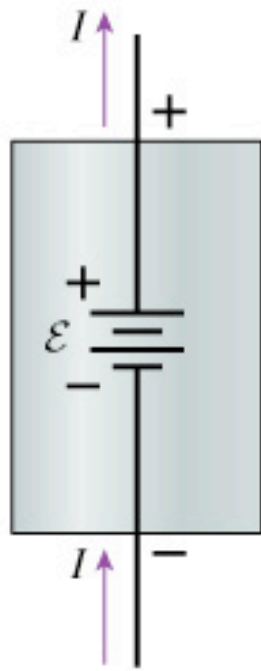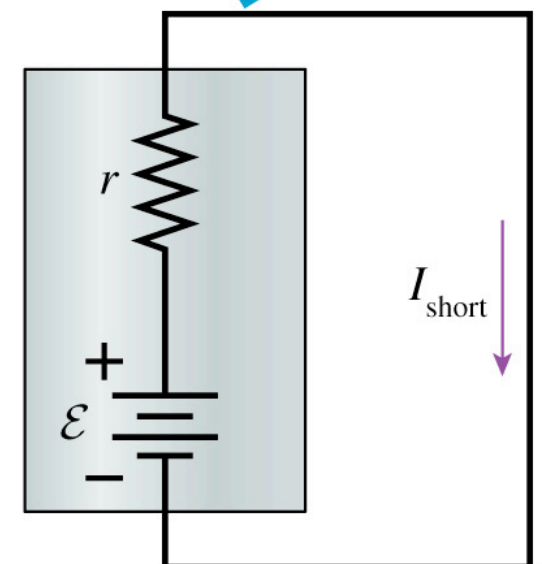

Ideal battery

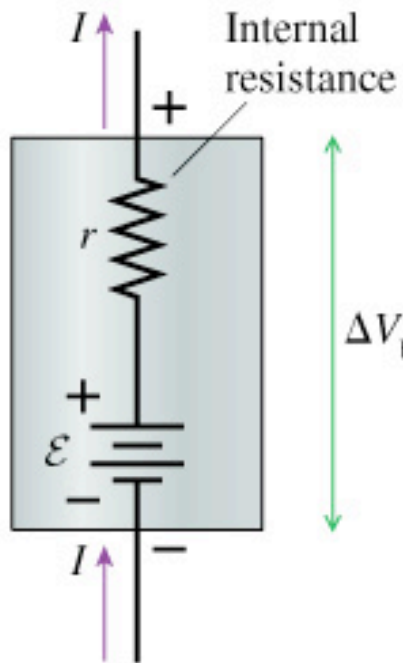

Real battery

Parallel Resistors

- potential differences same:

$$\Delta V_1 = \Delta V_2 = \dots = V_{cd}$$

- Kirchhoff's junction law: $I = I_1 + I_2$

- Ohm's law:

$$I = \frac{\Delta V_1}{R_1} + \frac{\Delta V_2}{R_2} = \Delta V_{cd} \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$


- Replace by equivalent resistance:

$$R_{cd} = \frac{\Delta V_{cd}}{I} = \left[\frac{1}{R_1} + \frac{1}{R_2} \right]^{-1}$$

$$R_{eq} = \left[\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N} \right]^{-1} \quad (\text{parallel resistors})$$

- Identical resistors ($R_1 = R_2$): $R_{series\ eq} = 2R$; $R_{parallel\ eq} = \frac{R}{2}$
- In general, $R_{eq} < R_1$ or R_2 ...in parallel

(a) Two resistors in parallel

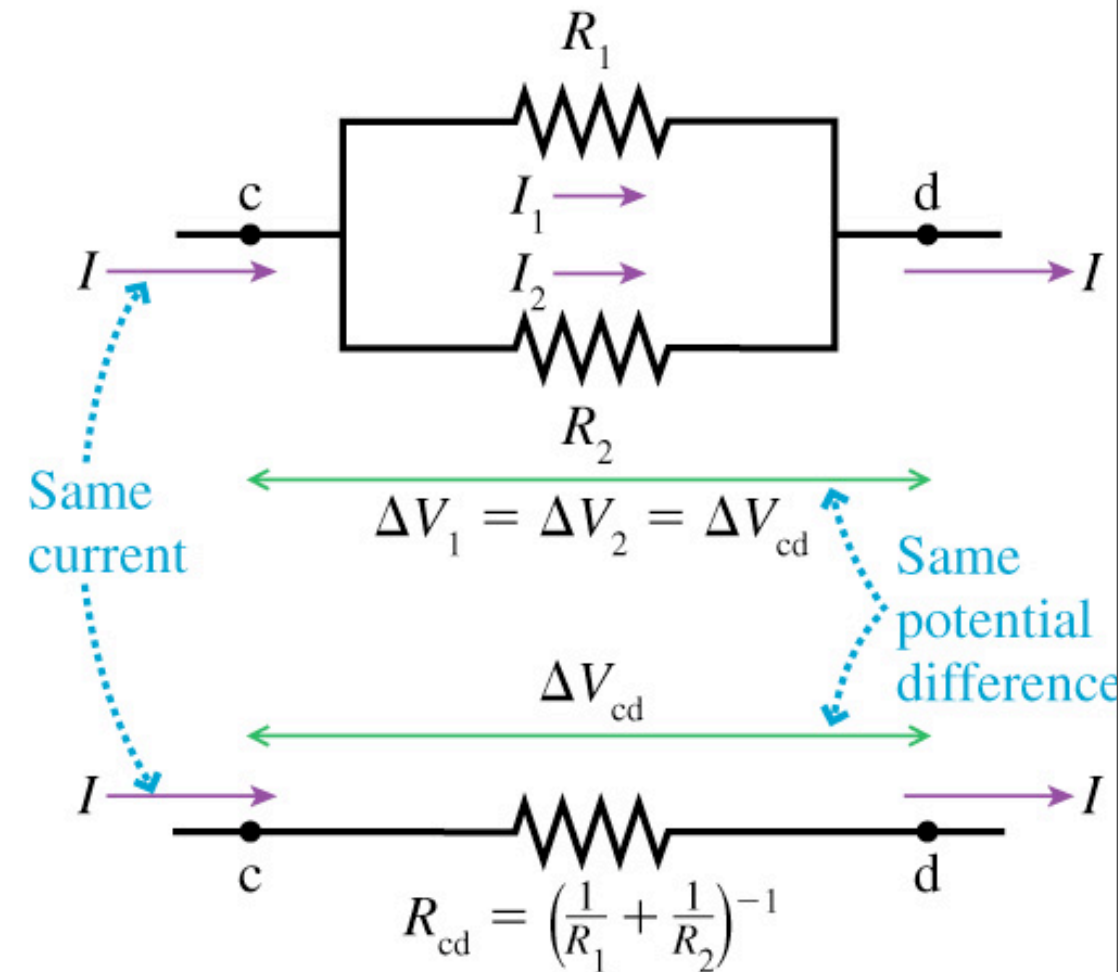

(b) An equivalent resistor

Copyright © 2004 Pearson Education, Inc., publishing as Addison Wesley

Voltmeters

- measure potential difference across circuit element (place in parallel; don't need to break connections, unlike for ammeter)



- total resistance: $R_{eq} = \frac{1}{R} + \frac{1}{R_{voltmeter}}$

- in order not to change voltage:

$$R_{voltmeter} \gg R \text{ (ideally, } \infty)$$


Strategy for Resistor Circuits

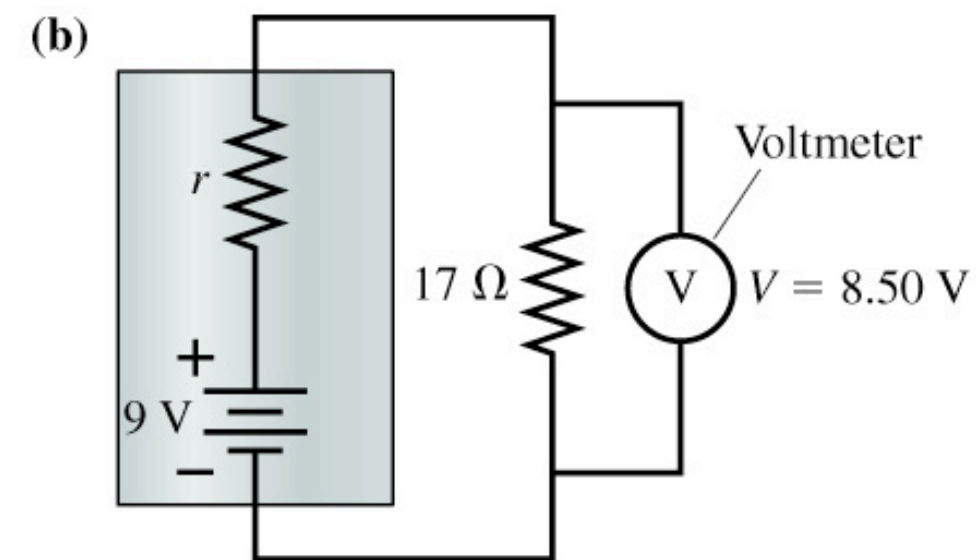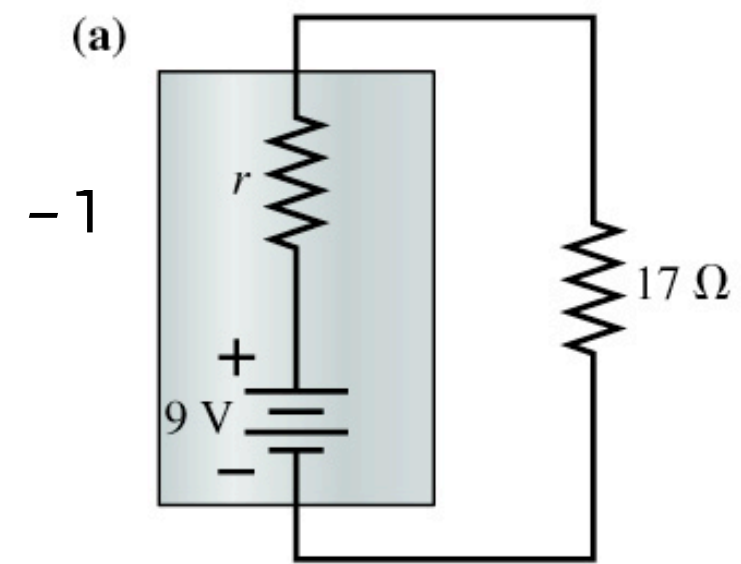- assume ideal wires, batteries
- use Kirchhoff's laws and rules for series and parallel resistors
- reduce to equivalent resistor (basic circuit)
- rebuild using current same for series and potential difference same for parallel




Example of Resistor Circuit


- Find I and ΔV for each resistor

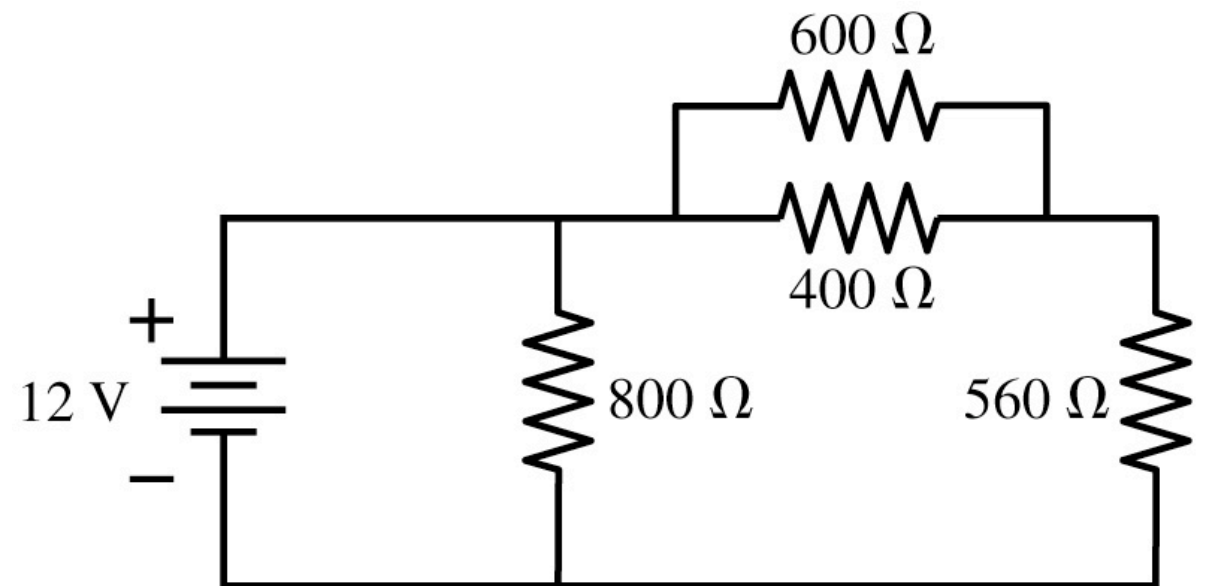

(a) Break down the circuit

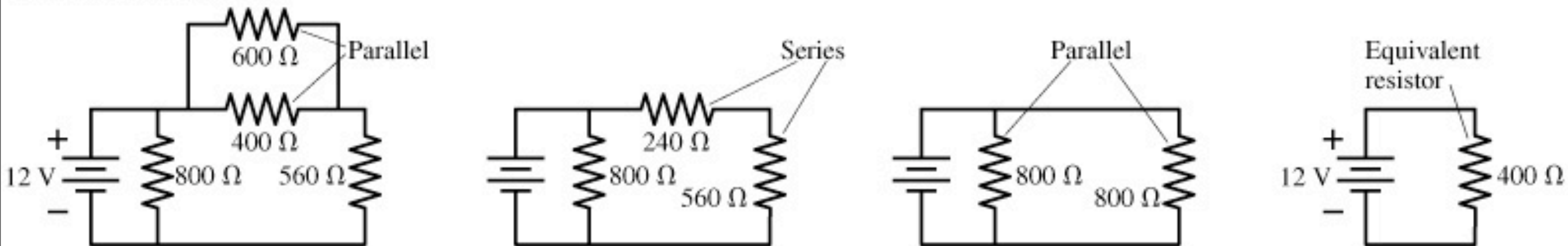


(b) Rebuild the circuit

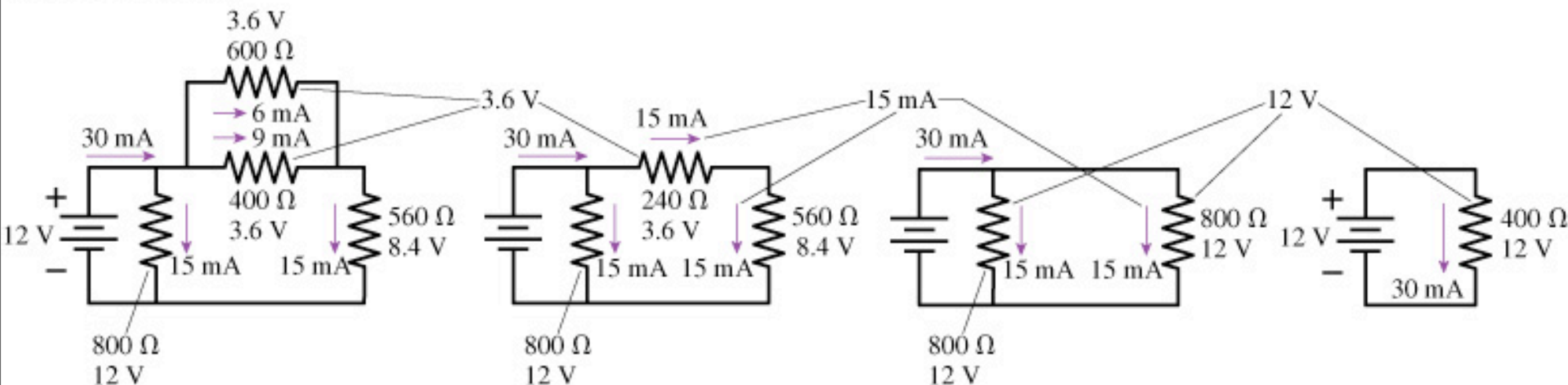

- so far, potential difference, ΔV (physically meaningful), enters Ohm's law (no need to establish zero point)
- need common reference point for connecting 2 circuits
- grounding: connect 1 point in circuit to earth ($V_{earth} = 0$) by ideal wire: no return wire (no current); wire is equipotential \rightarrow point in circuit has earth's potential \rightarrow specific value of potential at each point
- does not change how circuit functions... unless malfunction/breaking of circuit (enclose circuit in grounded case insulated from circuit): case comes in contact with circuit (\rightarrow touching would have caused electrocution) \rightarrow current thru' wire (fuse blows...)

Grounding

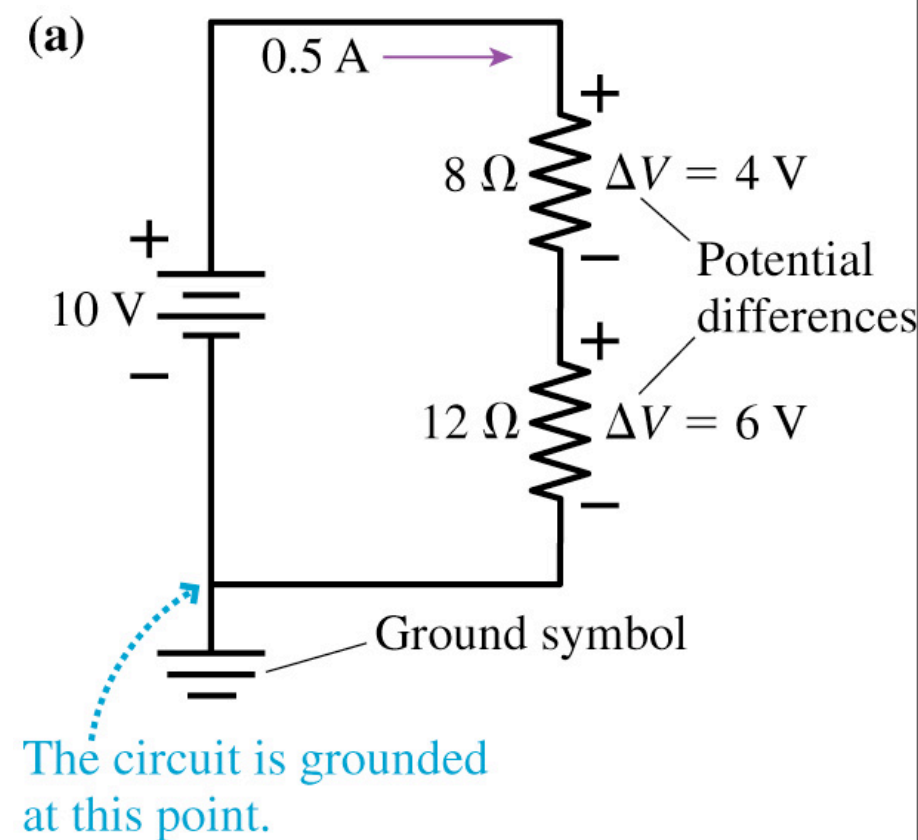

Copyright © 2004 Pearson Education, Inc., publishing as Addison Wesley

