

# EE 435

## Lecture 9:

### High-Gain Single-Stage Op Amps

- Regulated Folded Cascode Op Amp
- Current-mirror op amps
- OTA Applications


Textbook reference:

Some of the material we have been discussing appears in Chapter 3, some in Chapter 5, and some in Chapter 6 of the Martin and Johns text


In particular, the telescopic and folded cascode structures are referred to as advanced op amps and appear in later chapters of the text

Review from Last Time

# What circuit is this?

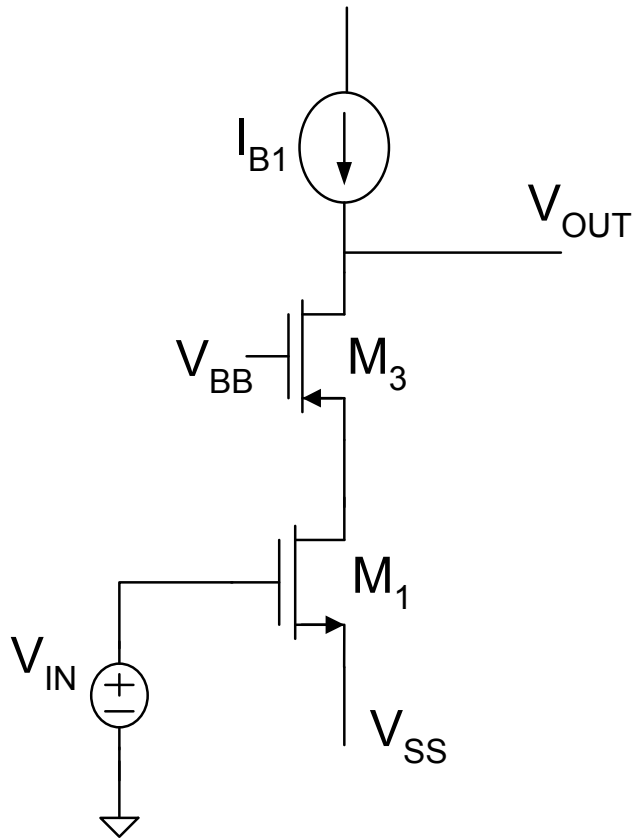


**Folded Cascode Amplifier**

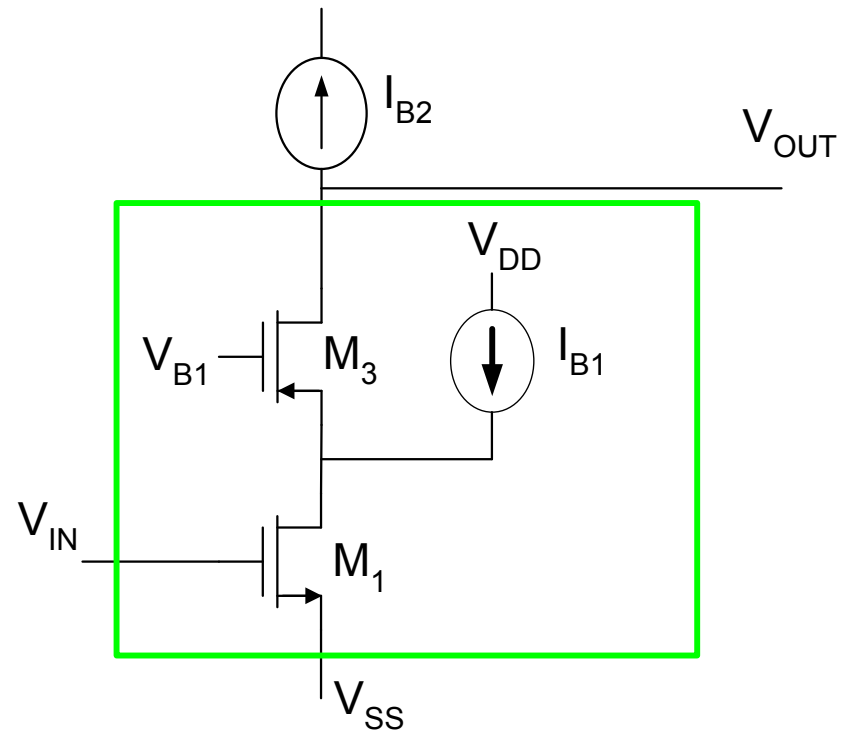

**Biased Folded Cascode**

# Folded Cascode Op Amp

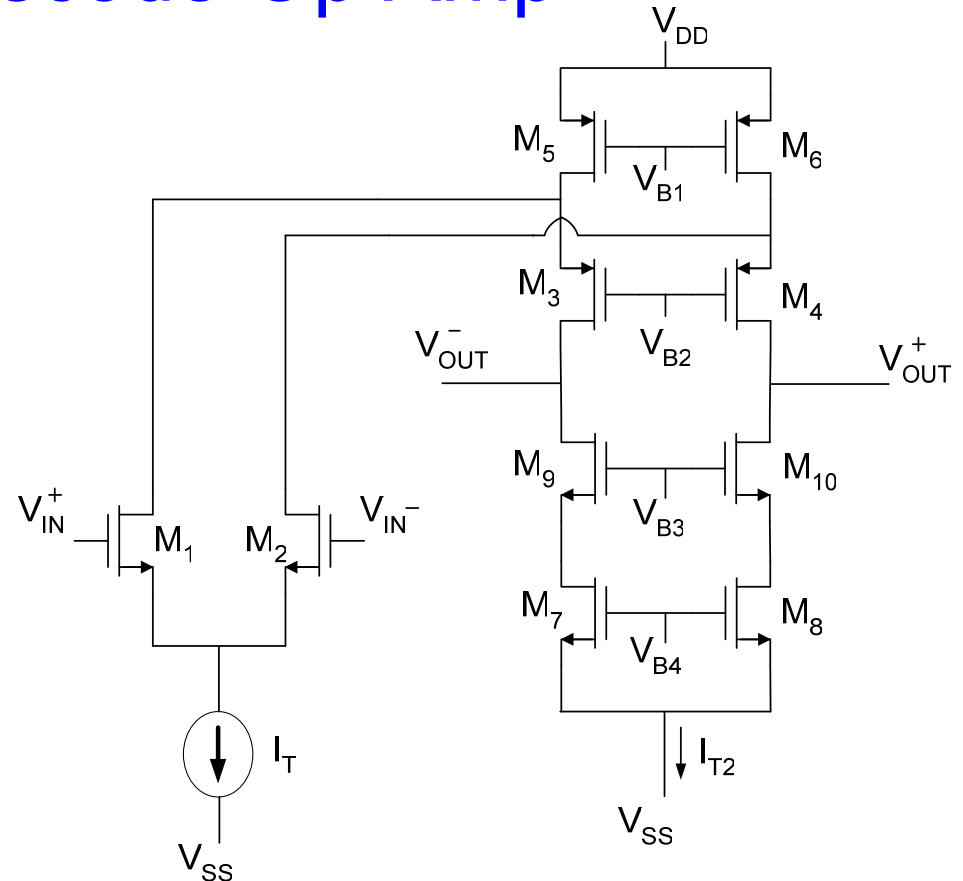


- Needs CMFB Circuit for  $V_{B4}$
- Either single-ended or differential outputs
- Can connect counterpart as current mirror to eliminate CMFB
- Folding caused modest deterioration of  $A_{v0}$  and GB energy efficiency
- Modest improvement in output swing

## Review from Last Time

# Folded Gain-boosted Telescopic Cascode Op Amp

$$A_o \approx \frac{-\frac{g_{m1}}{2}}{(g_{o1} + g_{o5}) \frac{g_{o3}}{A_3 g_{m3}} + g_{o7} \frac{g_{o9}}{A_1 g_{m9}}}$$

$$GB = \frac{g_{m1}}{2C_L}$$

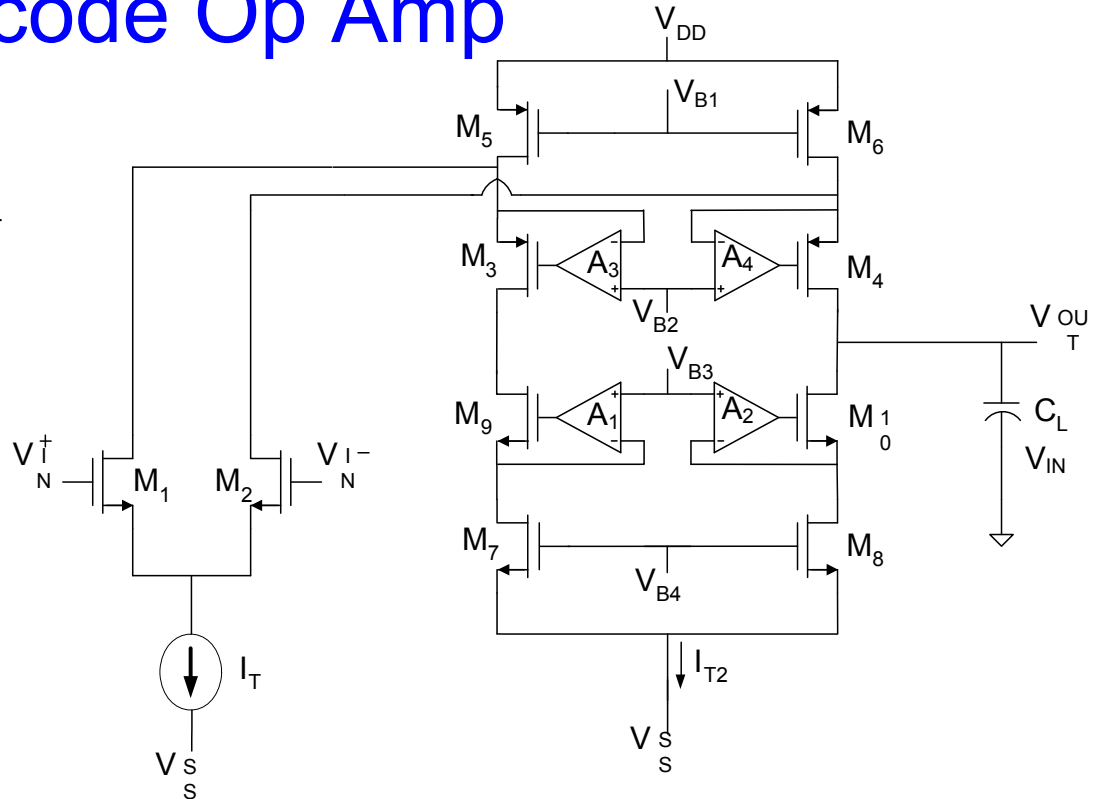

- Needs CMFB Circuit for  $V_{B4}$
- Either single-ended or differential outputs
- Can connect counterpart as current mirror to eliminate CMFB
- Folding caused modest deterioration in GB efficiency and gain
- Modest improvement in output swing

## Operational Amplifier Structure Comparison

Small Signal Parameter Domain			
Reference Op Amp	$A_{vo} = \frac{1}{2} \frac{g_{m1}}{g_{o1} + g_{o3}}$	$GB = \frac{g_{m1}}{2C_L}$	$SR = \frac{I_T}{2C_L}$
Telescopic Cascode	$A_o = \frac{\frac{g_{m1}}{2}}{g_{o1} \frac{g_{o3}}{g_{m3}} + g_{o7} \frac{g_{o5}}{g_{m5}}}$	$GB = \frac{g_{m1}}{2C_L}$	$SR = \frac{I_T}{2C_L}$
Regulated Cascode	$A_o \approx \frac{\frac{g_{m1}}{2}}{g_{o1} \frac{g_{o3}}{g_{m3} A_1} + g_{o7} \frac{g_{o9}}{g_{m9} A_3}}$	$GB = \frac{g_{m1}}{2C_L}$	$SR = \frac{I_T}{2C_L}$
Folded Cascode	$A_o = \frac{\frac{g_{m1}}{2}}{(g_{o1} + g_{o5}) \frac{g_{o3}}{g_{m3}} + g_{o7} \frac{g_{o9}}{g_{m9}}}$	$GB = \frac{g_{m1}}{2C_L}$	$SR = \frac{I_T}{2C_L}$
Folded Regulated Cascode	$A_o = \frac{\frac{g_{m1}}{2}}{(g_{o1} + g_{o5}) \frac{g_{o3}}{g_{m3} A_3} + g_{o7} \frac{g_{o9}}{g_{m9} A_9}}$	$GB = \frac{g_{m1}}{2C_L}$	$SR = \frac{I_T}{2C_L}$


## Summary of Folded Amplifier Performance

- + Modest improvement in output signal swing (from  $5 V_{DS SAT}$  to  $4V_{DS SAT}$ )
- - Deterioration in  $A_{V0}$  (maybe 30% or more)
- - Deterioration in GB power efficiency (can be significant)
- - Minor increase in circuit size

# Folded Gain-boosted Cascode Amplifier

$$A_o \approx \frac{-g_{m1}}{(g_{o1}) \frac{g_{o3}}{A g_{m3}}}$$

$$GB = \frac{g_{m1}}{2C_L}$$

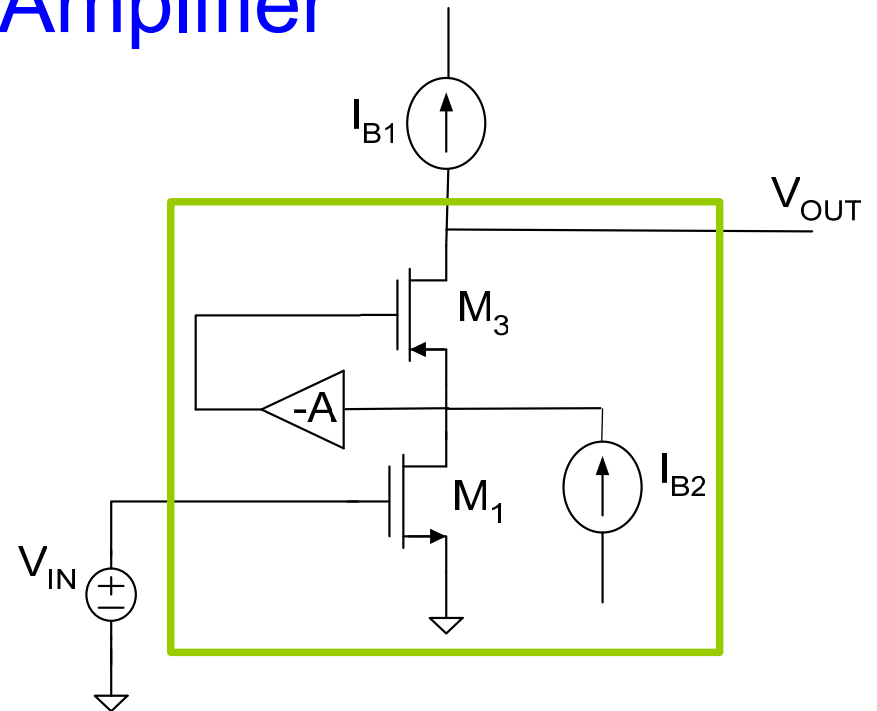

- with ideal current source bias
- modest improvement in output swing




# Folded Gain-boosted Cascode Amplifier

$$\frac{V_{OUT}}{V_{IN}} \approx \frac{-g_{m1}}{sC_L + \frac{(g_{o1} + g_{o5})g_{o3}}{g_{m3}A}}$$

$$A_0 \approx \frac{-g_{m1}g_{m3}A}{(g_{o1} + g_{o5})g_{o3}}$$

$$GB = \frac{g_{m1}}{C_L}$$

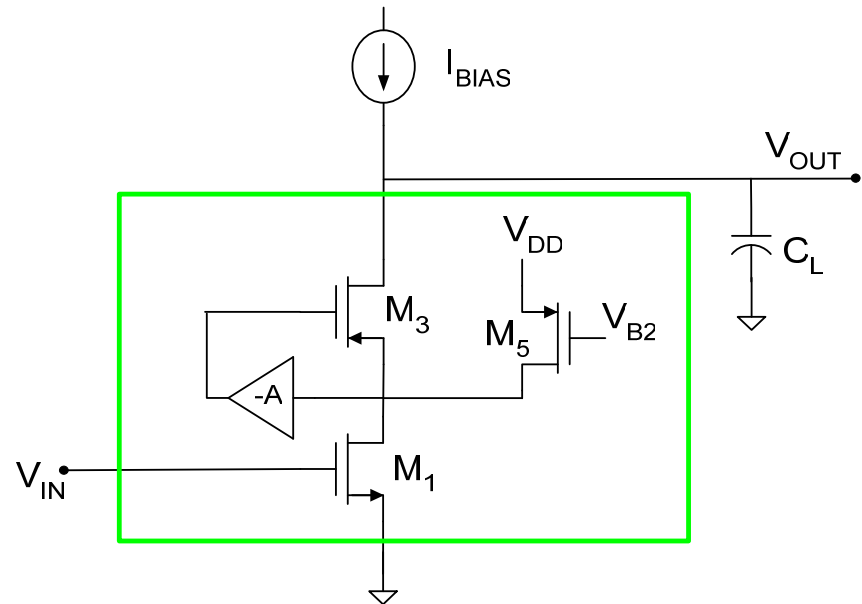

modest improvement in output swing

# Basic Amplifier Structure Comparisons

Small Signal Parameter Domain		
Common Source	$A_{VO} = \frac{g_m}{g_o}$	$GB = \frac{g_m}{C_L}$
Cascode	$A_{VO} = \frac{g_{m1} g_{m3}}{g_{o1} g_{o3}}$	$GB = \frac{g_{m1}}{C_L}$
Regulated Cascode	$A_{VO} \approx \frac{g_{m1} g_{m3}}{g_{o1} g_{o3}} A$	$GB = \frac{g_{m1}}{C_L}$
Folded Cascode	$A_{VO} = \frac{g_{m1}}{(g_{o1} + g_{o5})} \frac{g_{m3}}{g_{o3}}$	$GB = \frac{g_{m1}}{C_L}$
Folded Regulated Cascode	$A_{VO} = \frac{g_{m1}}{(g_{o1} + g_{o5})} \frac{g_{m3}}{g_{o3}} A$	$GB = \frac{g_{m1}}{C_L}$

# Basic Amplifier Structure Comparisons


## Practical Parameter Domain

Common Source	$A_{VO} = \left( \frac{2}{\lambda} \right) \left( \frac{1}{V_{EB}} \right)$	$GB = \left( \frac{2P}{V_{DD} C_L} \right) \left( \frac{1}{V_{EB}} \right)$
Cascode	$A_{VO} = \left( \frac{4}{\lambda_1 \lambda_3} \right) \left( \frac{1}{V_{EB1} V_{EB3}} \right)$	$GB = \left( \frac{2P}{V_{DD} C_L} \right) \left( \frac{1}{V_{EB1}} \right)$
Regulated Cascode $\Theta$ =pct power in A	$A_{VO} \approx \left( \frac{4}{\lambda_1 \lambda_3} \right) \left( \frac{A}{V_{EB1} V_{EB3}} \right)$	$GB = \left( \frac{2P}{V_{DD} C_L} \right) \left( \frac{(1-\Theta)}{V_{EB1}} \right)$
Folded Cascode $\Theta$ =fraction of current of $M_5$ that is in $M_1$	$A_{VO} \approx \left( \frac{4\theta}{(\theta\lambda_1 + \lambda_5)\lambda_3 V_{EB1} V_{EB3}} \right)$	$GB = \left( \frac{2P}{V_{DD} C_L} \right) \left[ \frac{\theta}{V_{EB1}} \right]$
Folded Regulated Cascode $\Theta_1$ =pct of total power in A $\Theta_2$ =fraction of current of $M_5$ that is in $M_1$	$A_{VO} \approx \left( \frac{A4\theta_2}{(\theta_2\lambda_1 + \lambda_5)\lambda_3 V_{EB1} V_{EB3}} \right)$	$GB = \left( \frac{2P}{V_{DD} C_L} \right) \left( \frac{\theta_2(1-\theta_1)}{V_{EB1}} \right)$

# Folded Gain-boosted Telescopic Cascode Op Amp

$$A_o \approx \frac{-\frac{g_{m1}}{2}}{(g_{o1} + g_{o5}) \frac{g_{o3}}{A_3 g_{m3}} + g_{o7} \frac{g_{o9}}{A_1 g_{m9}}}$$

$$GB = \frac{g_{m1}}{2C_L}$$

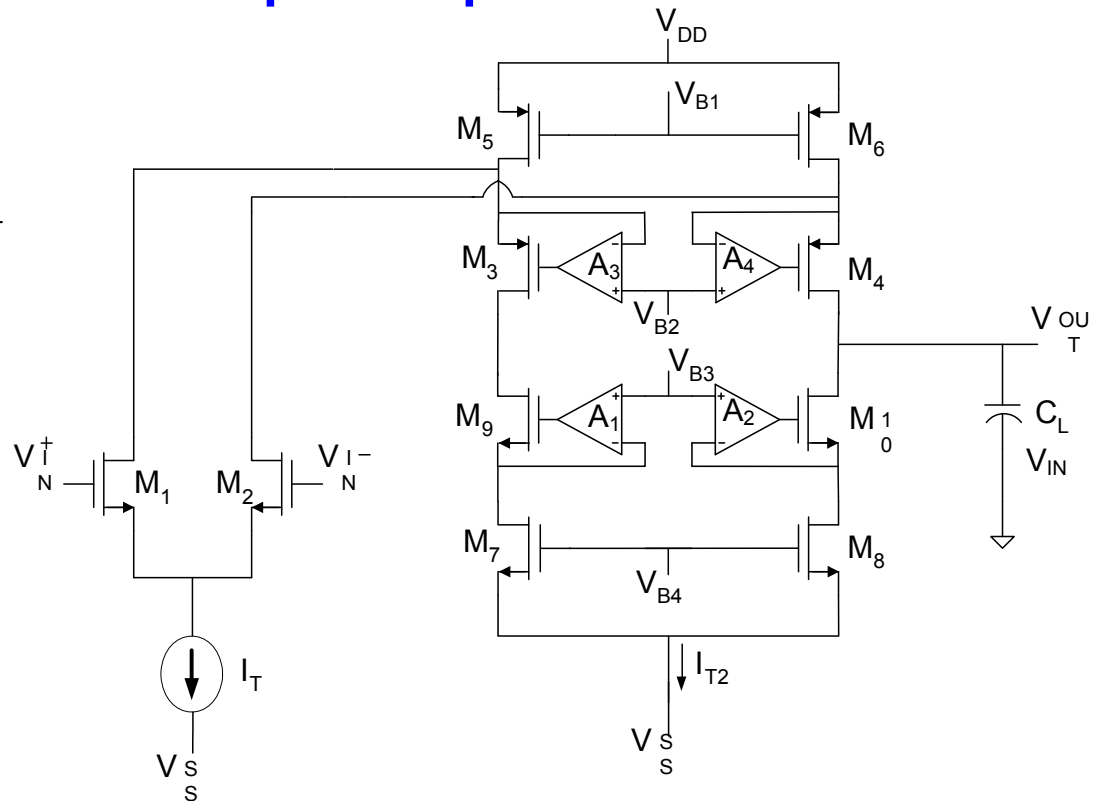

- Needs CMFB Circuit for  $V_{B4}$
- Either single-ended or differential outputs
- Can connect counterpart as current mirror to eliminate CMFB
- Folding caused modest deterioration in GB efficiency and gain
- Modest improvement in output swing

# Operational Amplifier Structure Comparison


Small Signal Parameter Domain			
Reference Op Amp	$A_{vo} = \frac{1}{2} \frac{g_{m1}}{g_{o1} + g_{o3}}$	$GB = \frac{g_{m1}}{2C_L}$	$SR = \frac{I_T}{2C_L}$
Telescopic Cascode	$A_o = \frac{\frac{g_{m1}}{2}}{g_{o1} \frac{g_{o3}}{g_{m3}} + g_{o7} \frac{g_{o5}}{g_{m5}}}$	$GB = \frac{g_{m1}}{2C_L}$	$SR = \frac{I_T}{2C_L}$
Regulated Cascode	$A_o \approx \frac{\frac{g_{m1}}{2}}{g_{o1} \frac{g_{o3}}{g_{m3} A_1} + g_{o7} \frac{g_{o9}}{g_{m9} A_3}}$	$GB = \frac{g_{m1}}{2C_L}$	$SR = \frac{I_T}{2C_L}$
Folded Cascode	$A_o = \frac{\frac{g_{m1}}{2}}{(g_{o1} + g_{o5}) \frac{g_{o3}}{g_{m3}} + g_{o7} \frac{g_{o9}}{g_{m9}}}$	$GB = \frac{g_{m1}}{2C_L}$	$SR = \frac{I_T}{2C_L}$
Folded Regulated Cascode	$A_o = \frac{\frac{g_{m1}}{2}}{(g_{o1} + g_{o5}) \frac{g_{o3}}{g_{m3} A_3} + g_{o7} \frac{g_{o9}}{g_{m9} A_9}}$	$GB = \frac{g_{m1}}{2C_L}$	$SR = \frac{I_T}{2C_L}$

# Summary of Folded Amplifier Performance

- + Modest improvement in output signal swing (from  $5 V_{DS SAT}$  to  $4V_{DS SAT}$ )
- - Deterioration in  $A_{V0}$  (maybe 30% or more)
- - Deterioration in GB power efficiency (can be significant)
- - Minor increase in circuit size

# Other Methods of Gain Enhancement

Recall:

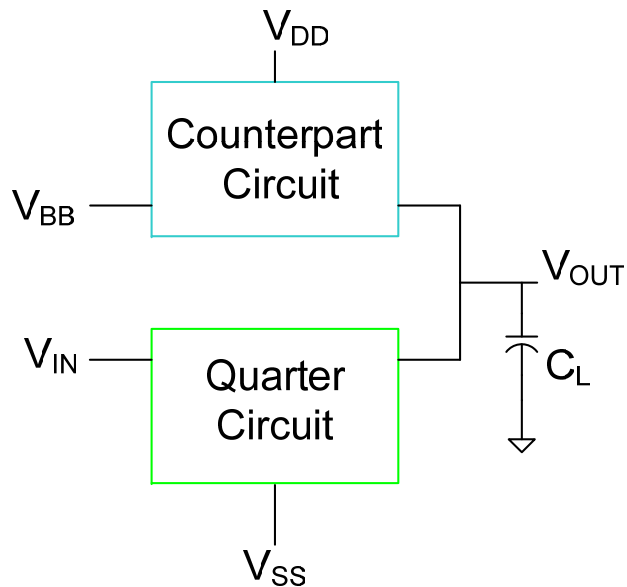

$$A_{V0} = \frac{-g_{mQC}}{g_{oQC} + g_{oCC}}$$

$$GB = \frac{g_{mQC}}{C_L}$$


Two Strategies:

1. Decrease denominator of  $A_{V0}$
2. Increase numerator of  $A_{V0}$

Previous approaches focused on decreasing denominator

**Consider now increasing numerator**

# $g_{mEQ}$ Gain Enhancement Strategy

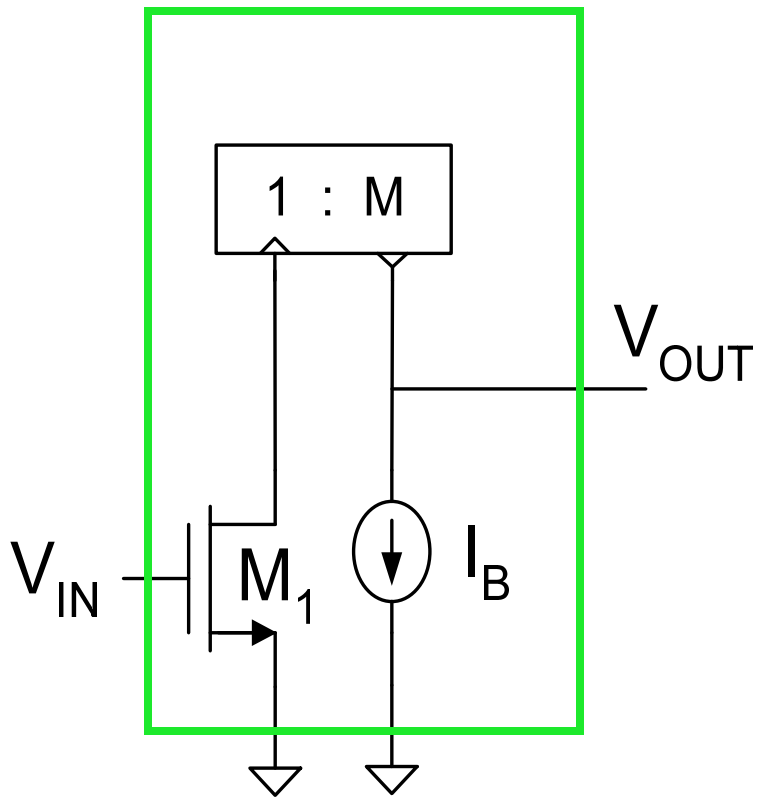

$$g_{MQC} = g_{m1} M$$


$g_m$  is increased by the mirror gain !

use the quarter circuit itself to form the op amp


Use this as a quarter circuit



# $g_{mEQ}$ Gain Enhancement Strategy

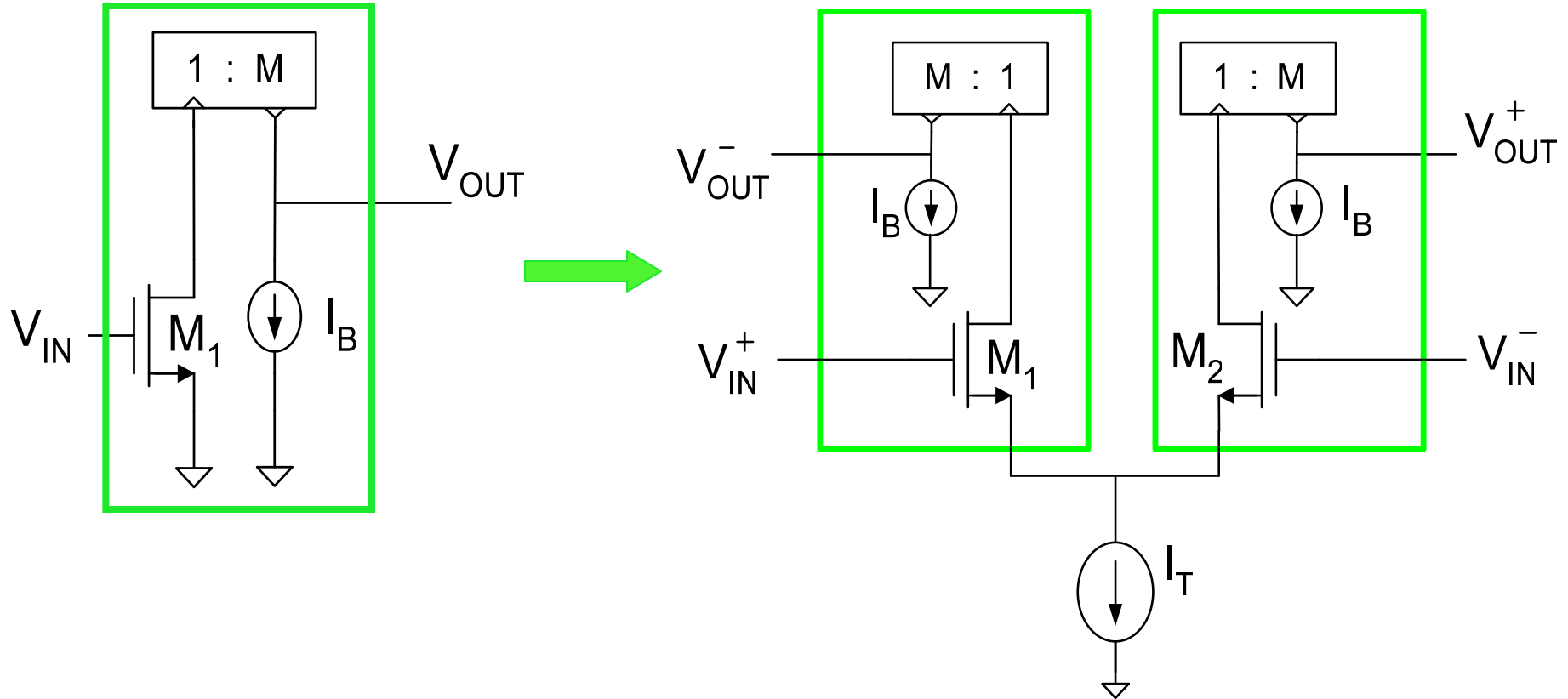

# Current Mirror Op Amps

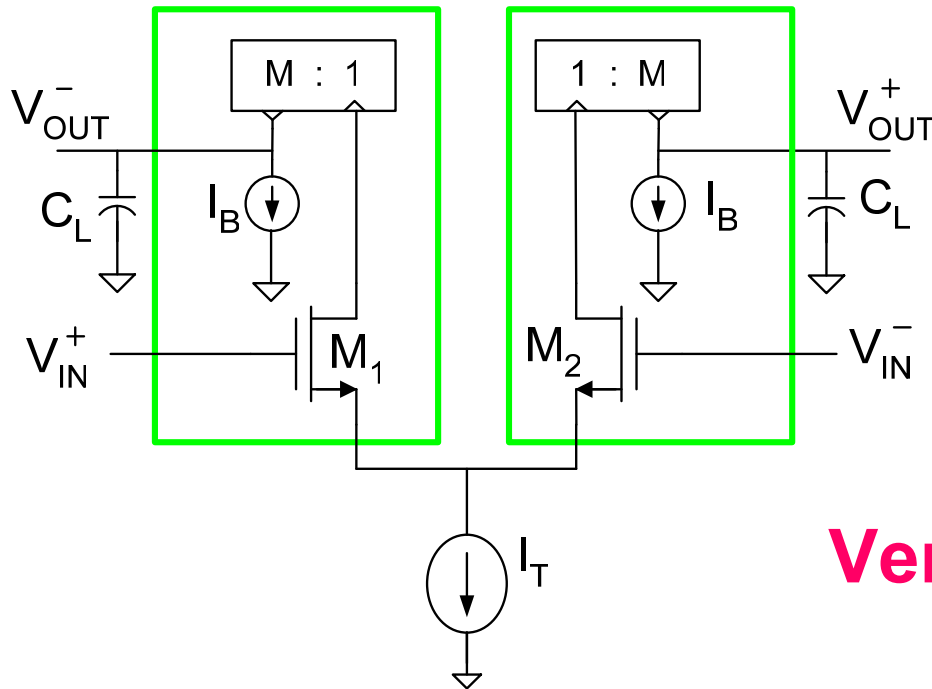

**Very Simple Structure!**

Premise: Transconductance gain increased by mirror gain  $M$

$$g_{mEQ} = M \frac{g_{m1}}{2}$$

Premise: If output conductance is small, gain can be very high



$$A_{V0} = - \frac{g_{mEQ}}{g_{oEQ}}$$

Premise: GB very good as well

Still need to generate the bias current  $I_B$

$$GB = \frac{g_{mEQ}}{C_L}$$

# Current Mirror Op Amps

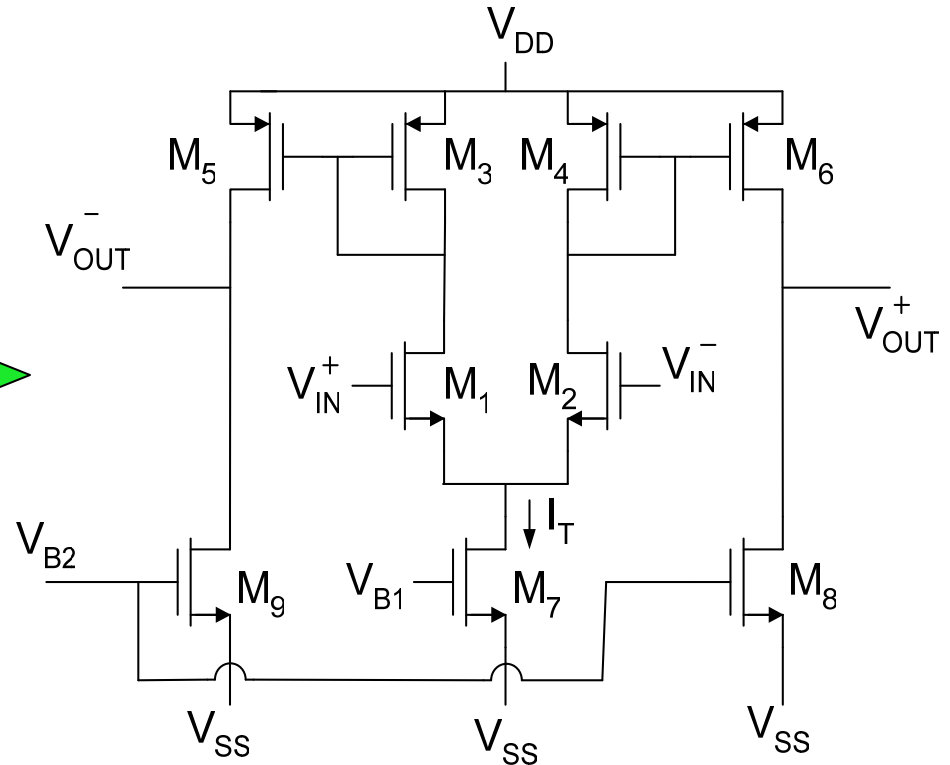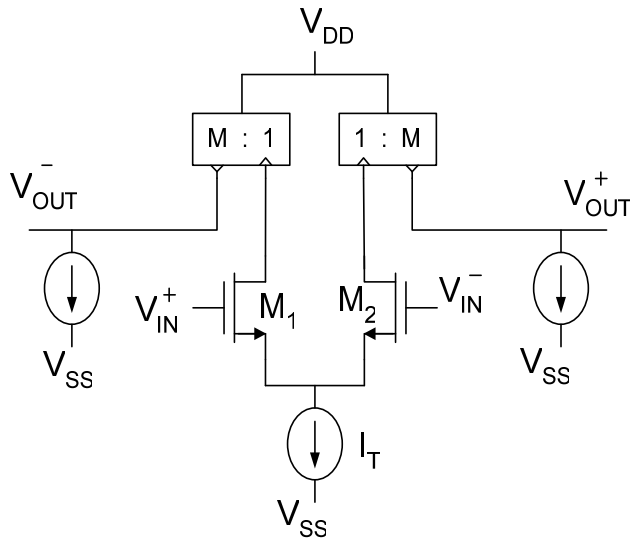

Need CMFB to establish  $V_{B2}$

**Basic Current Mirror Op Amp**


Can use higher output impedance current mirrors

Can use current mirror bias to eliminate CMFB but lose one output

Is this a real clever solution?



# Basic Current Mirror Op Amp

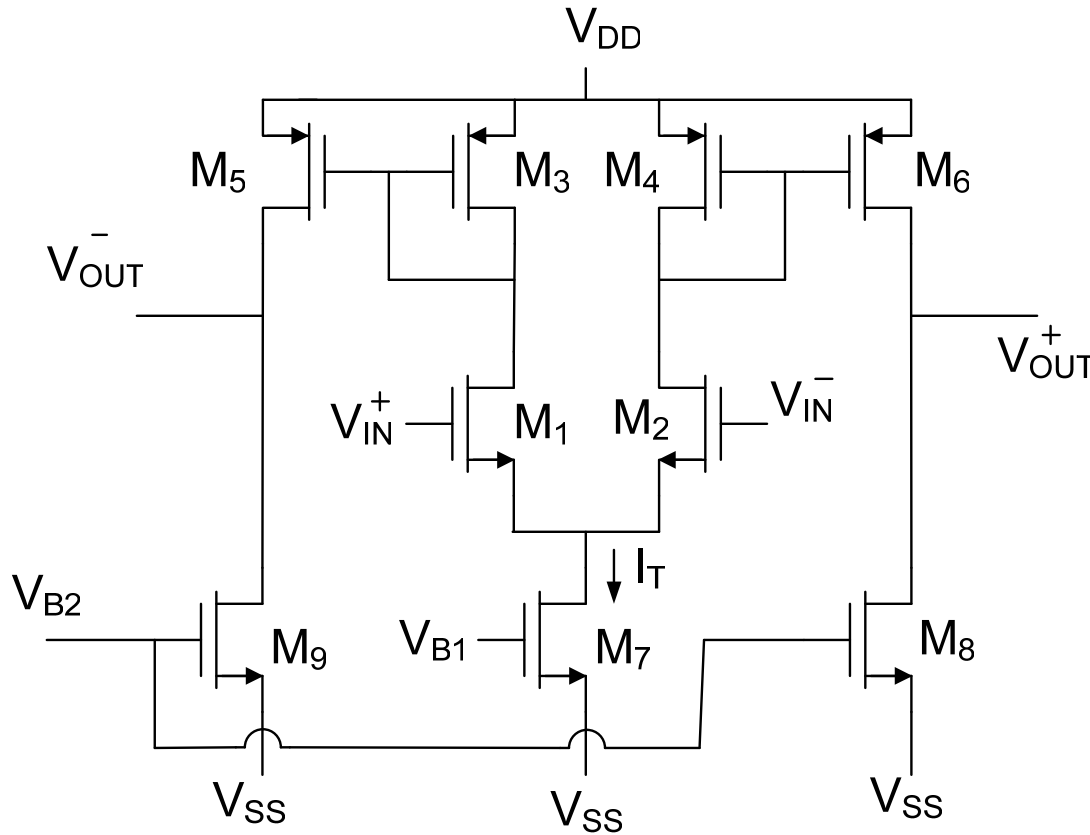

CMFB not shown

$$g_{mEQ} = M \frac{g_{m1}}{2}$$

$$g_{OEQ} = g_{O6} + g_{O8}$$

$$GB = M \frac{g_{m1}}{2C_L}$$

$$A_{VO} = - \frac{M \cdot \frac{g_{m1}}{2}}{g_{O6} + g_{O8}}$$

$$SR = \frac{M \cdot I_T}{2C_L}$$

- Current-Mirror Op Amp offers strategy for  $g_m$  enhancement
- Very Simple Structure
- Has applications as an OTA
- But – how good are the properties of the CMOA?

Is this a real clever solution?



# Seminal Work on the OTA



## **OTA Obsoletes Op Amp**

by C.F. Wheatley  
H.A. Wittlinger

From:

N.E.C. PROCEEDINGS

# Seminal Work on the OTA



## **OTA Obsoletes Op Amp**


by C.F. Wheatley  
H.A. Wittlinger

From:

1969 N.E.C. PROCEEDINGS  
December 1969



# Original OTA

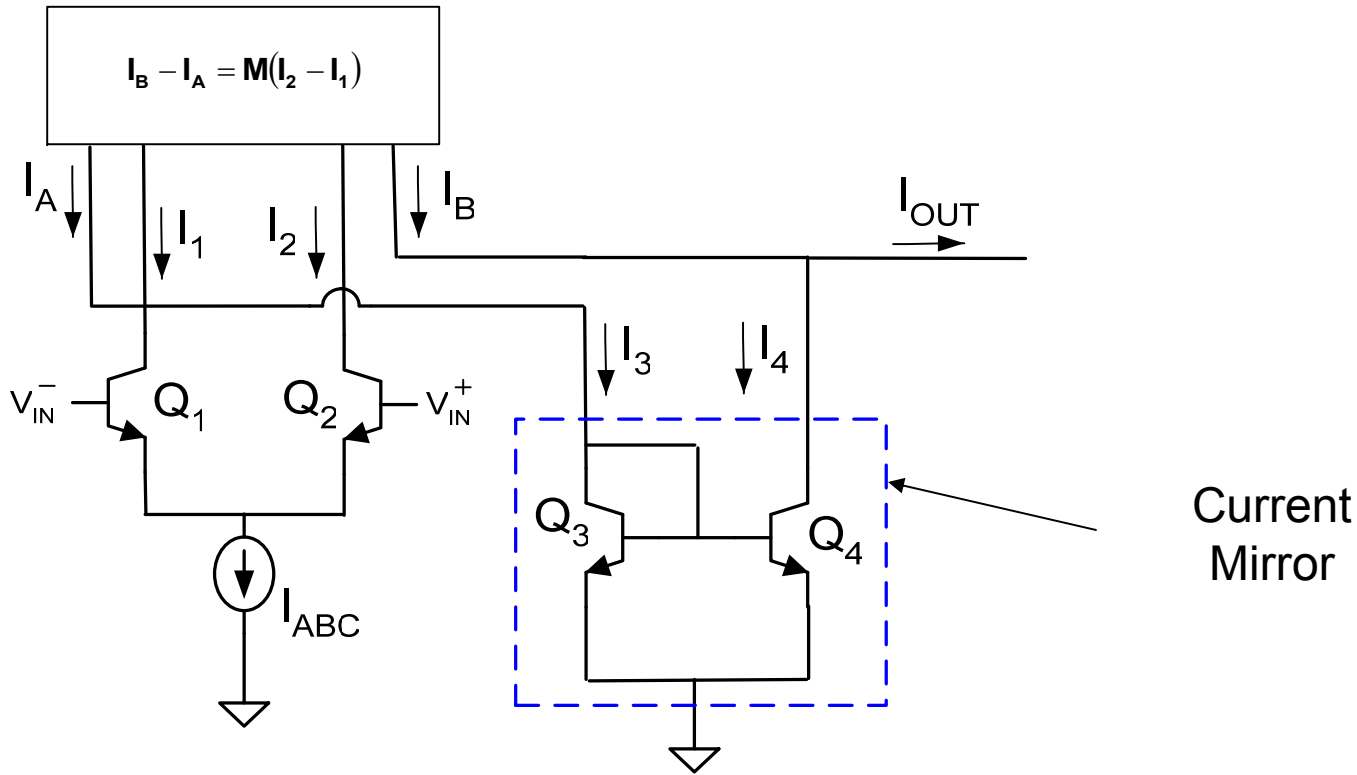


$$I_A = I_3$$

$$I_B = I_{OUT} + I_4 \quad \longrightarrow \quad I_{OUT} = M(I_B - I_A)$$


$$I_4 = I_3$$

# Original OTA

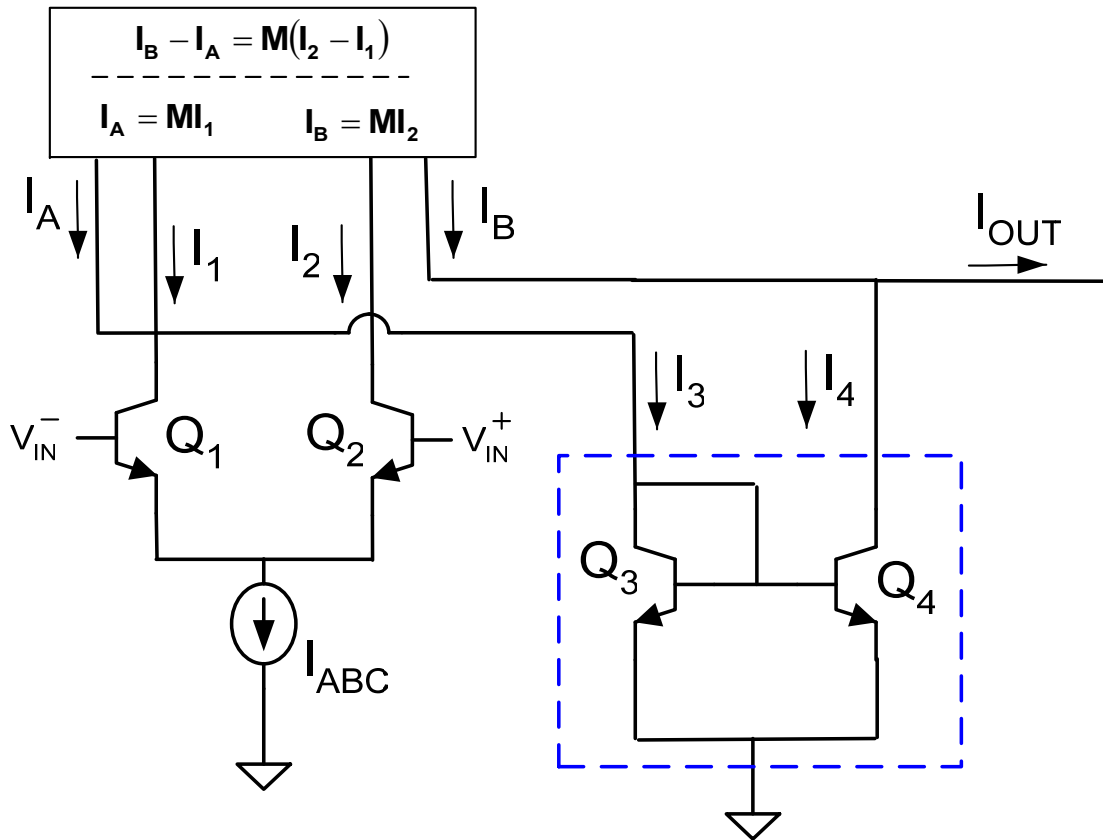


$$I_{OUT} = M(I_B - I_A)$$

# Original OTA

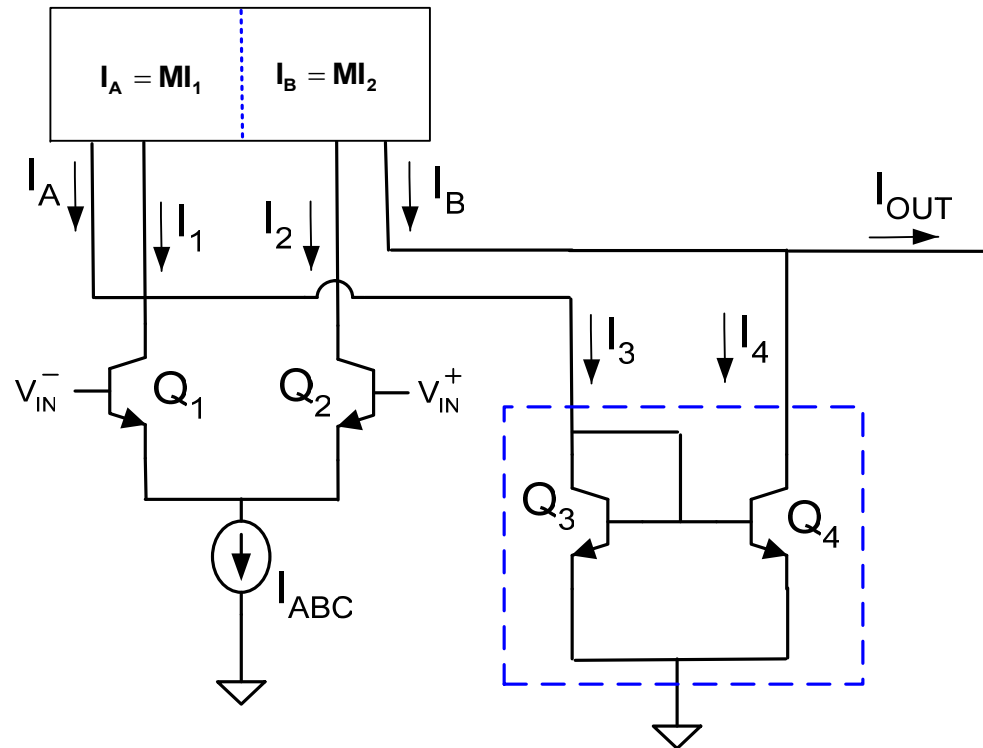

$$I_{OUT} = M(I_B - I_A)$$


# Original OTA

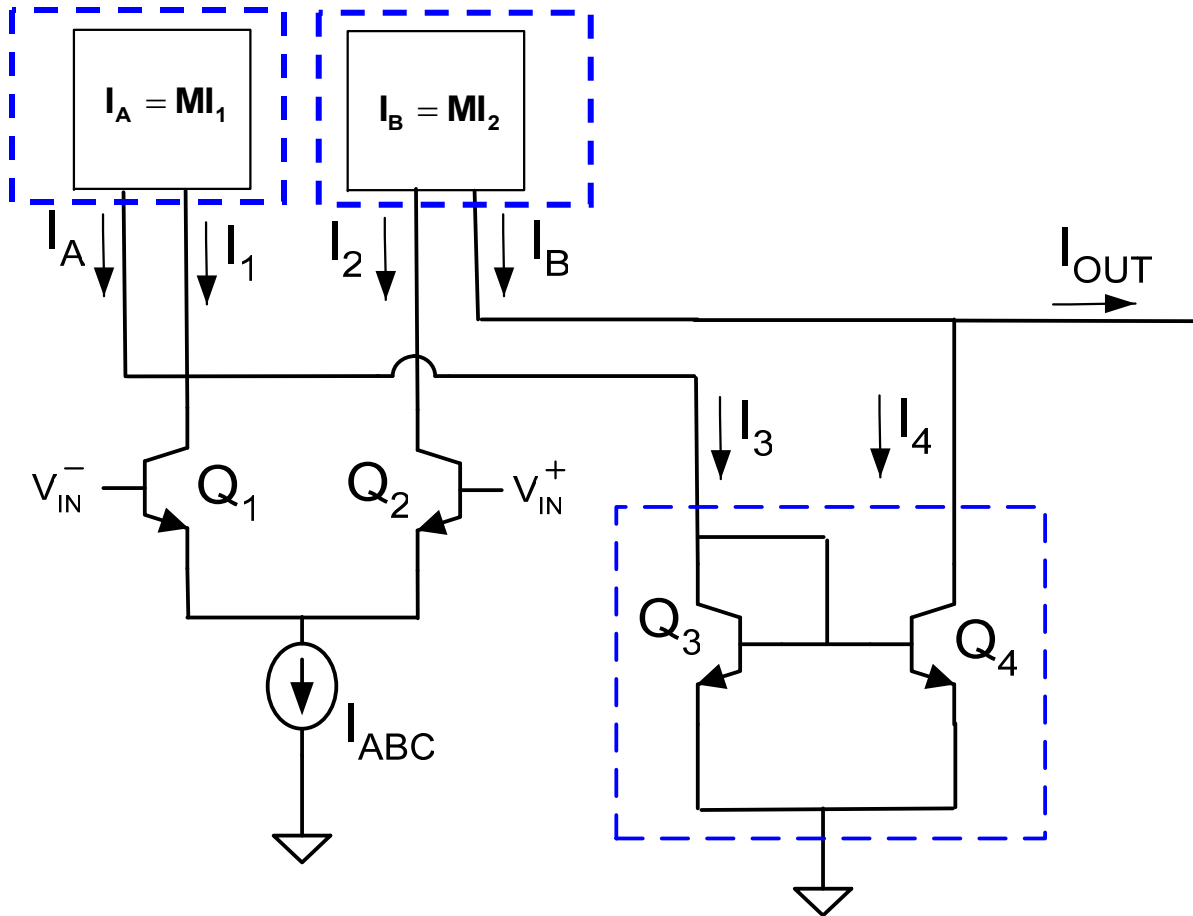

3-mirror OTA


$$I_{OUT} = M(I_B - I_A)$$

# Current Mirror Op Amp W/O CMFB

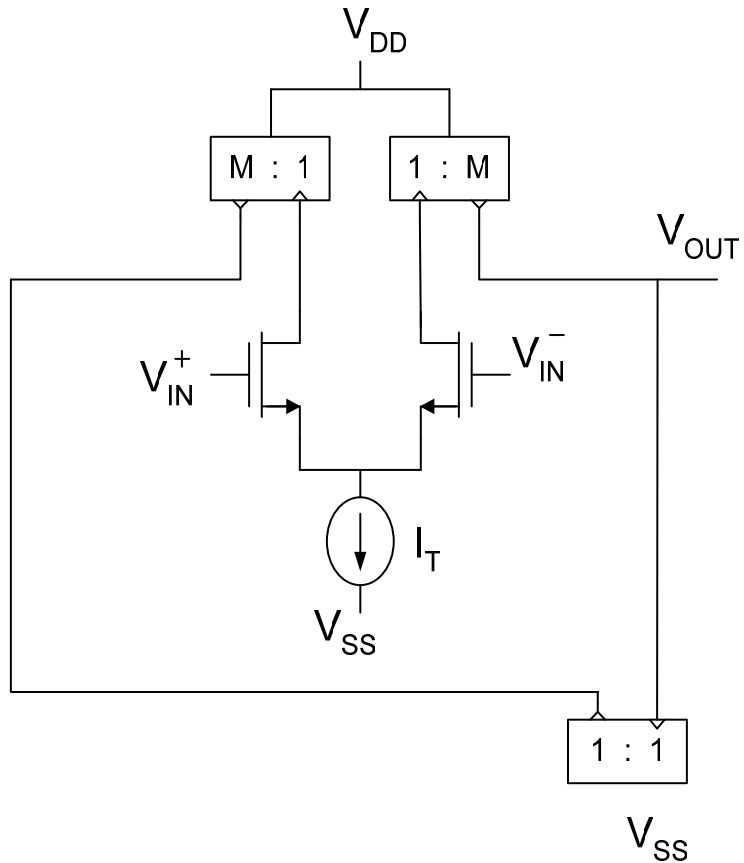

$$g_{mEQ} = Mg_{m1}$$

Often termed an OTA

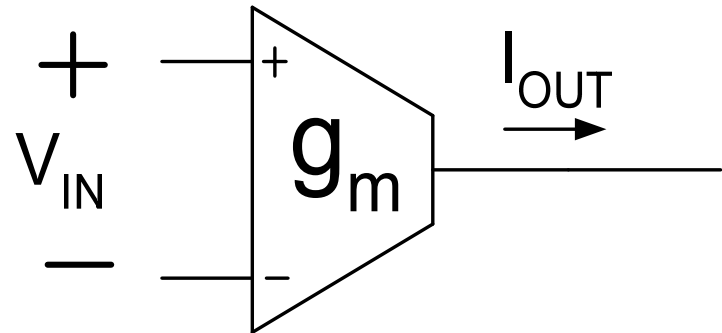


$$I_{OUT} = g_m V_{IN}$$

Introduced by Wheatley and Whitlinger in 1969
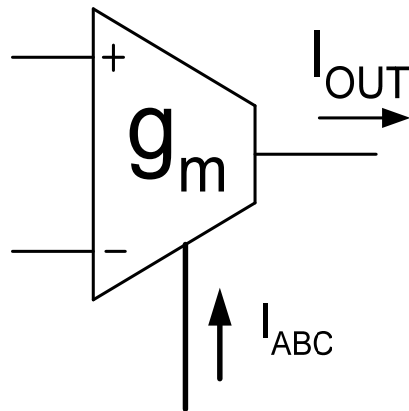
# OTA Circuits

- OTA often used open loop
- Excellent High Frequency Performance
- Gain can be made programmable with dc current
- Large or very large adjustment ranges possible




$$g_m = \begin{cases} K \cdot I_{ABC} & \text{for BJT circuits} \\ K \sqrt{I_{ABC}} & \text{for MOS circuits} \end{cases}$$

2 to 3 decades of adjustment for MOS

5 to 6 decades of adjustment for BJT

# OTA Applications

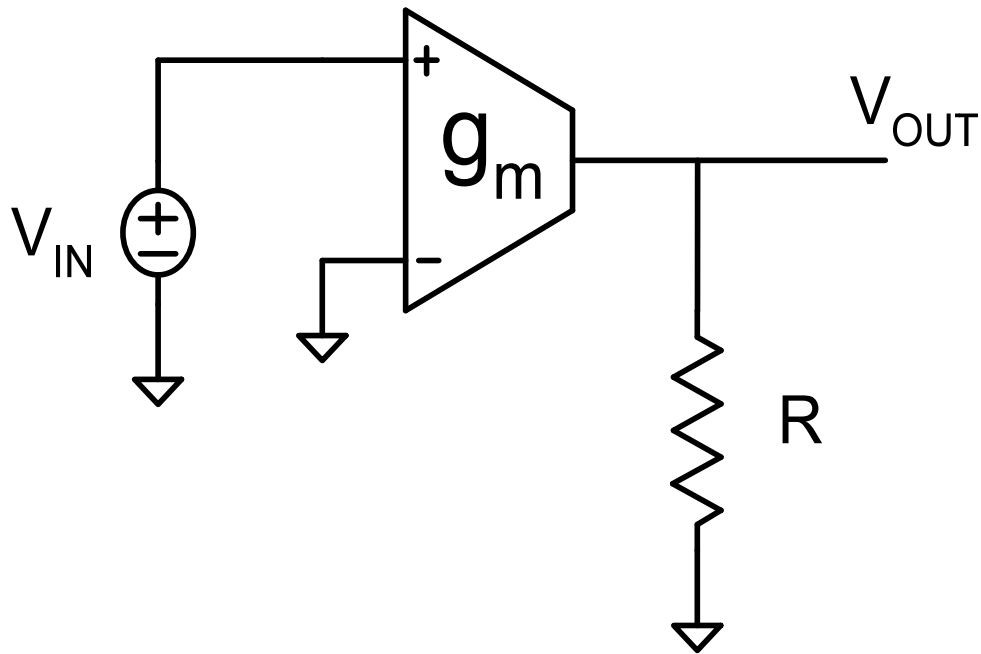


$$V_{OUT} = g_m R \bullet V_{IN}$$

$g_m$  is controllable with  $I_{ABC}$

## Voltage Controlled Amplifier

Note: Technically current-controlled, control variable not shown here and on following slides

# OTA Applications

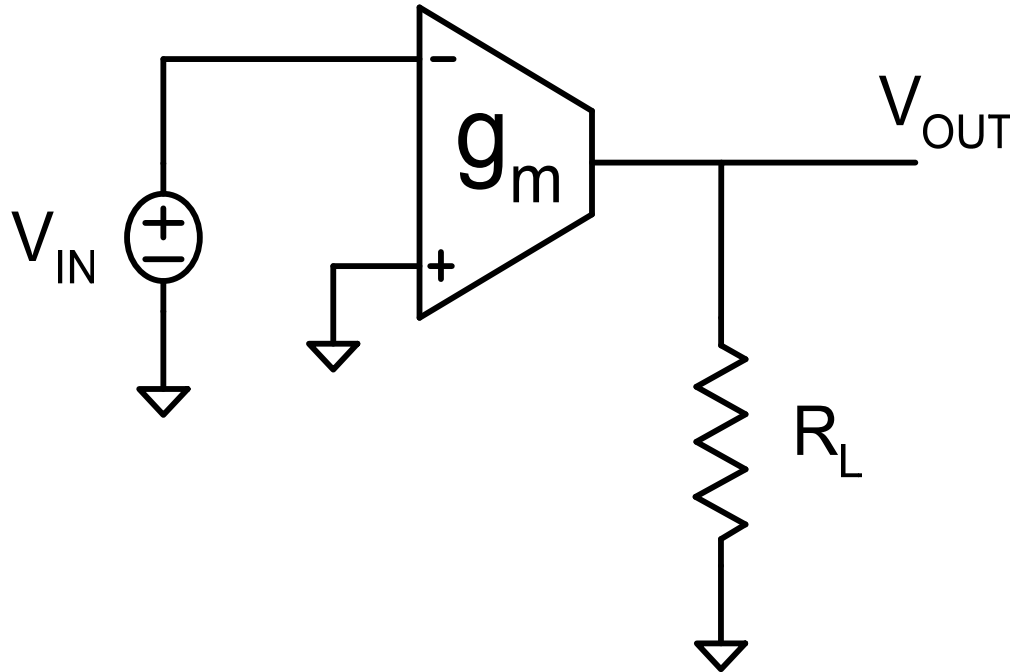


$$V_{OUT} = -g_m R \bullet V_{IN}$$


Voltage Controlled Inverting Amplifier



# OTA Applications

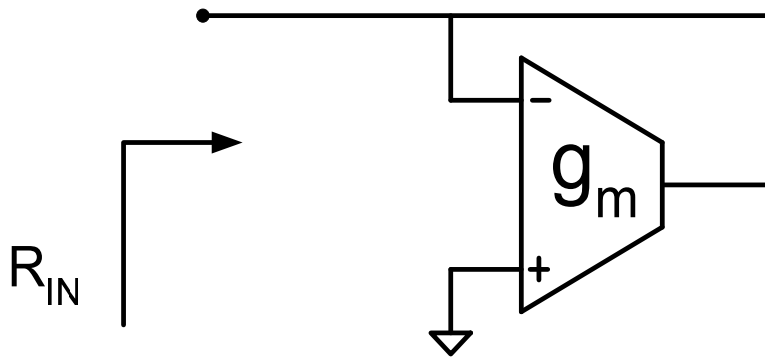


$$R_{IN} = \frac{1}{g_m}$$

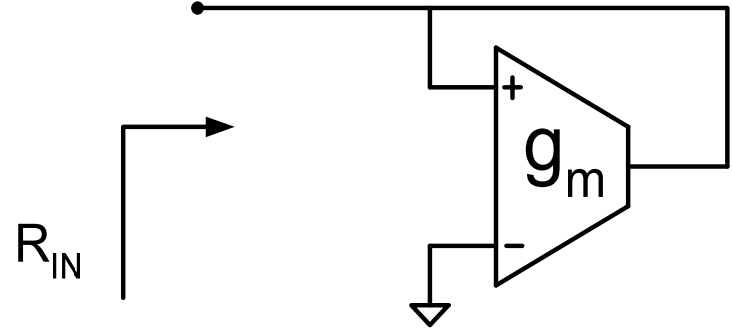

$$R_{IN} = -\frac{1}{g_m}$$


Voltage Controlled Resistances

# OTA Applications

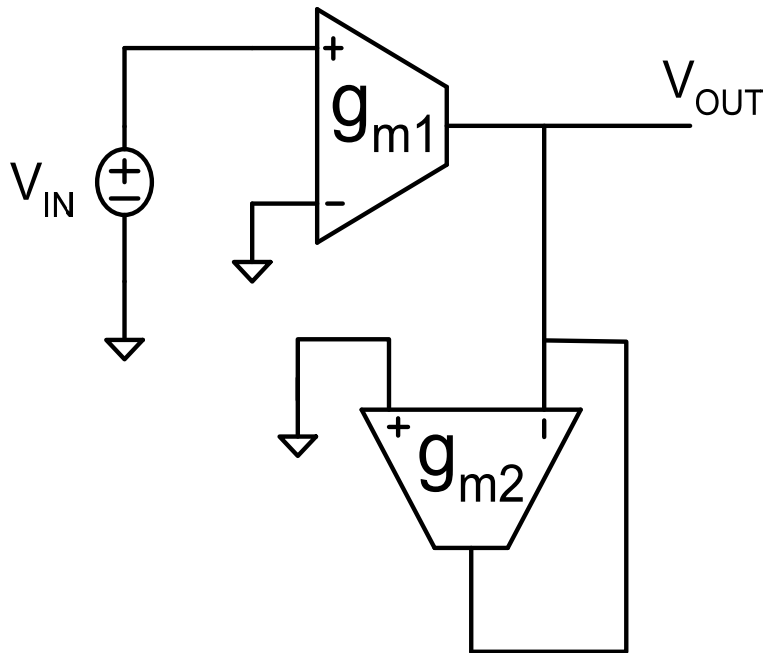

$$V_{\text{OUT}} = \frac{g_{m1}}{g_{m2}} V_{\text{in}}$$

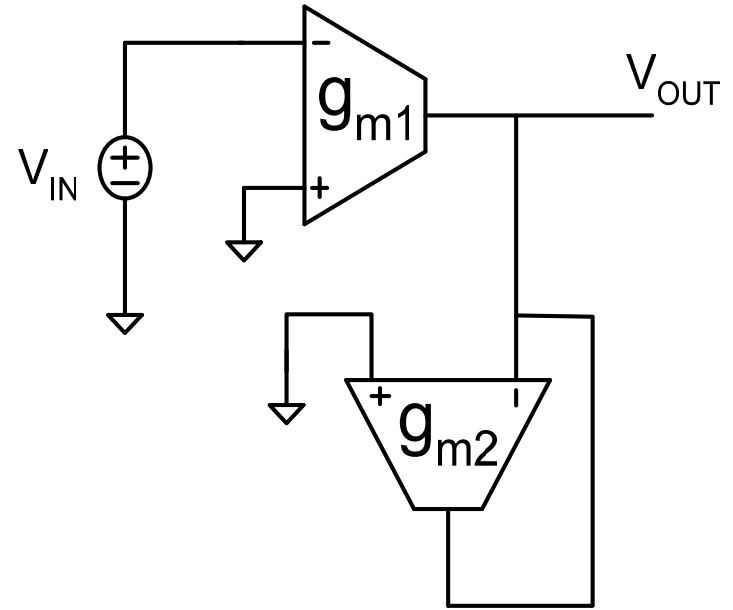Noninverting Voltage Controlled Amplifier




$$V_{\text{OUT}} = -\frac{g_{m1}}{g_{m2}} V_{\text{in}}$$

Inverting Voltage Controlled Amplifier


*Extremely large gain adjustment is possible*

**Voltage Controlled Resistorless Amplifiers**

# OTA Applications

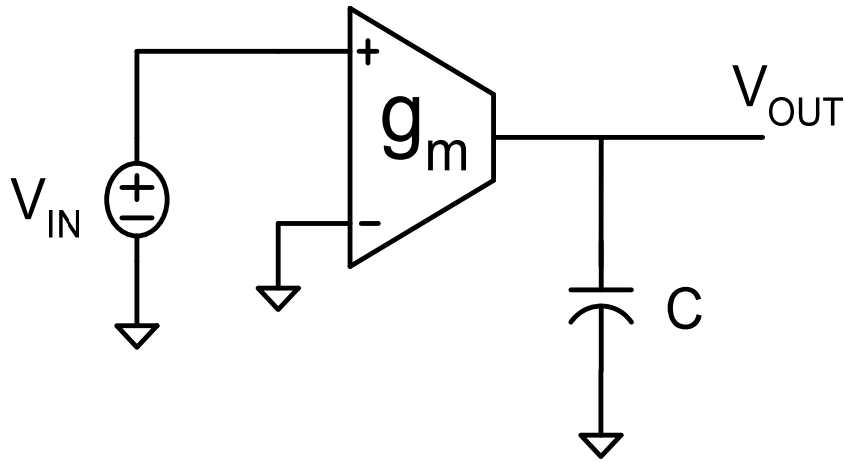
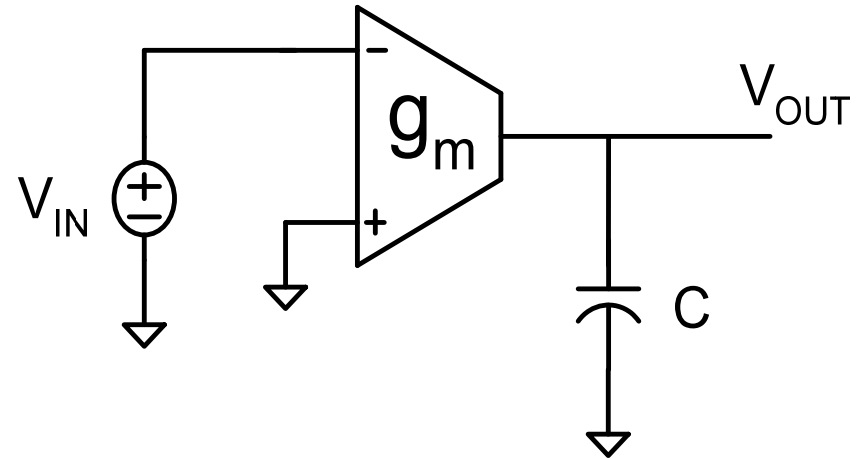
$$V_{\text{OUT}} = \frac{g_m}{sC} V_{\text{in}}$$





$$V_{\text{OUT}} = -\frac{g_m}{sC} V_{\text{in}}$$

Noninverting Voltage Controlled Integrator

Inverting Voltage Controlled Integrator

Voltage Controlled Integrators
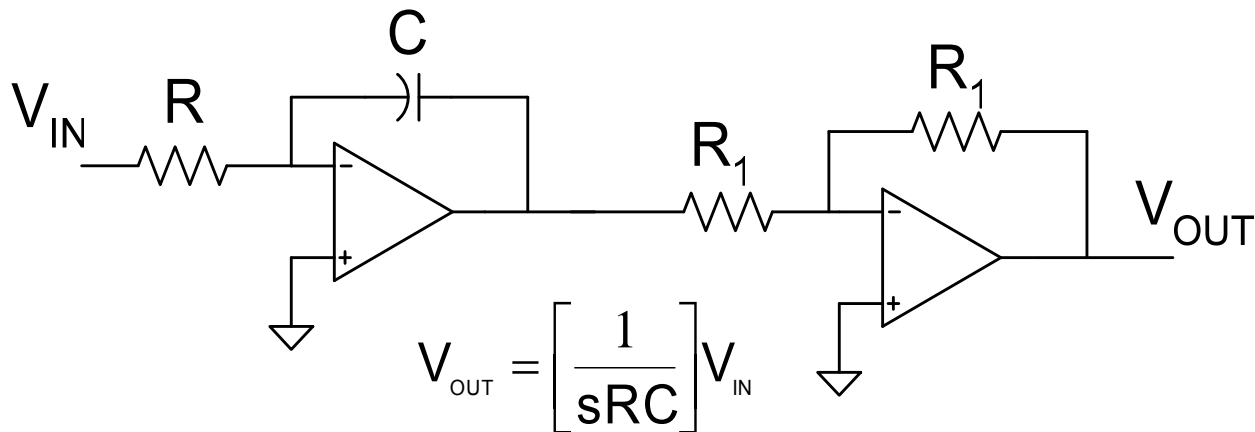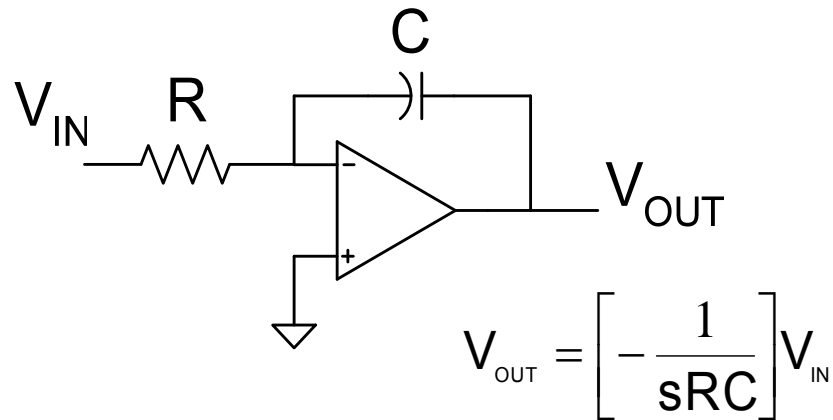
# Comparison with Op Amp Based Integrators



OTA-based integrators require less components and significantly less for realizing the noninverting integration function !

# Properties of OTA-Based Circuits


- Can realize arbitrarily complex functions
- Circuits are often simpler than what can be obtained with Op Amp counterparts
- Inherently offer excellent high frequency performance
- Can be controlled with a dc voltage or current
- Often used open-loop rather than in a feedback configuration (circuit properties depend directly on  $g_m$ )
- Other high output impedance op amps can also serve as OTA
- Linearity is limited
- Signal swing may be limited but can be good too
- Circuit properties process and temperature dependent

- Current-Mirror Op Amp offers strategy for  $g_m$  enhancement
- Very Simple Structure
- Has applications as an OTA
- But – how good are the properties of the CMOA?


Is this a real clever solution?



# Current Mirror Op Amp W/O CMFB

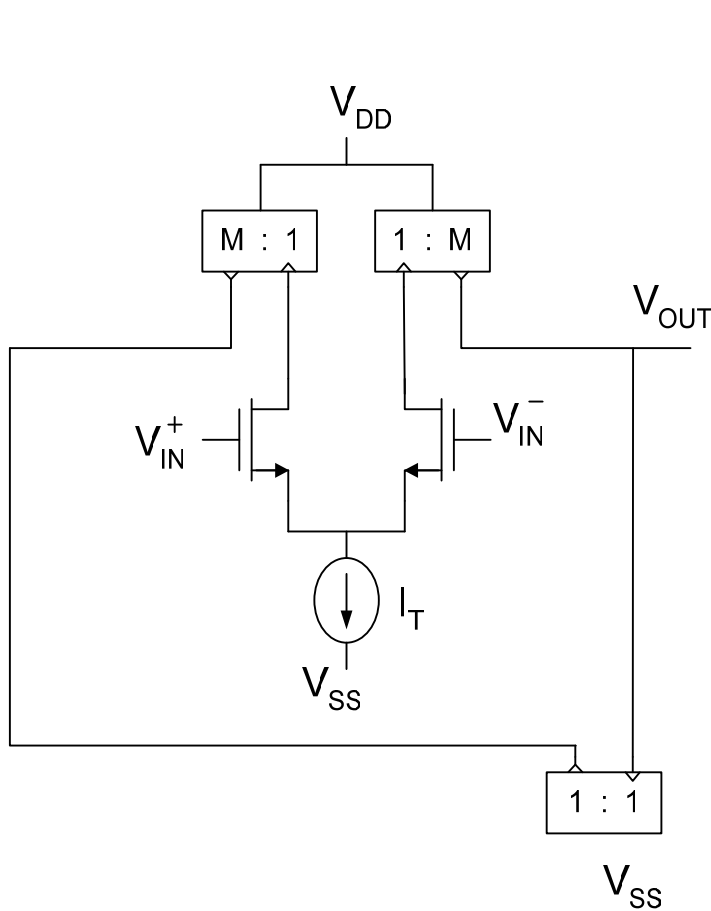

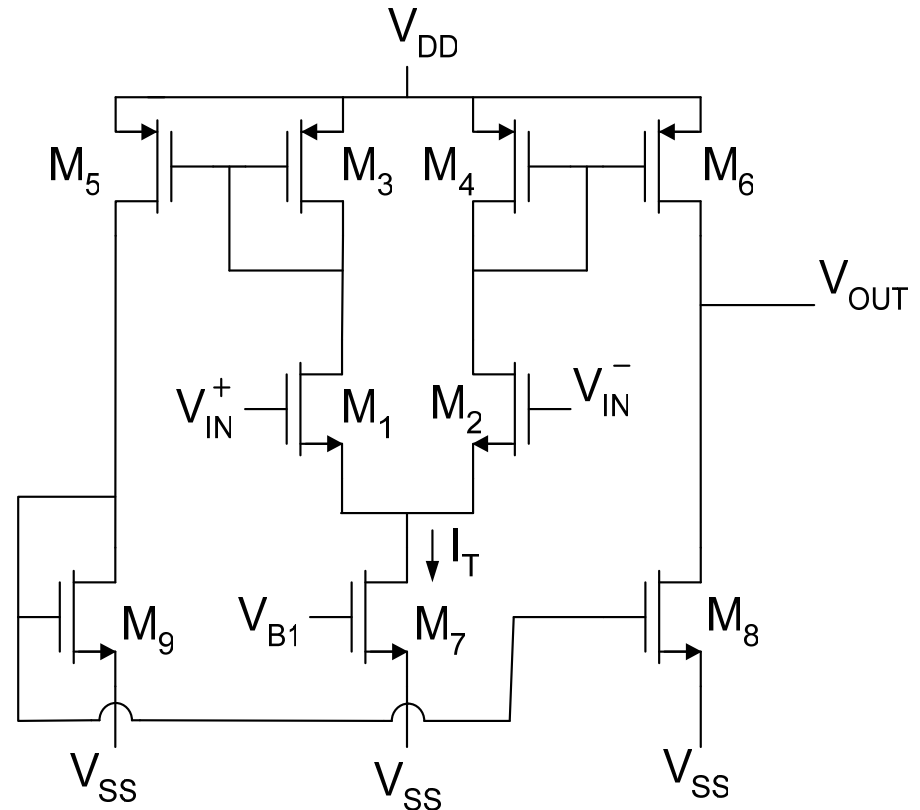Can use higher output impedance current mirrors to decrease  $g_{OEQ}$




$$g_{OEQ} = g_{O6} + g_{O8}$$

$$g_{mEQ} = M g_{m1}$$


$$A_{VO} = -\frac{M \cdot g_{m1}}{g_{O6} + g_{O8}}$$

$$SR = \frac{M I_T}{C_L}$$

# SR of Current Mirror Op Amp

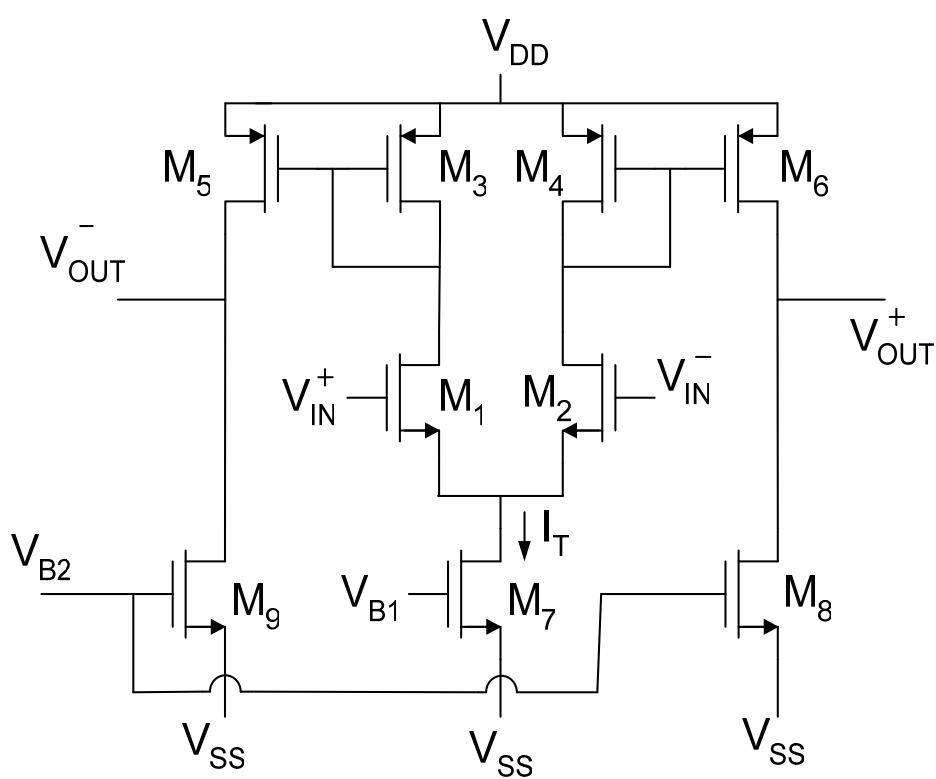


$$SR = \frac{MI_T}{2C_L}$$

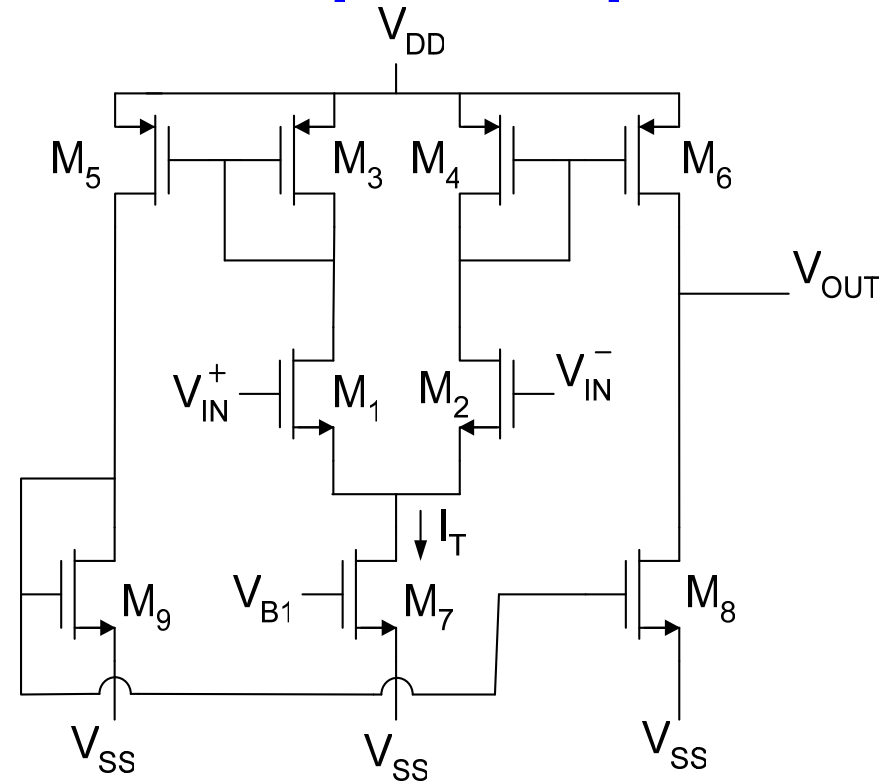

$$SR = \frac{MI_T}{C_L}$$



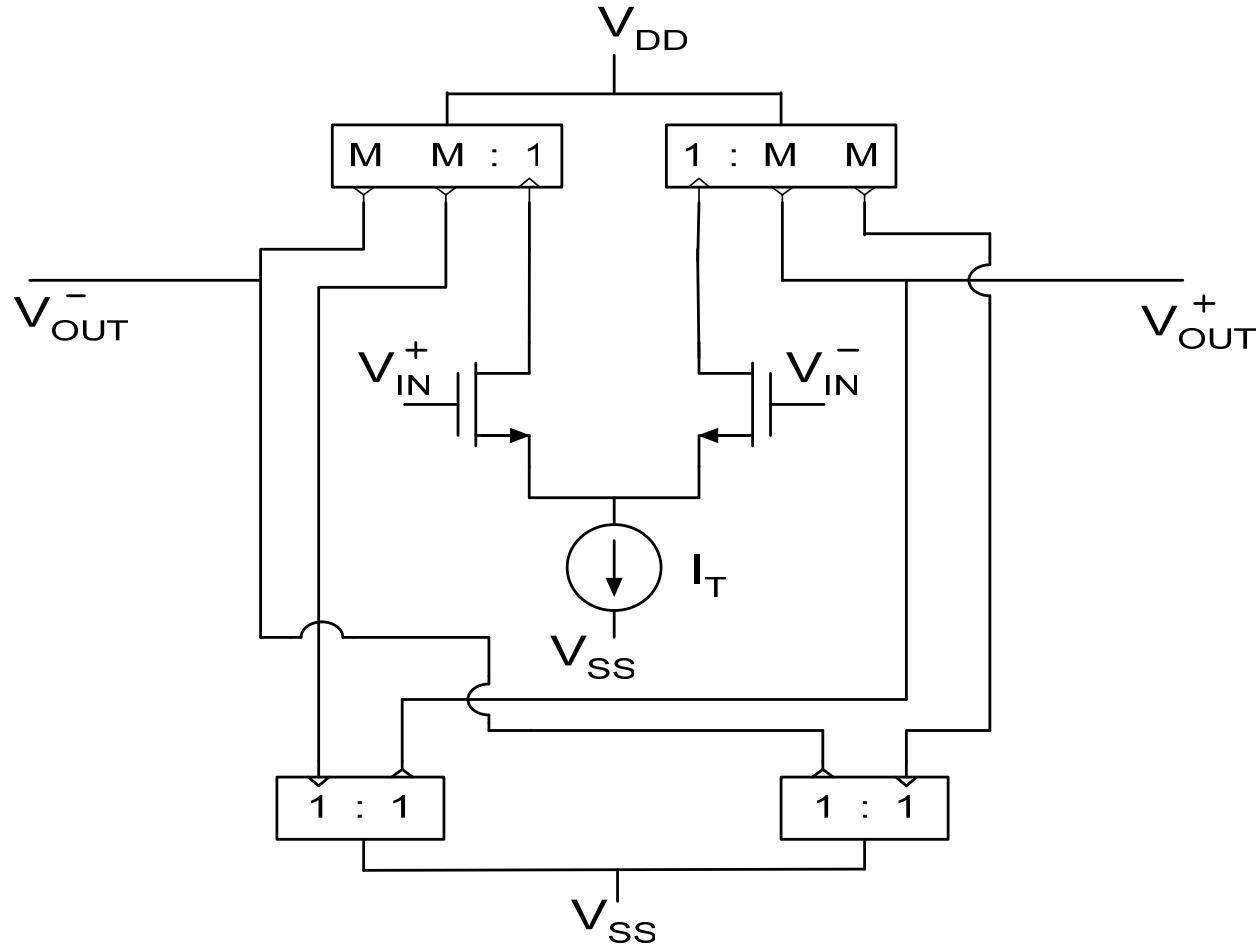
# Fully Differential Current Mirror Op Amp with Improved Slew Rate



Need CMFB circuit and requires modest circuit modification to provide CMFB insertion point

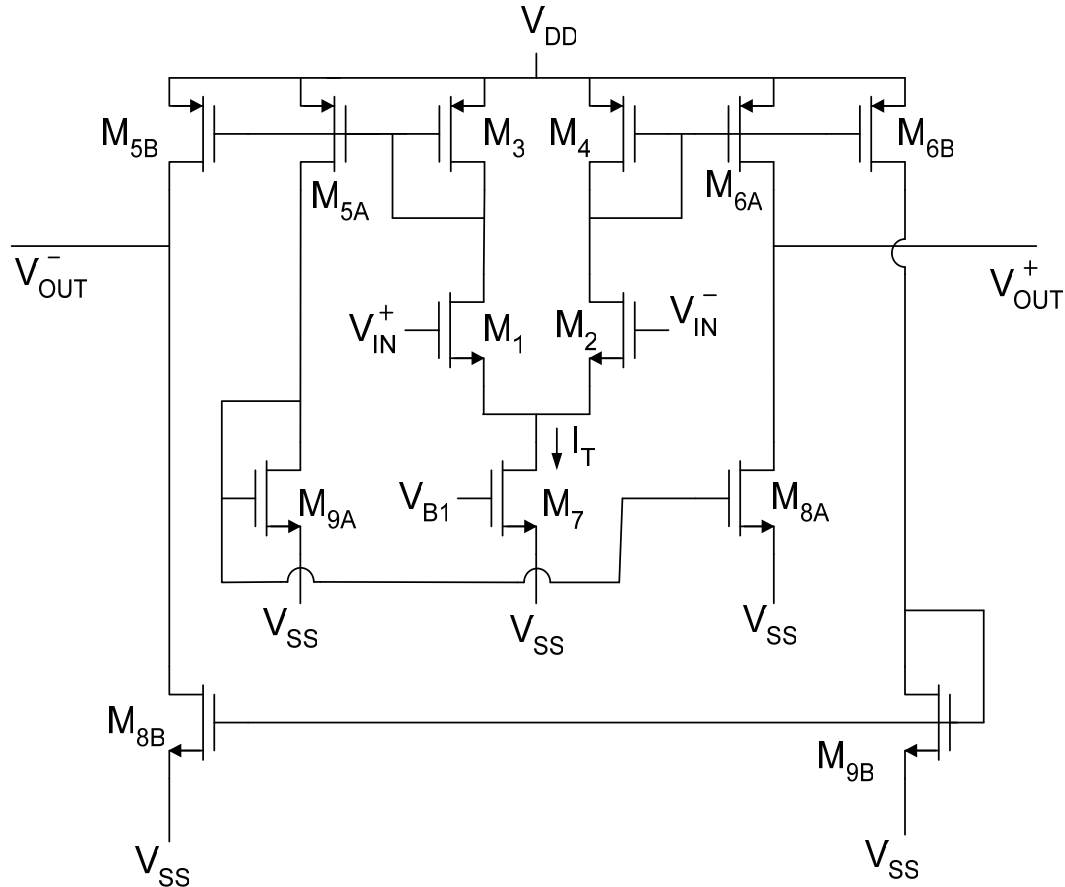
# Fully Differential Current Mirror Op Amp with Improved Slew Rate

This circuit was published because of the claim for improved SR (Fig 6.15 MJ)



Need CMFB circuit and requires modest circuit modification to provide CMFB insertion point
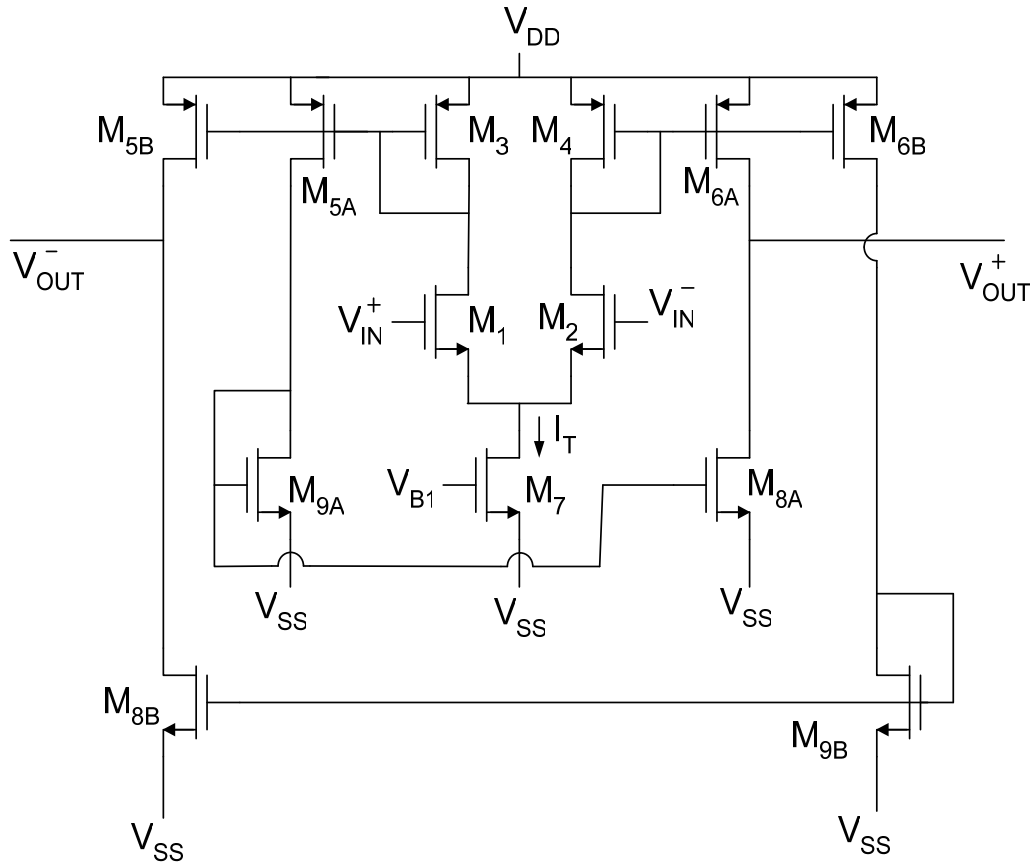
# Fully Differential Current Mirror Op Amp with Improved Slew Rate



$$SR = \frac{MI_T}{C_L}$$


$$SR_{CMOpAmp} = \frac{M \cdot I_T}{2C_L}$$

Improved a factor of 2 !

but ...

Need CMFB circuit and requires modest circuit modification to provide CMFB insertion point
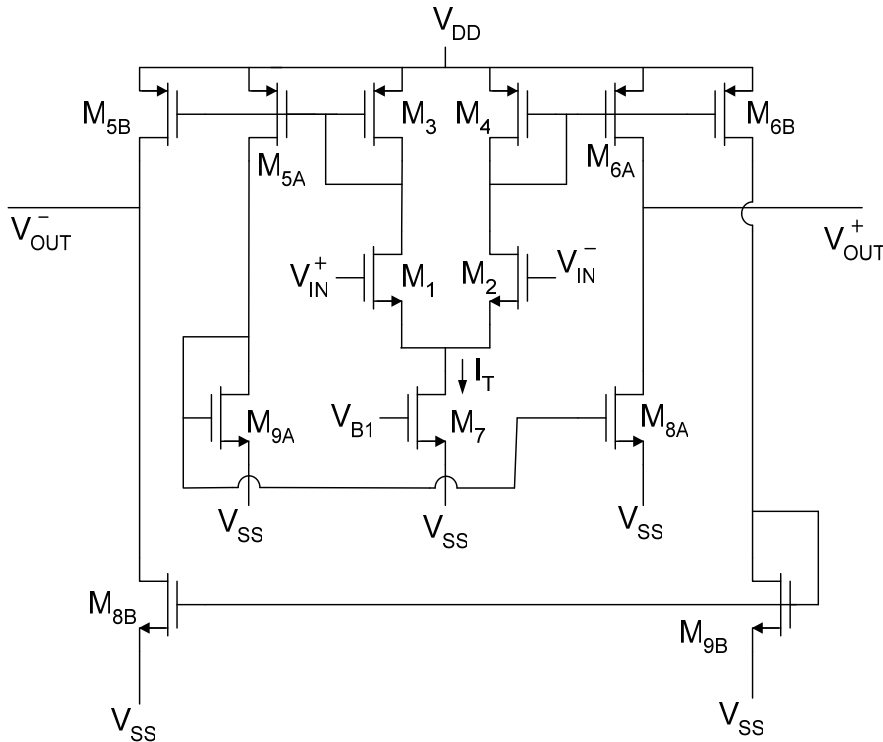
# Fully Differential Current Mirror Op Amp with Improved Slew Rate



$$SR = \frac{M I_T}{C_L}$$

$$SR_{CMOpAmp} = \frac{M \cdot I_T}{2C_L}$$

Improved a factor of 2 !

but ...

$$P_{CMOpAmp} = V_{DD} I_T (1 + M)$$

$$P = V_{DD} I_T (1 + 2M)$$


$$SR_{CMOpAmp} = \left( \frac{P}{V_{DD} C_L} \right) \left[ \frac{M}{2[1 + M]} \right]$$

$$SR = \left( \frac{P}{V_{DD} C_L} \right) \left[ \frac{M}{1 + 2M} \right]$$

**SR actually about the same for “improved SR circuit” and basic OTA**
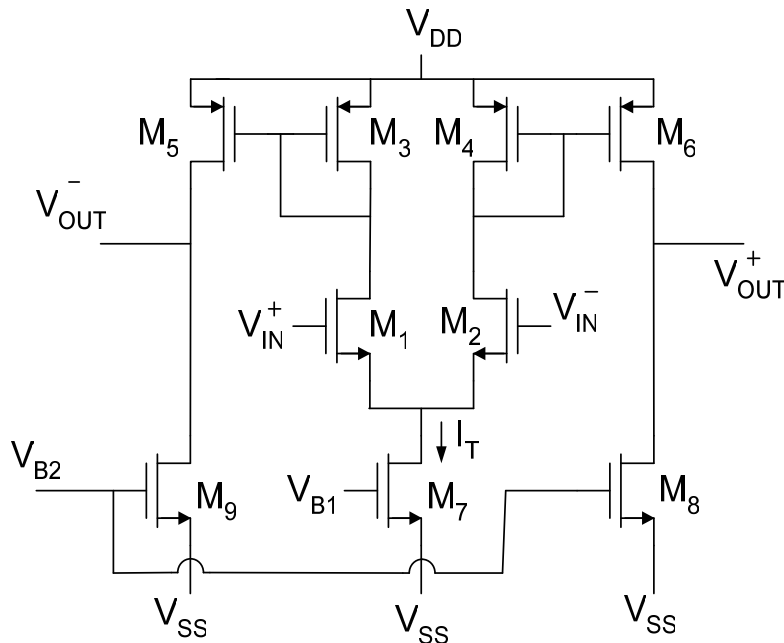
# Comparison of Current-Mirror Op Amps with Previous Structures

Does the simple mirror gain really provide an “almost free” gain enhancement ?



$$A_{VO} = - \frac{M \cdot \frac{g_{m1}}{2}}{g_{O6} + g_{O8}}$$

$$M = \frac{WL_{64}}{WL_{46}}$$

# Reference Op Amp

Consider single-ended output performance :

$$A(s) = \frac{g_{m1}}{sC_L + g_{o1} + g_{o3}}$$

$$A_{VO} = \frac{1}{2} \frac{g_{m1}}{g_{o1} + g_{o3}}$$


$$A_{VO} = \left[ \frac{1}{\lambda_1 + \lambda_3} \right] \left( \frac{1}{V_{EB1}} \right)$$

$$GB = \frac{g_{m1}}{2C_L}$$

$$GB = \left( \frac{P}{2V_{DD}C_L} \right) \cdot \left[ \frac{1}{V_{EB1}} \right]$$

$$SR = \frac{I_T}{2C_L}$$


$$SR = \frac{P}{2V_{DD}C_L}$$

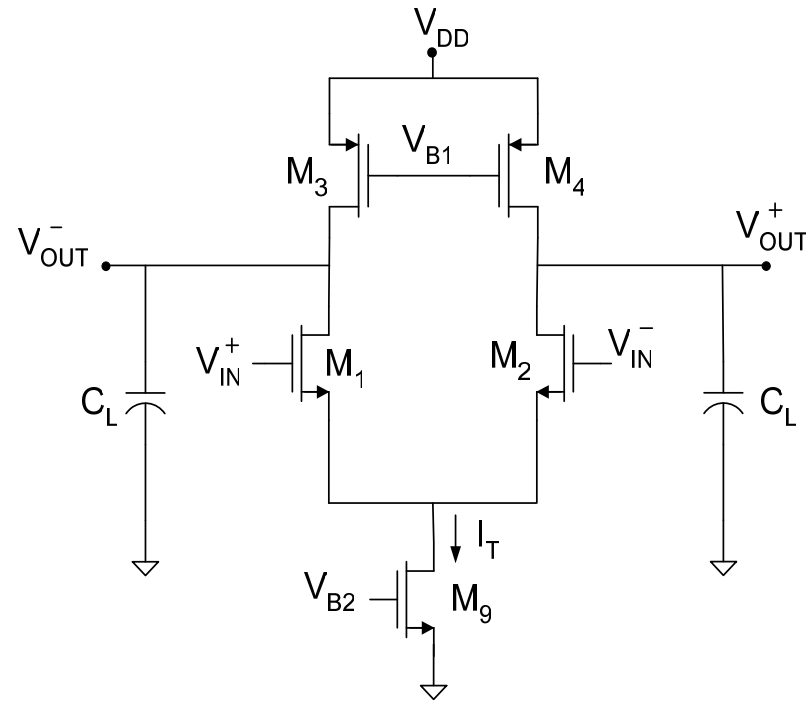
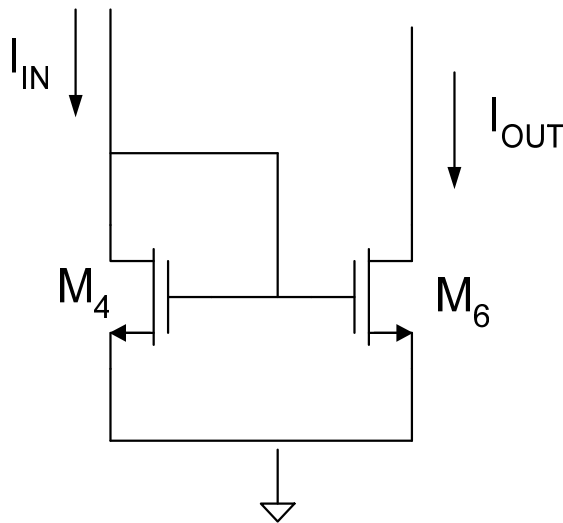
# Comparison of Current-Mirror Op Amps with Previous Structures

Does the simple mirror gain really provide an “almost free” gain enhancement ?

$$A_{vo} = -\frac{M \cdot \frac{g_{m1}}{2}}{g_{o6} + g_{o8}}$$



$$M = \frac{W_6 L_4}{W_4 L_6}$$

$$M = \frac{g_{m6}}{g_{m4}}$$


$$A_{vo} = -\frac{\frac{g_{m6}}{g_{m4}} \cdot \frac{g_{m1}}{2}}{g_{o6} + g_{o8}}$$

Gain Enhancement Potential Less Apparent but still Improved by  $g_{m6}/g_{m4}$  ratio
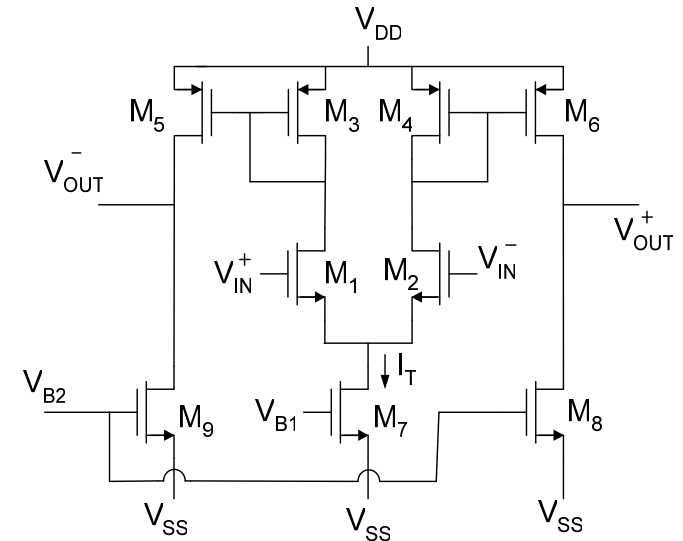
# Comparison of Current-Mirror Op Amps with Previous Structures

Does the simple mirror gain really provide an “almost free” gain enhancement ?

$$A_{VO} = -\frac{M \bullet \frac{g_{m1}}{2}}{g_{O6} + g_{O8}}$$



Consider how the gain appears in the practical parameter domain

$$A_{VO} = \frac{\frac{1}{2} \left( 2 \frac{I_T}{2} M \right)}{V_{EB1} (\lambda_{M6} + \lambda_{M8}) I_{D8Q}} = \frac{\frac{I_T}{2} M}{V_{EB1} (\lambda_{M6} + \lambda_{M8}) M \frac{I_T}{2}} = \frac{1}{V_{EB1} (\lambda_{M6} + \lambda_{M8})} \cong \frac{1}{2\lambda V_{EB1}}$$


This is exactly the same as was obtained for the simple differential amplifier!

For a given  $V_{EB1}$ , there is NO gain enhancement !


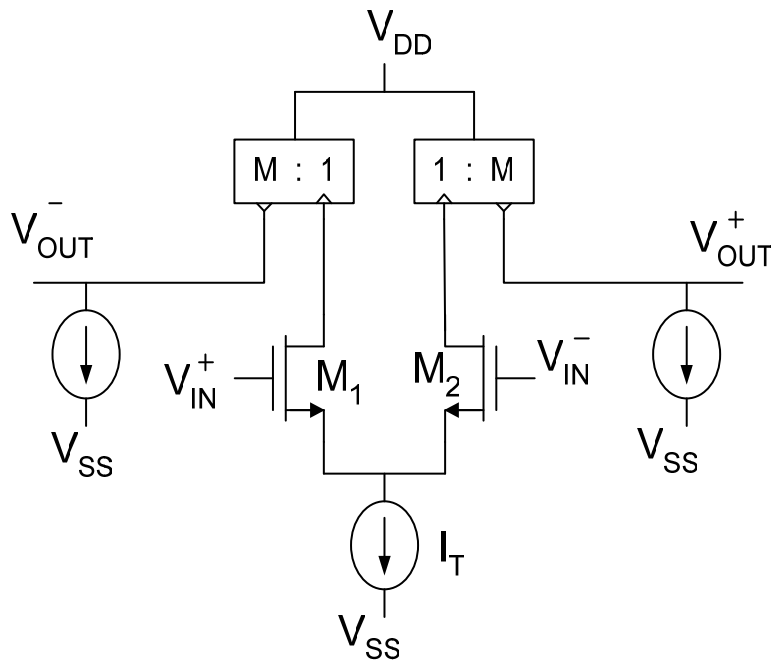
# Comparison of Current-Mirror Op Amps with Previous Structures

How does the GB power efficiency compare with previous amplifiers ?



$$GB = \frac{g_{mEQ}}{C_L} = \frac{M \frac{g_{m1}}{2}}{C_L} = \frac{MI_T}{2V_{EB1} C_L}$$

$$P = V_{DD} I_T (1 + M)$$


$$GB = \frac{MI_T}{2V_{EB1} C_L} = \left( \frac{P}{2V_{EB1} V_{DD} C_L} \right) \left[ \frac{M}{1+M} \right]$$

GB for Telescopic Cascode and Ref Op Amp !

GB efficiency decreased for small M !!
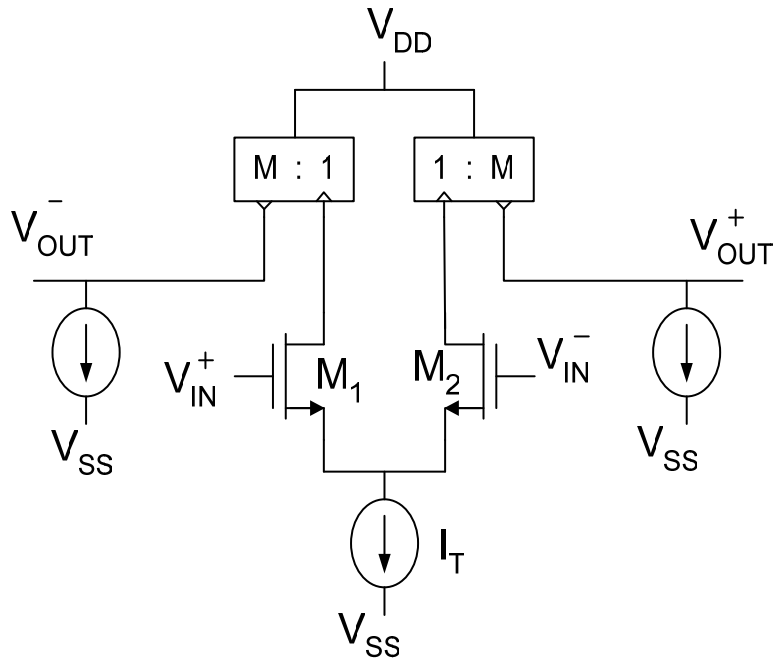
# Comparison of Current-Mirror Op Amps with Previous Structures

How does the SR compare with previous amplifiers ?



$$SR_{\text{Ref Op Amp}} = \frac{I_T}{2C_L}$$

$$SR = \frac{M \cdot I_T}{2C_L}$$

SR Improved by factor of M !  
but ...

$$P = V_{DD} I_T (1 + M)$$


$$SR = \frac{P}{2V_{DD} C_L} \left[ \frac{M}{1 + M} \right]$$

$$SR_{\text{Ref Op Amp}} = \frac{P}{2V_{DD} C_L}$$

SR Really Less than for Ref Op Amp !!
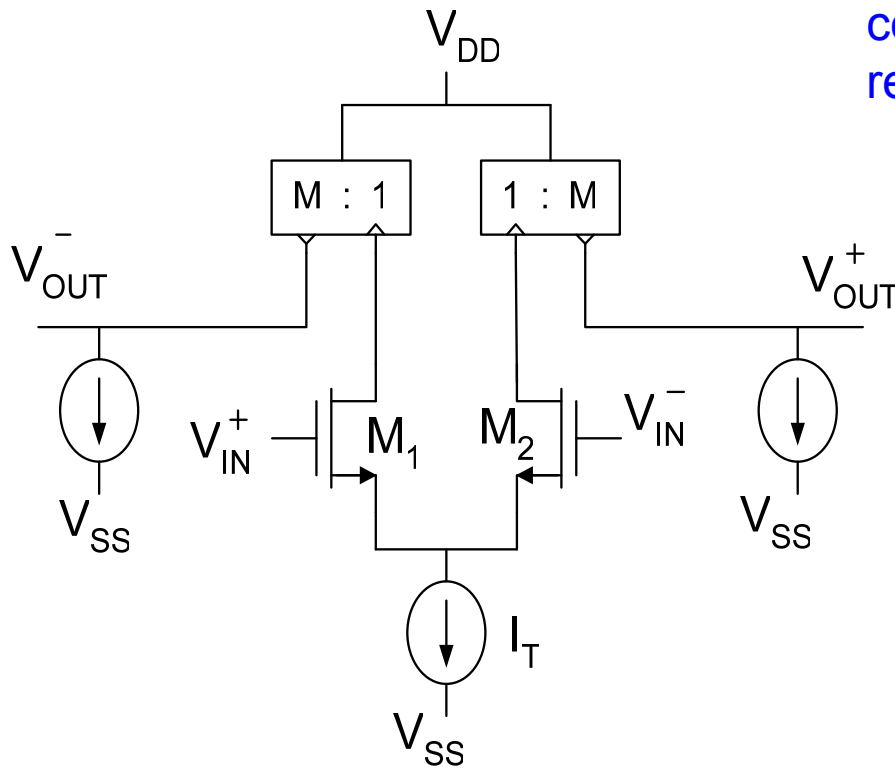
# Comparison of Current-Mirror Op Amps with Previous Structures

How does the Current Mirror Op Amp really compare with previous amplifiers or with reference amplifier?



Perceived improvements may appear to be very significant

Actual performance is not as good in almost every respect !

**End of Lecture 9**