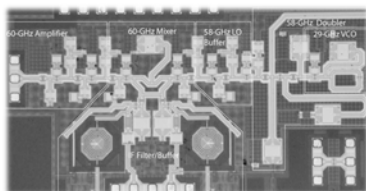


# Lecture 9: Smith Chart/ S-Parameters

Amin Arbabian  
Jan M. Rabaey



**EE142 – Fall 2010**

Sept. 23<sup>rd</sup>, 2010

University of California, Berkeley

## Announcements

- HW3 was due at 3:40pm today
  - You have up to tomorrow 3:30pm for 30% penalty. After that the solutions are posted and there will be no credit.
- Monday's Discussion section: figuring out the time for review OHs. Starts next week.
- HW4 due next Thursday, posted today

## Outline

- Last Lecture: Achieving Power Gain
  - Power gain metrics
  - Optimizing power gain
  - Matching networks
- This Lecture: Smith Chart and S-Parameters
  - Quick notes about matching networks
  - Smith Chart basics
  - Scattering Parameters

EE142-Fall 2010

3

## Matching Network Design


1. Calculate the boosting factor  $m = \frac{R_{hi}}{R_{lo}}$
2. Compute the required circuit Q by  
 $(1 + Q^2) = m$ , or  $Q = \sqrt{m - 1}$ .
3. Pick the required reactance from the Q. If you're boosting the resistance, e.g.  $R_s > R_L$ , then  $X_s = Q \cdot R_L$ .  
 If you're dropping the resistance,  $X_p = R_L / Q$
4. Compute the effective resonating reactance. If  $R_s > R_L$ , calculate  $X'_s = X_s(1 + Q^{-2})$  and set the shunt reactance in order to resonate,  $X_p = -X'_s$ . If  $R_s < R_L$ , then calculate  $X'_p = X_p/(1+Q^{-2})$  and set the series reactance in order to resonate,  $X_s = -X'_p$ .
5. For a given frequency of operation, pick the value of L and C to satisfy these equations.

EE142-Fall 2010

4
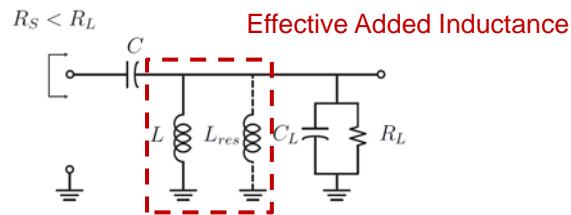
## Complex Source/ Load

- First “absorb” the extra reactance/ susceptance
- We can then move forward according to previous guidelines




- There might be multiple ways of achieving matching, each will have different properties in terms of BW (Q), DC connection for biasing, High-pass vs Low-Pass,...


EE142-Fall 2010

5

## Multi-Stage Matching Networks

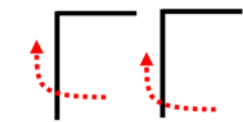

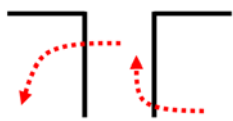1. Cascaded L-Match
  - Wide bandwidth
  - Only in one direction



- T-Match
  - First transform high then low
  - BW is lower than single L-Match



- Pi-Match
  - First low then high
  - BW is lower than single L-match

EE142-Fall 2010

6

# TRANSMISSION LINES

## A QUICK OVERVIEW

7

## Transmission Lines

- We are departing from our understandings of lumped element circuits
- Circuit theory concepts (KVL and KCL) do not *directly* apply, we need to take into account the distributed nature of the elements
  - Shorted quarter-wave line
  - KCL on a transmission line
- Main issue is with the delay in the circuit, signals cannot travel faster than speed of light. Once circuits become larger this will become a significant effect.
- We will use our circuit techniques to understand the behavior of a transmission line
  - Remember HW 1

EE142-Fall 2010

8


## T-Lines

- Transmission lines are NOT the main focus of this lecture (or course) and are extensively covered in EE117. We will have a brief introduction to help us understand some of the other concepts (Smith Chart and S-Parameters).
  - Please refer to Ch.9 of Prof. Niknejad's book (or Pozar, Gonzalez, Collin, etc)


EE142-Fall 2010

9

## Infinite Ladder Network

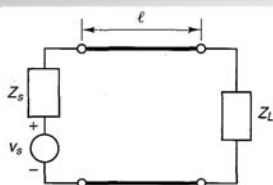

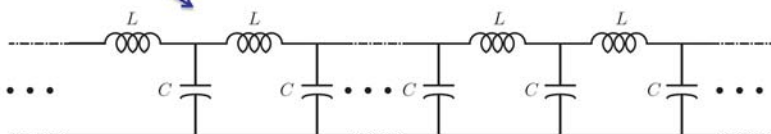Lossless Distributed Ladder Model for this transmission line



- From HW1, infinite ladder network with  $Z_{series} = j\omega L$  and  $Y_{shunt} = j\omega C$  leads to:

$$Z_{in} = \frac{j\omega L}{2} \pm \sqrt{-\frac{(\omega L)^2}{4} + \frac{L}{C}}$$

- For a “distributed” model in which the L and C segments are infinitesimal in size:


$$Z_{in} \approx \sqrt{\frac{L}{C}} \quad \text{This is } \textit{resistive} \text{ value (real) !}$$

EE142-Fall 2010

10
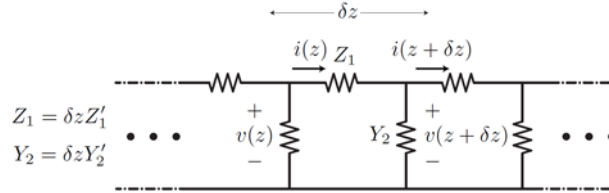
## Solving for Voltages and Currents

- We now know the input impedance of the infinite line in terms of the L and C parameters (per unit length values).
- We also know that if we terminate the line with  $Z_0$  we will still see the same impedance even if the line is finite.
- How about voltages and currents?



$$v(z + \delta z) = v(z) - i(z)Z_1'\delta z \quad \frac{dv}{dz} = -Z_1'i(z) \quad \frac{d^2v}{dz^2} = \gamma^2v(z)$$

$$i(z) = i(z + \delta z) + \delta zY_2'v(z + \delta z) \quad \frac{di}{dz} = -Y_2'v(z) \quad \frac{d^2i}{dz^2} = \gamma^2i(z)$$

$$\gamma^2 = Z_1'Y_2'$$

EE142-Fall 2010

11

## Deriving Voltages and Currents

- Interested in steady state solutions we solve the DEs:

$$v(z) = V^+e^{-\gamma z} + V^-e^{\gamma z}$$

$$i(z) = I^+e^{-\gamma z} + I^-e^{\gamma z}$$

Take the derivative and using

$$\frac{dv}{dz} = -Z_1'i(z) \quad -V^+\gamma e^{-\gamma z} + V^-\gamma e^{\gamma z} = -Z_1'(I^+e^{-\gamma z} + I^-e^{\gamma z})$$

$$\frac{di}{dz} = -Y_2'v(z) \quad -I^+\gamma e^{-\gamma z} + I^-\gamma e^{\gamma z} = -Y_2'(V^+e^{-\gamma z} + V^-e^{\gamma z})$$

z=0 yields:

$$-V^+\gamma + V^-\gamma = -Z_1'(I^+ + I^-)$$

$$-I^+\gamma + I^-\gamma = -Y_2'(V^+ + V^-)$$

$$\gamma^2 = Z_1'Y_2'$$

$$Z_0 = \sqrt{Z_1'/Y_2'}$$

$$v(z) = V^+e^{-\gamma z} + V^-e^{\gamma z}$$


$$i(z) = \frac{V^+}{Z_0}e^{-\gamma z} - \frac{V^-}{Z_0}e^{\gamma z}$$

Lossless T-line  $Z_0 = \sqrt{\frac{j\omega L}{j\omega C}} = \sqrt{\frac{L}{C}} \quad \gamma = j\sqrt{LC}\omega$

EE142-Fall 2010

12


### Terminated Transmission Line

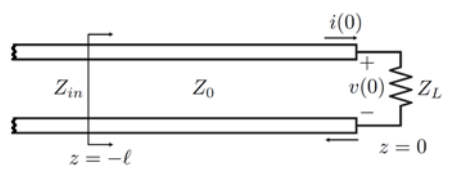

### SMITH CHART
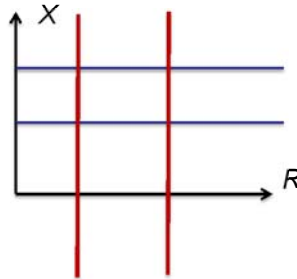
## Don't we have all we need?

- Smith Chart provides a visual tool for designing and analyzing **amplifiers, matching networks and transmission lines**. It is a convenient way of presenting **parameter variations with frequency**.
- You'll also see this is particularly useful for amplifier design in *potentially unstable* region ( $K < 1$ )
- Start by trying to "plot" impedance values:



But we want to present a very large range of impedances (open to short). This form may not be very useful!

EE142-Fall 2010

15

## Bilinear Transform

- We have seen this issue before (Laplace transform to Z-transform). A bilinear transform provided frequency warping there, can we use the same method here?
- Smith Chart plots the "reflection coefficient ( $\Gamma$ )" which is related to the impedance by:

$$\Gamma = \frac{Z - Z_0}{Z + Z_0} = U + jV$$

- Here  $Z_0$  is the characteristic impedance of *the* transmission line or just some reference impedance for the Smith Chart.
- The normalized impedance is often used:

$$z = \frac{Z}{Z_0} = \frac{R + jX}{Z_0} = r + jx \qquad \Gamma = \frac{z - 1}{z + 1}$$

EE142-Fall 2010

16




### A closer look at Smith Chart

$$U + jV = \frac{r - 1 + jx}{r + 1 + jx} \implies U = \frac{r^2 - 1 + x^2}{(r + 1)^2 + x^2} \quad V = \frac{2x}{(r + 1)^2 + x^2}$$

- Now if we eliminate x:

$$\left(U - \frac{r}{r+1}\right)^2 + V^2 = \left(\frac{1}{r+1}\right)^2$$

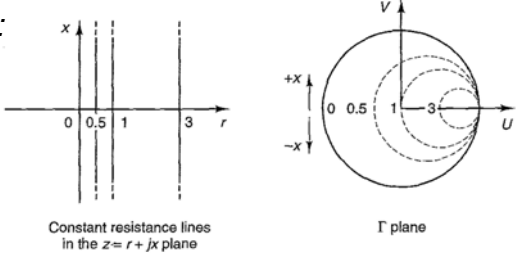
Circles with center at  $(r/r+1, 0)$  with radius  $1/r+1$




- Eliminating r:

$$(U - 1)^2 + \left(V - \frac{1}{x}\right)^2 = \left(\frac{1}{x}\right)^2$$

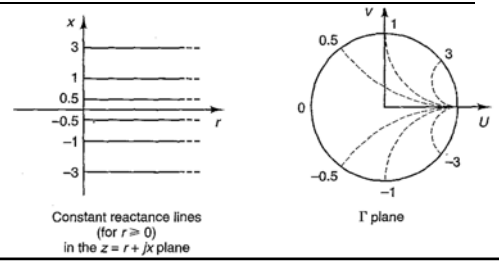
Circles with center at  $(1, 1/x)$  with radius  $1/x$



### Smith Chart

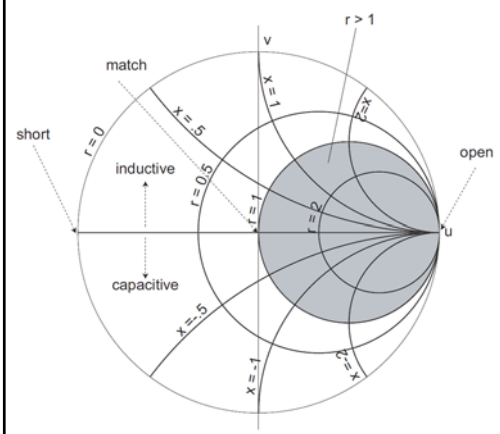

Refer to Niknejad, Ch.9

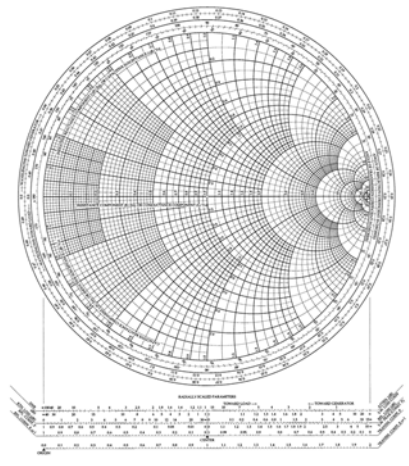


Phillip H. Smith, Murray Hill, NJ, 1977

### The Admittance Chart

$$Y = \frac{1}{Z} \text{ or } y = \frac{Y}{Y_0} = \frac{1}{\frac{Z}{Z_0}} \text{ where } Y_0 = \frac{1}{Z_0}$$

$$\Gamma = |\Gamma| \angle \theta = \frac{z - 1}{z + 1} = -\frac{y - 1}{y + 1} = -\Gamma' = \Gamma' \angle 180$$

- So to go from impedance point to an admittance point you just need to mirror the point around the center (or 180 degrees rotate)


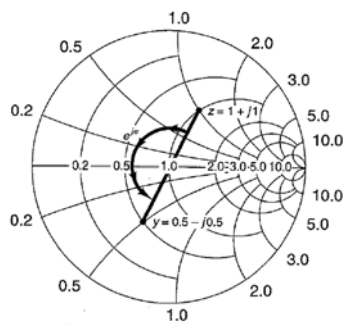


EE142-Fall 2010

Gonzalez, Prentice Hall, 1984

19


### Compound Impedances on a Smith Chart

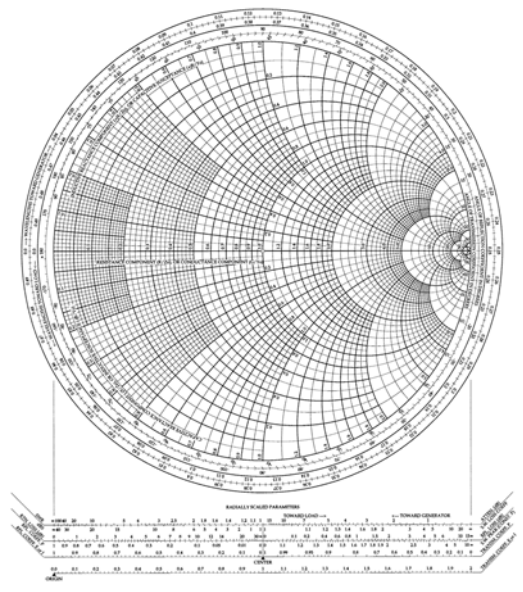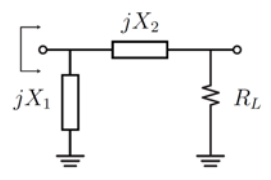

EE142-Fall 2010

20

# Transmission Lines

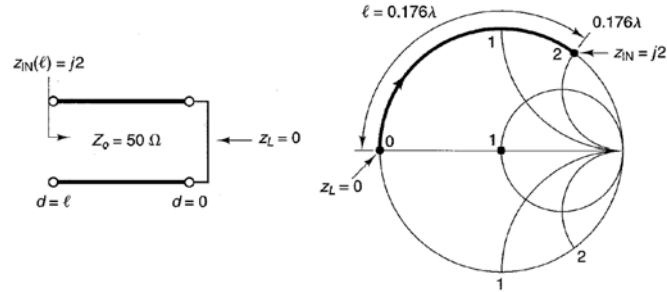

- Start from load, rotate clock-wise towards “generator”

# SCATTERING PARAMETERS

## Scattering Parameters

- Y, Z, H, G, ABCD parameters difficult to measure at HF
  - Very difficult to obtain broadband short or open at high frequencies
    - Remember parasitic elements and resonances
  - Difficult to measure voltages and currents at high frequency due to the impedance of equipment
  - Some microwave devices will be unstable under short/open loads
- Therefore, we use scattering parameters to define input and output characteristics. The actual voltages and currents are separated into scattered components (definitions will be given)

## Definitions for a One-Port

## Two-Port S-Parameters