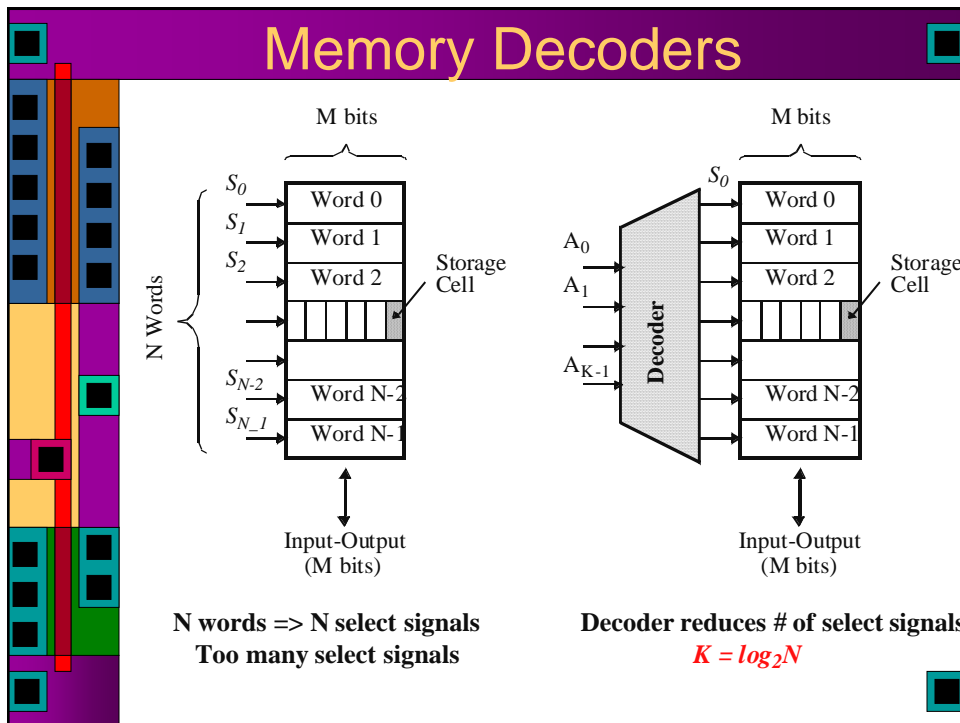



Memory

RWM		NVRWM	ROM
Random Access	Non-Random Access	EPROM E ² PROM FLASH	Mask-Programmed Programmable (PROM)
SRAM DRAM	FIFO LIFO Shift Register CAM		



Array-Structured Memory

Problem: ASPECT RATIO or HEIGHT >> WIDTH

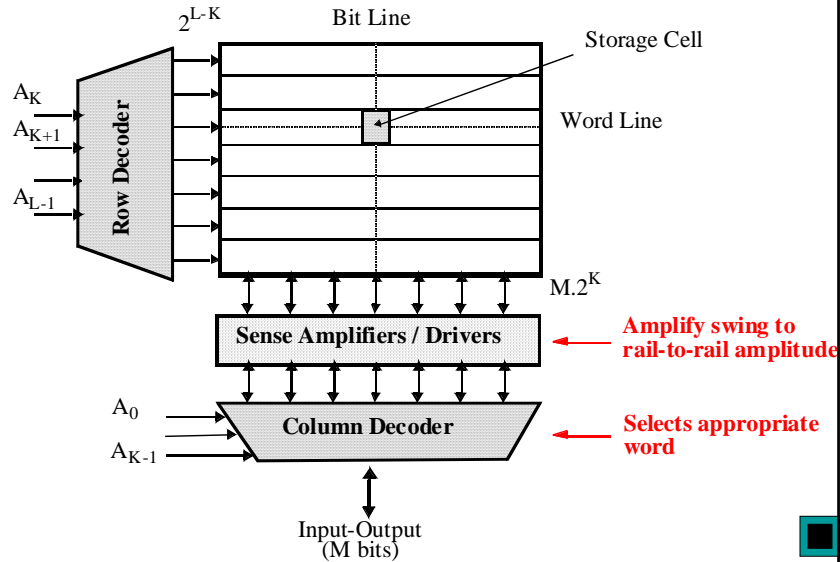

Array Decoding



- Typically want an aspect ratio that is not too far from square
- How to divide up the row, column address decoding?



Use an 8K x 32 SRAM = 256 Kb = 2^{18}

$2^{18} = 2^9$ rows x 2^9 columns

Row decoder is 9 to 512 decoder

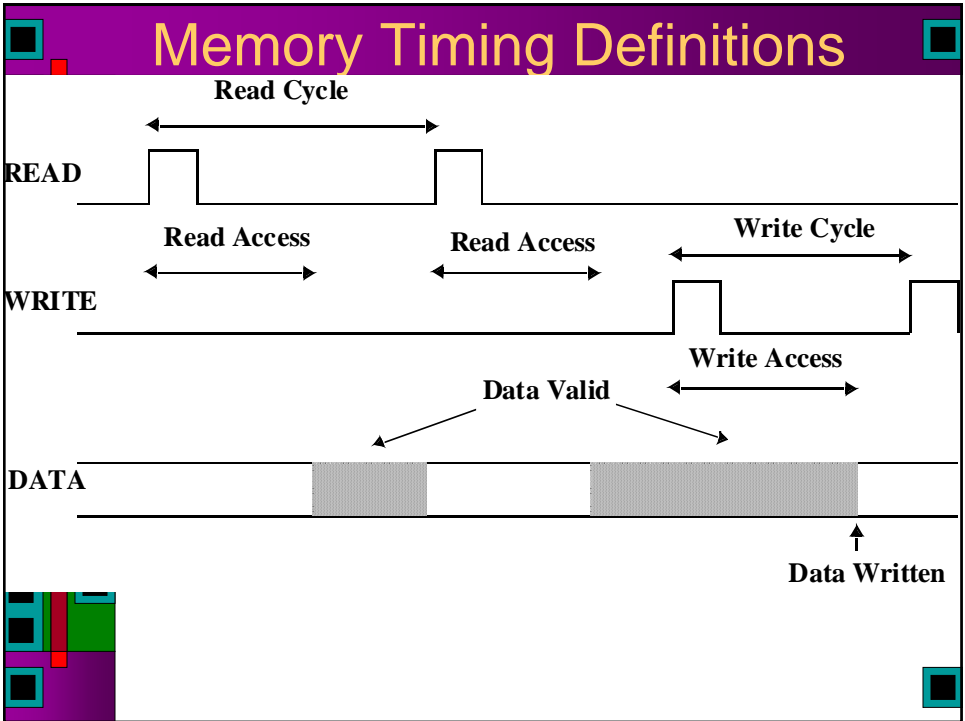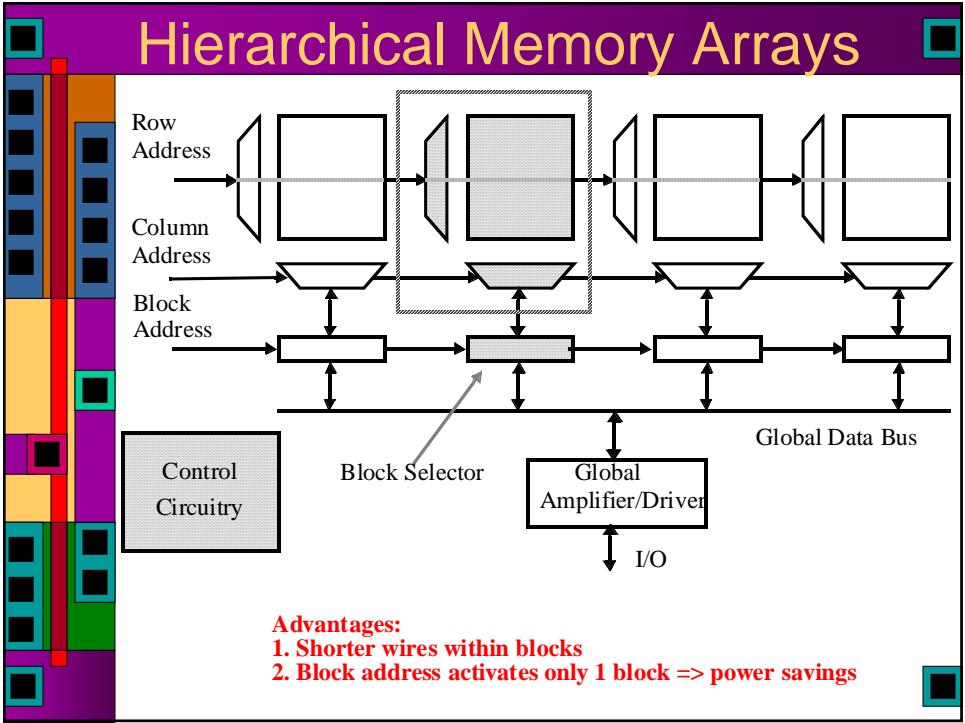
Every 32 (2^5) columns is a 'word', and we only need to decode words. So, column decoder needs to decode 2^4 words, so need a 4 to 16 column decoder.



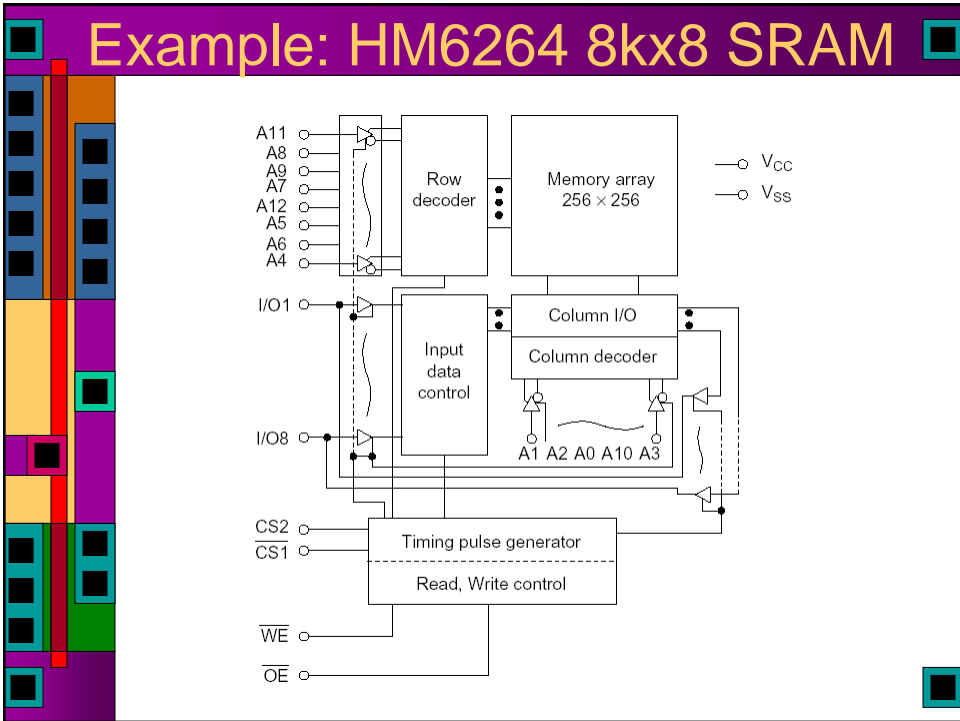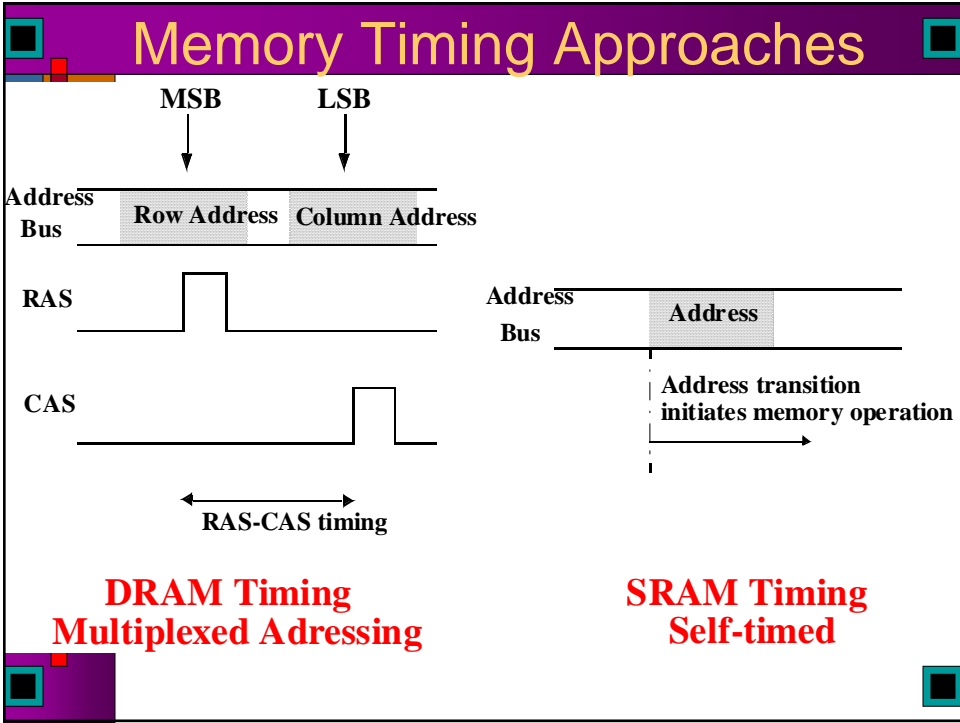

HM6264 Interface

HM6264BLP/BLSP/BLFP Series

 

(Top view)

Pin Description

Pin name	Function	Pin name	Function
A0 to A12	Address input	\overline{WE}	Write enable
I/O1 to I/O8	Data input/output	\overline{OE}	Output enable
$\overline{CS1}$	Chip select 1	NC	No connection
$\overline{CS2}$	Chip select 2	V_{CC}	Power supply
		V_{SS}	Ground

Function Table

Function Table


\overline{WE}	$\overline{CS1}$	$\overline{CS2}$	\overline{OE}	Mode	V_{CC} current	I/O pin	Ref. cycle
x	H	x	x	Not selected (power down)	I_{SB}, I_{SB1}	High-Z	—
x	x	L	x	Not selected (power down)	I_{SB}, I_{SB1}	High-Z	—
H	L	H	H	Output disable	I_{CC}	High-Z	—
H	L	H	L	Read	I_{CC}	Dout	Read cycle (1)–(3)
L	L	H	H	Write	I_{CC}	Din	Write cycle (1)
L	L	H	L	Write	I_{CC}	Din	Write cycle (2)



Note: x: H or L


Timing

Parameter	Symbol	HM6264B-8L		HM6264B-10L		Unit	Notes	
		Min	Max	Min	Max			
Read cycle time	t_{RC}	85	—	100	—	ns		
Address access time	t_{AA}	—	85	—	100	ns		
Chip select access time	$\overline{CS1}$	t_{CO1}	—	85	—	100	ns	
	CS2	t_{CO2}	—	85	—	100	ns	
Output enable to output valid		t_{OE}	—	45	—	50	ns	
Chip selection to output in low-Z	$\overline{CS1}$	t_{LZ1}	10	—	10	—	ns	2
	CS2	t_{LZ2}	10	—	10	—	ns	2
Output enable to output in low-Z		t_{OLZ}	5	—	5	—	ns	2
Chip deselection in to output in high-Z	$\overline{CS1}$	t_{HZ1}	0	30	0	35	ns	1, 2
	CS2	t_{HZ2}	0	30	0	35	ns	1, 2
Output disable to output in high-Z		t_{OHZ}	0	30	0	35	ns	1, 2
Output hold from address change		t_{OH}	10	—	10	—	ns	

Read Cycle 1

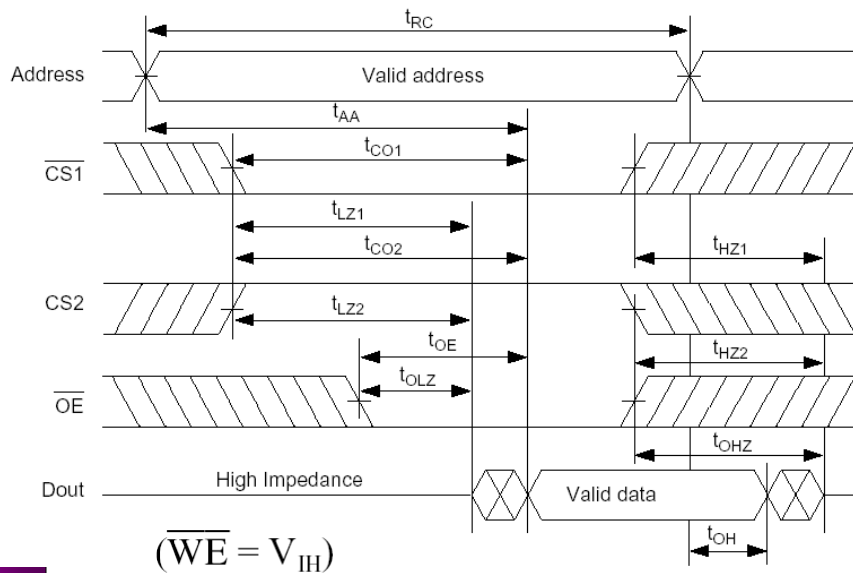

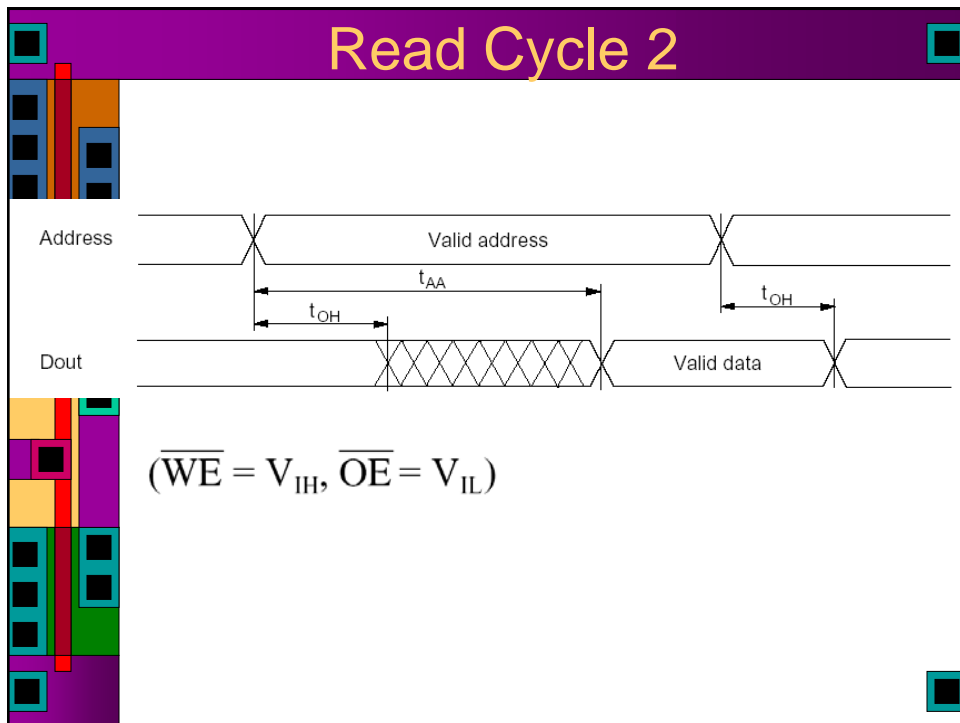
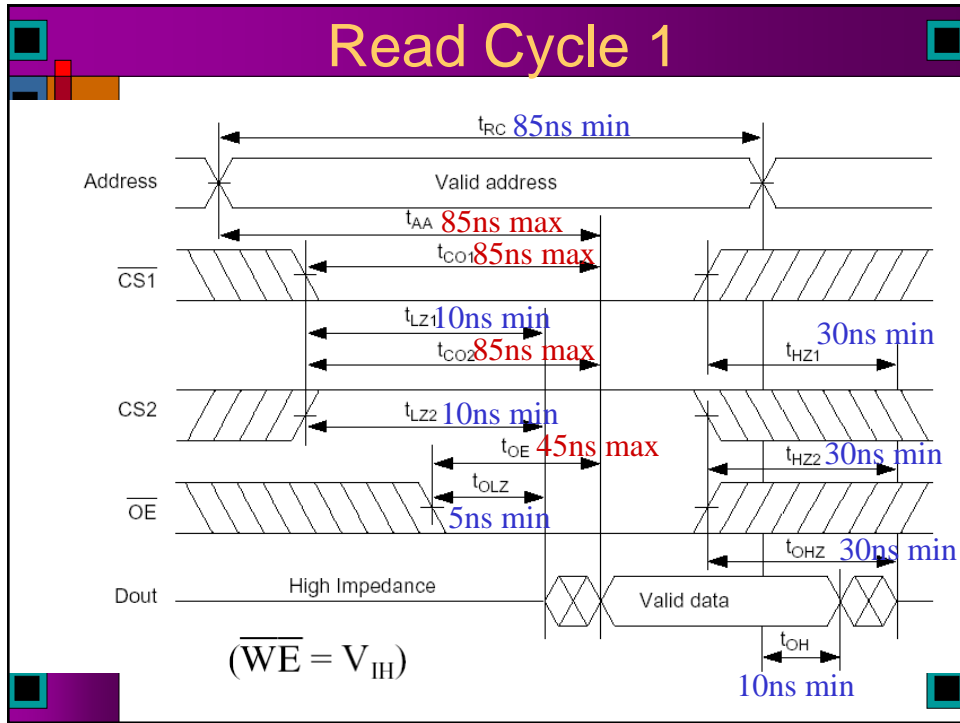


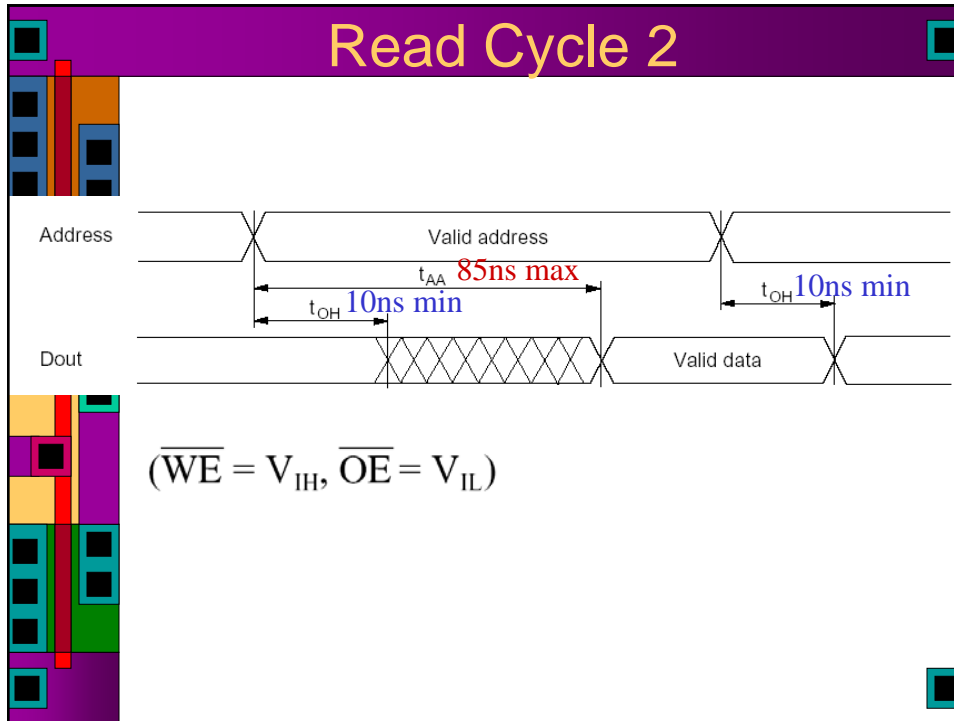


Write Timing

Parameter	Symbol	HM6264B-8L		HM6264B-10L		Unit	Notes
		Min	Max	Min	Max		
Write cycle time	t_{WC}	85	—	100	—	ns	
Chip selection to end of write	t_{CW}	75	—	80	—	ns	2
Address setup time	t_{AS}	0	—	0	—	ns	3
Address valid to end of write	t_{AW}	75	—	80	—	ns	
Write pulse width	t_{WP}	55	—	60	—	ns	1, 6
Write recovery time	t_{WR}	0	—	0	—	ns	4
\overline{WE} to output in high-Z	t_{WHZ}	0	30	0	35	ns	5
Data to write time overlap	t_{DW}	40	—	40	—	ns	
Data hold from write time	t_{DH}	0	—	0	—	ns	
Output active from end of write	t_{OW}	5	—	5	—	ns	
Output disable to output in high-Z	t_{OHZ}	0	30	0	35	ns	5

Notes: 1. A write occurs during the overlap of a low $\overline{CS1}$, and high $CS2$, and a high \overline{WE} . A write begins at the latest transition among $\overline{CS1}$ going low, $CS2$ going high and \overline{WE} going low. A write ends at the earliest transition among $\overline{CS1}$ going high $CS2$ going low and \overline{WE} going high. Time t_{WP} is measured from the beginning of write to the end of write.

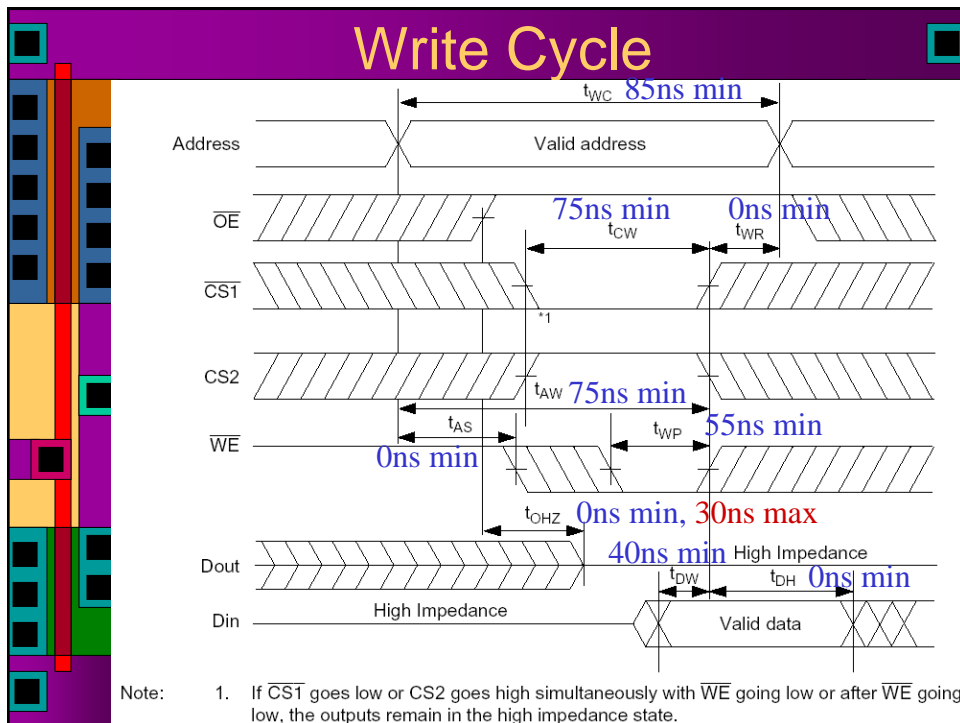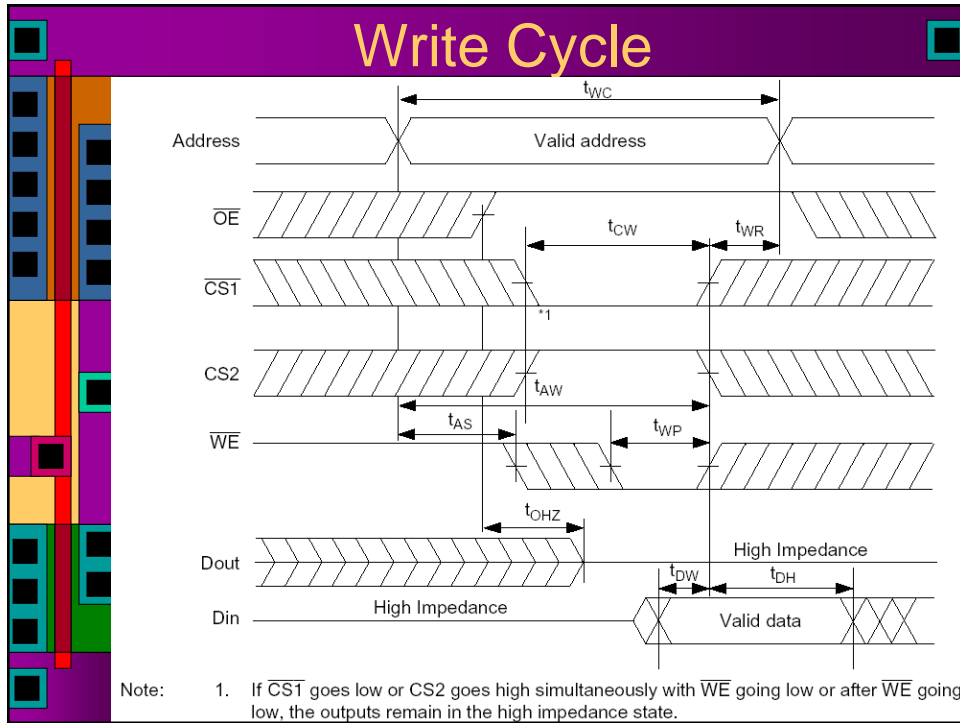


What Does All This Mean


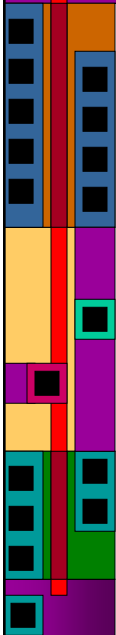


- ▶ For a read:
 - ▶ If you assert CS1, CS2, address, and OE all at the same time, it will be max 85ns before valid data are available at chip outputs
- ▶ For a write:
 - ▶ You can assert CS1, CS2, address, data, and WE all at the same time if you want to
 - ▶ You need to wait 55ns from WE edge, or 75ns from CS1/CS2 edge for write to have happened

R/W Memories In General

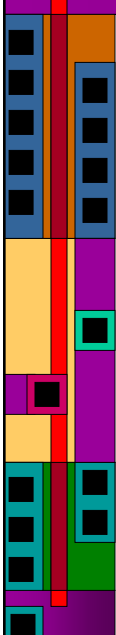


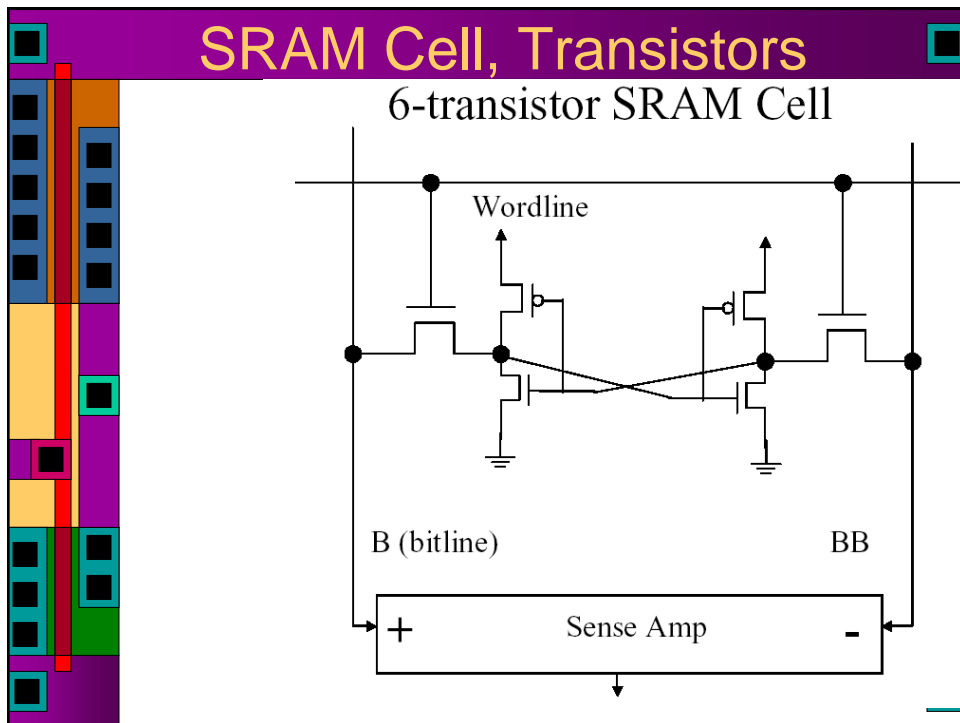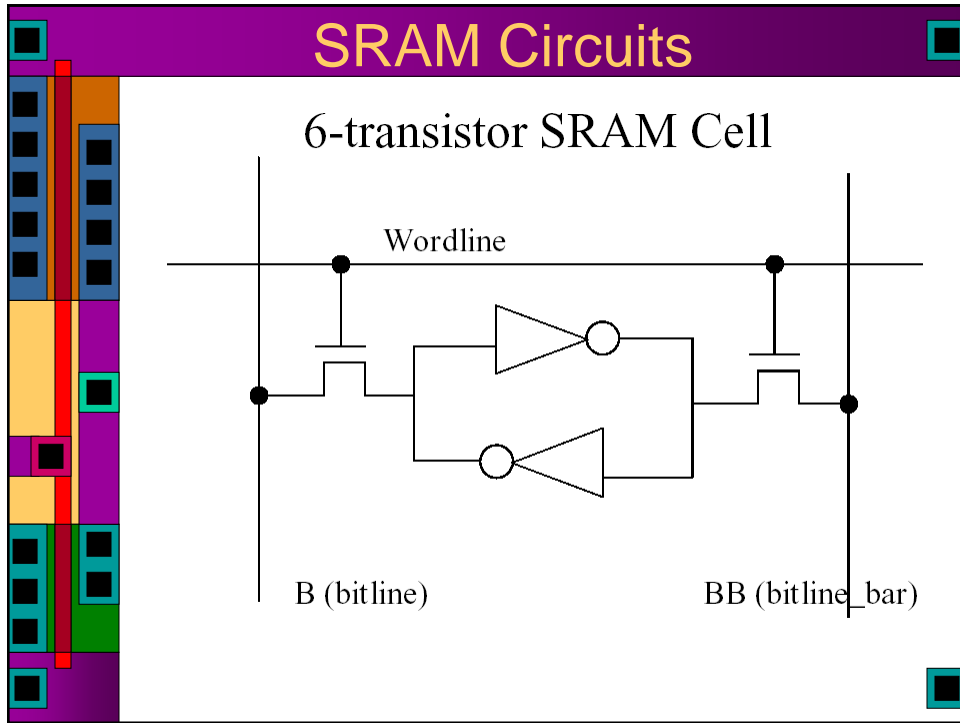- **STATIC (SRAM)**
 - Data stored as long as supply is applied
 - Large (6 transistors/cell)
 - Fast
 - Differential
- **DYNAMIC (DRAM)**
 - Periodic refresh required
 - Small (1-3 transistors/cell)
 - Slower
 - Single Ended




SRAM, Resistive Pullups

6-transistor SRAM Cell

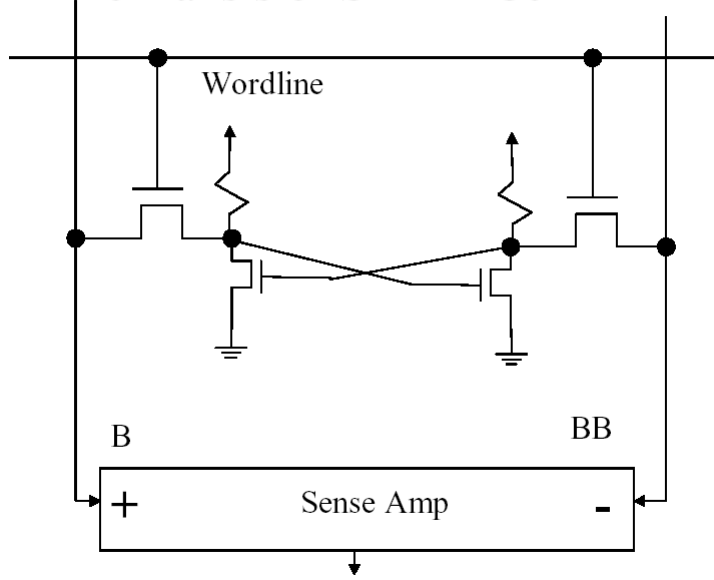


Array-Structured Memory

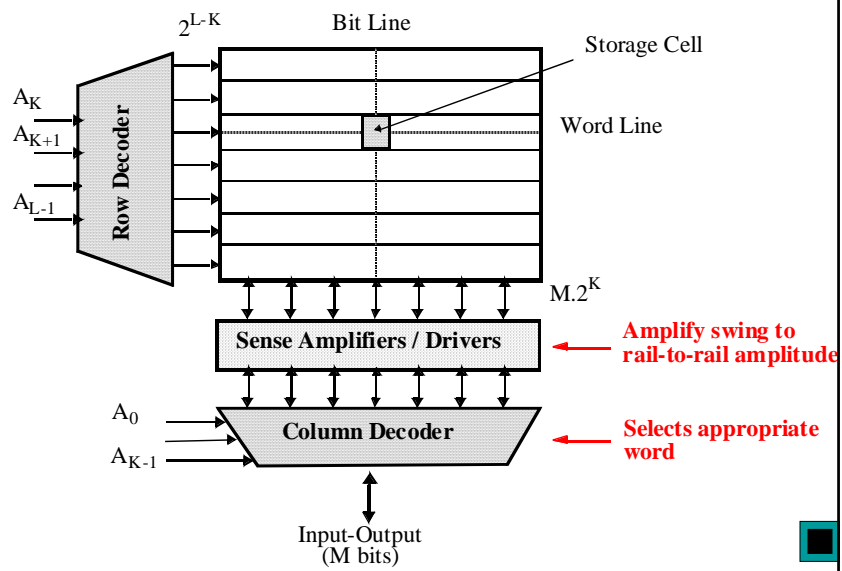Problem: ASPECT RATIO or HEIGHT \gg WIDTH




Memory Column

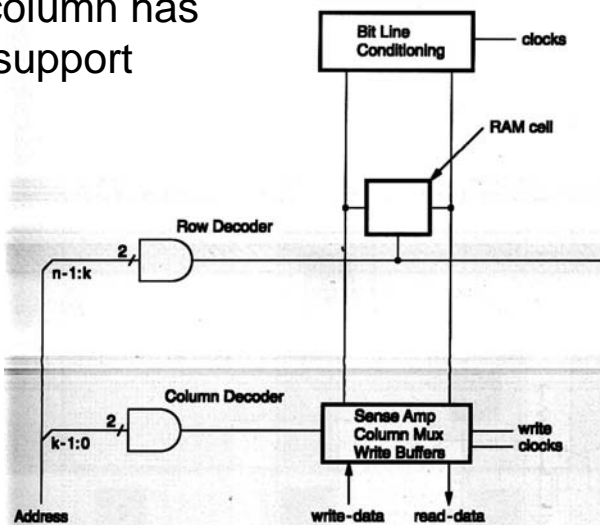- ▶ Each column has all the support circuits




Reading the Bit

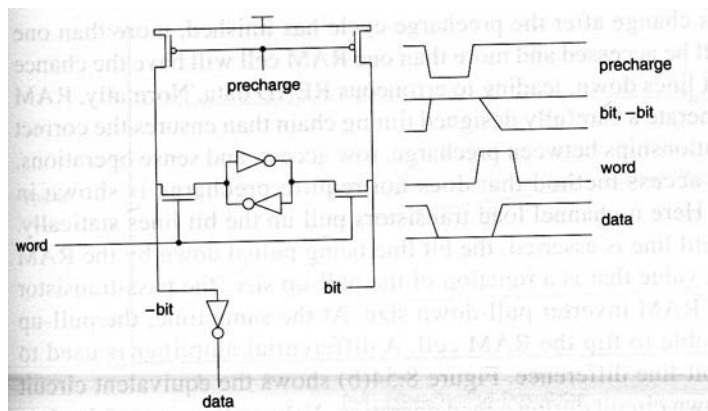


- ▶ Single-ended read using an inverter
- ▶ Dynamic pre-charge on the bit lines
 - ▶ P-types pull bit lines high

Reading the Bit 2

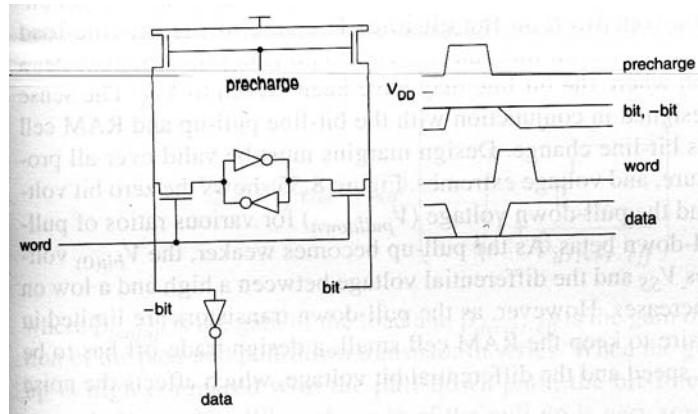


- ▶ Single-ended read using an inverter
- ▶ Dynamic pre-charge on the bit lines
 - ▶ Note the N-types used as pull-ups

Reading the Bit 3

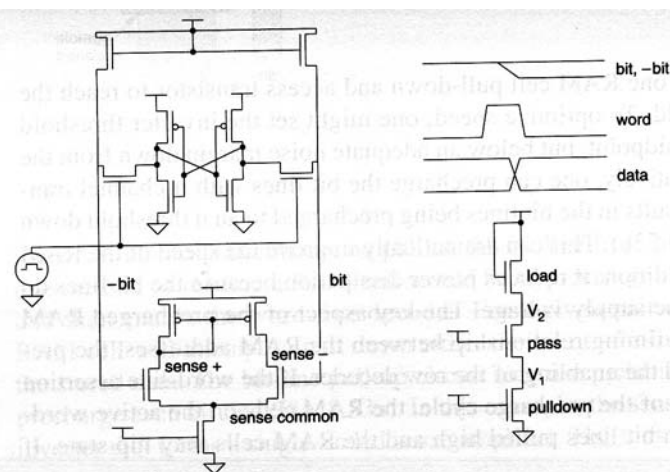


- ▶ Differential read using sense amp
- ▶ Static N-type pullup on the bit lines

Read Waveforms

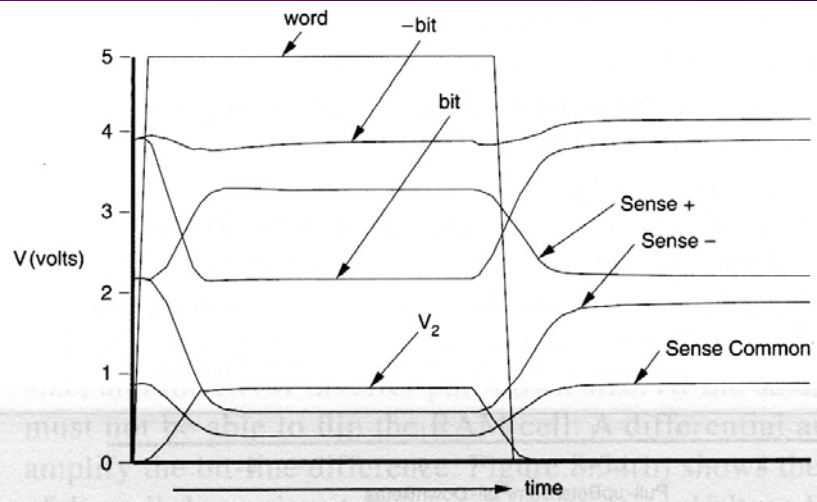

Sense Amp

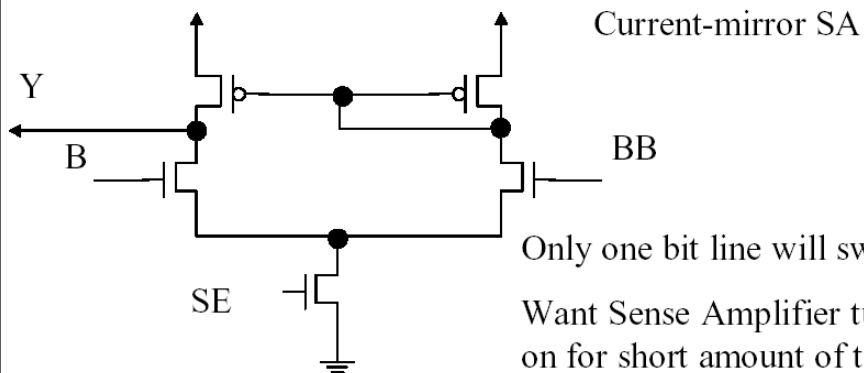

Current-mirror SA


BB

Only one bit line will swing.


Want Sense Amplifier turned on for short amount of time in order to save power.

Job of SA is to sense bit line swing, amplify to full swing output.


Sense Amp Transistors

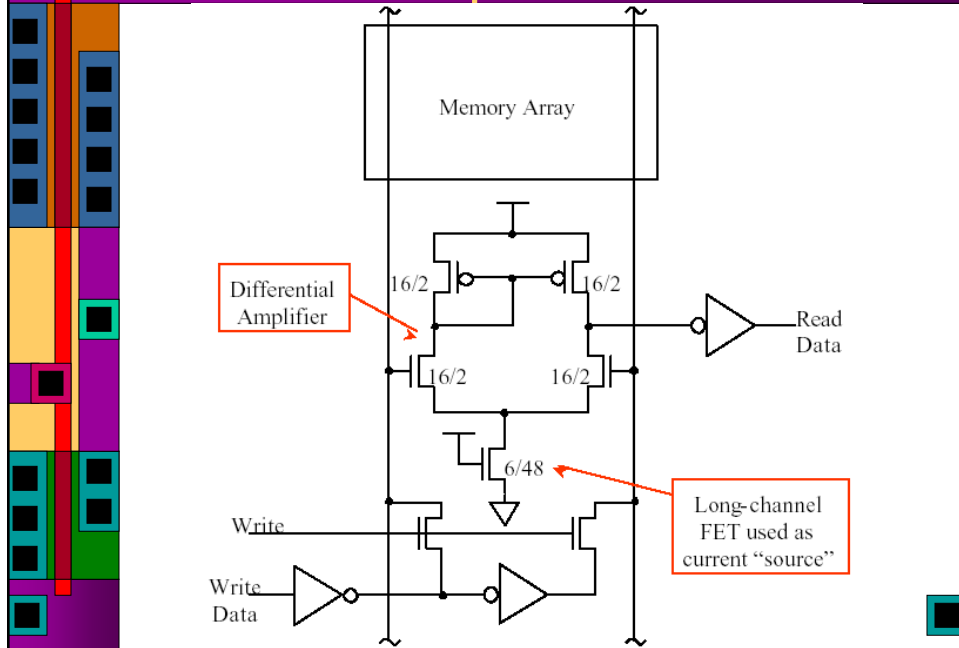


Column Organization


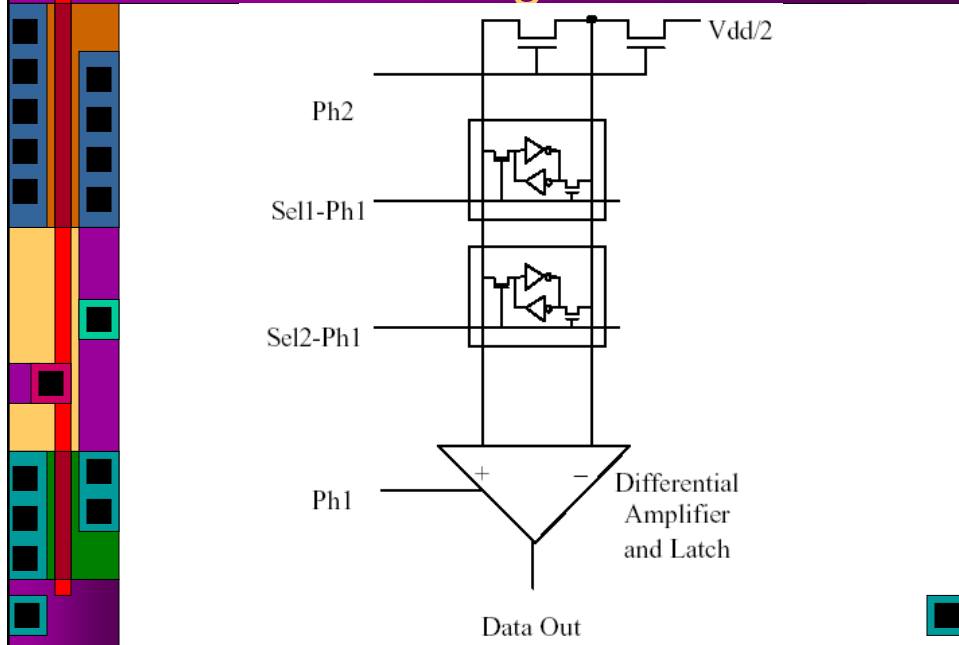


Write Circuits

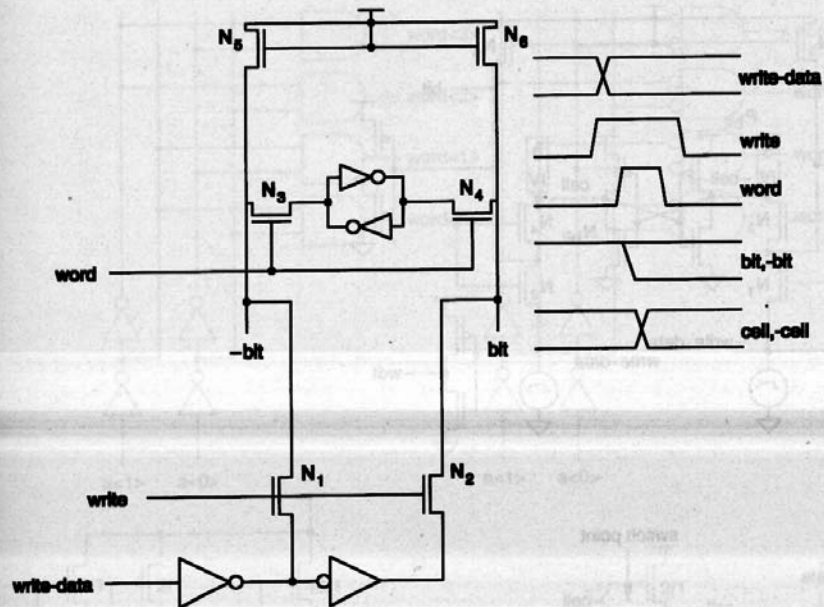


Write Circuit Simulation

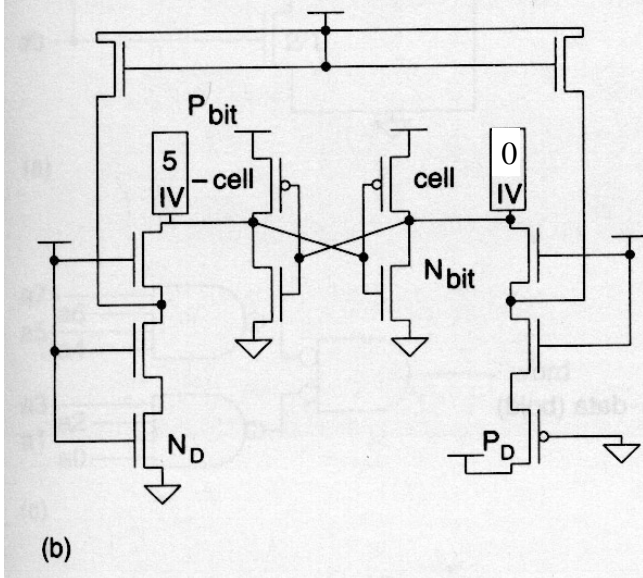

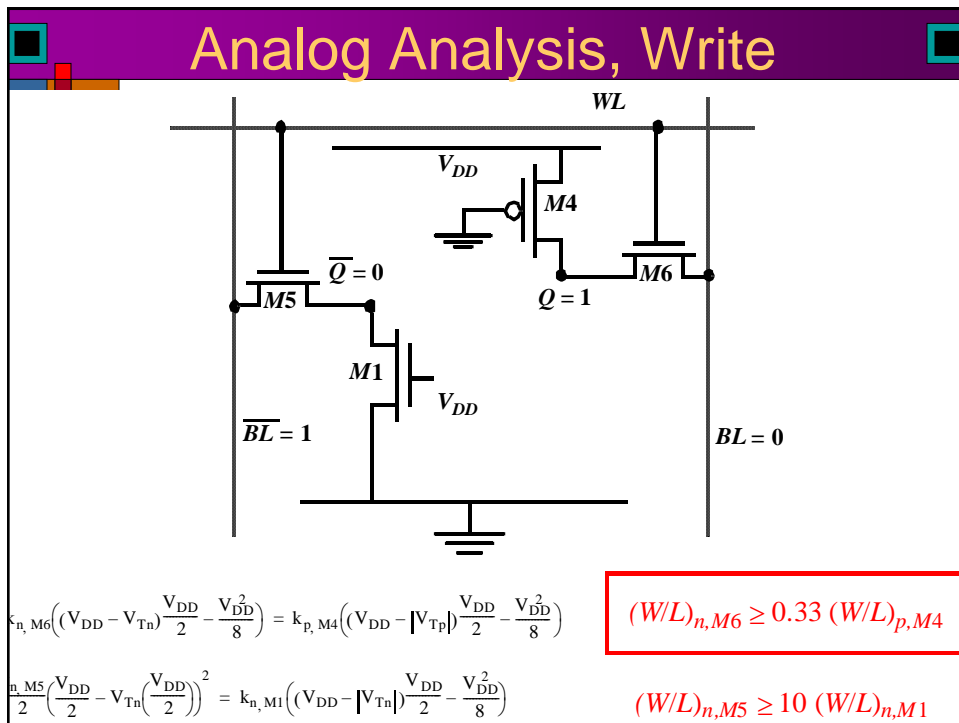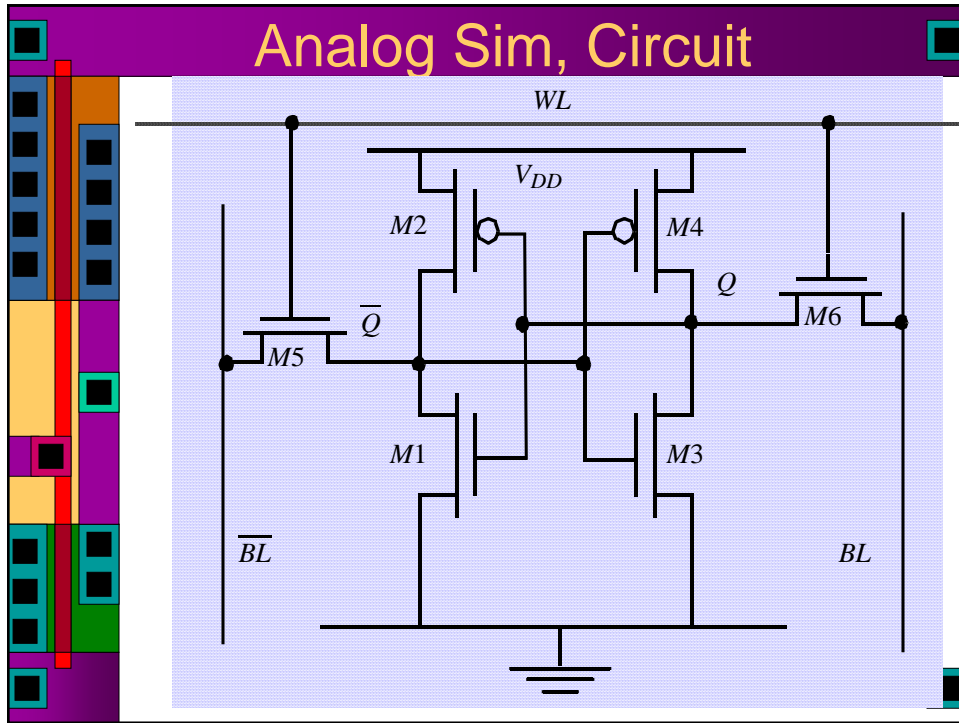


Analog Analysis, Read


 




$$\frac{k_{n,M5}}{2} \left(\frac{V_{DD}}{2} - V_{Tn} \left(\frac{V_{DD}}{2} \right) \right)^2 = k_{n,M1} \left((V_{DD} - |V_{Tn}|) \frac{V_{DD}}{2} - \frac{V_{DD}^2}{8} \right)$$

$$(W/L)_{n,M5} \leq 10 (W/L)_{n,M1}$$


6T SRAM Layout

 

 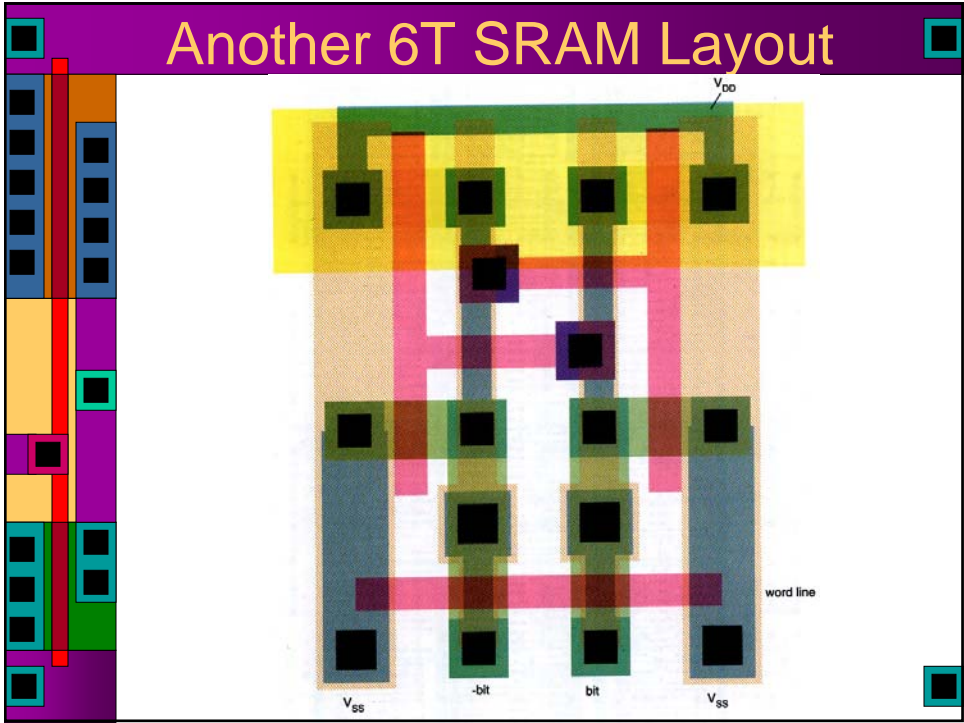

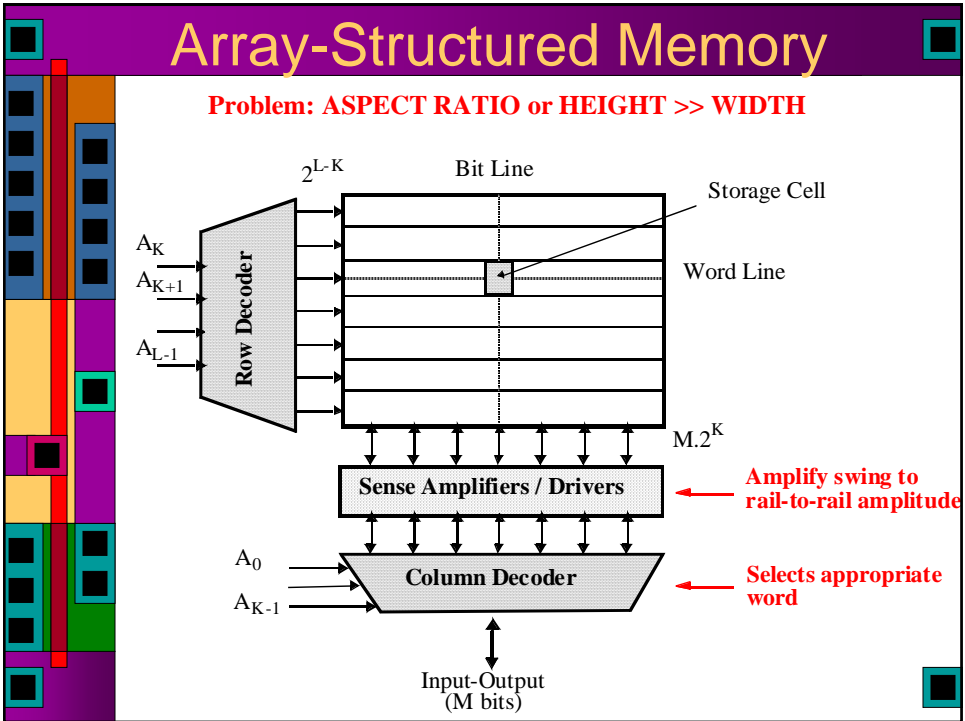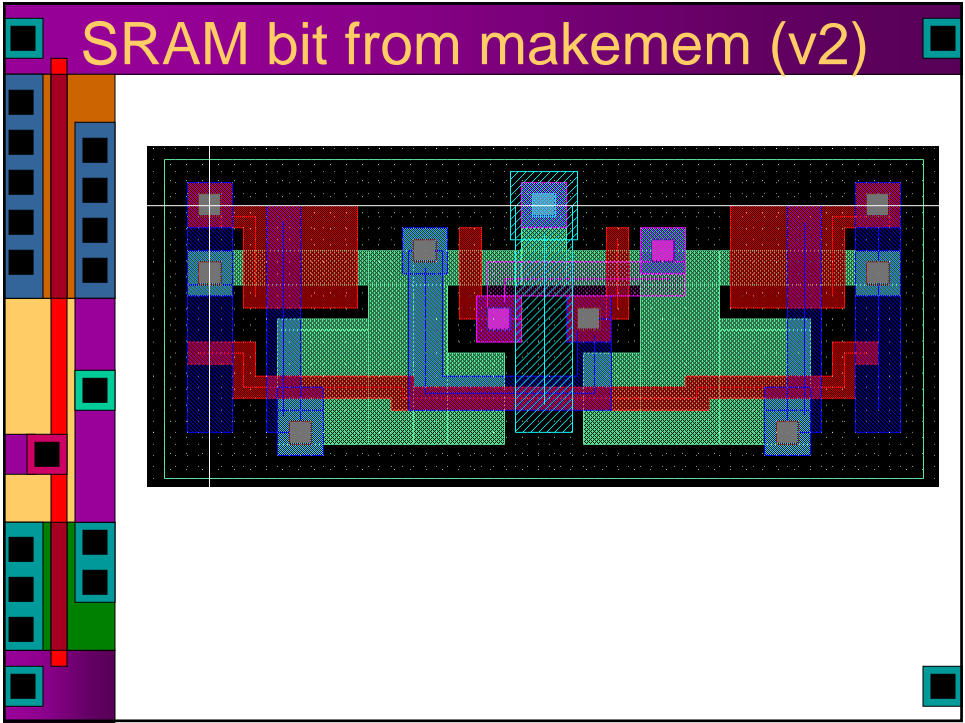


Row Decoders

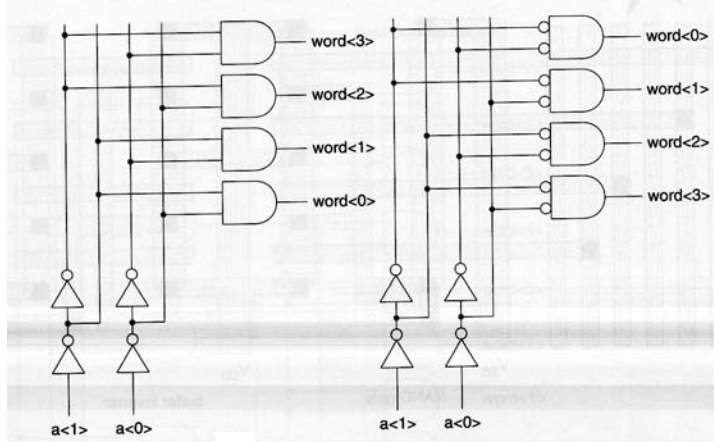

- ▶ Select exactly one of the memory rows
- ▶ Simple versions are just gates

Row Decoder Gates

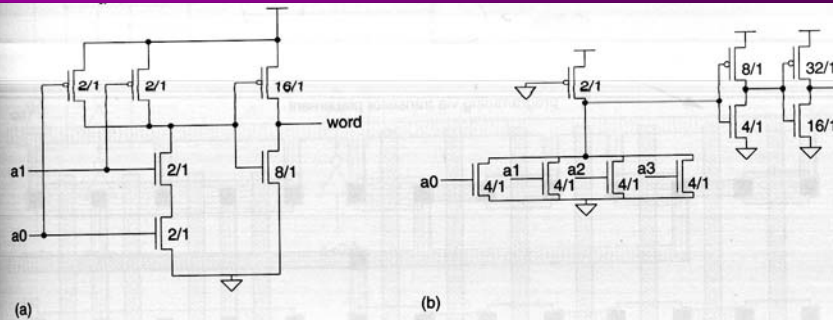



- ▶ Standard gates
- ▶ Or, pseudo-nmos gates with static pull up
 - ▶ Easier to make large fan-in NOR

Pre-decode Row Decoder

▶ Multiple levels of decoding can be more efficient layout


Pre-decode Row Decoder

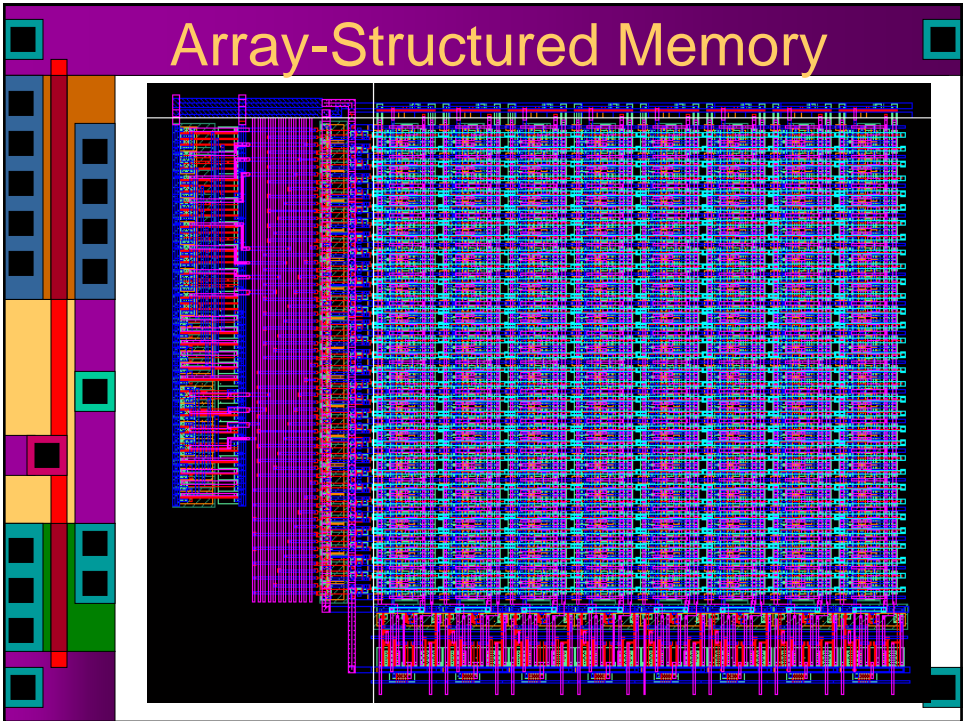 ▶ Other circuit tricks for building row decoders...




Sharing Sense Amps

Sharing Sense Amplifiers

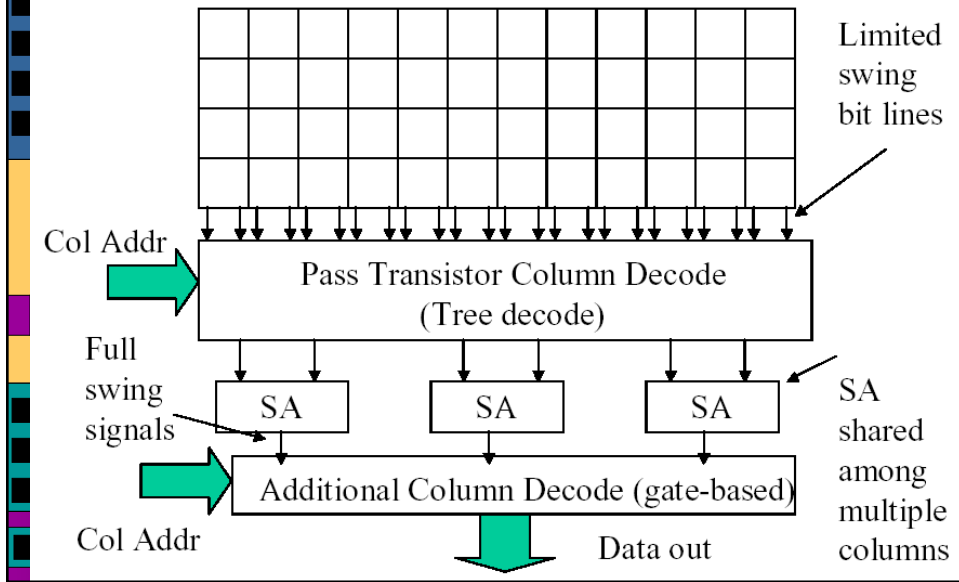

Sense Amp Mux


4 to 1 Tree Decoder (pg. 595, Rabaey)

 


Need to use pass transistors because of limited swing.

Number of pass transistors in series is a concern, but limited swing helps speed.

Sense Amp Mux

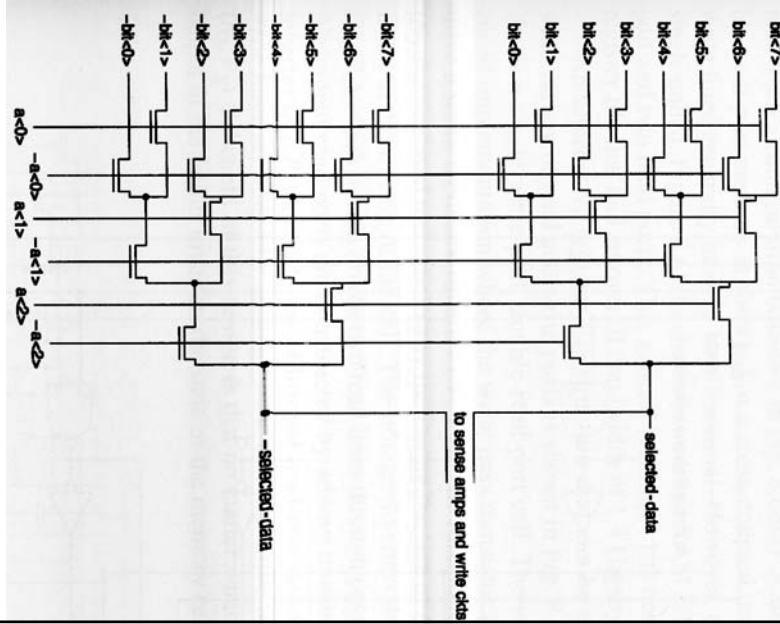

Decoded Column Decode

 


Improving Speed, Power

Critical path runs through row decode, word line assertion


- Need smaller decoding, less word line capacitance in order to improve speed.
- Break a large array into smaller sub-arrays, and use hierarchical decoding to select a sub array
 - PowerPC 32K x 8 cache broken into 32 blocks, each 1K x 8
 - Cypress 1Mb Dual Port broken into 32 blocks, each 32 K bits ($2^5 \times 2^5 \times 2^{10} = 2^{20}$). Each blocks is 512 rows x 64 columns
 - Mitsubishi SRAM (Rabaey text). 32 blocks of 128K bits (1024 rows x 128 columns)
- Only one sub-array will be activated, saves power!!!!

Multi-Port Memory

 


- ▶ Very common to require multiple read ports
 - ▶ Think about a register file, for example

Multi-Port Register

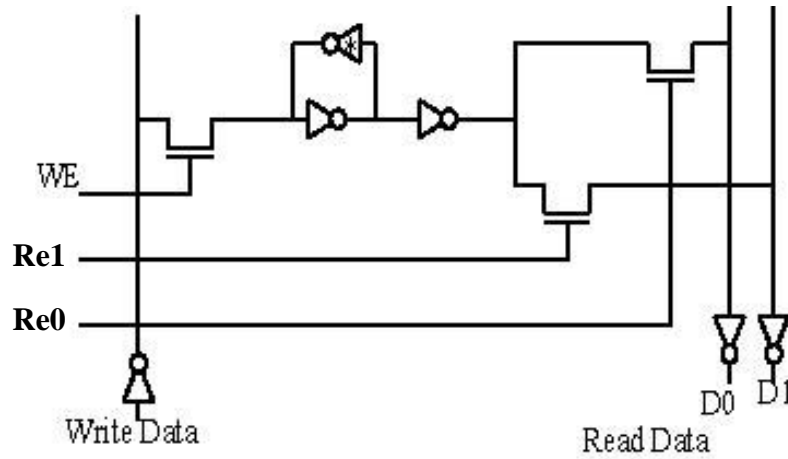


- ▶ Slightly larger cell, but with single-ended read – makes a great register file

Register File

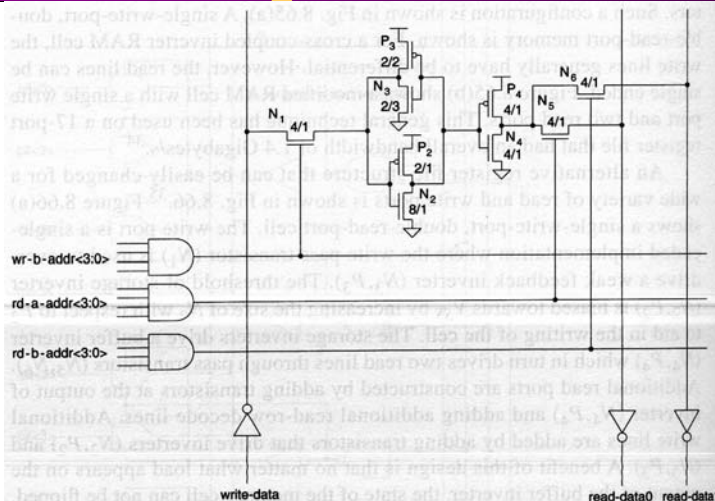



- ▶ Slightly larger cell, but with single-ended read – makes a great register file

Dynamic RAM

 


- ▶ Get rid of the pull-ups!
 - ▶ Store info on capacitors
 - ▶ Means that stored information leaks away



Dynamic RAM...

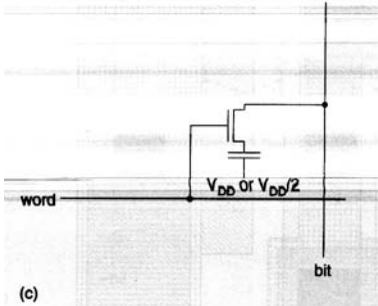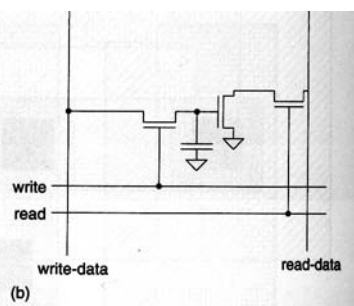

 - ▶ Once you agree to use a capacitor for charge storage there are other ways to build this...




3T DRAM Circuit

 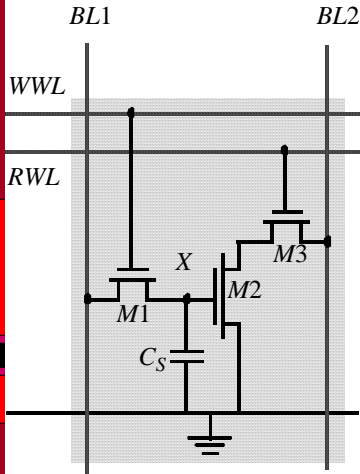


No constraints on device ratios
 Reads are non-destructive
 Value stored at node X when writing a "1" = $V_{WWL} - V_{Tn}$

3T DRAM Layout

 

1 T DRAM Circuit

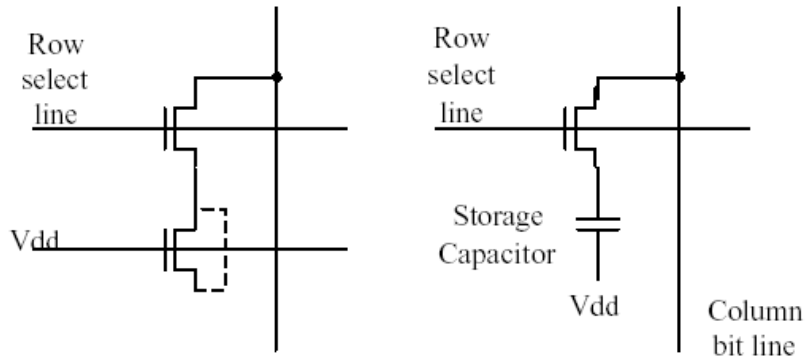


2 Transistor DRAM Cell

Equivalent Circuit

$$C_{storage} = C_{drain} + C_{gate} + C_{source}$$

2-T (1-T) DRAM layout

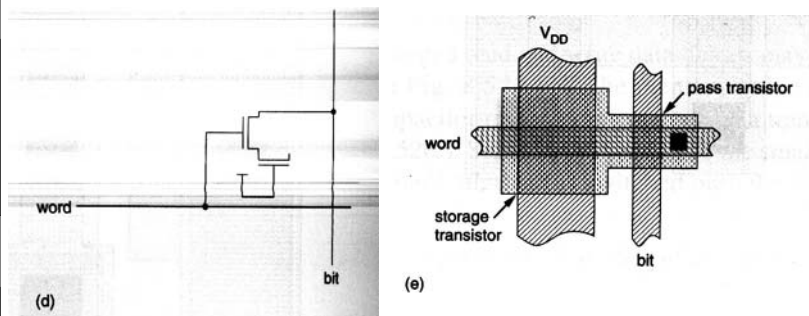

- ▶ Note the increased gate size of the storage transistor
 - ▶ Increases the capacitance

1T DRAM Observations

1T DRAM requires a sense amplifier for each bit line, due to charge redistribution read-out.



DRAM memory cells are single ended in contrast to SRAM cells.

The read-out of the 1T DRAM cell is destructive; read and refresh operations are necessary for correct operation.

Unlike 3T cell, 1T cell requires presence of an extra capacitance that must be explicitly included in the design.

When writing a “1” into a DRAM cell, a threshold voltage is lost. This charge loss can be circumvented by bootstrapping the word lines to a higher value than V_{DD} .

1T DRAM Read/Write

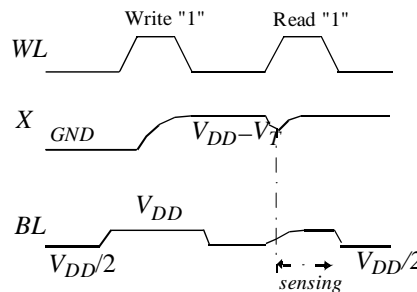
 


Write: C_S is charged or discharged by asserting WL and BL.


Read: Charge redistribution takes place between bit line and storage capacitance

$$\Delta V = V_{BL} - V_{PRE} = (V_{BIT} - V_{PRE}) \frac{C_S}{C_S + C_{BL}}$$

 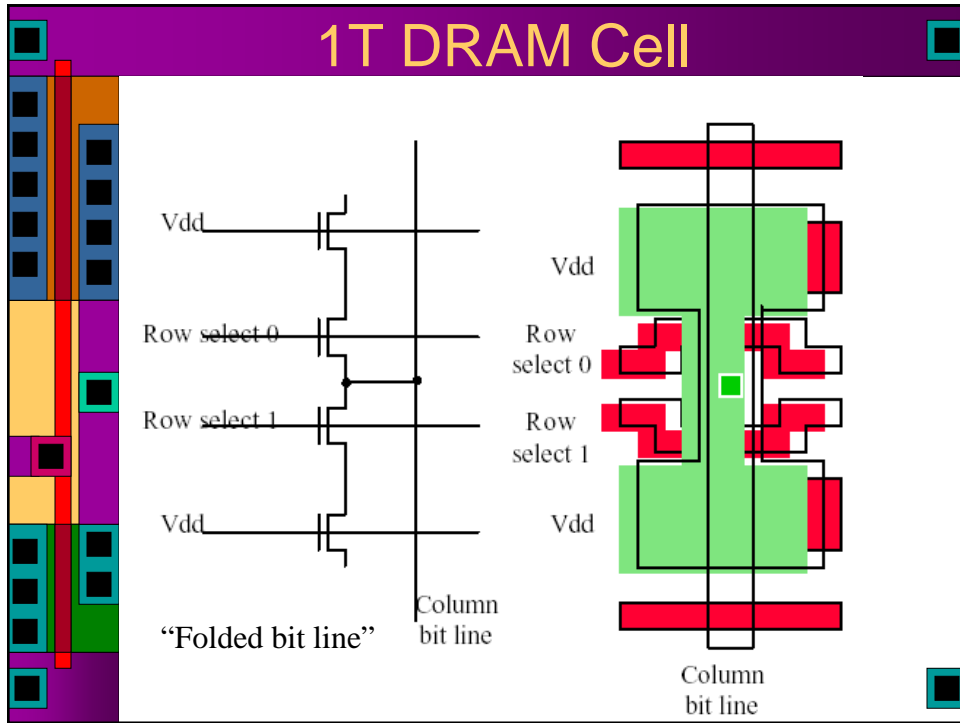
Voltage swing is small; typically around 250 mV.







Reading a 1T DRAM Cell

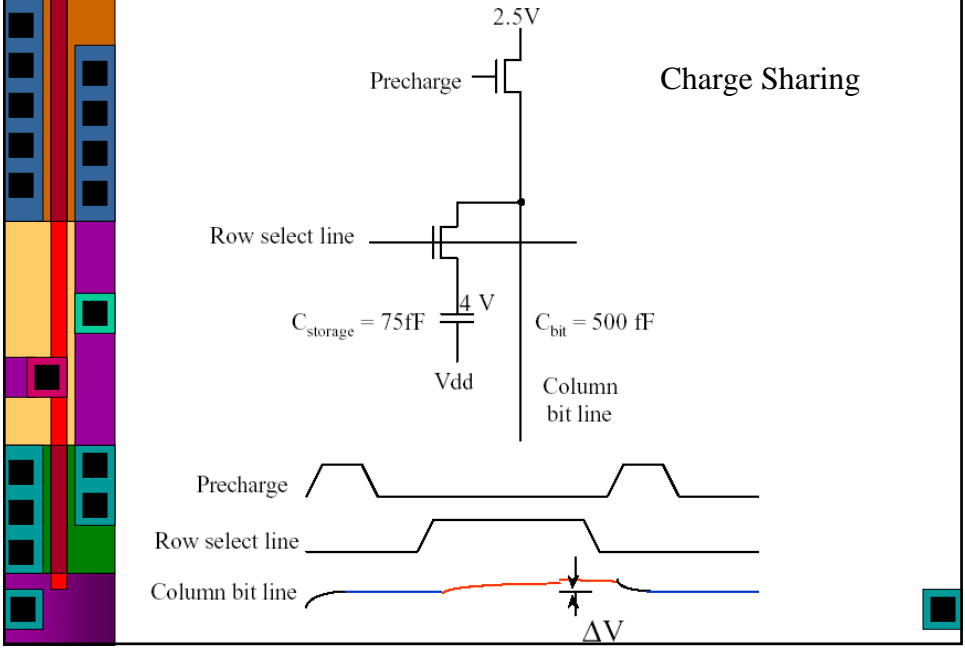

DRAM Sense Amp

 

  


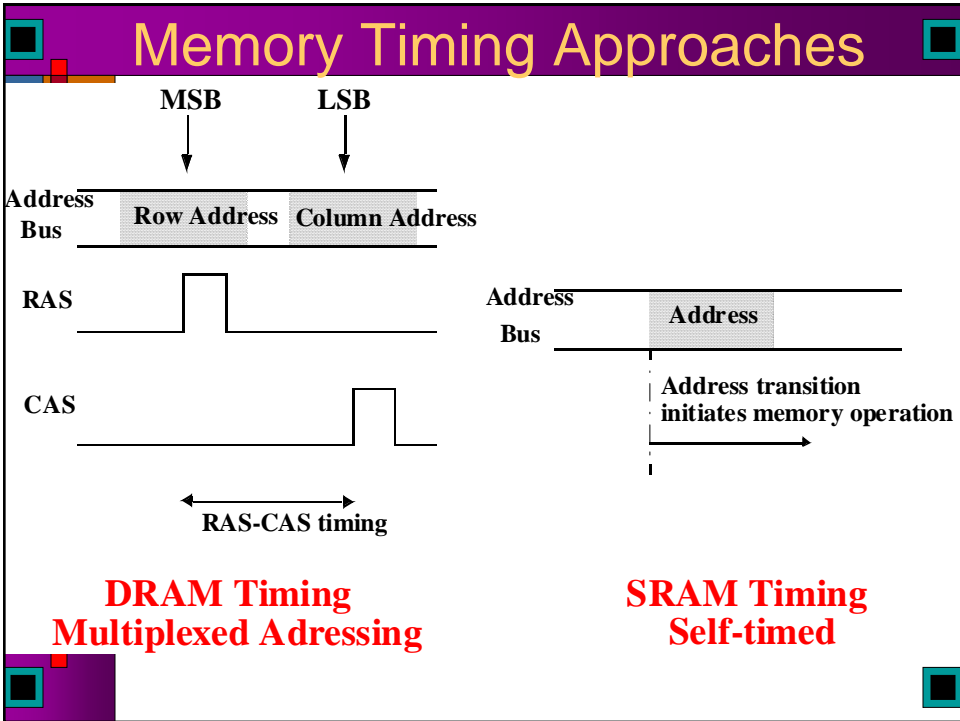 


DRAM Interface

Multiplexed Address bus (Row, Column). RAS# (Row Address Strobe), CAS#(Column Address Strobe) used to latch in address

READ CYCLE

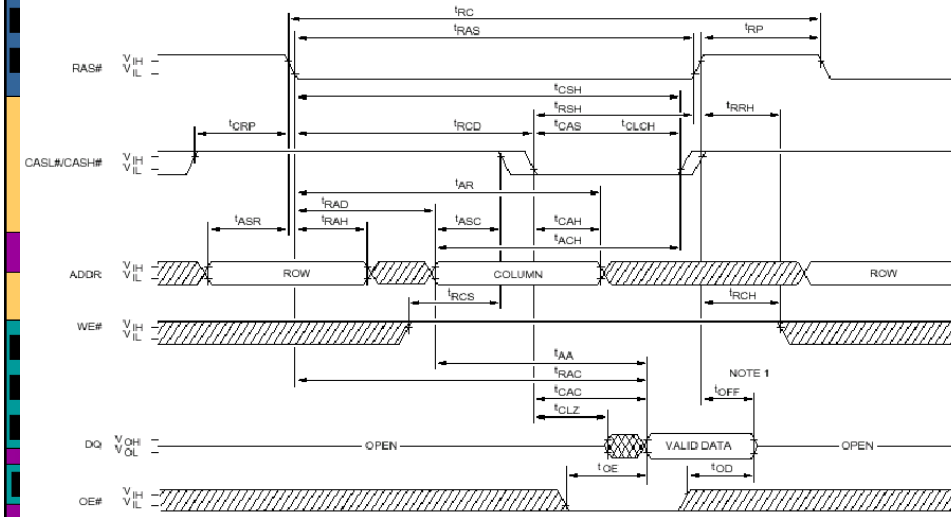

Extended Data Out Page Mode

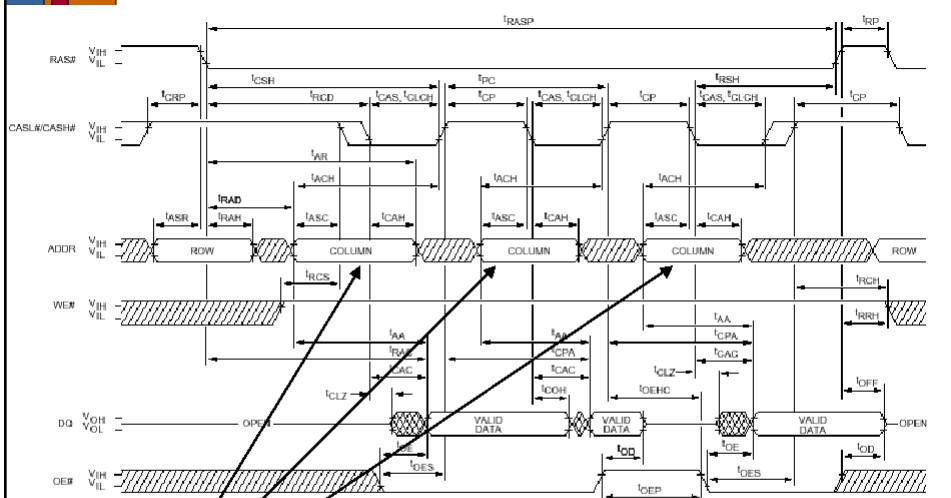

Block transfer. Access different bits on same row, change column address.

Comments on Timing


- Typical times are $T_{ras} = 60$ ns (RAS pulse width), $T_{rc} = 100$ ns
 - Extra time on Read cycle (RAS high) is needed to recharge bitlines
- Block mode transfers (Page mode transfers) read bits from same row
 - Only change column address
 - Time to first bit on row = 50ns, time to successive bits = 25 ns (we have access to all bits on this row, just need to mux them out).

Architectural Issues

- Need to support block transfers efficiently since DRAM used as main memory and reads/writes due to cache fills
- Add a clock to DRAM interface (SDRAM, DDR-SDRAM) to support burst mode operations for cache fills
 - Pentium burst mode is 2-1-1-1 (two clocks for first data, 1 clock for each successive data, address only provided for first data, internal counter on RAM used for address generation).
 - Pentium Pipelined burst mode is:
2-1-1-1; 1*-1-1-1; 1*-1-1-1;
Successive cycles pick up where the last cycle left off.


SDRAM - Use CAS for Bursts

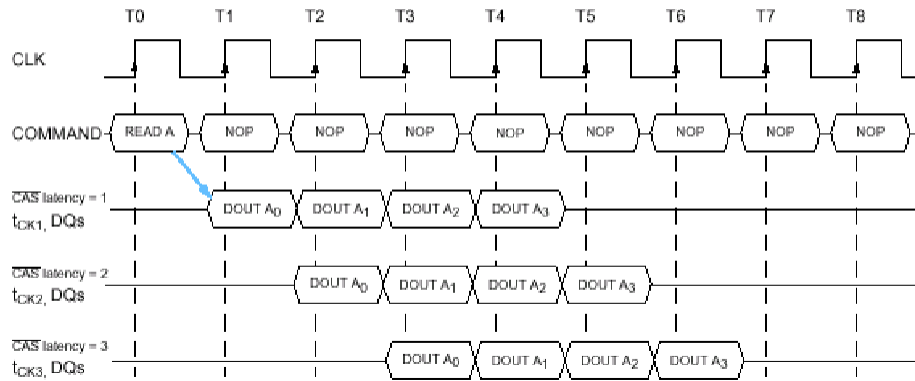Burst Read Operation (Burst Length = 4, CAS latency = 1, 2, 3)



DDR SDRAM

Differential Clocks

 

Two clock latency

Data transferred on each clock crossing

► Double Data Rate

DRAM Timing

- Clock Frequency – 133 Mhz, 100 Mhz
- Two clock latency to first data (20 ns for 100 Mhz clock)
 - SDRAM - 10 ns per location afterwards. For byte-wide, 100 MB/sec transfer rate. 400 MB/sec on 32-bit bus
 - DDR-SDRAM - 5 ns per location afterwards. For byte-wide, 200 MB/sec transfer rate. On 32-bit bus, 800 MB/sec transfer rate.

RAMBUS DRAM (RDRAM)



- DRAM with a high speed interface
- 400 Mhz differential clock, data transferred on each edge
- Reduced swing signaling about a reference voltage
 - Termination voltage is 1.5 V
 - Reference Voltage is 1.0 V
 - Signals swing +/- 200 mv about reference voltage
 - All traces are transmission lines

RDRAM Bandwidth

- External bus is 18 bits wide (2 bytes + 2 parity bits)
- External clock cycle is 400 Mhz, but data is clocked on each edge
 - Actually, external clock is a differential pair and data is sampled at each crossing
- Total Bandwidth is 1.6 GBytes/s
 - $2 \text{ bytes} * 400 \text{ Mhz} * 2 \text{ edges} \Rightarrow 1.6 \text{ Gbytes}$
 - Initial configurations are 4 M x 18 (72 Mbits)

Maximum Bandwidth

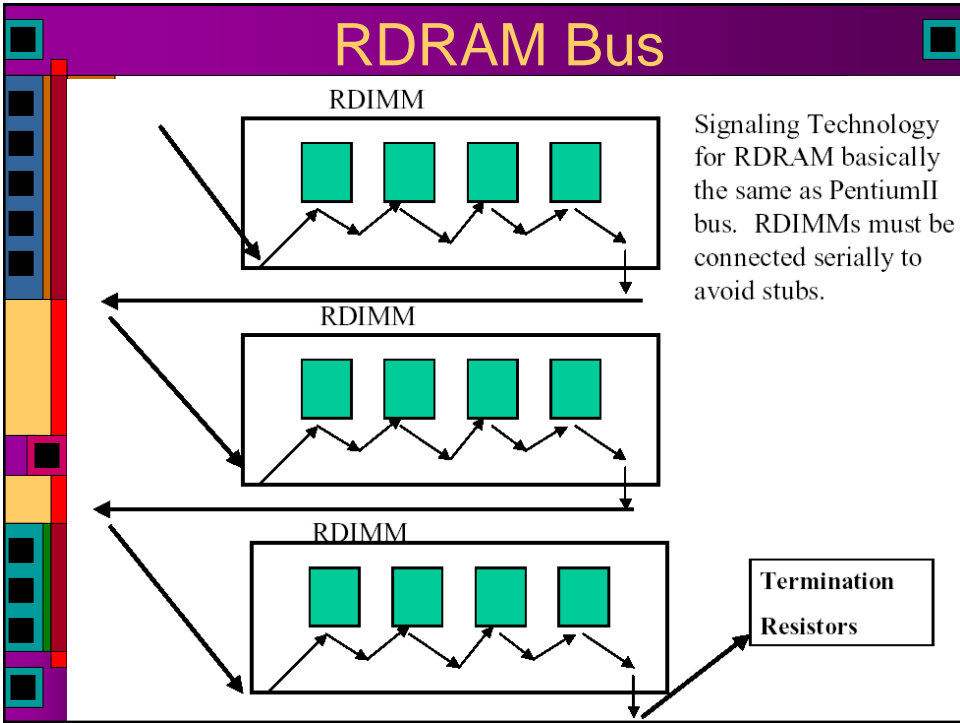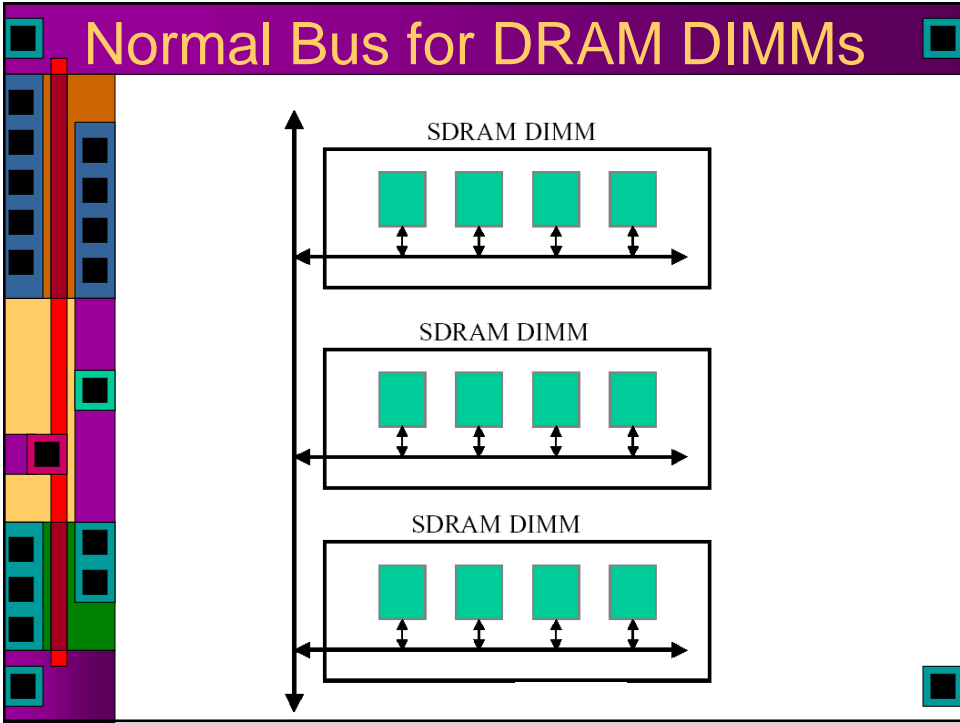- Note that maximum bandwidth with one RDRAM controller is 1.6GB/s.
 - Only one RDRAM chip can be active at a time on RDRAM bus.
 - More RDRAM chips increase capacity, not bandwidth.
 - With normal DRAM and SDRAM, can increase bandwidth by just adding more DRAM chips in parallel from same DRAM controller
 - To double the bandwidth, would need two separate RDRAM controllers



Deep Pipelining - High Latency

IEEE Micro Nov/Dec 1997


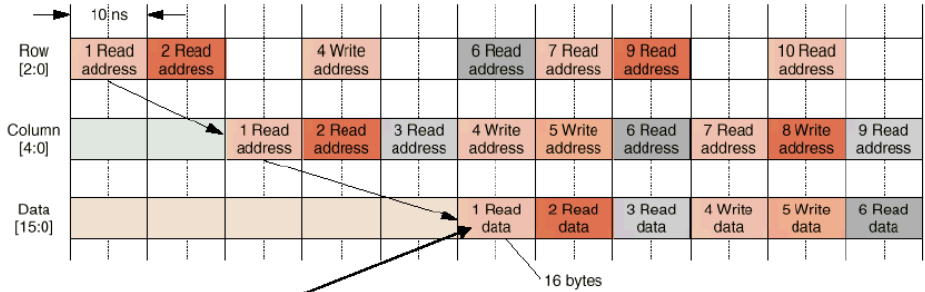




Figure 7. Direct RDRAM interleaved memory transactions at full-memory bandwidth (16 bytes/10 ns).

16 bytes transferred because $4 \text{ clocks} * 2 \text{ edges} * 2 \text{ bytes/transfer}$ (external bus is 16 or 18 bits wide). 20 clock latency, 20 ns from column address)


RDRAM Addressing

 

- 3-Bit Row bus used to give commands to RDRAM
- ROW Activate command used for read
 - 4 clocks transfers 8 groups of 3 bits over Row bus due to dual edge clocking (24 bits total)
 - 24 bits in Row Activate command split between device address (6 bits), bank select (4 bits), row select (9 bits), and reserved bits
- There are no chip select lines, internal register holds device address
 - All chips monitor bus - if bus device address matches internal id, then chip is selected.

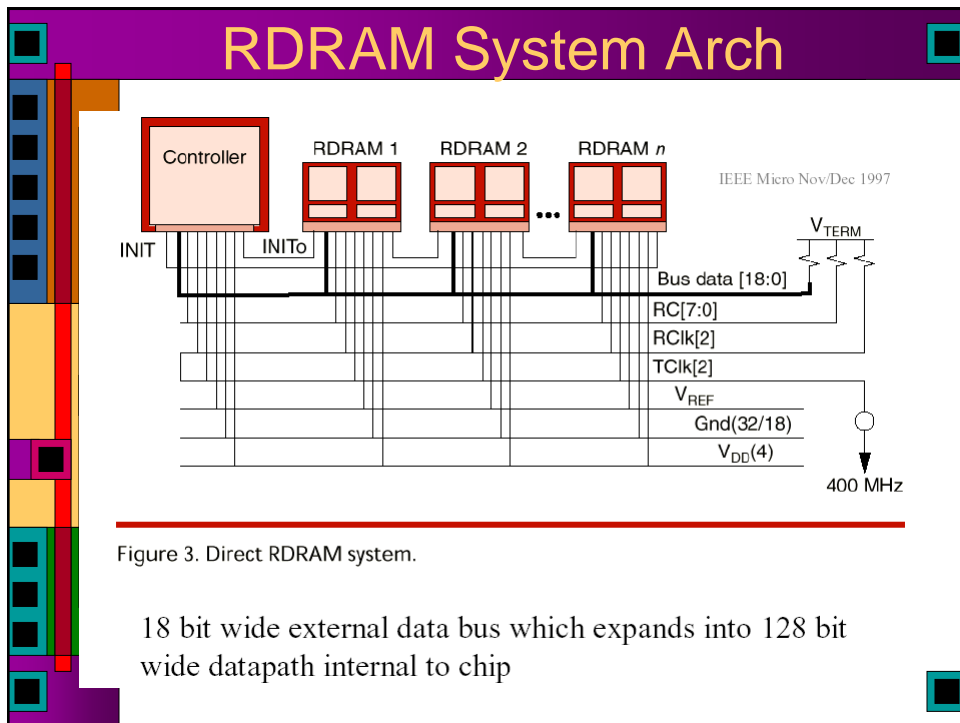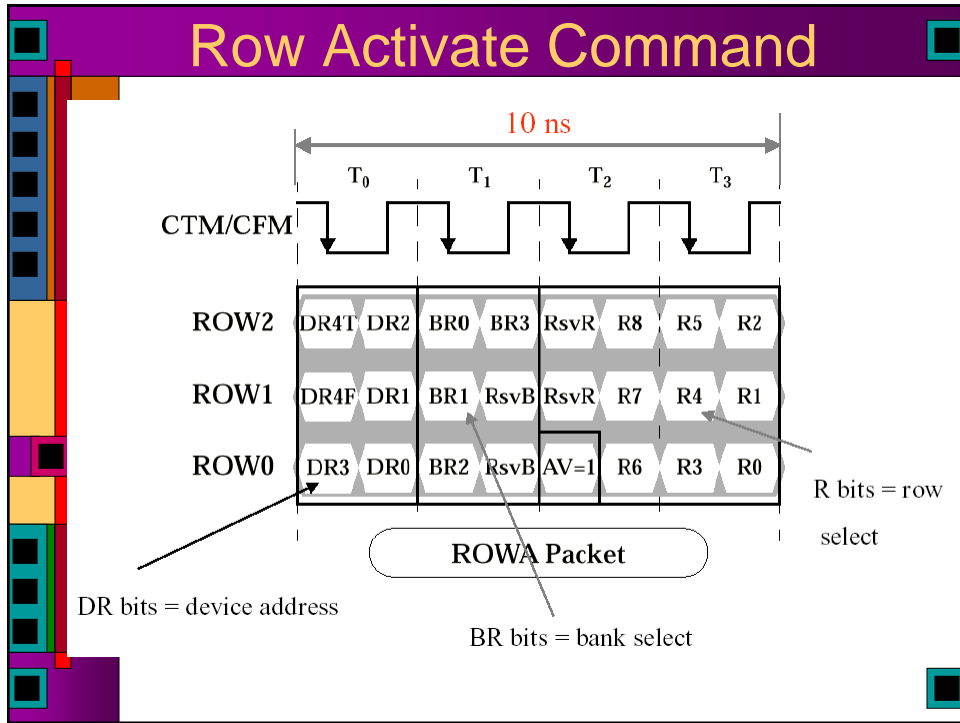

RDRAM Internal Arch

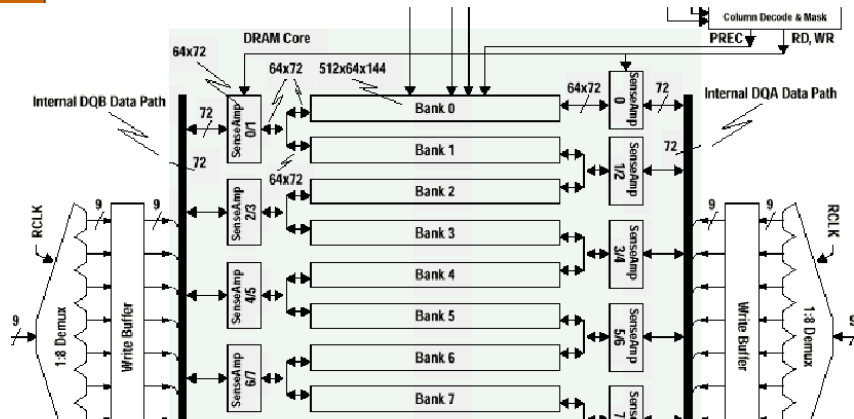

Portion of internal architecture (4M x 16 or 4M x 18)

16 banks of 512 rows of 64 dualocts (1 dualoct = 16 bytes = 128 bits)


2^4 (banks) * 2^9 (rows) * 2^6 (dualocts) * 2^7 (one dualoct) = 2^{26} (64 Mbit)

A dualoct is the smallest addressable unit.


Regular DRAM

- Multiple Banks are key to high throughput
- As one DRAM bank is recovering from read operation, next bank is being accessed
- Essentially on-chip memory interleaving
- Goal is to hide latency and bitline precharge time (recovery time)
 - Latency is access to first byte, critical path through row-decode and word line assertion
 - Bitline Precharge time (recovery time to next access) depends on number of bits in a column (number of rows)

Single Bank DRAM

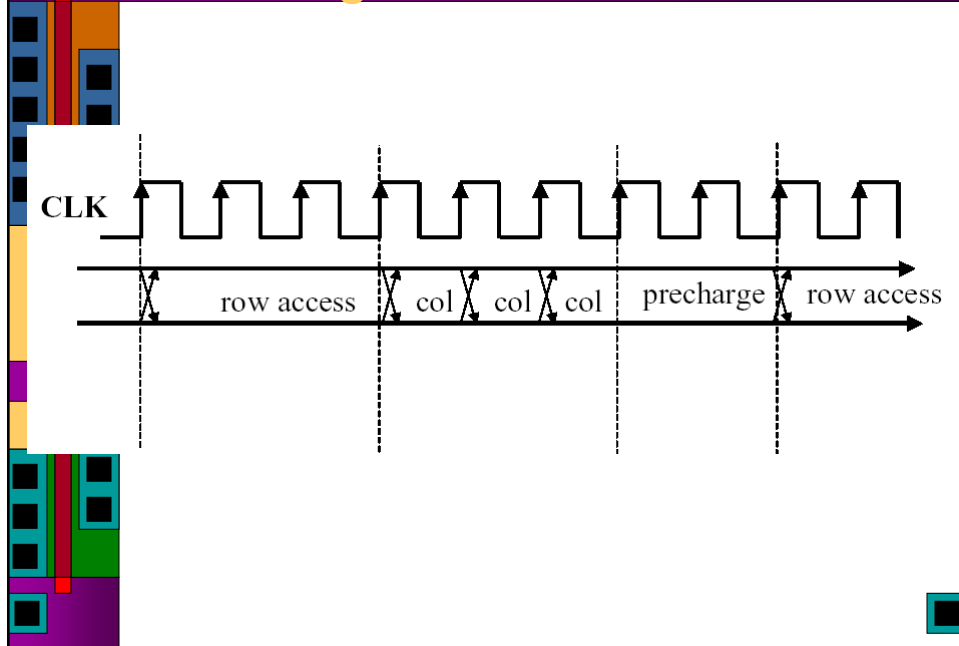

Multi-Bank DRAM

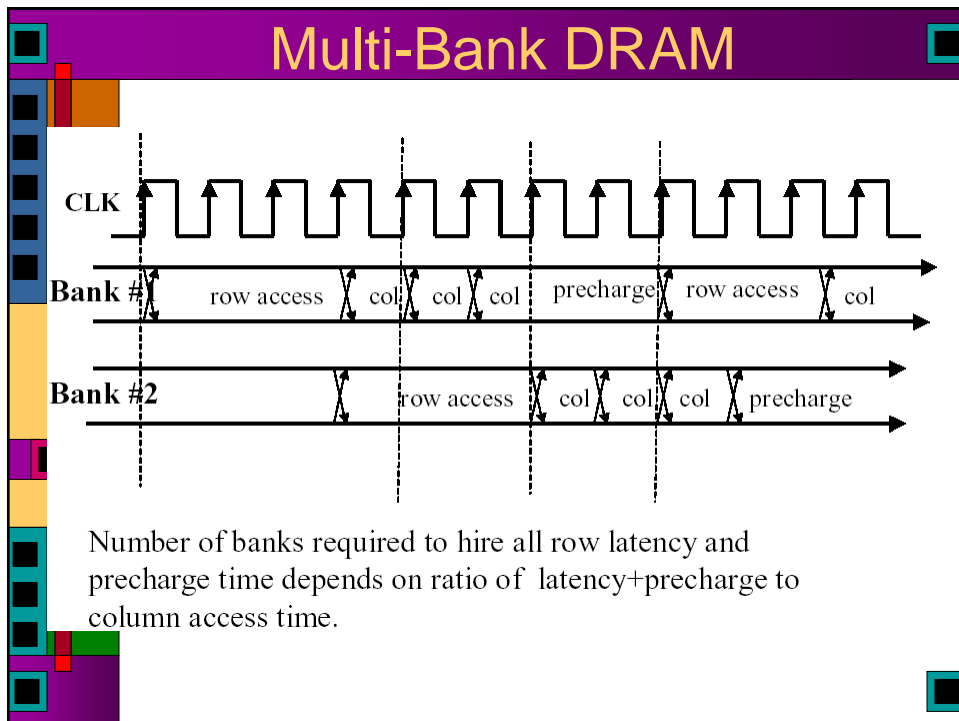

Peak Bandwidth



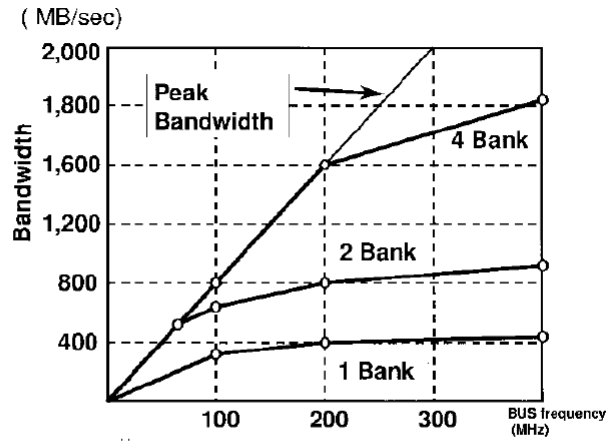
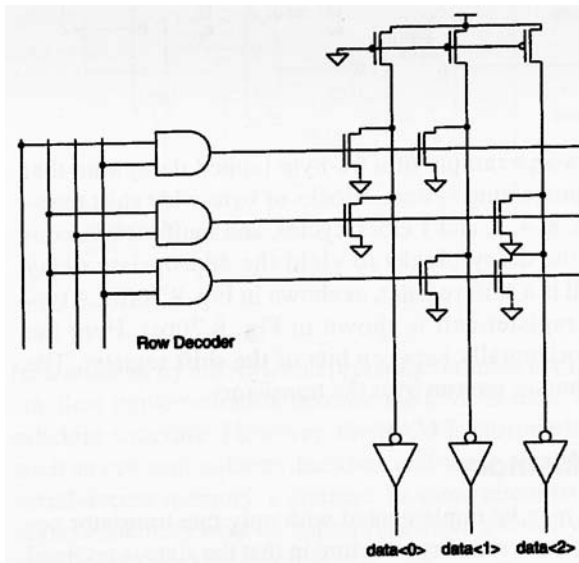




Fig. 11. Multibank system bandwidth calculations.

"High-Speed Dram Architecture Development", H. Ikeda and H. Inukai, IJSSC VOI 34, No 5, May 1999.


ROM

 

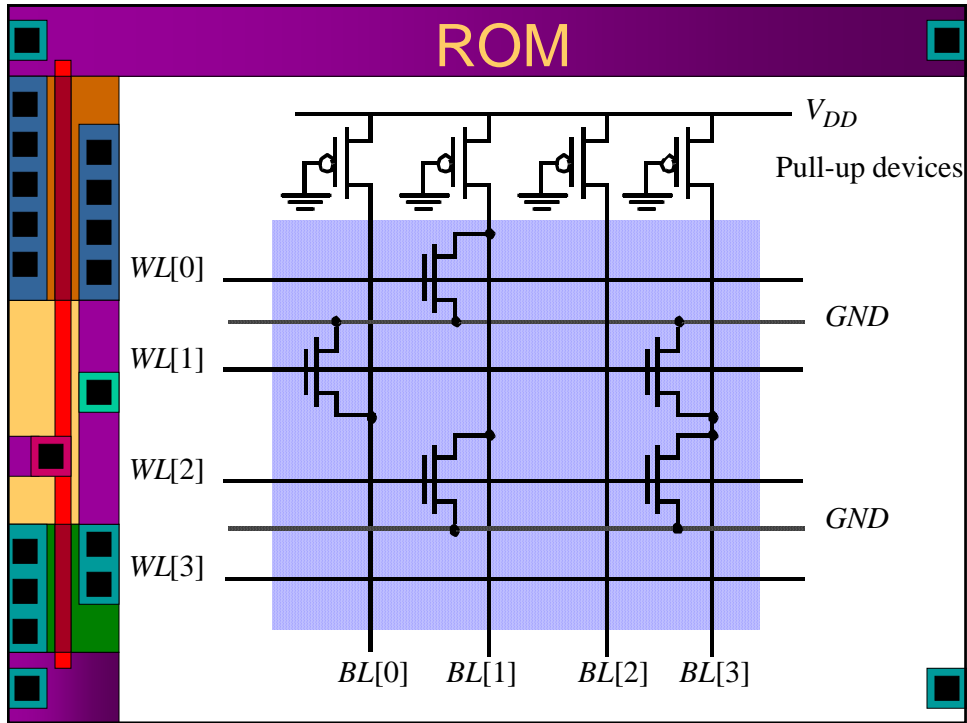


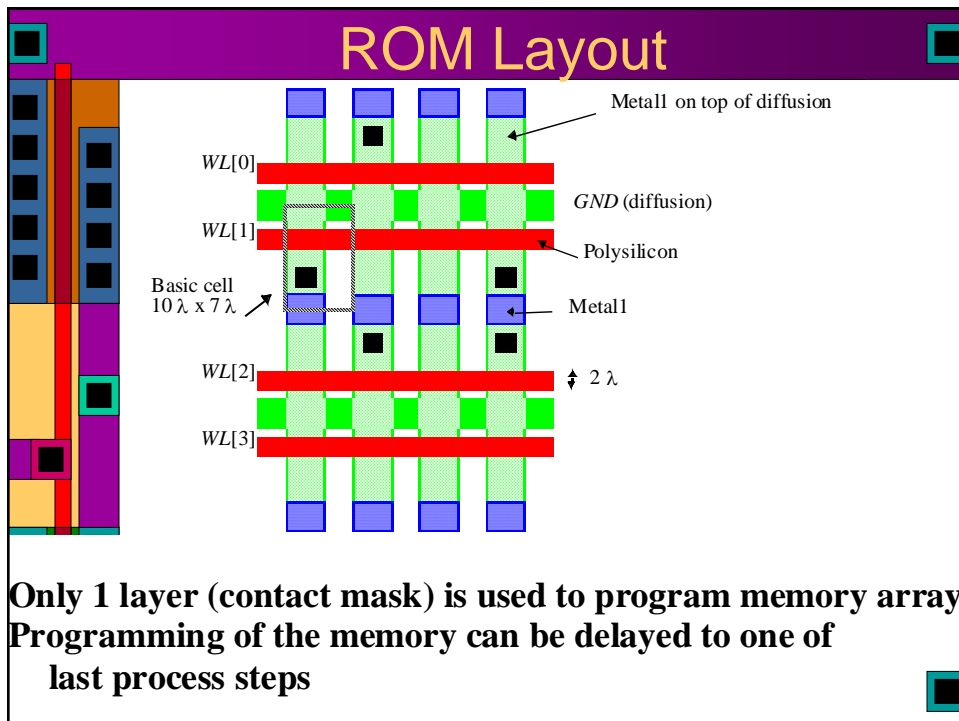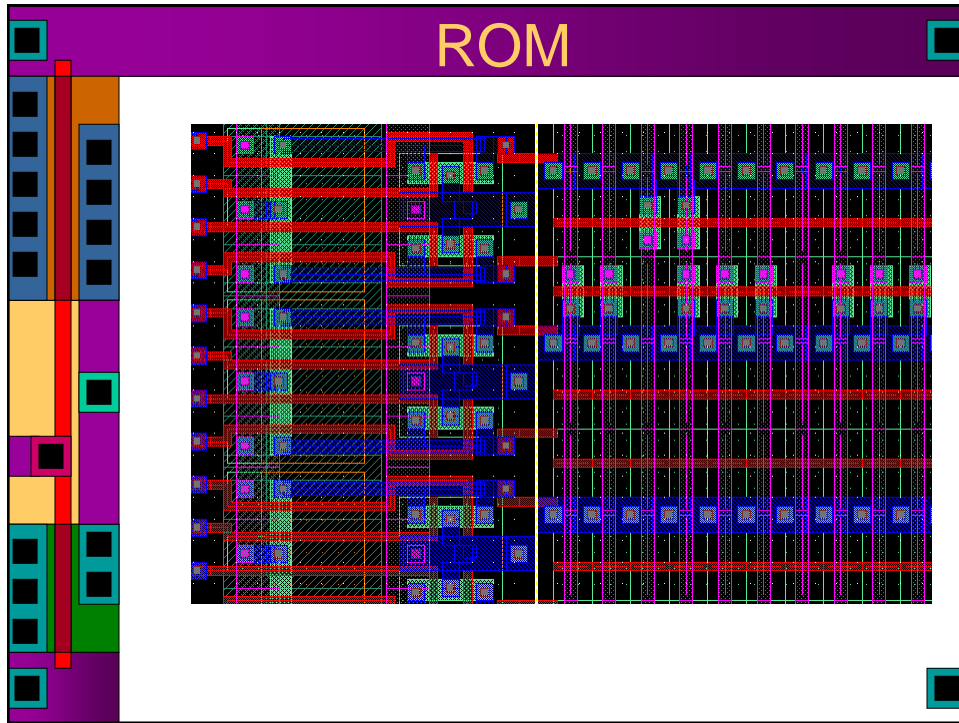

ROM Layout

 


(a)

 


(b)

Precharged ROM

 


PMOS precharge device can be made as large as necessary, but clock driver becomes harder to design.

Precharged ROM

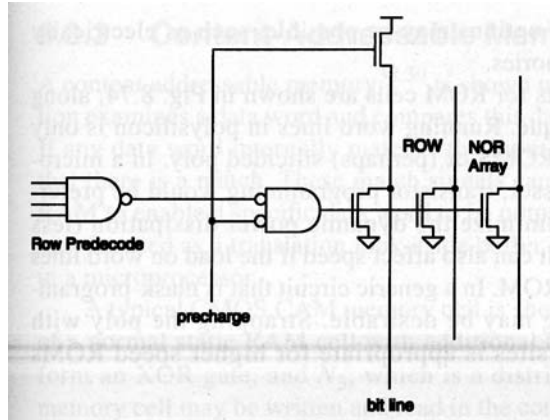


Other Memory Cells

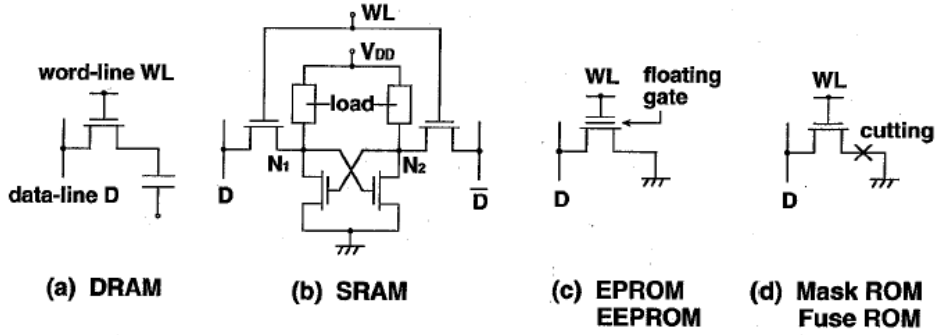


Non-Volatile ROM

- ▶ EPROM
 - ▶ Erasable Programmable ROM
- ▶ EEPROM
 - ▶ Electrically Erasable Programmable ROM
- ▶ Flash EEPROM
 - ▶ Electrically Erasable Programmable ROM that is erased in large chunks
- ▶ All these devices rely on trapping charge on a floating gate

EPROM

 


(a) Device cross-section

 

(b) Schematic symbol

Programming EPROM

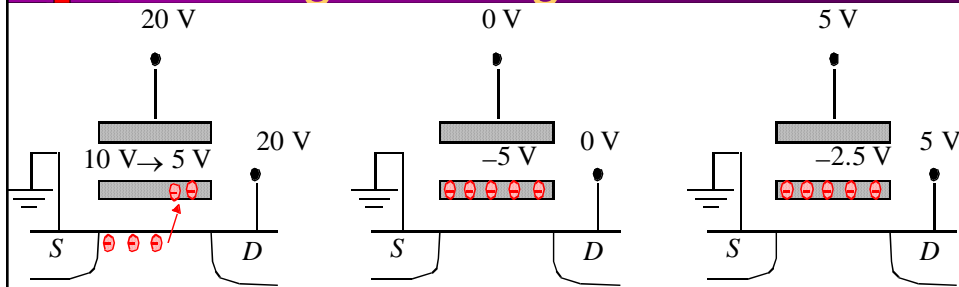

Avalanche injection.

Removing programming voltage
leaves charge trapped.


Programming results in
higher V_T .

- ▶ Higher V_{th} (around 7v) means that 5v V_{gs} no longer turns on the transistor
- ▶ SiO_2 is an excellent insulator
 - ▶ Trapped charge can stay for years


Erasing an EPROM

- ▶ Erase by shining UV light through window in the package
 - ▶ UV radiation makes oxide slightly conductive
 - ▶ Erasure is slow - from seconds to minutes depending on UV intensity
 - ▶ Also the erase/program cycles are limited (around 1000), mainly as a result of the UV erasing
- ▶ But, EPROMs are simple and dense

EEPROM

 


(a) Flotox transistor

 

(b) Fowler-Nordheim I - V characteristic

Floating Gate
Tunneling Oxide
transistor


 


(c) EEPROM cell during a read operation

- ▶ Thin oxide allows erasing in-system
- ▶ Fowler-Nordheim Tunneling

EEPROM

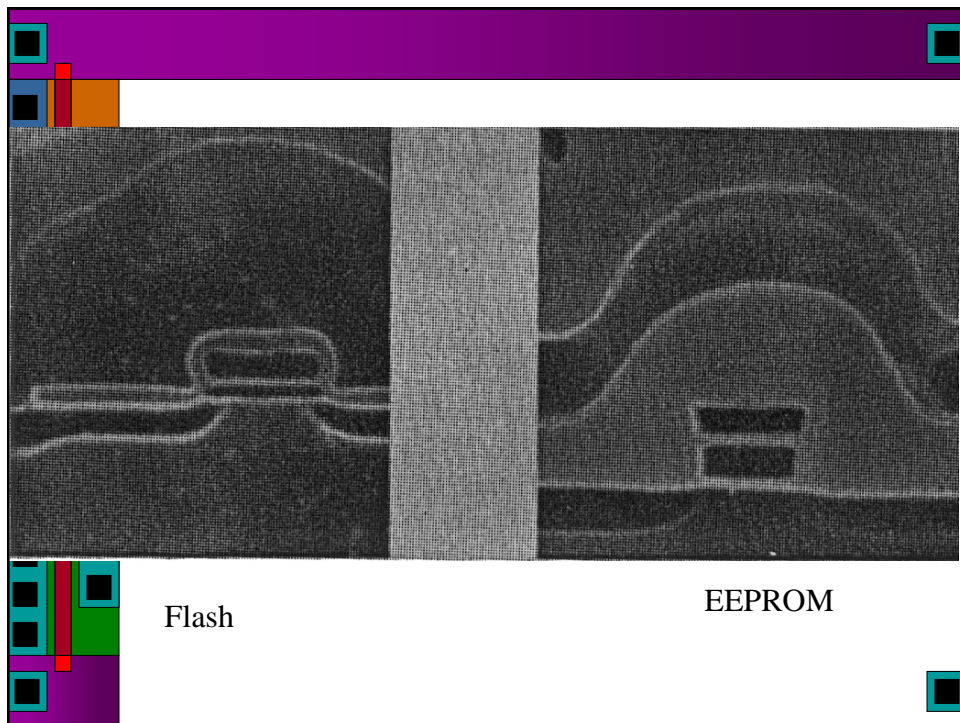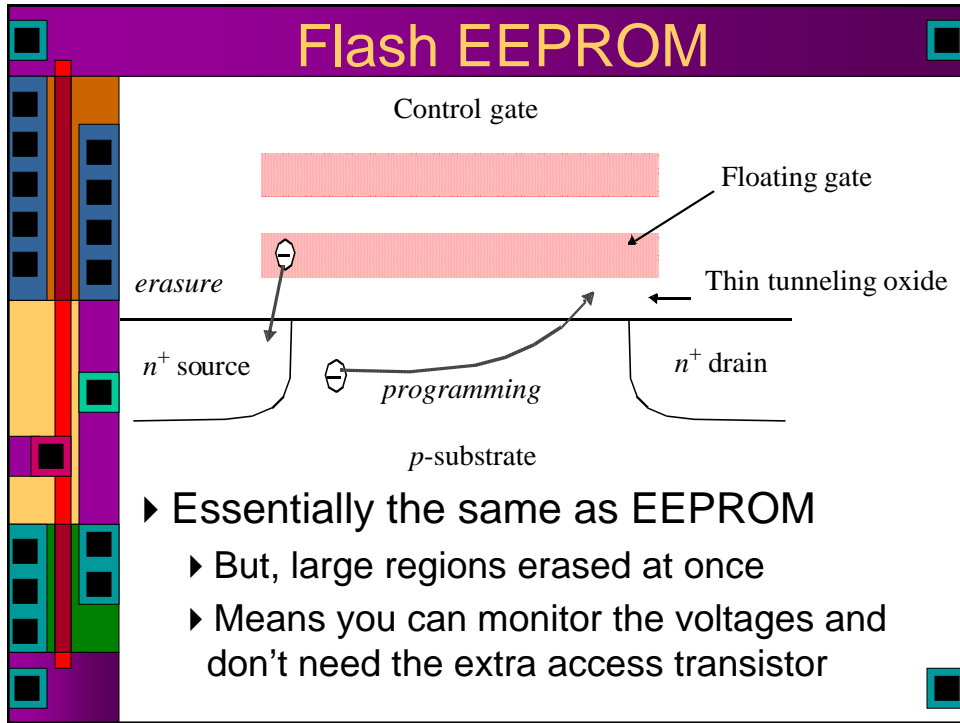
- ▶ Two transistors instead of one
 - ▶ The second keeps you from removing too much charge during erasure
- ▶ Bigger and not as dense as EPROM
- ▶ But, more erase/program cycles
 - ▶ On the order of 10^5
 - ▶ Eventually you get permanently trapped charge in the SiO_2



Realistic PROM Devices


	EPROM [Tomita91]	EEPROM [Terada89, Pashley89]	Flash EEPROM [Jinbo92]
Memory size	16 Mbit (0.6 μm)	1 Mbit (0.8 μm)	16 Mbit (0.6 μm)
Chip size	7.18 x 17.39 mm^2	11.8 x 7.7 mm^2	6.3 x 18.5 mm^2
Cell size	3.8 μm^2	30 μm^2	3.4 μm^2
Access time	62 nsec	120 nsec	58 nsec
Erasure time	minutes	N.A.	4 sec
Programming time/word	5 μsec	8 msec/word, 4 sec /chip	5 μsec
Erase/Write cycles [Pashley89]	100	10^5	10^3 - 10^5

Content Addressable Mem

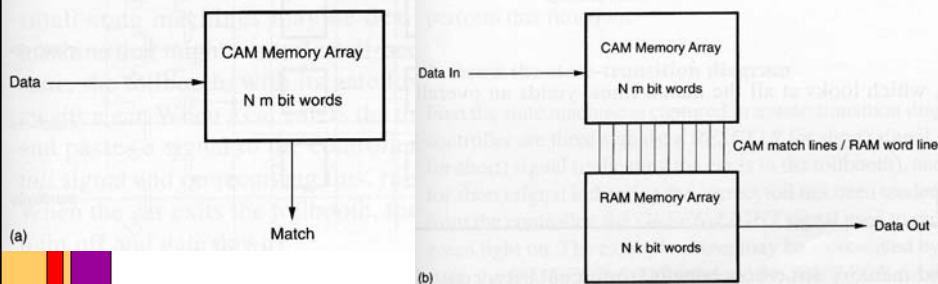


- ▶ Asks the question: Are there are any locations that hold this value?
 - ▶ Used for tag memories in associative caches
 - ▶ Or translation lookaside buffers
 - ▶ Or other pattern matching applications


Content Addressable Mem

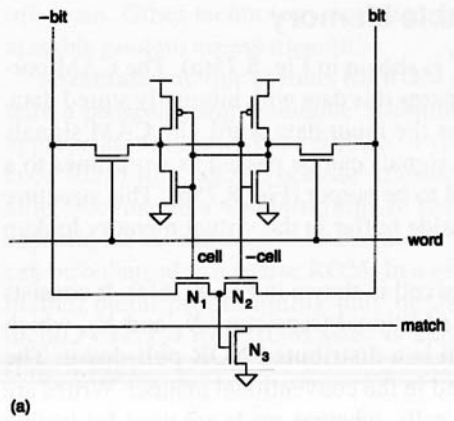



- ▶ Add the Match line
 - ▶ Essentially a distributed NOR gate


Content Addressable Mem

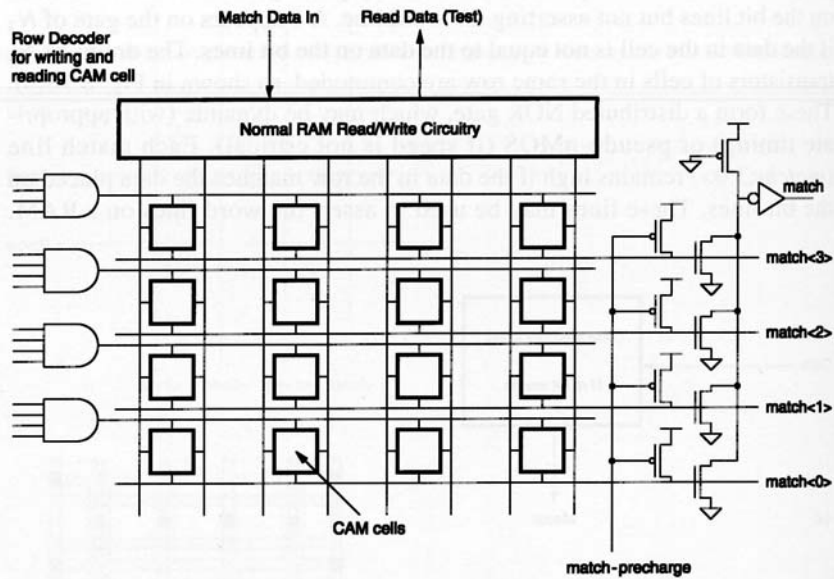

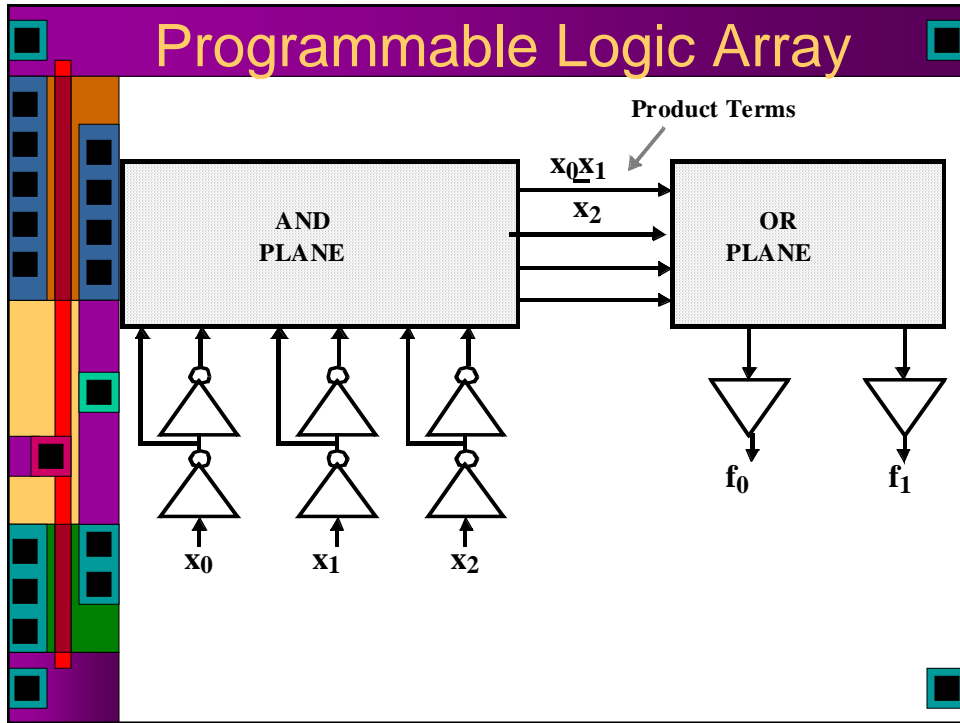

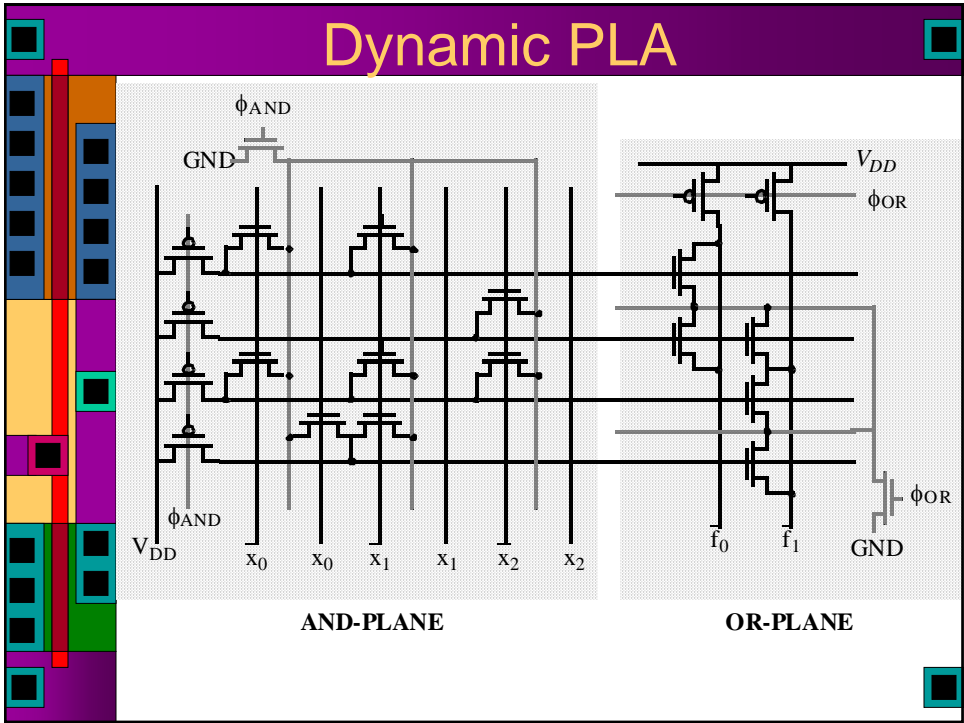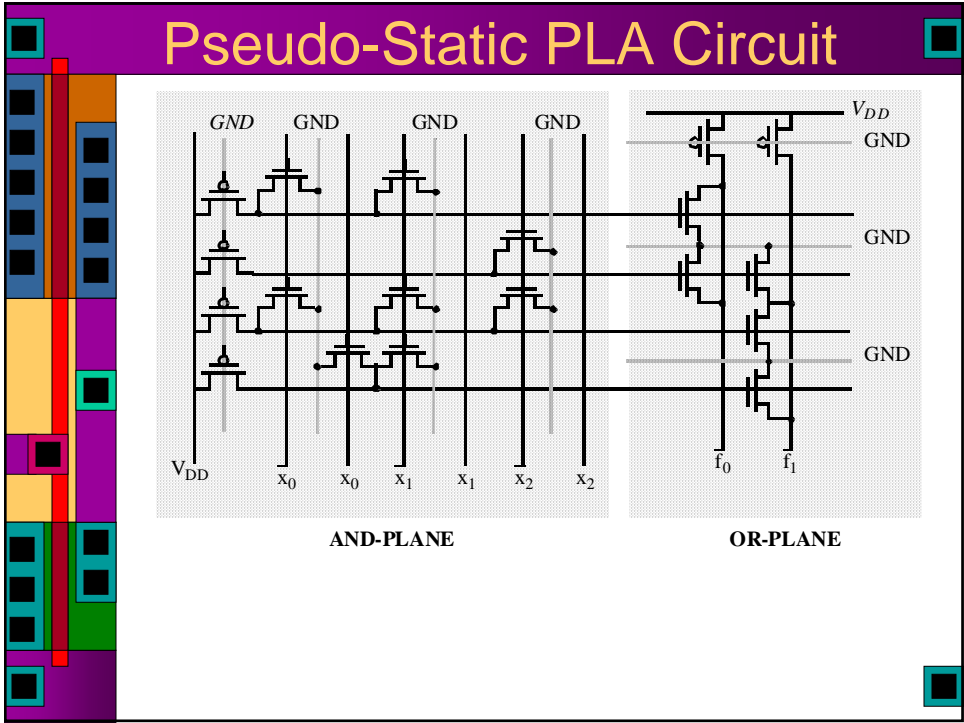- ## PLA
- ▶ Still useful for random combinational logic
 - ▶ Standard cell ASIC tools may be replacing them
 - ▶ They can generate dense AND-OR circuits



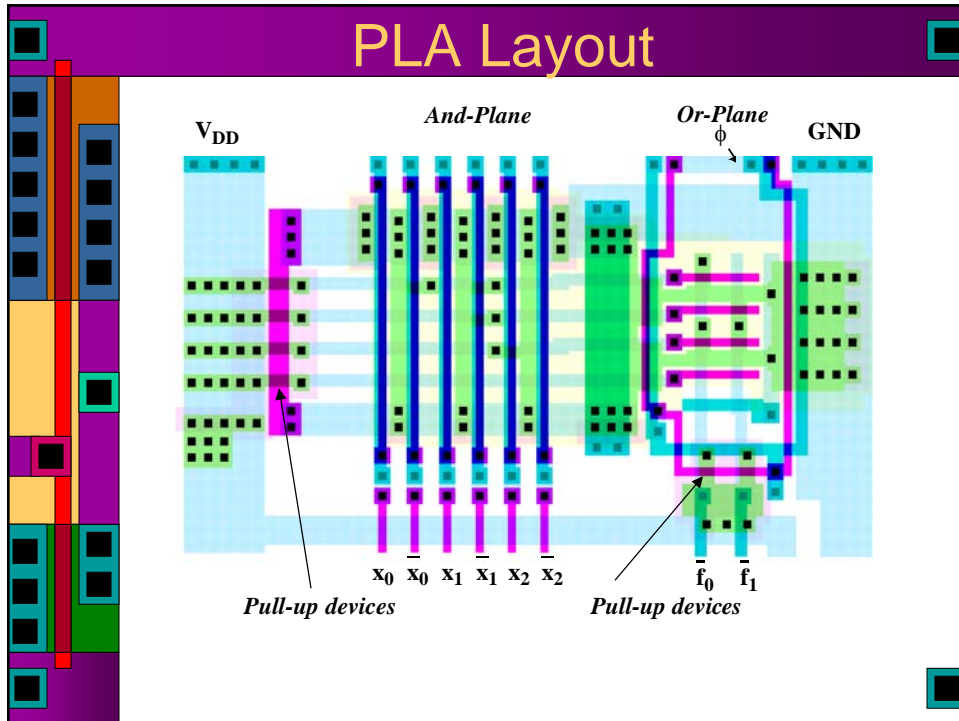

PLA vs. ROM

Programmable Logic Array
 structured approach to random logic
 “two level logic implementation”
 NOR-NOR (product of sums)
 NAND-NAND (sum of products)

IDENTICAL TO ROM!

Main difference
 ROM: fully populated
 PLA: one element per minterm

Note: Importance of PLA's has drastically reduced

1. slow
2. better software techniques (multi-level logic synthesis)

FPGAs

- ▶ Field Programmable Gate Arrays
 - ▶ Array of P-type and N-type transistors
 - ▶ Sources and drains connected to
 - ▶ Power and ground
 - ▶ Metal
 - ▶ Map gate structures to sea of gates
 - ▶ Less expensive – only modify metal masks