

Integrated Circuits for Communication



**Berkeley**



## MOS Wideband Noise and Distortion Amplifier Examples

Prof. Ali M. Niknejad

U.C. Berkeley

Copyright © 2014 by Ali M. Niknejad


# Wideband Noise Cancellation

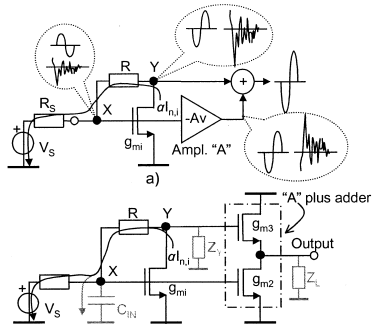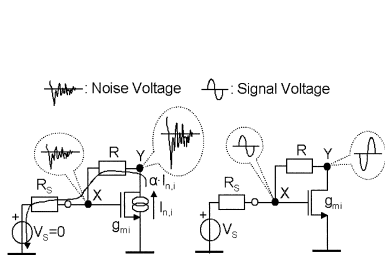


- Take advantage of amplifier topologies where the output thermal noise flows into the input (CG amplifier, shunt feedback amplifier, etc).
- Cancel thermal noise using a second feedforward path. Can we also cancel the distortion?
- Source: F. Bruccoleri, E. A. M. Klumperink, B. Nauta, "Wide-Band CMOS Low-Noise Amplifier Exploiting Thermal Noise Canceling," *JSSC*, vol. 39, Feb. 2004.
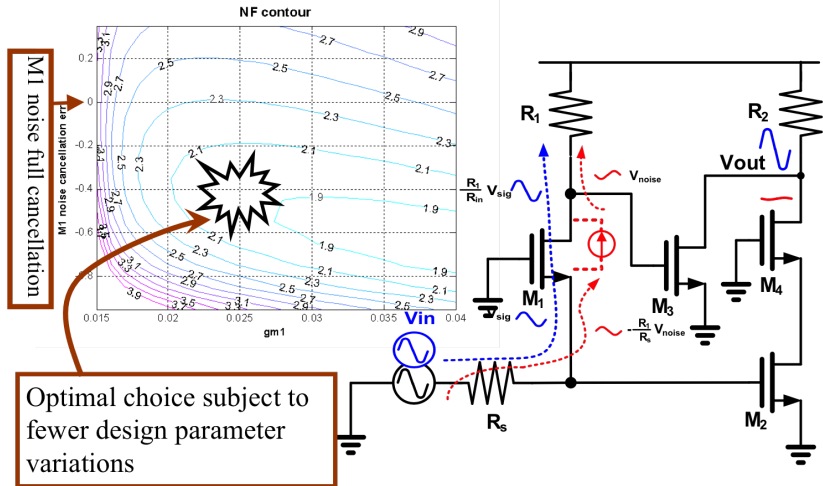
# Noise Cancellation LNA

- Motivated by [Bruccoleri, *et al.*, ISSCC 2002]




# 130nm LNA Prototype

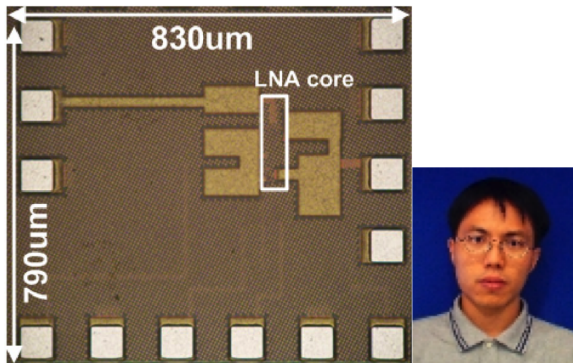


- 130nm CMOS, 1.5V, 12mA
- Employ only thin oxide transistors
- W.-H. Chen, G. Liu, Z. Boos, A. M. Niknejad, "A Highly Linear Broadband CMOS LNA Employing Noise and Distortion Cancellation," *IEEE Journal of Solid-State Circuits*, vol. 43, pp. 1164-1176, May 2008.

# Measured LNA S-Parameters

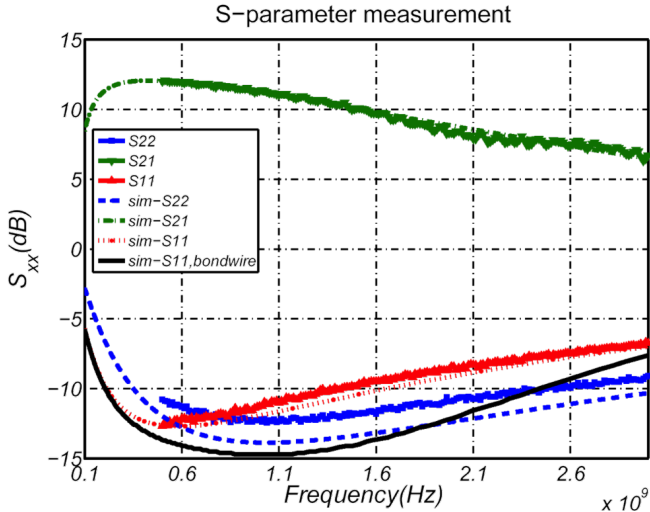


- Matches simulations well. Very broadband performance.

# Measured Noise Performance

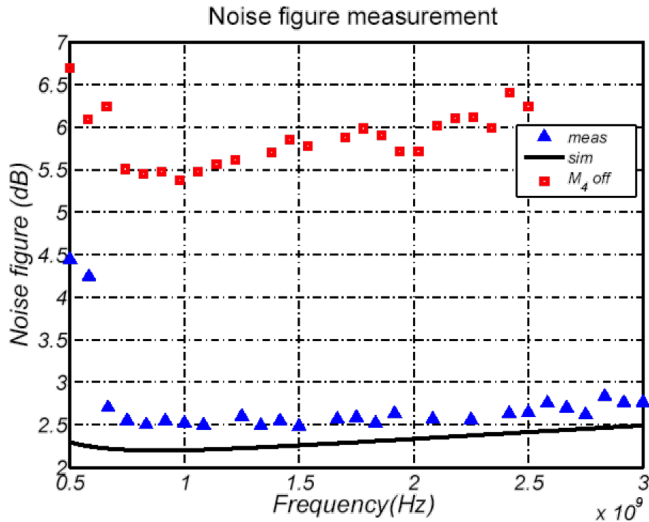


- Noise cancellation is clearly visible. This is also a “knob” for dynamic operation to save current.

# Measured Linearity

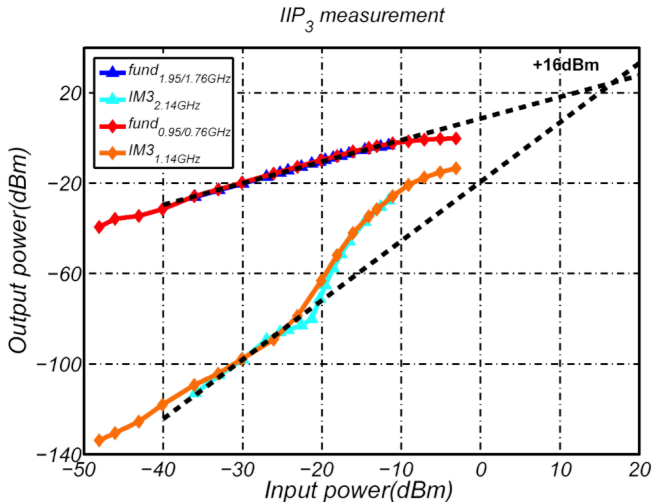

- Record linearity of +16 dBm for out of band blockers (at the time of publication).
- Linearity works over entire LNA band.


# Linearity Bias Dependence

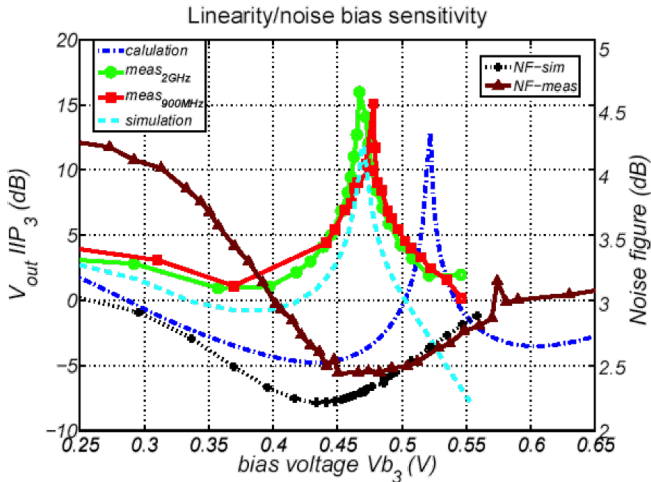

- As we vary the bias of key transistor, we simulate the effects of process/temp variation. There is a 50 mV window where the performance is still acceptable.



# LNA Distortion Analysis

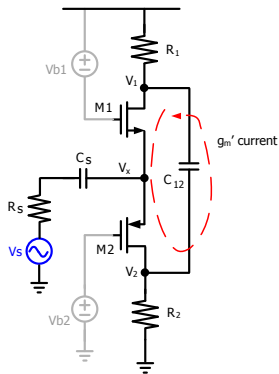


- Let's assume that the drain current is a power-series of the  $V_{gs}$  voltage:

$$i_d = g_{m1} V_{gs} + \frac{g_{m2}}{2!} V_{gs}^2 + \frac{g_{m3}}{3!} V_{gs}^3$$

- The purpose of the “differential” input is to cancel the 2nd order distortion of the first stage (to minimize 2nd order interaction):

$$i_{out} = i_{ds,n} + i_{ds,p} = (g_{mn} + g_{mp}) v_{in} + \frac{g'_{mn} - g'_{mp}}{2} v_{in}^2 + \frac{g''_{mn} + g''_{mp}}{6} v_{in}^3$$

# Distortion Equivalent Circuit

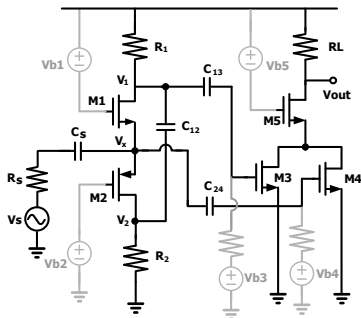

- Assume  $R1/R2$  and  $RL$  are small so that  $r_o$  non-linearity is ignored.

$$V_x = A_1(s_1) \circ V_s + A_2(s_1, s_2) \circ V_s^2 + A_3(s_1, s_2, s_3) \circ V_s^3$$

$$V_1 = B_1(s_1) \circ V_s + B_2(s_1, s_2) \circ V_s^2 + B_3(s_1, s_2, s_3) \circ V_s^3$$

$$V_2 = C_1(s_1) \circ V_s + C_2(s_1, s_2) \circ V_s^2 + C_3(s_1, s_2, s_3) \circ V_s^3$$

$$i_{m1} + \frac{V_x - V_1}{r_{o1}} + i_{m2} + \frac{V_x - V_2}{r_{o2}} + \frac{V_x}{Z_x(s)} = \frac{V_s - V_x}{Z_s(s)}$$

$$i_{m1} + \frac{V_x - V_1}{r_{o1}} = \frac{V_1}{Z_1(s)} + \frac{V_1 - V_2}{Z_{12}(s)}$$

$$i_{m2} + \frac{V_x - V_2}{r_{o2}} = \frac{V_2}{Z_2(s)} + \frac{V_2 - V_1}{Z_{12}(s)}$$

$$Z_1 = R_1 \parallel \frac{1}{sC_1}$$

$$Z_s = R_s + \frac{1}{sC_s}$$

$$Z_x = \frac{1}{sC_x}$$

# Drain Current Non-Linearity

- Assuming that the gates of the input transistors are grounded at RF:

$$\begin{aligned}i_{m1} &= - \left( g_{m1}(-V_x) + \frac{g'_{m1}}{2}(-V_x)^2 + \frac{g''_{m1}}{6}(-V_x)^3 \right) \\ &= g_{m1} V_x - \frac{g'_{m1}}{2} V_x^2 + \frac{g''_{m1}}{6} V_x^3 \\ i_{m2} &= g_{m2} V_x + \frac{g'_{m2}}{2} V_x^2 + \frac{g''_{m2}}{6} V_x^3\end{aligned}$$

- Solve for first order Kernels from:

$$g_{m1}A_1(s) + \frac{A_1(s) - B_1(s)}{r_{o1}} + g_{m2}A_1(s) + \frac{A_1(s) - C_1(s)}{r_{o2}} + \frac{A_1(s)}{Z_x(s)} = \frac{1 - A_1(s)}{Z_s(s)}$$

$$g_{m1}A_1(s) + \frac{A_1(s) - B_1(s)}{r_{o1}} = \frac{B_1(s)}{Z_1(s)} + \frac{B_1(s) - C_1(s)}{Z_{12}(s)}$$

$$g_{m2}A_1(s) + \frac{A_1(s) - C_1(s)}{r_{o2}} = \frac{C_1(s)}{Z_2(s)} + \frac{C_1(s) - B_1(s)}{Z_{12}(s)}$$

- At the frequency of interest,  $Z_{12} \sim 0$  and  $B_1 \sim C_1$

$$A_1(s) = \frac{(Z_1(s) \parallel Z_2(s)) + (r_{o1} \parallel r_{o2})}{H(s)}$$

$$B_1(s) = \frac{Z_1(s) \parallel Z_2(s)}{\left( \frac{Z_1(s) \parallel Z_2(s) + (r_{o1} \parallel r_{o2})}{1 + (g_{m1} + g_{m2})(r_{o1} \parallel r_{o2})} \right)} A_1(s)$$

$$H(s) = Z_s(s) \left( 1 + (g_{m1} + g_{m2})(r_{o1} \parallel r_{o2}) \right) + \left( (Z_1(s) \parallel Z_2(s)) + (r_{o1} \parallel r_{o2}) \right) \left( 1 + \frac{Z_s(s)}{Z_x(s)} \right)$$

- Retaining only 2nd order terms in the KCL equations:

$$g_{m1}A_2(s_1, s_2) - \frac{g'_{m1}}{2}A_1(s_1)A_1(s_2) + \frac{A_2(s_1, s_2) - B_2(s_1, s_2)}{r_{o1}} +$$

$$g_{m2}A_2(s_1, s_2) + \frac{g'_{m2}}{2}A_1(s_1)A_1(s_2) + \frac{A_2(s_1, s_2) - C_2(s_1, s_2)}{r_{o2}} + \frac{A_2(s_1, s_2)}{Z_x(s_1 + s_2)} = \frac{-A_2(s_1, s_2)}{Z_s(s_1 + s_2)}$$

$$g_{m1}A_2(s_1, s_2) - \frac{g'_{m1}}{2}A_1(s_1)A_1(s_2) + \frac{A_2(s_1, s_2) - B_2(s_1, s_2)}{r_{o1}} = \frac{B_2(s_1, s_2)}{Z_1(s_1 + s_2)} + \frac{B_2(s_1, s_2) - C_2(s_1, s_2)}{Z_{12}(s_1 + s_2)}$$

$$g_{m2}A_2(s_1, s_2) + \frac{g'_{m2}}{2}A_1(s_1)A_1(s_2) + \frac{A_2(s_1, s_2) - C_2(s_1, s_2)}{r_{o2}} = \frac{C_2(s_1, s_2)}{Z_2(s_1 + s_2)} + \frac{C_2(s_1, s_2) - B_2(s_1, s_2)}{Z_{12}(s_1 + s_2)}$$

# Second-Order Kernels

- Solving above equations we arrive at:

$$A_2(s_1, s_2) = \frac{\frac{1}{2}(g'_{m1} - g'_{m2})(r_{o1} \parallel r_{o1})Z_s(s_1 + s_2)A_1(s_1)A_1(s_2) + \Delta A_2(s_1, s_2)}{H(s_1 + s_2) + \Delta H(s_1, s_2)}$$

$$B_2(s_1, s_2) = \frac{-\frac{Z_1(s_1+s_2) \parallel Z_2(s_1+s_2)}{Z_x(s_1+s_2) \parallel Z_s(s_1+s_2)} \left( \frac{1}{2}(g'_{m1} - g'_{m2})(r_{o1} \parallel r_{o1})Z_s(s_1 + s_2)A_1(s_1)A_1(s_2) \right) + \Delta B_2(s_1, s_2)}{H(s_1 + s_2) + \Delta H(s_1, s_2)}$$

$$\Delta A_2(s_1, s_2) = \frac{1}{2}Z_{12}(s_1 + s_2)A_1(s_1)A_1(s_2) \frac{Z_s(s_1 + s_2)}{Z_1(s_1 + s_2) + Z_2(s_1 + s_2)} \times \\ \left( (g'_{m1} - g'_{m2})(r_{o1} \parallel r_{o2}) + \frac{g'_{m1}r_{o1}Z_2(s_1 + s_2) - g'_{m2}r_{o2}Z_1(s_1 + s_2)}{r_{o1} + r_{o2}} \right)$$

$$\Delta B_2(s_1, s_2) = -\frac{1}{2}Z_{12}(s_1 + s_2)A_1(s_1)A_1(s_2) \frac{Z_1(s_1 + s_2)}{Z_1(s_1 + s_2) + Z_2(s_1 + s_2)} \frac{1}{r_{o1} + r_{o2}} \times \\ \left( g'_{m1}r_{o1} \left( Z_2(s_1 + s_2) + r_{o2} \right) \left( 1 + \frac{Z_s(s_1 + s_2)}{Z_x(s_1 + s_2)} \right) + \right. \\ \left. Z_s(s_1 + s_2) \left( g'_{m2}r_{o2}(1 + g_{m1}r_{o1}) + g'_{m1}r_{o1}(1 + g_{m2}r_{o2}) \right) \right)$$

$$\Delta H(s_1, s_2) = Z_{12}(s_1 + s_2) \frac{Z_s(s_1, s_2)}{Z_1(s_1, s_2) + Z_2(s_1, s_2)} \frac{1}{r_{o1} + r_{o2}} \times \\ \left( \frac{(r_{o1} + Z_1(s_1 + s_2))(r_{o2} + Z_2(s_1 + s_2))}{Z_x(s_1 + s_2) \parallel Z_s(s_1 + s_2)} + \left( (1 + g_{m1}r_{o1})(r_{o2} + Z_2(s_1 + s_2)) + (1 + g_{m2}r_{o2})(r_{o1} + Z_1(s_1 + s_2)) \right) \right)$$

# Third-Order Terms

$$\begin{aligned} & g_{m1} A_3(s_1, s_2, s_3) + \frac{g_{m1}''}{6} A_1(s_1) A_1(s_2) A_1(s_3) - g_{m1}' \overline{A_1(s_1) A_2(s_2, s_3)} + \frac{A_3(s_1, s_2, s_3) - B_3(s_1, s_2, s_3)}{r_{o1}} \\ + g_{m2} A_3(s_1, s_2, s_3) + \frac{g_{m2}''}{6} A_1(s_1) A_1(s_2) A_1(s_3) + g_{m2}' \overline{A_1(s_1) A_2(s_2, s_3)} + \frac{A_3(s_1, s_2, s_3) - C_3(s_1, s_2, s_3)}{r_{o2}} \\ &= - \frac{A_3(s_1, s_2, s_3)}{Z_s(s_1 + s_2 + s_3)} \\ & g_{m1} A_3(s_1, s_2, s_3) + \frac{g_{m1}''}{6} A_1(s_1) A_1(s_2) A_1(s_3) - g_{m1}' \overline{A_1(s_1) A_2(s_2, s_3)} + \frac{A_3(s_1, s_2, s_3) - B_3(s_1, s_2, s_3)}{r_{o1}} \\ &= \frac{B_3(s_1, s_2, s_3)}{Z_1(s_1 + s_2 + s_3)} + \frac{B_3(s_1, s_2, s_3) - C_3(s_1, s_2, s_3)}{Z_{12}(s_1 + s_2 + s_3)} \\ & g_{m2} A_3(s_1, s_2, s_3) + \frac{g_{m2}''}{6} A_1(s_1) A_1(s_2) A_1(s_3) + g_{m2}' \overline{A_1(s_1) A_2(s_2, s_3)} + \frac{A_3(s_1, s_2, s_3) - C_3(s_1, s_2, s_3)}{r_{o1}} \\ &= \frac{C_3(s_1, s_2, s_3)}{Z_2(s_1 + s_2 + s_3)} + \frac{C_3(s_1, s_2, s_3) - B_3(s_1, s_2, s_3)}{Z_{12}(s_1 + s_2 + s_3)} \end{aligned}$$

- Assuming  $Z_{12} \sim 0$  (at  $s_1 + s_2 + s_3$ ):

$$A_3(s_1, s_2, s_3) = \frac{-Z_s(r_{o1} \parallel r_{o2}) \left( -(g'_{m1} + g'_{m2}) \overline{A_1(s_1) A_2(s_2, s_3)} + \frac{1}{6} (g''_{m1} + g''_{m2}) A_1(s_1) A_1(s_2) A_1(s_3) \right)}{H(s_1 + s_2 + s_3)}$$

$$B_3(s_1, s_2, s_3) = \frac{-Z_1(s_1 + s_2 + s_3)}{Z_x(s_1 + s_2 + s_3) \parallel Z_s(s_1 + s_2 + s_3)} A_3(s_1, s_2, s_3)$$



# Output Voltage

- The output voltage is given by a new Volterra series. Assume for simplicity the following:

$$V_{out} = \left( g_{m3} V_1 + g_{m4} V_x + \frac{g'_{m3}}{2} V_1^2 + \frac{g'_{m4}}{2} V_x^2 + \frac{g''_{m3}}{6} V_1^3 + \frac{g''_{m4}}{6} V_x^3 \right) \times Z_L$$

- The fundamental and third-order output are therefore:

$$V_{out, fund} = ((A_1(s) \circ V_s) \times g_{m4} + (B_1(s) \circ V_s) \times g_{m3}) \times Z_L$$

$$\begin{aligned} V_{out, 3^{rd}} = & \left( ((A_3(s_1, s_2, s_3) \circ V_s^3) \times g_{m4} + (B_3(s_1, s_2, s_3) \circ V_s^3) \times g_{m3}) \right. \\ & + ((A_1(s) \circ V_s)^3 \times \frac{g''_{m4}}{6} + (B_1(s) \circ V_s)^3 \times \frac{g''_{m3}}{6}) \\ & \left. + ((\overline{A_1(s_1)A_2(s_2, s_3)} \circ V_s^3) \times g'_{m4} + (\overline{B_1(s_1)B_2(s_2, s_3)} \circ V_s^3) \times g'_{m3}) \right) \times Z_L \end{aligned}$$


# Focus on Third-Order Output

- At low frequencies:
  - $A_1/B_1 \sim R_{in}/R_1$
  - $A_2/B_2 \sim -R_s/R_1$
  - $A_3/B_3 \sim -R_s/R_1$

$$V_{out,3rd} = \left( \begin{aligned} & ((A_3(s_1, s_2, s_3) \circ V_s^3) \times g_{m4} + (B_3(s_1, s_2, s_3) \circ V_s^3) \times g_{m3}) \\ & + ((A_1(s) \circ V_s)^3 \times \frac{g_{m4}''}{6} + (B_1(s) \circ V_s)^3 \times \frac{g_{m3}''}{6}) \\ & + ((\overline{A_1(s_1)A_2(s_2, s_3)} \circ V_s^3) \times g_{m4}' + (\overline{B_1(s_1)B_2(s_2, s_3)} \circ V_s^3) \times g_{m3}') \end{aligned} \right) \times Z_L$$


- First term cancels like thermal noise
- Second term: New distortion generated at output. Cancel with MGTR.
- Third term: Due to second-order interaction: Must use  $g' = 0$

# Two-Tone Spacing Dependence

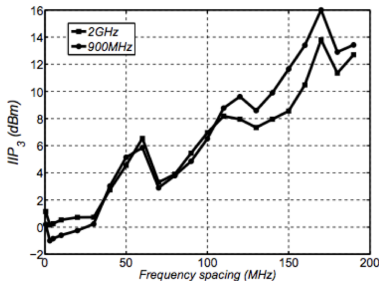


- Because 2nd order interaction is minimized by using a PMOS and NMOS in parallel, the capacitor  $C_{12}$  plays an important role.
- When second order distortion is generated at low frequencies,  $f_1 - f_2$ , the capacitor  $C_{12}$  has a high reactance and distortion cancellation does not take place.
- There is therefore a dependency to the two-tone spacing.

# Power Supply Ripple

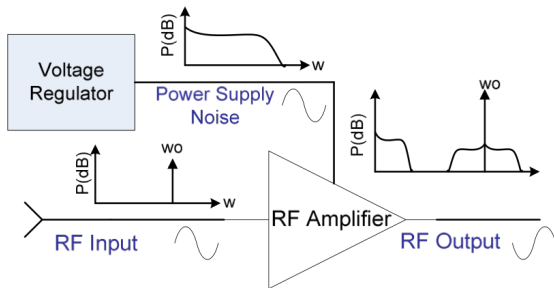

- In RF systems, the supply ripple can non-linearly transfer noise modulation on the supply to the output.
- This problem was analyzed by Jason Stauth: *Energy Efficient Wireless Transmitters: Polar and Direct-Digital Modulation Architectures*, Ph.D. Dissertation, U.C. Berkeley.

# Supply Noise Sources

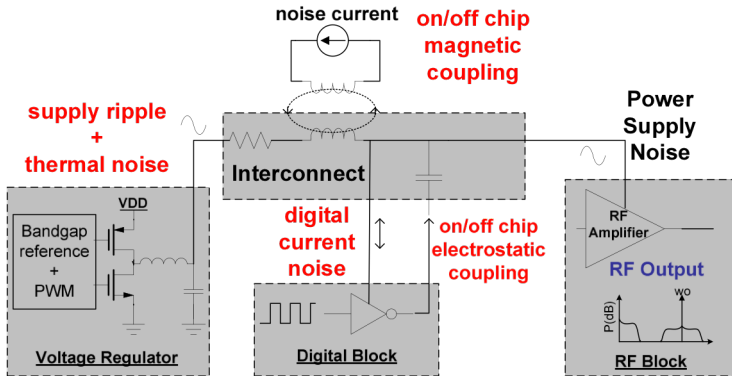

# Multi-Port Memoryless Non-linearity

- The output voltage is a non-linear function of both the supply voltage and the input voltage. A two-variable Taylor series expansion can be used if the system is memory-less:

$$\begin{aligned} S_{out}(S_{in}, S_{vdd}) = & a_{10}S_{in} + a_{20}S_{in}^2 + a_{30}S_{in}^3 + \dots \\ & + a_{11}S_{in}S_{vdd} + a_{21}S_{in}^2S_{vdd} + \dots \\ & + a_{01}S_{vdd} + a_{02}S_{vdd}^2 + a_{03}S_{vdd}^3 + \dots \end{aligned}$$

# Supply Noise Sideband

- Assume the input is at RF and the supply noise is a tone. Then the output signal will contain a noise sideband given by:


$$S_{in} = v_i \cos(\omega_0 t)$$

$$S_{vdd} = v_s \cos(\omega_s t)$$

$$v_{out}(\omega_0 \pm \omega_s) = \frac{1}{2} a_{11} v_i v_s$$

$$\text{Sideband(dBc)} = dB \left( \frac{2a_{10}}{a_{11}} \cdot \frac{1}{v_s} \right)$$
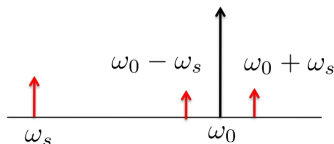
$$PSSR = dB \left( \frac{2a_{10}}{a_{11}} \right)$$



# Multi-Port Volterra Series

- Extending the concept of a Volterra Series to a two input-port system, we have


$$v_{out}(t) = \sum_{m=0}^{\infty} \sum_{n=0}^{\infty} F_{mn}(v_1(t), v_2(t))$$

$$F_{mn}(v_1(t), v_2(t)) = \int_{-\infty}^{\infty} \cdots \int_{-\infty}^{\infty} h_{mn}(\tau_1, \dots, \tau_{m+n}) \\ v_1(t - \tau_1) \cdots v_1(t - \tau_m) v_2(t - \tau_{m+1}) \cdots v_2(t - \tau_{m+n}) \\ \times d\tau_1 \cdots d\tau_{m+n}$$

$$S_{out} = A_{10}(j\omega_a)^\circ S_1 + A_{20}(j\omega_a, j\omega_b)^\circ S_1^2 + A_{30}(j\omega_a, j\omega_b, j\omega_c)^\circ S_1^3 + \cdots \\ + A_{01}(j\omega_a)^\circ S_2 + A_{02}(j\omega_a, j\omega_b)^\circ S_2^2 + A_{03}(j\omega_a, j\omega_b, j\omega_c)^\circ S_2^3 + \cdots \\ + A_{11}(j\omega_a, j\omega_b)^\circ S_1 S_2 + A_{21}(j\omega_a, j\omega_b, j\omega_c)^\circ S_1^2 S_2 + A_{12}(j\omega_a, j\omega_b, j\omega_c)^\circ S_1 S_2^2 + \cdots$$



# Example

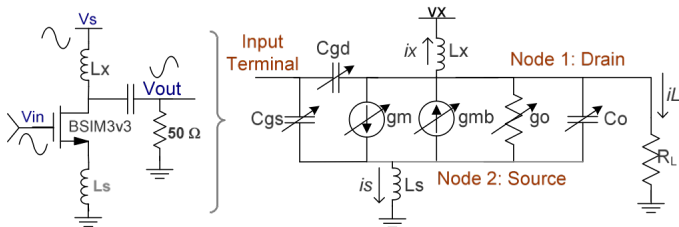

$$\begin{aligned}
 i_d = & g_{m1} v_{gs} + g_{m2} v_{gs}^2 + g_{m3} v_{gs}^3 + \dots \\
 & - g_{mb1} v_{sb} - g_{mb2} v_{sb}^2 - g_{mb3} v_{sb}^3 + \dots \\
 & + g_{mo11} v_{ds} \cdot v_{gs} + g_{mo12} v_{ds} \cdot v_{gs}^2 + g_{mo21} v_{ds}^2 v_{gs} + \dots \\
 & + C_1 \frac{d}{dt}(v_{db}) + \frac{C_2}{2} \frac{d}{dt}(v_{db}^2) + \frac{C_3}{3} \frac{d}{dt}(v_{db}^3) + \dots
 \end{aligned}$$

- Several important terms:
  - $g_m$ , and  $g_o$  non-linearity is usual transconductance and output resistance terms
  - $g_{mo}$  is the interaction between the input/output
  - $C_j$  is the output voltage non-linear capacitance

$$y_1(j\omega) = g_{o1} + j\omega C$$

$$y_x(j\omega) = (j\omega L_C)^{-1}$$

$$y_s(j\omega) = (j\omega L_S)^{-1}$$

- First-order transfer function: (RF Node Transfer)

$$A_{10}^1(j\omega) = -y_s(j\omega) \frac{g_{m1}}{K_0(j\omega)}$$

$$K_0(j\omega) = (g_{m1} + g_{mb1} + y_1)(y_x + y_L) + y_s(y_x + y_1 + y_L)$$

- Supply Node Transfer: (superscripts are node numbers)

$$A_{01}^1(j\omega) = \frac{g_{m1}(y_x + y_L)}{K_0(j\omega)}$$

$$A_{10}^2(j\omega) = \frac{y_x(g_{m1} + y_1 + g_{mb1} + y_s)}{K_0(j\omega)}$$

$$A_{01}^2(j\omega) = \frac{y_x y_L}{K_0(j\omega)}$$

- The most important term for now is the supply-noise mixing term:

$$v_{out}(\omega_0 \pm \omega_s) = A_{11}^1(j\omega_0, j\omega_s)^\circ [V_i(\omega_0), V_s(\omega_s)]$$

$$A_{11}^1(j\omega_a, j\omega_b) = y_s \frac{g_{mO11}K_1 + 2y_2K_2 + 2g_{m2}K_3 - 2g_{mb2}K_4}{K_0}$$

$$K_1(j\omega_a, j\omega_b) = A_{01}^2[1 + A_{10}^1(j\omega_a) - 2A_{10}^2(j\omega_a)] - A_{01}^1(j\omega_b)[1 - A_{10}^2(j\omega_a)]$$

$$K_2(j\omega_a, j\omega_b) = A_{01}^2(j\omega_b)[A_{10}^1(j\omega_a) - A_{10}^2(j\omega_a)] + A_{01}^1(j\omega_b)[A_{10}^2(j\omega_a) - A_{10}^1(j\omega_a)]$$

$$K_3(j\omega_a, j\omega_b) = A_{01}^2(j\omega_b)[1 - A_{10}^1(j\omega_a)]$$

$$K_4(j\omega_a, j\omega_b) = A_{10}^2(j\omega_a)A_{01}^2(j\omega_b)$$

$$PSRR = dB\left[\frac{gm_1}{gmo_{11}K_1 + 2y_2K_2 + 2gm_2K_3 - 2gmb_2K_4}\right]$$

- Increase  $gm_1$
- Reduce second order conductive non-linearity at drain ( $go_2$ )
- Reduce the non-linear junction capacitance at drain
- Reduce cross-coupling term by shielding the device drain from supply noise (cascode)

# Output Conductance Non-Linearity

- For short-channel devices, due to DIBL, the output has a strong influence on the drain current. A complete description of the drain current is therefore a function of  $f(v_{ds}, v_{gs})$ .
- This is especially true if the device is run close to triode region (large swing or equivalently high output impedance):

$$i_{ds}(v_{gs}, v_{ds}) = g_{m1}v_{gs} + g_{ds1}v_{ds} + g_{m2}v_{gs}^2 + g_{ds2}v_{ds}^2 + \\ x_{11}v_{gs}v_{ds} + g_{m3}v_{gs}^3 + g_{ds3}v_{ds}^3 + \\ x_{12}v_{gs}v_{ds}^2 + x_{21}v_{gs}^2v_{ds} + \dots$$

$$g_{mk} = \frac{1}{k!} \frac{\partial^k I_{ds}}{\partial V_{gs}^k}; g_{dsk} = \frac{1}{k!} \frac{\partial^k I_{ds}}{\partial V_{ds}^k}; x_{pq} = \frac{1}{p!q!} \frac{\partial^{p+q} I_{ds}}{\partial V_{gs}^p \partial V_{ds}^q}$$

- Including the output conductance non-linearity modifies the distortion as follows

$$v_{ds} = c_1 v_{gs} + c_2 v_{gs}^2 + c_3 v_{gs}^3 + \dots$$

$$c_1 = -g_{m1}(R_{CS} \parallel g_{ds1}^{-1})$$

$$c_2 = -(g_{m2} + g_{ds2}c_1^2 + x_{11}c_1) \cdot (R_{CS} \parallel g_{ds1}^{-1})$$

$$c_3 = -(g_{m3} + g_{ds3}c_1^3 + 2g_{ds2}c_1c_2 + x_{11}c_2 + x_{12}c_1^2 + x_{21}c_1) \cdot (R_{CS} \parallel g_{ds1}^{-1})$$

- Source: S. C. Blaakmeer, E. A. M. Klumperink, D. M. W. Leenaerts, B. Nauta, "Wideband Balun-LNA With Simultaneous Output Balancing, Noise-Canceling and Distortion-Canceling," *JSSC*, vol. 43, Jun. 2008.

# Example IIP Simulation

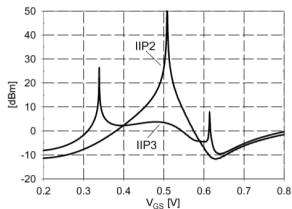


Fig. 6. Simulated IIP2 and IIP3 of a resistively loaded CS-stage.

$$\text{IIP2}_{\text{dBm}} = 20 \cdot \log_{10} \left( \left| \frac{c_1}{c_2} \right| \right) + 10 \text{ dB}$$

$$\text{IIP3}_{\text{dBm}} = 20 \cdot \log_{10} \left( \sqrt{\left| \frac{4}{3} \frac{c_1}{c_3} \right|} \right) + 10 \text{ dB}$$

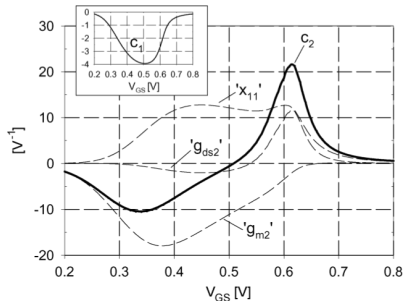


Fig. 5. Simulated second-order nonlinearity coefficient ( $c_2$ ) and individual contributions due to the transistor coefficients ( $g_{m2}$ ,  $g_{ds2}$  and  $x_{11}$ ). Inset: linear gain coefficient ( $c_1$ ) of the CS-stage.

- Contributions to  $c_2$  are shown above.
- For low bias,  $g_{ds2}$  contributes very little but  $x_{11}$  and  $g_{m2}$  are significant. They also have opposite sign.


# PA Power Supply Modulation

- When we apply a 1-tone to a class AB PA, the current drawn from the supply is constant.
- For when we apply 2-tones, there is a low-frequency component to the input:

$$\begin{aligned}V_{in} &= A \sin(\omega_1 t) + A \sin(\omega_2 t) \\ &= 2A \cos\left(\frac{\omega_1 - \omega_2}{2} t\right) \sin\left(\frac{\omega_1 + \omega_2}{2} t\right) \\ &= 2A \cos(\omega_m t) \sin(\omega_c t)\end{aligned}$$

- This causes a low frequency current to be drawn from the supply as well, even for a balanced circuit.

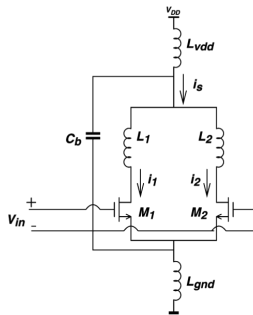- P. Haldi, D. Chowdhury, P. Reynaert, G. Liu, A. M. Niknejad, "A 5.8 GHz 1 V Linear Power Amplifier Using a Novel On-Chip Transformer Power Combiner in Standard 90 nm CMOS," *IEEE Journal of Solid-State Circuits*, vol. 43, pp.1054-1063, May 2008.





# Supply Current

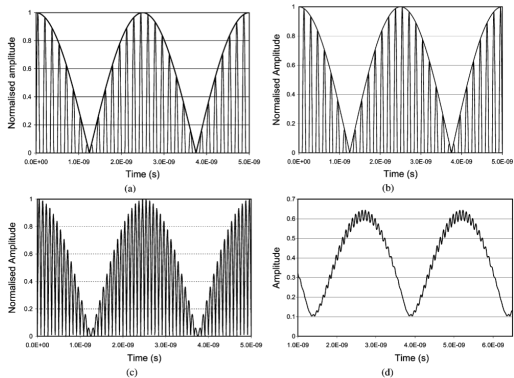


Fig. 9. (a) Drain current waveform of M1, operating in Class B, under two-tone excitation. (b) Drain current waveform of M2. (c) Sum of drain currents of M1 and M2. (d) Supply current after on-chip bypassing.

- The supply current is a full-wave rectified sine.

# Fourier Components of Supply Current

- Substitute the Fourier series for the sine and cosine.
- Note that an on-chip bypass can usually absorb the higher frequencies ( $2f_c$ ) but not the low frequency beat ( $f_s$  and harmonics)

$$\begin{aligned}i_s &= k \left( \frac{2}{\pi} + \frac{4 \cos(2\omega_m t)}{\pi \cdot 3} - \dots \right) \times \left( \frac{2}{\pi} - \frac{4 \cos(2\omega_c t)}{\pi \cdot 3} - \dots \right) \\ &= k \left( \dots - \frac{8 \cos(2\omega_c t)}{\pi^2 \cdot 3} + \frac{8 \cos(2\omega_m t)}{\pi^2 \cdot 3} - \dots \right) \\ &= k \left( \dots - \frac{8 \cos(2\omega_c t)}{\pi^2 \cdot 3} + \frac{8 \cos(\omega_s t)}{\pi^2 \cdot 3} - \dots \right)\end{aligned}$$

# Supply Ripple Voltage

- The finite impedance of the supply means that the supply ripple has the following form.

$$V_{dd} = V_{DD} + A_2 \cdot \cos(\omega_s t) + \dots$$

- Assuming a multi-port Volterra description for the transistor results in:

$$\begin{aligned} S_o = & F_1(\omega_a) \circ S_1 + F_2(\omega_a, \omega_b) \circ S_1^2 + F_3(\omega_a, \omega_b, \omega_c) \circ S_1^3 + \dots \\ & G_1(\omega_a) \circ S_2 + G_2(\omega_a, \omega_b) \circ S_2^2 + G_3(\omega_a, \omega_b, \omega_c) \circ S_3^3 + \dots \\ & H_{11}(\omega_a, \omega_b) \circ (S_1 \cdot S_2) + H_{12}(\omega_a, \omega_b, \omega_c) \circ (S_1 \cdot S_2^2) + \\ & H_{21}(\omega_a, \omega_b, \omega_c) \circ (S_1^2 \cdot S_2) + \dots \\ S(\omega_1 \pm \omega_s) = & H_{11} \circ (S_1 \cdot S_2) \end{aligned}$$

# Experimental Results

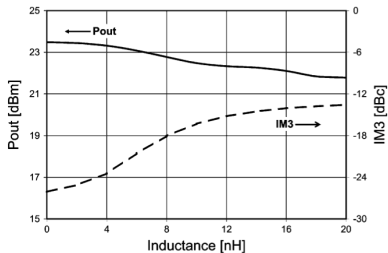


Fig. 14. Degradation in IM3 with increased supply inductance.

- Even though the PA is fully balanced, the supply inductance impacts the linearity.
- Measurements confirm the source of the  $IM_3$  at low offsets arising from supply modulation.


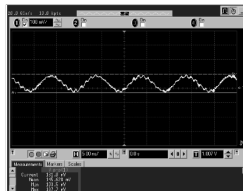




Fig. 15. Measured supply voltage ripple in a two-tone test with 100 MHz tone spacing.

# MOS CV Non-Linearity

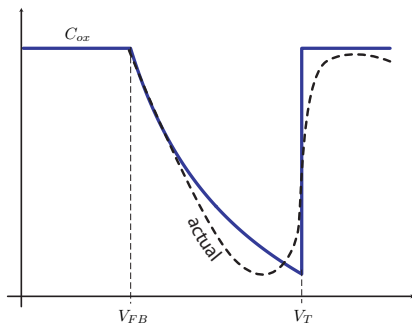


- $C_{gs}$ ,  $C_{\mu}$  and  $C_{db}$  all contribute to the non-linearity.
- As expected, the contribution is frequency dependent and very much a strong function of the swing (drain, gate).
- Gate cap is particular non-linear around the threshold of the device.

# PMOS Compensation Technique

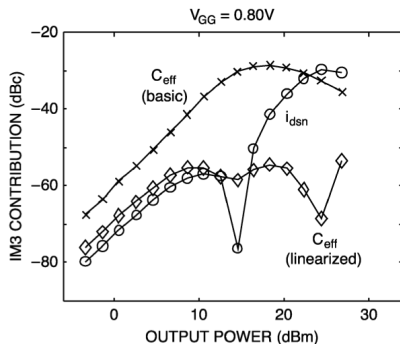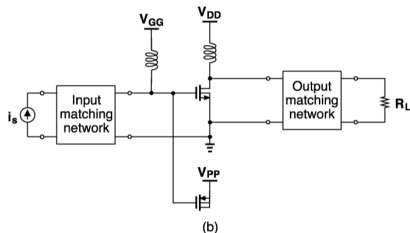

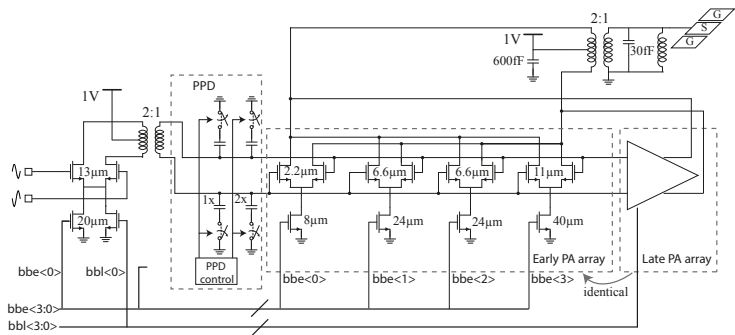- Make an overall flat  $C-V$  curve by adding an appropriately sized PMOS device.
- Source: C. Wang, M. Vaidyanathan, L. Larson, "A Capacitance-Compensation Technique for Improved Linearity in CMOS Class-AB Power Amplifiers," *JSSC*, vol. 39, Nov. 2004.



- “Digital” PA cell at 60 GHz uses non-binary weighted elements for RF-DAC to compensate for amplitude compression.
- Phase AM-to-PM distortion is compensated by switching in capacitance versus codeword.
- Source: Jiashu Chen, Lu Ye, D. Titz, F. Giansello, R. Pilard, A. Cathelin, F. Ferrero, C. Luxey, A. Niknejad, “A digitally modulated mm-Wave cartesian beamforming transmitter with quadrature spatial combining,” *IEEE International Solid-State Circuits Conference Digest of Technical Papers (ISSCC)*, 17-21 Feb. 2013, pp. 232-233.