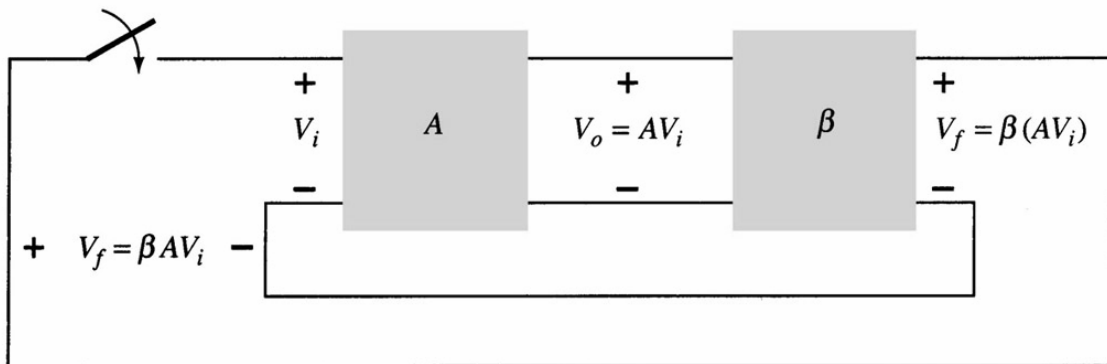


# **Oscillator Circuits**

## II. Oscillator Operation


For self-sustaining oscillations:

- the feedback signal must positive
- the overall gain must be equal to one (unity gain)



If the feedback signal is not positive or the gain is less than one, then the oscillations will dampen out.

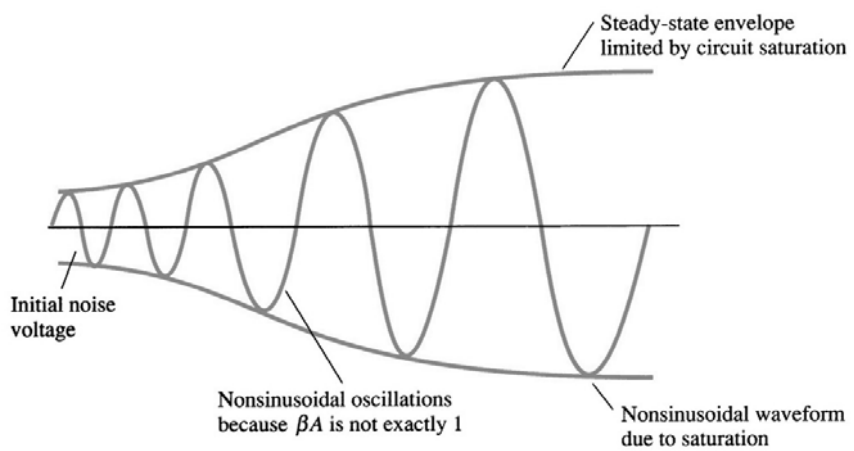
If the overall gain is greater than one, then the oscillator will eventually saturate.



## **Types of Oscillator Circuits**

- A. Phase-Shift Oscillator
- B. Wien Bridge Oscillator
- C. Tuned Oscillator Circuits
- D. Crystal Oscillators
- E. Unijunction Oscillator

## A. Phase-Shift Oscillator

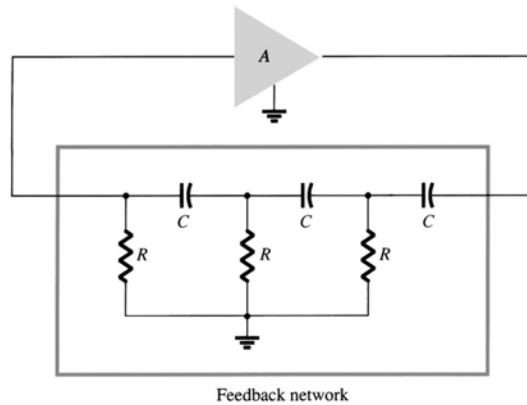

Frequency of the oscillator:  $f_0 = \frac{1}{2\pi RC\sqrt{6}}$  (the frequency where the phase shift is 180°)

Feedback gain  $\beta = 1/[1 - 5\alpha^2 - j(6\alpha - \alpha^3)]$  where  $\alpha = 1/(2\pi fRC)$


Feedback gain at the frequency of the oscillator  $\beta = 1/29$

The amplifier must supply enough gain to compensate for losses. The overall gain must be unity. Thus the gain of the amplifier stage must be greater than  $1/\beta$ , i.e.  $A > 29$

The RC networks provide the necessary phase shift for a positive feedback. They also determine the frequency of oscillation.

## Example of a Phase-Shift Oscillator

FET Phase-Shift Oscillator

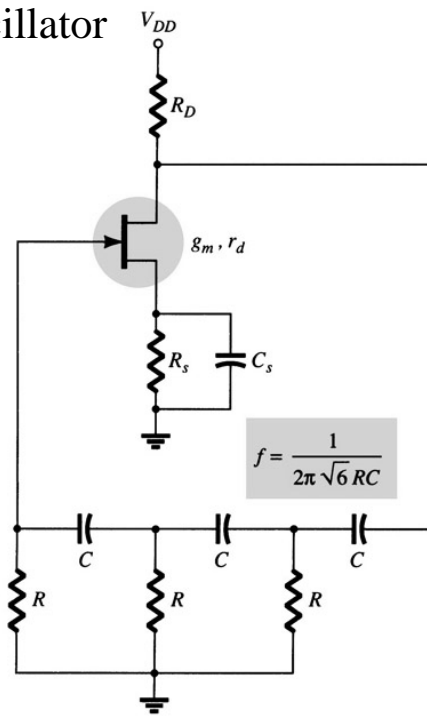

$$f = \frac{1}{2\pi\sqrt{6}RC}$$

(a)

## Example 1

It is desired to design a phase-shift oscillator (as in Fig. 18.21a) using an FET having  $g_m = 5000 \mu\text{S}$ ,  $r_d = 40 \text{ k}\Omega$ , and feedback circuit value of  $R = 10 \text{ k}\Omega$ . Select the value of  $C$  for oscillator operation at  $1 \text{ kHz}$  and  $R_D$  for  $A > 29$  to ensure oscillator action.

Equation (18.33) is used to solve for the capacitor value. Since  $f = 1/2\pi RC\sqrt{6}$ , we can solve for  $C$ :

$$C = \frac{1}{2\pi Rf\sqrt{6}} = \frac{1}{(6.28)(10 \times 10^3)(1 \times 10^3)(2.45)} = 6.5 \text{ nF}$$

Using Eq. (18.36), we solve for  $R_L$  to provide a gain of, say,  $A = 40$  (this allows for some loading between  $R_L$  and the feedback network input impedance):


$$|A| = g_m R_L$$

$$R_L = \frac{|A|}{g_m} = \frac{40}{5000 \times 10^{-6}} = 8 \text{ k}\Omega$$

Using Eq. (18.37), we solve for  $R_D = 10 \text{ k}\Omega$ .

$$R_L = \frac{R_D r_d}{R_D + r_d}$$

## BJT Phase-Shift Oscillator

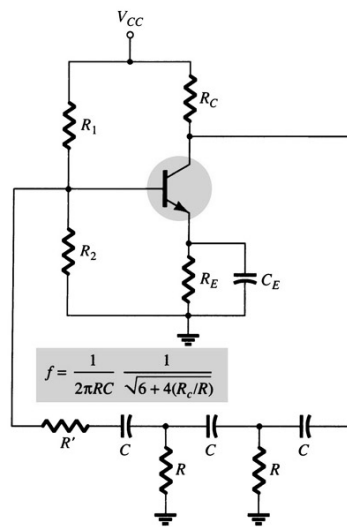


$$R' = R - h_{ie}$$


$$h_{fe} > 23 + 29 \frac{R_C}{R} + 4 \frac{R}{R_C}$$



## Phase-shift oscillator using op-amp

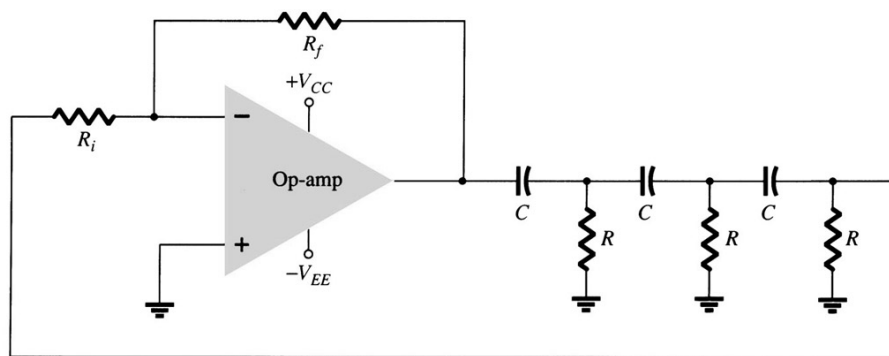

## B. Wien Bridge Oscillator

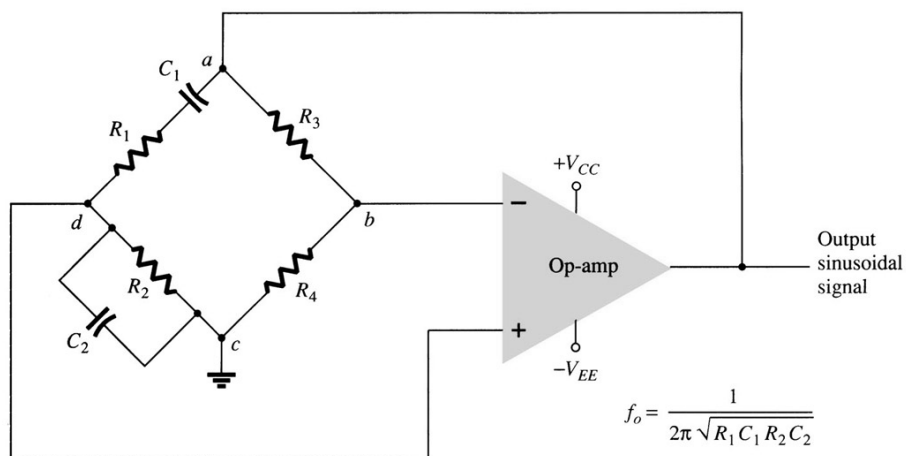

$$\beta = \frac{V_i}{V_o} = \frac{V_d - V_b}{V_a} = \frac{Z_2}{Z_1 + Z_2} - \frac{R_4}{R_3 + R_4} = \frac{1}{\frac{Z_1}{Z_2} + 1} - \frac{1}{\frac{R_3}{R_4} + 1}$$

$$\beta = 0 \Rightarrow \frac{R_3}{R_4} = \frac{R_1}{R_2} + \frac{C_2}{C_1}$$


$\frac{Z_2}{Z_1 + Z_2}$ , i.e.,  $\frac{Z_1}{Z_2}$  should have zero phase at the oscillation frequency

When  $R_1 = R_2 = R$  and  $C_1 = C_2 = C$  then

So frequency of oscillation is  $f_0 = \frac{1}{2\pi\sqrt{(R_1C_1R_2C_2)}}$

$$f_0 = \frac{1}{2\pi RC}, \text{ and } \frac{R_3}{R_4} \geq 2$$

## Example 2

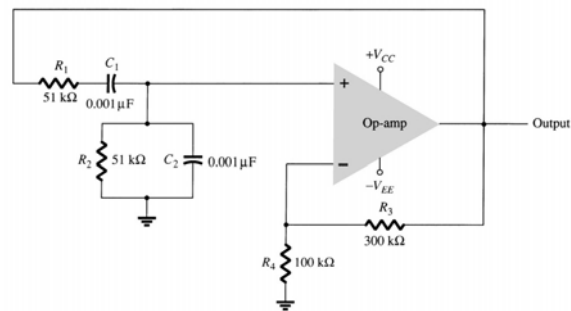

Calculate the resonant frequency of the Wien bridge oscillator shown above

$$f_0 = \frac{1}{2\pi RC} = \frac{1}{2\pi(51 \times 10^3)(1 \times 10^{-9})} = 3120.7 \text{ Hz}$$


Design the  $RC$  elements of a Wien bridge oscillator as in Fig. 18.24 for operation at  $f_o = 10 \text{ kHz}$ .

Using equal values of  $R$  and  $C$  we can select  $R = 100 \text{ k}\Omega$  and calculate the required value of  $C$  using Eq. (18.42):

$$C = \frac{1}{2\pi f_o R} = \frac{1}{6.28(10 \times 10^3)(100 \times 10^3)} = \frac{10^{-9}}{6.28} = 159 \text{ pF}$$

We can use  $R_3 = 300 \text{ k}\Omega$  and  $R_4 = 100 \text{ k}\Omega$  to provide a ratio  $R_3/R_4$  greater than 2 for oscillation to take place.

## C. Tuned Oscillator Circuits

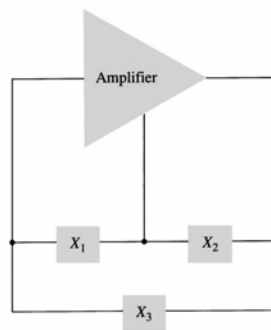


Oscillator Type	Reactance Element		
	$X_1$	$X_2$	$X_3$
Colpitts oscillator	$C$	$C$	$L$
Hartley oscillator	$L$	$L$	$C$
Tuned input, tuned output	$LC$	$LC$	—

Tuned Oscillators use a parallel LC resonant circuit (LC tank) to provide the oscillations.

There are two common types:


- **Colpitts** – The resonant circuit is an inductor and two capacitors.
- **Hartley** – The resonant circuit is a tapped inductor or two inductors and one capacitor.

## Colpitts Tuned Oscillator Circuit

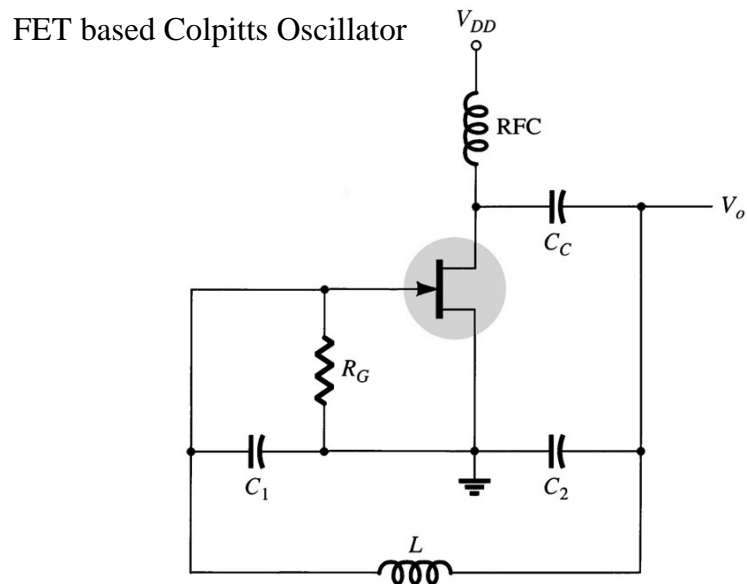


Frequency of oscillations:  $f_0 = \frac{1}{2\pi\sqrt{LC_{eq}}}$ , where  $C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$

## Transistor Colpitts oscillator.

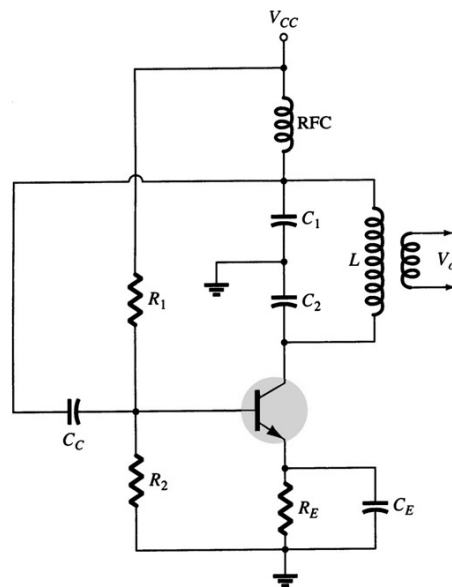


### Op-amp Colpitts oscillator.

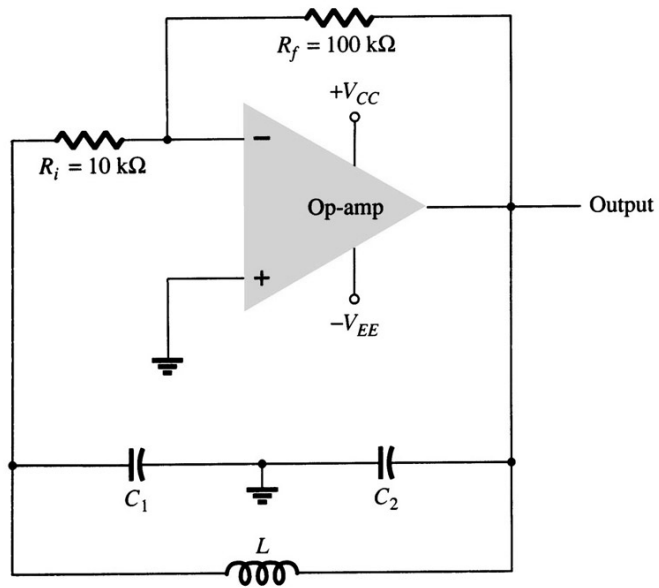

## Hartley Tuned Oscillator Circuit


FET Hartley Oscillator

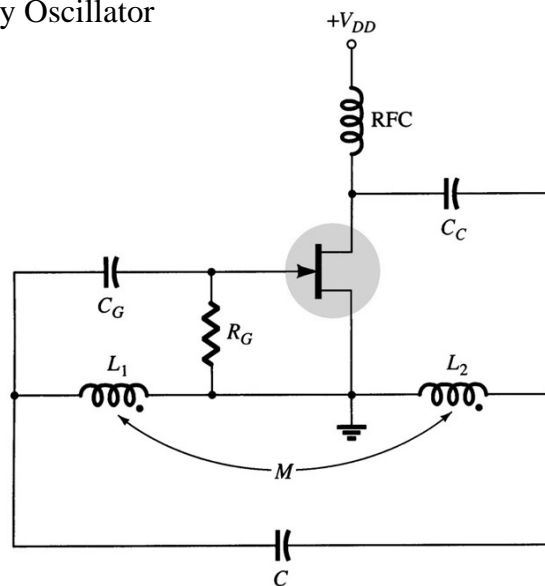

Frequency of oscillations:  $f_0 = \frac{1}{2\pi\sqrt{L_{eq}C}}$ , where  $L_{eq} = L_1 + L_2 + 2L_{12}$




# BJT based Hartley Oscillator

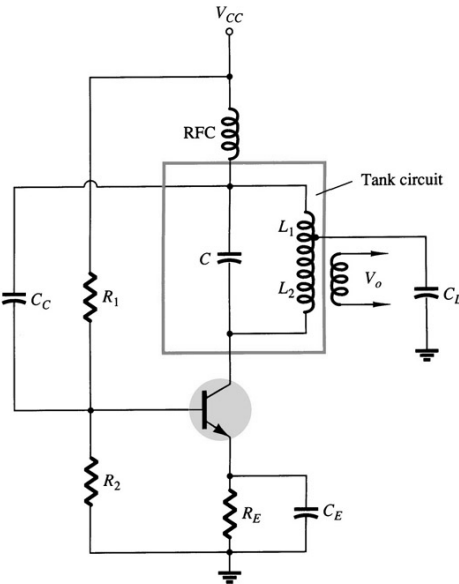
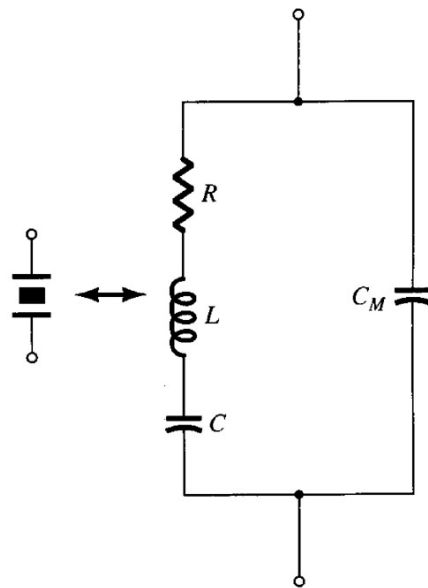
## D. Crystal Oscillators

The crystal appears to the rest of the circuit as a resonant circuit.




## Crystal Resonant Frequencies

The crystal has two resonant frequencies:


**Series resonant:** RLC determine the resonant frequency. The crystal has a low impedance.

**Parallel resonant:** RL and  $C_M$  determine the resonant frequency. The crystal has a high impedance.

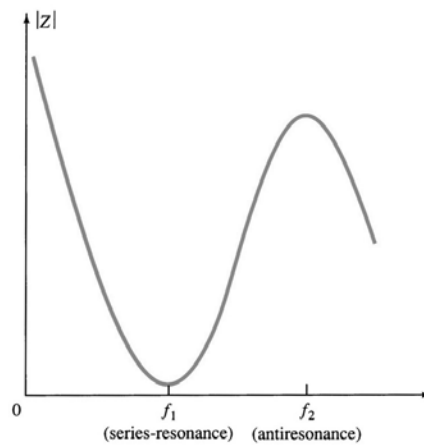The series and parallel resonant frequencies are very close, within 1% of each other.




## Series Resonant Crystal Oscillator

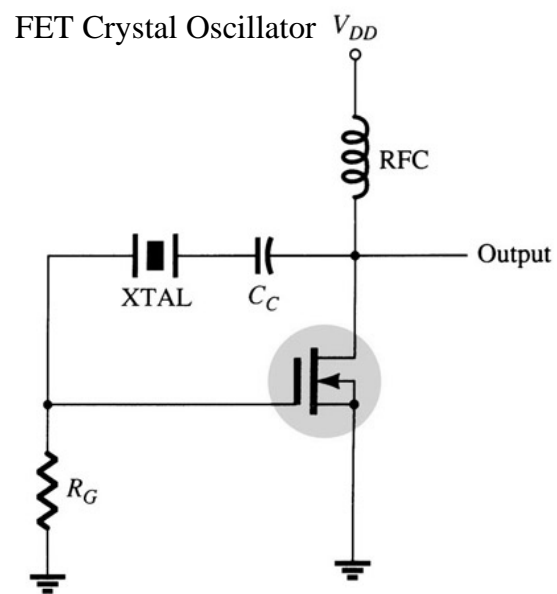


## Parallel Resonant Crystal Oscillator


BJT Crystal Oscillator

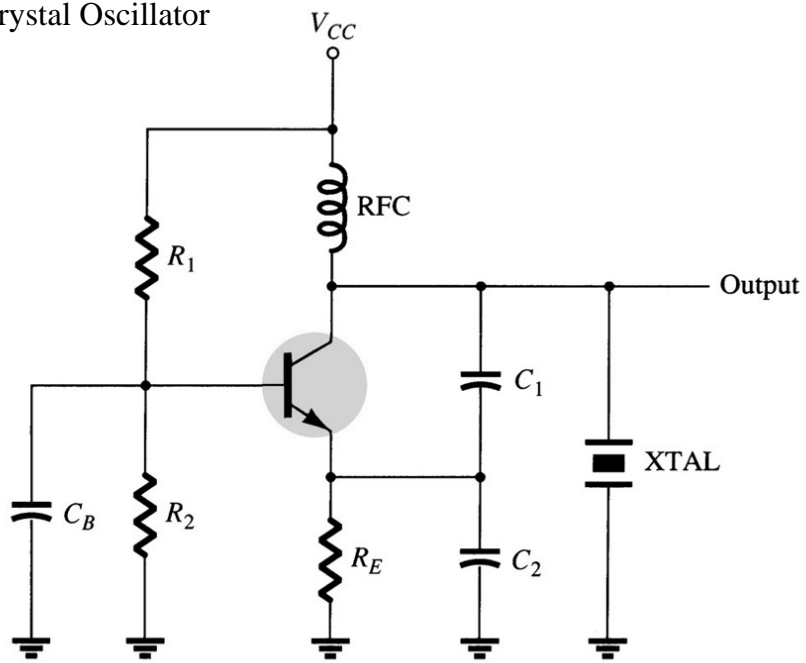

## Crystal Oscillator using Op-amp

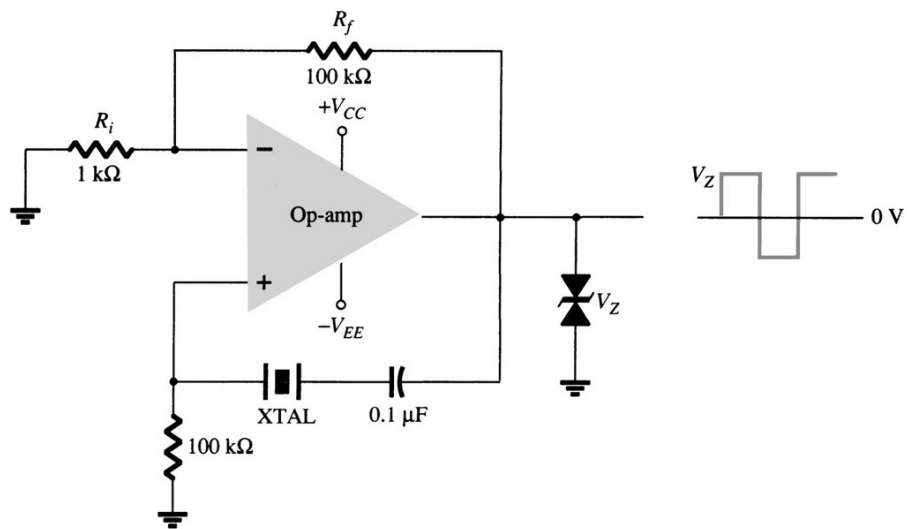


## E. Unijunction Oscillator

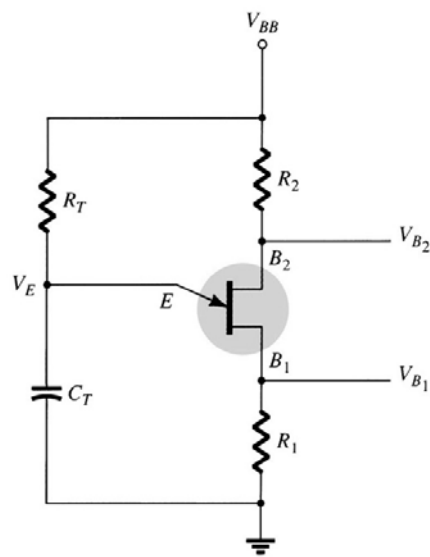

Frequency of oscillations: 
$$f_0 = \frac{1}{R_T C_T \ln[1/(1-\eta)]}$$




where  $\eta = 0.4$  to  $0.6$   
 $\eta$  is a rating of the unijunction transistor.

## Unijunction Oscillator Waveforms

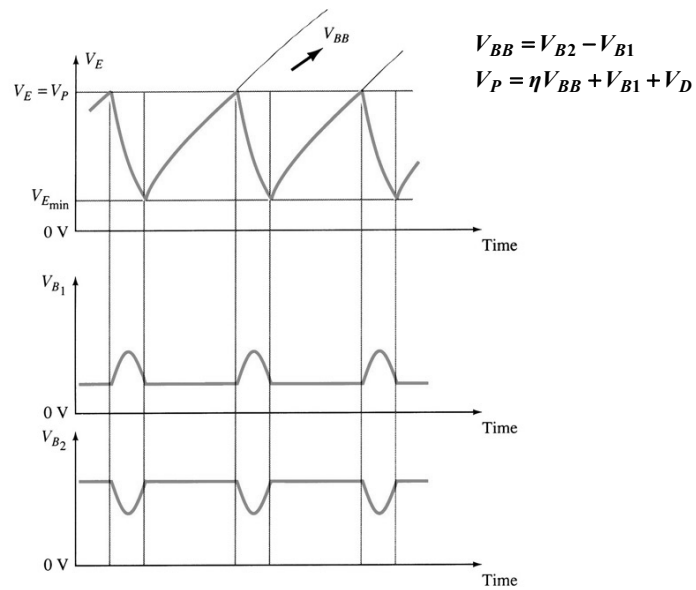


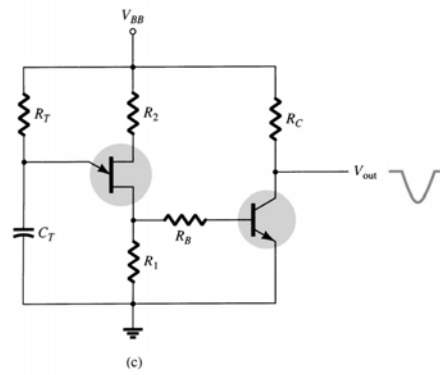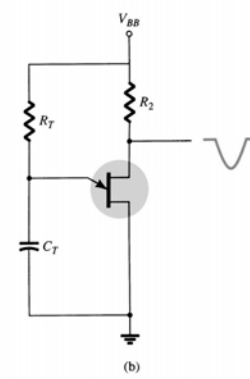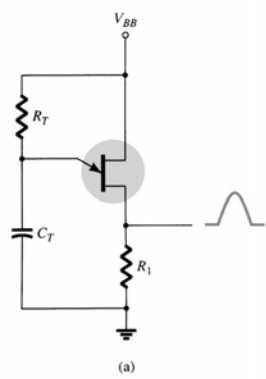The unijunction oscillator (or relaxation oscillator) produces a sawtooth waveform.





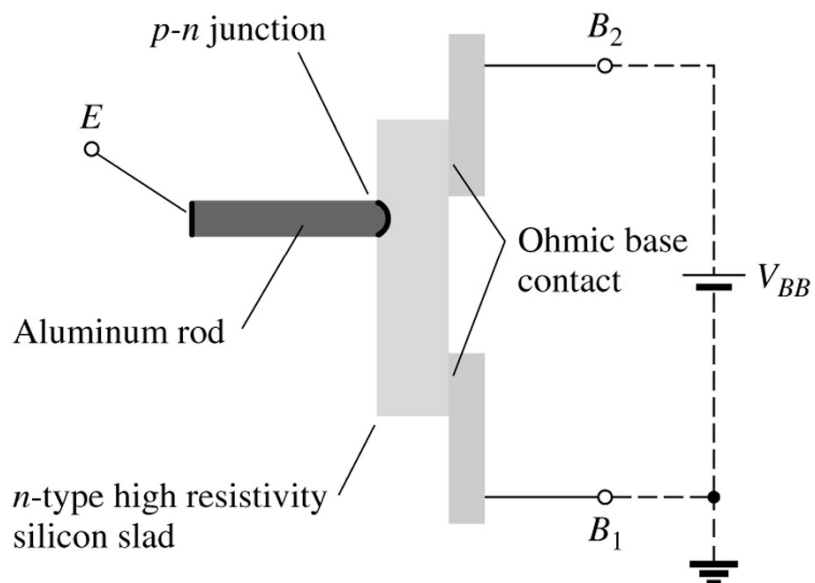
### Unijunction transistor (UJT): basic construction.



## UJT – Unijunction Transistor


The UJT is also basically a switching device.

Schematic Symbol:

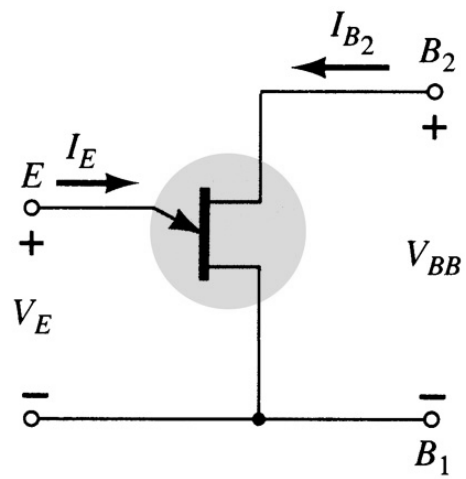

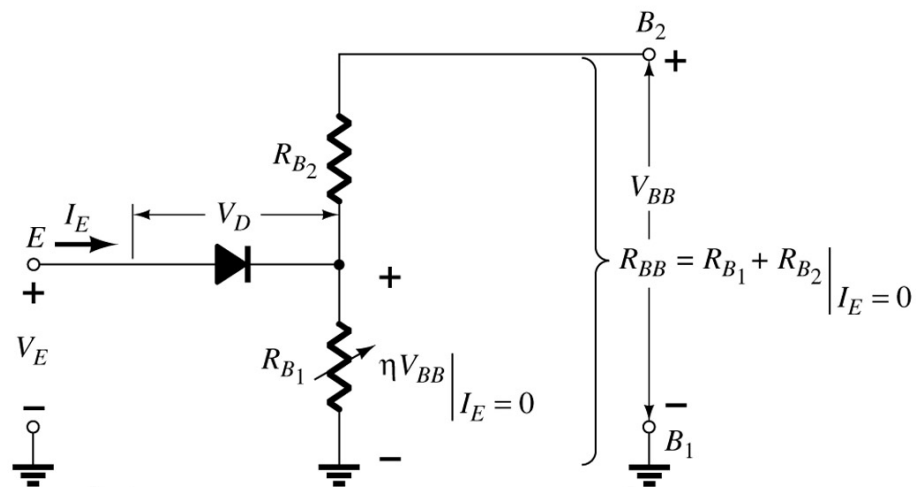
## UJT Basic Operation

Even though the UJT is a switching device it works very differently from the SCR variety of devices.



The equivalent circuit indicates that the UJT is like a diode and a resistive voltage divider circuit. The resistance exhibited by  $R_{B_1}$  is variable; it is dependent on the value of current  $I_E$ .

## UJT Characteristic Curve

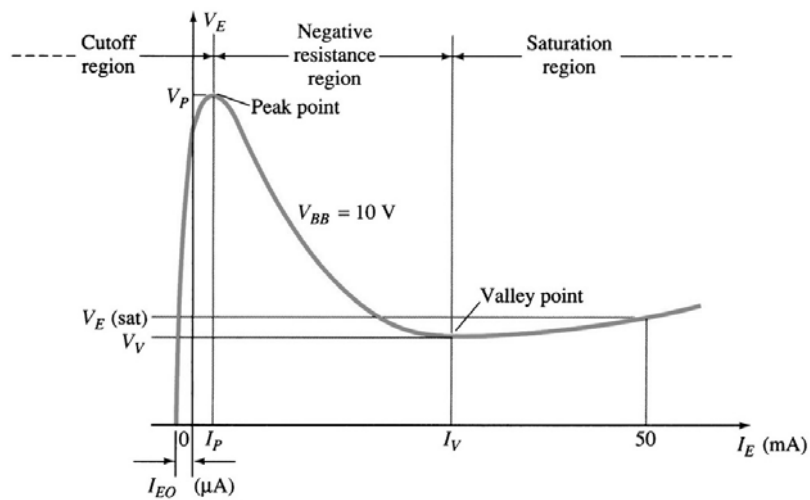

A voltage is applied across the UJT ( $V_{BB}$ ) and to the Emitter input ( $V_E$ ). Once  $V_E$  reaches a peak value ( $V_p$ ) the UJT begins to conduct. At the point where  $V_E = V_p$ , the current  $I_E$  is at minimum. This is the threshold value of  $V_E$  that puts the UJT into conduction. Once conducting,  $I_E$  increases and  $V_E$  decreases. This phenomenon occurs because the internal resistance labeled  $R_{B1}$  in the equivalent circuit decreases as the UJT conducts more and more. This is called negative resistance.