

Passive electrical properties of the neuron

Ricardo C. Araneda
rca23@columbia.edu/4-4539
Fall 2004

The following books were used for the lecture:

"From neuron to brain" Nicholls et al., 3rd Ed.


"Ion channels of excitable membranes" B. Hille, 3rd Ed.

"Fundamental neuroscience" Zigmond et al.

"Principles of neuroscience" Kandel et al., 4th Ed.


Review of basic concepts

Experiment 1

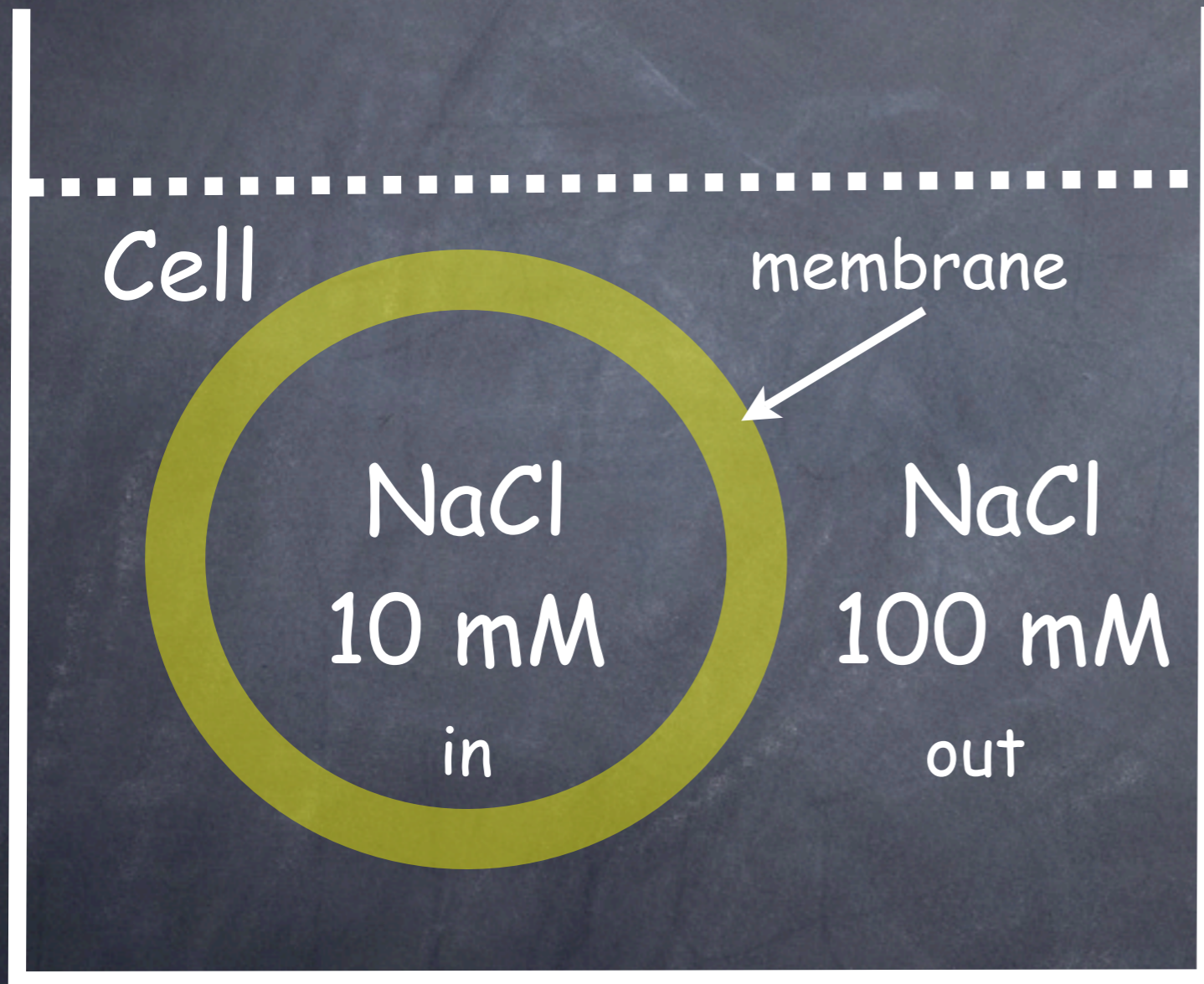

◆ Concentration Gradient


Measure membrane potential

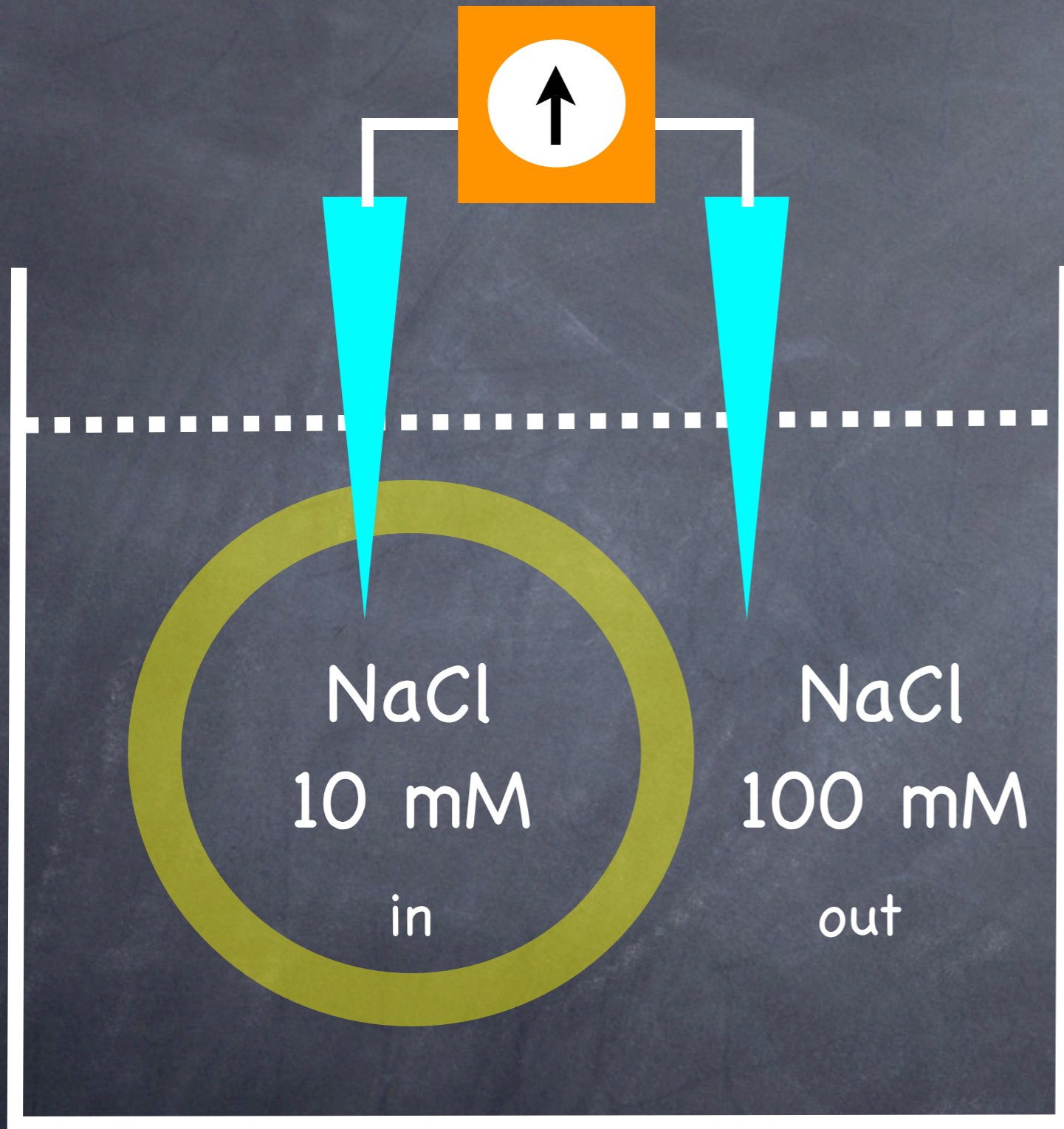

◆ Concentration Gradient

$$V = ??$$

Measure membrane potential

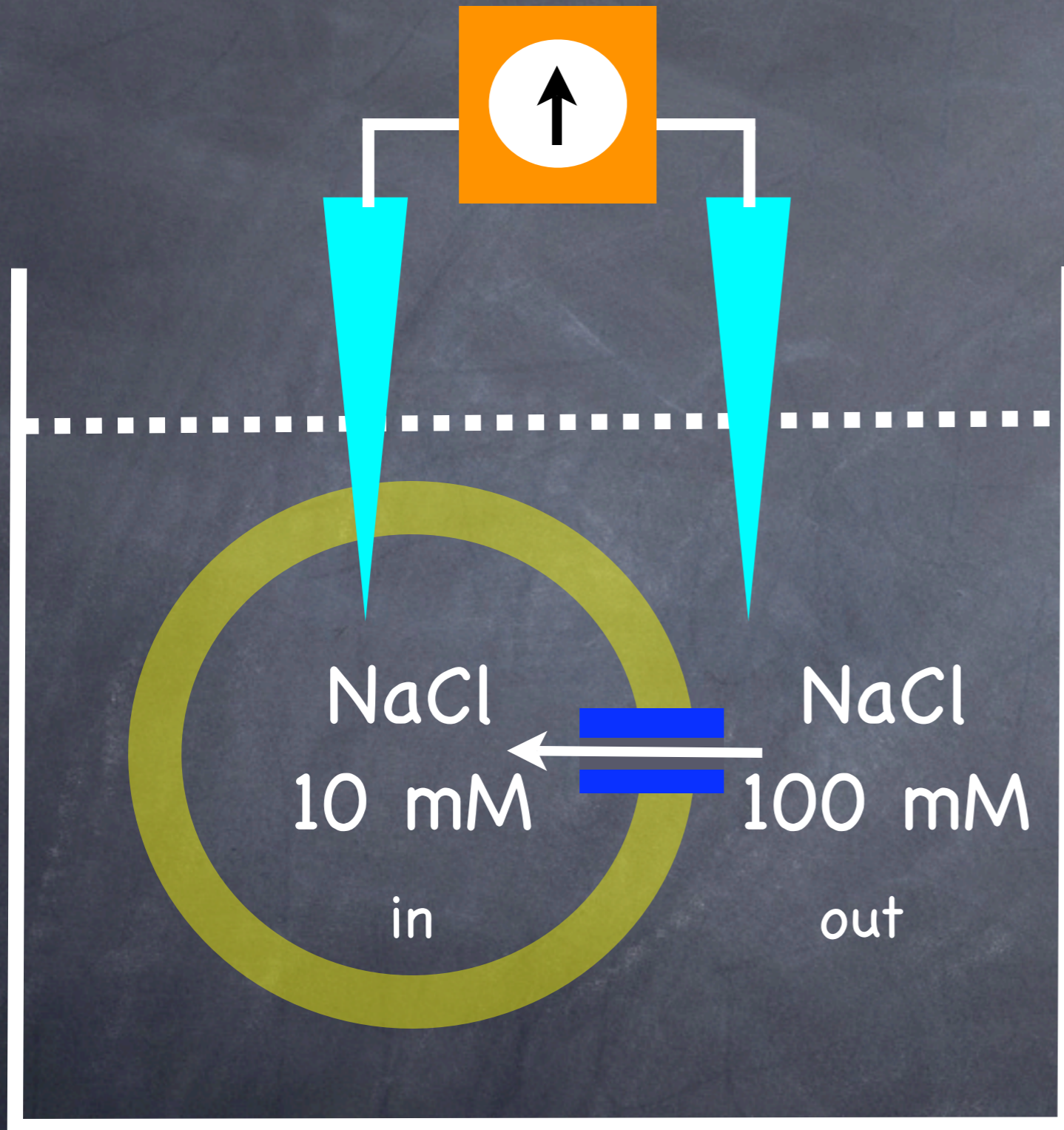


◆ Concentration Gradient


◆ membrane is equally permeable to both Na and Cl

$$V = ??$$

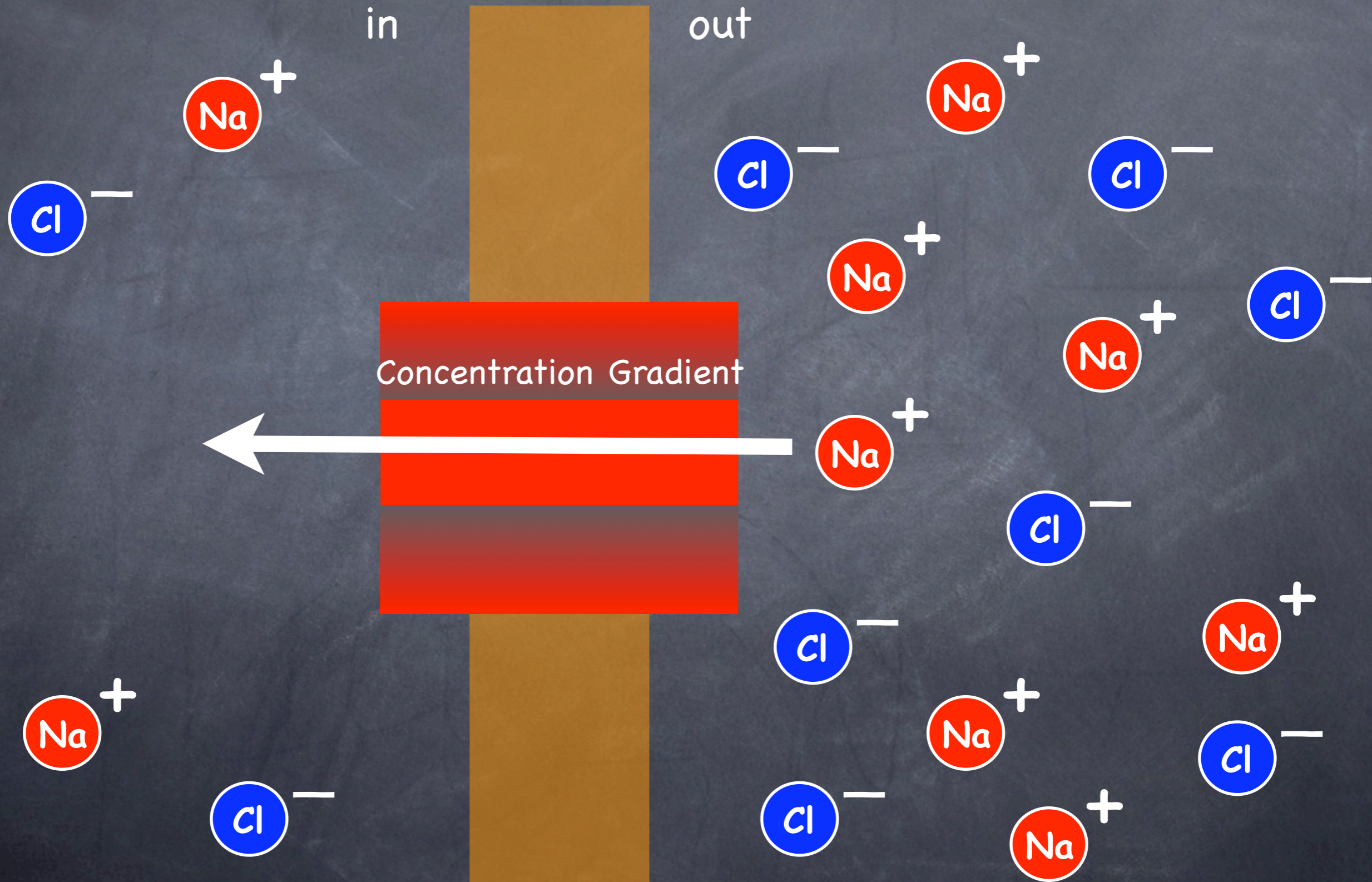
Membrane is **selectively** permeable to Sodium



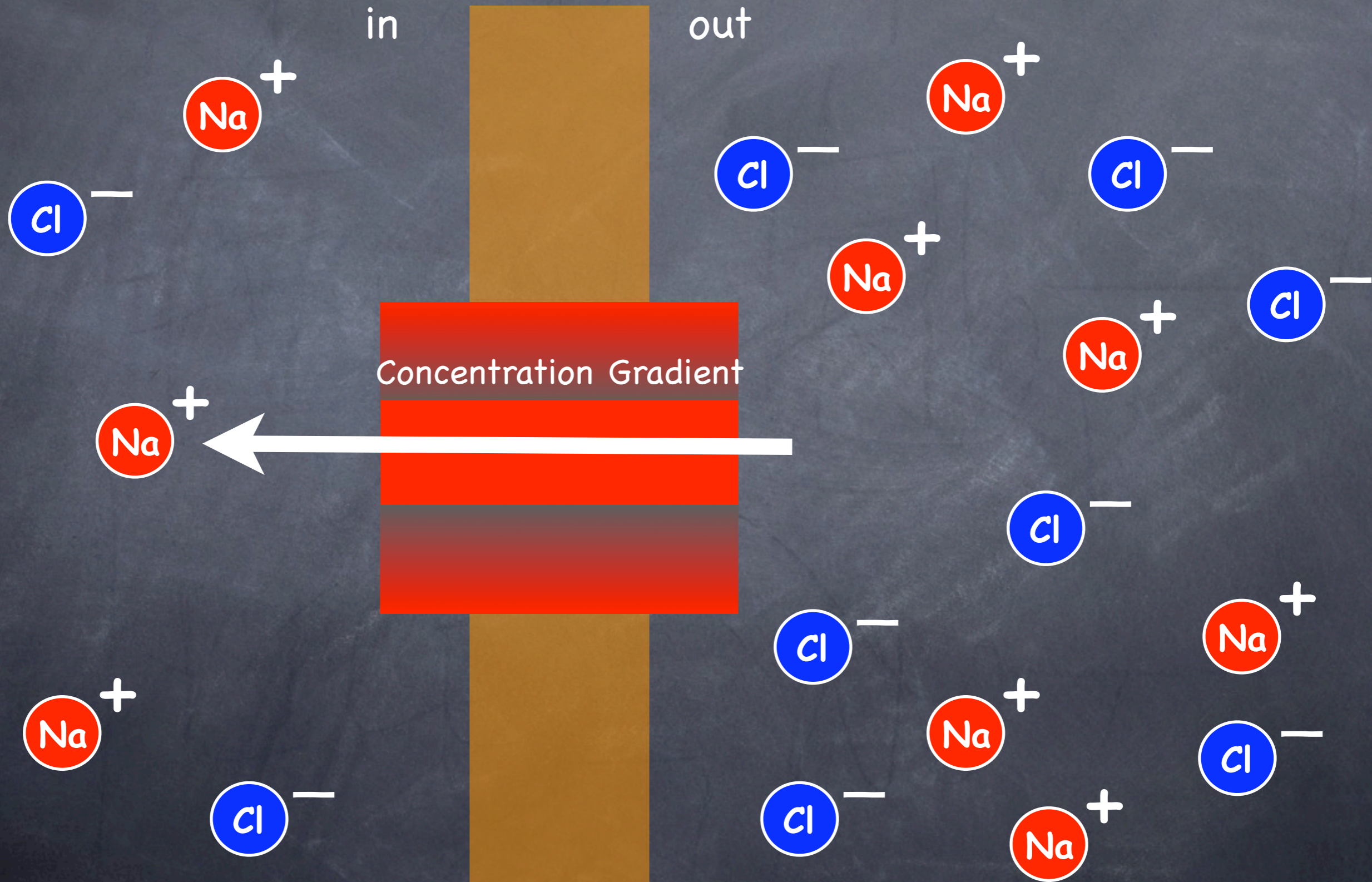
Membrane is **selectively** permeable to Sodium



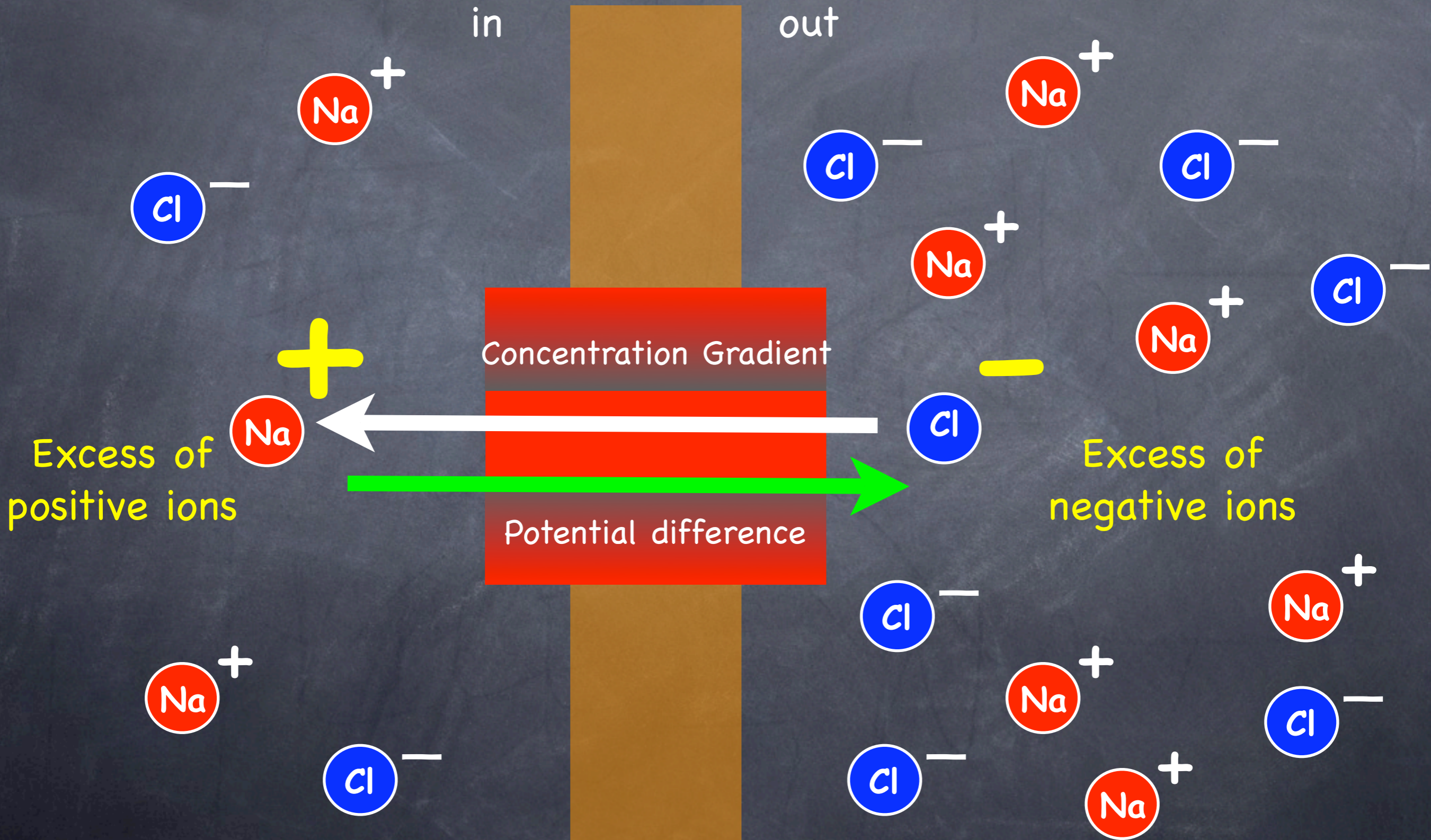Membrane is **selectively** permeable to Sodium



Membrane potential

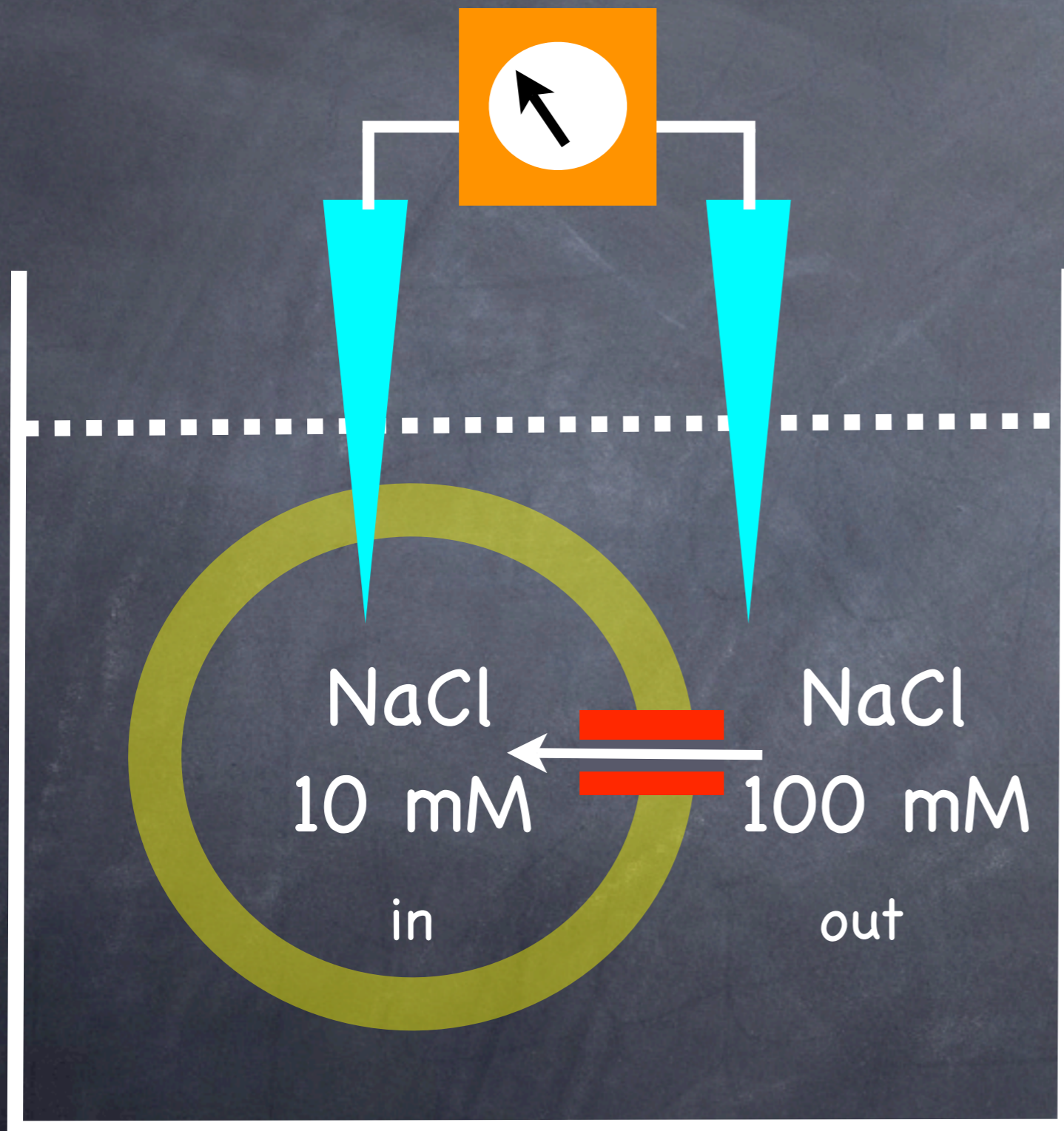

◆ Concentration Gradient across the membrane


◆ Membrane is selectively permeable to ions

$$V = \frac{RT}{F} \log \frac{[\text{out}]}{[\text{in}]}$$


$$V_{\text{Na}} = + 58 \text{ mV}$$

$$V_{\text{Cl}} = - 58 \text{ mV}$$

Membranes as capacitors

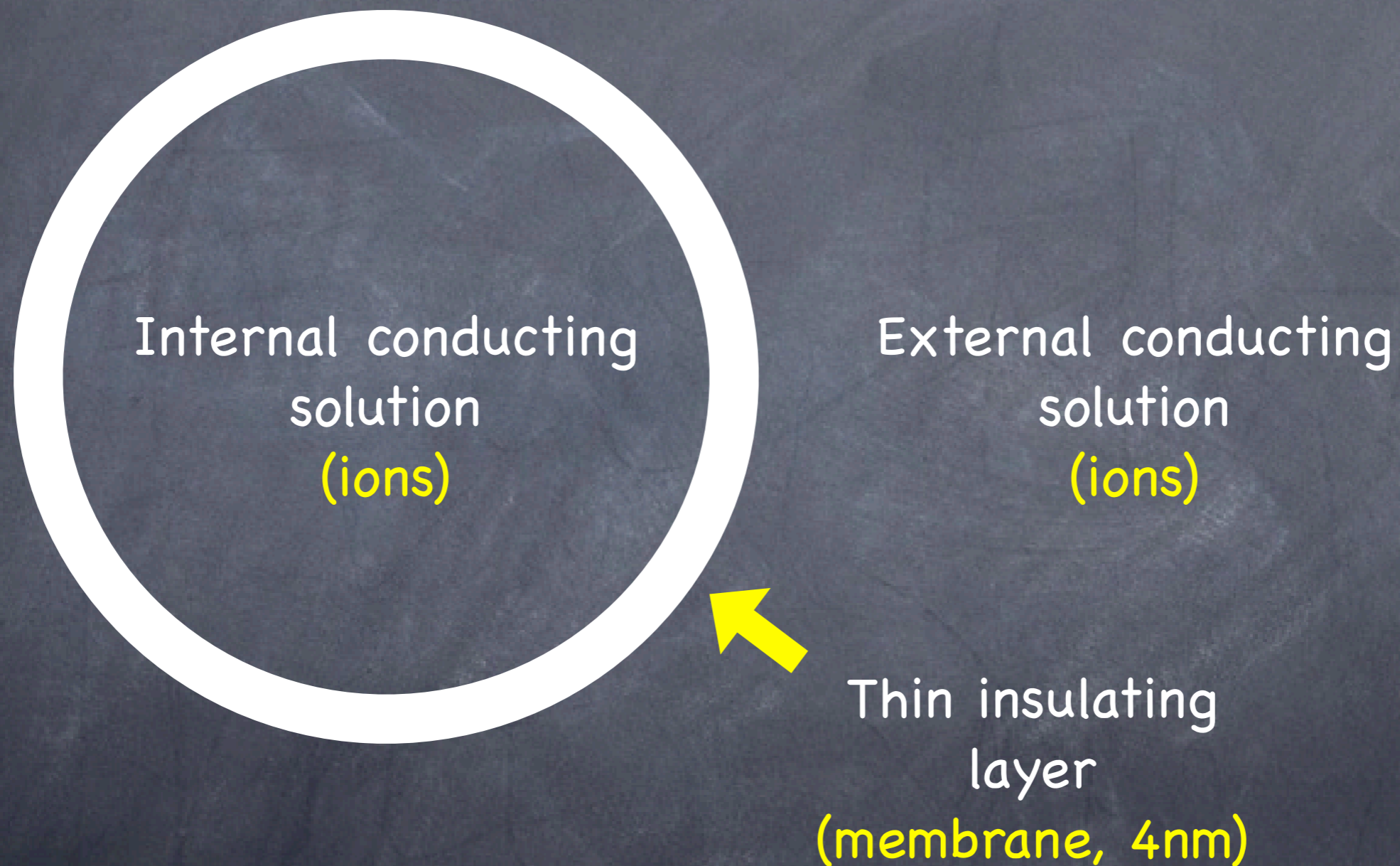


Membranes as Resistors

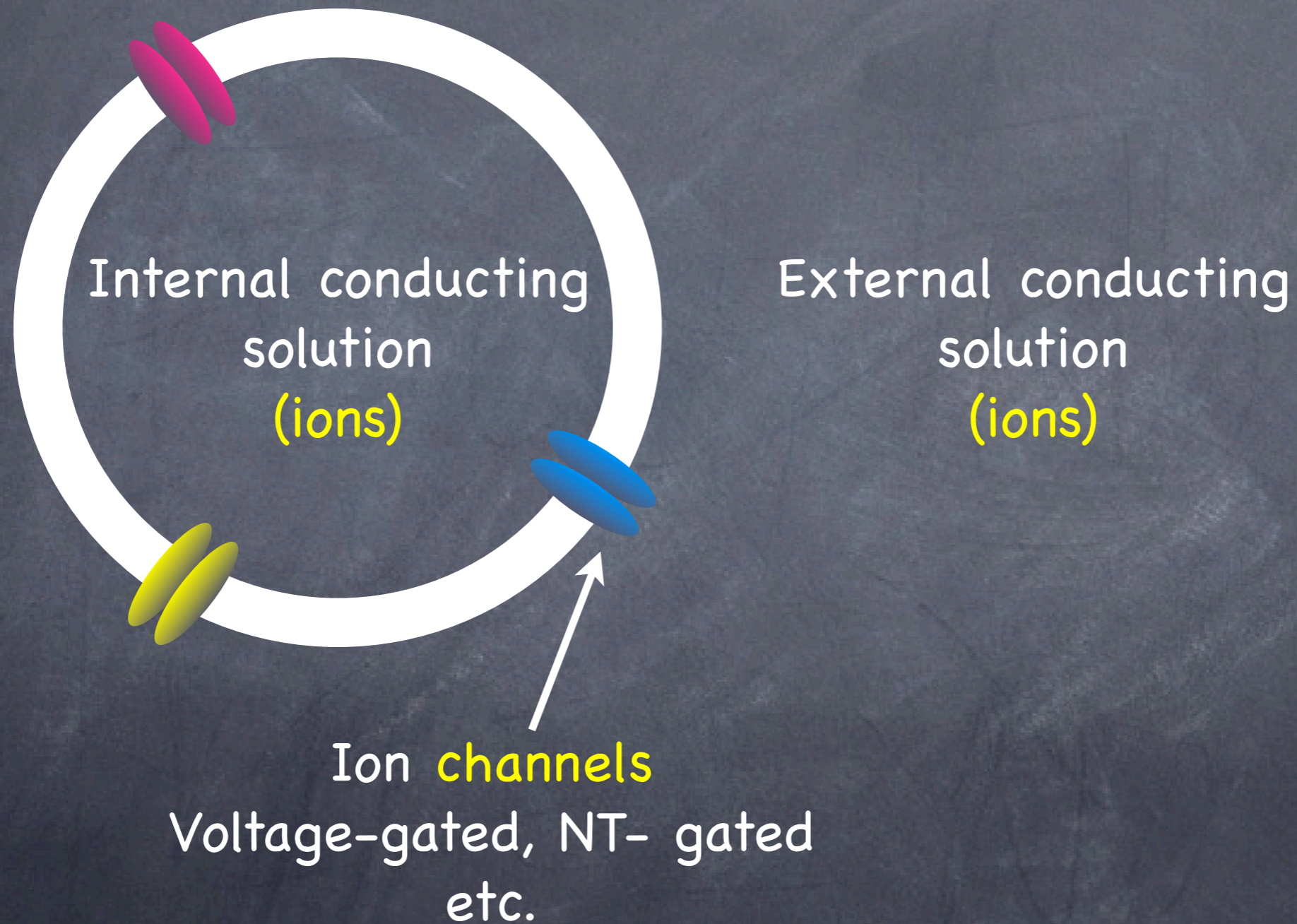


Electrical model of the cell membrane

Ion channel
RESISTOR

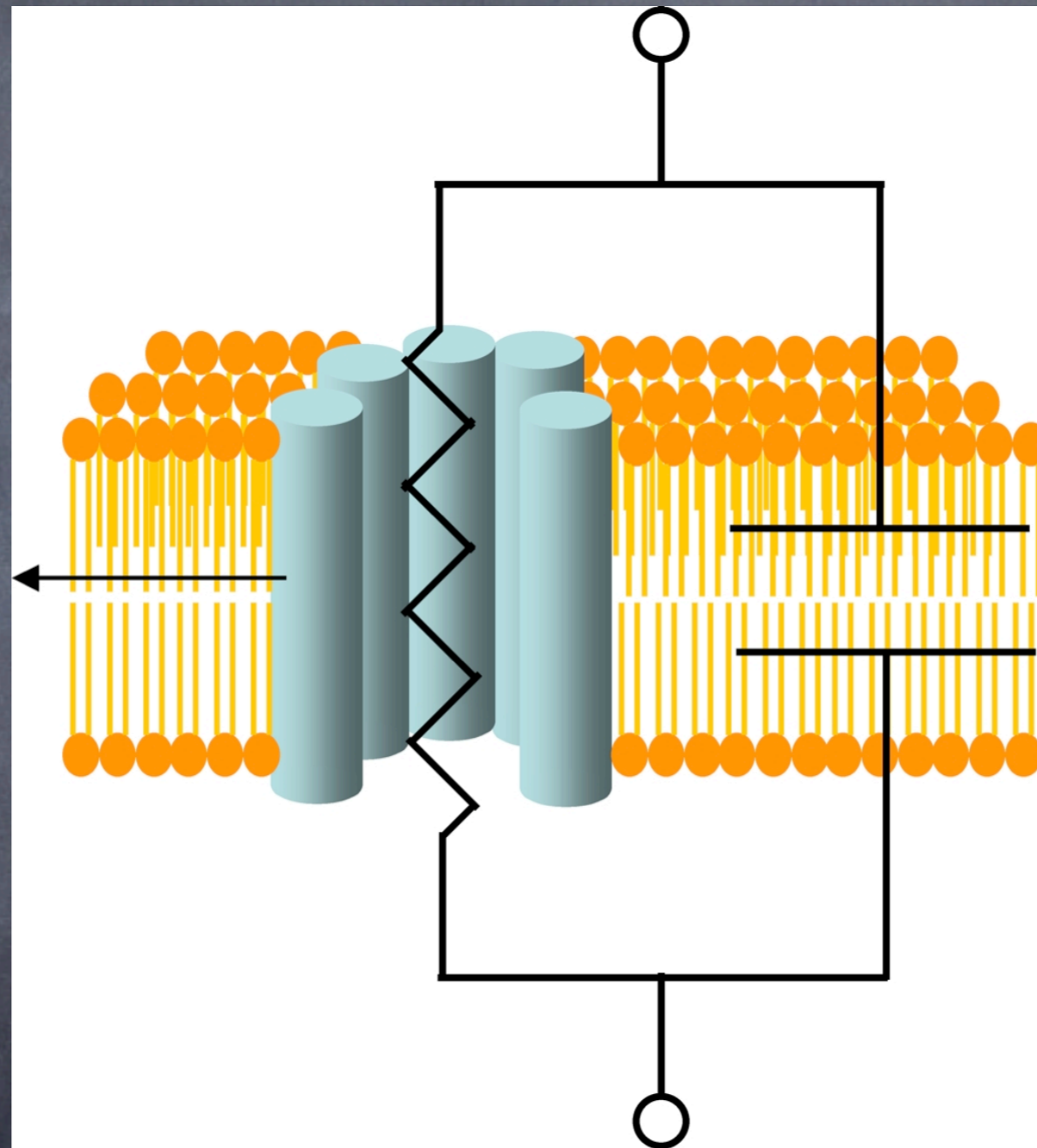

Membrane
CAPACITOR

Capacitor

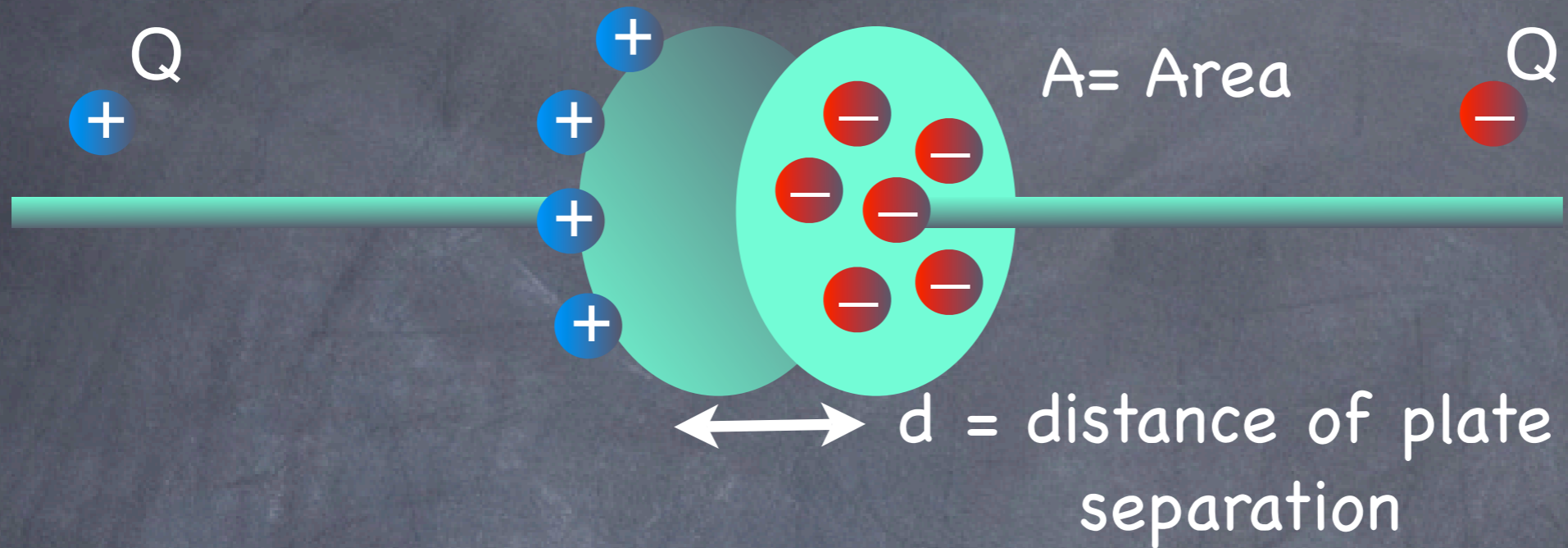

Capacitance

$$C = Q/V \quad \text{Coulomb/Volt} \quad \text{or Farads (F)}$$

$$C = \epsilon_e A/d$$


ϵ_e electrostatic permittivity

$\uparrow A = \uparrow C$


$\uparrow d = \downarrow C$

Capacitor


rubber membrane

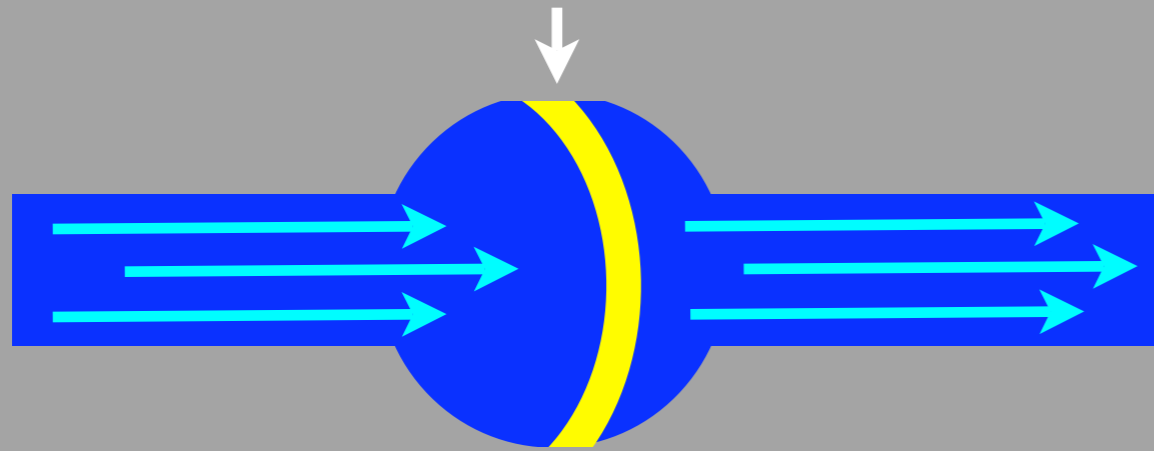


Water pressure

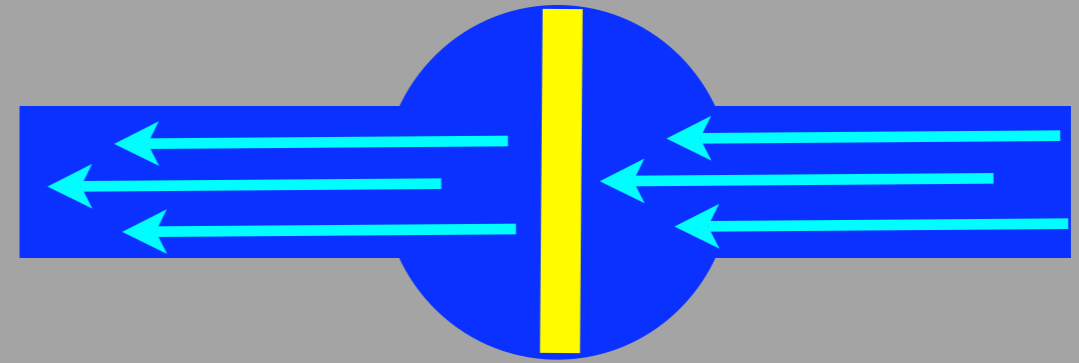

Release of pressure

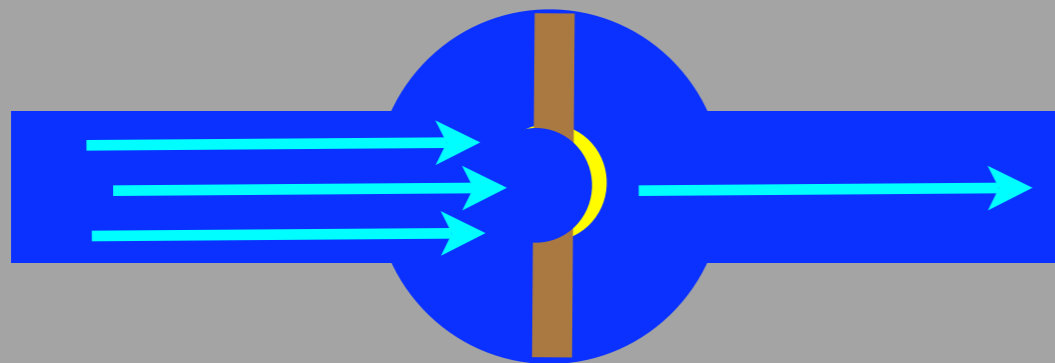


Small Capacitance

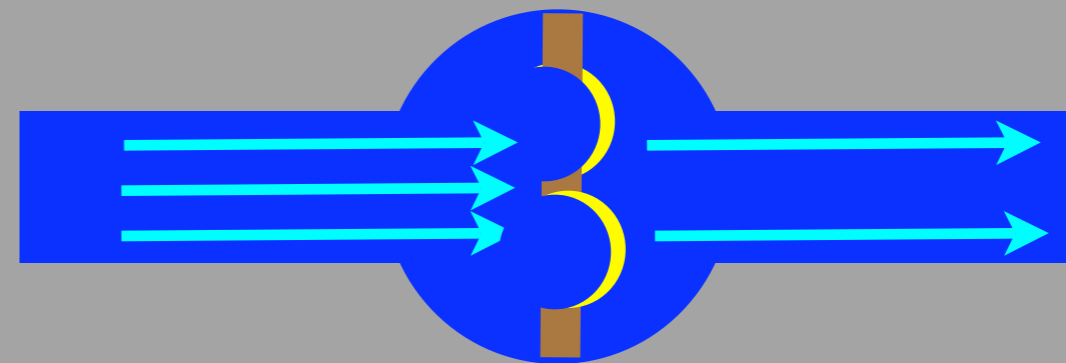

Capacitors in parallel add larger Capacitance

Resistance

A = Area

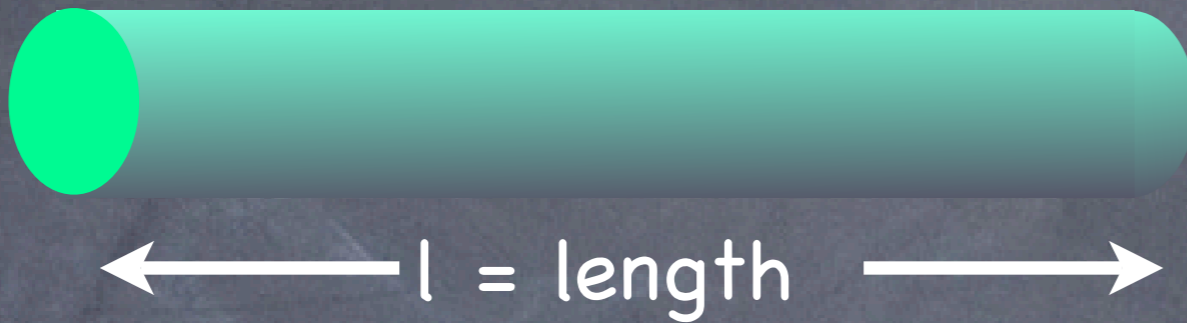

Ohm's law

$$R = V/I \text{ Ohms } (\Omega)$$


$$R = \rho l/A \quad \rho \text{ resistivity}$$

$$\uparrow I = \uparrow R$$

$$\uparrow A = \downarrow R$$


For the same current, a larger R produces larger V

Resistors

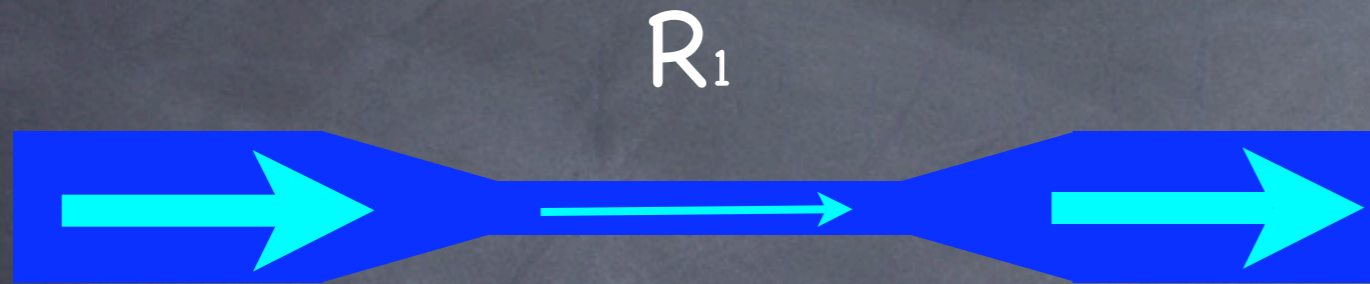

For ion channels is better to think in terms of conductance

$$R_1 = 1/g_1$$

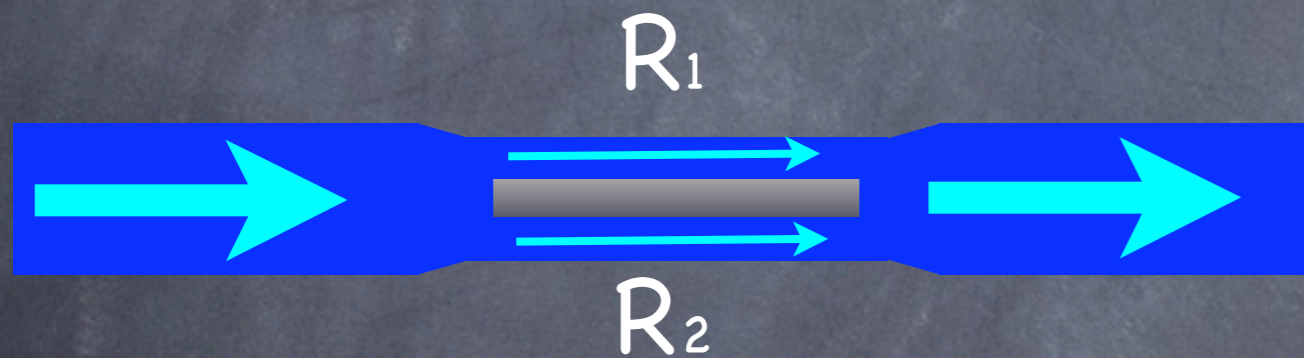


As the # of Rs in parallel increases R_T decreases!

$$1/R_T = 1/R_1 + 1/R_2$$

More (open) channels in the membrane more conductance

$$g_T = g_1 + g_2$$

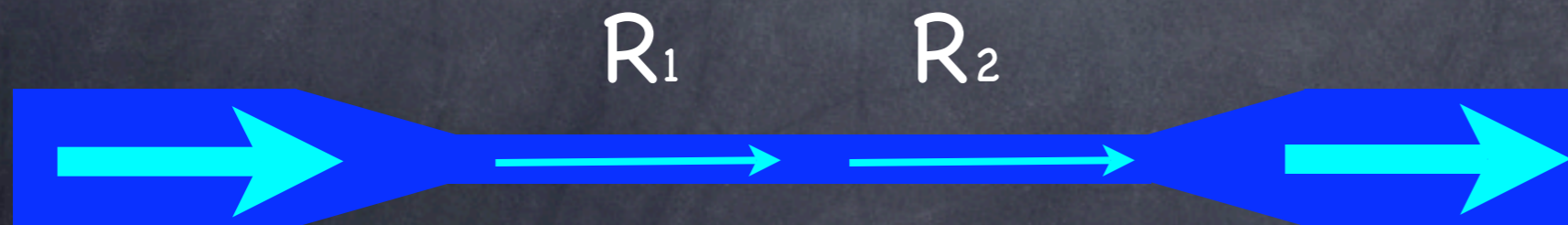

$$R_T = R_1 + R_2$$

Long, thin parts of a neuron have large resistance!

Some useful equations

Current

$$I = \text{Coulombs/second Amperes (A)}$$

Ohm's law

$$V = IR$$

Capacitance

$$C = Q/V \text{ Coulombs/Volts (F)}$$

Voltage across capacitor

$$V = Q/C$$

Changing the voltage
in a capacitor

$$\Delta V = \Delta Q/C$$

We change the charge
by passing current


$$I_c = \Delta Q/\Delta t$$

The change in V depends
on the duration of I_c

$$\Delta V = I_c \Delta t / C$$

Also remember...

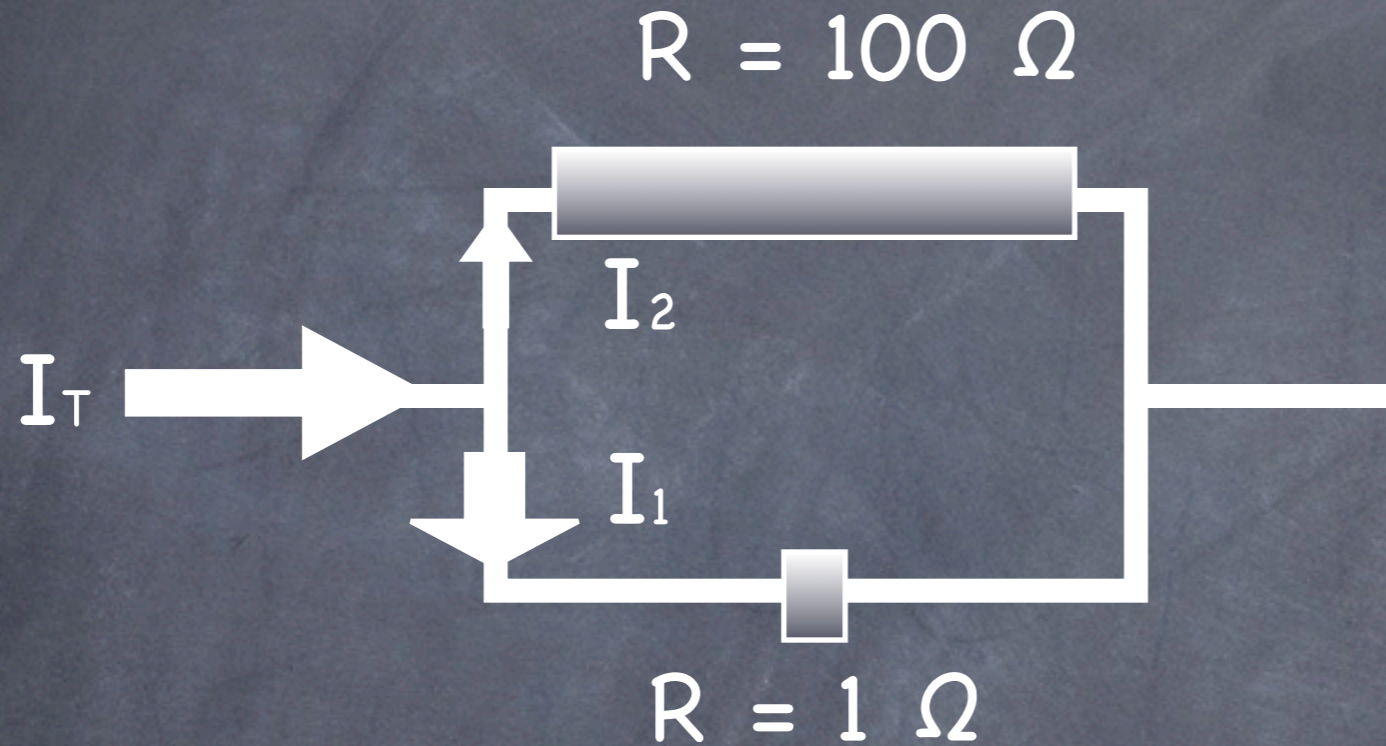
Current likes to flow through the path with less resistance




And

$$I_T = I_1 + I_2$$

Electrical model of the cell membrane

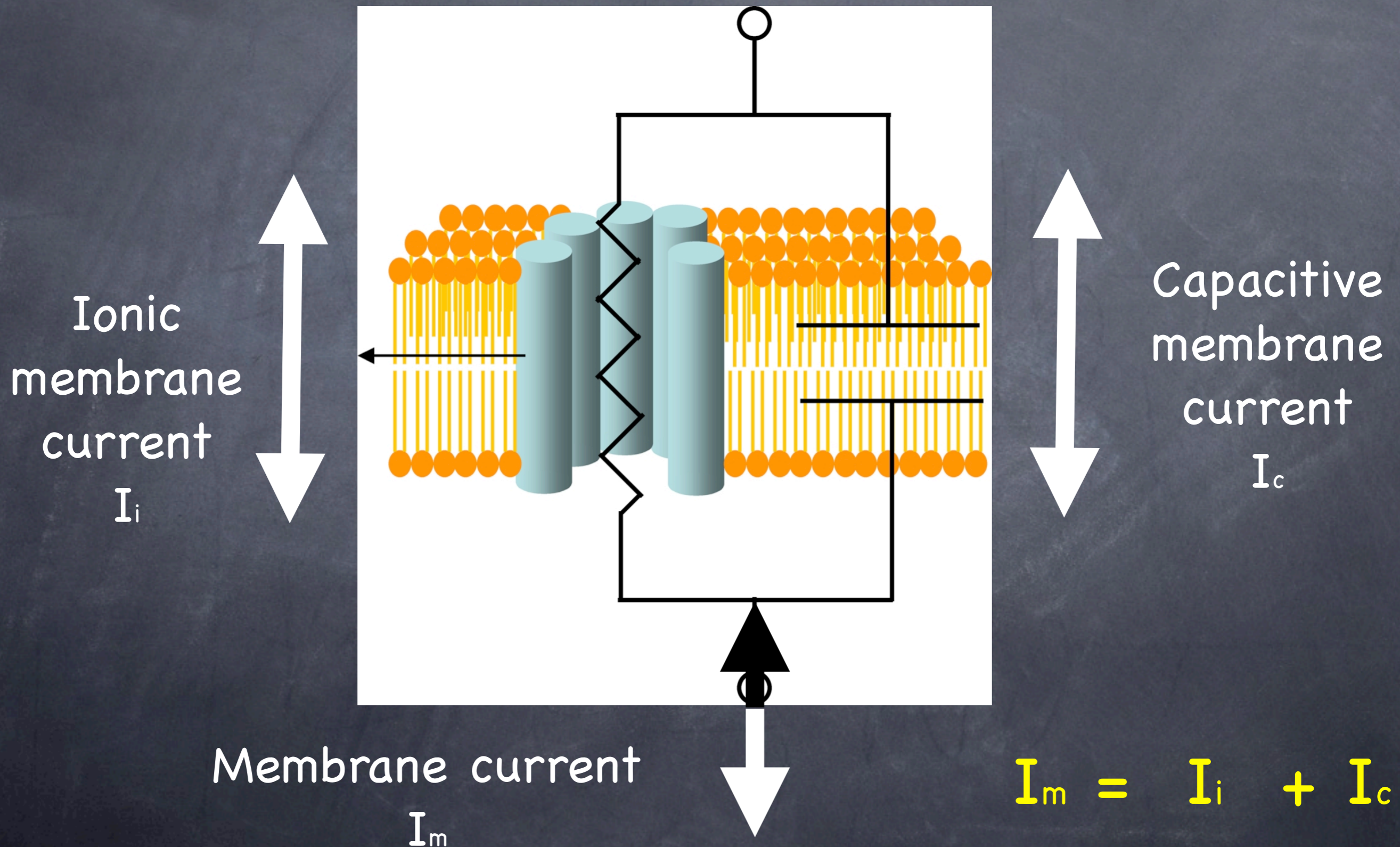

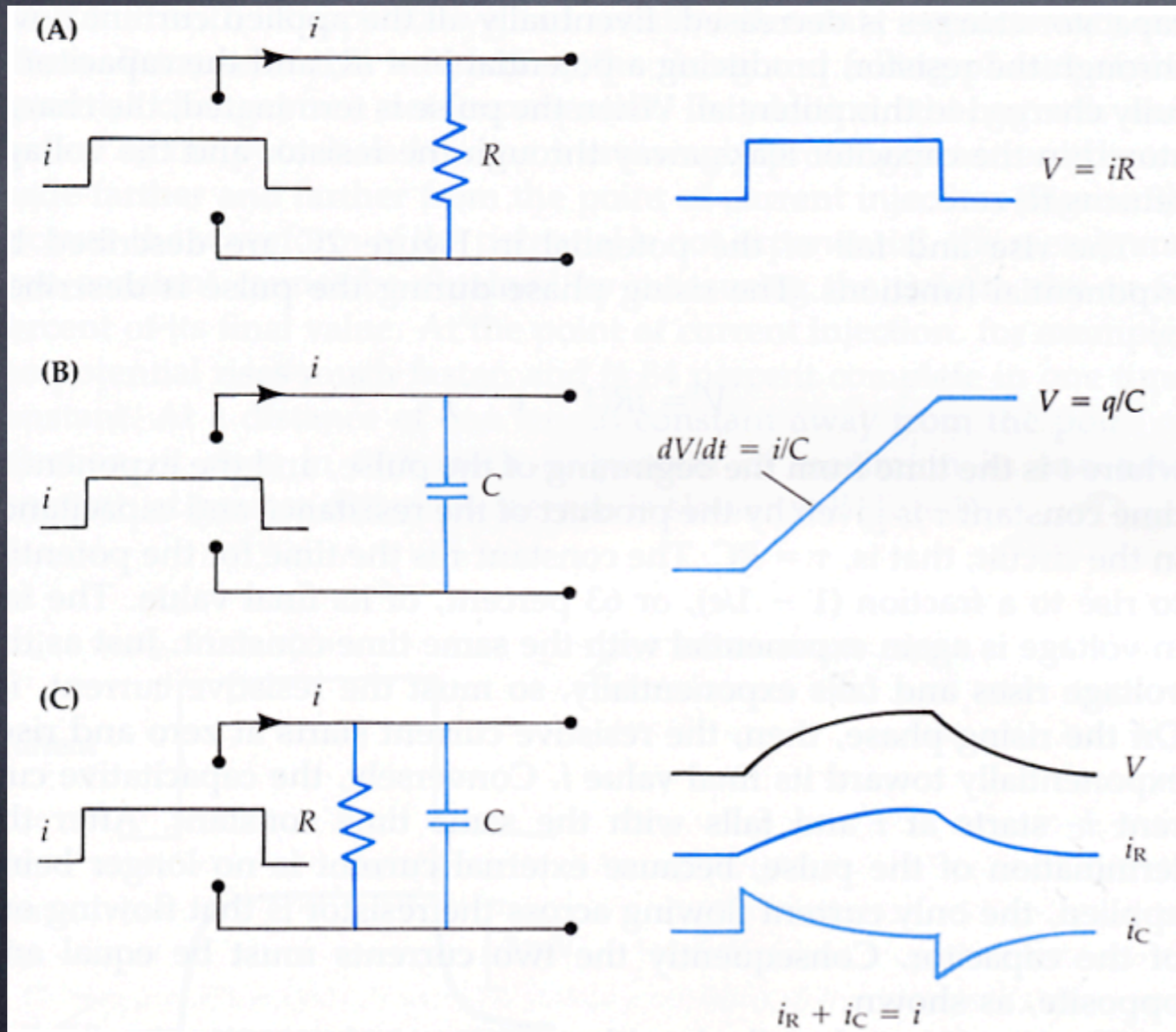Effects of passing current on circuits containing **R** and **C**




V changes instantaneously with I

V changes linearly in time with I


V changes exponentially with a time constant = RC

RC circuits

(A) CIRCUIT

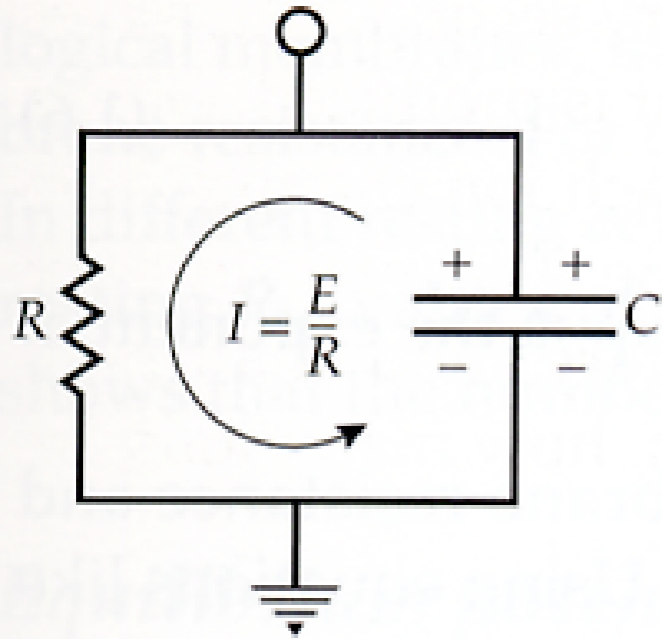

(B) TIME COURSE OF DISCHARGE

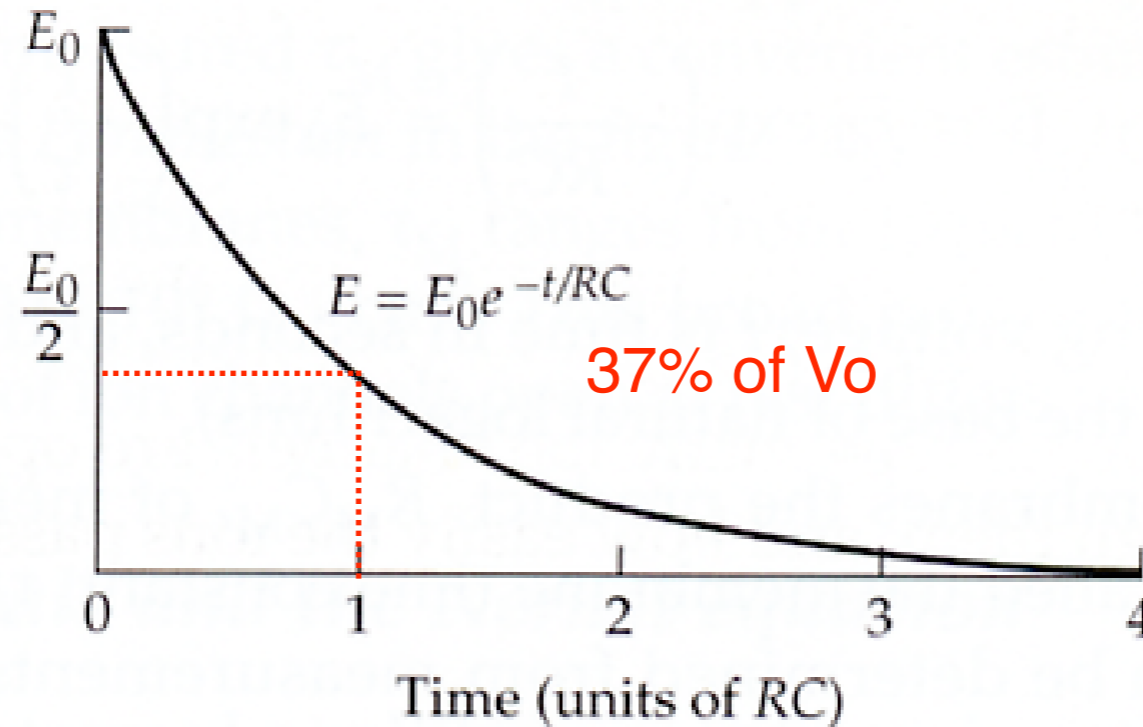


(E and V are the same)

For a rising exponential

$$V = V_0 \left(1 - e^{-t/RC} \right)$$

Experiment 2

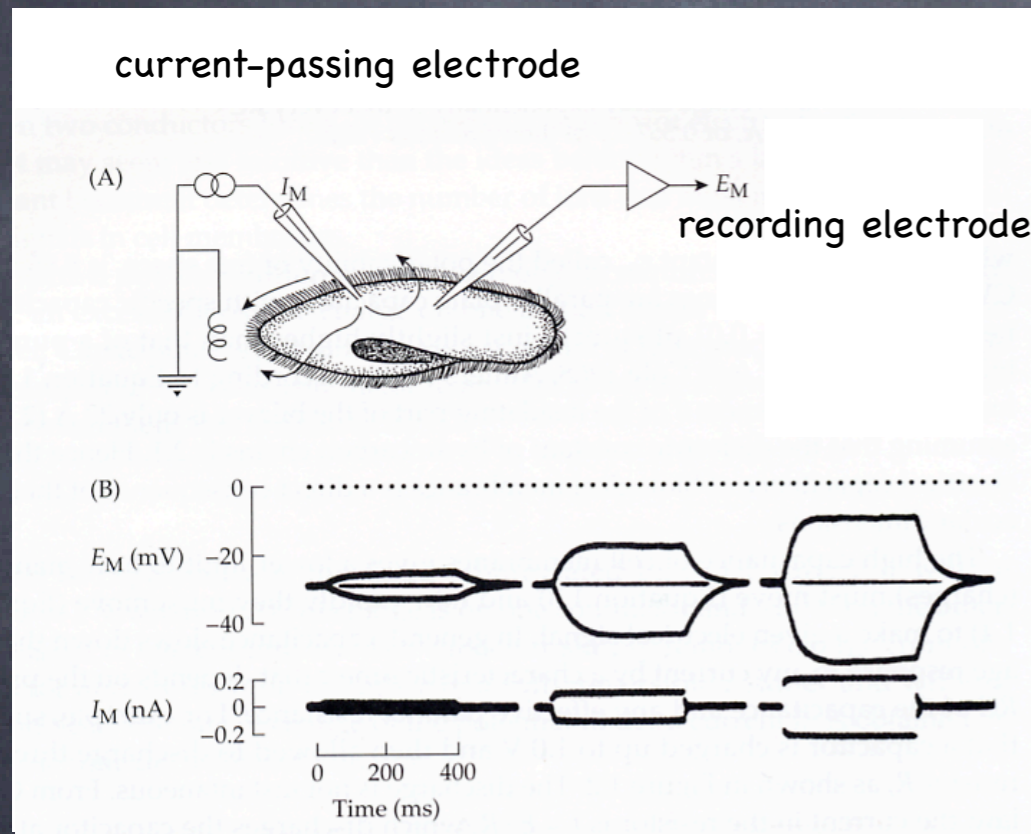Passing current and recording the membrane potential from a paramecium





Negative current makes the membrane potential more negative
hyperpolarization

Positive current makes the membrane potential more positive
depolarization

“electrotonic potential”

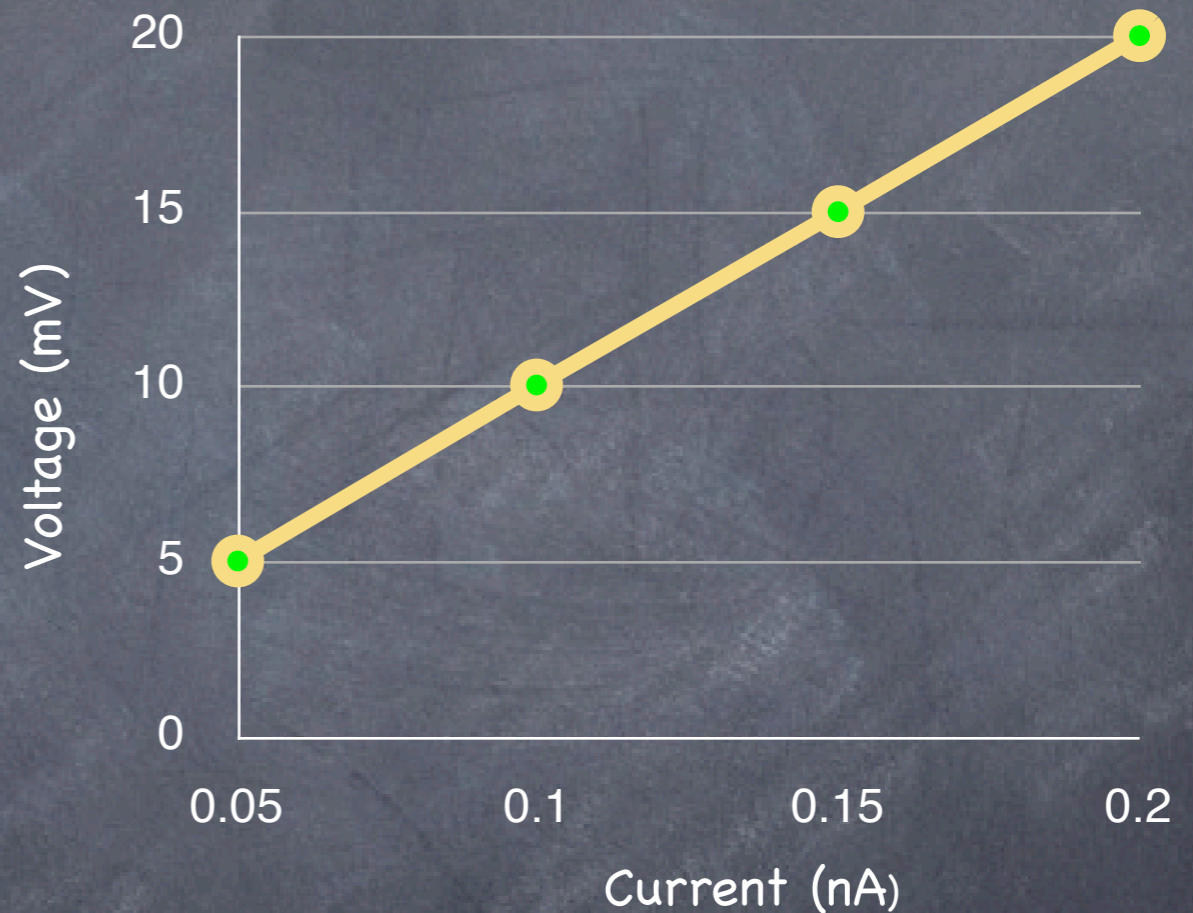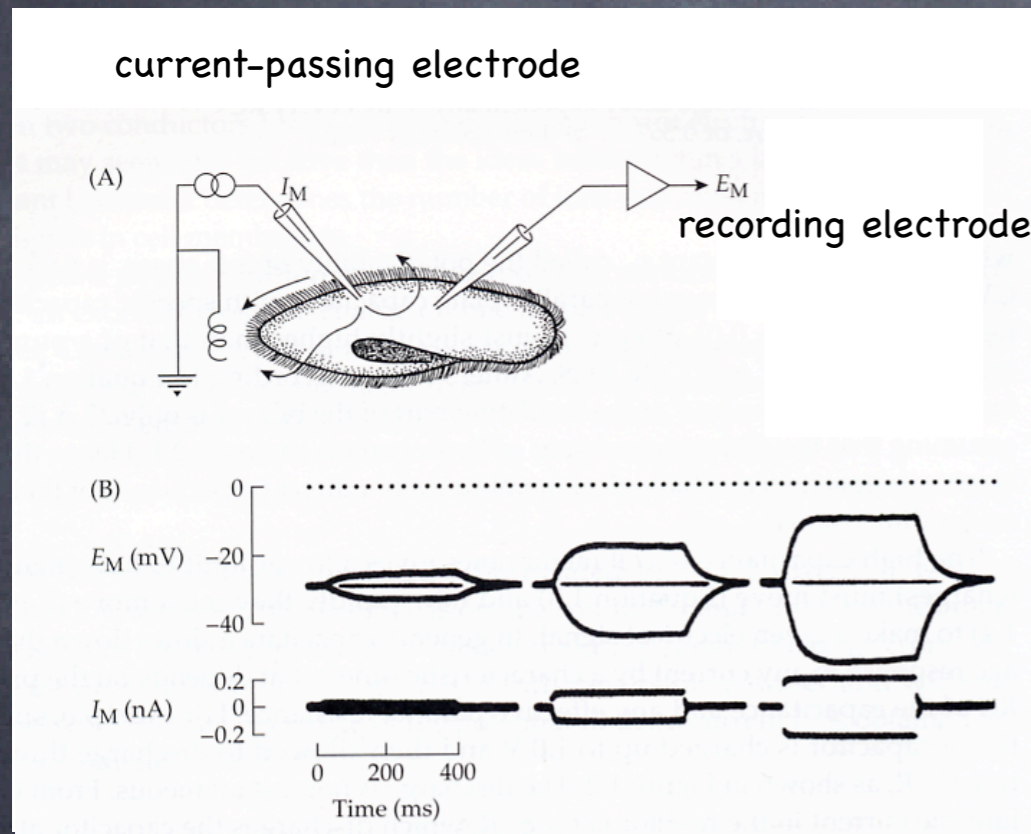Linear relationship between current and voltage




“electrotonic potential”

$$V = I \square R_{in}$$

Input Resistance $R_{in} = 100 \text{ M}\Omega$

Specific membrane resistance

cross section of a cell

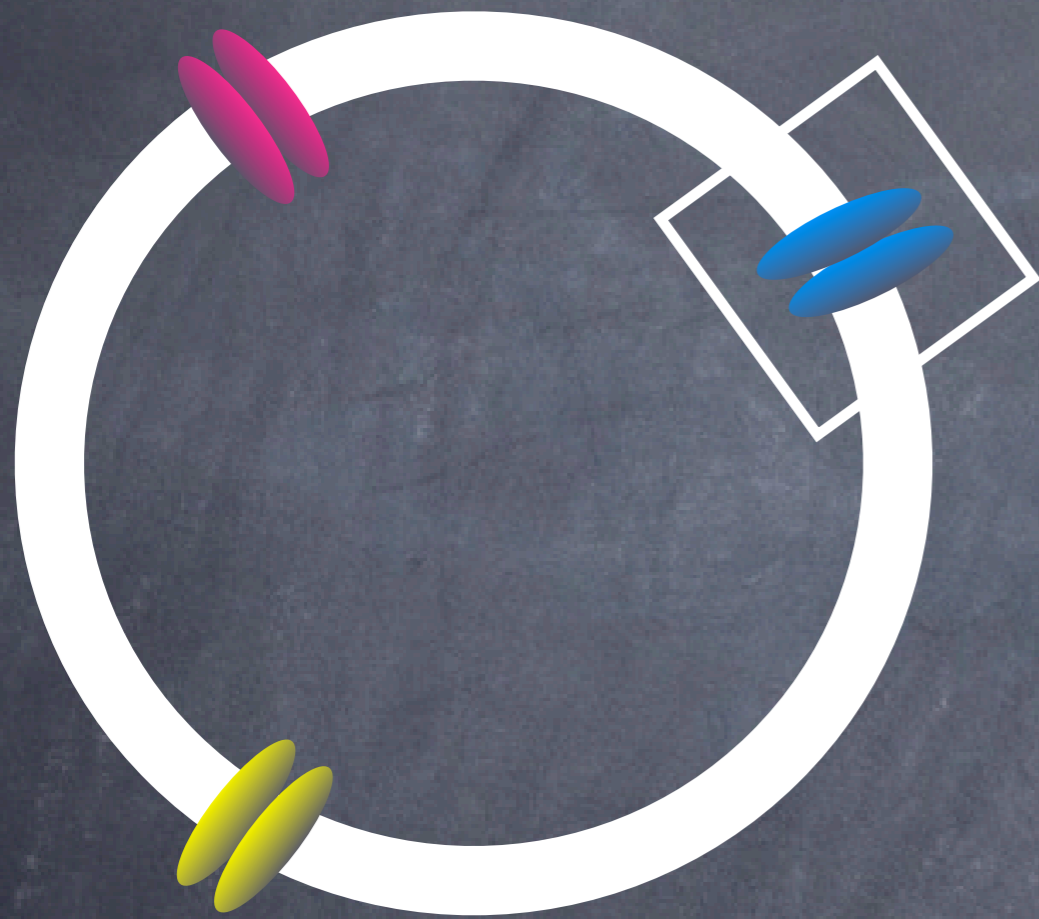

To compare cell with different sizes

The specific membrane resistance
(resistance per area)

$$R_M = \Omega \square \text{cm}^2$$

depends on the # of channels per cm^2

More channels make R_M smaller


For a spherical cell

$$R_{in} = R_M / 4\pi a^2 \quad a = \text{radius}$$

R_{in} determines how much the cell depolarizes in response to a steady current

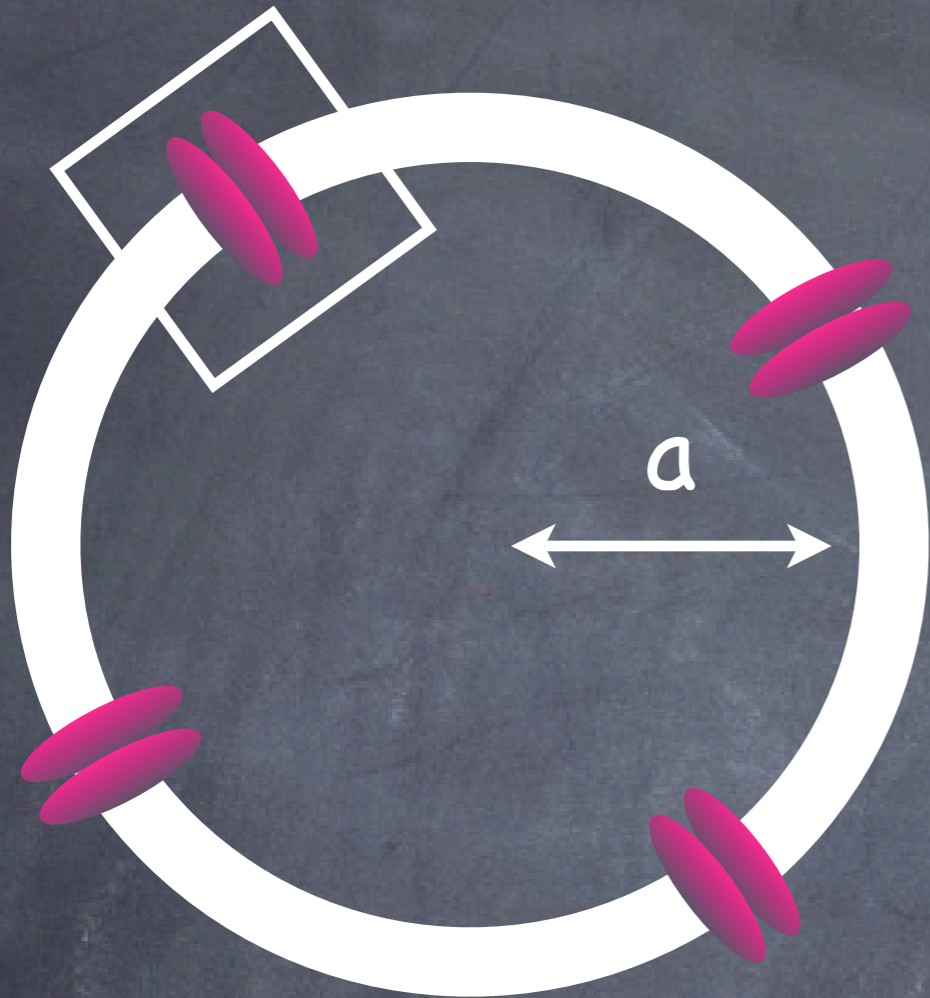Example

same $R_M = 2000 \Omega \cdot \text{cm}^2$




Cell diameter is 50 μm

$$a = 25 \mu\text{m} = 25 \cdot 10^{-4} \text{cm}$$

$$R_{in} = R_M / 4\pi a^2$$

$$R_{in} = 2000 \Omega \cdot \text{cm}^2 / 4\pi (25 \cdot 10^{-4} \text{cm})^2$$

$$R_{in} = 25 \text{ M}\Omega$$

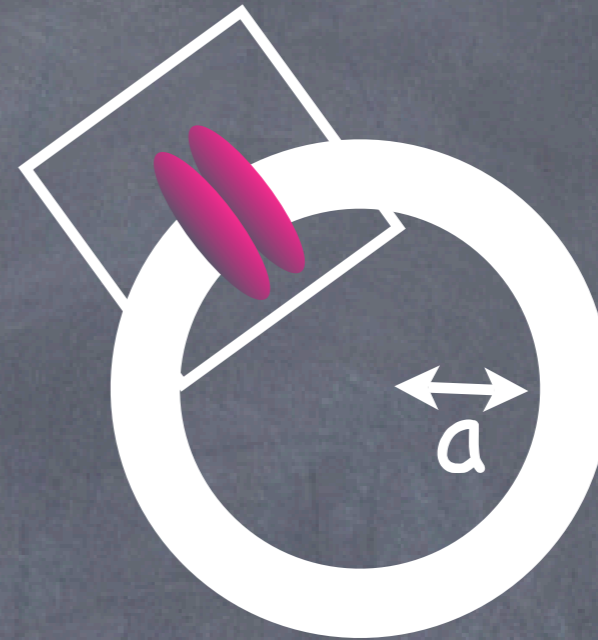


Cell diameter is 5 μm

your numbers here...

$$R_{in} = 637 \text{ M}\Omega$$

R_{in} is larger in a smaller cell

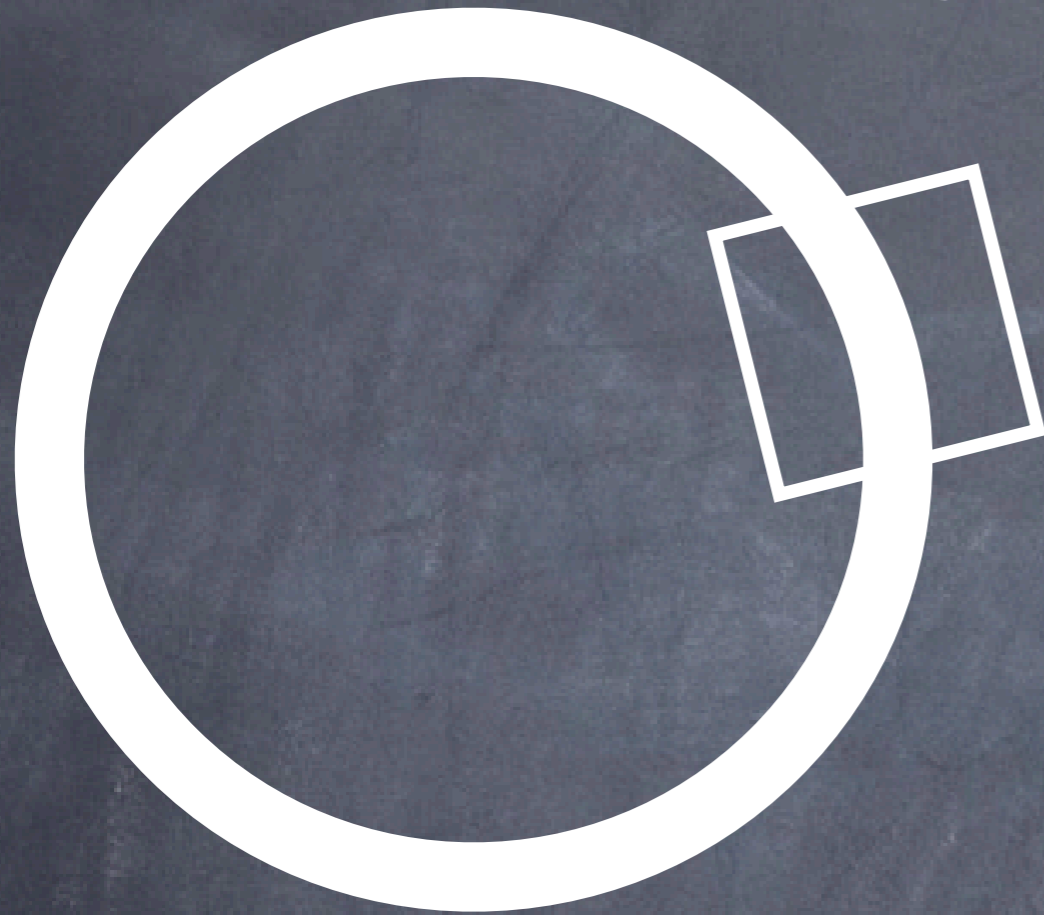Specific membrane capacitance of biological membranes



$$C_M = 1 \text{ F/cm}^2$$

For a cell at -80 mV how many ions is this?

$$C_M = Q/V$$

$$Q = 10^{-6} \text{ C/V} \times 0.08 \text{ V}$$


$$Q = 8 \times 10^{-8} \text{ C/cm}^2$$

Faraday constant $\approx 10^5$ Coulombs/mole

Avogadro's number = 6.02×10^{23} mole⁻¹

Then this is 4.8×10^{11} ions/cm² Is this a lot???

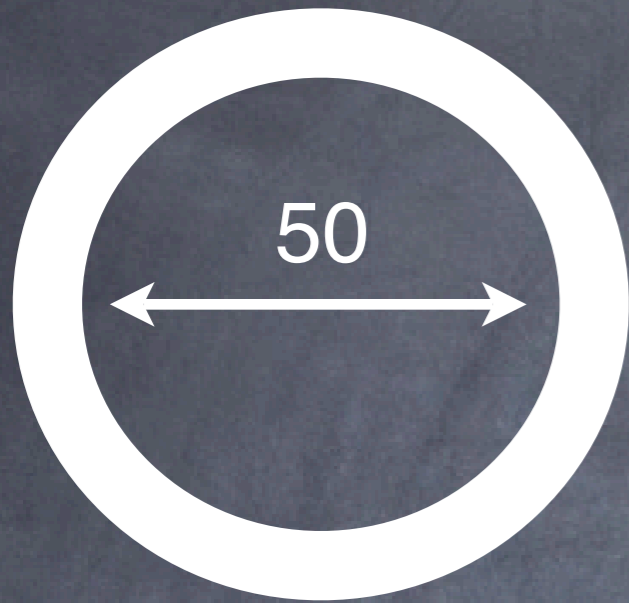Let's assume the cell is 50 μ m in diameter



$$a = 25 \mu\text{m} = 25 \times 10^{-4} \text{cm}$$

surface of sphere $A = 4\pi a^2$

$$A = 7.85 \times 10^{-5} \text{cm}^2$$

$$4.8 \times 10^{11} \text{ ions in } 1 \text{ cm}^2 \quad \text{So total is } 4 \times 10^7 \text{ ions}$$

The volume of this cell is $6.55 \times 10^{-8} \text{cm}^3$

Then this number of ions is $\sim 10^{-6} \text{M}$

If KCl inside is 120 mM this means that only
 $\sim 1/120,000$ ions is in excess!

Large cell
large capacitance

Small cell
small capacitance





“ C_M ” is the same
(same membrane)

For a spherical cell, the **input capacitance**

$$C_{in} = C_M \square 4\pi a^2 \quad a = \text{radius}$$

More charge (current) is required to change the voltage
across a large cell

In summary

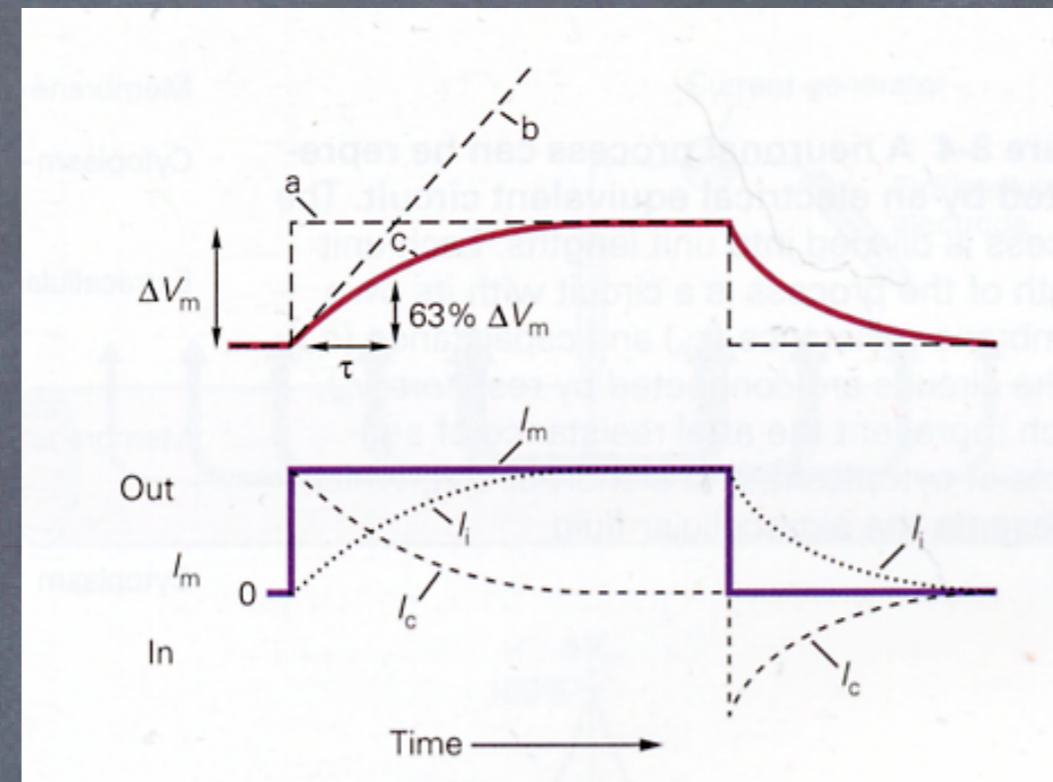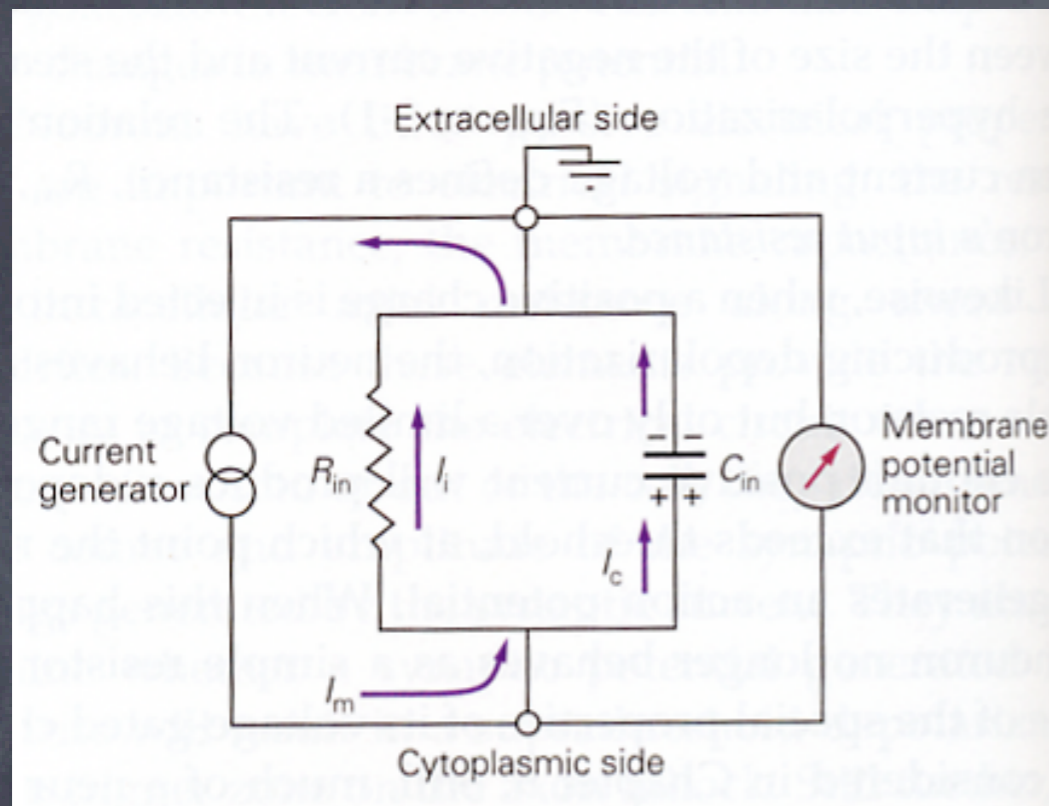

$$R_{in} = R_M / 4\pi a^2$$



$$C_{in} = C_M \square 4\pi a^2$$

$$\tau = R_{in} \square C_M$$

The product of input Capacitance and Resistance (τ) determines the time it takes change the potential


Notice that (τ) is not affected by "a"

Real Neurons

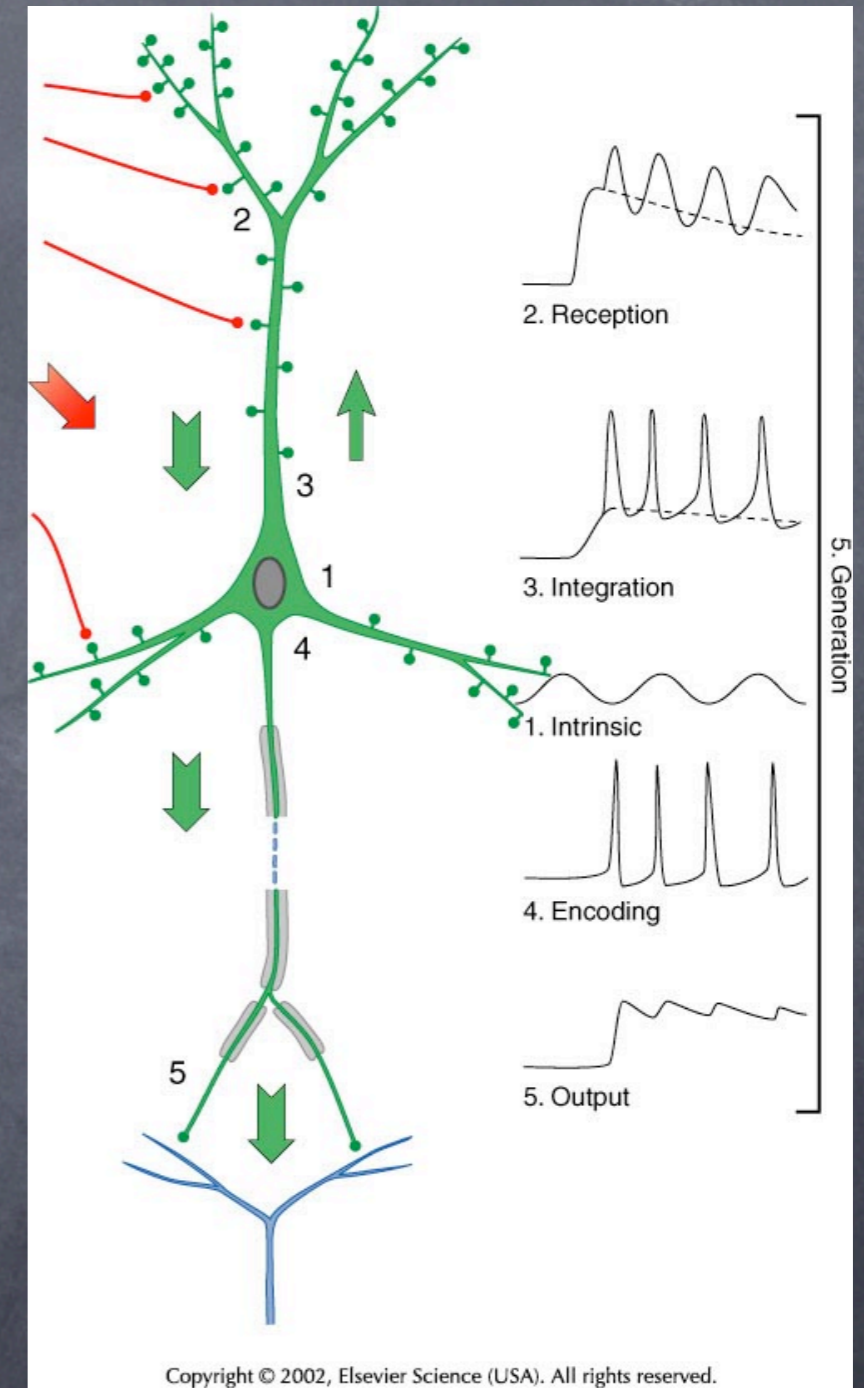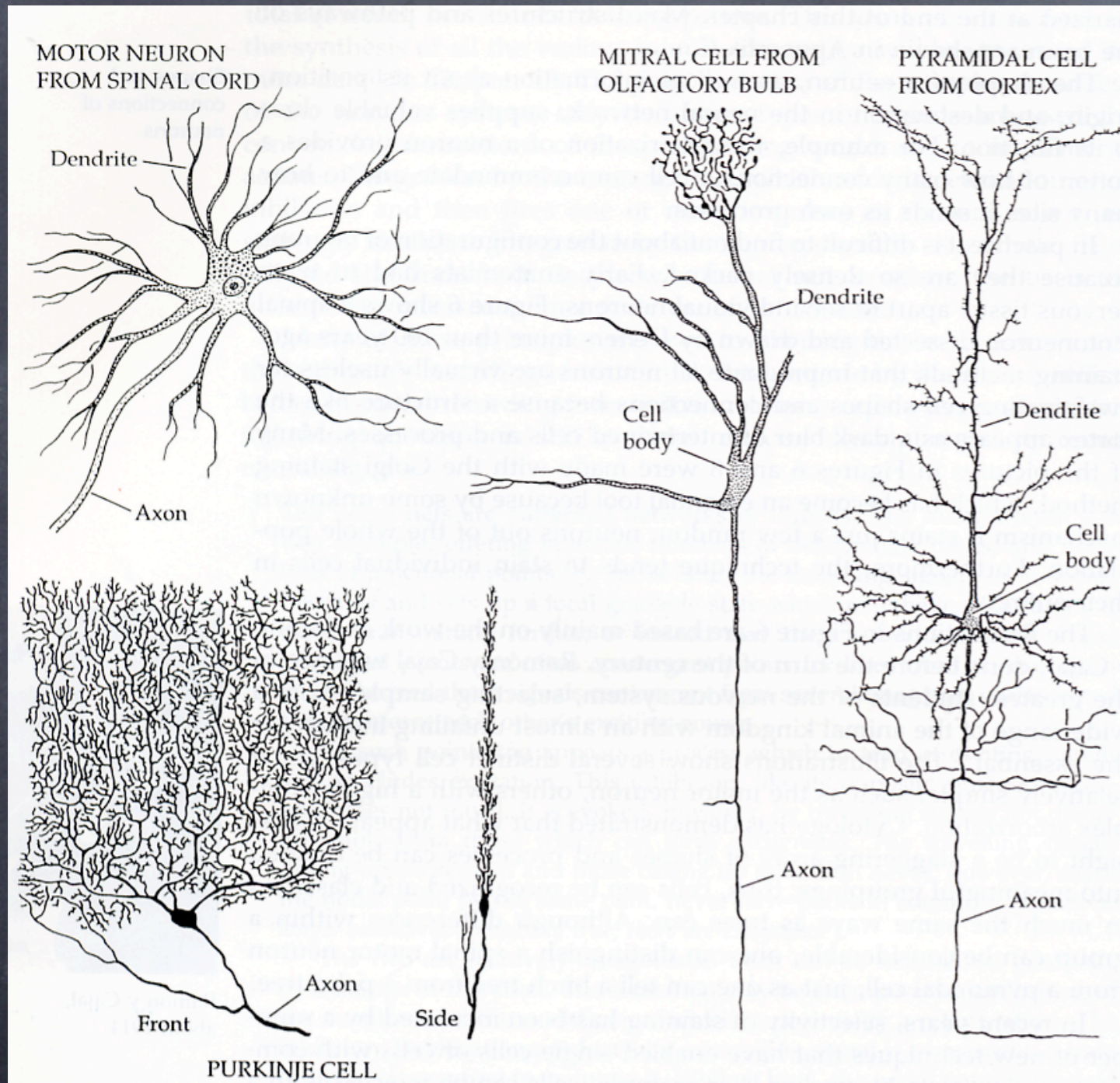

How are signals affected by the passive properties of the membrane ?

Experiment 3

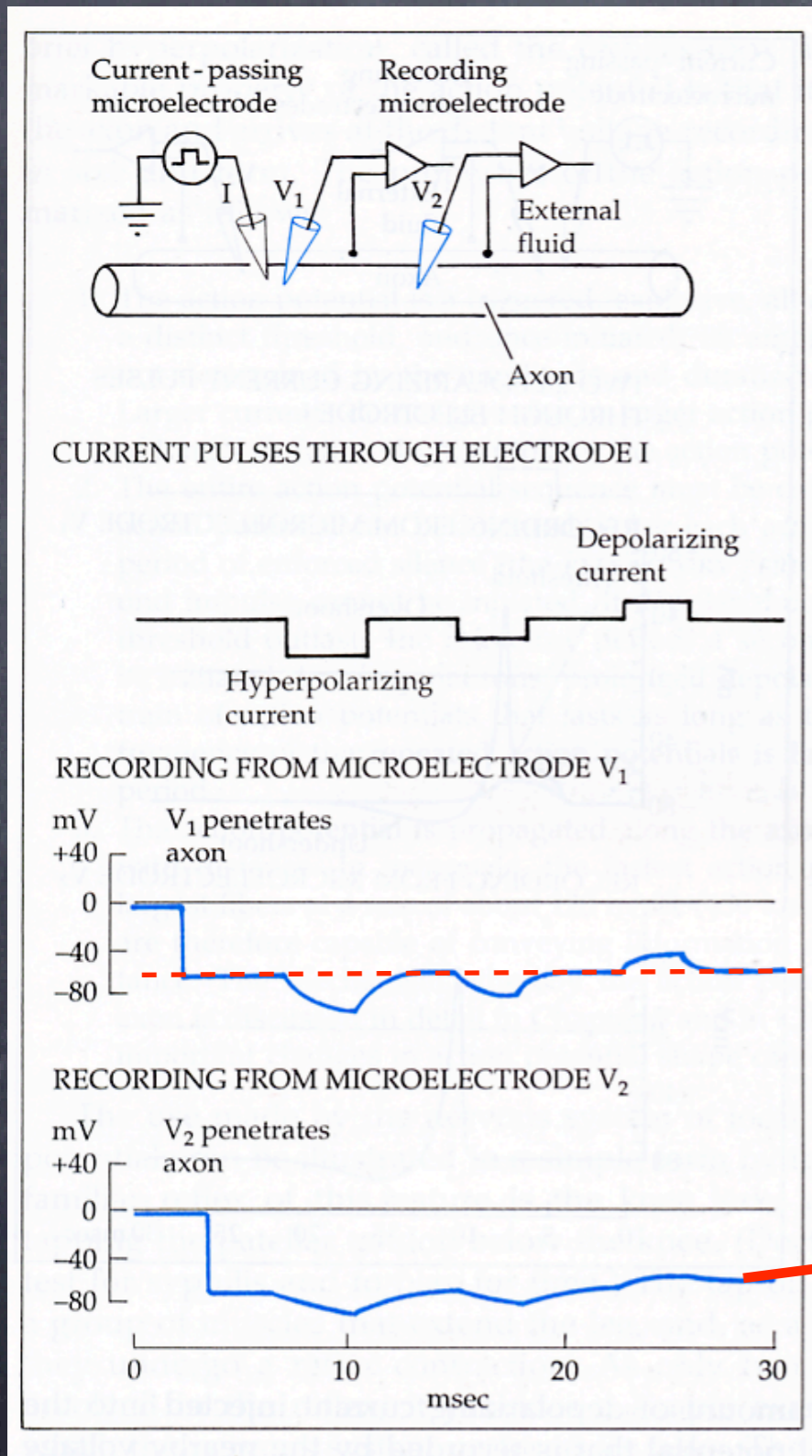


Local potentials are graded

resting potential

Almost no potential change is observed, why?

Current in axons and dendrites

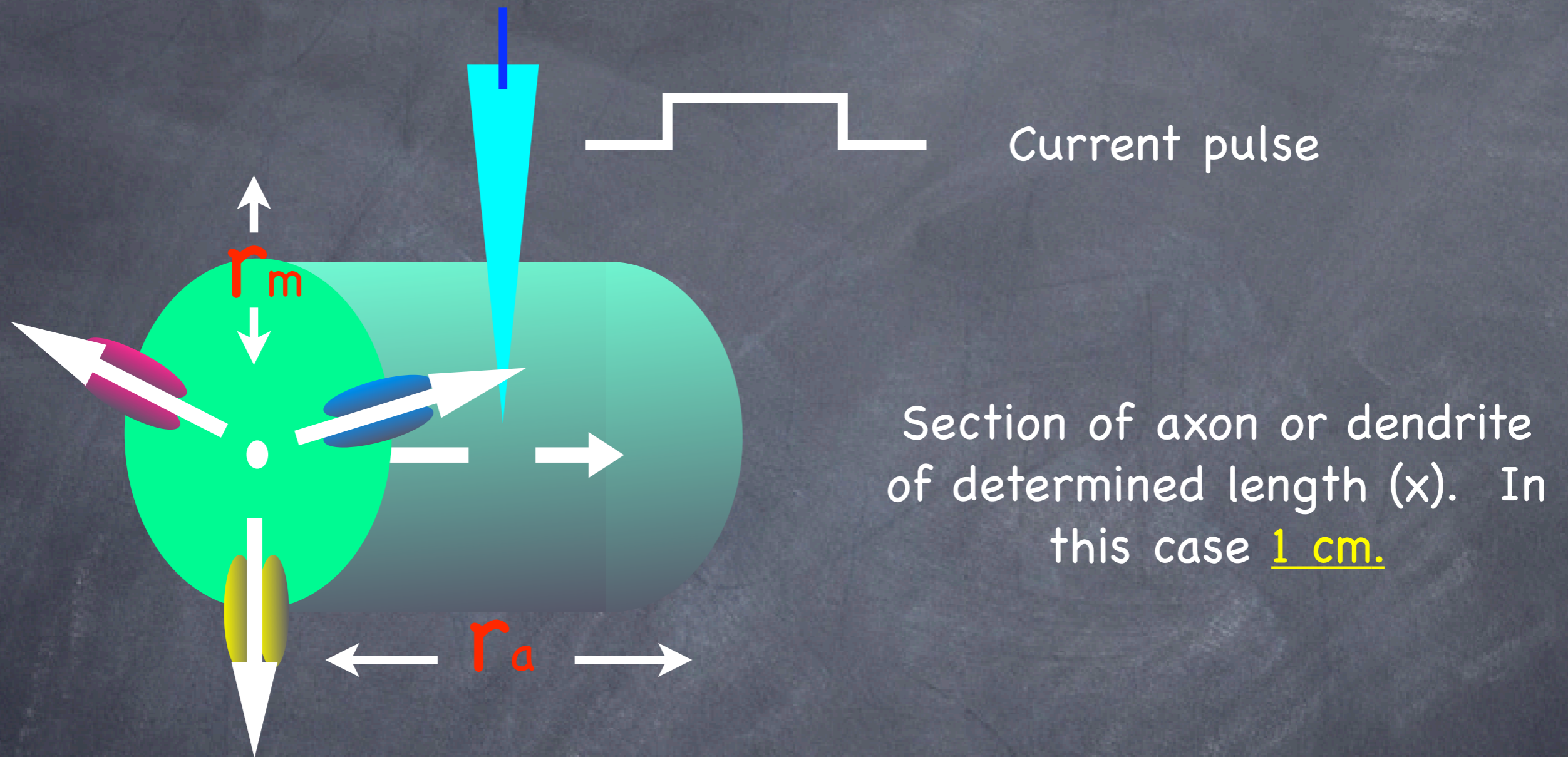

Section of axon or dendrite of determined length (x). In this case 1 cm.

r_a axial resistance (Ω/cm)

r_m membrane resistance ($\Omega \cdot \text{cm}$)

Axial resistance **increases** with distance (x)



r_{a1}

r_{a2}

r_{a3}

r_{a4}

Total axial resistance

$$r_x = r_a \cdot x \quad (x = 4)$$


(remember $R_T = R_1 + R_2$)

Near the site of injection, the current flows
 V_o through r_m (less resistance)



$$\text{Then } V_o = I_m \cdot r_m$$

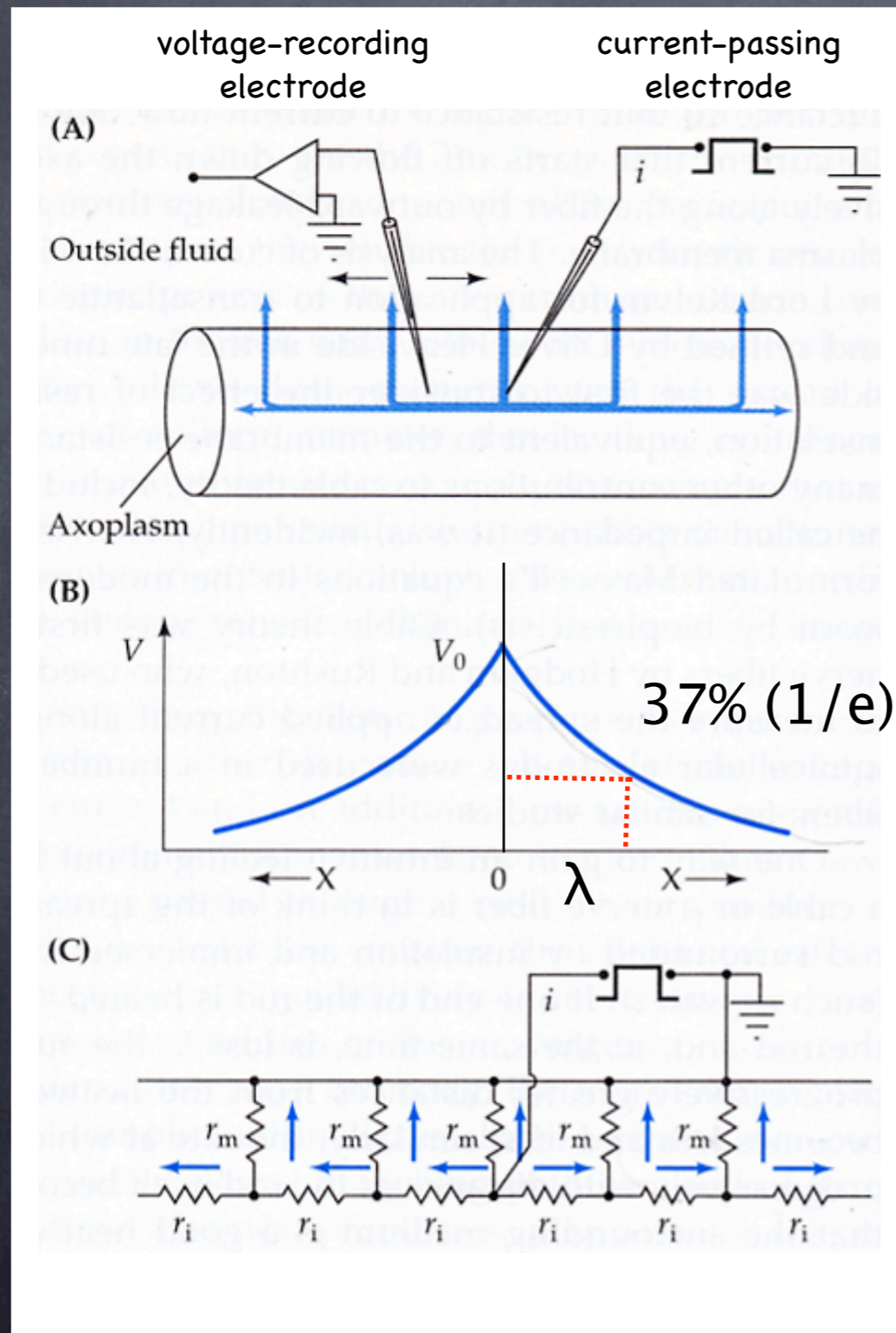What is the value of V at increasing distances from the site of current injection?



$$V = V_0 e^{-x/\lambda}$$

λ is the length constant

$$\lambda = \sqrt{r_m / r_a} \quad (\text{cm})$$


Increasing r_m increases λ

Decreasing r_a increases λ

i.e. V is closer to V_0


For 1 cm of cytoplasm (dendrites or axon)

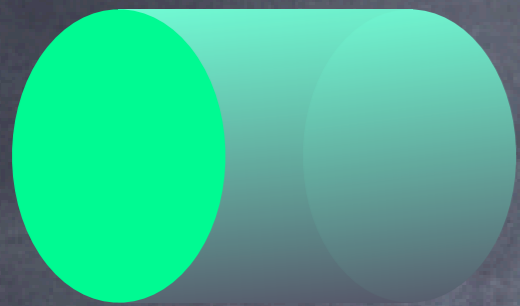ρ ($\Omega \cdot \text{cm}$) resistive property of 1 cm^3 of cytoplasm (dendrites or axon)



$$r_a = \rho / (\pi a^2)$$

← 1 cm ←

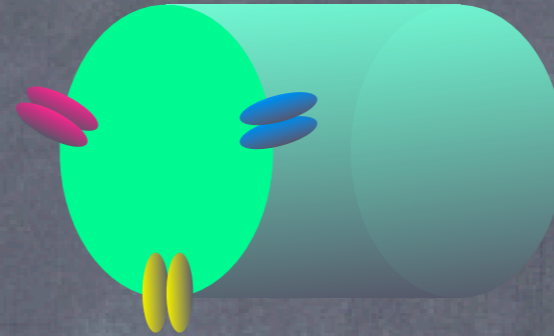

$$r_m = R_m / (2\pi a)$$

$$\lambda = \sqrt{r_m / r_a}$$

$$\lambda = \sqrt{\frac{R_m \rho a}{2\rho}}$$


If R_m and ρ are constant

$$\lambda = \sqrt{K a}$$

The length constant is proportional to the square root of the radius of the process


For neurons is usually 0.1 to 1 mm

Effect of length constant

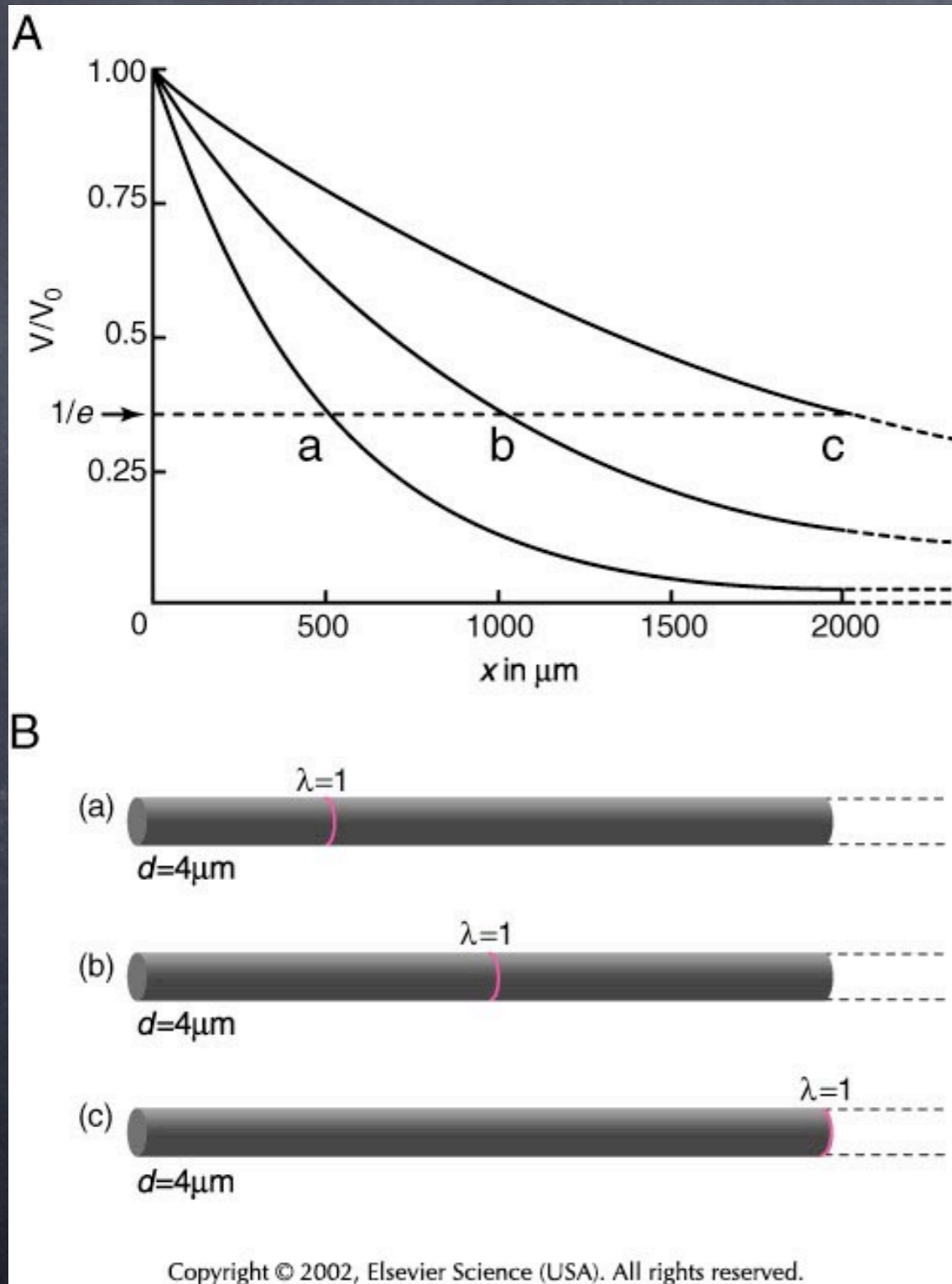



For a dendrite or axon with the same diameter as the length constant increases the potential decreases less with distance.

Effect of diameter

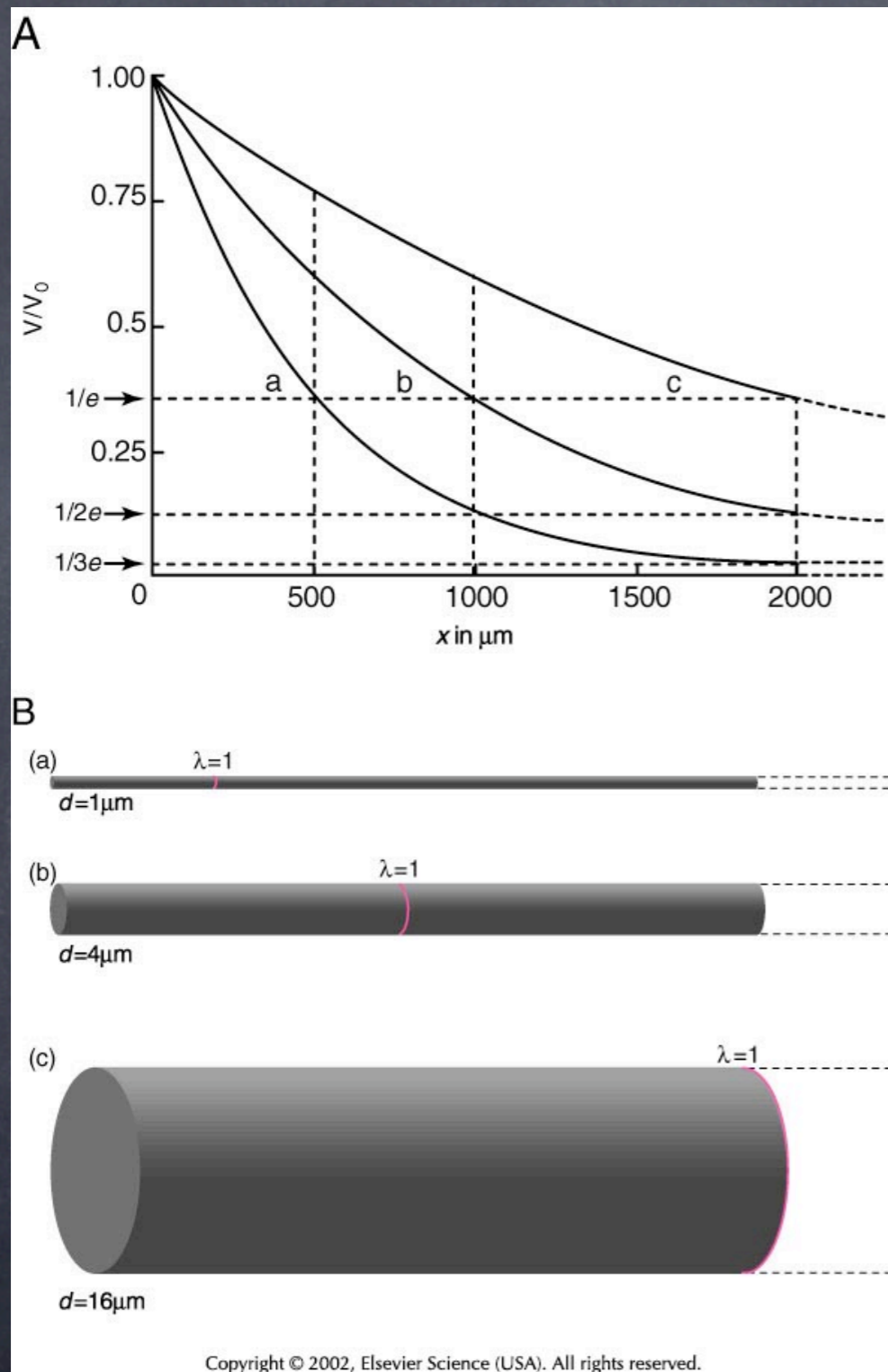

For a dendrite or axon with increasing diameters the length constant increases and the potential decreases less with distance.

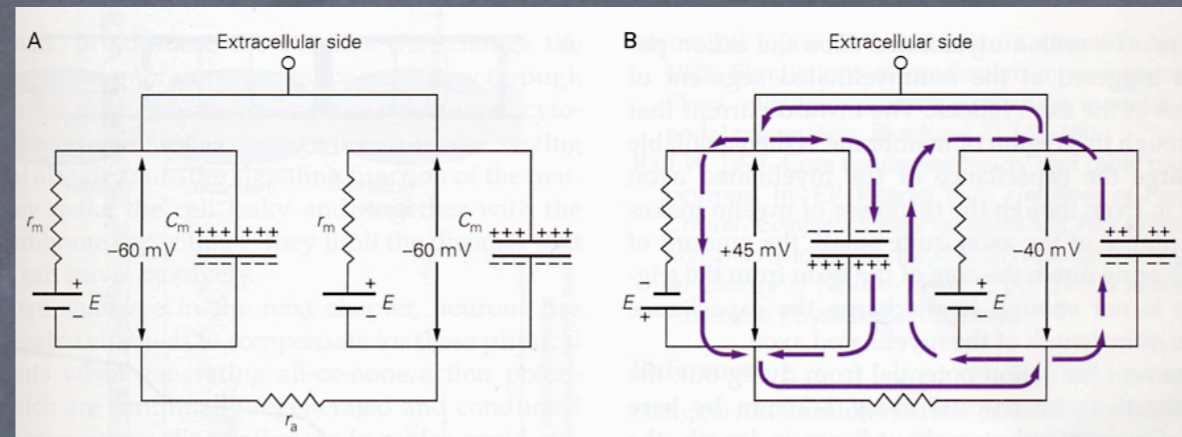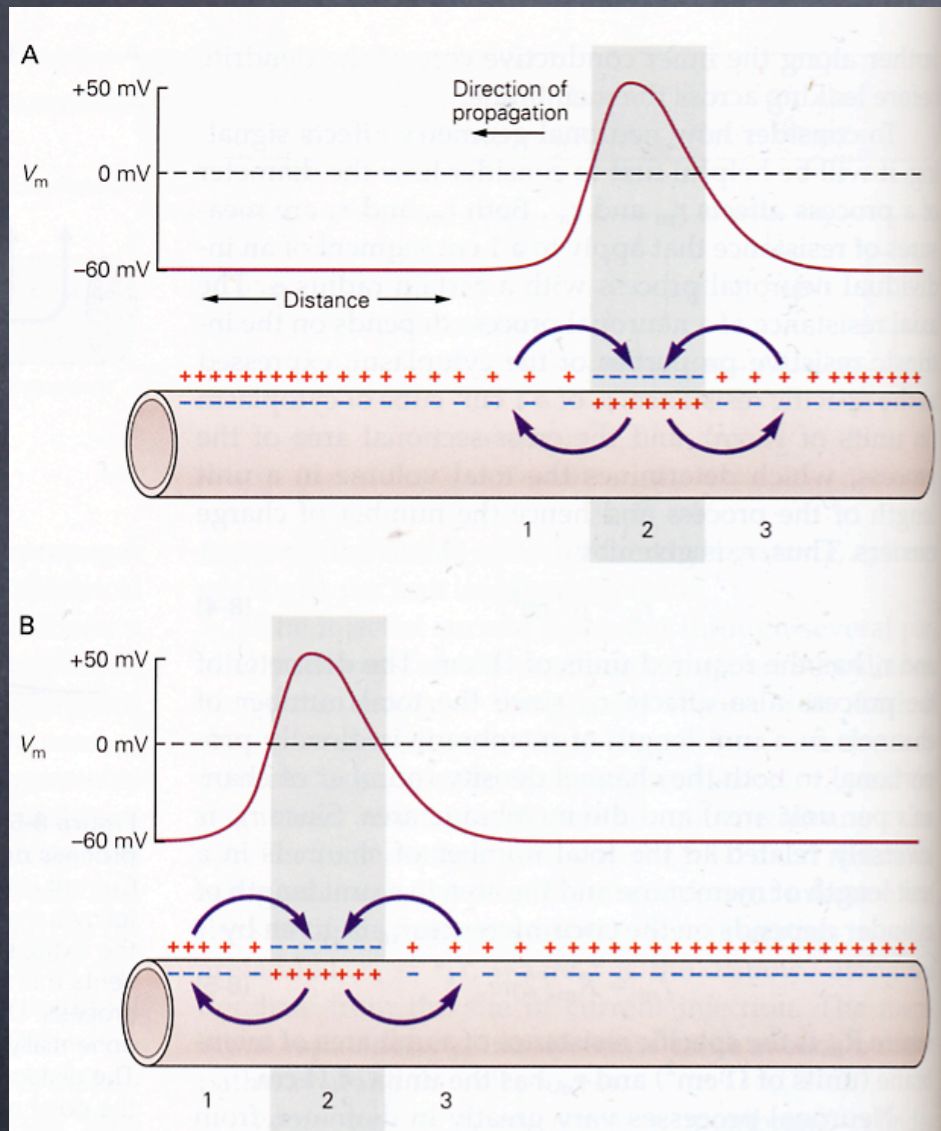The passive properties of membranes and axon diameter affect the speed of conduction of action potentials




speed of conduction of action potentials is inversely related to $r_a \square C_m$

speed of conduction is increased by increasing the diameter of the axon which decreases r_a

The giant axon of the squid 1 mm !

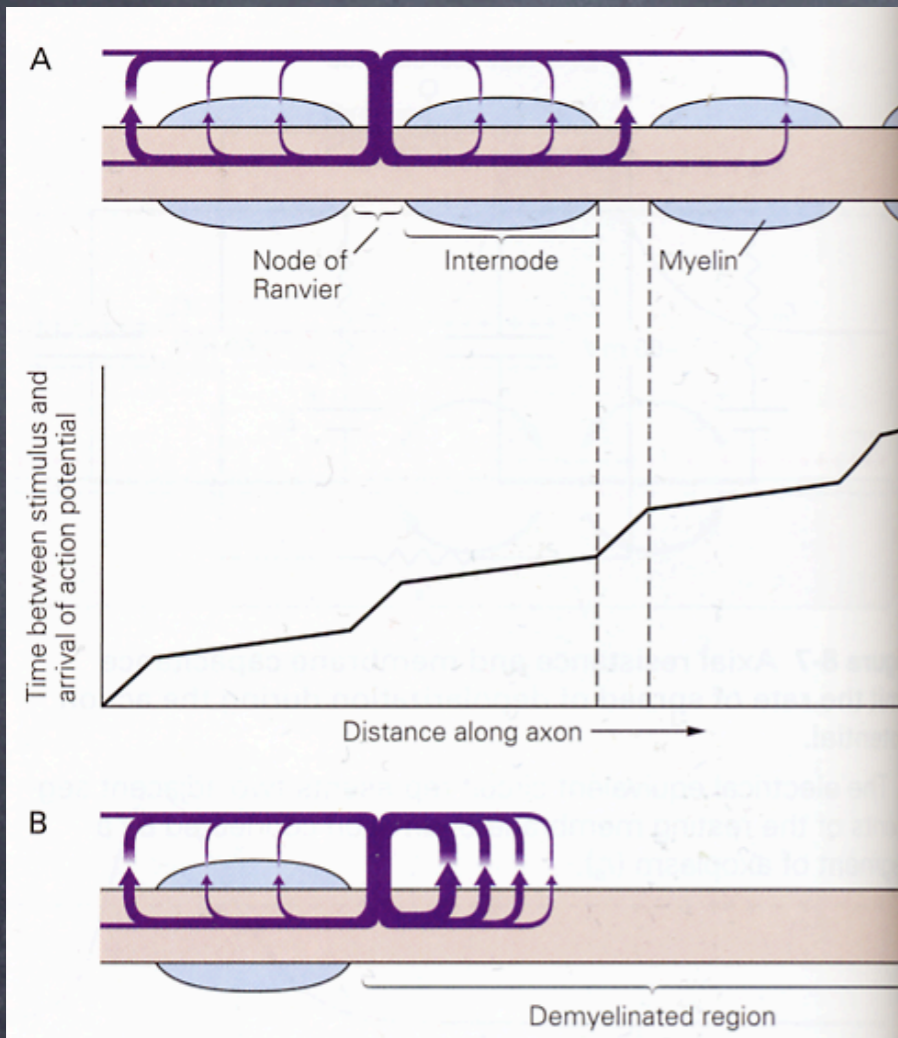Myelination, the alternative to increasing the diameter of the axon.



Glial cell wrap around axons many times (20-160 times) this like adding 320 membranes (in series).

This increases R_m and decreases C_m