



PAST EXAM PAPERS AND MEMOS
Get All Your Engineering Past Exam Papers With Answers

Website: www.previouspapers.co.za

Email: info@previouspapers.co.za

CELL: 073 770 3028

PAST EXAM PAPER & MEMO N2

ABOUT THE QUESTION PAPERS AND ONLINE INSTANT ACCESS:

THANK YOU FOR DOWNLOADING THE PAST EXAM PAPER AND ITS MEMO, WE HOPE IT WILL BE OF HELP TO YOU. SHOULD YOU NEED MORE QUESTION PAPERS AND THEIR MEMOS PLEASE SEND US AN EMAIL TO INFO@PREVIOUSPAPERS.CO.ZA AND WE WILL SEND YOU A FULL DOWNLOAD VERSION OF THESE THOUGH A FULL DOWNLOAD COMES AT A COST.

ALTERNATIVELY YOU CAN PURCHASE THEM ONLINE FROM OUR WEBSITE WWW.PREVIOUSPAPERS.CO.ZA TO AVOID DELAYS AND YOU FOLLOW ALL THE NEEDED STEPS TO GET INSTANT DOWNLOAD. **WITH ONLINE PAYMENT YOU CAN GET INSTANT DOWNLOADS OF YOUR PURCHASE.**

WE SELL PREVIOUS PAPERS AND MEMOS FOR THE SUBJECTS MENTIONED AND THE PAPERS ARE BETWEEN 2014-2019. THE PAPERS ARE IN PDF FORM AND EACH PDF HAS A MINIMUM OF SEVEN DIFFERENT PAPERS. THE YEARS FOR THE PAPERS YOU ARE PURCHASING ARE ALSO INCLUDED ON THE WEBSITE.

PRICE OF THE PAPERS AT A BIG DISCOUNT

Previous papers are very important in ensuring you pass your final exams. The actual value of the papers we are making you access is way more than R1 000 and we are making these very cheap as we have you in mind. For a small amount you can have these papers.

THE COST PER SUBJECT IS R300.



higher education & training

Department:
Higher Education and Training
REPUBLIC OF SOUTH AFRICA

**T700(E)(M31)T
APRIL EXAMINATION**

NATIONAL CERTIFICATE

INDUSTRIAL ELECTRONICS N2

(8080602)

**31 March 2016 (Y-Paper)
13:00–16:00**

This question paper consists of 7 pages and 1 formula sheet of 3 pages.

DEPARTMENT OF HIGHER EDUCATION AND TRAINING
REPUBLIC OF SOUTH AFRICA
NATIONAL CERTIFICATE
INDUSTRIAL ELECTRONICS N2
TIME: 3 HOURS
MARKS: 100

INSTRUCTIONS AND INFORMATION

1. Answer ALL the questions.
 2. Read ALL the questions carefully.
 3. Number the answers according to the numbering system used in this question paper.
 4. ALL the sketches and diagrams must be in pencil, large, clear and neat.
 5. ALL answers with decimals must be rounded off to the third decimal place after the comma.
 6. Write neatly and legibly.
-

QUESTION 1

Indicate whether the following statements are TRUE or FALSE. Choose the answer and write only 'true' or 'false' next to the question number (1.1–1.5) in the ANSWER BOOK.

- 1.1 Electrons that orbit the outermost shell of an atom are called valence electrons.
- 1.2 The hydrogen atom is an example of an atom that can exist on its own as a stable element.
- 1.3 Insulators are also called non-conductors or dielectrics.
- 1.4 Free electrons are those electrons that have left the outermost shell a parent atom.
- 1.5 The energy level of any electron is proportional to that electron's distance from the nucleus.

(5 x 1)

[5]**QUESTION 2**

Draw the IEC symbol of each of the following diodes:

- 2.1 P-N junction semiconductor diode
- 2.2 Zener diode
- 2.3 Varactor diode
- 2.4 Light-emitting diode

(4 x 1)

[4]

QUESTION 3

3.1 Study FIGURE 1 below and answer the questions.

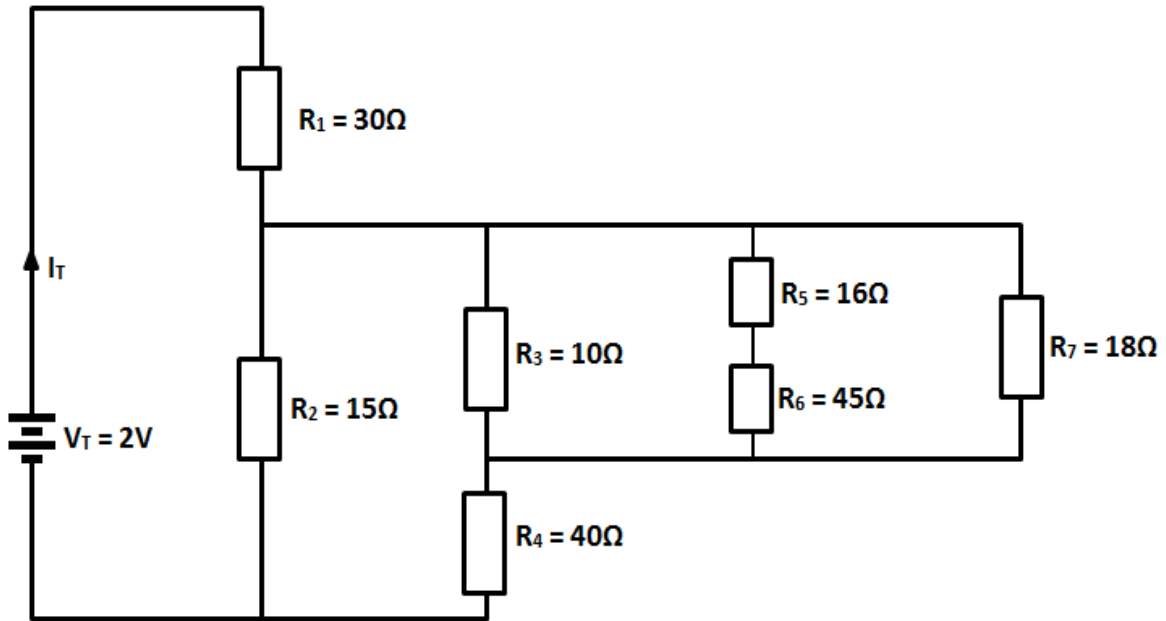


FIGURE 1

Calculate:

- 3.1.1 Total resistance R_T (11)
- 3.1.2 Total current I_T (2)
- 3.1.3 The power dissipated in R_1 (2)

3.2 Study FIGURE 2 below and then use KCL to calculate the unknown current I_T .

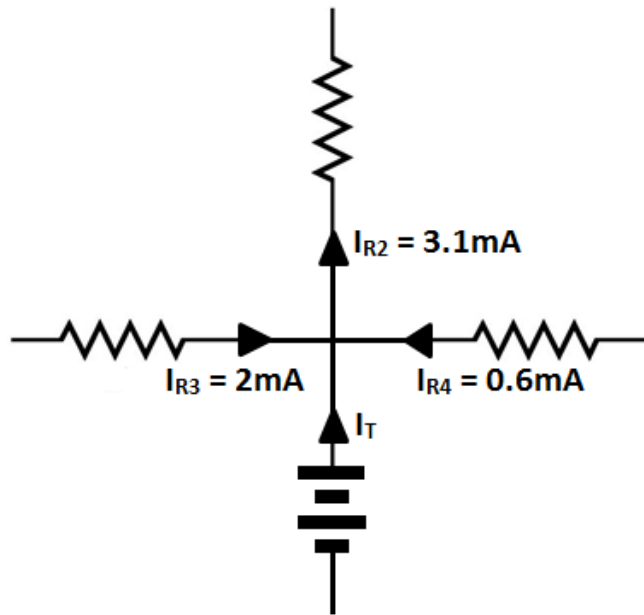


FIGURE 2

(5)
[20]

QUESTION 4

- 4.1 Give the value of the standard frequency supplied by power companies in South Africa as well as the standard voltage supplied for home use. (2)
- 4.2 Define the *form factor* and the *crest factor* of a waveform. (2)
- 4.3 Study FIGURE 3 below and answer the questions.

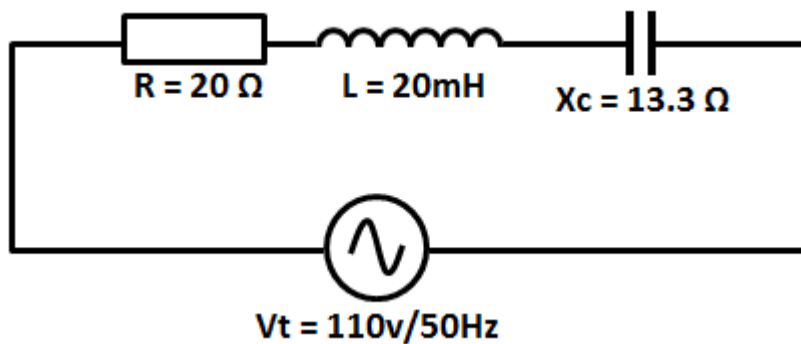


FIGURE 3

Calculate:

- 4.3.1 The value of the capacitor (3)
- 4.3.2 The inductive reactance (X_L) (2)
- 4.3.3 The total impedance (Z_T) (3)
- 4.3.4 The total current (I_T) (2)
- 4.3.5 The voltage drop across the resistor (V_R) (2)
- 4.3.6 The voltage drop across the inductor (2)
- 4.3.7 The phase angle (θ) (2)
- [20]**

QUESTION 5

- 5.1 A moving-coil measuring instrument with a resistance of 5Ω gives a full scale deflection of 10 milliamperes.

Calculate:

- 5.1.1 The value of the shunt resistance (R_{SH}) required in order to use the instrument as an ammeter for a 2 A current flow (5)
- 5.1.2 The series resistance (R_S) required to use the instrument as a voltmeter of up to 12 V (3)
- 5.2 Name the TWO methods/means through which the damping process can be facilitated. (2)
- [10]**

QUESTION 6

- 6.1 In terms of the doping process, differentiate between the anode terminal and the cathode terminal of a semiconductor diode. (4)
- 6.2 Make a neat, labelled circuit diagram of a full-wave bridge rectifier circuit. (6)
- [10]**

QUESTION 7

- 7.1 Make a neat, labelled circuit diagram of an NPN transistor amplifier that is connected in the common collector configuration mode. (5)
- 7.2 Name the output current of a common emitter transistor amplifier and then compare it to the base current of the same amplifier in terms of magnitude. (3)
- 7.3 Name the THREE classes of operation of transistor amplifiers. (3)
- [11]**

QUESTION 8

- 8.1 Describe the operating principle of a thermocouple, by drawing a neat, labelled circuit diagram. Insert a voltmeter in your sketch to indicate a voltage which depends upon the difference in the temperature of the two junctions of the thermocouple. (7)
- 8.2 Describe in detail the difference between negative temperature coefficient and positive temperature coefficient of materials in terms of the resistance of a material. (4)
- 8.3 State THREE advantages of a synchro system over a mechanical system. (3)
- [14]**

QUESTION 9

A 6,6 V input signal to a car audio system produces a current of 5,6 A in a subwoofer speaker system which has an impedance 7,6 Ω . The impedance on the input of the amplifier is 7,6 Ω .

Calculate:

- 9.1 The input power of the amplifier
- 9.2 The output power of the amplifier
- 9.3 The gain of the amplifier
- (3 x 2) **[6]**

TOTAL: 100

INDUSTRIAL ELECTRONICS N2**FORMULA SHEET****DC THEORY**

(i) $V = I \times R$

(ii) $R_T = R_1 + R_2$

(iii) $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$

(iv) $P = V \times I$

(v) $P = I^2 \times R$

(vi) $P = \frac{V^2}{R}$

AC THEORY

(i) $t = \frac{1}{f}$

(ii) $e = E_m \sin 2\pi ft$

(iii) $i = I_m \sin 2\pi ft$

(iv) $\theta = 2\pi ft$

(v) $I_{AVE} = \frac{I_1 + I_2 + I_3}{n}$

(vi) $I_{RMS} = \sqrt{\frac{I_1^2 + I_2^2 + I_3^2}{n}}$

(vii) $V_{AVE} = \frac{V_1 + V_2 + V_3}{n}$

(viii) $V_{RMS} = \sqrt{\frac{V_1^2 + V_2^2 + V_3^2}{n}}$

(ix) $V_{AVE} = V_M \times 0,637$

(x) $V_{RMS} = V_M \times 0,707$

(xi) Form factor = $\frac{RMS \text{ value}}{AVE \text{ value}}$

$$(xii) \quad \text{Crest factor} = \frac{\text{Maximum value}}{\text{RMS value}}$$

$$(xiii) \quad \omega = 2\pi f$$

$$(xiv) \quad X_C = \frac{1}{2\pi f C}$$

$$(xv) \quad X_L = 2\pi f L$$

$$(xvi) \quad V_T = \sqrt{V_R^2 + V_L^2}$$

$$(xvii) \quad V_T = \sqrt{V_R^2 + V_C^2}$$

$$(xviii) \quad V_T = \sqrt{V_R^2 + (V_L \approx V_C)^2}$$

$$(xix) \quad Z = \sqrt{R^2 + X_C^2}$$

$$(xx) \quad Z = \sqrt{R^2 + X_L^2}$$

$$(xxi) \quad Z = \sqrt{R^2 + (X_L \approx X_C)^2}$$

$$(xxii) \quad I_T = \frac{V_T}{Z}$$

$$(xxiii) \quad V_C = I_T \times X_C$$

$$(xxiv) \quad V_R = I_T \times R$$

$$(xxv) \quad V_L = I_T \times X_L$$

$$(xxvi) \quad \theta = \cos^{-1} \frac{R}{Z}$$

$$(xxvii) \quad f_0 = \frac{1}{2\pi\sqrt{LC}}$$

MEASURING INSTRUMENTS

$$(i) \quad R_{SH} = \frac{I_M \times R_M}{I_{SH}}$$

$$(ii) \quad R_S = \frac{V_T}{I_M} - R_M$$

TRANSISTORS

$$(iii) \quad I_e = I_c + I_b$$

DECIBEL RATIOS

$$(iv) \quad N = 10 \log \frac{P_0}{P_1}$$

$$(v) \quad N = 20 \log \frac{I_0}{I_1} + 10 \log \frac{R_0}{R_1}$$

$$(vi) \quad N = 20 \log \frac{V_0}{V_1} + 10 \log \frac{R_1}{R_0}$$

If/As $R_1 = R_0$

$$(vii) \quad \text{then } N = 20 \log \frac{I_0}{I_1}$$

$$(viii) \quad N = 20 \log \frac{V_0}{V_1}$$

(ix) **RESISTANCE**

$$R = \frac{p\ell}{a}$$

$$(x) \quad a = \frac{\pi d^2}{4}$$



higher education
& training

Department:
Higher Education and Training
REPUBLIC OF SOUTH AFRICA

MARKING GUIDELINE

NATIONAL CERTIFICATE

APRIL EXAMINATION

INDUSTRIAL ELECTRONICS N2

31 MARCH 2016

This marking guideline consists of 9 pages.


QUESTION 1

- 1.1 True
- 1.2 True
- 1.3 True
- 1.4 True
- 1.5 True

(5 x 1) [5]

QUESTION 2

2.1

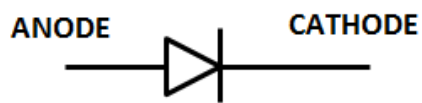


2.2



2.3



2.4

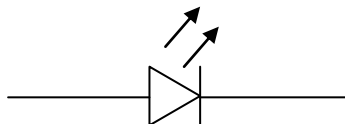

(4 x 1) [4]

QUESTION 3

- 3.1 3.1.1 (a) $R_{s1} = R_5 + R_6$
 $= 16 + 45$
 $= 61 \Omega \quad \checkmark$
- (b) $\frac{1}{R_{p1}} = \frac{1}{R_3} + \frac{1}{R_{s1}} + \frac{1}{R_7}$
 $= \frac{1}{10} + \frac{1}{61} + \frac{1}{18} \quad \checkmark$
 $= 0,172 \quad \checkmark$
 $= R_{p1} = 5,816 \Omega \quad \checkmark$
- (c) $R_{s2} = R_{p1} + R_4$
 $= 5,816 + 40 \quad \checkmark$
 $= 45,816 \Omega \quad \checkmark$
- (d) $R_{p2} = \frac{R_{s2} \times R_2}{R_{s2} + R_2}$
 $= \frac{45,816 \times 15}{45,816 + 15}$
 $= 11,3 \Omega \quad \checkmark \checkmark$
- (e) $R_T = R_1 + R_{p2}$
 $= 30 + 11,3 \quad \checkmark$
 $= 41,3 \Omega \quad \checkmark$ (11)
- 3.1.2 $I_T = V_T / R_T$
 $= 2 / 41,3 \quad \checkmark$
 $= 48,426 \text{ mA} \quad \checkmark$ (2)

$$\begin{aligned}
 3.1.3 \quad P &= I^2 \times R \\
 &= (48,426 \times 10^{-3})^2 \times 30 \quad \checkmark \\
 &= 0,07 \text{ W} \quad \checkmark
 \end{aligned}$$

(2)

$$\begin{aligned}
 3.2 \quad I_1 + I_{R3} + I_{R4} &= I_{R2} \checkmark \\
 I_1 &= I_{R2} - (I_{R3} + I_{R4}) \checkmark \\
 &= 3,1 \times 10^{-3} - (2 \times 10^{-3} + 0,6 \times 10^{-3}) \checkmark \\
 &= 3,1 \times 10^{-3} - (2,6 \times 10^{-3}) \checkmark \\
 &= 0,5 \text{ mA} \checkmark
 \end{aligned}$$

(5)
[20]

QUESTION 4

$$\begin{aligned}
 4.1 \quad \text{Frequency} &= 50 \text{ Hz} \checkmark \\
 \text{Voltage} &= 220 \text{ V} - 240 \text{ V} \checkmark \quad (220\text{V is acceptable})
 \end{aligned}$$

(2)

4.2 The form factor of a wave refers to ratio of the RMS value relative to the average of the wave while the crest factor refers to ratio of the maximum value to the RMS value of the wave. $\checkmark\checkmark$

(2)

$$\begin{aligned}
 4.3 \quad 4.3.1 \quad X_c &= \frac{1}{2\pi fC} \\
 C &= \frac{1}{2\pi fX_c} \quad \checkmark \\
 C &= \frac{1}{2\pi \times 50 \times 13,3} \quad \checkmark \\
 C &= 239,33 \times 10^{-6} \text{ F} \quad \checkmark
 \end{aligned}$$

(3)

$$\begin{aligned}
 4.3.2 \quad X_L &= 2\pi fL \\
 &= 2\pi(50)(20 \times 10^{-3}) \quad \checkmark \\
 &= 6,283 \Omega \quad \checkmark
 \end{aligned}$$

(2)

$$\begin{aligned} 4.3.3 \quad Z_T &= \sqrt{R^2 + (X_L - X_C)^2} \quad \checkmark \\ &= \sqrt{20^2 + (13,3 - 6,283)^2} \quad \checkmark \\ &= 21,195 \Omega \quad \checkmark \end{aligned} \quad (3)$$

$$\begin{aligned} 4.3.4 \quad I_T &= \frac{V_T}{Z_T} \\ &= \frac{110}{21,195} \quad \checkmark \\ &= 5,189 \text{ A} \quad \checkmark \end{aligned} \quad (2)$$

$$\begin{aligned} 4.3.5 \quad V_R &= I_T R \\ &= 5,189 \times 20 \quad \checkmark \\ &= 103,780 \text{ V} \quad \checkmark \end{aligned} \quad (2)$$

$$\begin{aligned} 4.3.6 \quad V_L &= I_T \times X_L \\ &= 5,189 \times 6,283 \quad \checkmark \\ &= 32,602 \text{ V} \quad \checkmark \end{aligned} \quad (2)$$

$$\begin{aligned} 4.3.7 \quad \theta &= \cos^{-1} \frac{R}{Z} \\ &= \cos^{-1} \frac{20}{21,195} \quad \checkmark \\ &= 19,333^\circ \quad \checkmark \end{aligned} \quad (2)$$

[20]

QUESTION 5

5.1 5.1.1 Using an instrument as an ammeter

$$I_{SH} = I_T - I_M \quad \checkmark$$

$$= 2 - 10 \times 10^{-3} \quad \checkmark$$

$$= 1,99 \text{ A} \quad \checkmark$$

Then

$$R_{SH} = \frac{I_M \times R_M}{I_{SH}}$$

$$= \frac{10 \times 10^{-3} \times 5}{1,99} \quad \checkmark$$

$$= 25 \times 10^{-3} \Omega \quad \checkmark$$

(5)

5.1.2 Using an instrument as a voltmeter

$$I_M = I_{SH}$$

$$R_S = \frac{V_T}{I_M} - R_M \quad \checkmark$$

$$= \frac{12}{10 \times 10^{-3}} - 5 \quad \checkmark$$

$$= 1,195 \text{ k}\Omega \quad \checkmark$$

(3)


- 5.2
- Electromagnetic damping
 - Mechanical damping

(2)

[10]


QUESTION 6

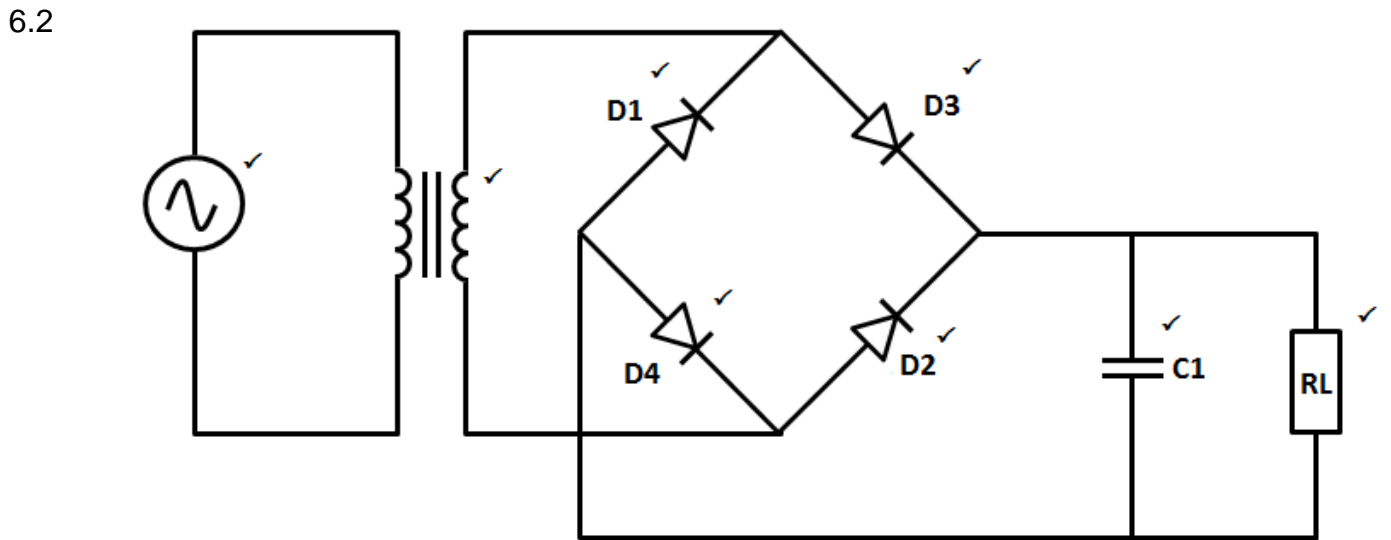- 6.1
- The anode terminal is heavily doped with P-type material, wherein trivalent impurity atoms are added to pure intrinsic semiconductor material.
 - The cathode terminal is heavily doped with N-type material, wherein pentavalent impurity atoms are added to pure intrinsic semiconductor material.
- (2 x 2) (4)




(one full mark per diode, half marks for the other components) (6) [10]

QUESTION 7

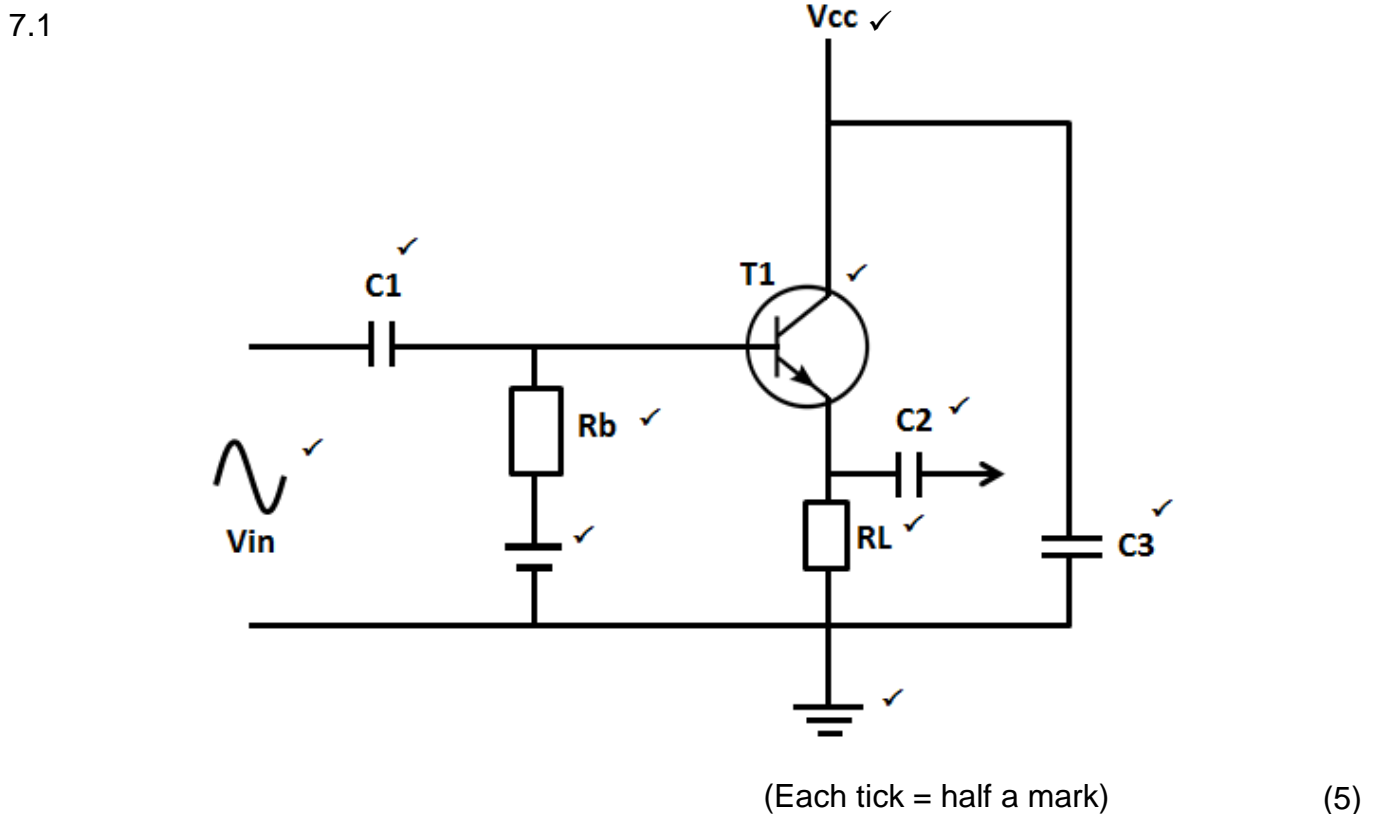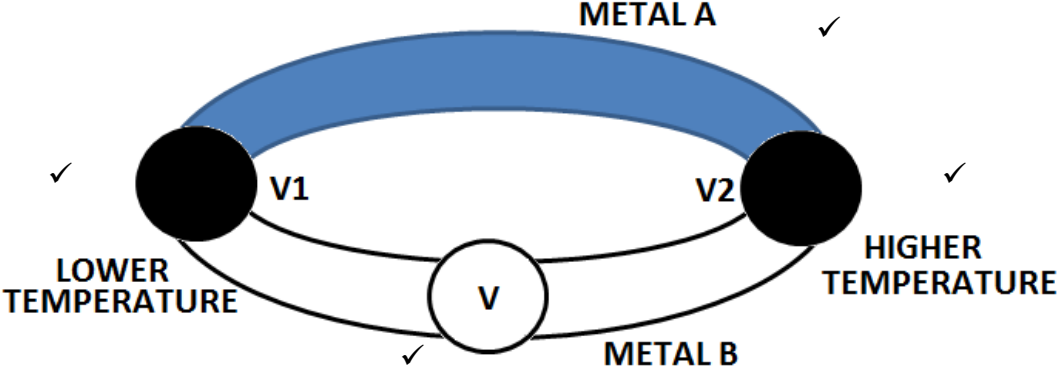

- 7.2
- Collector current ✓
 - In terms of magnitude, the collector current of a common emitter transistor amplifier configuration is much larger in value than the corresponding base current, such that the base current is in the order of micro-amperes while the collector current is in the order of milliamperes. ✓✓ (3)
- 7.3
- Class A
 - Class B
 - Class C (3)
- [11]

QUESTION 8

- 8.1
- 
- When a temperature difference exists between the hot and cold junctions, a potential difference is produced ($V_2 - V_1$) ✓, causing a current flow ✓
 - When the meter is connected as shown, the meter reading will be proportional to the difference in temperature between the hot and cold junctions ✓ (7)
- 8.2
- Positive temperature coefficient – The resistance of a material increases with an increase in temperature.
 - Negative temperature coefficient – The resistance of a material decreases with an increase in temperature. (2 x 2) (4)
- 8.3
- The controlling shaft and the controlled shaft can be very far apart. ✓
 - Contact between the systems can be through wires, radio or telemetering. ✓
 - A synchro system uses very little electrical energy compared to the energy used by a mechanical system. ✓ (3)
- [14]

QUESTION 9

9.1
$$P_{IN} = \frac{V_{IN}^2}{R_{IN}}$$
$$= \frac{(6,6)^2}{7,6} \quad \checkmark$$
$$= 5,732 \text{ W} \quad \checkmark$$

9.2
$$P_{OUT} = I_{OUT}^2 \times R_{OUT}$$
$$= (5,6)^2 \times 7,6 \quad \checkmark$$
$$= 238,336 \text{ W} \quad \checkmark$$

9.3
$$N = 10 \text{Log} \frac{P_{OUT}}{P_{IN}}$$
$$= 10 \text{Log} \frac{238,336}{5,732} \quad \checkmark$$
$$= 16,189 \text{ dB} \quad \checkmark$$

(3 x 2) [6]

TOTAL: 100



PAST EXAM PAPERS AND MEMOS
Get All Your Engineering Past Exam Papers With Answers

Website: www.previouspapers.co.za

Email: info@previouspapers.co.za

CELL: 073 770 3028

THANK YOU FOR
DOWNLOADING
PAST EXAM PAPER &
MEMO FOR N2

IF YOU NEED MORE PAPERS WE SELL THEM FOR R300

VISIT OUR WEBSITE AT WWW.PREVIOUSPAPERS.CO.ZA

OR SEND US AN EMAIL AT INFO@PREVIOUSPAPERS.CO.ZA AND

WE WILL GLADLY HELP YOU.