
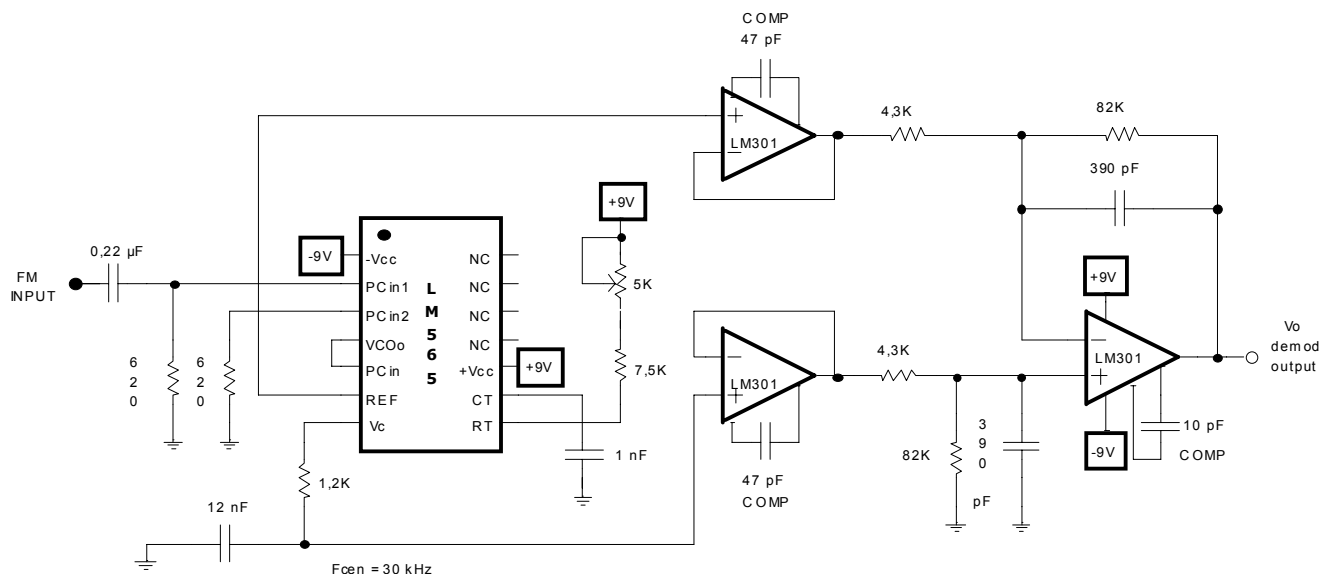


No.1 FM demodulator Analysis

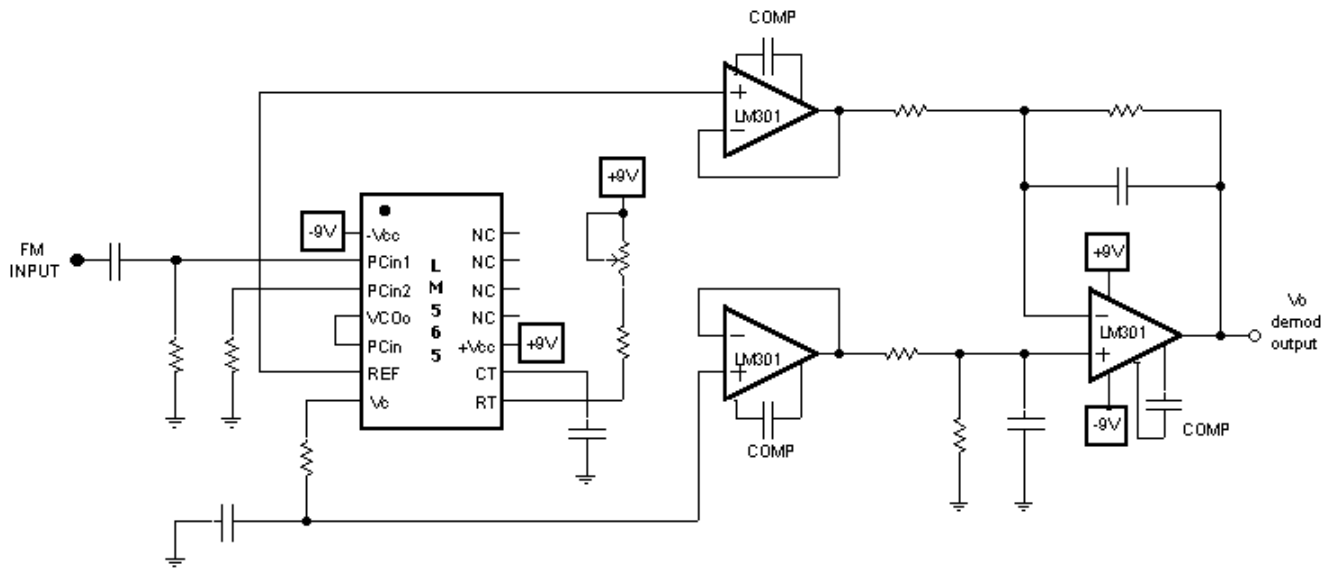

- A) Draw a block diagram of the overall FM demodulator and derive its TF $\Delta V_o(s)/\Delta \omega_{in}(s)$
- B) Determine K_d , K_v , F_{n1} , ζ_1 and F_{n2} of the PLL demodulator and then sketch its gain response - label with relevant parameters. Explain why the demodulator has a Butterworth response.
- C) If $F_{car} = 30$ kHz, $\Delta F = 2$ kHz and $F_{mod} = 500$ Hz, sinewave modulation, what is the minimum, maximum and average phase error and the demodulated voltage? Use pages 10 or 11 of theory notes to read peak phase error.
- D) Repeat for $F_{mod} = 5$ kHz.
- E) Derive the general TF for $\Delta \Phi_e(s)/\Delta \omega_{in}(s)$ and then calculate the exact values of the phase error for steps C and D.
- F) For what modulation frequency is the phase error maximum?
- G) Explain the function of the last stage.
- H) What is amplitude of the demodulated O/P signal, the HF ripple at the final output and the % ripple if the FM input has $F_{mod} = 500$ Hz, $\Delta F = 2$ kHz at $F_{car} = 30$ kHz.
- I) Simulate the demodulator gain response and the phase error response to an FM input with sinewave modulation.
- J) Simulate for determination of lock range and capture range.
- K) Simulate for determination of output HF ripple.

No.2 FM demodulator Design




Design a 3rd order FM demodulator that has a low-pass Bessel response, given the following input signal.

FM input: $F_{car} = 100 \text{ kHz}$ $\Delta F = 0 \text{ to } 10 \text{ kHz}$ Modulation: sinewave, $F_{mod} = 0 \text{ to } 3 \text{ kHz}$

Final output: $0 \text{ to } 5V_p$

Select F_n of PLL for a reasonable phase error and large enough to pass the demod signal.

No.3 FSK demodulator Design

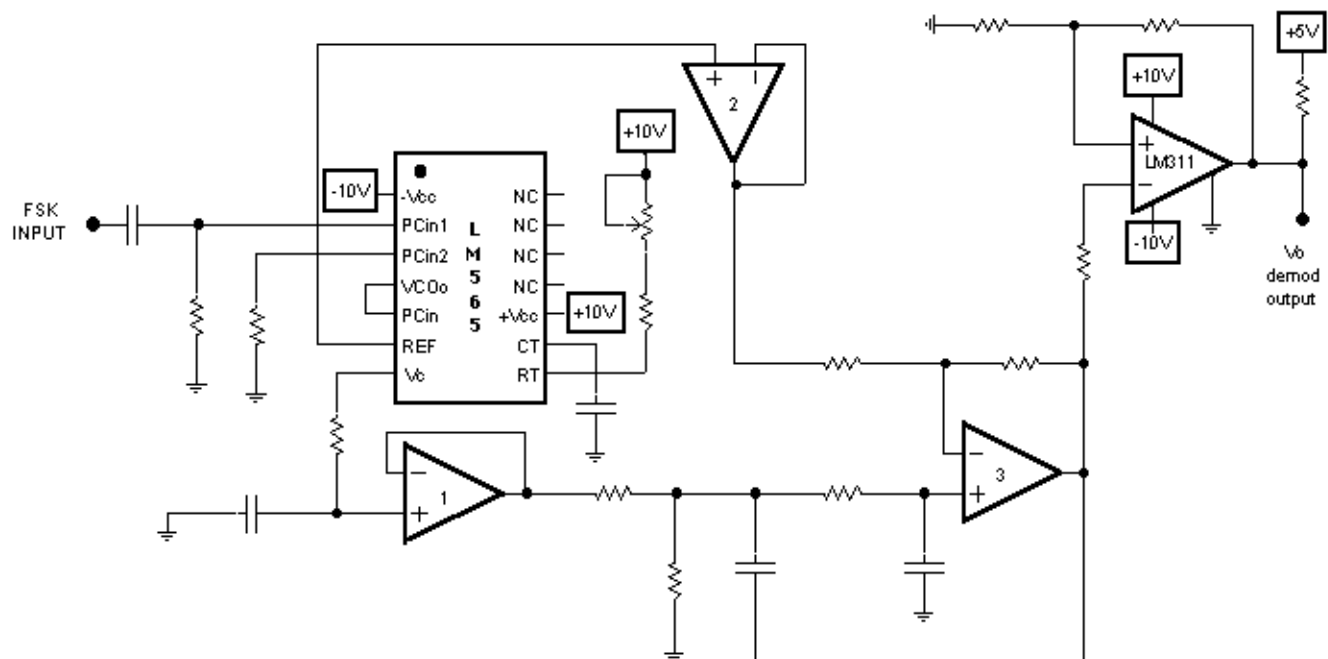


Design a 4th order FSK demodulator that has a Bessel low-pass response with a bandwidth of 15 kHz .

The two input frequencies are 100 kHz and 110 kHz .

What is the maximum bit rate that can be demodulated?

No.4 PLL Frequency Synthesiser Analysis

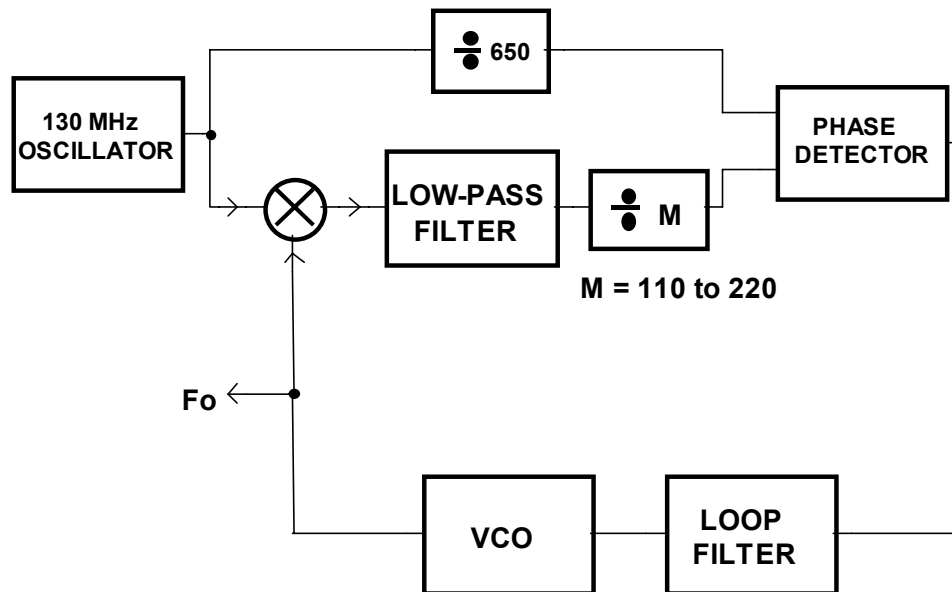

- A) Determine the two possible sets of output frequencies.
- B) How do we ensure operation of the synthesiser on one set of frequencies only?
- C) Why is there spurious FM sidetones in the spectrum of the output signal? Is this good or bad? How can they be minimized?
- D) Are ζ and ω_n constant in this system? Explain.

No.5 RF PLL Synthesizer Design and Analysis


Re-do the example on pages 33 to 40 with the following data:

Using the same frequencies, re-design for a phase margin of 55° , an ω_p value of $2\pi \cdot 10$ kHz and additional spurious sideband attenuation of 20 dB from the R_3C_3 section added to the loop filter.

Modify the SystemView file given for the theory example to simulate your new design.

SOLUTIONS

No.1A)

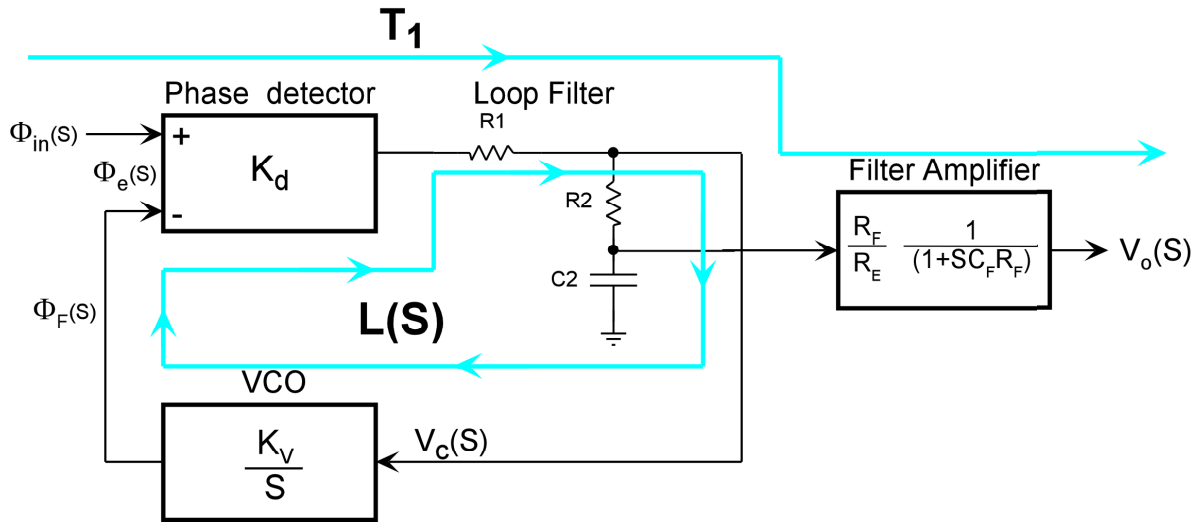

$$\frac{V_o(s)}{\Phi_{in}(s)} = \frac{T_1 N_1}{1 - L(s)} = \frac{K_d \times \frac{1}{SC_2} \times \left(\frac{R_F}{R_E} \times \frac{1}{1 + SC_F R_F} \right)}{1 - \left[-K_d \times \frac{R_2 + \frac{1}{SC_2}}{R_1 + R_2 + \frac{1}{SC_2}} \times \frac{K_V}{S} \right]}$$

$$\frac{V_o(s)}{\Phi_{in}(s)} = \frac{T_1 N_1}{1 - L(s)} = \frac{K_d \times \frac{1}{1 + SC_2(R_1 + R_2)} \times \left(\frac{R_F}{R_E} \times \frac{1}{1 + SC_F R_F} \right)}{1 + \left[K_d \times K_V \times \frac{1 + SC_2 R_2}{1 + SC_2(R_1 + R_2)} \times \frac{1}{S} \right]}$$

$$\frac{V_o(s)}{\omega_m(s)} = \frac{\frac{S K_d}{C_2(R_1 + R_2)}}{\left(S^2 + S \left(\frac{1 + K_d K_V R_2 C_2}{C_2(R_1 + R_2)} \right) + \frac{K_d K_V}{C_2(R_1 + R_2)} \right)} \times \left(\frac{R_F}{R_E} \times \frac{1}{1 + SC_F R_F} \right)$$

$$\frac{\Delta V_o(s)}{\Delta \omega_{in}(s)} = \frac{\frac{K_d}{C_2(R_1 + R_2)}}{\left(S^2 + S \left(\frac{1 + K_d K_V R_2 C_2}{C_2(R_1 + R_2)} \right) + \frac{K_d K_V}{C_2(R_1 + R_2)} \right)} \times \left(\frac{R_F}{R_E} \times \frac{1}{1 + SC_F R_F} \right)$$


B) $K_d = 0.68 \text{ V/r}$ if $V_{in} > 100 \text{ mV}_{pp}$, that is if LM565 phase detector O/P is saturated - see data sheets.

$$K_v = 49.4 F_{\text{cen}}/\Delta V_{\text{cc}} = 49.4 \cdot 30\text{K}/18 = 82333 \text{ r/s or } 13.1 \text{ kHz/V.}$$

$$F_{n1} = \frac{1}{2\pi} \sqrt{\frac{K_v K_d}{C_2(R_1 + R_2)}} = \frac{1}{2\pi} \sqrt{\frac{82333 \cdot 0.68}{12n \cdot (3.6k + 1.2k)}} = 4962 \text{ Hz} \quad \zeta_1 = \frac{1 + K_d K C_2 R_2}{2\omega_{n1} C_2 (R_1 + R_2)} = 0.5029$$

$$F_{n2} = (2\pi R C_F)^{-1} = 4977 \text{ Hz}$$

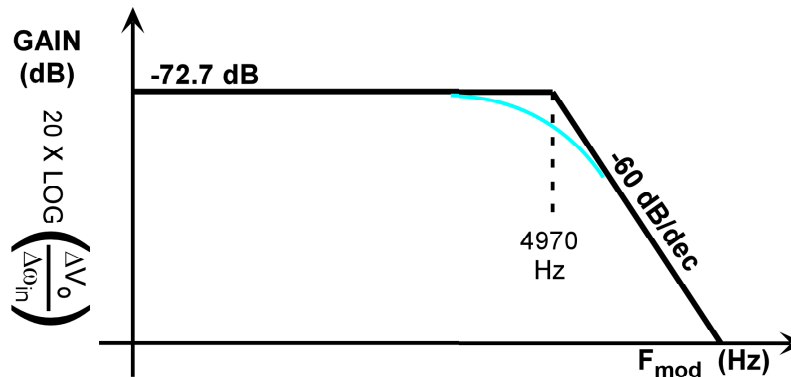F_{n1} and F_{n2} are almost equal and $\zeta_1 \approx 0.5$ which corresponds to a third order Butterworth response whose normalised poles are $\bar{S}_1 = 1 / 180^\circ$ and $\bar{S}_{2,3} = 1 / \pm 120^\circ$. $\frac{\Delta V_o(s)}{\Delta \omega_{in}(s)} = \frac{1}{K_v} \times \frac{R_F}{R_E} = 231.6 \mu$




C) $\Delta F = 2 \text{ kHz}$, $F_{\text{mod}} = 500 \text{ Hz}$, $F_{\text{car}} = 30 \text{ kHz}$

$$\omega_{n1}(\tau_1 + \tau_2) = 2\pi \times 4962 (12n \times (3.6k + 1.2k)) = 1.8 \quad \text{and} \quad \frac{F_{\text{mod}}}{F_{n1}} = \frac{500}{4962} = 0.10076$$

For all phase error graphs, the LF frequency value of $\frac{\Delta \Phi_e}{(\Delta F_{in}/F_{n1})} \approx \frac{1}{\omega_{n1}(\tau_1 + \tau_2)} = \frac{1}{1.8}$, therefore we have
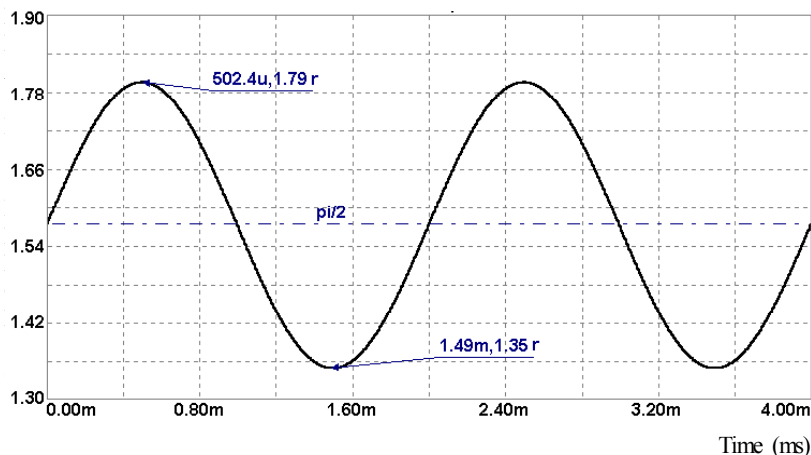
$$\Delta \Phi_e(\text{peak}) \approx \frac{(\Delta F_{in}/F_{n1})}{1.8} = \frac{2000/4962}{1.8} = 0.224 \text{ } r_p \quad \text{Average phase error is } \pi/2 \text{ if } F_{\text{cen}} = F_{\text{car}} \text{ for LM565}$$



D) $\Delta F = 2 \text{ kHz}$, $F_{\text{mod}} = 5 \text{ kHz}$, $F_{\text{car}} = 30 \text{ kHz}$

$$\omega_{n1}(\tau_1 + \tau_2) = 2\pi \times 4962 (12n \times (3.6k + 1.2k)) = 1.8 \quad \text{and} \quad \frac{F_{\text{mod}}}{F_{n1}} = \frac{5000}{4962} = 1.0077$$

At $\frac{F_{\text{mod}}}{F_{n1}} = 1$, we read on the phase error graphs (pp 10-11)



$$\frac{\Delta\Phi_e(\text{peak})}{(\Delta F_{\text{in}}/F_{n1})} \approx 1.5 \quad \text{for} \quad \omega_{n1}(\tau_1 + \tau_2) = 1$$

$$\frac{\Delta\Phi_e(\text{peak})}{(\Delta F_{\text{in}}/F_{n1})} \approx 1.0 \quad \text{for} \quad \omega_{n1}(\tau_1 + \tau_2) = 5$$


Using linear interpolation, we have

$$\Delta\Phi_e(\text{peak}) \approx \frac{(\Delta F_{\text{in}}/F_{n1})}{1.4} = \frac{2000/4962}{1.4} = 0.288 r_p$$

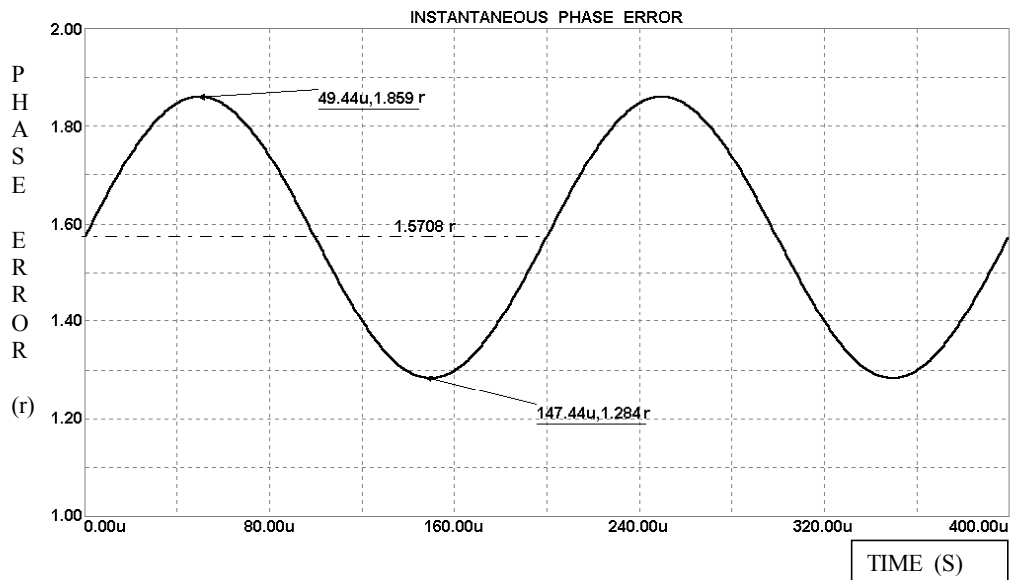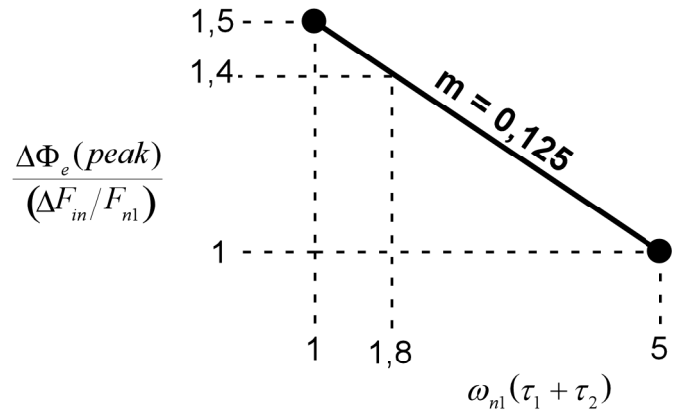Average phase error is $\pi/2$ if $F_{\text{cen}} = F_{\text{car}}$ for LM565



E)

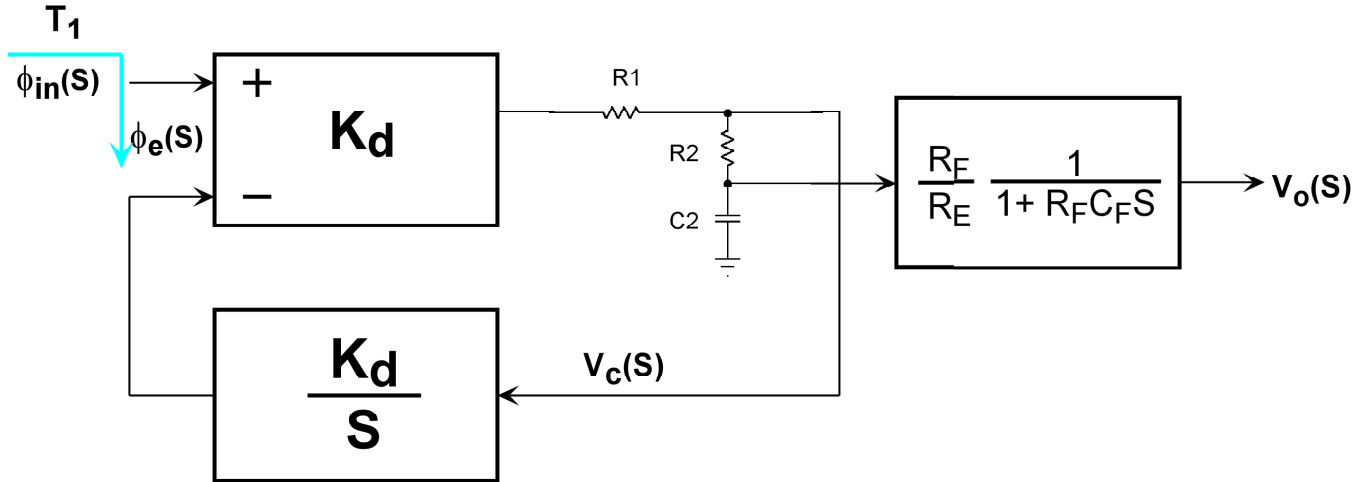

$$\frac{\Phi_e(s)}{\Phi_{in}(s)} = \frac{T_1 N_1}{1 - L(s)} = \frac{1 \times 1}{1 - \left[-K_d \times \frac{R_2 + \frac{1}{SC_2}}{R_1 + R_2 + \frac{1}{SC_2}} \times \frac{K_v}{s} \right]} = \frac{1}{1 + \left[K_d \times K_v \times \frac{1 + SC_2 R_2}{1 + SC_2 (R_1 + R_2)} \times \frac{1}{s} \right]}$$

$$\frac{\Phi_e(s)}{\omega_m(s)} = \frac{\frac{S(1 + SC_2(R_1 + R_2))}{C_2(R_1 + R_2)}}{\left(S^2 + S \left(\frac{1 + K_d K_v R_2 C_2}{C_2(R_1 + R_2)} \right) + \frac{K_d K_v}{C_2(R_1 + R_2)} \right)}$$

$$\frac{\Delta \Phi_e(s)}{\Delta \omega_{in}(s)} = \frac{\left(S + \frac{1}{C_2(R_1 + R_2)} \right)}{\left(S^2 + S \left(\frac{1 + K_d K_v R_2 C_2}{C_2(R_1 + R_2)} \right) + \frac{K_d K_v}{C_2(R_1 + R_2)} \right)}$$

$$\Delta \Phi_e(s) = \Delta \omega_{in}(s) \times \frac{\left(S + \frac{1}{C_2(R_1 + R_2)} \right)}{\left(S^2 + S \left(\frac{1 + K_d K_v R_2 C_2}{C_2(R_1 + R_2)} \right) + \frac{K_d K_v}{C_2(R_1 + R_2)} \right)}$$

$$\Delta \Phi_e(j\omega_m) = \Delta \omega_{in}(j\omega_m) \times \frac{\left(j\omega_m + \frac{1}{C_2(R_1 + R_2)} \right)}{\left((j\omega_m)^2 + \frac{K_d K_v}{C_2(R_1 + R_2)} + j\omega_m \left(\frac{1 + K_d K_v R_2 C_2}{C_2(R_1 + R_2)} \right) \right)}$$

$$\Delta \Phi_e(j\omega_m) = \Delta \omega_{in}(j\omega_m) \times \frac{(j\omega_m + 17361)}{((j\omega_m)^2 + 972 \times 10^6 + j\omega_m(31357.8))}$$

$$\Delta \Phi_e(peak) = \Delta \omega_{in}(peak) \times \frac{(j\omega_m + 17361)}{((972 \times 10^6 - \omega_m^2) + j\omega_m 31357.8)}$$

For $F_m = 500$ Hz we have

$$\Delta\Phi_e(\text{peak}) = 2\pi \times 2000 \times \frac{(j1000\pi + 17361)}{((972 \times 10^6 - (1000\pi)^2) + j1000\pi \times 31357.8)} = 0,2258 r / 0.179r$$

Compared to $0.224 r_p$ found in step C. The phase angle of the phase error signal is the phase shift between the modulation signal and the phase error signal.

For $F_m = 5$ kHz we have

$$\Delta\Phi_e(\text{peak}) = 2\pi \times 2000 \times \frac{(j10000\pi + 17361)}{((972 \times 10^6 - (10000\pi)^2) + j10000\pi \times 31357.8)} = 0,2302 r / 1.066r$$

Compared to $0.288 r_p$ found in step D – I guess the graph was not that accurate.


F) For $\omega_{n1}(\tau_1 + \tau_2)$ values of 5 and over the maximum phase error occurs at $F_m = F_{n1} = 4962$ Hz.

But for $\omega_{n1}(\tau_1 + \tau_2) = 1$ the peak has shifted to about $0,8 F_{n1}$, so my estimate is that for $\omega_{n1}(\tau_1 + \tau_2) = 1.8$ the maximum phase error will occur at approximately $0.9 F_{n1} = 4466$ Hz

G) All yours to answer.

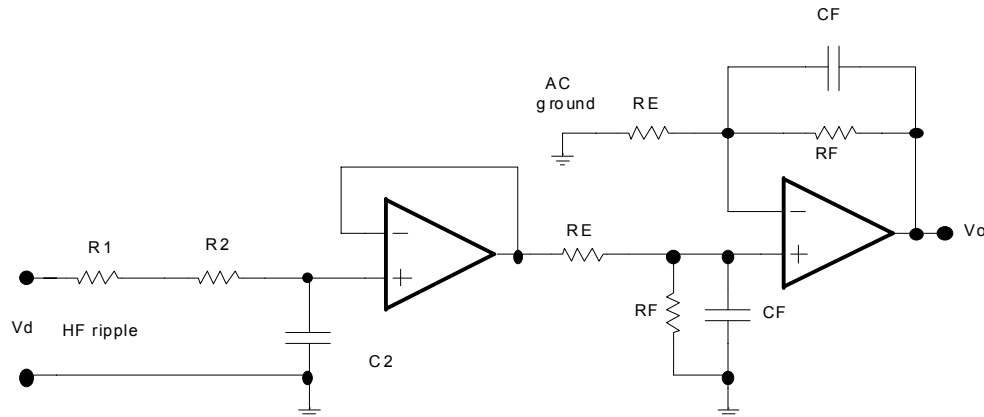H) Ripple calculation (see chart page 19 of theory section)

From phase detector O/P to final O/P, we have





$$\frac{V_o(s)}{V_d(s)} = \frac{\frac{1}{SC_2}}{R_1 + R_2 + \frac{1}{SC_2}} \times \frac{R_F \parallel \frac{1}{SC_F}}{R_E} \approx \frac{1}{SC_2(R_1 + R_2)} \times \frac{1}{SC_F R_E} = \frac{A_1}{S} \times \frac{A_2}{S}$$

$$\Delta V_o(pp) = \Delta V_o(pp) \times \frac{A_1 A_2}{4 \times 8 \times F_{rip}^2} = 2.16 \times \frac{1}{(4300 \times 390 \times 10^{-12}) \times (12 \times 10^{-9} \times 4800) \times 4 \times 8 \times 60K^2} = 194.1 mV_{pp}$$

$$\text{O/P signal level } V_o(\text{peak}) = \frac{\Delta\omega_{in}}{K_V} \times \frac{R_F}{R_E} = \frac{2\pi \times 2000}{82333} \times \frac{82k}{4.3k} = 2.91 V_p$$

$$\% \text{ ripple} = 194.1m / (2.91 \times 2) \times 100 = 3.33\%$$

I)

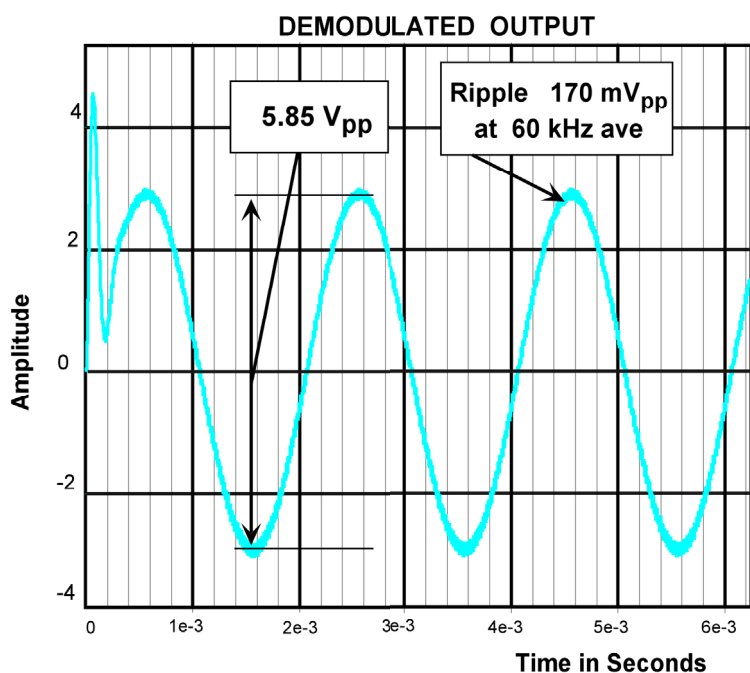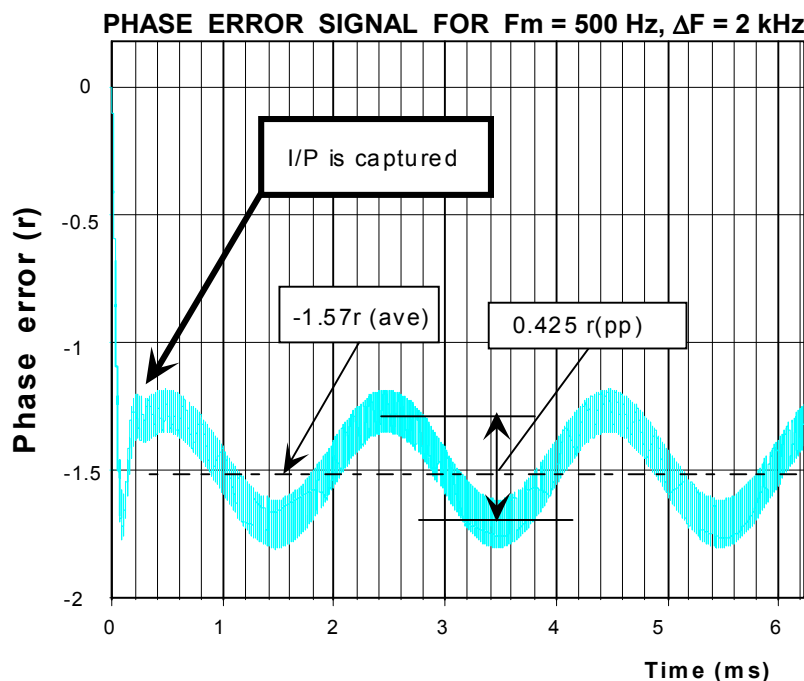


From the previous page, we obtained the following theoretical values:

$$V_o = 5.82 V_{pp} \text{ and ripple of } 191.4 \text{ mV}_{pp}$$

The ripple component is off because the duty cycle was assumed to be 50% at an average frequency of $F_{rip} = 2F_{car}$ at the phase detector O/P. At F_{min} and F_{max} of the FM signal, the duty cycle is above and below 50% and $F_{rip} = 2F_{min}$ and $2F_{max}$ respectively.

Read ripple at top and bottom of demod O/P and average the two values which should come close to the predicted value for 50% duty cycle.

PLL EXERCISE

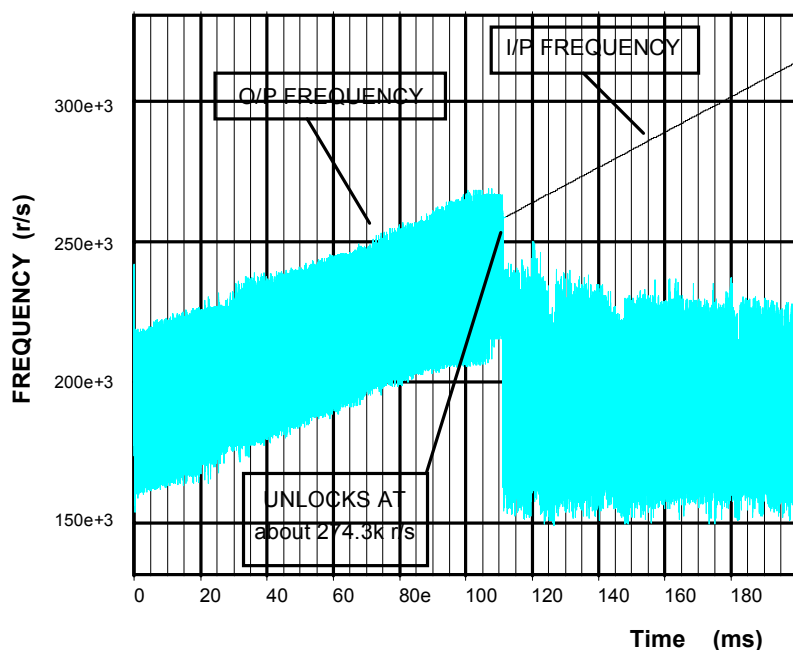

From the S/V simulation, the lock range is:

$$F_{\max} = \frac{274.3k}{2\pi} = 43.656 \text{ kHz}$$

$$F_{\text{cen}} = 30 \text{ kHz}$$

$$\Delta F_L = F_{\max} - F_{\text{cen}} = F_{\text{cen}} - F_{\min}$$

$$\Delta F_L = 43.656k - 30k = 13.66 \text{ kHz}$$

Theoretically we have:


$$\Delta F_{\text{LOCK}} \approx \pm \frac{8 \times F_{\text{cen}}}{\Delta V_{CC}}$$

$$\Delta F_{\text{LOCK}} = \pm \frac{8 \times 30k}{18} = 13.33 \text{ kHz}$$

NOTE: The simulation shown beside is not to scale – run sim file for a better look at results.

The above simulation was done starting at $F_{\text{in}} = 30 \text{ kHz}$ and then ramping up F_{in} at a rate of 100 kHz/sec . If the ramp rate is too fast then the lock range will be less – lock range is defined for a slow variation of F_{in} . You can find F_{\min} by starting at 30 kHz again but now ramping down F_{in} at -100 kHz/sec (Try it!)

CAPTURE RANGE SIMULATION

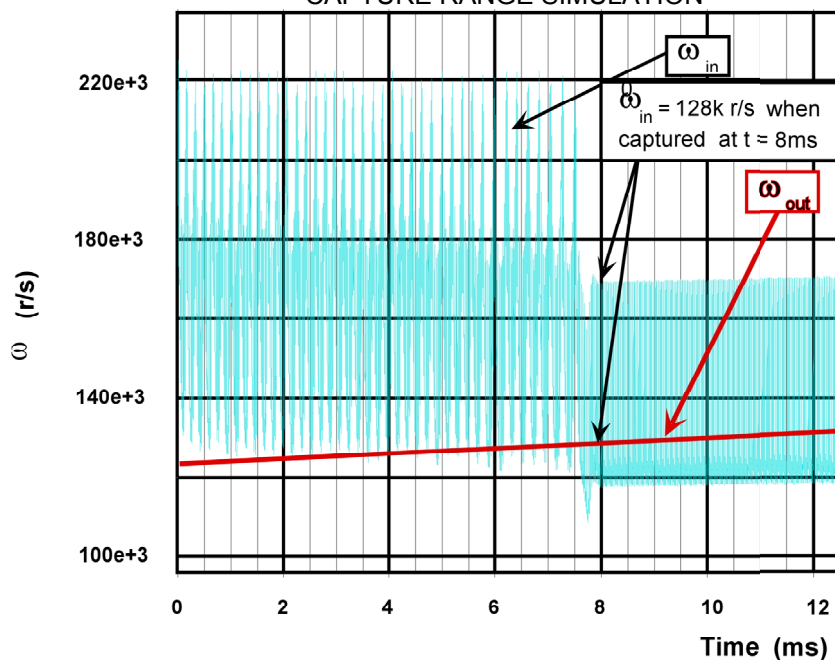

From the S/V simulation, the capture range is:

$$F_{\min} = \frac{128k}{2\pi} = 20.37 \text{ kHz}$$

$$F_{\text{cen}} = 30 \text{ kHz}$$

$$\Delta F_L = F_{\text{cen}} - F_{\min} = F_{\max} - F_{\text{cen}}$$

$$\Delta F_L = 30k - 20.37k = 9.63 \text{ kHz}$$

Theoretically we have:

$$\Delta F_{\text{CAP}} \approx \pm \frac{\sqrt{2}}{2\pi} \times \sqrt{2\zeta\omega_n K_o K_d - \omega_n^2} = \pm \frac{\sqrt{2}}{2\pi} \times \sqrt{2 \times 0.5 \times (2\pi \times 4962) \times 82333 \times 0.68 - (2\pi \times 4962)^2}$$

$$\Delta F_{\text{CAP}} = \pm 1.73 \text{ kHz}$$

Nos.2, 3 and 5 you are on your own – see theory examples for help.

N0.4 A) $F_o = 86 \text{ MHz}$ to 108 MHz or $F_o = 152 \text{ MHz}$ to 174 MHz with steps of $\Delta F_o = 200 \text{ kHz}$
B, C and D are yours.