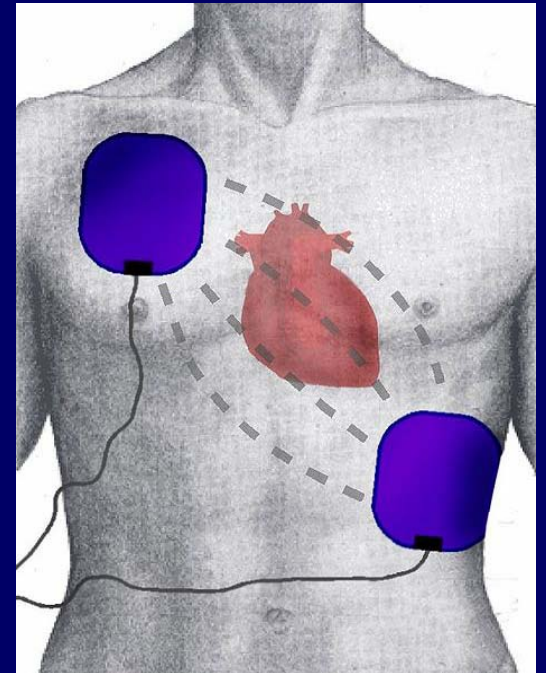




# Physics 102: Lecture 7

## RC Circuits


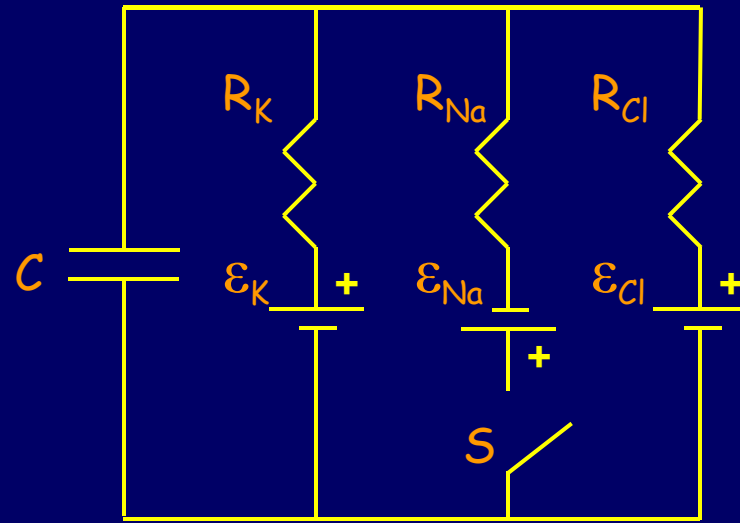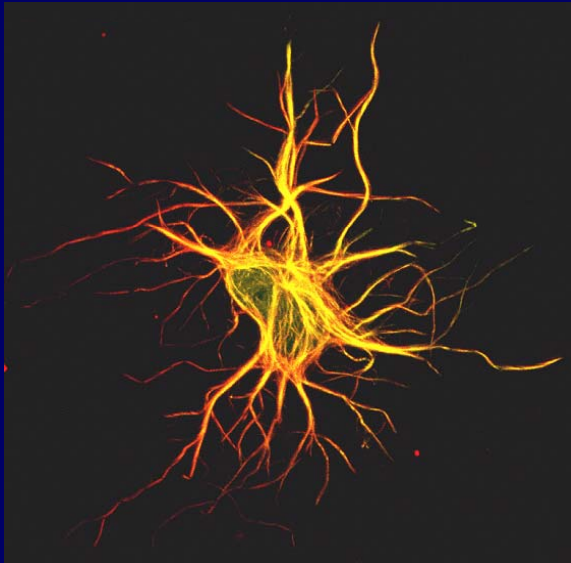
# RC Circuits

- Circuits that have both resistors and capacitors:



- With **resistance** in the circuits, **capacitors** do not **charge** and **discharge** instantaneously – it takes time (even if only fractions of a second).

# RC Circuits

Used to controllably store and release energy



## Today:

- RC Circuits
- Charging Capacitors
- Discharging Capacitors
- Intermediate Behavior
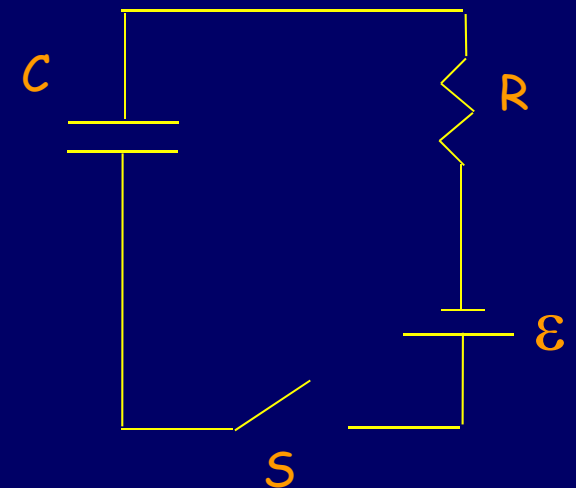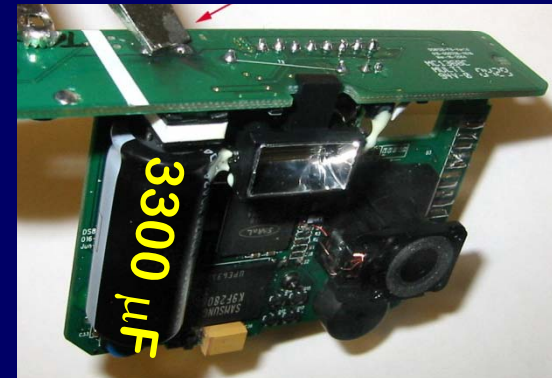
# Charging Capacitors

Storing energy to use later

- Capacitor is initially uncharged and switch is open. Switch is then closed.
- What is current  $I_0$  in circuit immediately thereafter?
- What is current  $I_\infty$  in circuit a long time later?





# Charging Capacitors: $t = 0$

- Capacitor is initially uncharged and switch is open. Switch is then closed.
- What is current  $I_0$  in circuit immediately thereafter?

- Capacitor initially uncharged
- Therefore  $V_C = 0$  (since  $V = Q/C$ )
- **Therefore C behaves as a wire (short circuit)**  $KLR: +\mathcal{E} - IR = 0$
- Ohm's law!

$$I_0 = \mathcal{E}/R$$

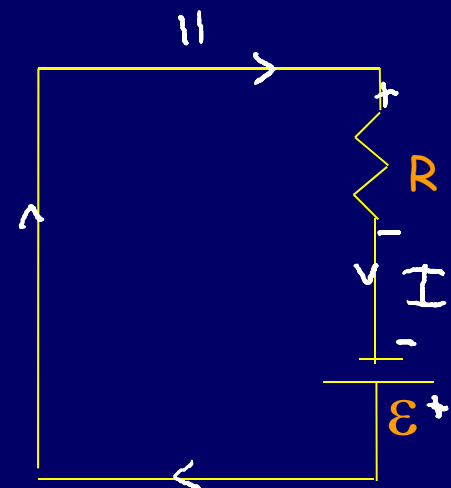
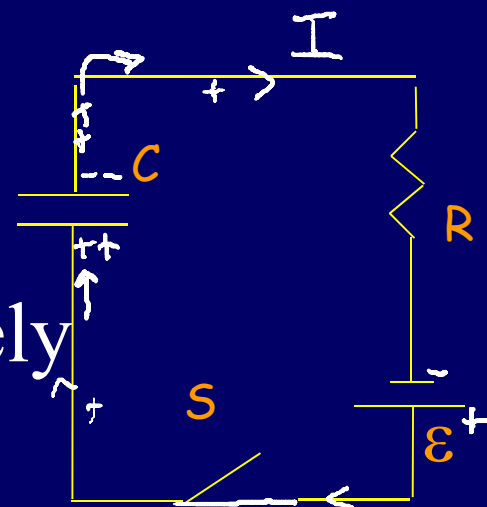


# Charging Capacitors: $t > 0$

- $I_0 = \mathcal{E}/R$      $Q_0 = 0$
- **Positive charge flows**
  - Onto bottom plate (+Q)
  - Away from top plate (-Q)
  - As charge builds up,  $V_C$  rises ( $V_C = Q/C$ )
  - Loop:  $\mathcal{E} - V_C - IR = 0$ 
    - $I = (\mathcal{E} - V_C)/R < I_0$
    - Therefore  $I$  falls as  $Q$  rises
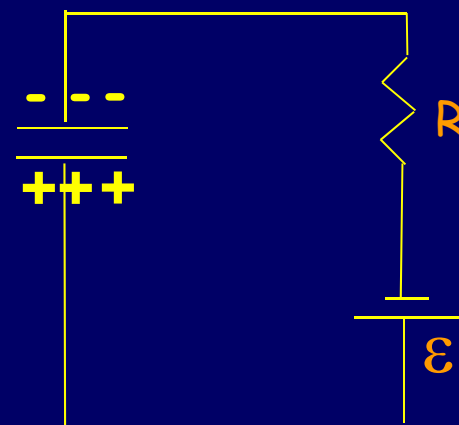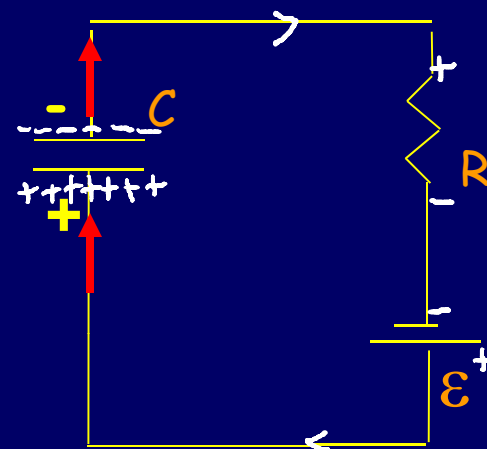
## – When $t$ is very large ( $\infty$ )

- $I_\infty = 0$ : no current flow into/out of capacitor at long times
- $V_C = \mathcal{E}$      $Q_\infty = C\mathcal{E}$





# ACT/CheckPoint 1

Both switches are initially open, and the capacitor is uncharged. What is the current through the battery just after switch  $S_1$  is closed?

1)  $I_b = 0$


2)  $I_b = \mathcal{E} / (3R)$

3)  $I_b = \mathcal{E} / (2R)$

4)  $I_b = \mathcal{E} / R$

Capacitor acts like a wire the instant the switch is closed:

$$\Rightarrow I = \mathcal{E} / (2R)$$

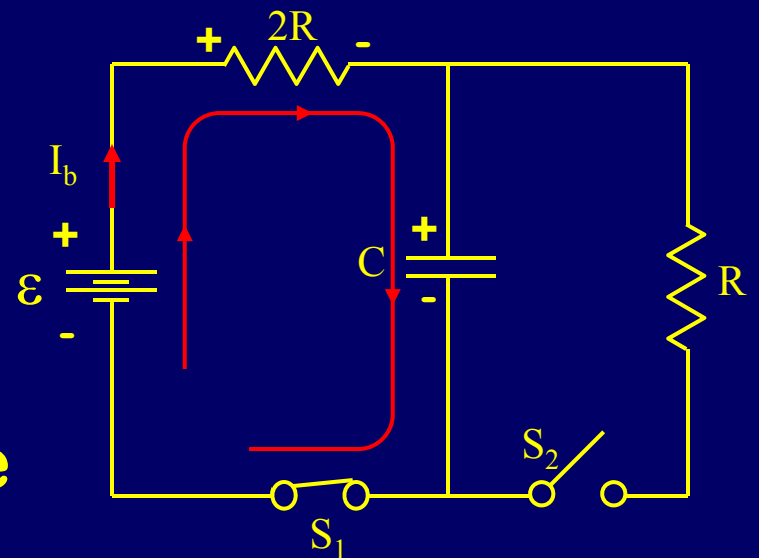



# ACT/CheckPoint 3


Both switches are initially open, and the capacitor is uncharged.  
What is the current through the battery after switch 1 has been closed a long time?

1)  $I_b = 0$

2)  $I_b = \mathcal{E}/(3R)$

3)  $I_b = \mathcal{E}/(2R)$

4)  $I_b = \mathcal{E}/R$

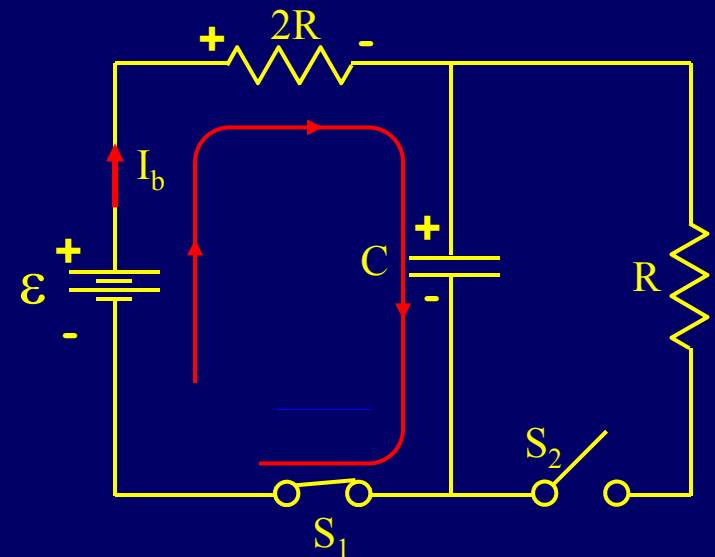



- Long time  $\Rightarrow$  current through capacitor is zero
- $I_b = 0$  because the battery and capacitor are in series.
- **KLR:**  $\mathcal{E} - 0 - q_{\infty}/C = 0 \Rightarrow q_{\infty} = \mathcal{E}C$


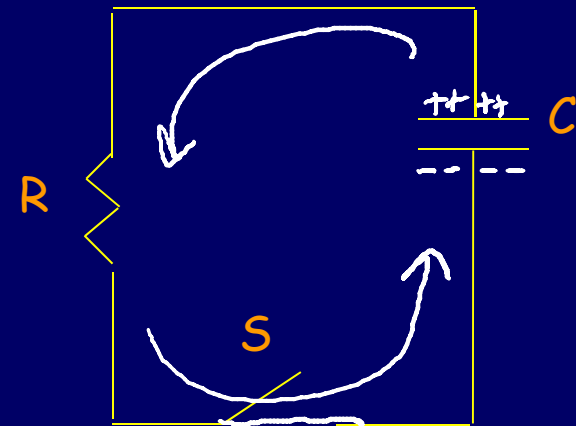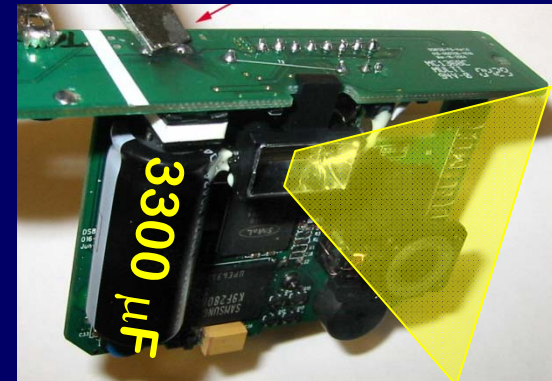
# Discharging Capacitors


Time to use that stored energy!

- Capacitor is initially charged ( $Q$ ) and switch is open. Switch is then closed.
- What is current  $I_0$  in circuit immediately thereafter?
- What is current  $I_\infty$  in circuit a long time later?


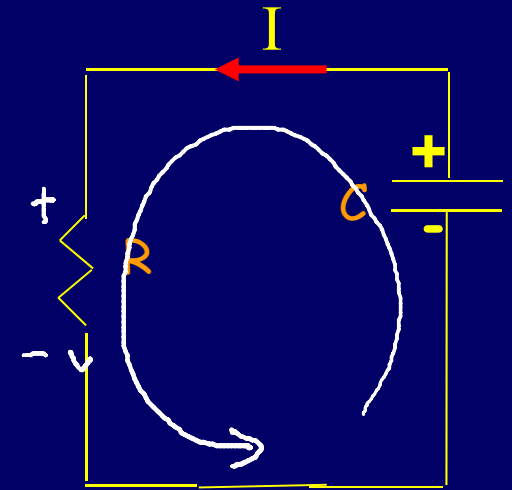
# Discharging Capacitors

- Capacitor is initially charged ( $Q$ ) and switch is open. Switch is then closed.
- What is current  $I_0$  in circuit immediately thereafter?
  - KLR:  $Q/C - I_0 R = 0$
  - So,  $I_0 = Q/RC$
- What is current  $I_\infty$  in circuit a long time later?
  - $I_\infty = 0$       $Q_\infty = 0$





# ACT/CheckPoint 5

After switch 1 has been closed for a long time, it is opened and switch 2 is closed. What is the current through the right resistor just after switch 2 is closed?


$$t = 0$$

1)  $I_R = 0$

2)  $I_R = \varepsilon / (3R)$

3)  $I_R = \varepsilon / (2R)$

4)  $I_R = \varepsilon / R$

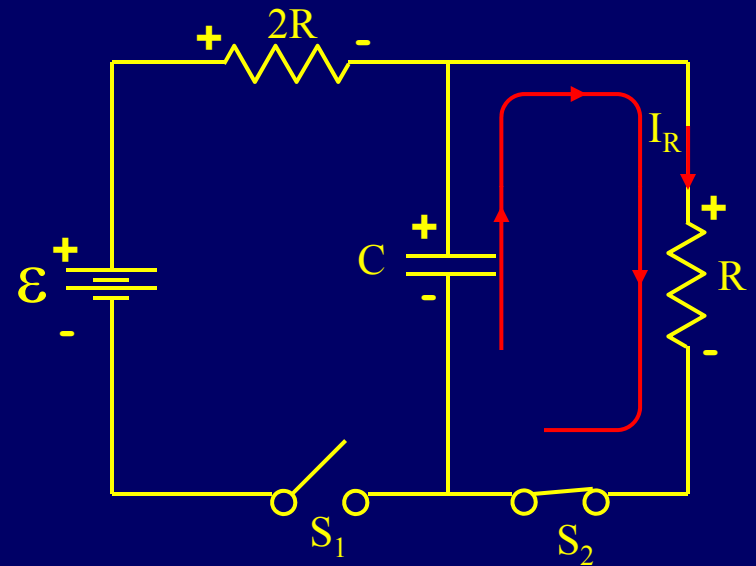

KLR:  $q_0/C - IR = 0$

Recall  $q$  is charge on capacitor after charging:


$$q_0 = \varepsilon C \quad (\text{since charged w/ switch 2 open!})$$

$$\varepsilon - IR = 0 \Rightarrow I = \varepsilon / R$$

# Summary: charging & discharging



- Charge (and therefore voltage) on Capacitors cannot change instantly: remember  $V_C = Q/C$
- Short term behavior of Capacitor:
  - If the capacitor starts with no charge, it has no potential difference across it and acts as a wire
  - If the capacitor starts with charge, it has a potential difference across it and acts as a battery.
- Long term behavior of Capacitor: Current through a Capacitor is eventually zero.
  - If the capacitor is charging, when fully charged no current flows and capacitor acts as an open circuit
  - If capacitor is discharging, potential difference is zero and no current flows

# RC Circuits: Charging

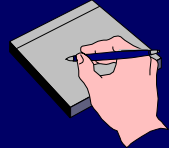


The switches are originally open and the capacitor is uncharged. Then switch  $S_1$  is closed.



- **Loop:**  $\varepsilon - I(t)R - q(t) / C = 0$
- **Just after...:**  $q = 0$   $t = 0$ 
  - Capacitor is uncharged  $q_0 = 0$
  - $\varepsilon - I_0 R = 0 \Rightarrow I_0 = \varepsilon / R$
- **Long time after:**  $I_\infty = 0$ 
  - Capacitor is fully charged
  - $\varepsilon - q_\infty / C = 0 \Rightarrow q_\infty = \varepsilon C$
- **Intermediate (more complex)**  
 $q(t) = q_\infty (1 - e^{-t/RC})$   
 $I(t) = I_0 e^{-t/RC}$

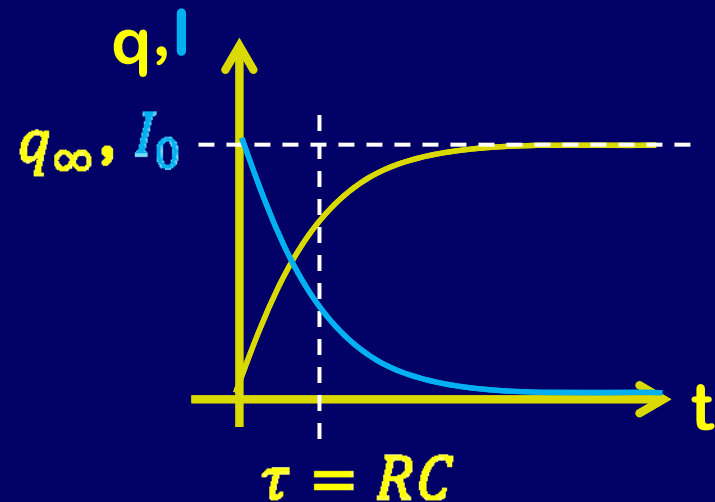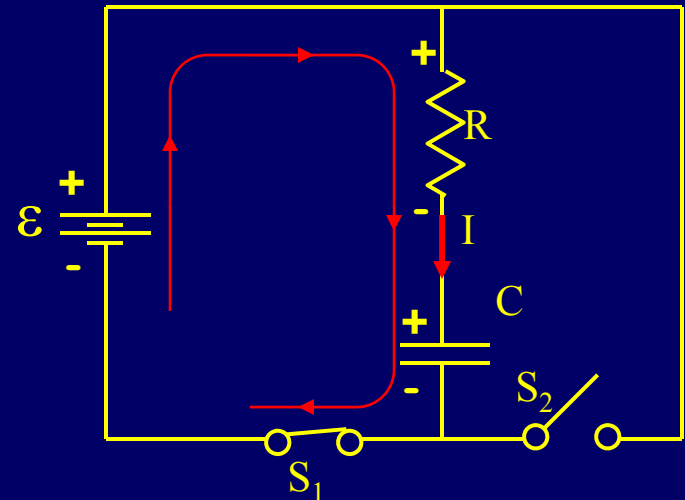

# RC Circuits: Discharging

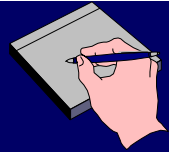


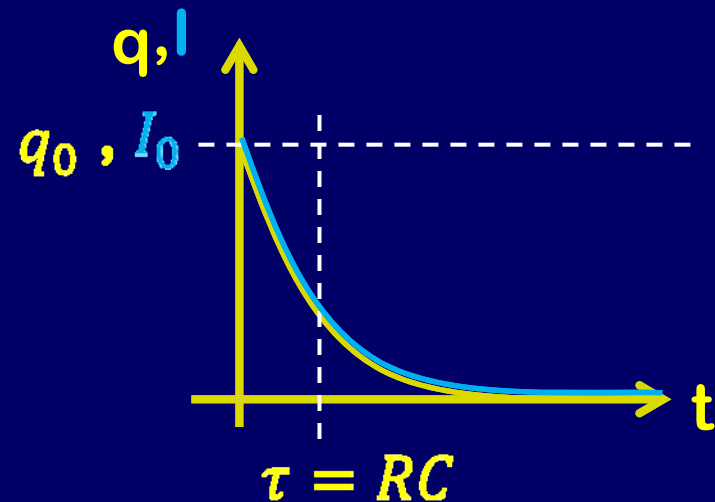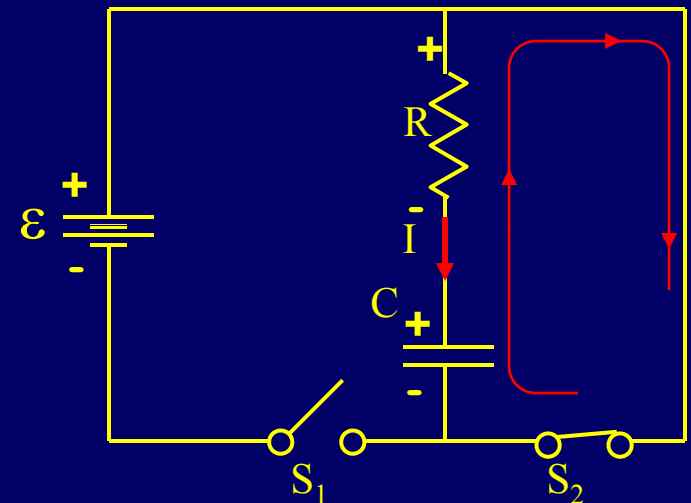- **Loop:**  $q(t) / C + I(t) R = 0$
- **Just after...:**  $q=q_0$   $t=0$ 
  - Capacitor is still fully charged
  - $q_0 / C + I_0 R = 0 \Rightarrow I_0 = -q_0 / (RC)$
- **Long time after:**  $I_\infty=0$   $t=\infty$ 
  - Capacitor is discharged
  - $q_\infty / C = 0 \Rightarrow q_\infty = 0$
- **Intermediate (more complex)**  
 $q(t) = q_0 e^{-t/RC}$   
 $I(t) = I_0 e^{-t/RC}$


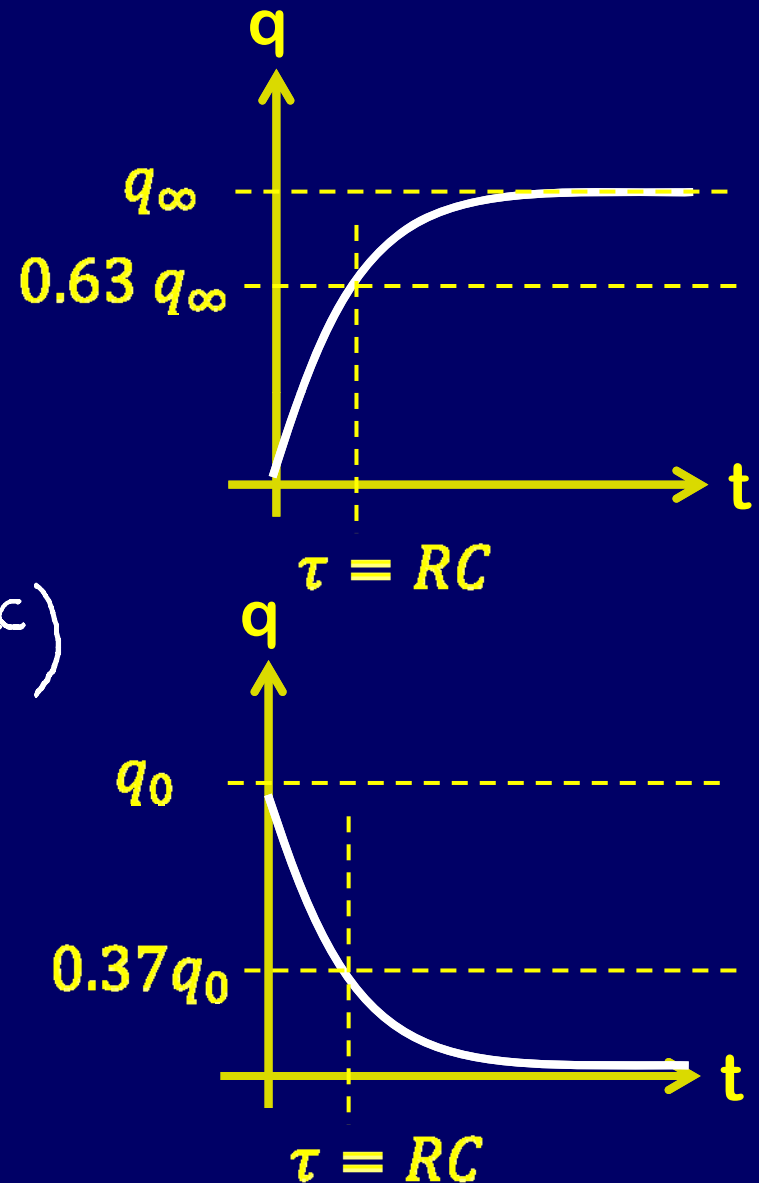
# What is the time constant?

- The time constant  $\tau = RC$ .
- Given a capacitor starting with no charge, the **time constant** is the amount of time an RC circuit takes to charge a capacitor to about **63%** of its final value.  $q(t) = q_{\infty} (1 - e^{-t/RC})$
- The **time constant** is the amount of time an RC circuit takes to discharge a capacitor to about **37%** of its original value.  $q = q_0 e^{-t/RC}$



## Example

# Time Constant Demo

Each circuit has a 1 F capacitor charged to 100 Volts.  
When the switch is closed:



- Which system will be brightest?
- Which lights will stay on longest?
- Which lights consumes more energy?

(2)  $I = V/R$

(1)

Same

$U = 1/2 CV^2$

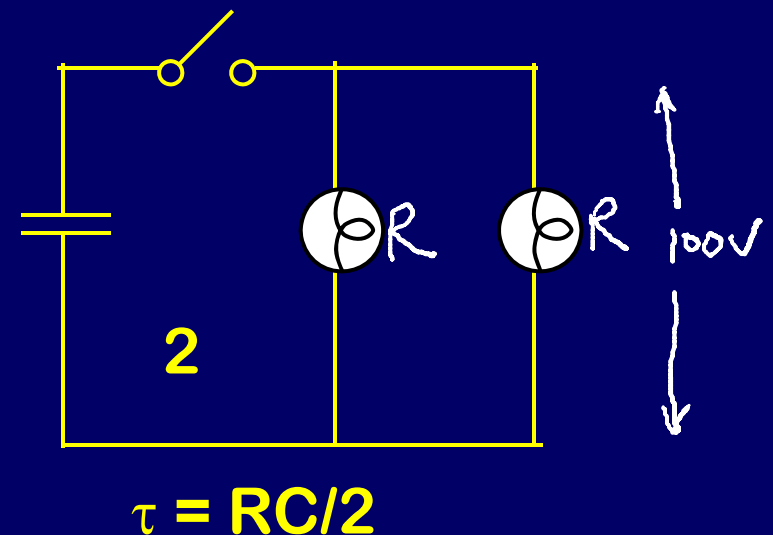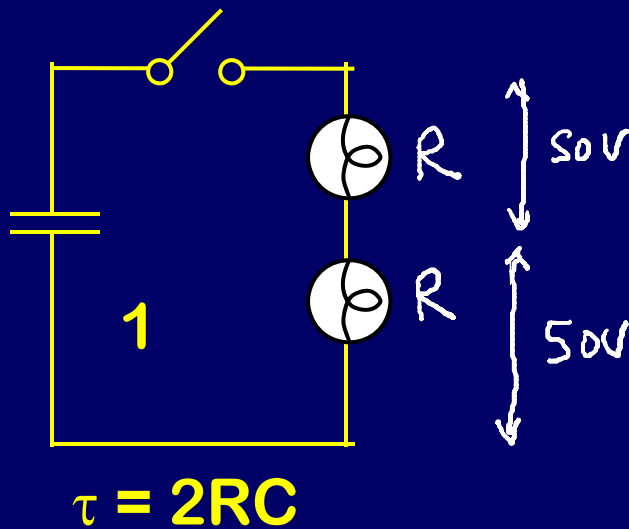





# Summary of Concepts

- Charge (and therefore voltage) on Capacitors cannot change instantly: remember  $V_C = Q/C$
- Short term behavior of Capacitor:
  - If the capacitor starts with no charge, it has no potential difference across it and acts as a wire
  - If the capacitor starts with charge, it has a potential difference across it and acts as a battery.
- Long term behavior of Capacitor: Current through a Capacitor is eventually zero.
  - If the capacitor is charging, when fully charged no current flows and capacitor acts as an open circuit.
  - If capacitor is discharging, potential difference is zero and no current flows.
- Intermediate behavior: Charge and current exponentially approach their long-term values  $\tau = RC$

Example

# Practice: defibrillator

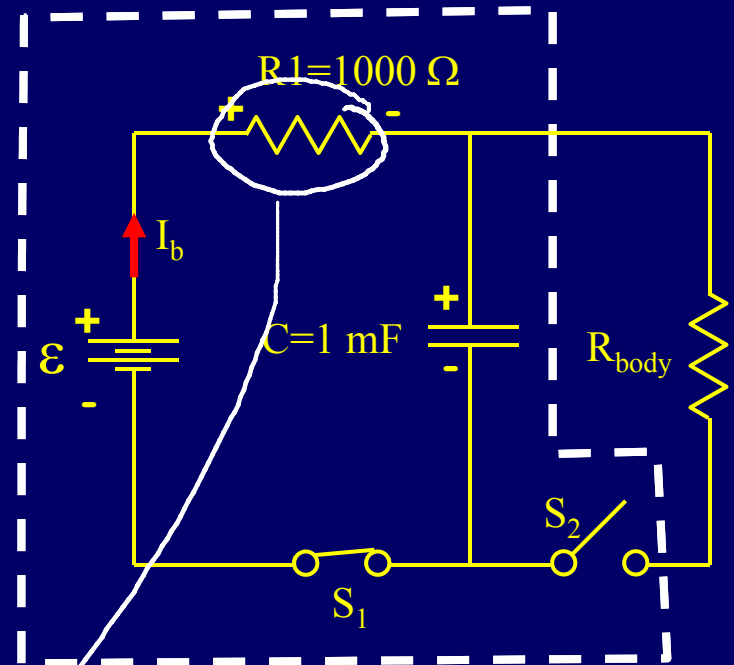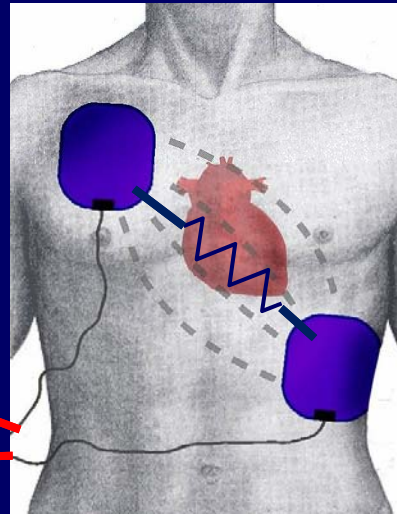

A 500 V battery is used to charge the 1 mF capacitor for 2 seconds. How much charge is stored on the capacitor?



$$q(t) = q_{\infty}(1 - e^{-t/RC}) \quad q_{\infty} = C\epsilon = (0.001 \text{ F})(500 \text{ V}) = 0.5 \text{ C}$$

$$q(2 \text{ s}) = 0.5 \text{ C}(1 - e^{-2\text{s}/1000\Omega \times 0.001\text{F}}) = 0.4 \text{ C}$$

$$V_C = Q/C = 0.4\text{C}/0.001\text{F} = 400 \text{ V}$$

Example



# Practice: defibrillator

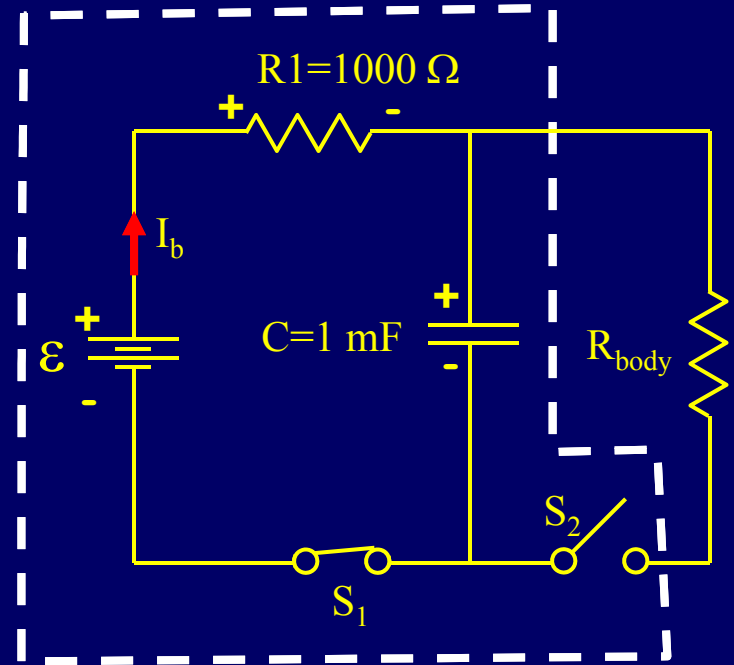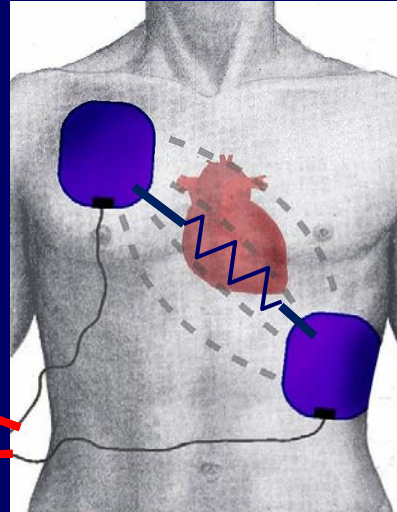

A 500 V battery is used to charge the 1 mF capacitor for 2 seconds. How much energy is stored in the capacitor?

$$U = Q^2 / 2C = (0.4C)^2 / (2 \times 0.001 \text{ F}) = 80 \text{ J}$$

# ACT: defibrillator

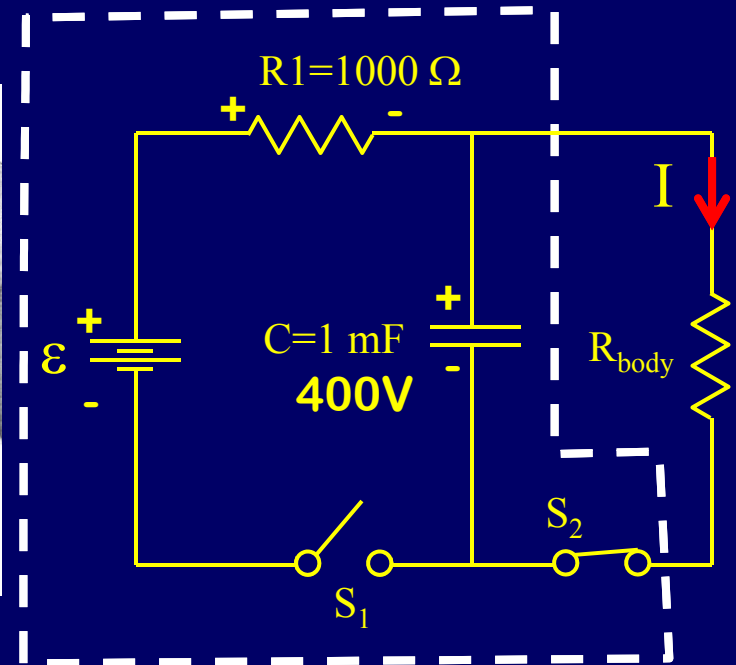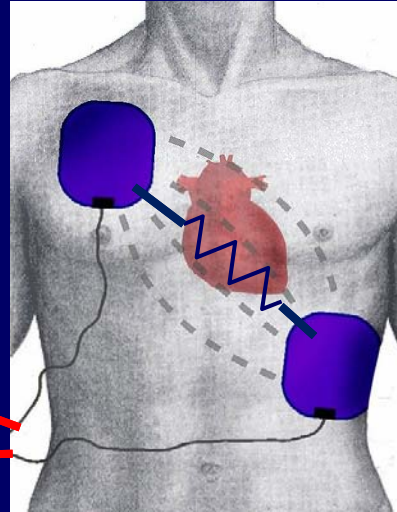

After charging for 2 seconds,  $S_1$  is opened; What is the current through the patient right after  $S_2$  is closed if  $R_{\text{body}} = 100 \Omega$ ?

(A) 0 A



(B) 4 A

(C) 0.25 A

$$I = V/R = 400V/100\Omega = 4 A$$


Example

# Practice: defibrillator

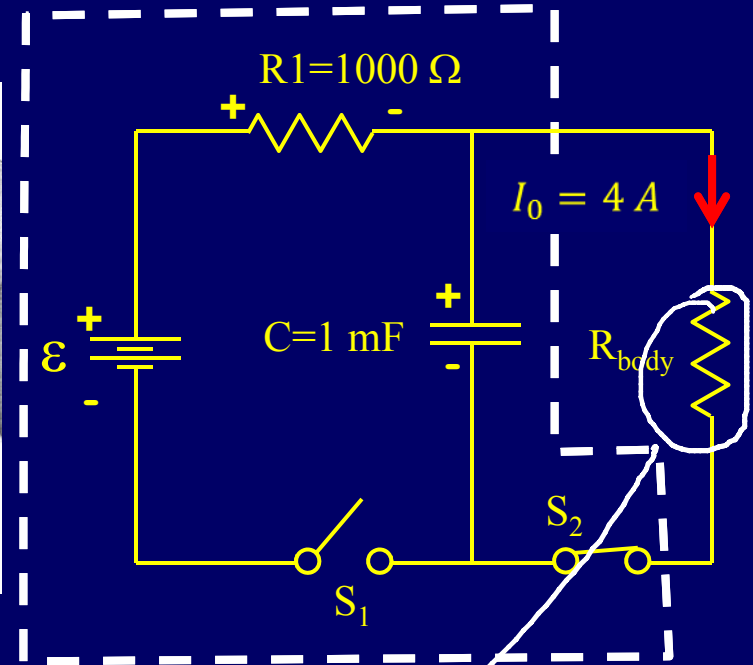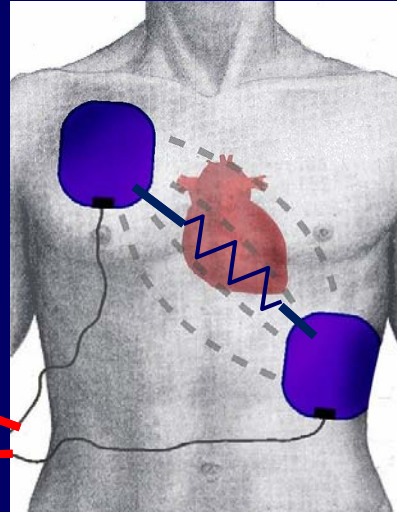

After charging for 2 s,  $S_1$  is opened. What is the current through the patient 0.1 s after  $S_2$  is closed if  $R_{\text{body}} = 100 \Omega$ ?
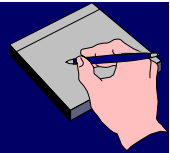
$$I(0.1\text{s}) = I_0 e^{-t/RC} = 4 \text{ A } e^{-0.1 \text{ s} / 100 \Omega \times 0.001 \text{ F}} = 1.5 \text{ A}$$



# RC Summary

## Charging

$$q(t) = q_{\infty}(1 - e^{-t/RC})$$

$$V(t) = V_{\infty}(1 - e^{-t/RC})$$

$$I(t) = I_0 e^{-t/RC}$$

## Discharging

$$q(t) = q_0 e^{-t/RC}$$

$$V(t) = V_0 e^{-t/RC}$$

$$I(t) = I_0 e^{-t/RC}$$

**Time Constant  $\tau = RC$**

Large  $\tau$  means long time to charge/discharge

**Short term:** Charge doesn't change (often zero or max)

**Long term:** Current through capacitor is zero.