

REVIEW EXAM 3


INEL 4202 - Fall 2015

TOPICS


18 (10/16)	Integrators and differentiators, Applications	2.5	2.79, 2.80
19 (10/21)	Current sources	7.(4,5)	7.(46, 47, 48, 55, 56, 58, 67, 70, 76, 77, 78)
20 (10/23)	The differential amplifier	8.(1-3, 5)	8.(1, 2, 9, 25, 27, 29, 32, 33, 53, 60, 61, 62, 63, 64, 85, 91, 94, 102)
21 (10/28)	DC analysis of the 741 opamp	12.(3,4)	12.(23, 24, 25, 28, 29, 37, 39)
22 (10/30)	AC analysis of the 741 op-amp	12.5	12.(42, 43, 47, 50)
23 (11/4)	Frequency response and slew rate	12.6	12.(59, 62, 63)
24 (11/6)	CMOS opamp DC and AC analysis	12.1	12.(2, 3, 5, 6)
25 (11/10)	Freq. resp. and slew rate of CMOS opamp		12.(9, 10, 11)
26 (11/13)	Folded cascode opamp	12.2	12.(15, 16, 18, 19)

OP-AMP & APPLICATIONS


DUAL-OPAMP IA WITH VARIABLE GAIN

 


GROUNDING-LOAD CURRENT AMP

 

CURRENT SOURCES & ACTIVE LOADS

 


Basic C.S.

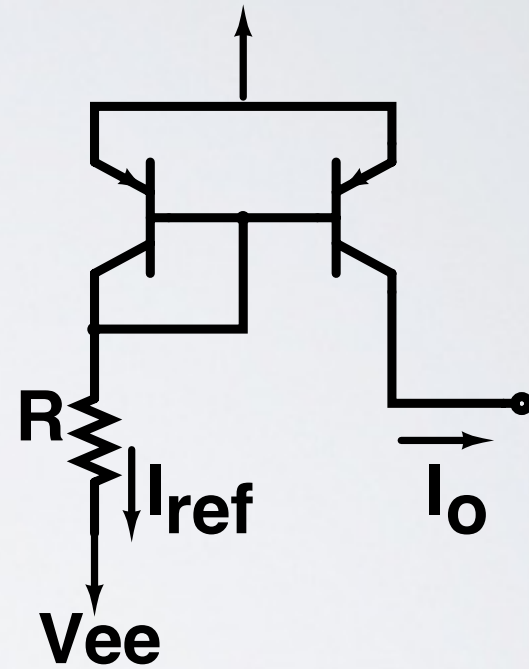

Basic C.S. with PNP BJTs

MOSFET CSs

 



$$v_{GS,1} = v_{GS,2} = v_{DS,1}$$

$$i_{D,1} = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L} \right)_1 (v_{GS,1} - V_t)^2$$


$$i_{D,2} = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L} \right)_2 (v_{GS,1} - V_t)^2$$
 
$$\frac{i_{D,2}}{i_{D,1}} = \frac{I_O}{I_{REF}} = \frac{(W/L)_1}{(W/L)_2}$$




 

Mirror with base-current compensation


 


**Basic Source with
Emitter Resistors**

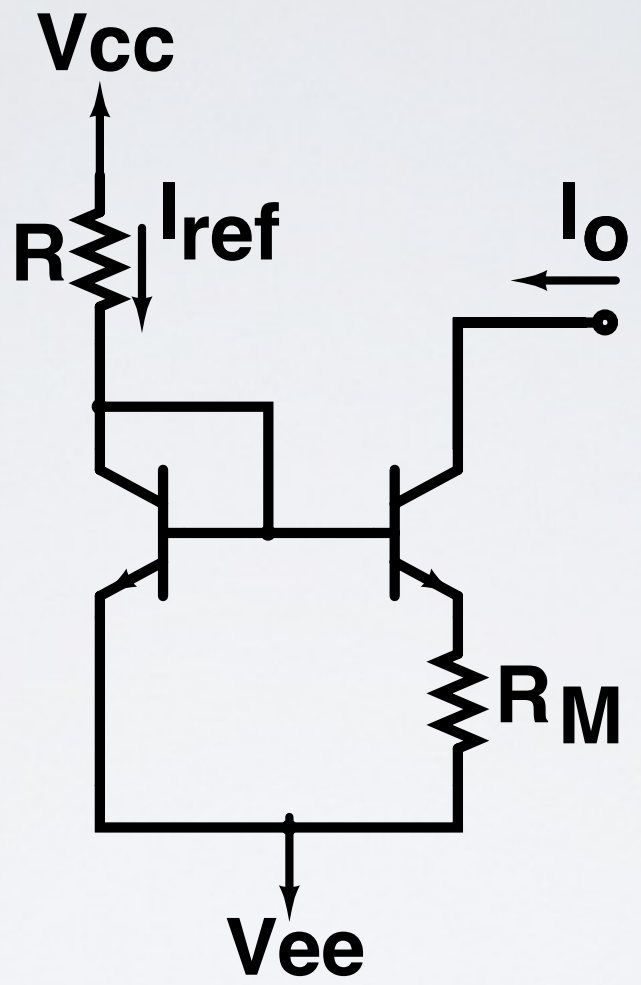


Widlar C.S.

Active Loads

  


DIFFERENTIAL AMPLIFIERS



Basic Configuration

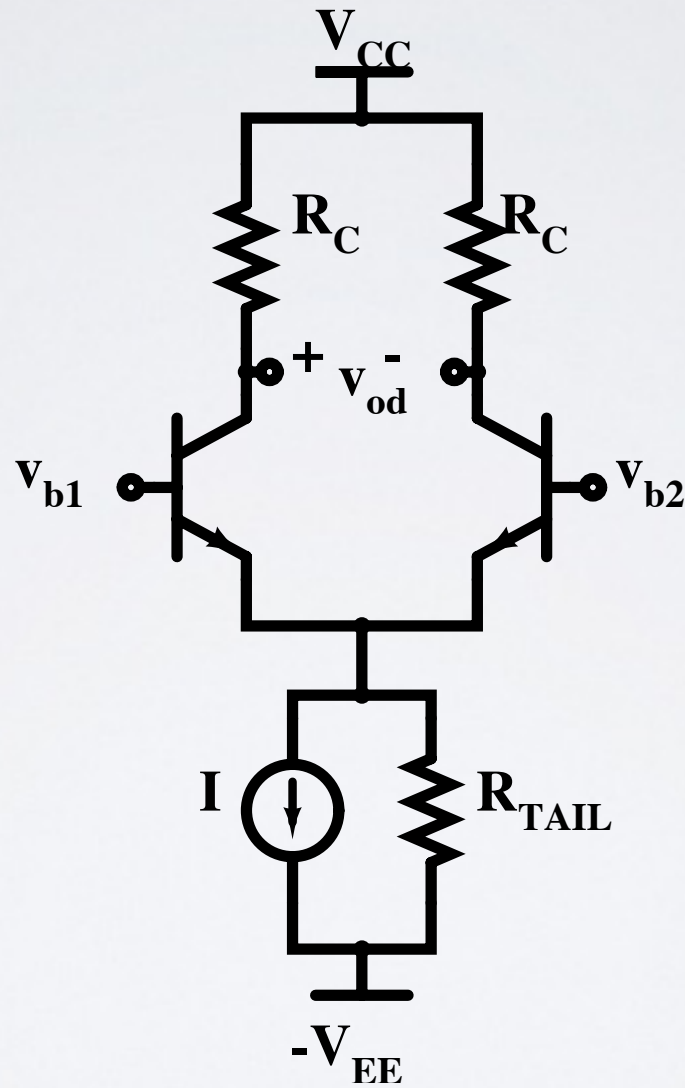

 
Differential-mode gain and input resistance.



Common-mode gain and input resistance.

  

Active Loads

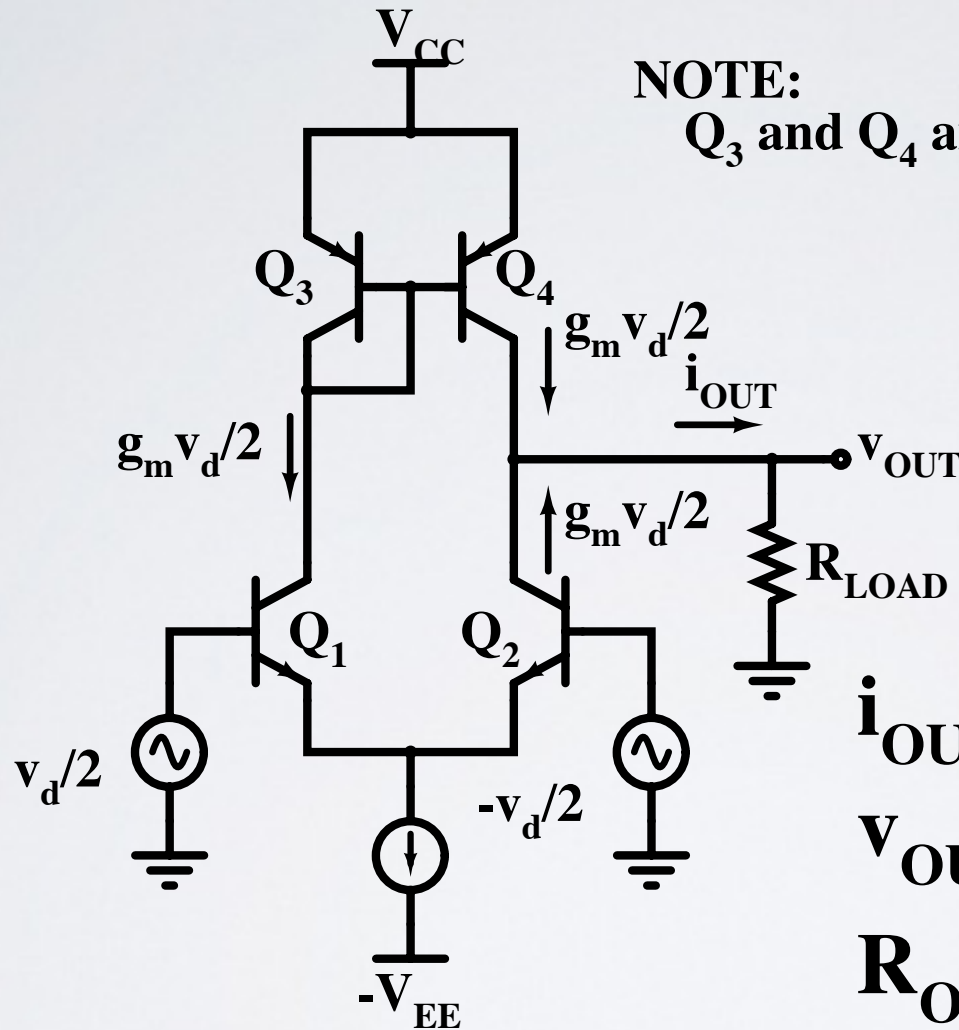


NOTE:
 Q_3 and Q_4 are PNP BJTs

$$i_{OUT} = g_m v_d$$

$$v_{OUT} = i_{OUT} R_O$$
 
$$R_O = R_{LOAD} \parallel r_{O2} \parallel r_{O4}$$




$$i_{OUT} = g_m v_d$$

$$v_{OUT} = i_{OUT} R_O$$

$$R_O = R_{LOAD} \parallel r_{O6} \parallel (1 + \beta) r_O$$

CMOS OPAMPS

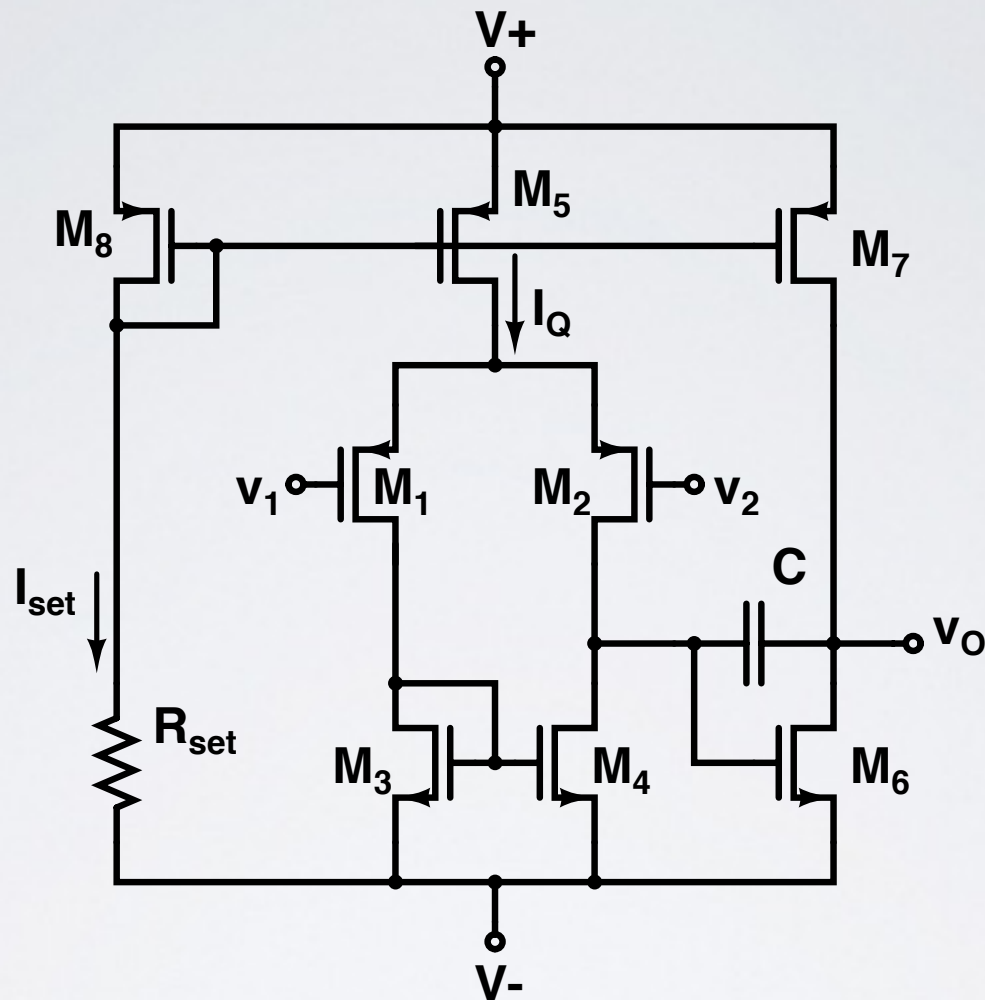

Example 13.8: Find DC bias current when $V_{TN}=0.5V$, $\frac{1}{2}\mu_n C_{ox}=20\mu A/V^2$, $\lambda_n=0.02V^{-1}$, $V_{TP}=-0.5V$, $\frac{1}{2}\mu_p C_{ox}=10\mu A/V^2$, $\lambda_p=0.02V^{-1}$, $R_{SET}=225k\Omega$, $(W/L)_3=(W/L)_4=6.25$, $(W/L)_{OTHER}=12.5$, $V_+=5V$, $V_-=-5V$. (ANSWER: $I_{REF}=39.7\mu A$)

Example 13.9: Find gain. (ANSWER: $A_v=(125)(125)=15,625$)


A_{CM} for differential stage with active load due to and error ϵ in K (for example, $(W/L)_1 = (1 + \epsilon) (W/L)_2$)

$$\begin{aligned}
 i_{d,1} &= g_{m1} v_{gs,1} \\
 v_{gs,1} &= v_{g,1} - v_{s,1} \\
 v_{g,1} &= v_{cm} \\
 v_{s,1} &= 2R_{CS} \times i_{d,1} \\
 i_{d,1} &= g_{m1} (v_{cm} - 2R_{CS} \times i_{d,1}) \\
 i_{d,1} (1 + g_{m1} 2R_{CS}) &= g_{m1} v_{cm} \\
 i_{d,1} &= \frac{g_{m1} v_{cm}}{1 + g_{m1} 2R_{CS}} \\
 i_{d,2} &= \frac{g_{m2} v_{cm}}{1 + g_{m2} 2R_{CS}} \\
 g_{m1} &= g_{m2} (1 + \epsilon) \\
 i_{o,1} &= i_{d,1} - i_{d,2} = \frac{g_{m2} (1 + \epsilon) v_{cm}}{1 + g_{m2} (1 + \epsilon) 2R_{CS}} - \frac{g_{m2} v_{cm}}{1 + g_{m2} 2R_{CS}} \\
 v_{o,1} &= i_{o,1} (r_{o4} \parallel r_{o2})
 \end{aligned}$$

If $2g_{m2}\epsilon R_{CS} \ll 1$, (or equivalently, $\epsilon \ll \frac{1}{2g_{m2}R_{CS}}$)


$$\begin{aligned}
 i_{o,1} &\simeq \frac{g_{m2}\epsilon v_{cm}}{1 + g_{m2} 2R_{CS}} \\
 A_{cm,1} &= \frac{v_{o,1}}{v_{cm}} = \frac{g_{m2}\epsilon (r_{o4} \parallel r_{o2})}{1 + g_{m2} 2R_{CS}} \Rightarrow CMRR = \frac{1 + g_{m2} 2R_{CS}}{\epsilon}
 \end{aligned}$$

Three-stage cmos opamp

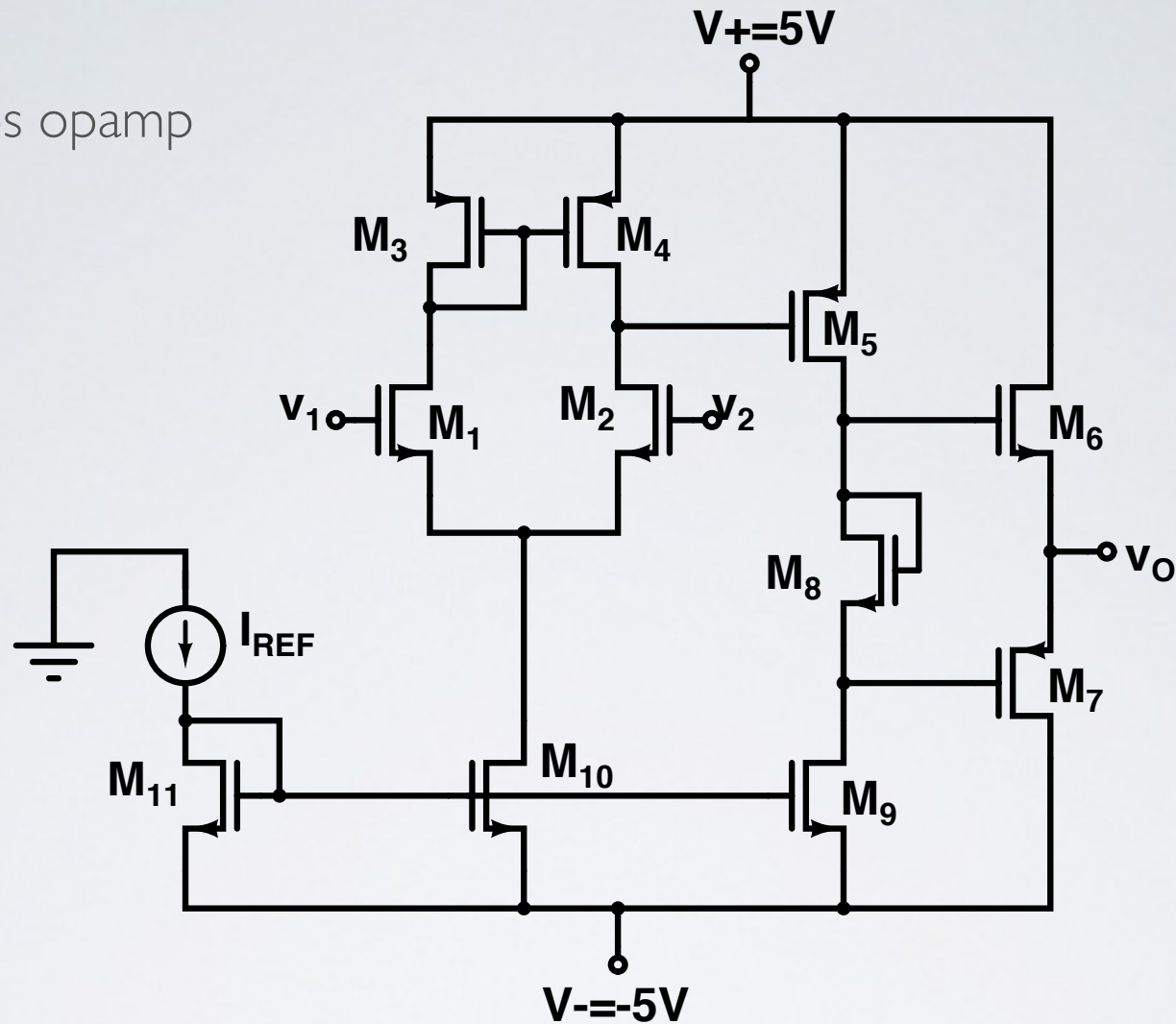


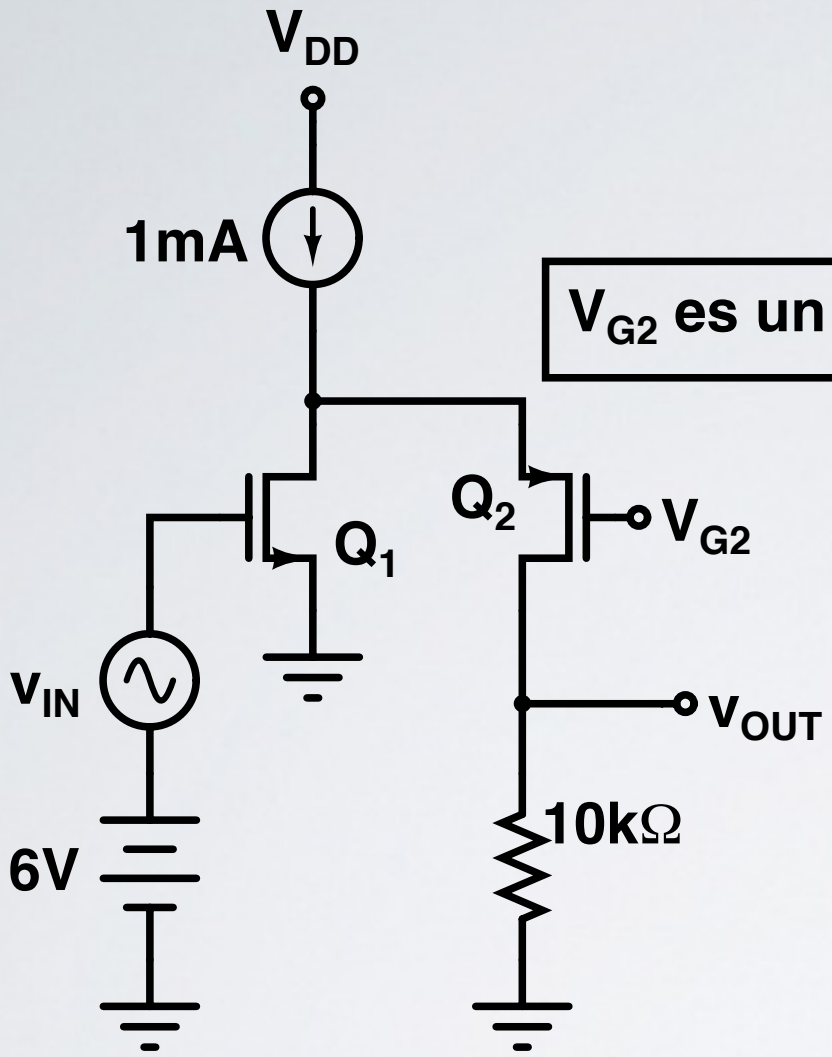Example: Find DC and AC characteristics. $V_{TN} = 0.7V$, $k_n' = 80\mu A/V^2$, $\lambda_n = 0.01V^{-1}$, $V_{TP} = -0.7V$, $k_p' = 40\mu A/V^2$, $\lambda_p = 0.015V^{-1}$, $I_{REF} = 160\mu A$, $(W/L)_1 = (W/L)_2 = 15/1$, $(W/L)_3 = (W/L)_4 = 40/1$, $(W/L)_5 = 80/1$, $(W/L)_6 = 25/1$, $(W/L)_7 = 50/1$, $(W/L)_9 = (W/L)_{10} = (W/L)_{11} = 20/1$. Select $(W/L)_8$ so that $V_{GS6} = V_{GS7} = 0.85V$.

ANSWER: $(W/L)_8 = 4$; $I_{D6} = I_{D7} = 22.5\mu A$; $A_v = (219)(-253) = -55407 V/V$.



 
$K_{n,p} = 20\text{mA/V}$
 $V_{Tn} = -V_{Tp} = 1\text{V}$




For the following CMOS amplifier, where V_{b1} and V_{b2} are DC voltages for proper operation of the circuit:

- identify the negative and the positive terminals
- find the expression for the differential gain $A_{id} = V_{out}/V_{id}$
- find the expression for the differential input resistance R_{ind}
- find the expression for the output resistance R_{out}


Assume: I_{ss} = ideal current source

 


 


Example: $I_{REF}=100\mu A$, $k_n'=80\mu A/V^2$, $K_p'=40\mu A/V^2$, $(W/L)=25$, γ , $\lambda_n=\lambda_p=0.02V^{-1}$. Find voltage gain. (ANSWER: $A_d=32000$)

BJT OPAMPS & UA741

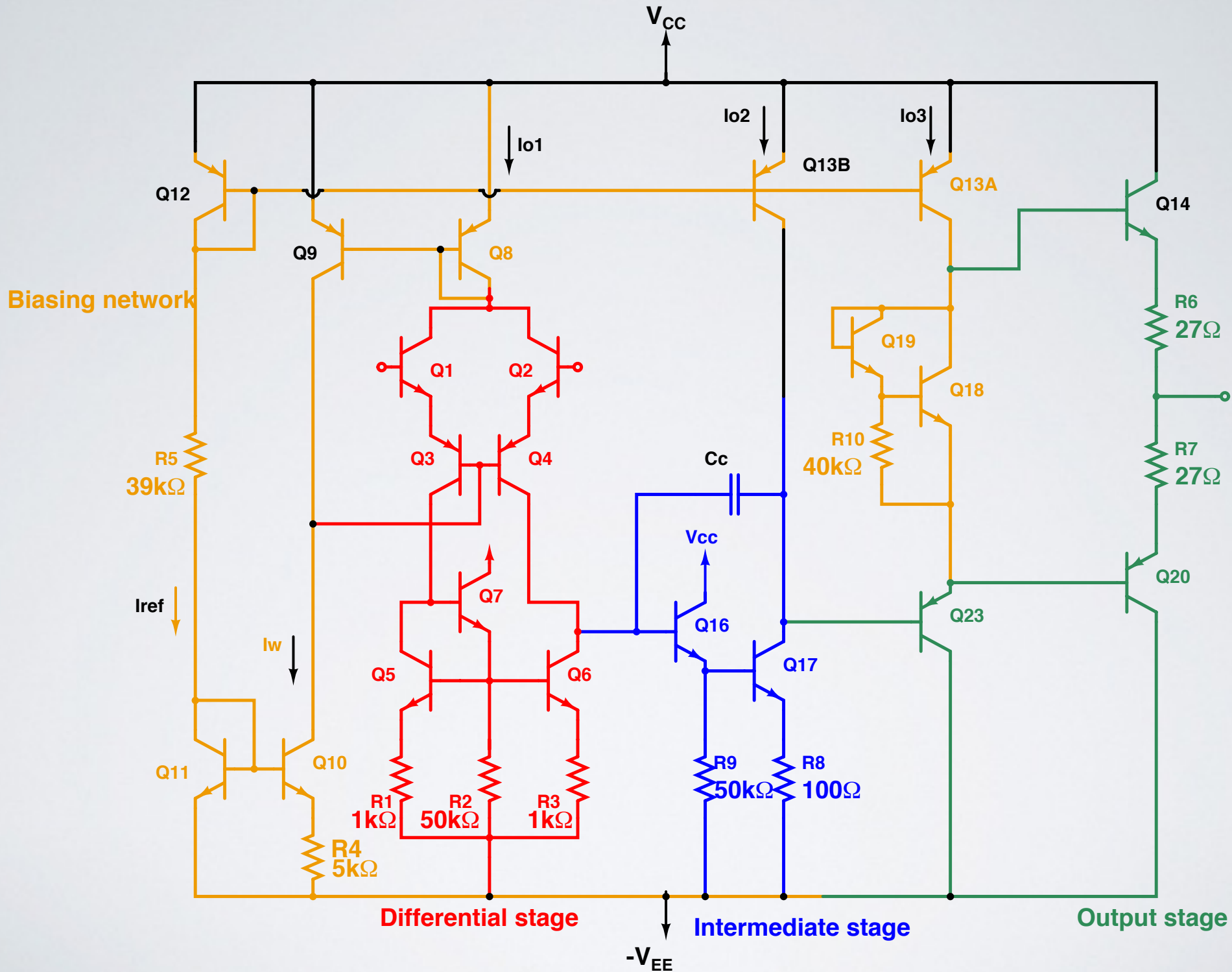

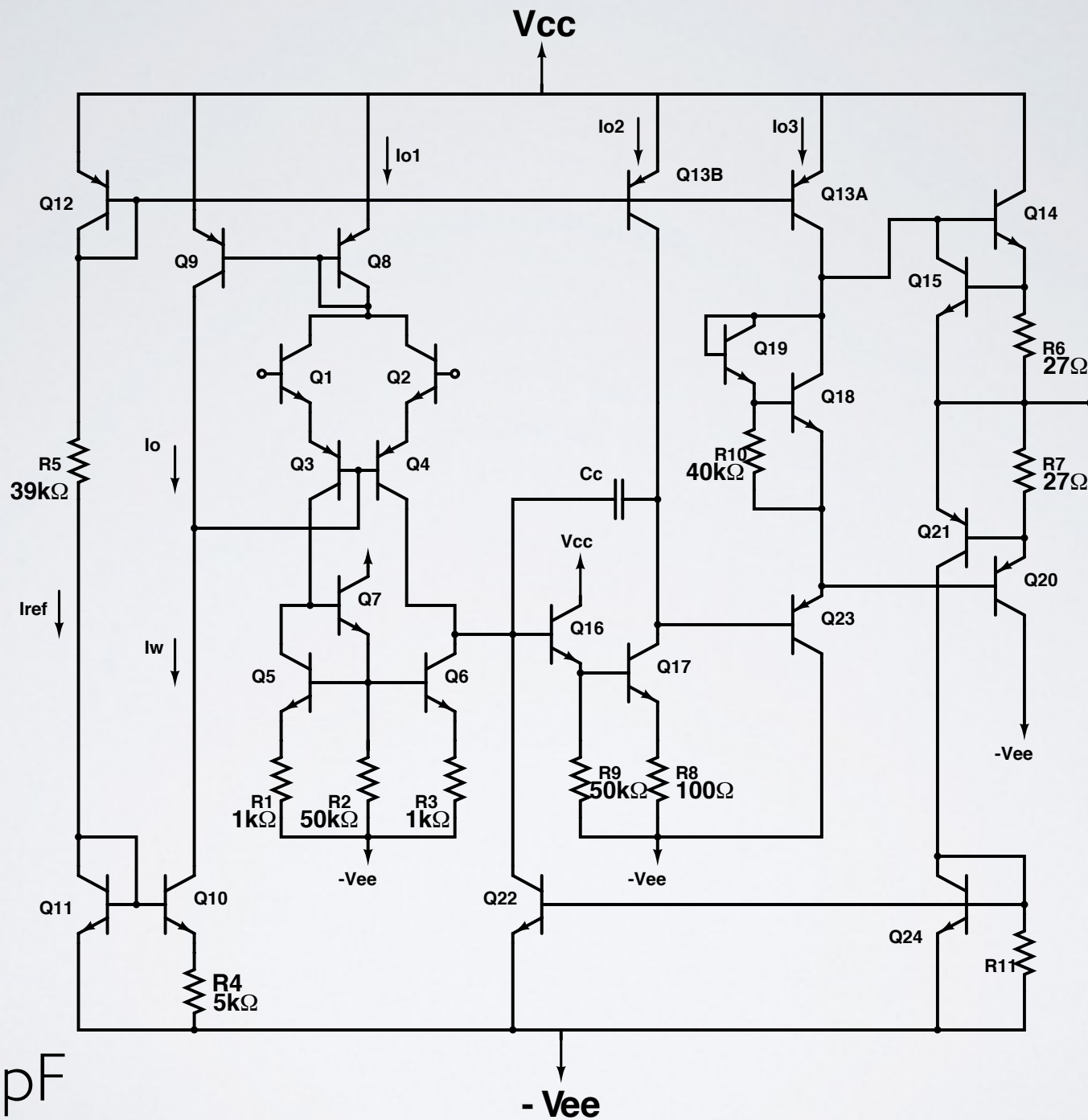

$C_c = 30\text{pF}$

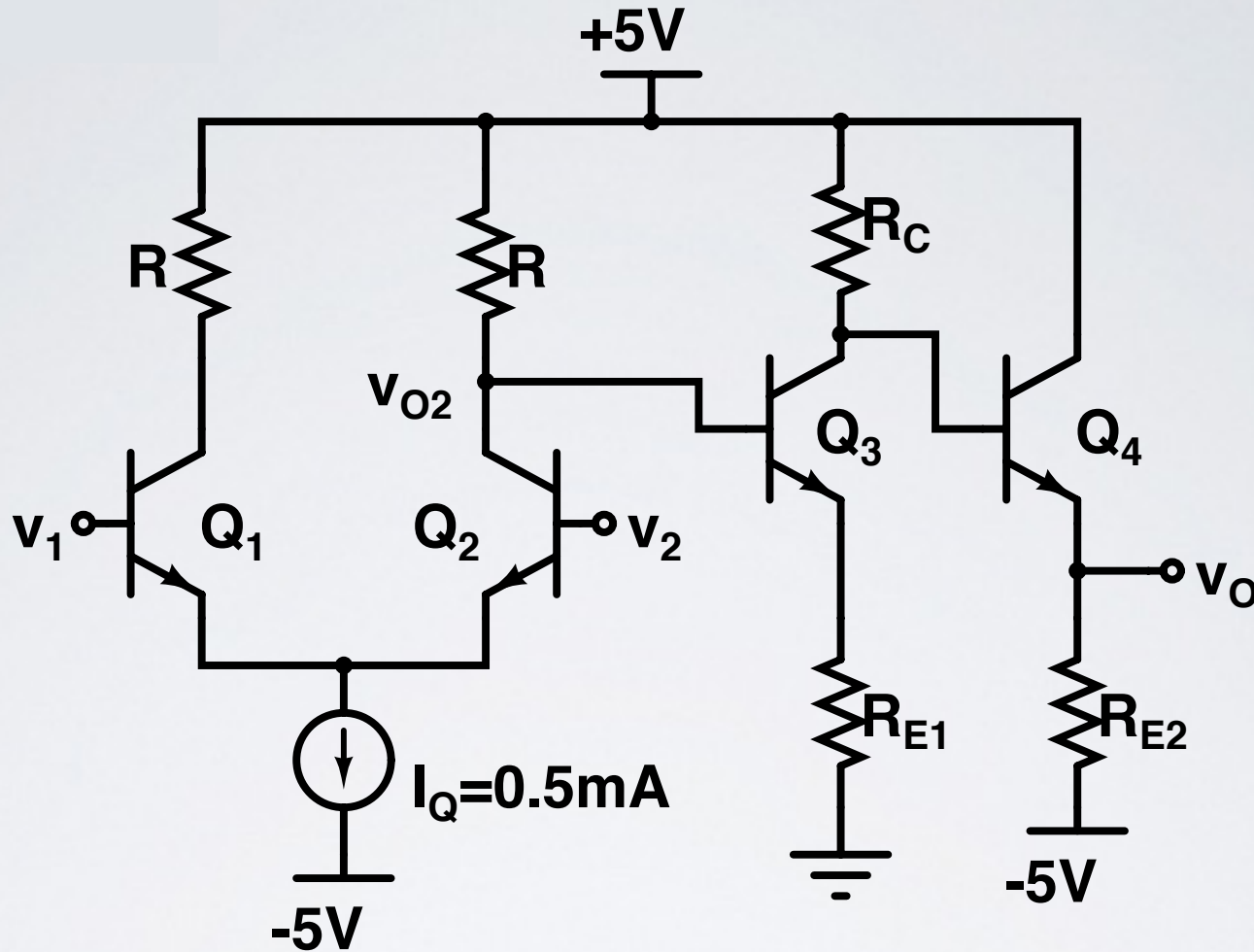

Assume $h_{FE} = 100$, $V_{BE} = 0.7V$, $V_A = \infty$, $R_{O(CS)} = 100k\Omega$ (a) For $v_1 = v_2 = 0V$, design so that $v_{O2} = 2V$, $v_{C3} = 3V$, $I_{CQ3} = 0.5mA$, $I_{CQ4} = 3mA$; (b) Find $A_{d1} = v_{O2}/v_d$ & $A_d = v_O/v_d$; c) Find $A_{cm1} = v_{O2}/v_{cm}$ and $A_{cm} = v_O/v_{cm}$, and the overall CMRR


****2.69** To obtain a high-gain, high-input-resistance difference amplifier, the circuit in Fig. P2.69 employs positive feedback, in addition to the negative feedback provided by the resistor R connected from the output to the negative input of the op amp. Specifically, a voltage divider (R_5 , R_6) connected across the output feeds a fraction β of the output, that is, a voltage βv_O , back to the positive-input terminal of the op amp through a resistor R . Assume that R_5 and R_6 are much smaller than R so that the current through R is much lower than the current in the voltage divider, with the result that $\beta \approx R_6 / (R_5 + R_6)$. Show that the differential gain is given by

$$A_d \equiv \frac{v_O}{v_{Id}} = \frac{1}{1 - \beta}$$

(Hint: Use superposition.)


Design the circuit to obtain a differential gain of 10 V/V and differential input resistance of 2 M Ω . Select values for R , R_5 , and R_6 , such that $(R_5 + R_6) \leq R/100$.

P2.69

 

D *8.121** In the CMOS op amp shown in Fig. P8.121, all MOS devices have $|V_t| = 1$ V, $\mu_n C_{ox} = 2\mu_p C_{ox} = 40 \mu\text{A}/\text{V}^2$, $|V_A| = 50$ V, and $L = 5 \mu\text{m}$. Device widths are indicated on the diagram as multiples of W , where $W = 5 \mu\text{m}$.

- Design R to provide a $10\text{-}\mu\text{A}$ reference current.
- Assuming $v_o = 0$ V, as established by external feedback, perform a bias analysis, finding all the labeled node voltages, V_{GS} and I_D for all transistors.
- Provide in table form I_D , V_{GS} , g_m , and r_o for all devices.
- Calculate the voltage gain $v_o/(v_+ - v_-)$, the input resistance, and the output resistance.
- What is the input common-mode range?
- What is the output signal range for no load?
- For what load resistance connected to ground is the output negative voltage limited to -1 V before Q_7 begins to conduct?
- For a load resistance one-tenth of that found in (g), what is the output signal swing?

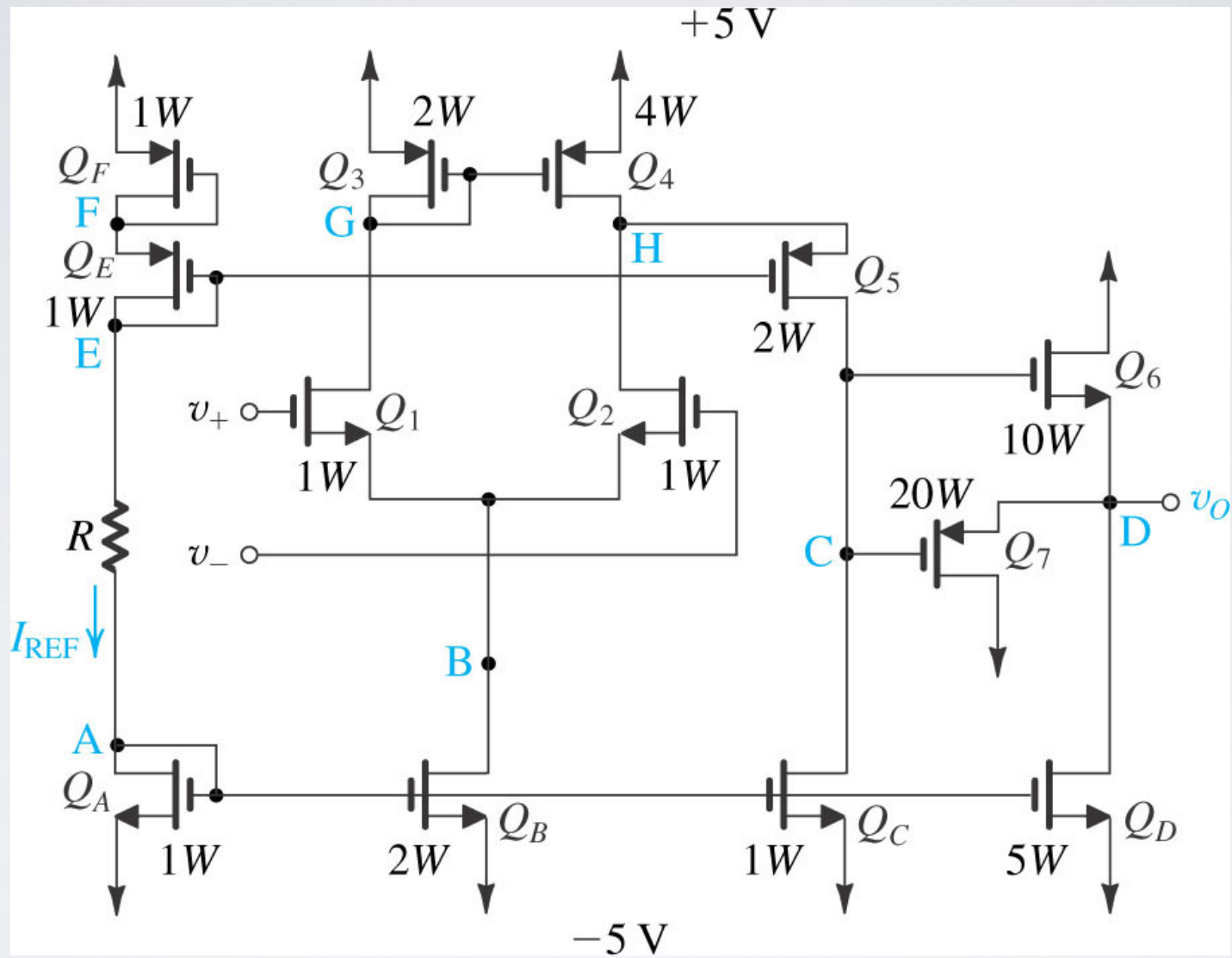

D *12.63 Figure P12.63 shows a circuit suitable for op-amp applications. For all transistors $\beta = 100$, $V_{BE} = 0.7$ V, and $r_o = \infty$.

- For inputs grounded and output held at 0 V (by negative feedback) find the collector currents of all transistors. Neglect base currents.
- Calculate the input resistance.
- Calculate the gain of the amplifier with a load of 5 k Ω .
- With load as in (c) calculate the value of the capacitor C required for a 3-dB frequency of 100 Hz.

P12.63

