

Sequential Circuit Design

COE 202

Digital Logic Design

Dr. Muhamed Mudawar

King Fahd University of Petroleum and Minerals

Presentation Outline

- ❖ The Design Procedure
- ❖ Moore Sequence Detector
- ❖ Mealy Sequence Detector
- ❖ Tracing State Diagrams and Verifying Correctness
- ❖ Sequential Comparator
- ❖ Binary Counter
- ❖ Up/Down Counter with Enable

The Design Procedure

Given a Description (or Specification) of the Problem

1. Obtain a state diagram for the sequential circuit
2. Assign binary codes to the states and fill the state table
3. Select the type of Flip-Flops and derive the FF input equations
4. Derive the output equations
5. Draw the circuit diagram
6. Verify the correctness of the final design (verification)

The State Diagram

- ❖ A **state** is an abstraction of memory
- ❖ A state **remembers** a history of inputs applied to the circuit
- ❖ Examples:
 - ✧ State **S0** represents the fact that the last input is a **0**
 - ✧ State **S1** represents the fact that the last input is a **1**
 - ✧ State **S2** represents the fact that the last two-input sequence is **"11"**
- ❖ Obtaining the state diagram is the most important step
- ❖ Requires experience and good understanding of the problem

Example: Sequence Detector

- ❖ A sequence detector is a sequential circuit
- ❖ Detects a specific sequence of bits in the input
- ❖ The input is a serial **bit stream**:

One input bit x is fed to the sequence detector each cycle


- ❖ The output is also a **bit stream**: One output bit z each cycle

Indicates whether a given sequence is detected or not



State Diagram for a Sequence Detector

- ❖ Example: Design a circuit that detects the input sequence "111"
- ❖ Begin in an initial state: call it S_0
 S_0 indicates that a **1** is NOT detected yet
As long as the input x is **0**, remain in the initial state S_0
- ❖ Add a state (call it S_1) that detects the first **1** in the input
- ❖ Add a state (call it S_2) that detects the input sequence "11"
- ❖ Add a state (call it S_3) that detects the input sequence "111"

 

Complete the State Diagram

Moore Design: Assign Output to States


The output in S_0 , S_1 , and S_2 should be **0**

The output in S_3 should be **1**

Now complete the state diagram:

Add transitions from S_1 , S_2 , S_3
back to S_0 if the input is **0**

 Add transition from S_3 to itself if
the input is **1** to detect sequences
longer than three **1**'s



State Assignment

- ❖ Each state must be assigned a unique binary code

- ❖ If there are m states then

The minimum number of state bits: $n = \lceil \log_2 m \rceil$

$\lceil x \rceil$ is the smallest integer $\geq x$ (ceiling function)

- ❖ In our example, there are four states: **S₀**, **S₁**, **S₂**, and **S₃**


Therefore, the minimum number of state bits (Flip-Flops) = 2

- ❖ State assignment: **S₀ = 00**, **S₁ = 01**, **S₂ = 10** and **S₃ = 11**

- ❖ If n bits are used, the number of unused states = $2^n - m$

- ❖ In our example, there are NO unused states

From State Diagram to State Table

 


State Assignment
 $S_0 = 00, S_1 = 01$
 $S_2 = 10, S_3 = 11$

Present State	Next State		Output z
	$x = 0$	$x = 1$	
S_0	S_0	S_1	0
S_1	S_0	S_2	0
S_2	S_0	S_3	0
S_3	S_0	S_3	1

Present State	Next State		Output z
	$x = 0$	$x = 1$	
00	00	01	0
01	00	10	0
10	00	11	0
11	00	11	1

Structure of a Moore Sequence Detector

 

- ❖ In our design examples, only D-type Flip-Flops will be used
- ❖ They are the simplest to analyze and implement
- ❖ Next, we need minimal expressions for
 1. Next State Logic
 2. Output Logic

Derive Next State and Output Equations

Present State	Next State		Output z
	$x = 0$	$x = 1$	
00	00	01	0
01	00	10	0
10	00	11	0
11	00	11	1

		D_1	
		0	1
$Q_1 Q_0$	00	0	0
	01	0	1
11	0	1	
10	0	1	

$$Q_1 x + Q_0 x$$

		D_0	
		0	1
$Q_1 Q_0$	00	0	1
	01	0	0
11	0	1	
10	0	1	

$$Q_1 x + Q_0' x$$

Two D-type Flips-Flops

Present State = Flip-Flop Outputs Q_1 and Q_0

Next State = Flip-Flop Inputs D_1 and D_0


Next State equations: $D_1 = Q_1 x + Q_0 x$ and $D_0 = Q_1 x + Q_0' x$

Output equation: $z = Q_1 Q_0$ (from the state diagram)

Draw the Moore Sequence Detector Circuit


$$D_1 = Q_1 x + Q_0 x, \quad D_0 = Q_1 x + Q_0' x$$

$$z = Q_1 Q_0$$

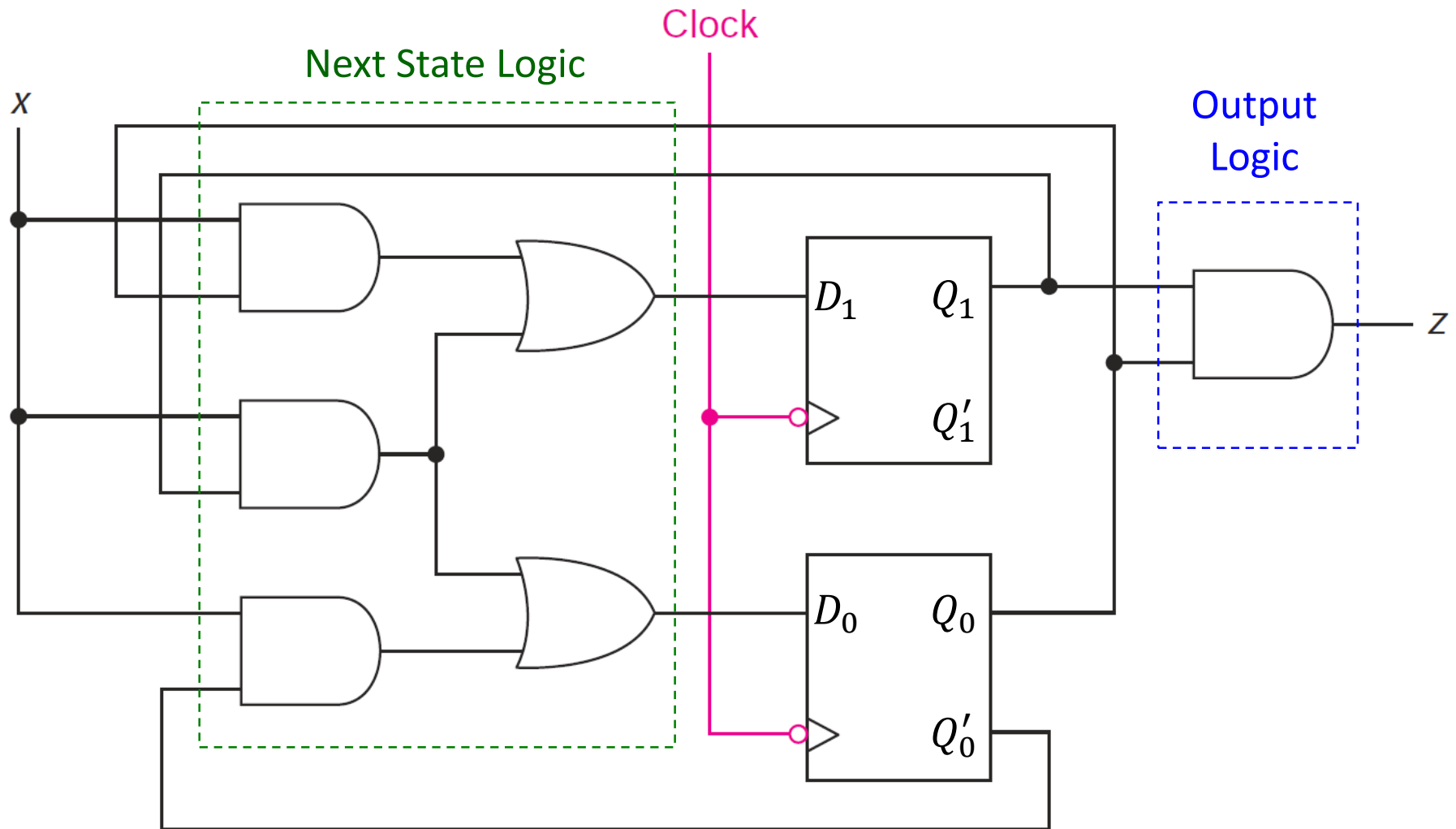

Mealy Type Sequence Detector

 - ❖ Let us redesign a Mealy type "111" sequence detector
- ❖ The initial state S_0 indicates that a 1 is NOT detected yet
 - As long as the input x is 0, remain in the initial state S_0
 - Notice that **input / output** is written on the arc (Mealy type)
- ❖ Add a state (call it S_1) that detects the first 1 in the input
- ❖ Add a state (call it S_2) that detects the input sequence "11"



Complete the Mealy State Diagram

❖ State S_2 is reached after detecting the input sequence "11"


❖ At S_2 , if the next input is 1 then the output should be 1

Make a transition from S_2 back to itself labeled 1 / 1

No need for state S_3 , because output is on the arc

❖ Now complete the state diagram

 Add transitions from S_1 and S_2 back to S_0 when input is 0




Mealy Machines
typically use
less states than
Moore Machines

State Assignment and State Table

Three States → Minimum number of state bits (Flip-Flops) = 2

 Assign: $S_0 = 00$, $S_1 = 01$, and $S_2 = 10$ (State 11 is **Unused**)




Present State	Next State		Output z	
	x = 0	x = 1	x = 0	x = 1
S_0	S_0	S_1	0	0
S_1	S_0	S_2	0	0
S_2	S_0	S_2	0	1



Present State	Next State		Output z	
	x = 0	x = 1	x = 0	x = 1
00	00	01	0	0
01	00	10	0	0
10	00	10	0	1

Derive Next State and Output Equations

Present State	Next State		Output z	
	x = 0	x = 1	x = 0	x = 1
00	00	01	0	0
01	00	10	0	0
10	00	10	0	1
11	XX	XX	X	X

 

Present State = Flip-Flop Outputs Q_1 and Q_0 (state 11 is unused)

Next State = Flip-Flop Inputs D_1 and D_0

Flip-Flop Input equations: $D_1 = Q_1 x + Q_0 x$ and $D_0 = Q_1' Q_0' x$


Output equation: $z = Q_1 x$

Draw the Mealy Sequence Detector Circuit

$$D_1 = Q_1 x + Q_0 x$$


$$D_0 = Q_1' Q_0' x$$

$$z = Q_1 x$$

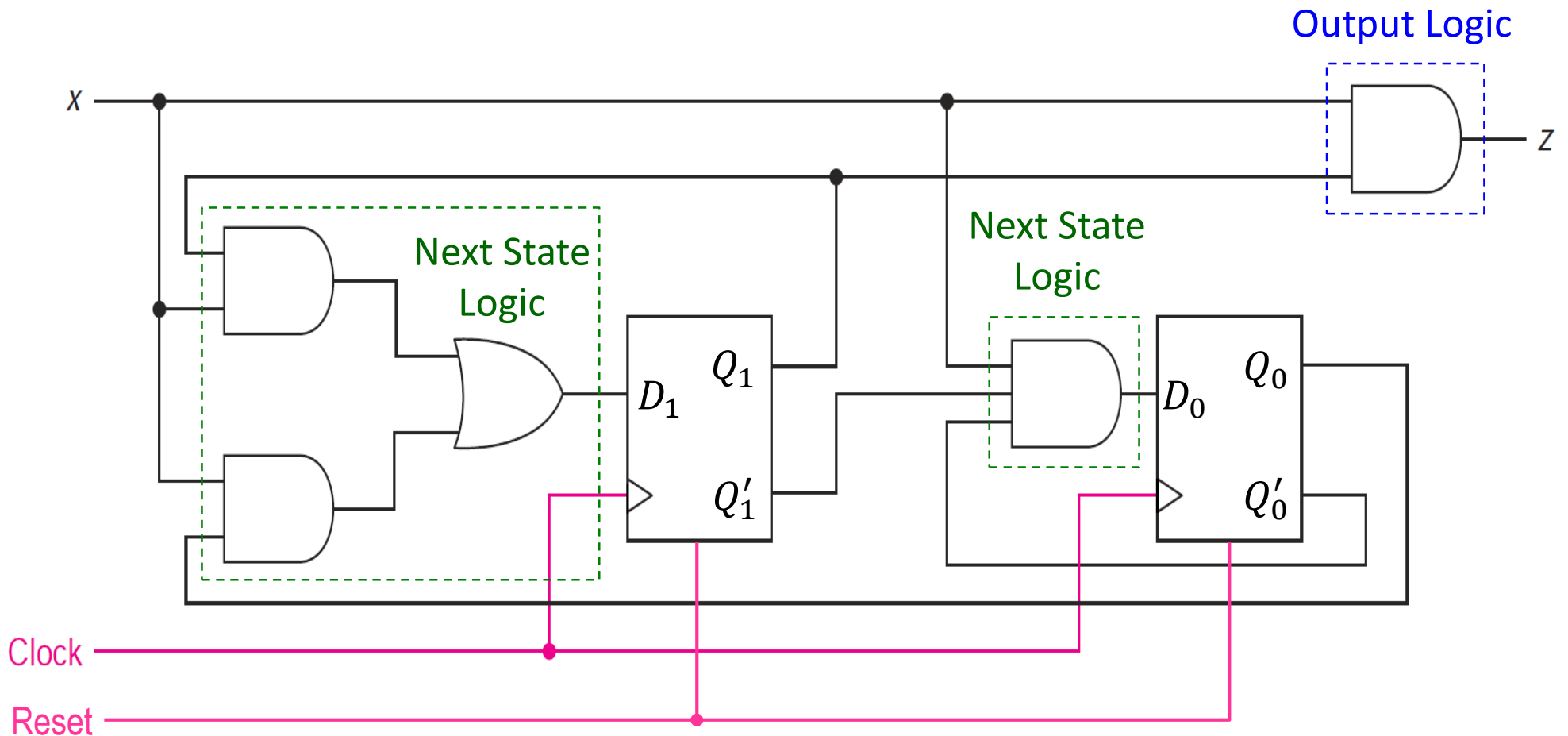

Mealy versus Moore Sequence Detector


Mealy Sequence Detector

 

In general, Moore state diagrams have **more states** than corresponding Mealy.

The drawback of Mealy is that **glitches** can appear in the output if the input is not synchronized with the clock.

Moore Sequence Detector

 


Verification

- ❖ Sequential circuits should be verified by showing that the circuit produces the original state diagram
- ❖ Verification can be done manually, or with the help of a simulation program
- ❖ All possible input combinations are applied at each state and the state variables and outputs are observed
- ❖ A **reset** input is used to reset the circuit to its initial state
- ❖ Apply a sequence of inputs to test all the state-input combinations, i.e., **all transitions** in the state diagram
- ❖ Observe the output and the next state that appears after each clock edge in the timing diagram


Input Test Sequence

- ❖ Required to verify the correct operation of a sequential circuit
- ❖ It should test each state transition of the state diagram
- ❖ Test sequences can be produced from the state diagram
- ❖ Consider the Mealy sequence detector, starting at S_0 (**reset**), we can use an input test sequence to verify all state transitions:

 
Input test sequence: reset then $x = 0, 1, 0, 1, 1, 0, 1, 1, 1, 1$



Verifying the Mealy Sequence Detector

 

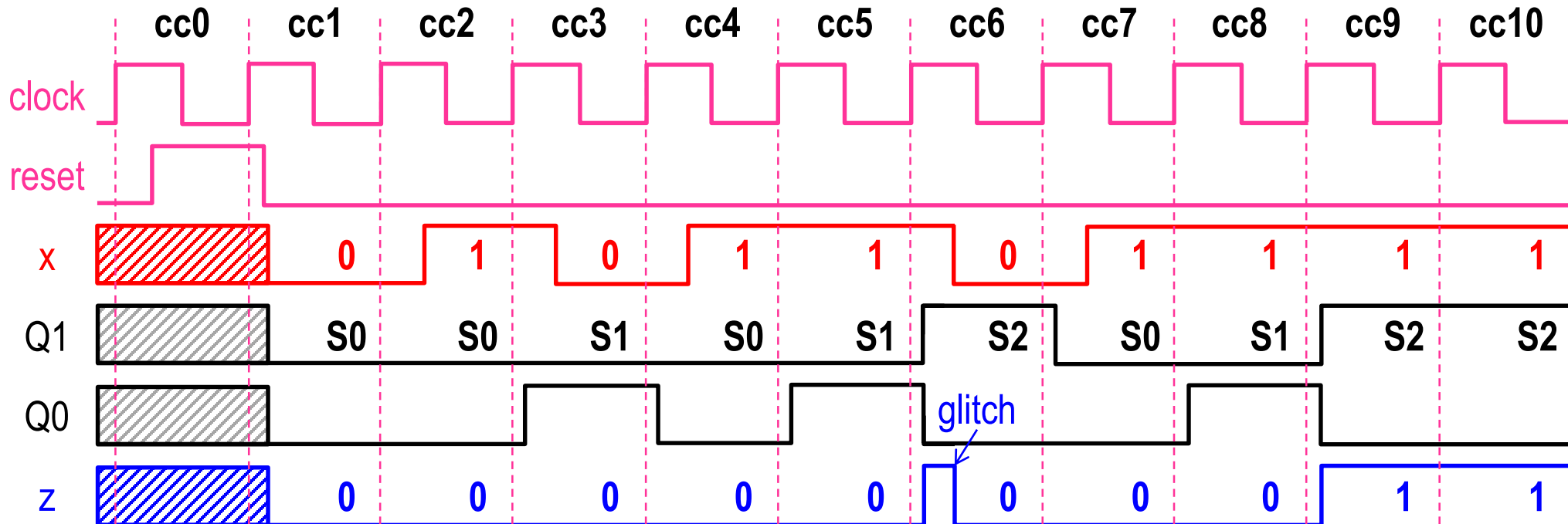Input test sequence: **reset** then $x = 0, 1, 0, 1, 1, 0, 1, 1, 1, 1$



Sequential Comparator

Problem Description:

❖ Design a sequential circuit that compares two numbers A and B

❖ Two Inputs: A and B

A consists of n bits

B consists of n bits


Bit streaming starting at bit 0

Compare A_0 with B_0 , A_1 with B_1 , etc. (Bit 0 is least significant bit)

❖ A reset signal resets the comparator to its initial state

Reset is required before starting a new comparison

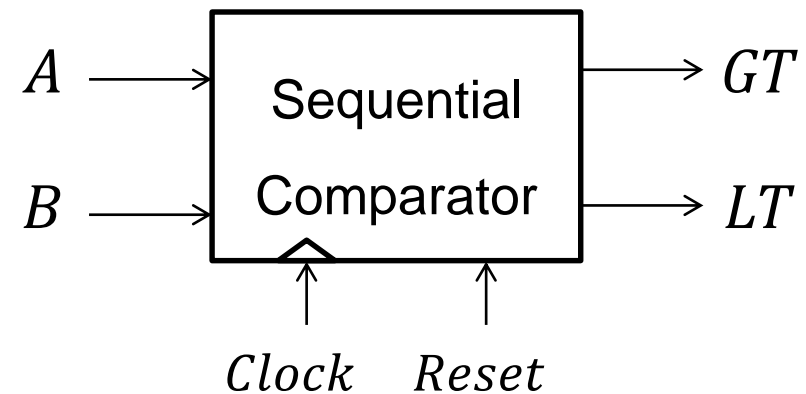❖ Two outputs: GT (Greater Than) and LT (Less Than)



Designing the State Diagram

- ❖ Reset: start initially in state **EQ**

EQ indicates Equality (output is **00**)

Stay in **EQ** as long as $A_i B_i = \mathbf{00}$ or $\mathbf{11}$

- ❖ Go to **LT** if $A_i < B_i$ ($A_i B_i = \mathbf{01}$)

LT indicates Less Than (output is **01**)

- ❖ Go to **GT** if $A_i > B_i$ ($A_i B_i = \mathbf{10}$)


GT is Greater Than (output is **10**)

- ❖ Complete the state diagram

LT \rightarrow **GT** and **GT** \rightarrow **LT**

LT \rightarrow **LT** and **GT** \rightarrow **GT**

Moore State Diagram

 

State Assignment and State Table


Three States → Two Flip-Flops

D-type Flip-Flops will be used

State Assignment: **EQ** = 00, **LT** = 01, **GT** = 10

Output = Present State (Q_1 and Q_0)

Present State $Q_1 Q_0$	Next State ($D_1 D_0$)			
	A B 0 0	A B 0 1	A B 1 0	A B 1 1
0 0	0 0	0 1	1 0	0 0
0 1	0 1	0 1	1 0	0 1
1 0	1 0	0 1	1 0	1 0
1 1	X X	X X	X X	X X

 

Deriving the Next State Equations

Present State $Q_1 Q_0$	Next State ($D_1 D_0$)			
	AB	AB	AB	AB
	00	01	10	11
00	00	01	10	00
01	01	01	10	01
10	10	01	10	10
11	X X	X X	X X	X X

State 11 is **unused**

When present state is 11, **don't cares** are used to fill the next state.

Output = Present state

D_1

$Q_1 Q_0 \backslash AB$	00	01	11	10
00	0	0	0	1
01	0	0	0	1
11	X	X	X	X
10	1	0	1	1

D_0

$Q_1 Q_0 \backslash AB$	00	01	11	10
00	0	1	0	0
01	1	1	1	0
11	X	X	X	X
10	0	1	0	0

$$D_1 = Q_1 A + Q_1 B' + AB'$$

$$D_1 = Q_1 (A + B') + AB'$$


$$D_0 = Q_0 A' + Q_0 B + A'B$$

$$D_0 = Q_0 (A' + B) + A'B$$

Sequential Comparator Circuit Diagram

$$D_1 = Q_1(A + B') + AB'$$

$$D_0 = Q_0(A' + B) + A'B$$

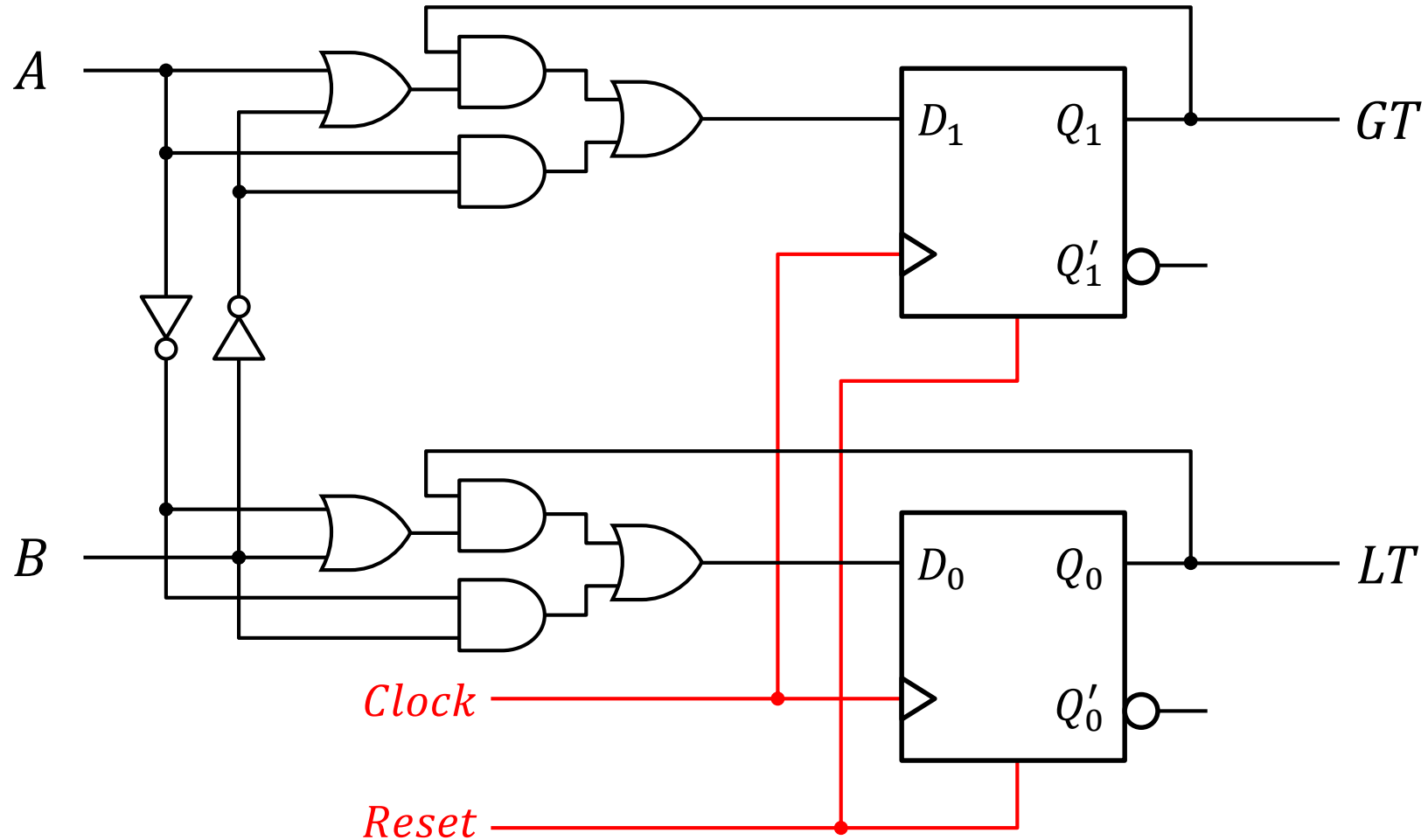

Designing with Unused States

- ❖ A circuit with n flip-flops has 2^n binary states
- ❖ However, the state diagram may have m states
- ❖ Therefore, the number of unused states = $2^n - m$
- ❖ Unused states do not appear in the state diagram
 - ✧ Sometimes treated as don't cares when simplifying expressions in K-maps
- ❖ However, it is possible to enter an unused state!
 - ✧ Caused by outside interference or a circuit malfunction
- ❖ Must specify the output and next state values for unused states
- ❖ A special (invalid) output can be used to indicate an unused state
- ❖ A return to a valid state must be possible without reset
 - ✧ Next state for unused states should be specified (NOT don't cares!)

Design of a Binary Counter

Problem Specification:

- ❖ Design a circuit that counts up from 0 to 7 then back to 0


000 → 001 → 010 → 011 → 100 → 101 → 110 → 111 → 000

When reaching 7, the counter goes back to 0 then goes up again

- ❖ There is no input to the circuit
- ❖ The counter is incremented each cycle
- ❖ The output of the circuit is the present state (count value)
- ❖ The circuit should be designed using D-type Flip-Flops

Designing the State Diagram

 - ❖ Eight states are needed to store the count values 0 to 7
- ❖ No input, state transition happens at the edge of each cycle




Three Flip-Flops
are required for
the eight states

Each state is
assigned a unique
binary count value

State Table

Only two columns: Present State and Next State

State changes each cycle

 

Present State			Next State		
Q_2	Q_1	Q_0	D_2	D_1	D_0
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

Deriving the Next State Equations

Present State			Next State		
Q_2	Q_1	Q_0	D_2	D_1	D_0
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

		D_2	
		Q_0	
Q_2Q_1	Q_0	0	1
00		0	0
01		0	1
11		1	0
10		1	1

		D_1	
		Q_0	
Q_2Q_1	Q_0	0	1
00		0	1
01		1	0
11		1	0
10		0	1

		D_0	
		Q_0	
Q_2Q_1	Q_0	0	1
00		1	0
01		1	0
11		1	0
10		1	0

$$D_2 = Q_2Q_1' + Q_2Q_0' + Q_2'Q_1Q_0$$

$$D_2 = Q_2(Q_1' + Q_0') + Q_2'Q_1Q_0$$

$$D_2 = Q_2(Q_1Q_0)' + Q_2'(Q_1Q_0) = Q_2 \oplus (Q_1Q_0)$$

$$D_1 = Q_1Q_0' + Q_1'Q_0 = Q_1 \oplus Q_0$$


$$D_0 = Q_0'$$

3-Bit Counter Circuit Diagram

$$D_2 = Q_2 \oplus (Q_1 Q_0)$$

$$D_1 = Q_1 \oplus Q_0$$

$$D_0 = Q_0'$$

 

Output = 3-bit Count Value


Up/Down Counter with Enable

Problem Specification:

- ❖ Design a 2-bit Up / Down counter
- ❖ Two inputs: E (Enable) and U (Up)
 - If $E = 0$ then counter remains in the same state (regardless of U)
 - If $EU = 11$ then count up from 0 to 3, then back to 0
 - If $EU = 10$ then count down from 3 down to 0, then back to 3
- ❖ The output of the counter is the present state (count value)
- ❖ The circuit should be designed using T Flip-Flops
- ❖ A reset signal resets the counter to its initial state


Designing the State Diagram

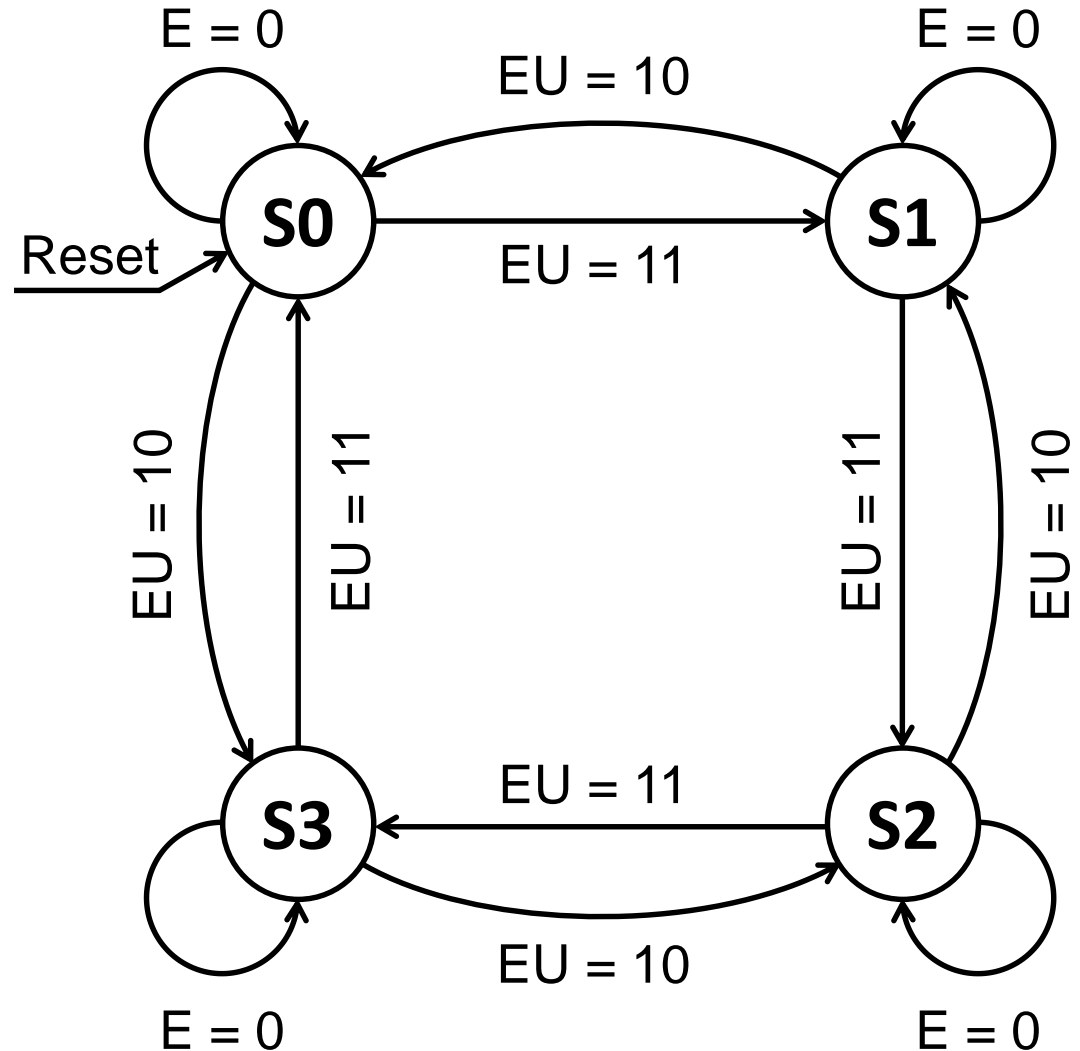- ❖ Four states are required to store the count 0 to 3
- ❖ Count up if $EU = 11$
- ❖ Count down if $EU = 10$
- ❖ Disable counter if $E = 0$
Transition to same state if $EU = 00$ or 01
- ❖ Asynchronous reset to start initially at state $S0$



State Assignment and State Table

 - ❖ Four States → Two State variables (2 Flip-Flops)
- ❖ State Assignment: $S_0 = 00$, $S_1 = 01$, $S_2 = 10$, and $S_3 = 11$



Present State $Q_1 Q_0$	Next State			
	EU 00	EU 01	EU 10	EU 11
00	00	00	11	01
01	01	01	00	10
10	10	10	01	11
11	11	11	10	00

Excitation Table for Flip-Flops

❖ Excitation Table:

Lists the required input for next state transition

❖ For D Flip-Flop: Input $D = \text{Next State } Q(t + 1)$

❖ For T Flip-Flop: Input $T = Q(t) \oplus Q(t + 1)$

❖ Excitation tables are used to find the Flip-Flop input equations

Excitation Tables for the D and T Flip-Flops

$Q(t)$	$Q(t + 1)$	D
0	0	0
0	1	1
1	0	0
1	1	1

$Q(t)$	$Q(t + 1)$	T
0	0	0
0	1	1
1	0	1
1	1	0

Deriving the T-Flip-Flop Input Equations

Present State $Q_1 Q_0$	Next State at $(t+1)$			
	EU 00	EU 01	EU 10	EU 11
00	00	00	11	01
01	01	01	00	10
10	10	10	01	11
11	11	11	10	00



Present State $Q_1 Q_0$	Flip-Flop Inputs $T_1 T_0$			
	EU 00	EU 01	EU 10	EU 11
00	00	00	11	01
01	00	00	01	11
10	00	00	11	01
11	00	00	01	11

$Q_1 Q_0$	T_1			
	EU 00	EU 01	EU 11	EU 10
00	0	0	0	1
01	0	0	1	0
11	0	0	1	0
10	0	0	0	1

$Q_1 Q_0$	T_0			
	EU 00	EU 01	EU 11	EU 10
00	0	0	1	1
01	0	0	1	1
11	0	0	1	1
10	0	0	1	1

$$T_1 = Q_0 EU + Q_0' EU'$$

$$T_1 = E(Q_0 \oplus U)'$$

$$T_0 = E$$

2-bit Up/Down Counter Circuit Diagram

