

# Series Circuits

## Topics Covered in Chapter 4

- 4-1: Why  $I$  Is the Same in All Parts of a Series Circuit
- 4-2: Total  $R$  Equals the Sum of All Series Resistances
- 4-3: Series  $IR$  Voltage Drops
- 4-4: Kirchhoff's Voltage Law (KVL)
- 4-5: Polarity of  $IR$  Voltage Drops

# Topics Covered in Chapter 4

- 4-6: Total Power in a Series Circuit
- 4-7: Series-Aiding and Series-Opposing Voltages
- 4-8: Analyzing Series Circuits with Random Unknowns
- 4-9: Ground Connections in Electrical and Electronic Systems
- 4-10: Troubleshooting: Opens and Shorts in Series Circuits

# 4-1: Why $I$ Is the Same in All Parts of a Series Circuit

- Characteristics of a Series Circuit
  - The current is the same everywhere in a series circuit.
  - The total resistance is equal to the sum of the individual resistance values.
  - The total voltage is equal to the sum of the  $IR$  voltage drops across the individual resistances.
  - The total power is equal to the sum of the power dissipated by each resistance.

## 4-1: Why $I$ Is the Same in All Parts of a Series Circuit

- Current is the movement of electric charge between two points, produced by the applied voltage.
- The free electrons moving away from one point are continuously replaced by free electrons flowing from an adjacent point in the series circuit.
- All electrons have the same speed as those leaving the voltage source.
- Therefore,  $I$  is the same in all parts of a series circuit.

# 4-1: Why $I$ Is the Same in All Parts of a Series Circuit

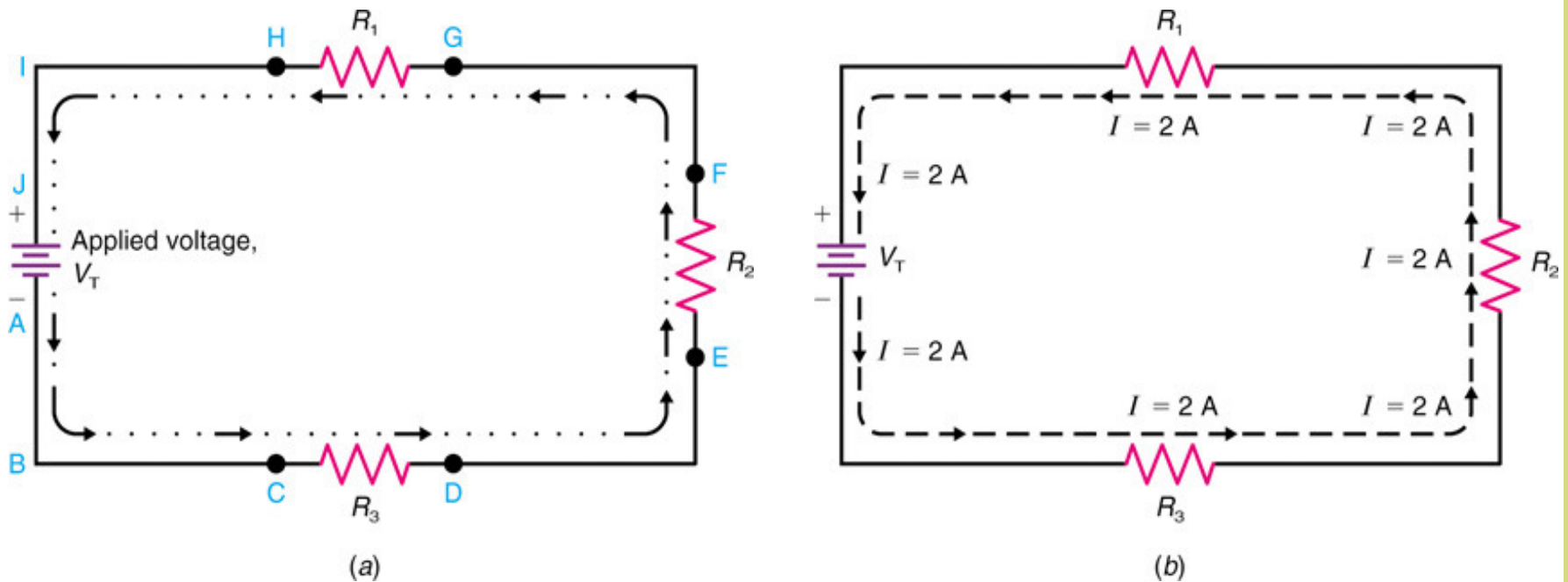


Fig. 4-2: There is only one current through  $R_1$ ,  $R_2$ , and  $R_3$  in series. (a) Electron drift is the same in all parts of a series circuit. (b) Current  $I$  is the same at all points in a series circuit.

# 4-1: Why $I$ Is the Same in All Parts of a Series Circuit

- Series Current Formulas

- Total current is the same as the individual currents in the series string:

$$I_T = I_1 = I_2 = I_3 = \dots = \text{etc.}$$

- Total current is equal to total voltage divided by total resistance:

$$I_T = \frac{V_T}{R_T}$$

## 4-2: Total $R$ Equals the Sum of All Series Resistances

- When a series circuit is connected across a voltage source, the free electrons must drift through all the series resistances.
- There is only one path for free electrons to follow.
- If there are two or more resistances in the same current path, the total resistance across the voltage source is the sum of all the resistances.

## 4-2: Total $R$ Equals the Sum of All Series Resistances


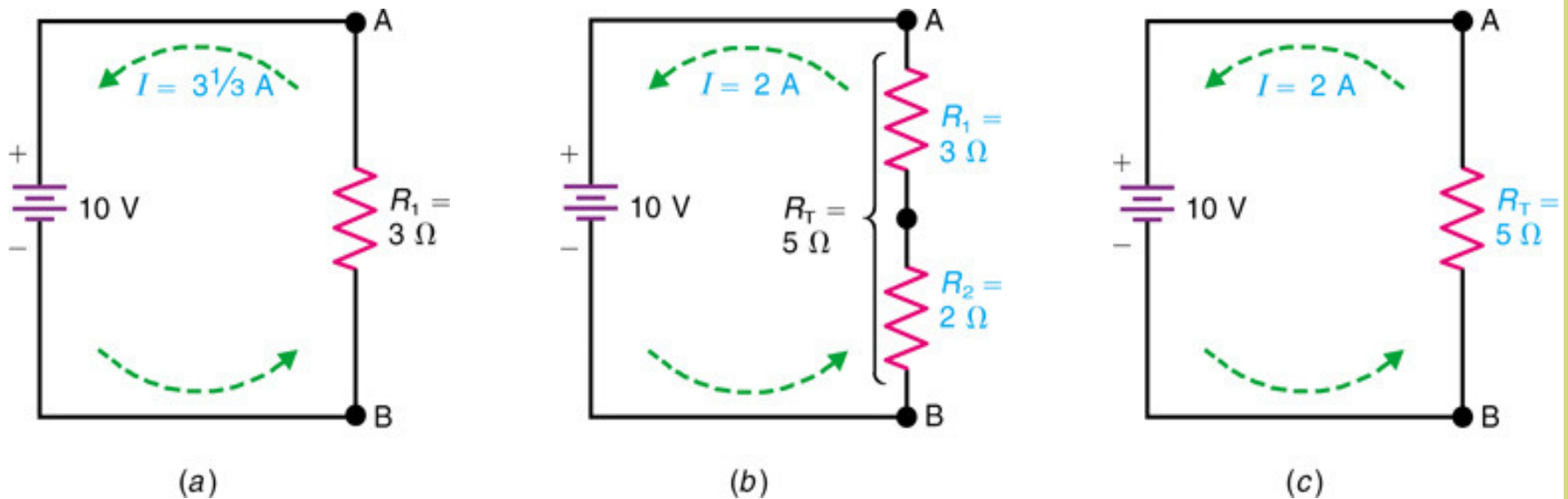


Fig. 4-4: Series resistances are added for the total  $R_T$ . (a)  $R_1$  alone is  $3 \Omega$ . (b)  $R_1$  and  $R_2$  in series together total  $5 \Omega$ . (c) The  $R_T$  of  $5 \Omega$  is the same as one resistance of  $5 \Omega$  between points A and B.

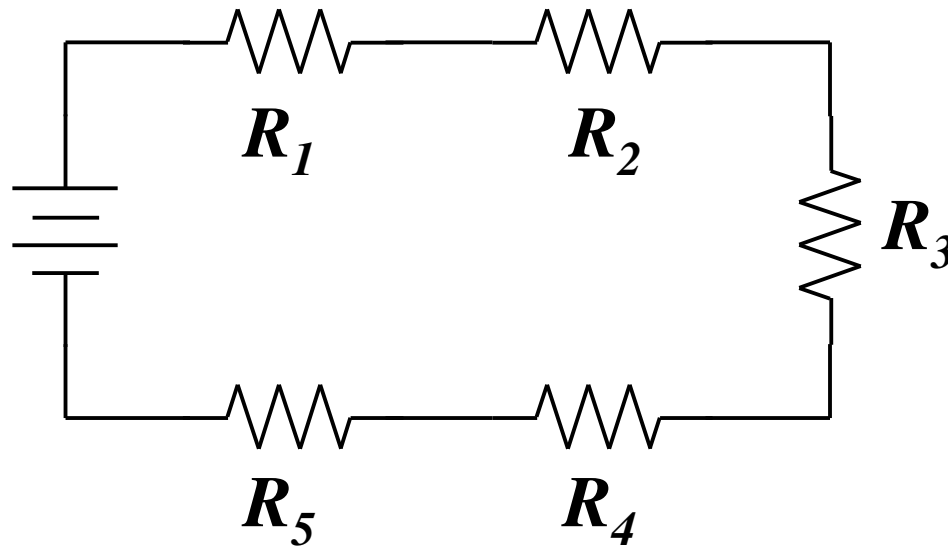

## 4-2: Total $R$ Equals the Sum of All Series Resistances

- Series Resistance Formulas
  - The total resistance is the sum of the individual resistances.



$$R_T = R_1 + R_2 + R_3 + R_4 + R_5$$


## 4-2: Total $R$ Equals the Sum of All Series Resistances

- Series Resistance Formulas
  - Total resistance is equal to total voltage divided by the circuit current:

$$R_T = \frac{V_T}{I_T}$$

## 4-2: Total $R$ Equals the Sum of All Series Resistances

- Determining the Total Resistance

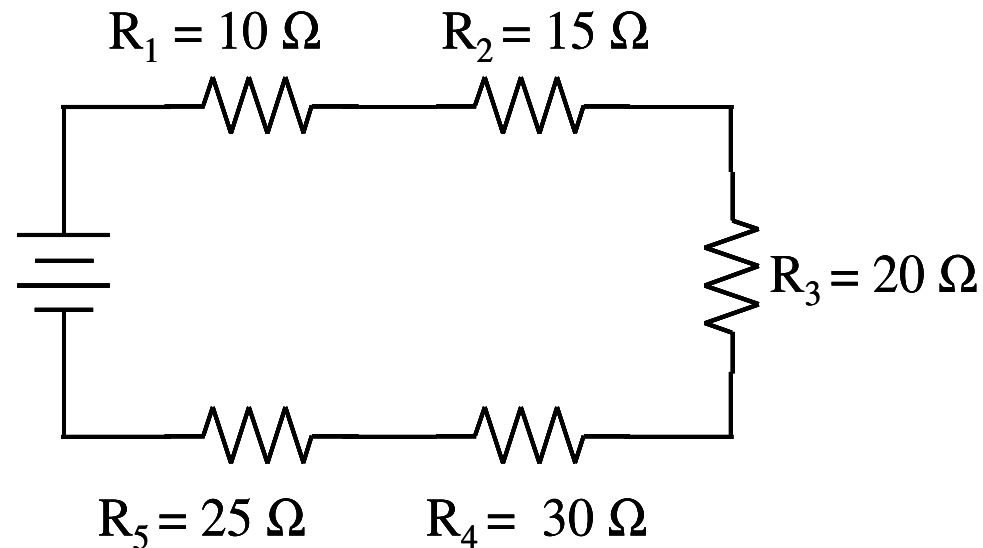

$$R_T = R_1 + R_2 + R_3 + R_4 + R_5$$

$$R_T = 10 \Omega + 15 \Omega + 20 \Omega + 30 \Omega + 25 \Omega = 100 \Omega$$

## 4-3: Series $IR$ Voltage Drops

- By Ohm's Law, the voltage across a resistance equals  $I \times R$ .
- In a series circuit, the  $IR$  voltage across each resistance is called an  **$IR$  drop** or **voltage drop**, because it reduces the potential difference available for the remaining resistances in the circuit.

# 4-3: Series $IR$ Voltage Drops


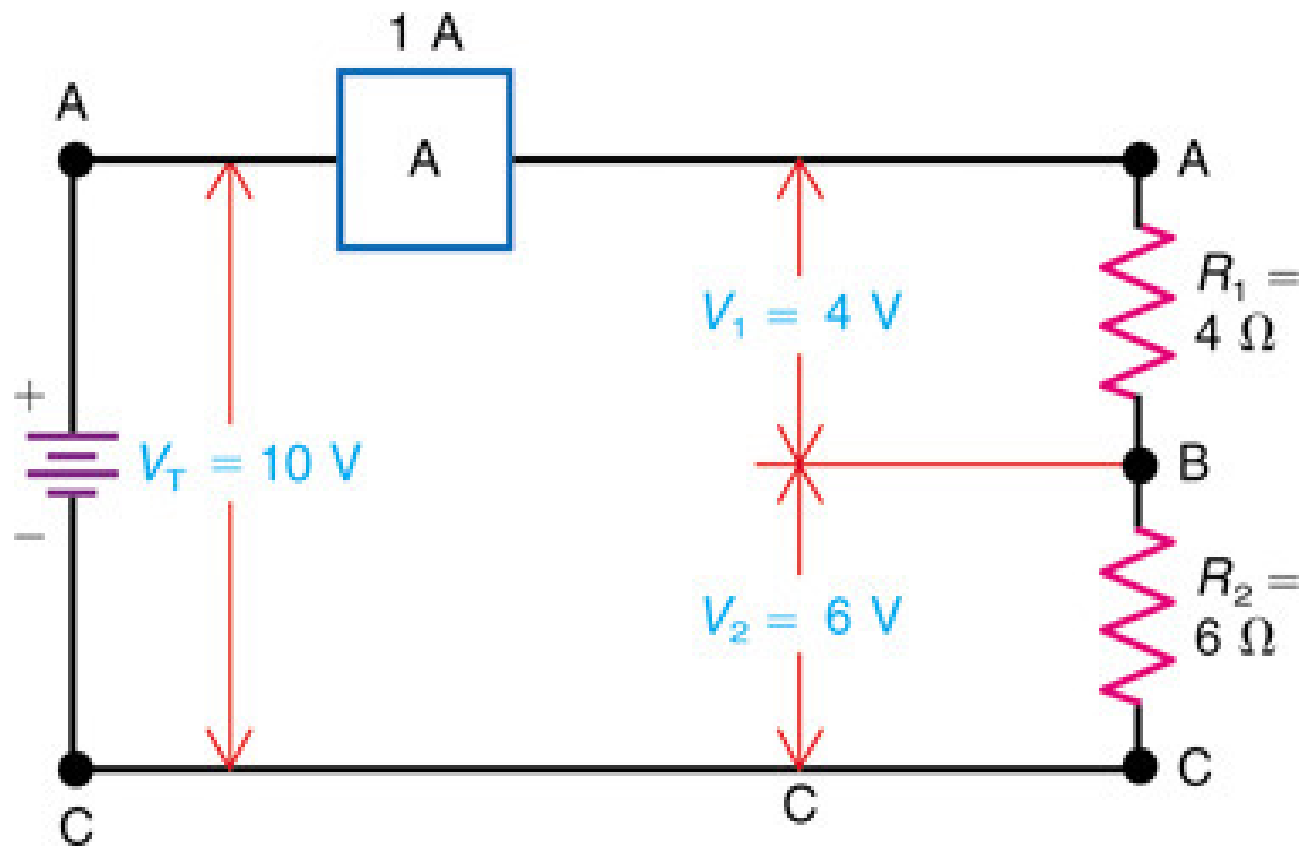


Fig. 4-5: An example of  $IR$  voltage drops  $V_1$  and  $V_2$  in a series circuit.
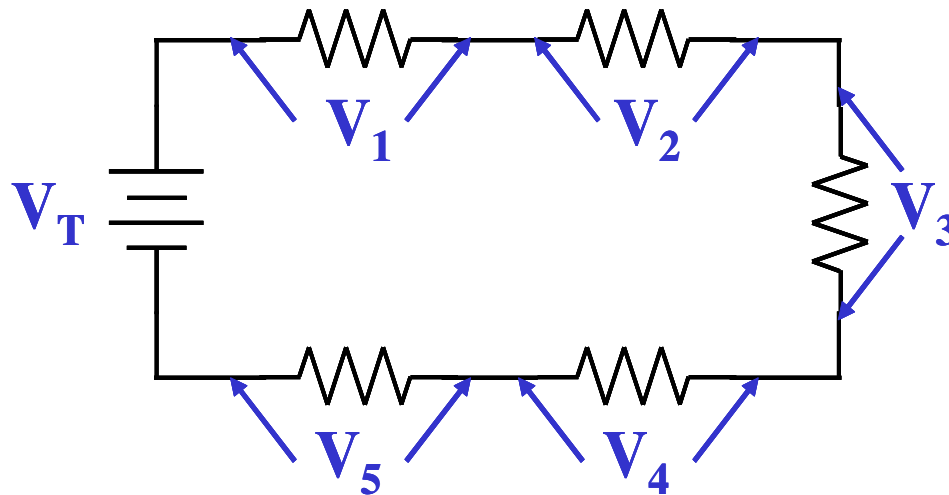
## 4-4: Kirchhoff's Voltage Law (KVL)

The total voltage is equal to the sum of the drops.




$$V_T = V_1 + V_2 + V_3 + V_4 + V_5$$

This is known as  
**Kirchhoff's voltage law (KVL).**
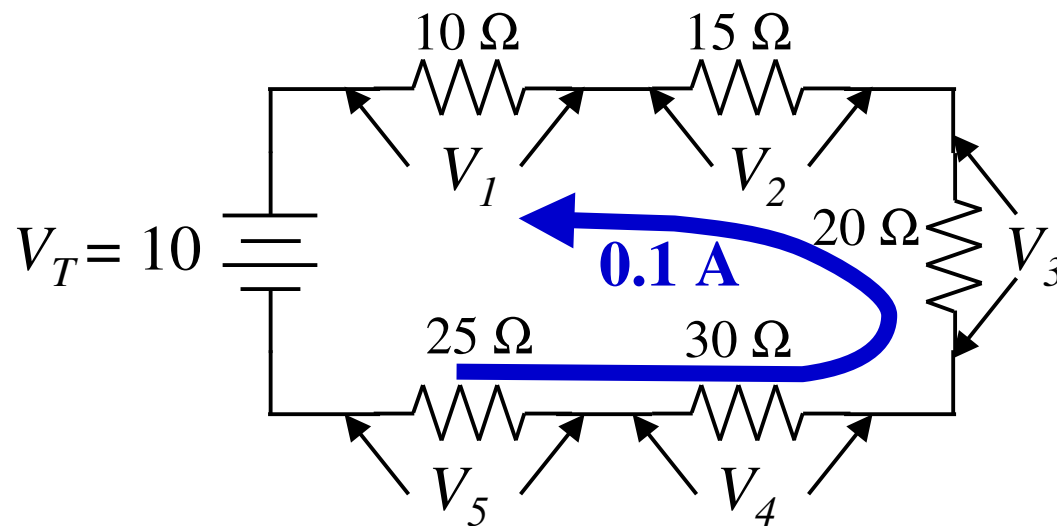
## 4-4: Kirchhoff's Voltage Law (KVL)

The  $IR$  drops must add to equal the applied voltage (KVL).



$$V_T = V_1 + V_2 + V_3 + V_4 + V_5$$

$$V_T = IR_1 + IR_2 + IR_3 + IR_4 + IR_5$$

$$V_T = 0.1 \times 10 + 0.1 \times 15 + 0.1 \times 20 + 0.1 \times 30 + 0.1 \times 25$$

$$V_T = 1\ \text{V} + 1.5\ \text{V} + 2\ \text{V} + 3\ \text{V} + 2.5\ \text{V} = 10\ \text{V}$$

## 4-5: Polarity of $IR$ Voltage Drops

- When current flows through a resistor, a voltage equal to  $IR$  is dropped across the resistor. The polarity of this  $IR$  voltage drop is:
  - Negative at the end where the electrons enter the resistor.
  - Positive at the end where the electrons leave the resistor.



## 4-5: Polarity of $IR$ Voltage Drops

- The rule is reversed when considering conventional current: positive charges move into the positive side of the  $IR$  voltage.
- The polarity of the  $IR$  drop is the same, regardless of whether we consider electron flow or conventional current.

# 4-5: Polarity of $IR$ Voltage Drops

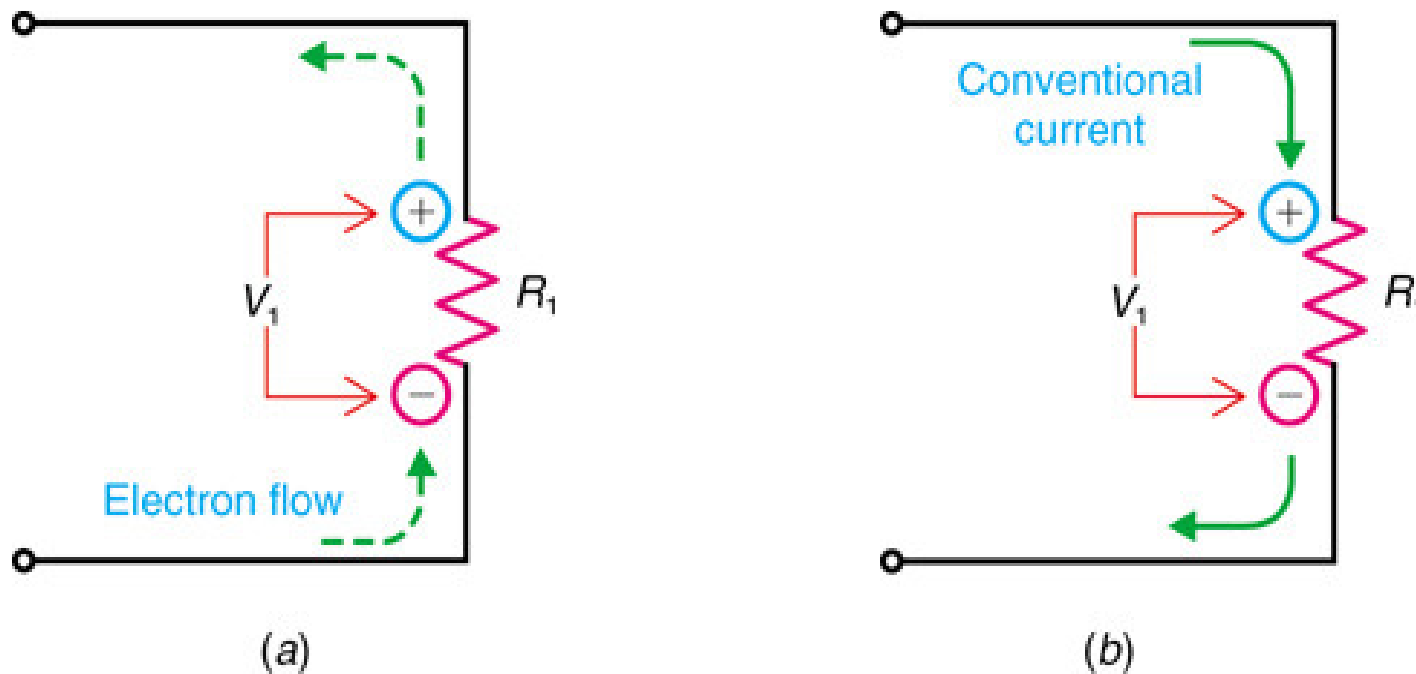


Fig. 4-8: Polarity of  $IR$  voltage drops. (a) Electrons flow into the negative side of  $V_1$  across  $R_1$ . (b) Same polarity of  $V_1$  with positive charges into the positive side.

# 4-6: Total Power in a Series Circuit

- The power needed to produce current in each series resistor is used up in the form of heat.
- The total power used in the circuit is equal to the sum of the individual powers dissipated in each part of the circuit.
- Total power can also be calculated as  $V_T \times I$


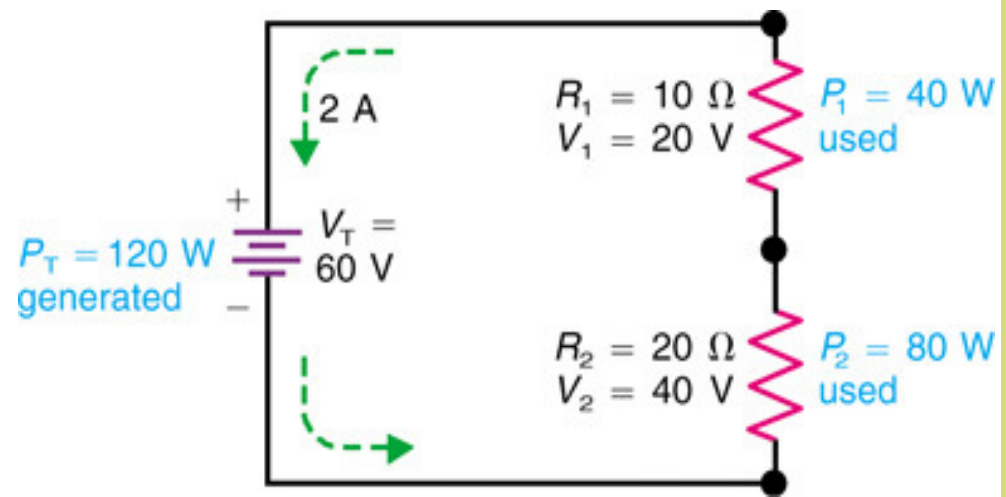


Fig. 4-10: The sum of the individual powers  $P_1$  and  $P_2$  used in each resistance equals the total power  $P_T$  produced by the source.

# 4-6: Total Power in a Series Circuit

## Finding Total Power

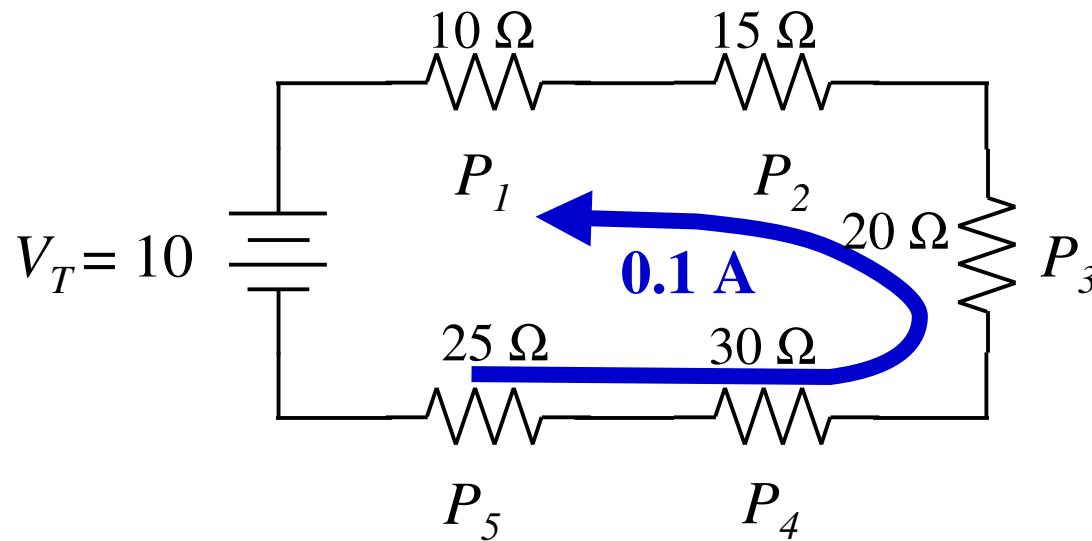

$$P_T = P_1 + P_2 + P_3 + P_4 + P_5$$

$$P_T = I^2 R_1 + I^2 R_2 + I^2 R_3 + I^2 R_4 + I^2 R_5$$

$$P_T = 0.1\text{ W} + 0.15\text{ W} + 0.2\text{ W} + 0.3\text{ W} + 0.25\text{ W} = 1\text{ W}$$

$$\text{Check: } P_T = V_T \times I = 10\text{ V} \times 0.1\text{ A} = 1\text{ W}$$

# 4-7: Series-Aiding and Series-Opposing Voltages

- Series-aiding voltages are connected with polarities that allow current in the same direction:
  - The positive terminal of one is connected to the negative terminal of the next.
- They can be added for the total voltage.

## 4-7: Series-Aiding and Series-Opposing Voltages

- Series-opposing voltages are the opposite: They are connected to produce opposing directions of current flow.
  - The positive terminal of one is connected to the positive terminal of another.
- To obtain the total voltage, subtract the smaller voltage from the larger.
- Two equal series-opposing voltage sources have a net voltage of zero.

# 4-7: Series-Aiding and Series-Opposing Voltages

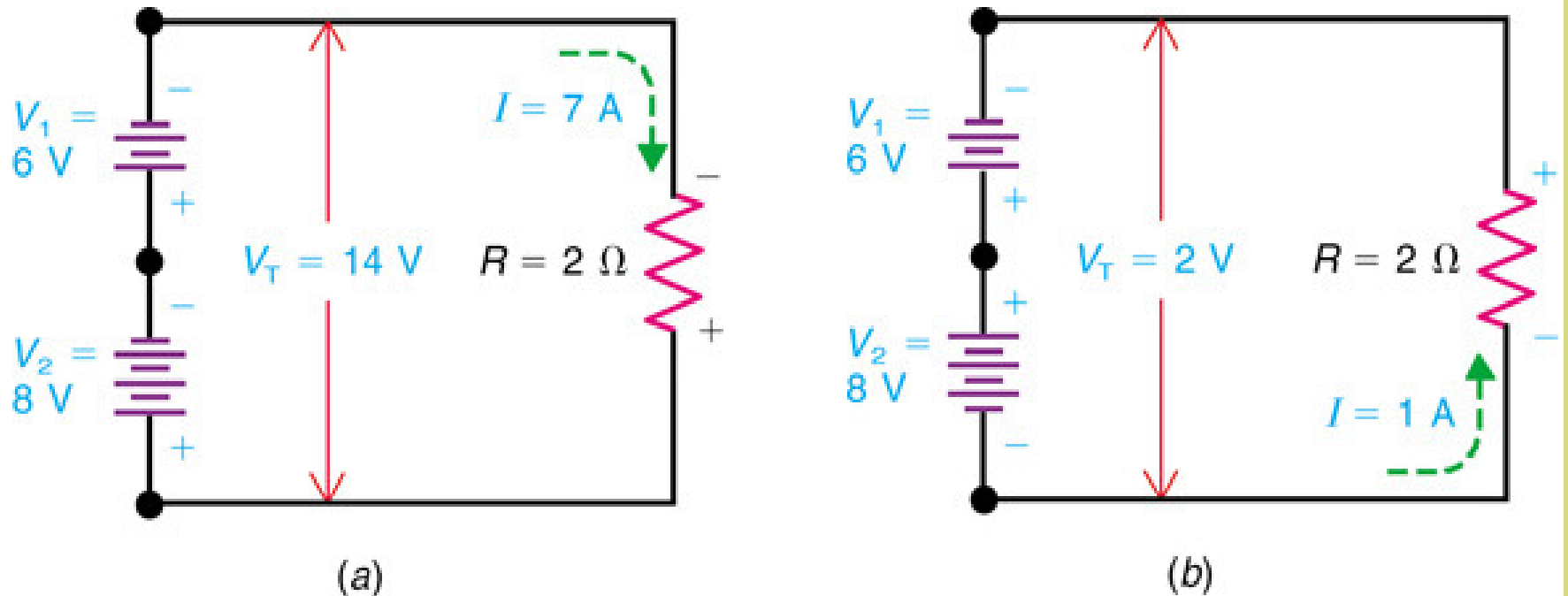


Fig. 4-11: Example of voltage sources  $V_1$  and  $V_2$  in series. (a) Note the connections for series-aiding polarities. Here  $8\text{ V} + 6\text{ V} = 14\text{ V}$  for the total  $V_T$ . (b) Connections for series-opposing polarities. Now  $8\text{ V} - 6\text{ V} = 2\text{ V}$  for  $V_T$ .

## 4-8: Analyzing Series Circuits with Random Unknowns

- When trying to analyze a series circuit, keep the following principles in mind:
  1. If  $I$  is known for one component, use this value in all components. The current is the same in all parts of a series circuit.
  2. If  $I$  is unknown, it may be calculated in one of two ways:
    - Divide  $V_T$  by  $R_T$
    - Divide an individual  $IR$  drop by its  $R$ .
    - Remember not to mix a total value for an entire circuit with an individual value for part of the circuit.



## 4-8: Analyzing Series Circuits with Random Unknowns

3. If all individual voltage drops are known, add them to determine the applied  $V_T$ .
  - A known voltage drop may be subtracted from  $V_T$  to find a remaining voltage drop.


## 4-9: Ground Connections in Electrical and Electronic Systems

- In most electrical and electronic systems, one side of the voltage source is connected to ground.
- The reason for doing this is to reduce the possibility of electric shock.

# 4-9: Ground Connections in Electrical and Electronic Systems

- Figure 4-16 shows several schematic ground symbols:

earth  
ground

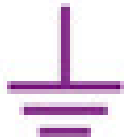

chassis  
ground



common  
ground



- Ground is assumed to have a potential of 0 V regardless of the schematic symbol shown.
- These symbols are sometimes used inconsistently with their definitions. However, these symbols always represent a common return path for current in a given circuit.

# 4-9: Ground Connections in Electrical and Electronic Systems

- Voltages Measured with Respect to Ground
  - When a circuit has a ground as a common return, measure the voltages with respect to this ground.

# 4-9: Ground Connections in Electrical and Electronic Systems

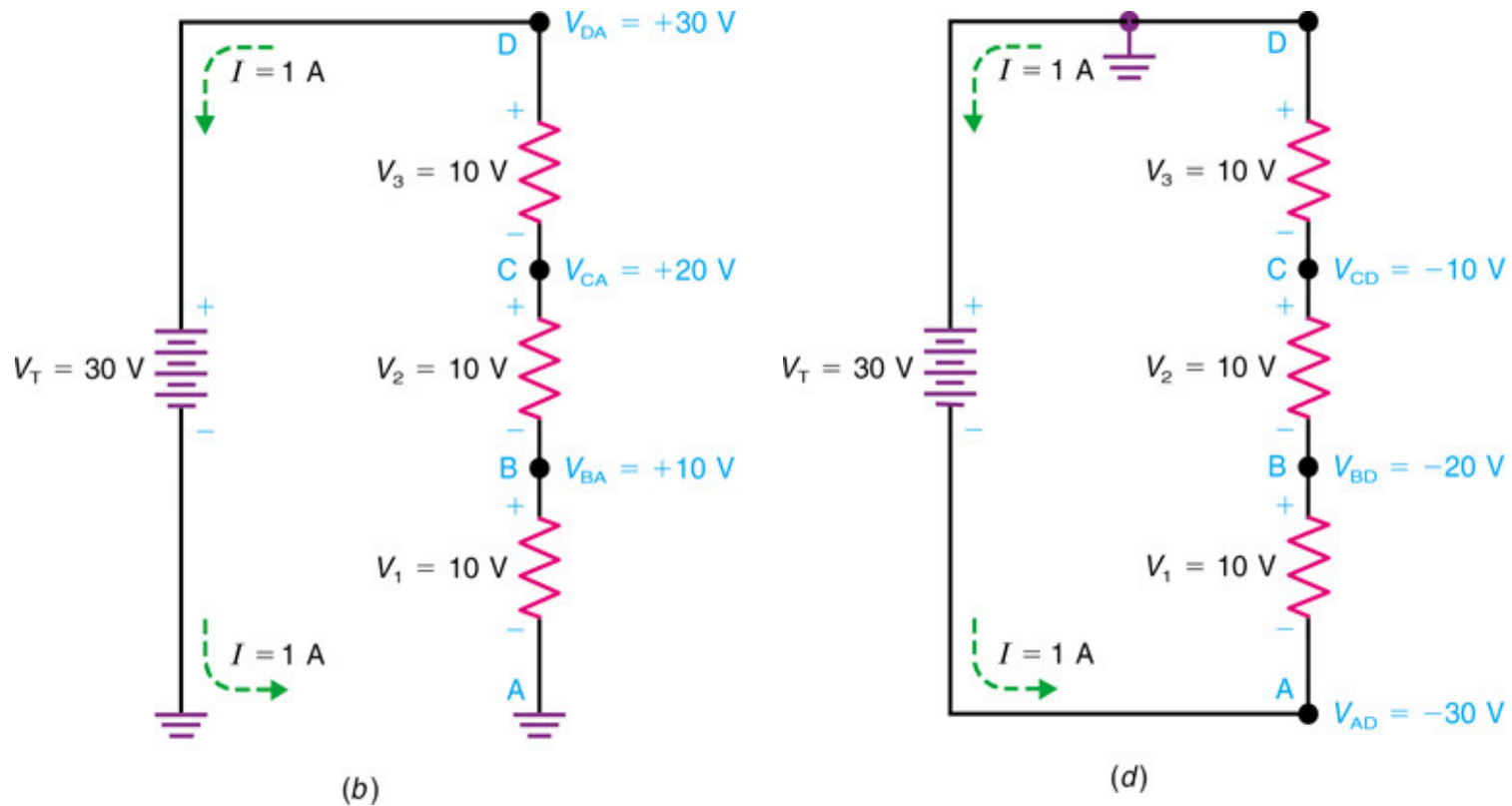


Fig. 4-18: An example of how to calculate dc voltages measured with respect to ground. (b) Negative side of  $V_T$  grounded to make all voltages positive with respect to ground. (d) Positive side of  $V_T$  grounded, all voltages are negative to ground.

# 4-10: Troubleshooting: Opens and Shorts in Series Circuits

- The Effect of an Open in a Series Circuit
  - An open circuit is a circuit with a break in the current path. When a series circuit is open, the current is zero in all parts of the circuit.
  - The total resistance of an open circuit is infinite ohms.
  - When a series circuit is open, the applied voltage appears across the open points.

# 4-10: Troubleshooting: Opens and Shorts in Series Circuits

- The Effect of an Open in a Series Circuit

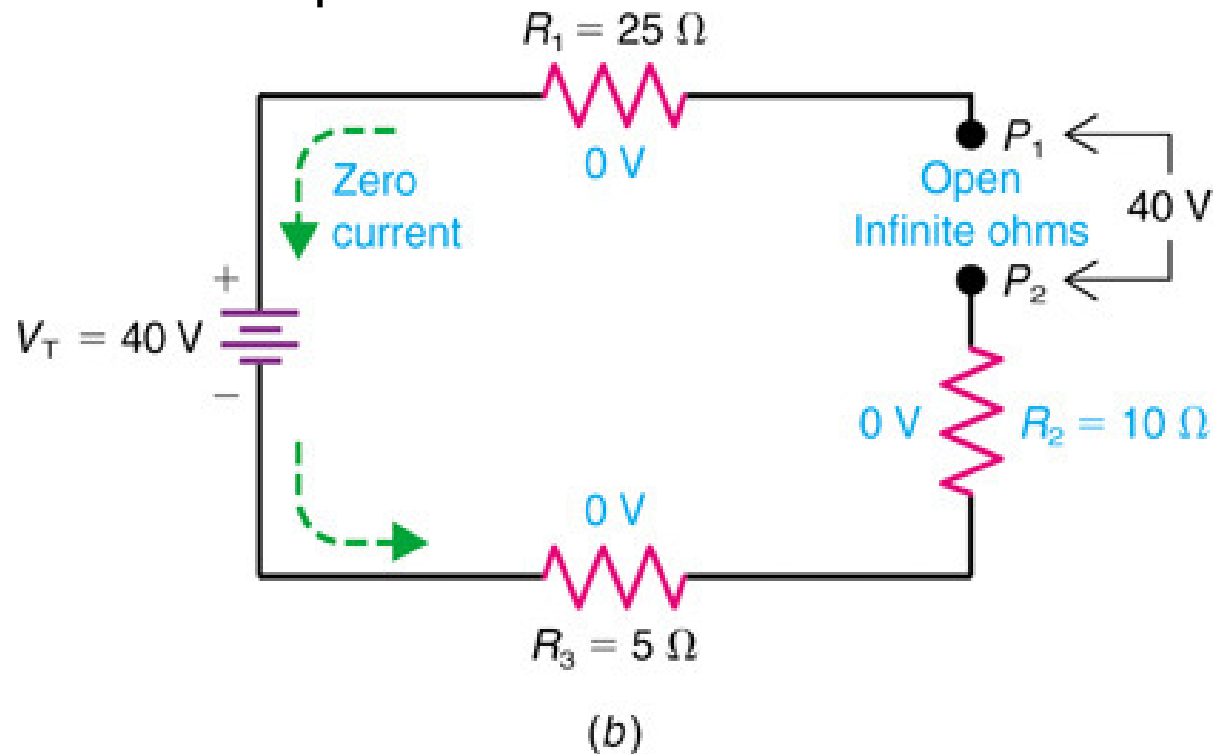


Fig. 4-19: Effect of an open in a series circuit. (b) Open path between points  $P_1$  and  $P_2$  results in zero current in all parts of the circuit.

## 4-10: Troubleshooting: Opens and Shorts in Series Circuits

- Applied voltage  $V_T$  is still present, even with zero current.
- The voltage source still has its same potential difference across its positive and negative terminals.
  - Example: The 120-V potential difference is always available from the terminals of a wall outlet.
    - If an appliance is connected, current will flow.
    - If you touch the metal terminals when nothing else is connected, you will receive a shock.



# 4-10: Troubleshooting: Opens and Shorts in Series Circuits

- The Effect of a Short in a Series Circuit
  - When part of a series circuit is shorted, the current flow increases.
  - When part of a series circuit is shorted, the voltage drops across the non-shortened elements increase.
  - The voltage drop across the shorted component drops to 0 V.

# 4-10: Troubleshooting: Opens and Shorts in Series Circuits

- The Effect of a Short in a Series Circuit

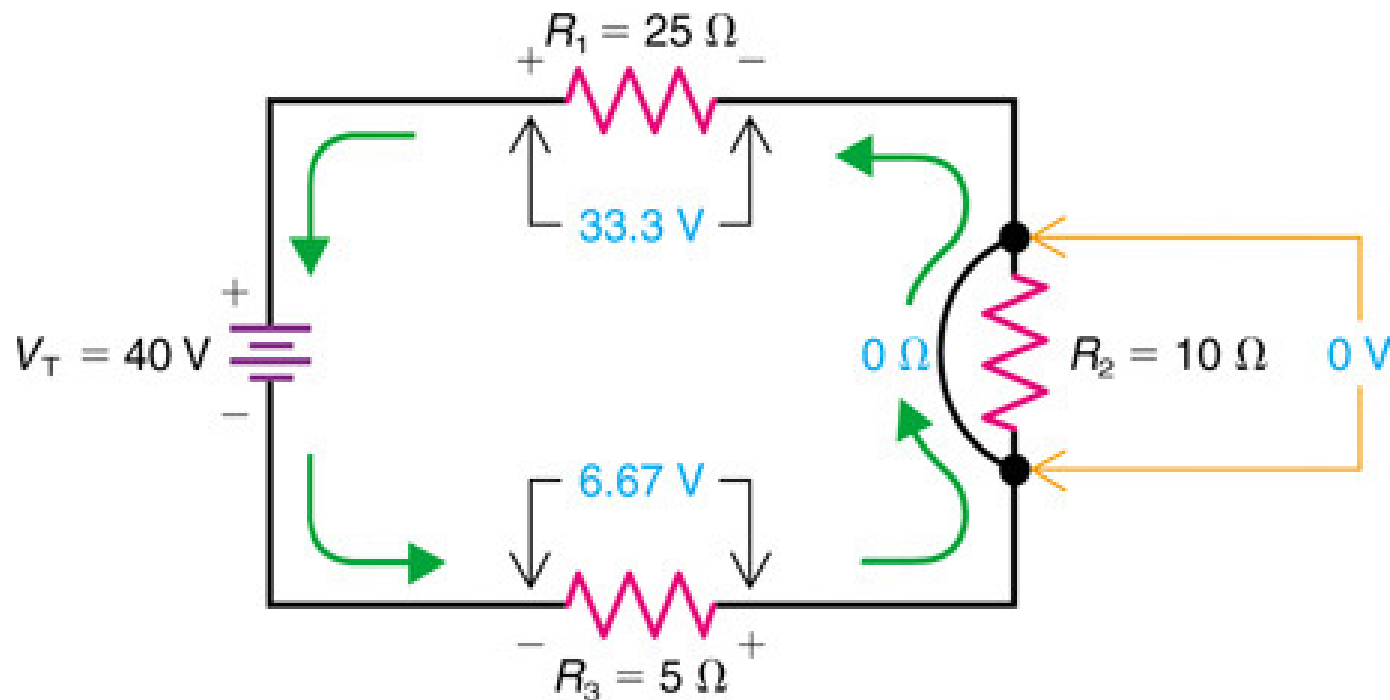


Fig. 4-21: Series circuit of Fig. 4-18 with  $R_2$  shorted.

## 4-10: Troubleshooting: Opens and Shorts in Series Circuits

- When troubleshooting a series circuit containing three or more resistors, remember:
  - The component whose voltage changes in the opposite direction of the other components is the defective component.